

Fast input-voltage transient response with digitally-controlled isolated DC/DC converters

By **Frank Tang**, System Solutions and Applications Manager of China, High-Voltage Power Solutions

Tan Jack, Firmware Engineer, High-Voltage Power Solutions

Mark Ng, Marketing Manager, High-Power Controller Solutions

Natarajan Ramanan, Worldwide Systems Solutions and Applications Manager, High-Voltage Power Solutions

Introduction

Telecommunications equipment is often subjected to environmental and other electrical stresses such as lightning strikes, equipment faults, and capacitor-bank switching. These events can cause input-voltage transients of up to 100 V for durations of 10 ms. Various telecommunications standards, including the American National Standard (ANSI T1.315-2001 Specification) and Alliance for Telecommunications Industry Solutions (ATIS-0600315.2007 Specification), dictate the behavior of DC-powered equipment used in telecommunications environments.

In particular, these standards stipulate required behaviors when exposed to overvoltage transients. Overvoltage-transient conformance to the above specifications requires that a power supply must:

- Be able to handle an input surge voltage of 100 V for 10 ms
- Not be damaged or result in performance degradation

The design goals for today's state-of-the-art isolated DC/DC converters generally target an output voltage disturbance of less than 10% for all transient conditions of the input voltage. A large overshoot at the output may damage the downstream equipment and a big output-voltage undershoot can cause the equipment to shut down or reset. In the case of isolated DC/DC converters with synchronous rectification, a large reverse current may be generated that subjects electrical components to overstress and increases system noise, thus, disturbing the converter's normal operation.

One condition that a designer must be mindful of is the input-voltage slew rate. An extremely-fast voltage slew rate (for example, 50 V to 75 V in 2 μ s) often can cause the output-voltage disturbance to exceed $\pm 10\%$. It is unlikely that these standards will be relaxed any time soon. In fact, these conditions most likely will become even more stringent. Therefore, today's isolated DC/DC power supplies must have a very good control method (or voltage feed forward) to limit the


magnitude of the output-voltage undershoot and overshoot caused by an input-voltage transient.

Input-voltage feed forward within the power supply's nominal input range

A huge challenge for designers of digitally-controlled isolated DC/DC converters is the attenuation of the output-voltage fluctuations during abrupt input-voltage transients that are within the power supply's nominal input voltage range. However, in traditional primary-side controlled solutions (Figure 1), this is easy to manage. The sawtooth signal to the comparator has a peak value that is proportional to the input voltage and is used to terminate the duty cycle of the pulse-width modulator (PWM). In this way, the product of the input voltage and primary turn-on time is almost a constant value, no matter how fast the input voltage changes. Using this method, the output voltage has a very fast response for line-input transients.

In digitally-controlled solutions, the digital controller is usually located on the transformer's secondary or output side. This allows the controller to achieve a better load-transient response and to easily perform communication with the host microcontroller via I²C or PMBus™.

Figure 1. Analog controller with PWM generation

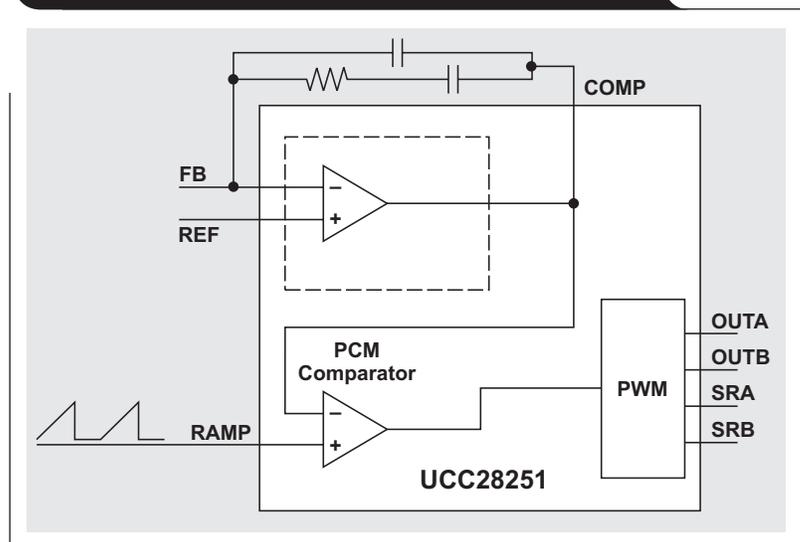

Compared with a primary analog controller solution, it becomes more difficult for the digital controller to quickly and accurately detect the input voltage transients occurring on the transformer's primary side. In a purely digital solution, the designer must consider further complexities such as A/D conversion delay, digital processing delay, and digital pulse-width modulator (DPWM) generating delay.


Solution

It is possible for a digitally-controlled solution to control duty cycle much like the analog solution. This means that the digital-power controller in Figure 2 can be configured with similar performance to the analog controller in Figure 1 while maintaining its digital flexibility.

The key challenge is how to generate a ramp similar to the analog solution. In buck-derived DC/DC isolated topologies, input voltage can be reflected on the transformer's secondary winding during the effective on time of the primary switch. The hard-switching full-bridge (HSFB) topology shown in Figure 3 is an example of the method for generating this ramp.


T1 represents the power transformer used in the HSFb topology. When a pair of primary switches are turned on, the input voltage reflected on the secondary winding charges C1 through R1 and R3. This continues until the

Figure 2. A digital controller configured similar to an analog PWM controller

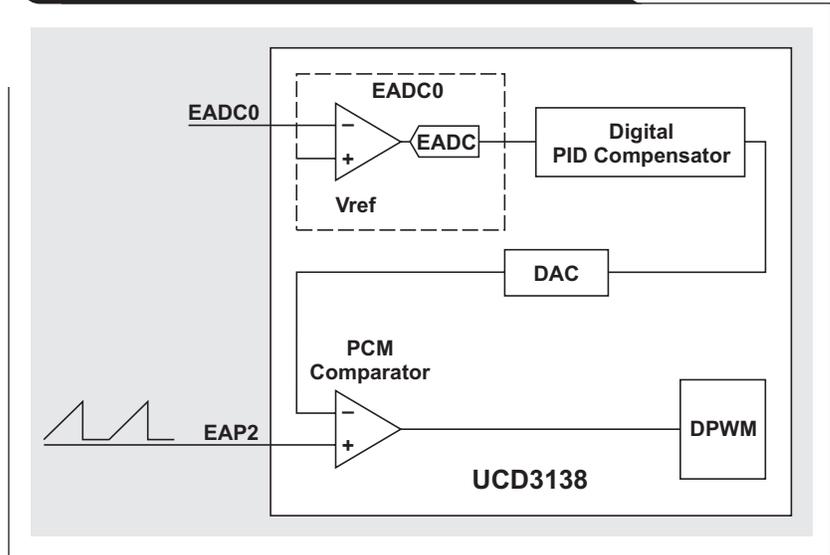

PCM comparator terminates the pulse of the primary gate driver when the sawtooth voltage on the EAP2 pin exceeds the DAC's output. DPWM3A is a complementary signal of the primary gate driver that is generated by the digital controller. This controller is used to discharge C1 at every half switching cycle. R2 is added to limit the voltage on the EAP2 pin, which is lower than its maximum voltage rating at any condition.

Figure 3. RAMP generation with HSFb topology

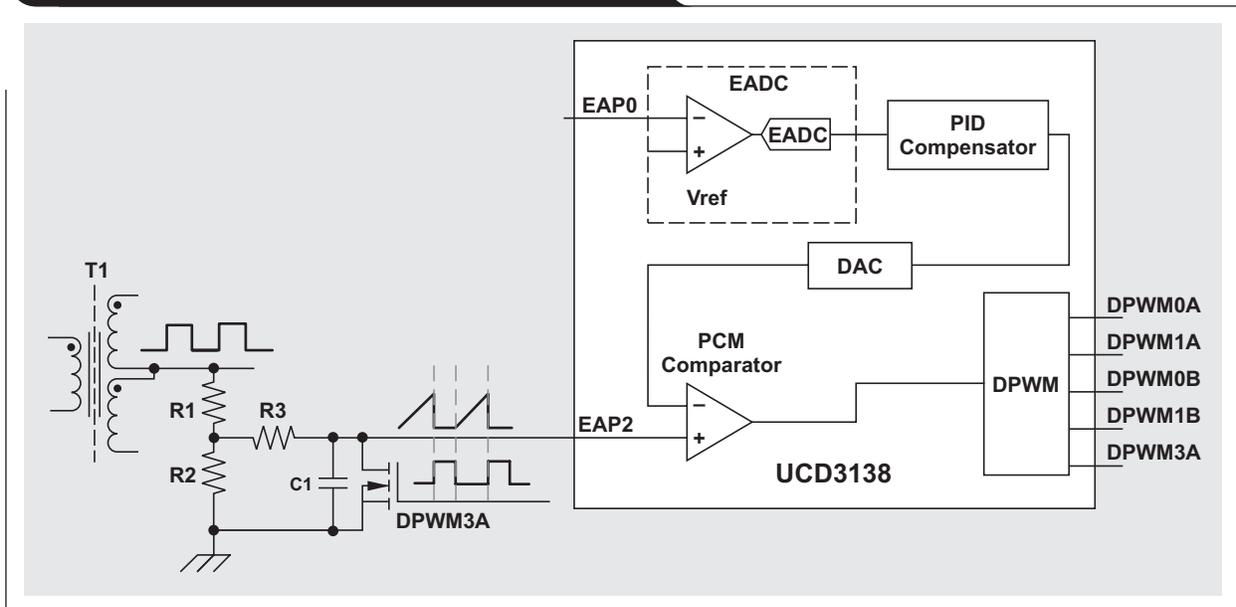

Test results


The test comparison in Figure 4 was generated with the UCD3138HSFBEVM-029 evaluation module (EVM), which is a HSFb demo module with a 12-V output. This EVM employs a non-linear multiplier solution to implement input-voltage feed-forward control that can achieve a good output response. However, the method proposed here can achieve an even better performance. The amplitude of both overshoot and undershoot is reduced by four times when the input voltage steps between 36 V and 60 V with a voltage slew rate of 1 V/ μ s. The 36-V minimum voltage of this transient test was chosen because the output voltage cannot maintain below that limit, or output voltage-hold threshold.

Avoid reverse current when input voltage drops below the output voltage-hold threshold

When the input voltage drops below the output voltage-hold threshold, the duty cycle reaches its maximum value. Now the product of the input voltage and duty cycle decreases. If the power stage still operates in the synchronous rectification mode, this causes the energy stored in the output capacitor to flow in a reverse direction to the input.

The reverse current could be huge, which may cause overcurrent stress on the power train. A popular solution is to add a reverse-current protection circuit where the synchronous rectifier (SR) is turned off when reverse

Figure 4. A comparison test for input-voltage transients between 36 V and 60 V

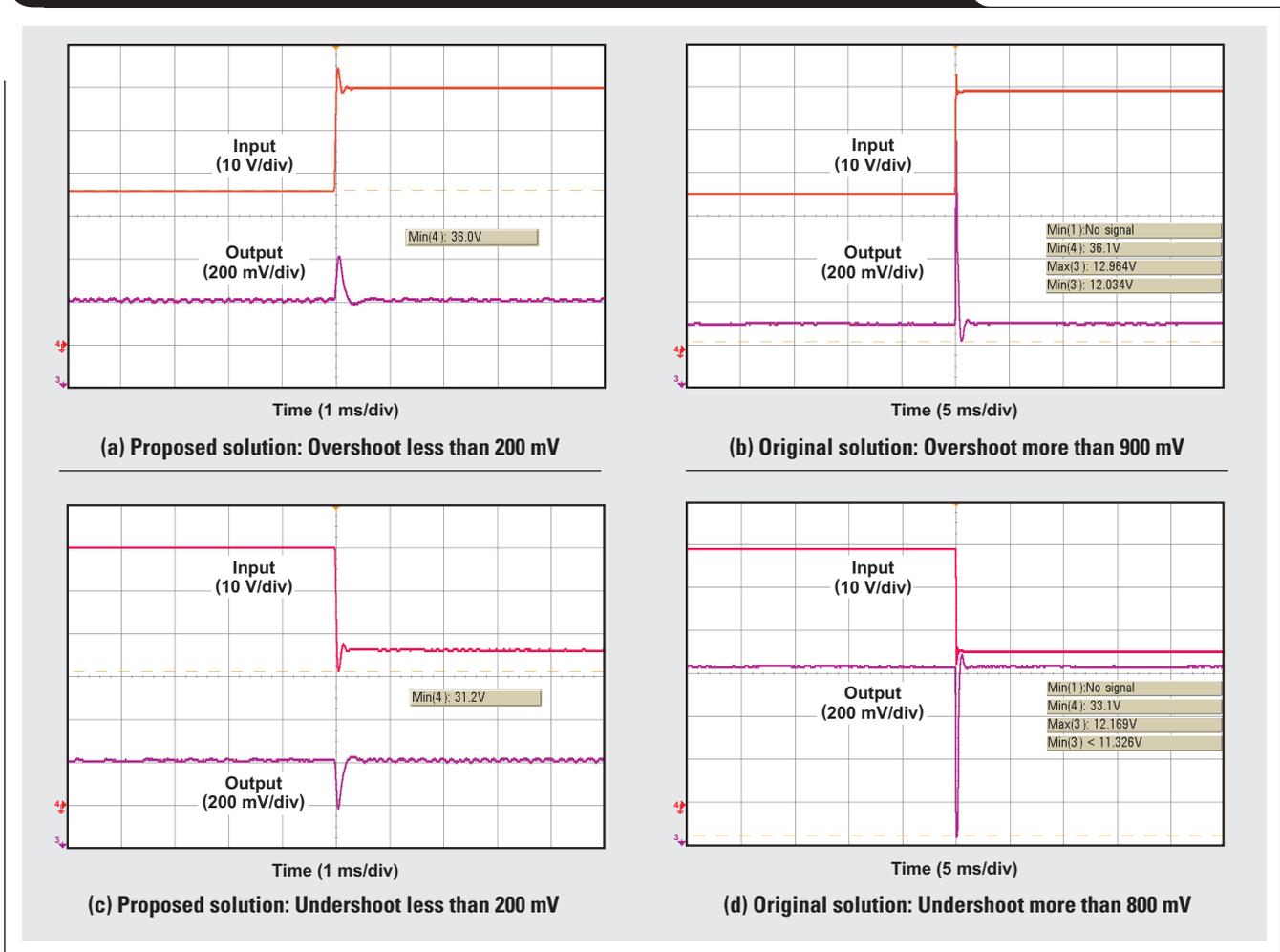

current is larger than a safe threshold. This way, the loop of the reverse current through the output inductance is cut off abruptly. The energy stored in the output inductance, causes an avalanche breakdown of the SR, which can cause SR failure.

Solution

To solve this problem, a voltage-detection circuit can turn off the SR immediately. This occurs before the reverse current is generated and when the input voltage drops to lower than the output voltage-hold threshold. The circuit shown in Figure 5 detects the input voltage from the transformer’s center tap (V_TAP). The EAP1 pin, which belongs to the UCD3138 front-end block, can be configured to sample the voltage only at the on-time of the primary switch when the V-TAP’s voltage reflects an input voltage.

In Figure 6, the scaled down input voltage is converted to a digital number stored in the ABS registers. A pair of digital window comparators inside the digital controller are configured to detect the under-voltage input and the input-voltage recovery. When an input voltage below the output voltage-hold threshold

is detected, within nanoseconds, digital comparator 0 issues a fault signal to the DPWM module to shut down the DMPM0B/1B, SR-gate drive signal. When the input voltage recovers, the digital comparator 1 triggers a fast firmware interruption that enables the SR-gate driver. A pre-bias startup routine is started so that the output voltage can recover in the shortest amount of time.

Figure 5. Input-voltage detection circuit

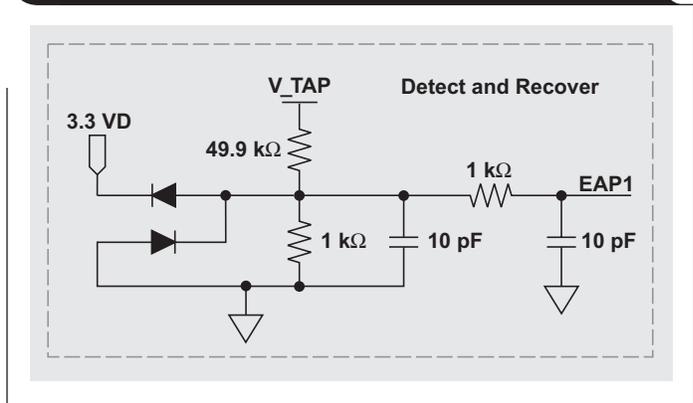


Figure 6. Turn-on/off control of a synchronous rectifier


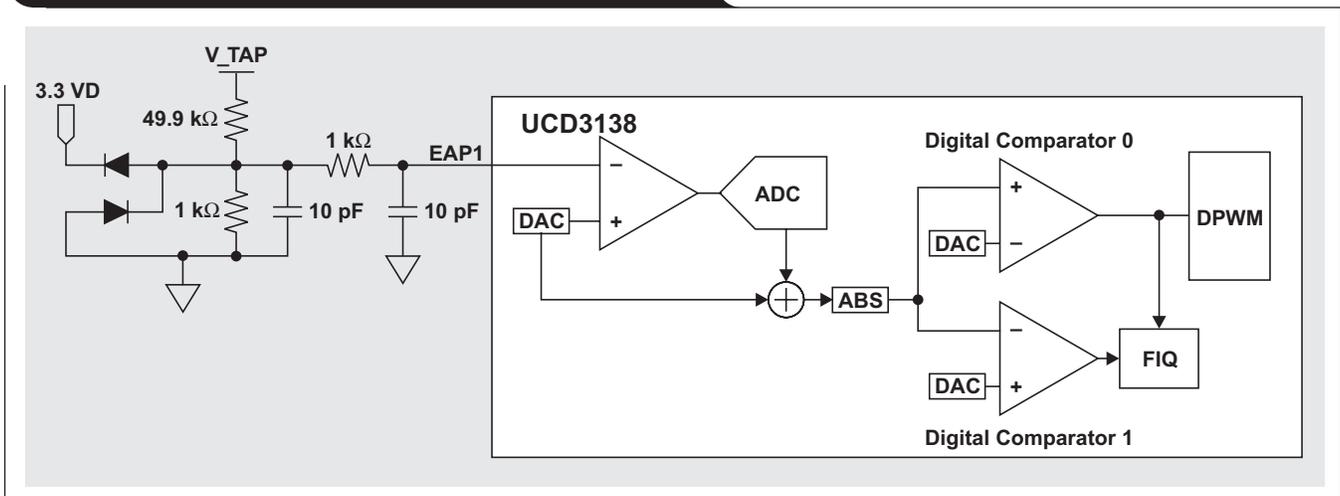


Figure 7. Test results when the input-voltage transient is between 60 V and 20 V

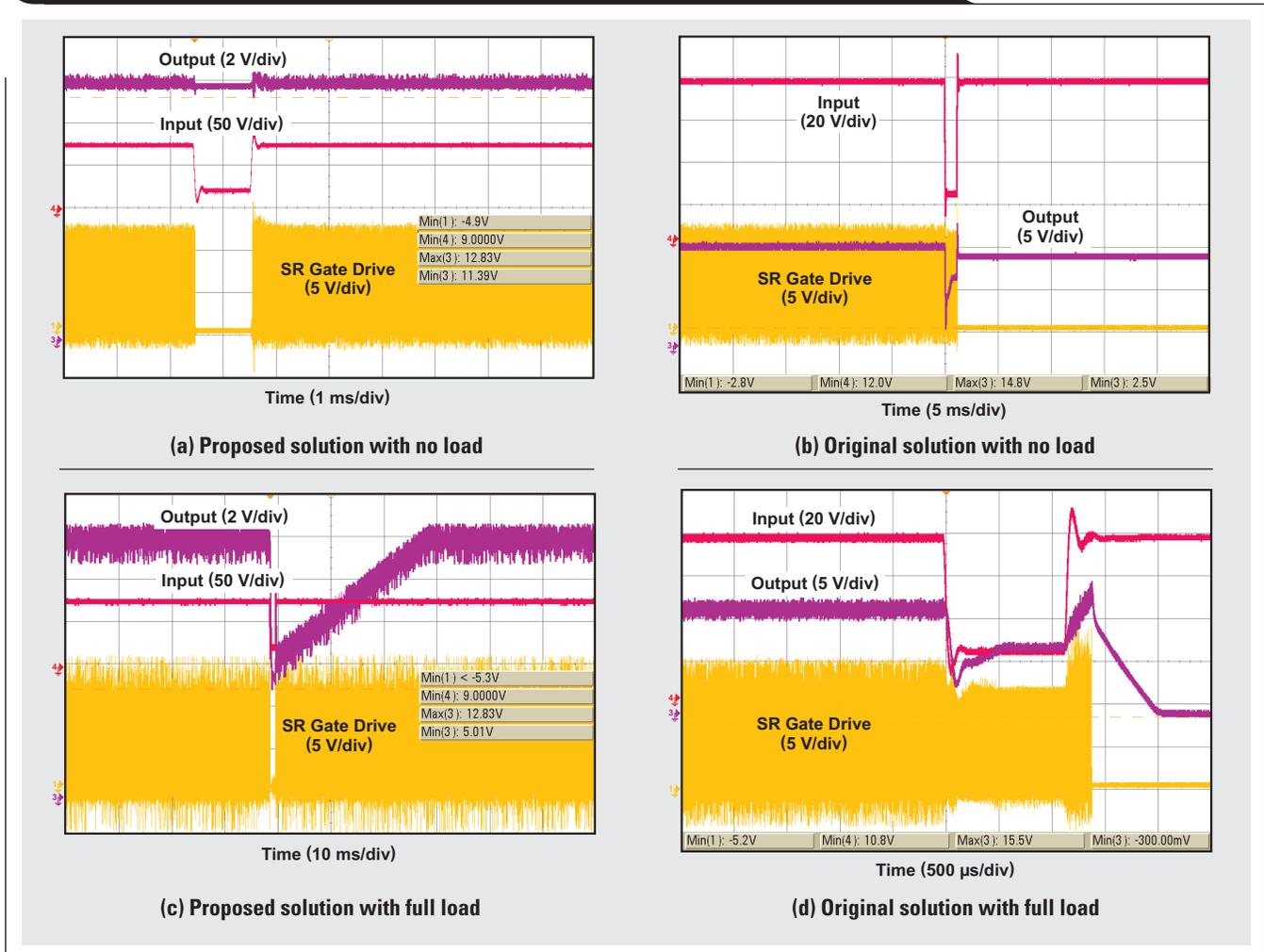

Test results

The proposed solution is designed to shut down the SR gate driver signal as soon as the input voltage drops below 36 V (Figure 7a). There is no reverse current discharging the output capacitor and the output voltage under no-load test barely changes while the input voltage stays at 22 V. In comparison, the original SR gate-driver EVM solution (Figure 7b) continues to run, even though the input voltage is below 36 V. The reverse current is generated, causing the output voltage to be discharged, even under no-load conditions.

The original EVM solution does not have a pre-bias startup function when the input voltage recovers to its normal value, which causes an output voltage overshoot and triggers OVP after the input voltage recovers (Figure 7d). For a full-load test, the output voltage in the proposed solution is discharged by the load (Figure 7c). When the input voltage recovers, the output can immediately and monotonously rise back to the regulated voltage, which is controlled by the pre-bias startup routine.

Conclusion

It was shown that a secondary-side, digitally-controlled solution provides good performance under line-transient test conditions.

A proposed solution showed that the output voltage remained almost unchanged as long as the input-voltage transient is above the output voltage-hold threshold. The solution also avoided reverse current from occurring when the input voltage was lower than the output voltage-hold threshold. Additionally, a stringent and monotonous startup waveform was achieved when the input voltage recovered.

Related Web sites

Product information:
UCD3138HSFBEM-029
UCC28251
UCD3138

Subscribe to the AAJ:
www.ti.com/subscribe-aaaj

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com