

# $V_{CM}$ vs. $V_{OUT}$ plots for instrumentation amplifiers with two op amps

By Pete Semig

Analog Applications Engineer, Precision Amplifiers

## Background

The most common issue found in the TI E2E™ Community for instrumentation amplifiers involves interpreting the datasheet plot for common-mode voltage versus output voltage ( $V_{CM}$  vs.  $V_{OUT}$ ). Misinterpretation or misunderstanding this plot results in forum posts that describe distorted output waveforms, incorrect device gain, or ‘stuck’ outputs. Verifying that the device is operating within the limits of the  $V_{CM}$  vs.  $V_{OUT}$  plot is always the first thing I check when responding to an application issue.

This article introduces the  $V_{CM}$  vs.  $V_{OUT}$  plot for an instrumentation amplifier with two operational amplifiers (op amps) and delivers a thorough treatment of this amplifier topology. Additionally, the internal node equations are derived and used to plot each internal amplifier’s input common-mode and output-swing limits as a function of the instrumentation amplifier’s common-mode voltage. Finally, a software tool that simulates the  $V_{CM}$  vs.  $V_{OUT}$  plot is introduced.

## The $V_{CM}$ vs. $V_{OUT}$ plot

The input common-mode and output-swing limitations of all internal amplifiers of an instrumentation amplifier are represented in the  $V_{CM}$  vs.  $V_{OUT}$  plot.

A typical  $V_{CM}$  vs.  $V_{OUT}$  plot for a two-op-amp instrumentation amplifier is shown in Figure 1. The interior of the plot defines the linear operating region of the instrumentation amplifier because each line in the plot corresponds to either an input or output limitation of one of the two internal amplifiers. The  $V_{CM}$  vs.  $V_{OUT}$  plot is specified for a particular supply voltage, reference voltage, and gain as shown in Figure 1.

Operating outside the boundaries of a  $V_{CM}$  vs.  $V_{OUT}$  plot causes the device to operate in a non-linear mode as shown in Figure 2.

A three-part series article and blog post discuss the  $V_{CM}$  vs.  $V_{OUT}$  plot for the ubiquitous three-op-amp instrumentation amplifier.<sup>[1, 2]</sup> Two-op-amp instrumentation amplifiers are popular because of their low-cost and relatively large  $V_{CM}$  vs.  $V_{OUT}$  plots.

Figure 1.  $V_{CM}$  vs.  $V_{OUT}$  plot for two-op-amp instrumentation amplifier


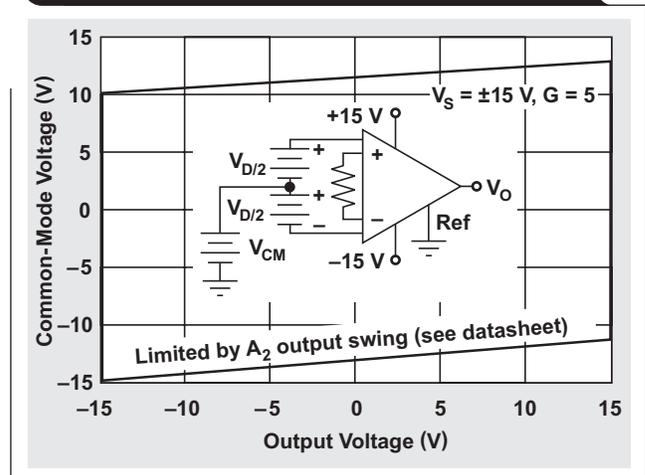


Figure 2. Instrumentation amplifier output distortion due to  $V_{CM}$  vs.  $V_{OUT}$  violation<sup>[1]</sup>

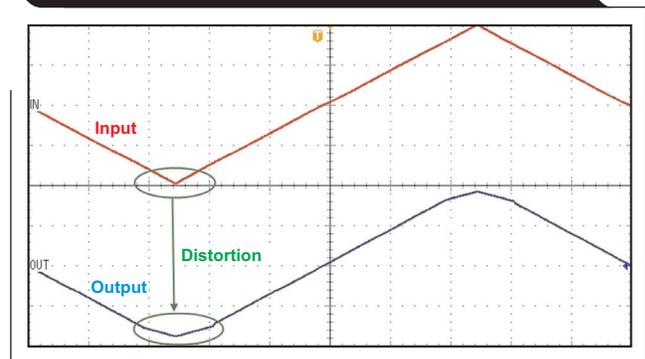

### Analysis of a two-op-amp instrumentation amplifier

Figure 3 depicts a typical two-op-amp instrumentation amplifier connected to an input signal. This topology has high input impedance and requires only one resistor,  $R_G$ , to set the gain, which is the same as the three-op-amp topology.

Figure 3 also depicts the definition of common-mode ( $V_{CM}$ ) and differential-mode ( $V_D$ ) voltages. A differential amplifier (for example, op amp, difference amplifier, instrumentation amplifier) ideally rejects the common-mode voltage,  $V_{CM}$ .

However, the signal-path imbalance from  $V_{+IN}$  and  $V_{-IN}$  to the output degrades the device's common-mode rejection ratio (CMRR), especially over frequency (Figure 4). This degradation in CMRR is one of the primary reasons why two-op-amp instrumentation amplifiers typically cost less than their three-op-amp counterparts.

The transfer function for the circuit in Figure 3 is given by Equation 1. Notice that the common-mode voltage does not appear in the equation because ideally it is rejected by the instrumentation amplifier.

$$V_O = (V_{+IN} - V_{-IN}) \times G + V_{REF} = V_D \times G + V_{REF} \quad (1)$$

Deriving the transfer function of this topology aids in understanding the  $V_{CM}$  vs.  $V_{OUT}$  plot.

Figure 5 depicts a more traditional drawing of the schematic in Figure 3. In order to determine the contribution of the reference voltage at the output,  $V_{O(VREF)}$ , apply superposition by shorting the input sources to ground.

Amplifier  $A_2$  applies an inverting gain to  $V_{REF}$  based on the ratio of  $R_{FA2}$  and  $R_R$ . Similarly,  $A_1$  applies an inverting gain to the output voltage of  $A_2$  based on the ratio of  $R_{FA1}$  and  $R_{OA2}$ . Equation 2 depicts the transfer function for  $V_{REF}$ .

$$\begin{aligned} V_{O\_VREF} &= V_{REF} \left( \frac{-R_{FA2}}{R_R} \right) \left( \frac{-R_{FA1}}{R_{OA2}} \right) \\ &= V_{REF} \left( \frac{R_{FA1} \times R_{FA2}}{R_R \times R_{OA2}} \right) \end{aligned} \quad (2)$$

Figure 3. Topology of a two-op-amp instrumentation amplifier

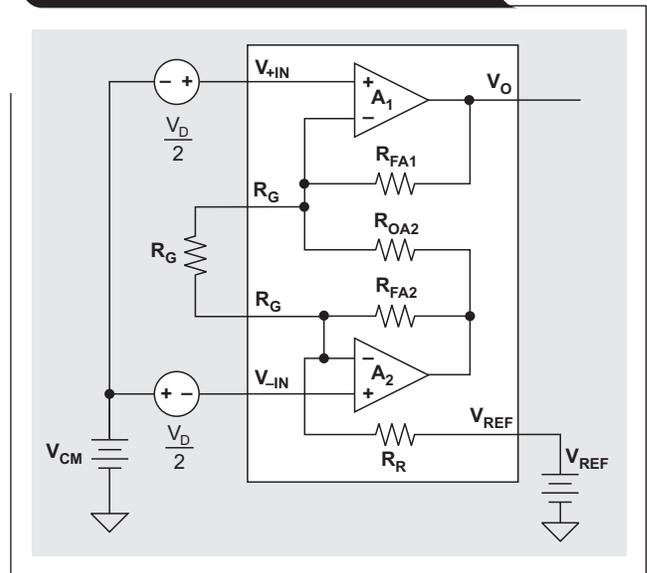


Figure 4. CMRR of two-op-amp vs. three-op-amp topologies


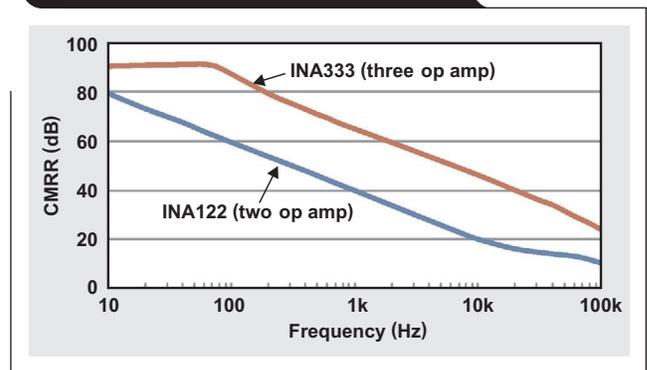



Figure 5. Alternate drawing for Figure 3

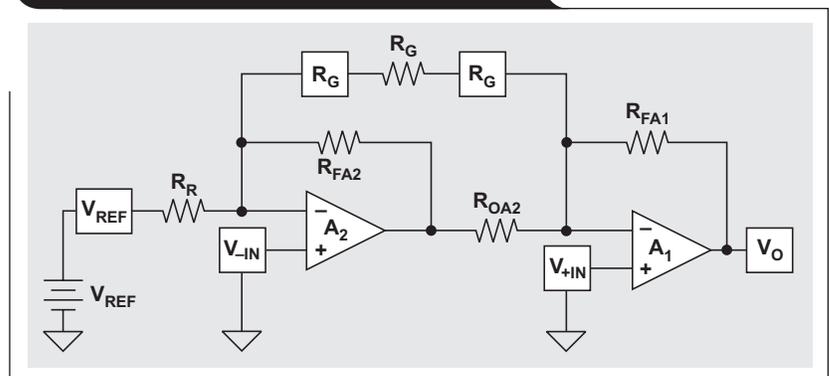

The gain applied to the instrumentation amplifier's reference voltage should be 1 V/V. To fulfill this requirement, set  $R_{FA1} = R_R$  and  $R_{FA2} = R_{OA2} = R_F$ . Figure 6 depicts the updated two-op-amp topology that results in unity gain for the reference voltage. Furthermore, the internal nodes are labeled for future analysis.

Despite just two amplifiers and five resistors, the circuit in Figure 6 has six gain terms. This is because each amplifier applies gain to three input signals. While it may be obvious that  $A_2$  applies gain to  $V_{-IN}$  and  $V_{REF}$ ,  $A_2$  also applies gain to  $V_{+IN}$  via the virtual short across the inputs of  $A_1$  and  $R_G$ . Similarly,  $A_1$  applies gain to  $V_{OA2}$ ,  $V_{+IN}$ , and  $V_{-IN}$ . Equations 3 through 8 depict the six gain terms associated with a two-op-amp instrumentation amplifier.

Figure 6. Two-op-amp topology with internal nodes labeled

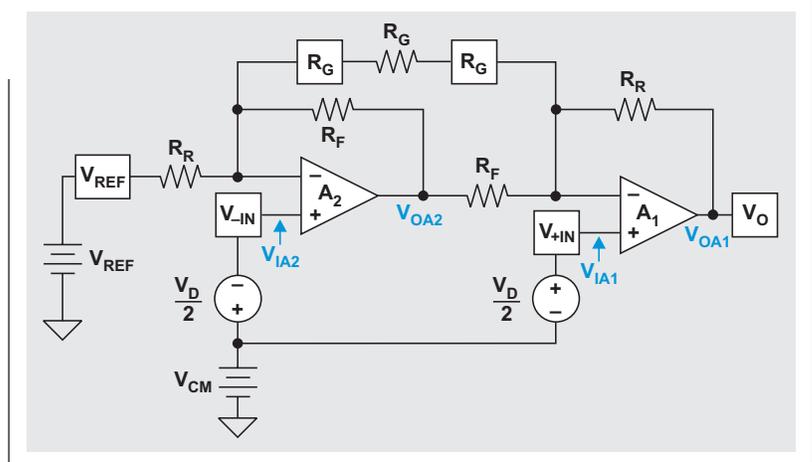

$$G_{A2VR} = \frac{-R_F}{R_R} \tag{3}$$

$$G_{A1VOA2} = \frac{-R_R}{R_F} \tag{6}$$

$$G_{A2V-IN} = 1 + \frac{R_F}{R_G \parallel R_R} \tag{4}$$

$$G_{A1V+IN} = 1 + \frac{R_R}{R_G \parallel R_F} \tag{7}$$

$$G_{A2V+IN} = \frac{-R_F}{R_G} \tag{5}$$

$$G_{A1V-IN} = \frac{-R_R}{R_G} \tag{8}$$

Equations 9 and 10 depict the output voltages of amplifiers  $A_1$  and  $A_2$ .

$$V_{OA1} = V_O = V_{+IN}(G_{A1V+IN}) + V_{-IN}(G_{A1V-IN}) + V_{OA2}(G_{A1VOA2}) \tag{9}$$

$$V_{OA2} = V_{+IN}(G_{A2V+IN}) + V_{-IN}(G_{A2V-IN}) + V_{REF}(G_{A2VR}) \tag{10}$$

Substituting Equation 10 for  $V_{OA2}$  in Equation 9 and simplifying yields Equation 11.

$$V_O = V_{+IN}(G_{A1V+IN} + G_{A2V+IN}G_{A1VOA2}) + V_{-IN}(G_{A1V-IN} + G_{A2V-IN}G_{A1VOA2}) + V_{REF} \tag{11}$$

The relationship between the gain terms in Equation 11 is shown in Equation 12.

$$\begin{aligned} G_{A1V+IN} + G_{A2V+IN}G_{A1VOA2} &= -(G_{A1V-IN} + G_{A2V-IN}G_{A1VOA2}) \\ &= G_{A1V+IN} - G_{A1V-IN} = 1 + \frac{R_R}{R_F} + \frac{2R_R}{R_G} \end{aligned} \tag{12}$$


Finally, using Equations 11 and 12, the transfer function for a two-op-amp instrumentation amplifier is shown by Equation 13, which is consistent with Equation 1.

$$\begin{aligned} V_O = V_{OA1} &= (V_{+IN} - V_{-IN}) \times G + V_{REF} \\ &= V_D \times \left( 1 + \frac{R_R}{R_F} + \frac{2R_R}{R_G} \right) + V_{REF} \end{aligned} \tag{13}$$

### Op amp limitations

Linear operation of an instrumentation amplifier is contingent upon the linear operation of its primary building block; op amps. An op amp operates linearly when the input and output signals are within the device's input common-mode and output-swing ranges, respectively. The supply voltages used to power the op amp ( $V_+$  and  $V_-$ ) define these ranges (Figure 7).

Figure 7: Op amp input common-mode and output-swing ranges depend on supplies<sup>[1]</sup>

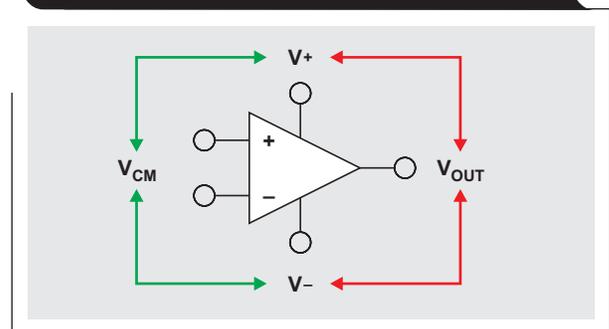

A real-world example of common-mode and output-swing limits is shown in Figure 8. Notice that the common-mode range and output-swing ranges are not necessarily the same.

### Two-op-amp node equations

With a solid understanding of the two-op-amp instrumentation amplifier and op-amp limitations, the next step is to examine the node equations as indicated in Figure 6. The equations for  $V_{OA2}$  and  $V_{OA1}$  are already given by Equations 10 and 13, respectively. Equations for  $V_{IA1}$  and  $V_{IA2}$  from Figure 6 are given as:

$$V_{IA1} = V_{+IN} = V_{CM} + \frac{V_D}{2} \quad (14)$$

$$V_{IA2} = V_{-IN} = V_{CM} - \frac{V_D}{2} \quad (15)$$

The  $V_{CM}$  vs.  $V_{OUT}$  plot can vary based on gain and reference voltage. Therefore, Equations 10 and 13 through 15 must be solved for  $V_O$  as a function of the gain terms,  $V_{CM}$ , and  $V_{REF}$ . One important relationship that allows for this is obtained by solving Equation 13 for  $V_D$ , as shown in Equation 16.

$$V_O = V_D \times G + V_{REF} \rightarrow V_D = \frac{V_O - V_{REF}}{G} \quad (16)$$

After making all of the proper substitutions and solving for  $V_O$ , Equations 17 through 20 capture the linear operating region of a two-op-amp instrumentation amplifier at its output as a function of the gain terms,  $V_{CM}$ ,  $V_{REF}$ , and the common-mode and output limitations of each amplifier ( $V_{IA1}$ ,  $V_{IA2}$ ,  $V_{OA1}$ ,  $V_{OA2}$ ).

$$V_{O\_IA1} = 2 \times G \times (V_{IA1} - V_{CM}) + V_{REF} \quad (17)$$


$$V_{O\_IA2} = -2 \times G \times (V_{IA2} - V_{CM}) + V_{REF} \quad (18)$$

$$V_{O\_OA1} = V_{OA1} \quad (19)$$

$$V_{O\_OA2} = 2V_{CM} - V_R + 2G_{A1}V_{OA2} (V_{OA2} - V_{CM}) \quad (20)$$

In order to operate in a linear region, the voltage at  $V_{IA1}$  must not violate the input common-mode range of  $A_1$ . Similarly, the voltage at node  $V_{OA1}$  must not violate the output swing limitation of  $A_1$ . The same holds true for  $V_{IA2}$  and  $V_{OA2}$  for op amp  $A_2$ . The values of the internal op amp limitations are not usually explicitly stated in an instrumentation amplifier's data sheet. In lieu of such

Figure 8. Op amp  $V_{CM}$  and  $V_{OUT}$  ranges for 3.3-V supply<sup>[1]</sup>

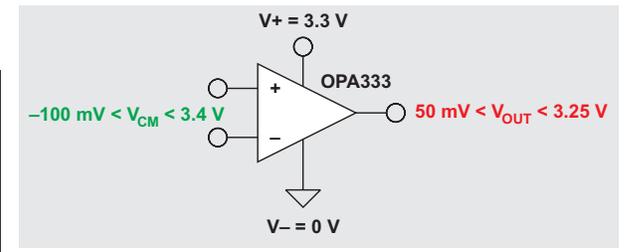

information, a combination of examining the device's limitations and measuring the linear operating region can be used to determine the values.

To move the input common-mode range closer to the negative supply voltage, some instrumentation amplifiers (for example, INA122) level-shift the inputs using precision transistor buffers.<sup>[1]</sup> This is particularly useful when operating with a single supply.

Figure 9 depicts a TINA-TI™ simulation that plots Equations 17 through 20 for both the maximum and minimum common-mode and output-swing limits for the internal amplifiers of the INA122. The linear operating region is the interior of all lines.

Figure 9.  $V_{CM}$  vs.  $V_{OUT}$  plot

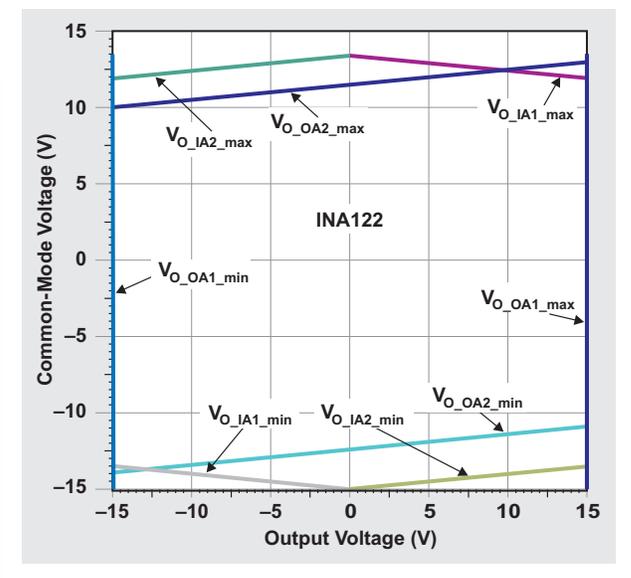
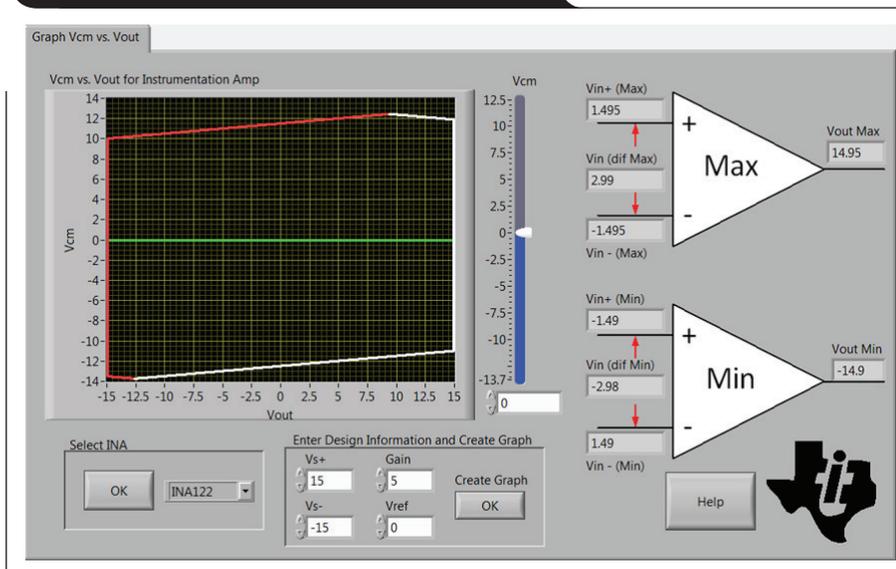


Figure 10.  $V_{CM}$  vs.  $V_{OUT}$  software tool

A software tool was developed to simplify the creation of  $V_{CM}$  vs.  $V_{OUT}$  plots for varying gains, reference voltages, and supply voltages. See Related Web sites at the end of this article for download links. Figure 10 depicts the  $V_{CM}$  vs.  $V_{OUT}$  plot for the INA122 given standard datasheet conditions. Notice that it compares well with Figure 1 and Figure 9. The datasheet plot in Figure 1, however, only depicts the output limitations of  $A_1$  and  $A_2$ , whereas the software tool includes the common-mode limitations. Finally, note that the software tool can be downloaded to generate  $V_{CM}$  vs.  $V_{OUT}$  plots for both two- and three-op-amp instrumentation amplifiers.

## Summary

This article addressed the most misunderstood concept of two-op-amp instrumentation amplifiers: the  $V_{CM}$  vs.  $V_{OUT}$  datasheet plot. A thorough analysis of the two-op-amp topology was delivered along with the derivation of the internal node equations. These equations were used to create the  $V_{CM}$  vs.  $V_{OUT}$  plots. The output from the downloadable software tool was found to correlate well with the plot in the INA122 datasheet. This tool gives designers a simple method for ensuring linear operation of the instrumentation amplifier in their design.

## Acknowledgements

The author would like to thank Art Kay at Texas Instruments for developing the  $V_{CM}$  vs.  $V_{OUT}$  software tool and Collin Wells for his technical contributions to this article.

## References

1. Peter Semig and Collin Wells, "Instrumentation amplifier  $V_{CM}$  vs.  $V_{OUT}$  plots," Part 1, Part 2 and Part 3, EDN Network, December 2014
2. Peter Semig, "How Instrumentation Amplifier  $V_{CM}$  vs.  $V_{OUT}$  plots change with supply and reference voltage," TI Precision Hub, January 30, 2015.

## Related Web sites

Software tool:

**$V_{CM}$  vs.  $V_{OUT}$  plot generator**

Product information:

**INA122**

**INA333**

**OPA333**

Subscribe to the AAJ:

[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)