

# Faster, cooler charging with dual chargers

By Jeff Falin

Applications Engineer, Power Management Battery Management Systems High Power Chargers

As the functionality and related power demands of the rechargeable battery-powered electronics such as smartphones and cameras grew, so did their batteries' capacities in order to extend run time. With higher-power wall adapters and USB 3.x providing higher currents at 5 V, 9 V and 12 V, increasing the charger's input current limit to accept the additional power gives more charging current for faster charging. This also results in more losses that the charger dissipates as heat. Historically, these losses have been distributed through the PCB ground plane by careful placement of the external FETs with the charge-controller IC's. Consumer demand for smaller portable electronics has forced IC manufacturers to develop battery-charger ICs with integrated FETs (I-FETs) and with smaller packaging. Including thermal considerations early in the design is critical to ensure that these high-current, I-FET chargers provide the designed charge current without overheating the PCB.

Thermal management in portable devices requires careful PCB layout. For example, removing the heat from an IC in a QFN package with an exposed bottom thermal pad requires that the thermal pad be connected to a copper ground plane that is not thermally saturated, preferably exposed (as opposed to internal). Too many ICs in close proximity that are trying to use the same heat-sinking ground plane can saturate the plane with heat, causing the ICs to overheat and go into lower-power thermal-regulation mode, or even shutdown.

Additionally, when the ground plane of the printed-circuit board (PCB) is thermally saturated, the device's outside case temperature rises to unacceptable levels. To prevent this, each IC and a section of its adjacent ground plane should be allocated a portion of a thermal budget. The thermal budget sets a hard limit to the amount of heat that a single, small-footprint, I-FET charger, outputting several amperes of current, can dissipate without raising the device's case temperature.

For a buck charger with integrated FETs, the IC's efficiency is


$$\eta = \frac{P_{OUT}}{P_{IN}} = \frac{V_{BAT} \times I_{CHRG}}{V_{BUS} \times I_{BUS}}$$

and loss through heat is

$$P_L = P_{IN} - P_{OUT} = P_{OUT} \times \left( \frac{1}{\eta} - 1 \right)$$

At higher currents, this loss is dominated by the  $I^2R$  losses across the internal FETs. Figure 1 shows the efficiency of a battery charger, such as the bq25890, at different charging currents and input voltages.

Figure 1. Example of I-FET charger efficiency

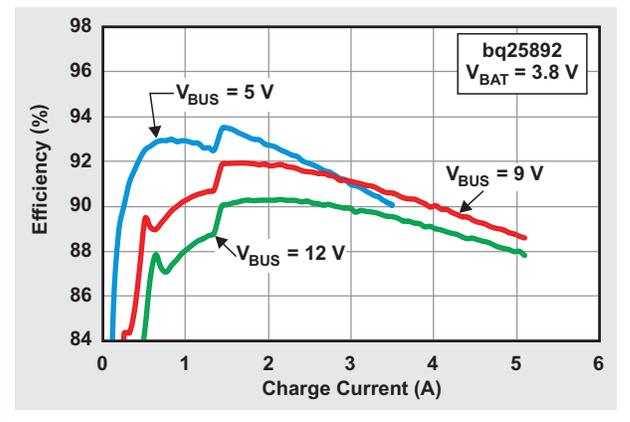


With a 9-V input adapter, a battery charger with 91% efficiency was set to provide a 3-A charging current to a 3.8-V charged battery with losses of

$$P_L = 3.8 \text{ V} \times 3 \text{ A} \times (1 / 0.91 - 1),$$

which equals 1.13 W in heat. The charger IC was soldered onto a four-layer, 31-mil thick, FR-4 board with 2-oz copper. The package's thermal pad was properly soldered down to the top-layer copper ground pour and through vias-to-ground pours on each of the internal and bottom layers. All of this copper acted as a heat sink. The image in Figure 2 shows a thermal image for a 4- by 4-mm QFN package where the temperature rise was 16.1°C at the IC's top-side case with a 25°C ambient air temperature. In this

Figure 2. Thermal image of single-charger operation (V<sub>IN</sub> = 9 V, V<sub>BAT</sub> = 3.8 V, I<sub>CHRG</sub> = 3 A)

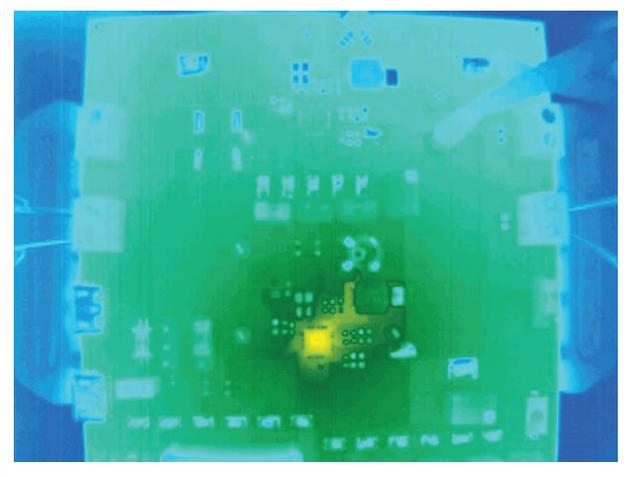

image, cool is shown as blue/green, warm as yellow, and hotter would show as red to white.

The PCB tested for Figure 2 contained no other power dissipating ICs, so the copper ground area approximates an infinite heat sink and was not saturated. This state is evidenced by the blue and green colors surrounding the yellow hot spot of the IC.


Increasing the charging current of this same charger by 50% to 4.5 A resulted in a temperature rise of 37°C compared to 25°C ambient. This temperature rise may be within the thermal budget of some devices, but not others.

Using the same concept of thermal distribution across the PCB as a charge controller with external FETs, two I-FET charger ICs in parallel, referred to as a dual-charger configuration, can be used. In general, there is no stability issue when connecting the battery-output pins of multiple chargers in parallel. This is because, while in constant-current (CC) mode, the charger's battery pin (BAT) has the characteristics of a high-impedance current source. While in constant-voltage (CV) mode, but well before termination, the battery pin characteristics are like a low-impedance voltage regulator. Dual-charger ICs in a parallel configuration are shown in Figure 3.

Charger-1 is configured for charging, however, if the internal battery FET (Q4) that provides a power path has low enough  $R_{DS(on)}$ , this IC also provides battery discharge through Q4. Charger-2 is configured only for charging. If required, charger-1 exclusively provides a USB On-The-Go (OTG) 5-V power rail at  $V_{BUS}$  after charger-2 has been configured for high-impedance mode. Even with the same termination voltage and current settings, and high regulation accuracy, one charger always attempts to terminate before the other due to the mismatch in each charger's internal reference voltages and currents. If both chargers are set to the same termination current, both chargers will have difficulty terminating the charge. Therefore, the termination current of one charger (typically charger-2) should be set higher than the other (typically charger-1) to allow for a smooth termination.

When the total required input current is high (for example,  $I_{CHARGE} > 5$  A with a 5-V adapter), the parallel configuration is recommended for best thermal distribution. With both input pins connected, neither charger can use its control loop for automatic input-current-limit

**Figure 3: Dual-charger ICs in a parallel configuration**

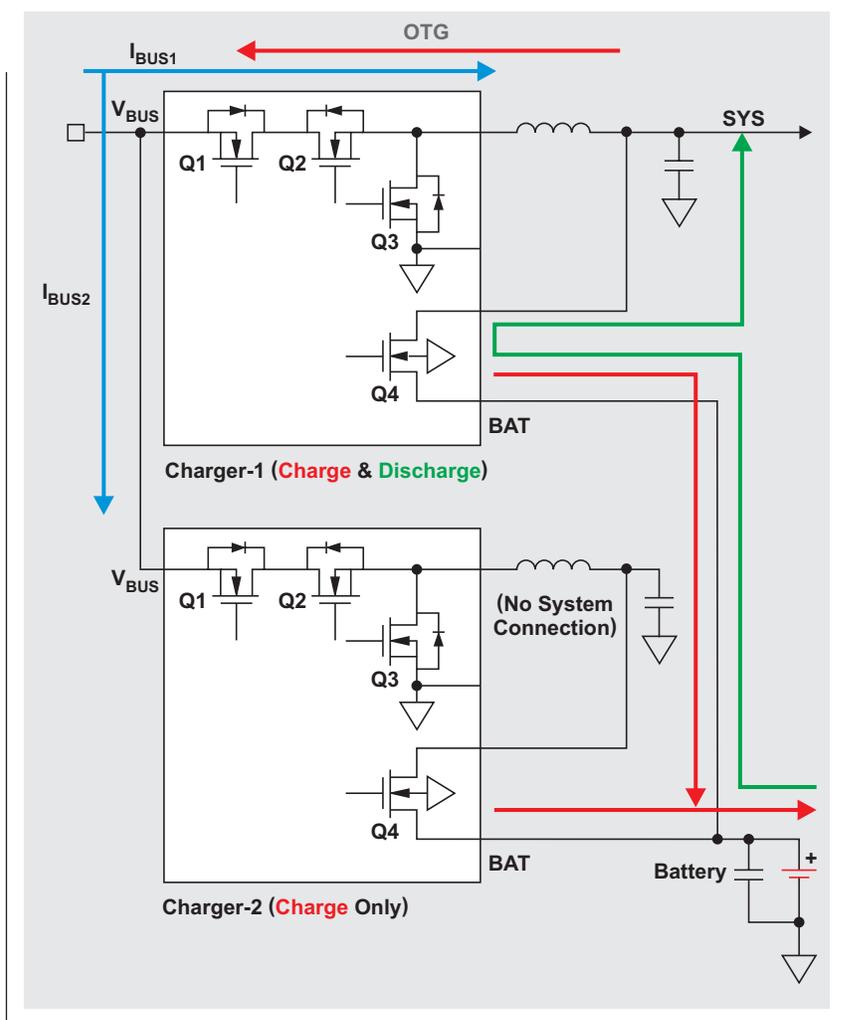

optimization (ICO) to extract maximum adapter power without causing loop instability at their mutual  $V_{BUS}$  node. Therefore, each charger's current-limit feature should be set to half the adapter's maximum output current. Inductor current ratings may also be reduced by half as well.

To prevent the  $V_{INDPM}$  loop from causing instability and to give charger-1 priority in powering the system, set the  $V_{INDPM}$  for charger-2 higher than that of charger-1. If the chargers have an integrated analog-to-digital converter (ADC) to provide real-time measurements of the charge current and the input, system and battery voltages, the host software must continuously monitor this information, as well as the loop status bits. The host software must then refresh each charger's current limit and charge current settings in order to maximize adapter power while balancing power and thermal loading between the two chargers.

When the total required input current is lower (for example,  $I_{CHARGE} < 5\text{ A}$  or an adapter change from 9 V to 12 V) and charger-1's reverse-blocking and current-limiting FET (Q1) has low enough  $R_{DS(on)}$ , the cascade configuration shown in Figure 4 may be a better option.

In the cascade configuration, charger-1 controls the total input current for both chargers. Host software development is greatly simplified because the  $V_{INDPM}$  and ICO features for charger-1 can be fully utilized to maximize adapter power extraction. In the event of a large system load transient while in the CV mode, the buck converter for charger-1 could see a higher input current. Therefore, the inductor for charger-1 needs to be sized to handle the adapter's full input current. If members of the same charger family with different I<sup>2</sup>C addresses are available, say the bq25890 for charger-1 and bq25892 for charger-2, development is even easier because no additional hardware is required to switch between the I<sup>2</sup>C communication lines of each charger.

Using the same PCB and test setup from Figure 2, the cascade chargers (Figure 4) were set to provide 2.25-A charge current to a 3.8-V battery and were 92% efficient. The heat loss for each charger was only

$$P_L = 3.8\text{ V} \times 2.25\text{ A} (1/0.92 - 1) = 0.74\text{ W.}$$

The top-side case temperature of both chargers rose above 25°C ambient by only 17°C, as measured by the thermal camera image in Figure 5. This is only 1°C above the single-charger case from Figure 2 for a 50% increase in charge current.

Figure 4: Dual-charger ICs in a cascade configuration

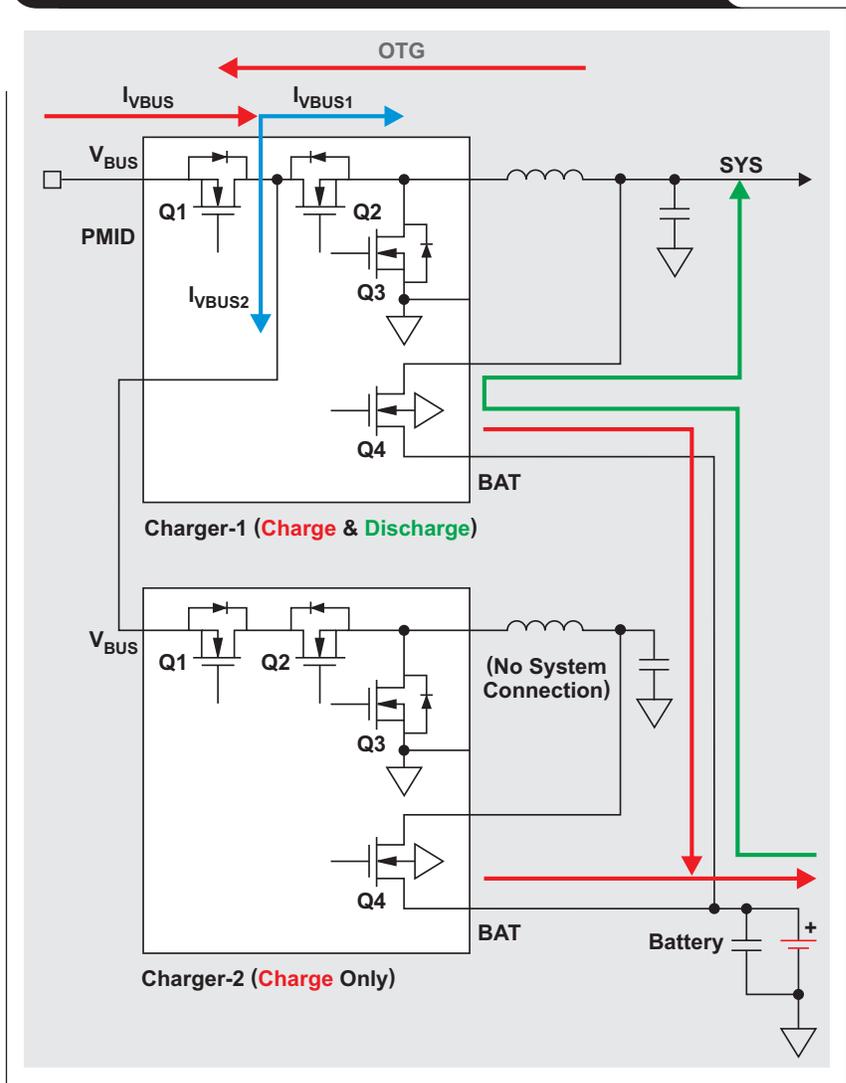


Figure 5. Thermal image of dual-charger operation ( $V_{IN} = 9\text{ V}$ ,  $V_{BAT} = 3.8\text{ V}$ ,  $I_{CHRG} = 4.5\text{ A}$ )

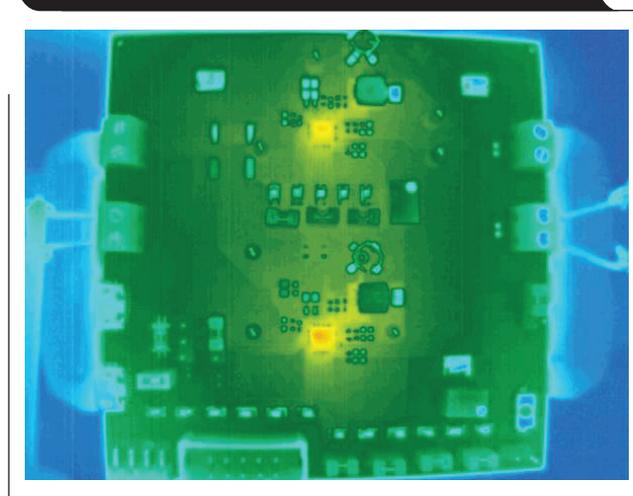


Figure 6 shows the typical charger-termination profile as the charger transitions from constant-current to constant-voltage regulation. Following the previous recommendation, for a clean termination, charger-2 terminates charging before charger-1.

## Conclusion

Most battery-charger ICs have a thermal regulation loop that reduces their charge current in order to protect the IC from damage due to overheating. As such, PCB thermal management is critical to maximize the charge current (which reduces charge time) into today's high-capacity batteries in addition to maintaining practical outside case temperatures. Thermal management includes assigning thermal budgets to all heat-producing ICs, careful IC placement, and heat-sink grounding on the PCB to distribute heat without thermally saturating the copper pours and planes of PCB ground. Using I-FET dual chargers, either in a parallel or cascade configuration as the application allows, gives better heat distribution for lower IC and case temperatures along with faster, cooler charging and longer device run times.

## Reference

1. "Dual Battery Charger IC Reference Design (connected in Cascode Configuration)," TI Designs, TIDA-00590

## Related Web sites

Product information:

**bq25890**


**bq25892**

**bq24715**

Subscribe to the AAJ:

[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)

**Figure 6. Dual-charger charge-termination profile**

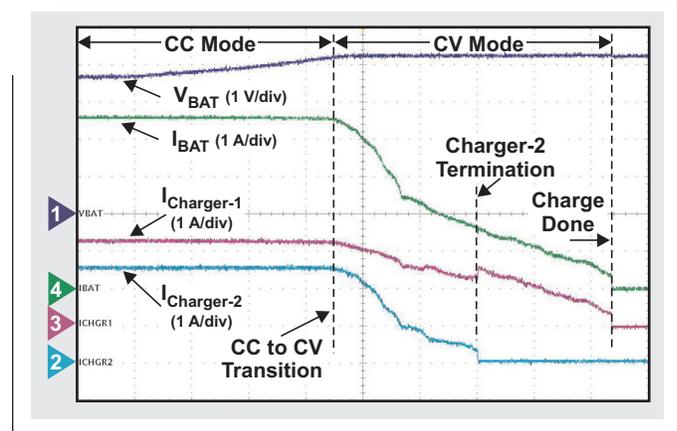

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)