

# Using op amps to reduce near-field EMI on PCBs

By Todd Toporski

Analog Applications

## Introduction

Automotive, industrial, medical, and many other applications use sensitive analog circuits that must perform their function while remaining immune to noise disturbances in their local environment. Many of these disturbances occur on nearby “noisy” circuits located on the same printed circuit board (PCB), while other interference can be picked up by cable interfaces that couple noise onto the PCB and its circuits.

One of the best ways to reduce electromagnetic interference (EMI) on PCB designs is through intelligent use of operational amplifiers (op amps). Unfortunately, op amps are often overlooked as a tool for reducing EMI in many applications. This may be due to the perception that op amps are susceptible to EMI and that extra steps must be taken to enhance their immunity to noise. While this is true of many older devices, designers may not be aware that newer op amps often have superior immunity performance over previous generations. Designers also may not understand or consider the key benefits that an op amp circuit can provide for reducing noise in their system and PCB designs. This article reviews sources of EMI and discusses op amp characteristics that aid in mitigating near-field EMI on sensitive PCB designs.

## EMI sources, victim circuits, and coupling mechanisms

EMI is a disturbance caused by a source of electrical noise that impacts a second electrical circuit in an unintentional and often undesirable manner. In all cases, an interfering noise signal is either a voltage, a current, electromagnetic radiation, or some combination of these three coupled from a noise source to a victim circuit.

EMI is not limited to radio frequency interference (RFI). Strong sources of EMI exist below radio bands in “lower” frequency ranges, sources such as switching


regulators, LED circuits, and motor drivers operating in the tens to hundreds of kilohertz range. A 60-Hz line noise is another example. Sources transfer noise to victim circuits through one or more of four possible coupling mechanisms. Three of the four are considered near-field coupling, including conducted coupling, electric-field coupling, and magnetic-field coupling. The fourth mechanism is far-field radiated coupling, in which electromagnetic energy is radiated over multiple wavelengths.

## Active filtering of differential-mode noise

Active op amp filters can significantly reduce EMI and noise on a PCB within the bandwidth of the circuit, but they are underutilized in many designs. The desired differential-mode (DM) signal can be band-limited while unwanted DM noise is filtered out. Figure 1 demonstrates DM noise coupled into an input signal through parasitic capacitance ( $C_p$ ). The combined signal and noise is received by a first-order active low-pass filter. The differential op amp circuit has its low-pass cutoff frequency set just above the desired signal bandwidth by  $R_2$  and  $C_1$ . Higher frequencies are attenuated by 20 dB per decade. Higher-order active filters (for example,  $-40$  or  $-60$  dB/decade) can be implemented if more attenuation is needed.

Resistor tolerances of one percent or lower are recommended. Likewise, capacitors having very good temperature coefficient (NPO, COG) and tolerances of 5% or lower are preferred for best filter performance.

Figure 1. DM and CM input noise applied to active op amp filter

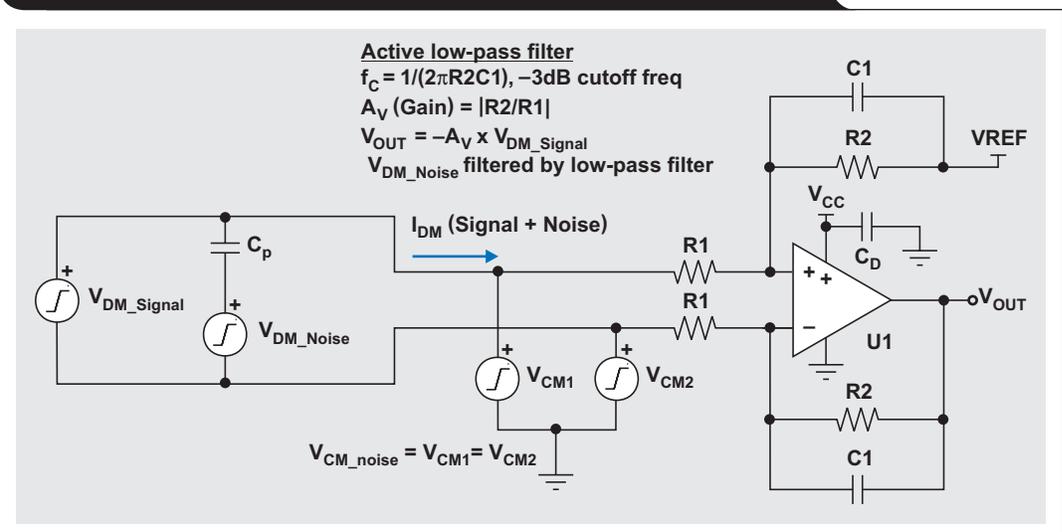

## Reducing input common-mode noise

In Figure 1, common-mode (CM) noise sources also present noise at the circuit's input. CM noise can be described as a noise voltage that is common (or the same) at both op amp inputs, and is not part of the intended differential mode signal that the op amp is trying to measure or condition. CM noise can occur in a number of ways. One example is a system where the ground reference of one circuit is at a different voltage potential than a second circuit to which it is interfacing. The difference in "ground" voltages may be in millivolts or many volts, and can also occur at many different frequencies. These differences in voltages cause unintended voltage drops and flow of currents that can interfere with the connected circuitry. Cars, aircraft, and large buildings with many circuits are often susceptible to this type of interference.

A key advantage of op amps is their differential input stage architecture, and their ability to reject CM noise when configured as a differential amplifier. Common-mode rejection ratio (CMRR) is specified for every op amp, but total CMRR of the circuit must also include the effects of input and feedback resistors. Resistor variation strongly impacts CMRR. Therefore, matched resistors with tolerances 0.1%, 0.01% or better, are needed to achieve a desired CMRR for the application. While good performance is achievable using external resistors, use of instrumentation or differential amplifiers with internally-trimmed resistors is another option. For example, the INA188 is an instrumentation amp with internally trimmed resistors and high CMRR of 104 dB.

In Figure 1 the CM noise ( $V_{CM\_noise} = V_{CM1} = V_{CM2}$ ) can be rejected by CMRR of the op amp circuit if the noise is within the active bandwidth of the circuit. The level of rejection depends on accurately-matched resistors to be chosen for  $R2/R1$ . Equation 1 can be used to determine  $CMRR_{TOTAL}$ , which includes the effects of resistor tolerance ( $R_{TOL}$ ) and op amp CMRR as specified in the data sheet. For example, if the op amp data sheet specifies its  $CMRR(dB) = 90$  dB, then  $(1/CMRR_{AMP}) = 0.00003$ . In many circuits, resistor tolerance will be the main limiting factor to achieve a target  $CMRR_{TOTAL}$ .

Equation 1 is derived from an equation in Reference 1 for CMRR of an ideal op amp, in which the  $CMRR_{AMP}$  term is assumed to be very large (infinity). For an ideal op amp, the  $(1/CMRR_{AMP})$  term is zero and  $CMRR_{TOTAL}$  is based only on resistors and  $A_V$ .  $CMRR_{TOTAL}$  can be converted to dB using Equation 2.

$$CMRR_{TOTAL} = \frac{\frac{1}{2}(1 + A_V)}{\frac{1}{2}(1 + A_V) \left( \frac{1}{CMRR_{AMP}} \right) + 2 \left( \frac{R_{TOL}}{100} \right)} \quad (1)$$

$$CMRR_{TOTAL} (dB) = 20 \log_{10} (CMRR_{TOTAL}) \quad (2)$$

where  $A_V$  = closed-loop gain of the op amp,  $R_{TOL}$  = % tolerance of  $R1$  and  $R2$  (for example, 0.1%, 0.01%, 0.001%), and  $CMRR_{AMP}$  = data-sheet specification for CMRR in decimal form (not dB).


## Enhancing immunity to RFI and other high-frequency EMI

As shown in previous sections, active filtering and CMRR can reliably reduce circuit noise in the device's band-limited range, including DM and CM EMI up into the MHz range. However, exposure to RFI noise above the intended operating frequency range may cause non-linear behavior in the device. Op amps are most susceptible to RFI on their high-impedance differential input stage because DM and CM RFI noise can be rectified by internal diodes (formed by p-n junctions on the silicon). This rectification creates a small DC voltage or offset that is amplified and may appear as an erroneous DC offset at the output. Depending on the accuracy and sensitivity of the system, this may create undesirable circuit performance or behavior.

Fortunately, enhancing op amp immunity (or reducing susceptibility) to RFI can be achieved using one of two methods. The first and best option is to use an EMI-hardened op amp that includes internal input filtering to reject noise in the range of tens of megahertz up to gigahertz. More than 80 TI devices exist today and can be found by searching "EMI Hardened" devices on the TI op amp parametric search engine. More details on EMI-hardened op amps can be found in References 2 and 3.

The second option is to add external EMI/RFI filters to the input of the op amp. This may be the only option if a design requires using a device that does not include internal EMI filters. Figure 2 shows a standard difference-amplifier configuration using external DM and CM filters that are targeted at higher EMI frequencies. Without input filters, the circuit gain is  $R2/R1$ . If passive input filters are added,  $R3$

**Figure 2. Passive EMI/RFI input filters improve high frequency immunity**

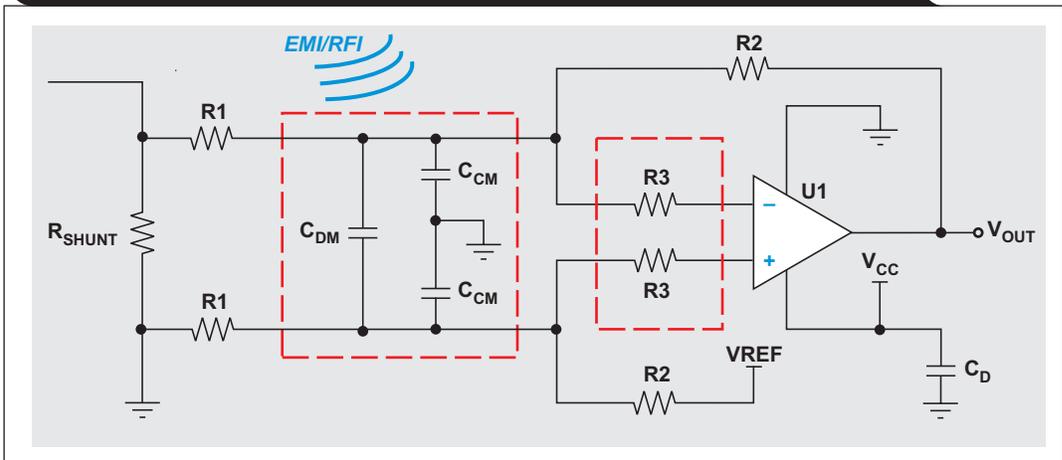

resistors are typically needed to prevent the  $C_{DM}$  capacitor from reducing the phase margin of the amplifier. The DM low-pass filter consists of both  $R1$  resistors,  $C_{DM}$ , and both  $C_{CM}$  capacitors. The CM low-pass filter uses both  $R1$  resistors and both  $C_{CM}$  capacitors.

Equations for the  $-3$ -dB cutoff frequencies of the DM and CM filters ( $f_{C\_DM}$  and  $f_{C\_CM}$ ) are shown below.  $f_{C\_DM}$  is set at a frequency above the desired bandwidth of the op amp circuit, and  $C_{DM}$  is typically determined first.  $C_{CM}$  capacitors are then chosen to be at least ten times smaller than  $C_{DM}$  to minimize their impact on  $f_{C\_DM}$ , and because  $C_{CM}$  capacitors are targeting higher frequencies. As a result,  $f_{C\_CM}$  will be set to a frequency higher than  $f_{C\_DM}$ . Note that an EMI-hardened device can be used to eliminate the components boxed in red and simplify the design.

$$f_{C\_DM} = \frac{1}{2\pi(2R1)(2C_{DM} + 2C_{CM})} \quad (3)$$


$$f_{C\_CM} = \frac{1}{2\pi(R1)(C_{CM})} \quad (4)$$

**Low output impedance reduces interference**

Another important characteristic of op amps is their very-low output impedance, typically a few ohms or less in most configurations. To understand how this is beneficial for reducing EMI, consider how EMI impacts low- and high-impedance circuits.

The diagram in Figure 3 represents two circuits. The first is an audio circuit that represents the input of an analog-to-digital converter (ADC) is comprised of a  $1-V_{P-P}$ , 2-kHz sinusoid ( $V_{S1}$ ), 600- $\Omega$  source impedance ( $R_{S1}$ ), and a 20-k $\Omega$  load impedance ( $R_{L1}$ ). Source impedances like 600  $\Omega$  are common in audio applications for sources such

**Figure 3. Clock noise source and audio victim circuit**

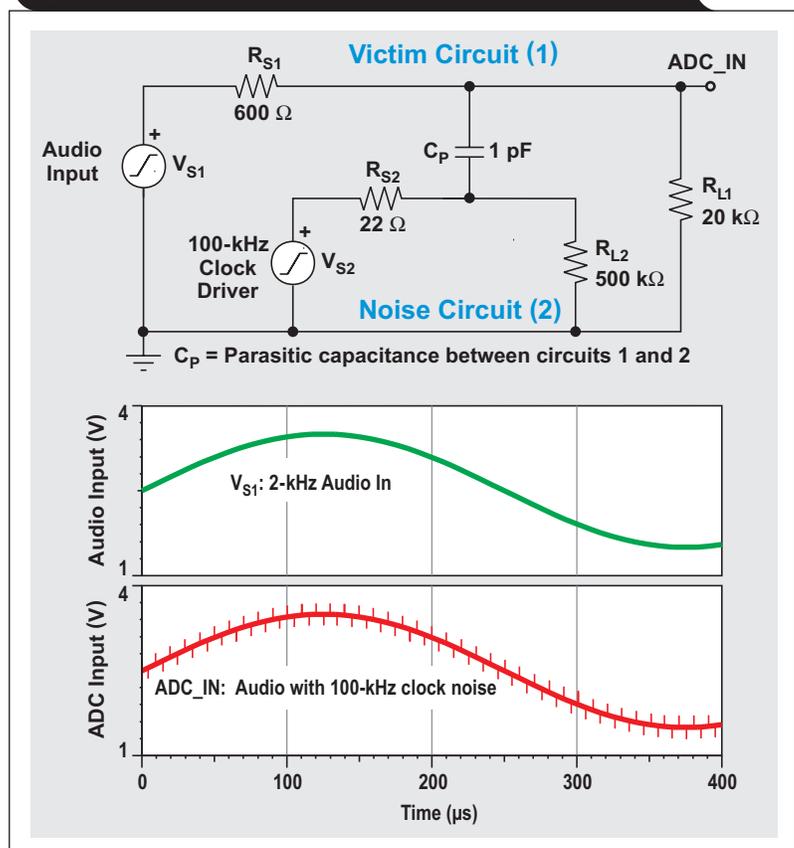

as microphones and high-input impedances like 20 k $\Omega$  are common for audio ADCs. The second circuit is a 100-kHz clock source driving a 3.3-V clock signal ( $V_{S2}$ ) with a series-termination resistor of 22  $\Omega$  ( $R_{S2}$ ) and load impedance of 500 k $\Omega$  ( $R_{L2}$ ). The high-impedance load represents the digital input of another device.

In a real system, I<sup>2</sup>C serial bus clocks in the 100- to 400-kHz range are common around audio ADCs and circuits. Although I<sup>2</sup>C clocks are typically driven in bursts

(not continuously), this simulation shows the possible impact during the time the clock is driving. A clock routed near a sensitive audio trace is a real possibility on high-density audio and infotainment PCB designs. For capacitive coupling to occur, it takes only a few picofarads of parasitic PCB capacitance to inject clock noise current into the victim audio signal. This is simulated using only 1 pF of parasitic capacitance, as shown in Figure 3.

How can noise be reduced in the audio circuit? As it turns out, reducing the impedance of a victim circuit is one way to reduce its susceptibility to coupled noise. For circuits with relatively high source impedance ( $> 50 \Omega$ ) coupled-noise can be reduced by minimizing the source impedance seen by the circuit load. In Figure 4, a non-inverting configuration of the OPA350 is added to the circuit to buffer the signal and isolate the source impedance from the load. Compared to  $600 \Omega$ , the output impedance of the op amp is very low, which significantly reduces the clock noise.

### Don't forget the importance of decoupling


Adding decoupling capacitors to power supply pins is extremely beneficial in filtering high-frequency EMI noise

and enhancing the immunity of the op amp circuit. All figures in this article show decoupling capacitor  $C_D$  as part of the circuit. While the subject of decoupling can get complex very quickly, a few good “rules of thumb” apply to any design. In particular, select capacitors with the following characteristics:

- Very-good temperature coefficient, such as X7R, NPO, or COG
- Very-low equivalent series inductance (ESL)
- Lowest possible impedance over the desired frequency spectrum
- Capacitor values in the 1- to 100-nF range usually work well, but criteria (b) and (c) above are more critical than the capacitor value.

Placement and connections are just as critical as the selected capacitor. Place capacitor as close to the supply pins as possible. Connections to PCB supply/ground should be as short as possible with short traces or via connections.

**Figure 4. Op amp circuit reduces EMI from clock source**

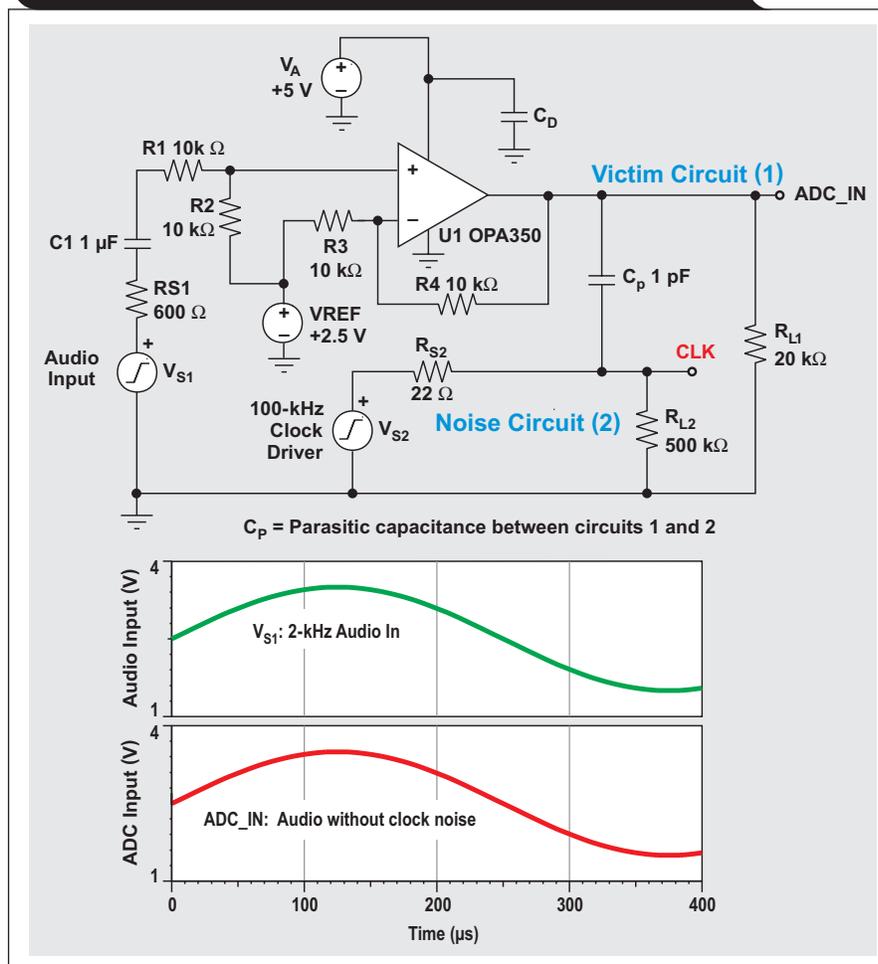

## Conclusion

Op amps can help to reduce near-field EMI on a PCB and enhance the system design. Here are some key points to consider for any design:

- Reduce input DM noise from cables/circuits using a well-chosen active filter configuration (Figure 1).
- Reduce input CM noise from cables/circuits by selecting an op amp with high CMRR and using precision matched resistors (Figure 1, Equations 1, 2).
- Further enhance immunity to high-frequency EMI or RFI (both DM/CM noise) by selecting an EMI-hardened device, or by using external passive EMI/RFI filters (Figure 2).
- Use the low impedance of the op amp output to reduce coupled noise when driving the signal to other circuits on the PCB.
- Finally, reduce supply noise by using a proper decoupling strategy for the op amp and all other circuits.

## References

1. S. Franco, "Circuits with Resistive Feedback," *Design with Operational Amplifiers and Analog Integrated Circuits*, 3rd ed. New York: McGraw-Hill, 2002, Ch. 2, pp 75-76
2. Chris Hall and Thomas Kuehl, "EMI Rejection Ratio of Operational Amplifiers," Texas Instruments Application Note (SBOA128), August 2011
3. "A Specification for EMI Hardened Operational Amplifiers," Texas Instruments Application Note (SNOA497B), April 2013
4. Jerry Freeman, "Techniques to enhance op amp signal integrity in low-level sensor applications, Part 4," *EETimes*, Dec. 18, 2008

## Related Web sites

TINA-TI™ amplifier design tool:

[www.ti.com/tool/tina-ti](http://www.ti.com/tool/tina-ti)

Product information:

**INA188**

**OPA350**

Subscribe to the AAJ:

[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)