

Modeling the output impedance of an op amp for stability analysis

By Collin Wells, *Application Engineer, Precision Analog*
Miro Oljaca, *End Equipment Lead, Industrial Systems*

Introduction


The interaction between the output stage of an operational amplifier (op amp) and capacitive loads can impact the stability of the circuit. Throughout the industry, op-amp output-stage requirements have changed greatly since their original creation. Classic output stages with the class-AB common-emitter bipolar junction transistor (BJT) have now been replaced with common-collector BJT and common-drain complementary metal-oxide semiconductor (CMOS) devices. Both of these technologies enable rail-to-rail output voltages for single-supply and battery-powered applications.

A result of changing these output-stage structures is that the op-amp open-loop output impedance (Z_O) changed from the largely resistive behavior of early BJT op amps to a frequency-dependent Z_O that features capacitive, resistive, and inductive portions. Proper understanding of Z_O over frequency is crucial for the understanding of loop gain, bandwidth, and stability analysis. This article develops a passive-component model of the Z_O curve for a three-stage op amp. This enables a deeper understanding of the different regions of a modern op-amp Z_O curve that will simplify op-amp stability analysis when designing circuits.

Op-amp output impedance


Output stages with the classic common-emitter BJTs feature flat resistive Z_O curves as shown in Figure 1a. Many CMOS rail-to-rail output amplifiers feature two-stage Z_O curves (Figure 1b). Three-stage BJT and CMOS-output topologies that create rail-to-rail outputs while achieving open-loop gains greater than 120 dB, often feature the three-stage Z_O curve shown in Figure 1c. The Z_O curves shown here should not be confused with the closed-loop output impedance (Z_{OUT}) curves that are also shown in op-amp data sheets.

Figure 1. Z_O for different op-amp output stages

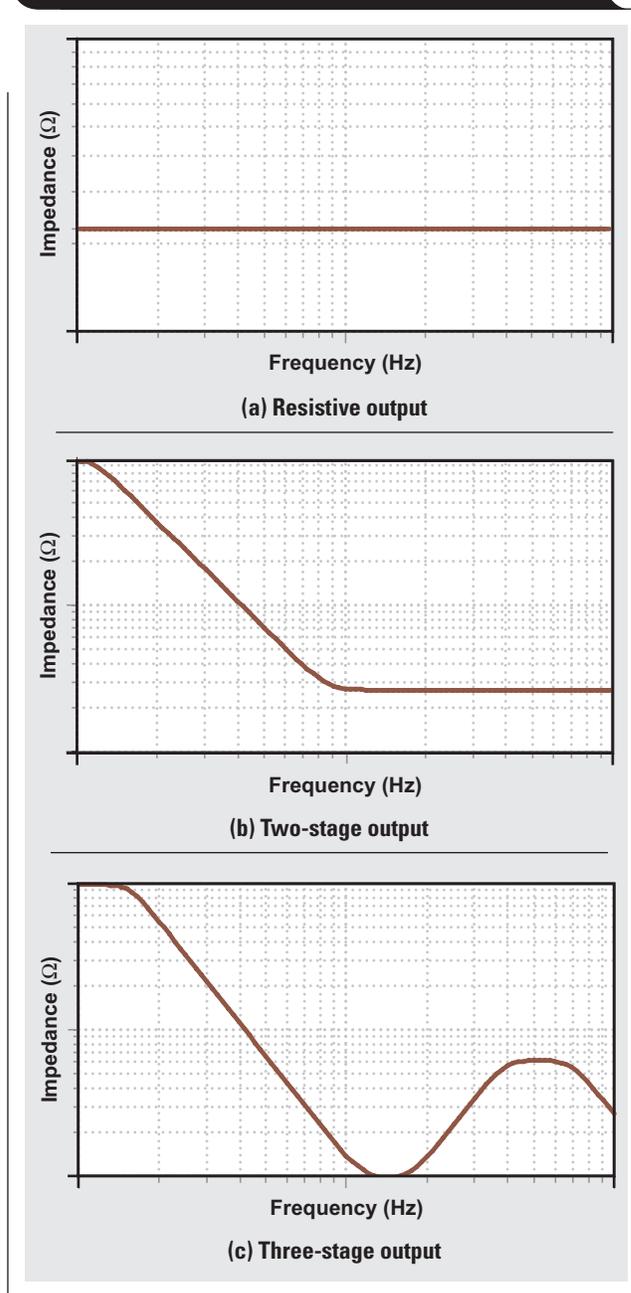

The test circuit to measure the open-loop output impedance of op amps in circuit-simulation programs (SPICE) is shown in Figure 2. The circuit uses a very large 1-TH inductor (L_T) and a 1-TF capacitor (C_T) as the feedback components. The L_T inductor provides a closed-loop unity-gain feedback path at very low frequencies near DC to define the circuit operating point, while opening the feedback loop for AC. This allows for an open-loop measurement of the output impedance for all frequencies of interest. The C_T capacitor is open at DC and then connects the inverting input to the same potential as the non-inverting input for all frequencies of interest. A current source can then be injected directly into the output while measuring the output voltage, V_{OUT} . The voltage probe on the output will be equal to Z_O in dB. The results must be converted from dB to a logarithmic scale in V/A to obtain Z_O in Ω .

Figure 2. Simulation circuit for open-loop output impedance (Z_O)

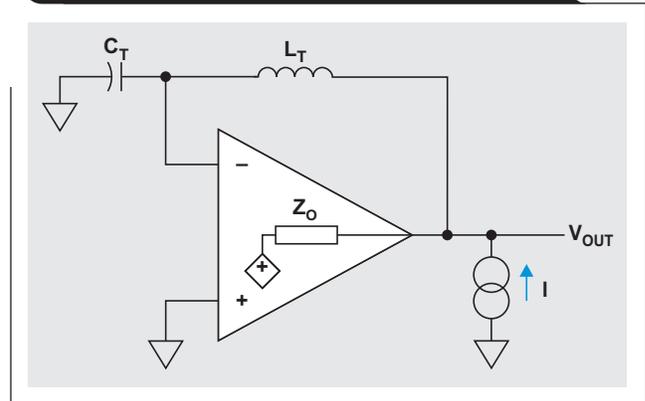

Calculating Z_O curve values

The Z_O simulation results for a typical three-stage op amp are shown in Figure 3. While each op amp will have different magnitudes of output impedance, the shape shown in this curve will typically exist.


The resistive, capacitive, and inductive portions of the Z_O curve from Figure 3 have been labeled to develop a more intuitive understanding of the Z_O behavior over frequency. Resistive regions are the easiest to identify as the flat regions of the curve. A three-stage output impedance typically has three resistive regions marked as R_{LOW} , R_{MID} , and R_{HIGH} . Capacitive regions result in an equivalent -20 -dB/decade decrease in Z_O with frequency as shown in the regions marked C_{LOW} and C_{HIGH} . The inductive region causes an equivalent 20 -dB/decade increase in Z_O over frequency as shown in the L_O region of the curve.

The values of the resistive regions of the curve can be read directly from the flat regions of the curve. Table 1 shows the resistive values from the curve in Figure 3.

Table 1. Resistance values in the resistive regions of the Z_O curve

Designator	Value	Units
R_{LOW}	4.87	$M\Omega$
R_{MID}	4.09	Ω
R_{HIGH}	1.03	$k\Omega$

Figure 3. Typical Z_O magnitude response of a three-stage op amp

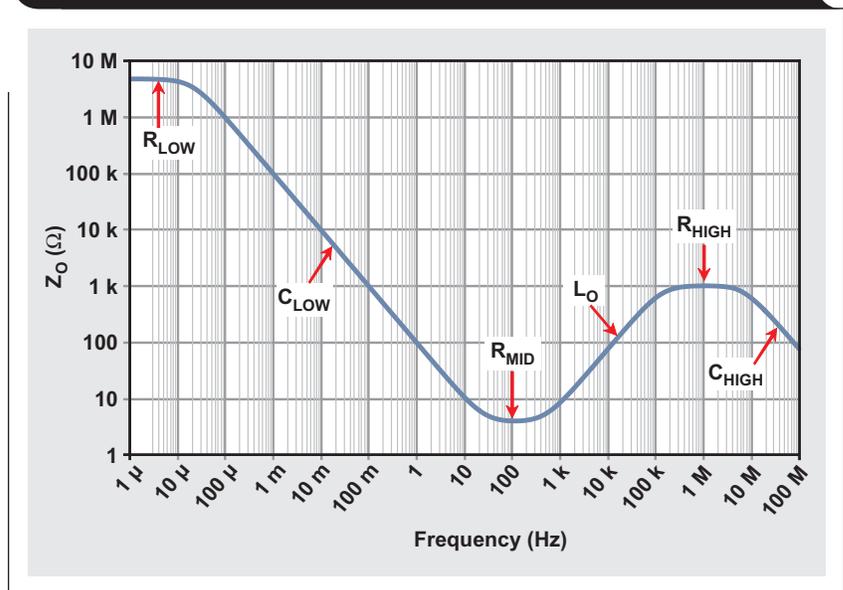

The inductance and capacitance equations, Equations 1 and 2, can be used to calculate the values in those regions of the curve.

$$Z_C(f) = \frac{1}{2\pi f \times C} \text{ or } C = \frac{1}{2\pi f \times Z_C(f)} \tag{1}$$

$$Z_L(f) = 2\pi f \times L \text{ or } L = \frac{Z_L(f)}{2\pi f} \tag{2}$$

Depending on the shape of the Z_O magnitude, it can be difficult to determine the correct frequency and impedance values to use in the calculations. This is especially true if there is little separation between the R, L, and C regions. The best frequency to use for the impedance

calculations is the frequency as a logarithmic scale that is in the middle of the poles and zeroes, which define the component's region of operation. The Z_0 phase-response curve shown in Figure 4 can be used to determine the location of the poles and zeros by identifying frequencies that correspond to $\pm 45^\circ$ phase shifts. A pole will have -45° of phase-shift from the initial value at the pole frequency, while a zero will have $+45^\circ$ of phase-shift from the initial value at the zero frequency.

The poles and zeros are marked in Figure 4 and their frequencies are listed in Table 2.

Table 2. Frequencies of the poles and zeros from the Z_0 phase curve shown in Figure 4

Name	Value	Units
f_{P1}	20.77	μHz
f_{Z1}	24.74	Hz
f_{Z2}	492.73	Hz
f_{P2}	143.33	kHz
f_{P3}	7.68	MHz

To calculate the value for the C_{LOW} region, first determine the average frequency (f_{C_LOW}) between the pole and zero frequencies that define the capacitive region, f_{P1} and f_{Z1} , using Equation 3.

$$f_{C_LOW} = \sqrt{f_{P1} \times f_{Z1}} = \sqrt{20.77 \mu\text{Hz} \times 24.74 \text{Hz}} = 22.67 \text{mHz} \tag{3}$$

The impedance of the curve at 22.67 mHz, $Z_{C_LOW}(f_{C_LOW})$, is equal to 4.47 k Ω . Equation 4 uses these values to calculate the 1.57 mF value of C_{LOW} .


$$Z_{C_LOW}(f_{C_LOW}) = \frac{1}{2\pi f_{C_LOW} \times C_{LOW}}$$

or

$$C_{LOW} = \frac{1}{2\pi f_{C_LOW} \times Z_{C_LOW}(f_{C_LOW})} = \frac{1}{2\pi \times 22.67 \text{mHz} \times 4472 \Omega} = 1.57 \text{mF} \tag{4}$$

The middle frequency for the L_0 inductance calculation (f_{L_0}) can be calculated in a similar way using f_{Z2} and f_{P2} (Equation 3). With a f_{L_0} of 8.403 Hz, the impedance is equal to 64.94 Ω , which can be used with f_{L_0} to calculate the L_0 inductance (Equation 5).

Figure 4. Typical Z_0 phase response over frequency for the three-stage op amp shown in Figure 3

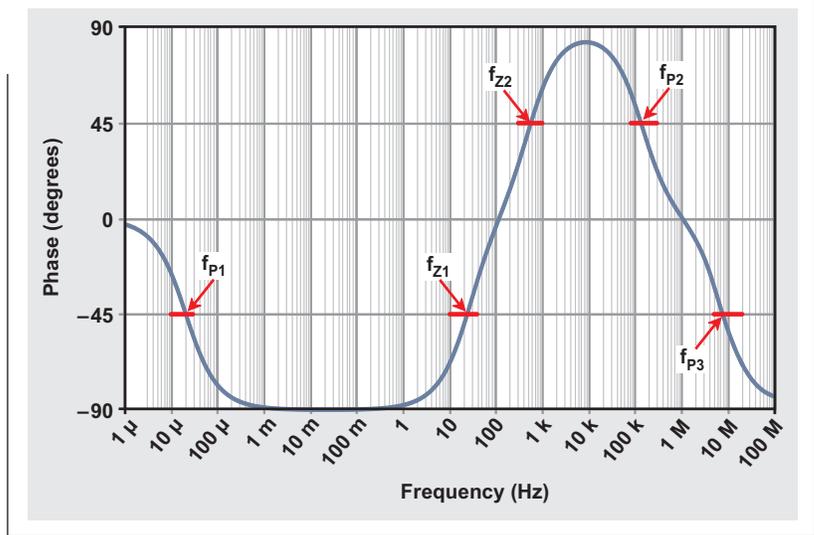

$$f_{L_0} = \sqrt{f_{Z2} \times f_{P2}} = \sqrt{492.73 \text{Hz} \times 143.33 \text{kHz}} = 8,403 \text{Hz}$$

$$Z_{L_0}(f_{L_0}) = 2\pi f_{L_0} \times L_0$$

or

$$L_0 = \frac{Z_{L_0}(f_{L_0})}{2\pi f_{L_0}} = \frac{64.94 \Omega}{2\pi \times 8,403 \text{Hz}} = 1.23 \text{mH} \tag{5}$$

The zero associated with C_{HIGH} is typically outside of the frequency range included in a Z_0 curve and, therefore, is unknown. C_{HIGH} can be calculated using the impedance at the maximum frequency shown in the graph (100 MHz) and adjusted later if required. Slight inaccuracies in the value of C_{HIGH} are not as critical as some of the other values because the C_{HIGH} region is typically outside of the op-amp's bandwidth. The values calculated from the Z_0 curve shown in Figure 3 are listed in Table 3.

Table 3. Values for all regions of the Z_0 curve

Designator	Value	Units
R_{LOW}	4.87	M Ω
C_{LOW}	1.57	mF
R_{MID}	4.09	Ω
L_0	1.23	mH
R_{HIGH}	1.03	k Ω
C_{HIGH}	20.14	pF

Lines representing the calculated passive R, L, and C impedances have been overlaid on the original Z_O curve in Figure 5. The impedance lines lay directly over the respective portions of the Z_O curve, confirming that the component value calculations are accurate.

Passive-component Z_O model of the three-stage op amp

A passive model of the three-stage op-amp Z_O curve using the calculated R, L, and C values is shown in Figure 6. Note that there are many ways to represent and model op-amp Z_O curves. Depending on the type of simulation being run, other methods may work better. However, the passive model presented here makes it easier to gain an intuitive understanding of the Z_O curve, which is critical for stability analysis.

While the component names and values from the calculations can be identified in the passive model, the arrangement of the components requires explanation. First, keep in mind that capacitors are open circuits at DC. Therefore, the path through the passive model can be identified as the series path through R_{LOW} and L_O , labeled as the first stage in Figure 6. The second stage, C_{LOW} and R_{MID} , are in parallel with R_{LOW} . When the impedance of C_{LOW} begins to encroach upon the value of R_{LOW} , the output impedance will decrease. The impedance stops decreasing once the impedance of C_{LOW} drops below the value of the series R_{MID} resistance.

Once the impedance of the L_O inductor increases above the level of R_{MID} , the curve will increase. The curve continues to increase until the impedance reaches the R_{HIGH} resistance in the third stage, which is in parallel with the first two stages. The C_{DAMP} capacitor is required to prevent R_{HIGH} from interfering with the Z_O curve at low frequencies. C_{DAMP} will be selected such that the R, L, C circuit formed from R_{HIGH} , L_O , and C_{DAMP} has a damping factor (ζ) greater than one, which prevents undesired peaking in the Z_O curve. The C_{HIGH} impedance in the fourth stage is in parallel with the entire model and will cause the curve to decrease at high frequencies once its impedance is lower than the R_{HIGH} resistance. The R_{VHIGH} resistance is included to flatten the curve back to a known resistance at frequencies much higher than the bandwidth of the op amp. Its value is not critical because it will have an effect well outside of the bandwidths of interest.

Figure 5. Simulated Z_O with equivalent R, L, and C impedances overlaid


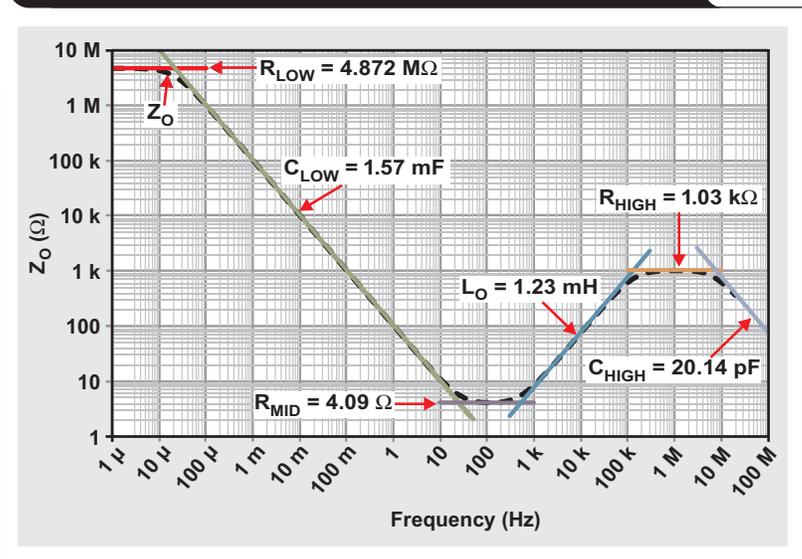


Figure 6. A passive-component Z_O model for a typical three-stage op amp

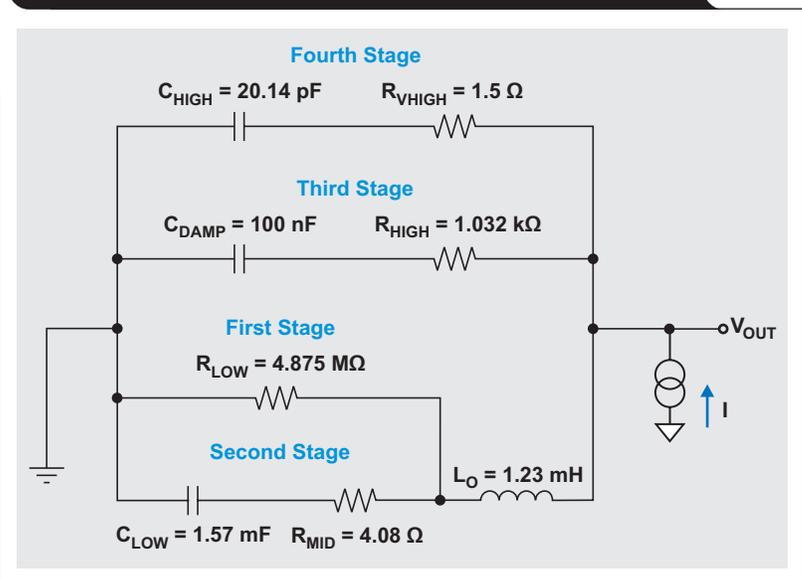

Verifying the passive model

The simulation results of the passive model are compared to the original simulated results from the full op-amp transistor-level model in Figure 7. As expected from the calculations, the passive-model output impedance lies directly on top of the results of the op-amp transistor-level model simulation.

A comparison of the phase results from the passive model and the op-amp transistor-level model are shown in Figure 8. Comparing the phase results is often a more rigorous verification because slight deviations in the magnitude are often easier to identify in the phase response. The passive-model results once again lie directly on top of the results for the op-amp transistor-level model simulated. This confirms that the passive model presented here is an accurate representation of the Z_O curve of a typical three-stage op amp.

Conclusion

Op-amp output stages have evolved from classic BJT output stages with resistive output impedances to the RLC three-stage output impedances found in many rail-to-rail output stages with high open-loop gain. To help develop a more intuitive understanding of these output impedance structures, a model of an example op-amp output impedance was created out of passive components. The passive model helped to intuitively determine what effects output loading have on the circuit performance in the different regions of the curve. The results for this passive model exactly matched the results from the original op-amp transistor-level simulation model. This proved that the passive RLC model is an accurate representation of the three-stage output impedance that can be used for stability analysis.

References

1. Jerald G. Graeme, "Optimizing op amp performance," ISBN: 978-0071590280.
2. Sergio Franco, "Design with operational amplifiers and analog integrated circuits," ISBN: 978-0078028168.
3. Miro Oljaca, Collin Wells, and Tim Green, "Understanding open loop output impedance of the PGA900 DAC gain amplifier," TI Application Report (SLDA033A), May 2015.
4. Tim Green and Collin Wells. "Solving op amp stability issues," TI E2E™ Community Precision Amplifier Forum, October 14, 2015.
5. Miro Oljaca and Collin Wells. "How system operating conditions affect CMOS op amp open-loop gain and output impedance," Industrial Embedded Systems, December 17, 2015.

Figure 7. Comparing the Z_O magnitude results of the passive model to the op-amp transistor-level model


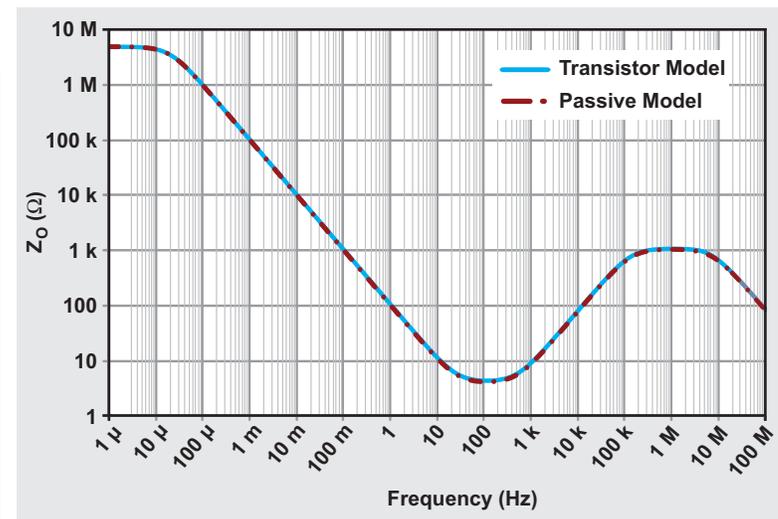


Figure 8. Comparing the Z_O phase response of the passive model to the op-amp transistor-level model

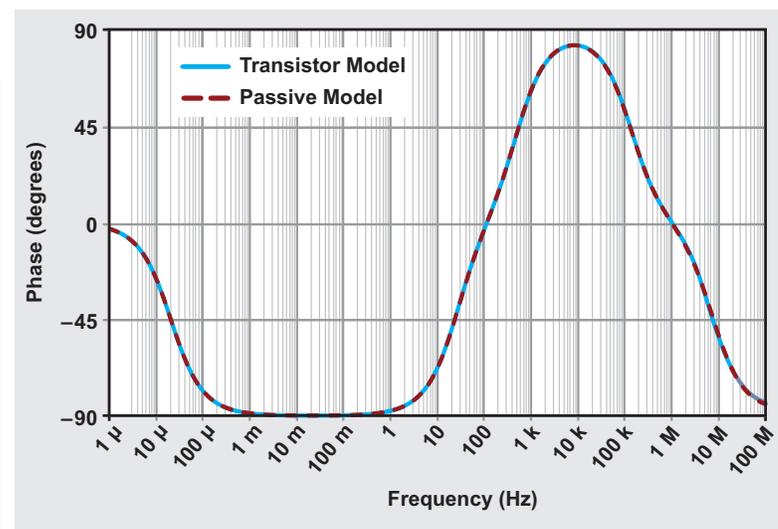

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com