

AN-2220 Precision Current Limiting with the LMP8646 and LMZ12003

ABSTRACT

This application report discusses how to design the Texas Instruments LMP8646 with the LMZ12003 voltage regulator and a resistive load application.

Contents

1	Overview	2
2	Example	2

List of Figures

1	Resistive Load Application with LMZ12003 Regulator and LMP8646 Precision Current Limiter.....	2
2	SuperCap Application with LMZ12003 Regulator Plot	3

Step 3: Choose the gain resistor, R_G, for LMP8646

R_G is chosen from I_{LIMIT}. As stated in Equation 1, since V_{OUT} = V_{FB} = 0.8V, I_{LIMIT} = 1A, and R_{SENSE} = 50 mOhm, R_G can be calculated as:

$$R_G = (V_{OUT} \times 5 \text{ kOhm}) / (R_{SENSE} \times I_{LIMIT}) \tag{2}$$

$$R_G = (0.8 \times 5 \text{ kOhm}) / (50 \text{ mOhm} \times 1A) = 80 \text{ kOhm (approximate)}$$

Step 4: Choose the Bandwidth Capacitance, C_G.

The product of C_G and R_G determines the bandwidth for the LMP8646. To see the range for the LMP8646 bandwidth and gain, see the Typical Performance Characteristics plots in *LMP8646 Precision Current Limiter (SNOSC63)*. Since each application is very unique, the LMP8646 bandwidth capacitance, C_G, needs to be adjusted to fit the appropriate application.

Bench data has been collected for the supercap application with the LMZ12003 regulator; it was discovered that this application works best for a bandwidth of 2 kHz to 30 kHz. Operating anything less than this recommended bandwidth might prevent the LMP8646 from quickly limiting the current. Choosing a bandwidth that is in the middle of this range is recommended and using the equation:

$$C_G = 1/(2 \times \pi \times R_G \times \text{Bandwidth}) \tag{3}$$

to find C_G (this example uses a C_G value of 0.1nF).

After selecting an initial C_G value, capture the plot for I_{LIMIT} and adjust C_G until a desired load current plot is obtained.

Step 5: Choose the Output Resistor, R_{OUT}

R_{OUT} plays a very small role in the overall system performance for the resistive load application. R_{OUT} is more important for a supercap load because the initial current error is typically large with a capacitive load. Because current is directly proportional to voltage for a resistive load, the output current is not large at startup. The bigger the R_{OUT}, the longer it takes for the output voltage to reach its final value. It is recommended that the value for R_{OUT} is at least 50 Ω, which is the value used for this example.

Step 6: Adjusting the Components

Capture the output current and output voltage plots and adjust the components as necessary. The most common components to adjust is C_G for the bandwidth. An example output current and voltage plot can be seen in Figure 2

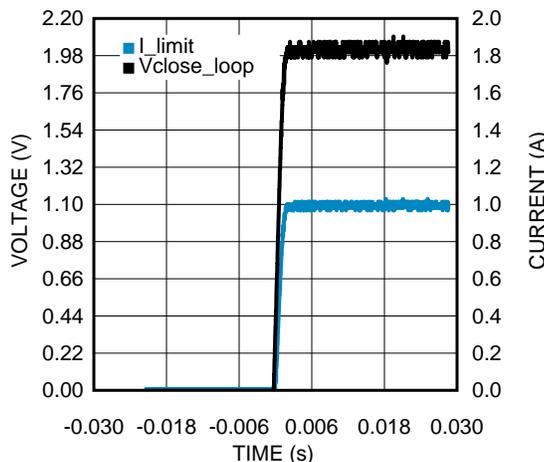


Figure 2. SuperCap Application with LMZ12003 Regulator Plot

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com