


**LMH0002,LMH0030,LMH0031,LMH0034,LMH0044,
LMH0046,LMH1981**

Timing is Everything ?Co The Broadcast Video Signal Path



Literature Number: SNLA207

High Performance Analog Video Solutions

 

AVAILABLE
LEAD-FREE

Product ID	Type	Supported Video Formats	Inputs	Outputs	Spec Supply Range (V)	Packaging
Sync Separators						
LMH1981	50% slicing	NTSC, PAL, SECAM, 480i/p, 576i/p, 720p, 1080i/p	0.5 to 2.0 Vpp	H-sync, V-sync, odd/even, burst/clamp, video format, composite sync	3.3 to 5	TSSOP-14
LM1881	70 mV fixed	NTSC, PAL, SECAM	0.5 to 2.0 Vpp	V-sync, odd/even, burst/clamp, composite sync	5 to 12	SOIC-8, DIP-8
Video Converters						
LMH1251	YPbPr to RGBHV converter	480i/p, 576i/p 720p, 1080i, 1080p XGA, SXGA, UXGA	YPbPr	RGBHV	5	TSSOP-24

AVAILABLE
LEAD-FREE

Product ID	Type	SSBW (MHz)	A _v (V/V)	Slew Rate (V/μs)	I _{cc} (mA/Ch)	Spec Supply Range (V)	Packaging
Analog Crosspoint Switches							
LMH6582	16 x 8	500	1	3000	110 mA (total)	±3.3V to ±5V	TQFP-64
LMH6583	16 x 8	500	2	3000	110 mA (total)	±3.3V to ±5V	TQFP-64
Analog Multiplexers							
LMH6570	2:1 Mux	500	2	2200	15	6 to 12	SOIC-8
LMH6572	Triple 2:1 Mux	350	2	1400	23	6 to 12	SSOP-16
LMH6574	4:1 Mux	500	2	2200	13	6 to 12	SOIC-14

For more information on National's video amplifiers, visit www.national.com/see/videoamps

Broadcast Video Signal Path

that is being supplied. In this edition of the Signal Path Designer, we will look at this application in detail, and examine the design considerations for each of the six blocks.

Cable Equalizer

The SDI inputs on video broadcast equipment typically support long cable lengths: over 140m for high definition signals, and over 300m for standard definition signals. In order to support long cables, there needs to be a cable equalizer.

Long cables have a low-pass characteristic, where the attenuation of the input signal is proportional to the length of the cable, and the square root of the frequency. *Figure 2* shows the frequency response of a 100m length of a common (Belden 1694A) cable used in video installations.

 


Figure 2. Belden 1694A Frequency Response

Although seeing the attenuation with frequency is helpful in designing the complementary filter that you will need to recover the signal, the image that you really want to see is the eye diagram. This tells you if there is there an opening big enough to recover the data. *Figure 3* shows the eye diagrams for a 1.5 Gbps signal (an HD-SDI signal) after it has gone through various different lengths of cable. From the standpoint of this article, the primary result of the skin effect is that as the frequency increases, a smaller and smaller portion of the cross section of the cable will be carrying the signal, so there will be greater signal attenuation at higher frequencies than at lower frequencies. The response curve for this loss will be proportional to the $\sqrt{\omega}$ which makes compensation difficult for standard types of filters.

 


Figure 3. Oscilloscope Traces of an HD-SDI Signal After Going Through Coax Cable

To attempt to match the frequency response of the cable, the designer carefully places the zeroes in his or her filter such that the resulting response is a close approximation to the $\sqrt{\omega}$ response of the cable.

To deal with the fact that both high gain and high bandwidth are required at the same time, equalizer circuits are realized in exotic, high-speed processes such as the National's 0.25 μm BiCMOS SiGe process. An example of one of these equalizers is the LMH0044 cable equalizer. With this part, you can recover signals at data rates of up to 1.5 Gbps through 200m of Belden 1694A cable.



 


Figure 4. Equalized Outputs

HDI-SDI Signal Path Solutions

 


SDI Signal Conditioning

 

For more information, be sure to visit National's Broadcast Video Owners's Manual at www.national.com/see/bvom

AVAILABLE
LEAD-FREE

Product ID	Function	Max Speed (Mbps)	Temp Range (°C)	Eval Board	Comments	Packaging
Cable Drivers						
LMH0002MA	HD/SD Serial cable driver	1485	-40 to 85	SD002EVK	Selectable slew rate	SOIC-8
LMH0202MT	Dual HD/SD Serial cable driver	1485	0 to 70	SD0202EVK	Dual differential input, dual differential output	TSSOP-16
Adaptive Equalizers						
LMH0034MA	HD/SD Adaptive cable equalizer	143 to 1485	0 to 85	SD0342EVK	SMPTE 292M/259M Serial recovery	SOIC-16
LMH0024MA	3.3V SD Adaptive cable equalizer	143 to 540	-40 to 85	SD024EVK	Footprint compatible with LMH0034	SOIC-16
LMH0044SQ	HD/SD Adaptive cable equalizer	1.485 Gbps	0 to 85	SD044EVK	Equalize up to 200m of cable at HD (1.485 Gbps)	LLP-16
Encoder/Decoders						
LMH0030VS	SMPTE 292M/259M Digital video serializer/encoder	270 to 1485	0 to 70	SD130EVK	Integrated cable driver, FIFO, BIST, and TPG	TQFP-64
LMH0031VS	SMPTE 292M/259M Digital video serializer/decoder	270 to 1485	0 to 70	SD131EVK	FIFO, BIST, and TPG	TQFP-64
Reclockers						
LMH0046MH	HD/SD Reclocker	1.485 Gbps	-40 to 85	SD046EVK	Dual differential outputs, optional data rate clock; 27 MHz reference	TSSOP-20

 

Broadcast Video Signal Path

Deserializer

Once you have done the hard work of opening the eye of the signal coming in, you have to make sense of the bits that are coming at you, and this is the job of the deserializer. Video images have a very regular, repetitive format. They are composed of individual bits which are, at the next highest level of organization, divided into 10-bit words which are in turn divided into pixels. A series of pixels comprises a line, a series of lines makes up a field, and one or more fields are needed to complete the video frame. To sort out this organization, the SMPTE data sends a special sequence known as a Timing Reference Signal (TRS) at the start and end of each line. By detecting this TRS, it allows the receiver to figure out both the word and line alignment for the signal. At the end of each line, there are a couple of extra words inserted which tell the receiver what the line number is. A CRC is also included, so that the receiver will know if it has properly received all of the data in the line. There are a couple of things that can wreak havoc with receivers: DC content and long periods of time with no transitions. Most communications systems have a way to control this. In the case of the SMPTE 292 serial standard (HD-SDI) it is done with a combination of scrambling and encoding the data.

A good deserializer will extract all of this information for you, and present you with what you need. For this application, it consists of the picture data and the timing data. A deserializer such as the LMH0031 will do this for us, presenting the

picture data on two 10-bit data busses. The timing data is presented in the form of three digital signals representing H (start of a horizontal line), V (start of a vertical interval), and F (start of Frame). If the raster format is not interlaced, then you can use just H and V because they are the same.

The serial data is brought into the deserializer where it is decoded and descrambled. Then it is analyzed to find the TRSs which allows the deserializer to know how to break the bits into words. The TRSs' are further analyzed to extract the timing information which is encoded and the data is scrambled, it decodes and descrambles, then the framing is determined so that the deserialized data can be properly word aligned. All of this activity is generally done in the deserializer.

Sync Separator & PLL

Although the video world has gone mostly digital, one area where analog is still very common is in the sync-reference signal, which the studio uses to synchronize all of their equipment. The most common reference to use is a video signal which does not include picture information. This will consist of a series of pulses indicating the start of each video line, with a specific pattern that indicates the end of each field or frame. In this block of our genlock circuit, a sync separator circuit extracts H, V, and F (start of a horizontal line, start of a field, and start of a new frame) from the reference signal, and a PLL circuit generates a pixel clock which is synchronous with the reference signal.

 


Figure 5. Block Diagram of the LMH1981 Sync Separator & PLL Generating the Pixel Clock

For example, the LMH1981 is a high-performance multi-format sync separator that accepts standard analog SD or HD video signals with either bi-level or tri-level sync. It automatically detects the input video format and applies 50% sync slicing to ensure accurate sync extraction even if the input has irregular amplitude, offset, or noise conditions. To generate the pixel clock, a PLL should be set up to lock to the Hsync output of the LMH1981 and generate the desired clock frequency, which is typically 27 MHz for SD or about 74 MHz for HD. Something to consider when using a PLL for clock generation is that the divide ratio can be quite large and reduce loop bandwidth, which could make the PLL quite sensitive to jitter on Hsync. This makes it especially important to select a sync separator with a very low jitter Hsync output.

Frame Buffer

The frame buffer is simply a block of memory large enough to hold at least one entire frame of the image. This buffer needs to be dual port so that the data coming from the deserializer can be written into one side of the buffer, while data can be read from the other side of the buffer to be fed to the serializer. The buffer is organized in the same way as the video image, with consecutive pixels forming complete lines and consecutive lines forming the complete frame.

Timing Control

The timing control is the heart of the entire genlock system. The basic function is to control the writing into the frame buffer and the reading from the frame buffer. The timing control needs to keep track of two different timing domains. On the input side it receives the data, the timing information, and a clock from the deserializer. This data is written into the frame buffer, with a series of counters that keep track of the pixel and line information. This data is written synchronously with the clock being recovered from the deserializer. At the same time, the timing control takes the timing information coming from the sync separator and the pixel clock. These are used with a second set of counters to read data out of the frame buffer. This data is being read synchronously with the reference sync signal so that the image which was received by the deserializer is now being read synchronously with the reference. The data, along with the pixel clock are fed to the

serializer for output. Although video signals have very tight timing specifications, there will be some difference between the input and the output data rates, which means that eventually the frame buffer will either empty out, or overflow. The timing control circuitry has to recognize this situation and periodically repeat a frame or drop a frame to maintain the timing difference between input and output smaller than the size of the frame buffer.

Serializer


Once the data is read out of the frame buffer, it is in parallel format. Before it can be sent to the next piece of equipment it needs to be serialized and formatted to meet the SMPTE 292M HD-SDI standard. From a digital standpoint, new TRS characters are generated and inserted, new line numbers and CRCs are calculated and inserted, the data is then scrambled via the SMPTE scrambling algorithm and converted to NRZI format before being shifted out of a parallel to serial shift register. The key to doing all of this properly is to use a clock clean enough to meet the tight video timing specifications to shift the data out. SMPTE 292M allows no more than 0.2UI of jitter peak-to-peak on the serialized output, which means that the clock jitter needs to be below about 100 ps p-p. Most serializers take a clock which is at the parallel data rate as their input clock (for HD this would be approx 74 MHz) and then multiply it up to the serial rate of 1.5 GHz. Most good serializers will use a PLL for this multiplication that will reject some of the jitter in the original parallel clock. However, for the best performance it is best to start with the cleanest clock possible. In the example sync separator/clock generation circuit, you generated a pixel clock with a VCXO that has very low jitter so that added to the jitter rejection characteristics of the serializer will lead to a very low jitter output. Using the LMH0030 serializer with the VCXO clock source, you could expect your serial jitter to be approx 75 ps, well below the 0.2UI limit.

Summary

Using a handful of simple, off-the-shelf components, you can take a radical input video signal, which is marching to the beat of a different drummer, and get it to straighten up, and march with the rest of our signals. This way, you can switch from one program to another without disrupting the image on your screen. ■

Design Tools

WEBENCH® Signal Path Designer® Tools

 

Design, simulate, and optimize amplifier circuits in this FREE online design and prototyping environment allowing you to:

- Synthesize an anti-alias filter
- Select the best amplifier/ADC combo for your system specs
- Make trade-offs based on SNR, SFDR, supply voltage
- Simulate real-world operating conditions using SPICE
- Receive samples in 24 hours

webench.national.com

WaveVision 4.0 Evaluation Board

Test and evaluate A/D converters with National's easy-to use WaveVision 4.0 evaluation board. Each evaluation board comes complete with USB cable and support software.

Features and benefits:

- Plug-n-play ADC evaluation board
- USB interface to PC
- PC-based data capture
- Easy data capture and evaluation
- Highlighted harmonic and SFDR frequencies
- Easy waveform examination
- Produces and displays FFT plots
- Dynamic performance parameter readout with FFT
- Produces and displays histograms



National Semiconductor

2900 Semiconductor Drive
PO Box 58090
Santa Clara, CA 95052
1 800 272 9959

Visit our website at:
signalpath.national.com

For more information,
send email to:
new.feedback@nsc.com

Don't miss a single issue!



Subscribe now to receive email alerts when new issues of Signal Path Designer® are available:

signalpath.national.com/designer

Also, be sure to check out our Power Designer! View online today at:
power.national.com/designer



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated