

AN-202 A Digital Multimeter Using the ADD3501

Introduction

This application report discusses how to use Texas Instruments ADD3501 as a digital multimeter.

Texas Instruments ADD3501 is a monolithic CMOS IC designed for use as a 3 1/2-digit digital voltmeter). The IC makes use of a pulse-modulation analog-to-digital conversion scheme that operates from a 2 V reference voltage, functions with inputs between 0 V and 1.999 V and operates from a single supply.

The conversion rate is set by an external resistor and capacitor combination, which controls the frequency of an on-chip oscillator. The ADD3501 directly drives 7-segment multiplexed LED displays, aided only by segment resistors and external digit buffers. The ADD3501 blanks the most significant digit whenever the MSD is zero; and, during over range conditions, the display will read either +OFL or -OFL (depending on the polarity of the input.)

These characteristics make the ADD3501 suitable for use in low-cost instrumentation. An example of such use is the inexpensive, accurate, digital multimeter (DMM) presented here; an instrument that measures AC and DC voltages and currents, and resistance.


Circuit Description

Figure 1 shows the circuit diagram of the ADD3501-based DMM, and **Table 1** summarizes its measurement capabilities. Since the accuracy of the ADD3501 is $\pm 0.05\%$, the DMM's performance is mainly determined by the choice of discrete components.

Supporting the ADD3501 is a DS75492 digit driver, an NSB5388 LED display, and an LM340 regulator for the VCC supply. A 2-V reference voltage-derived from the LM336 reference-diode circuitry permits the 3 1/2-digit system a 1 mV/LSD resolution (that is, the ADD3501's full-scale count of 1999 or 1999 mV).

DC Voltage Measurement.

The DMM's user places the (+) and (-) probes across the voltage to be measured and sets the voltage range switch as necessary. This switch scales the input voltage, dividing it down so that the maximum voltage across the ADD3501's V_{IN+} and V_{IN-} pins is limited to 2V full-scale on each input range. The ADD3501 performs an A/D conversion, and displays the value of the DMM's input voltage. The instrument's input impedance is at least 10 M Ω on all DC voltage ranges. Except for the 2V range, the DMM's survival voltage, the maximum safe DC input, is in excess of 1 kV. On the 2-V range, the maximum allowable input is 700 V.

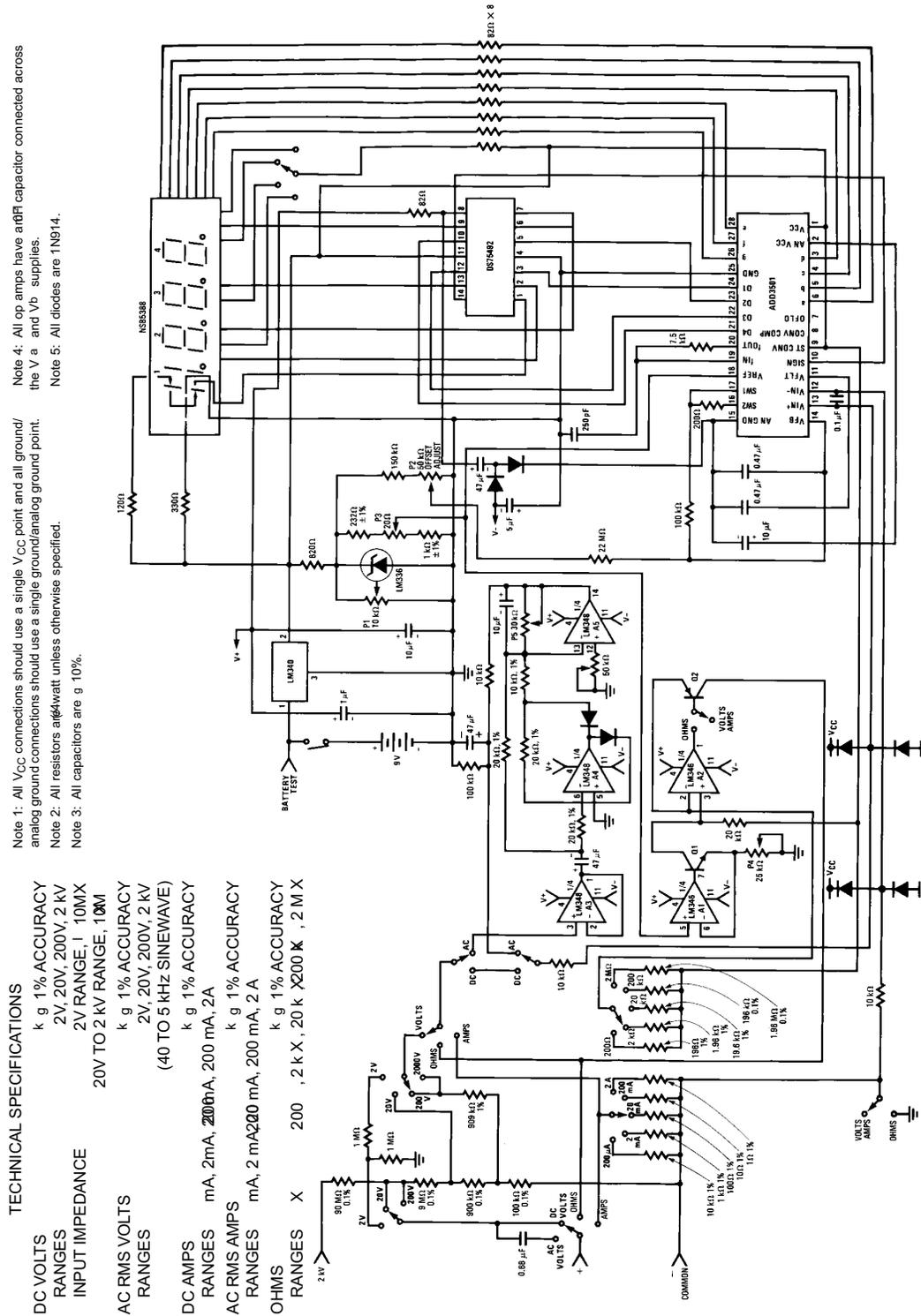

TL/H/5617±1

FIGURE 1. ADD3501 Low Cost Digital Multimeter

Figure 1. ADD3501 Low Cost Digital Multimeter

Table 1. DMM Performance

Measurement Mode	Range					Frequency Response	Accuracy	Overrange Display
	0.2	2	20	200	2000			
DC Volts	—	V	V	V	V	—	≤1% F.S.	±OFLO
AC Volts	—	V _{RMS}	V _{RMS}	V _{RMS}	V _{RMS}	40 Hz to 5 kHz	≤1% F.S.	±OFLO
DC Amps	mA	mA	mA	mA	mA	—	≤1% F.S.	±OFLO
AC Amps	mA _{RMS}	40 Hz to 5 kHz	≤1% F.S.	±OFLO				
Ohms	kΩ	kΩ	kΩ	kΩ	kΩ	—	≤1% F.S.	±OFLO

AC Voltage Measurement

Switching the DMM to its AC VOLTS mode brings the circuit of [Figure 2](#) into function. This circuit operates as an averaging filter to generate a DC output proportional to the value of the rectified AC input; this value, in turn, is "tapped down" by R5 to a level equivalent to the input's rms value, which is the value displayed by the DMM.

Op amp A3 is simply a voltage follower that lowers the input-attenuator's source impedance to a value suitable to drive into A4. This impedance conversion helps eliminate some of the possible offset-voltage problems (the A4 input-offset-current source impedance IR drop, for example) and noise susceptibility problems as well. C1 blocks the DC offset voltage generated by A3.

A4 and A5 comprise the actual AC-to-DC converter; to see how it works refer to [Figure 2](#), and consider first its operation on the negative portion of an AC input signal. At the output of A4 are 2 diodes, D1 and D2, which act as switches. For a negative input to A4's inverting input, D1 turns on and clamps A4's output to 0.7V, while D2 opens, disconnecting A4's output from A5's summing point (the inverting input). A5 now operates as a simple inverter: R2 is its input resistor, R5 its feedback resistor, and its output is positive.

Now consider what happens during the positive portion of an AC input. A4's output swings negative, opening D1 and closing D2, and the op amp operates as an inverting unity-gain amplifier. Its input resistor is R1, its feedback resistor is R3, and its output now connects to A5's summing point through R4. D2 does not affect A4's accuracy because the diode is inside the feedback loop.

A positive input to A4 causes it to pull a current from A5's summing point through R4 and D2; the positive input also causes a current to be supplied to the A5 summing point through R2. Because A4 is a unity-gain inverter, the voltage drops across R2 and R4 are equal, but opposite in sign. Since the value of R2 is double that of R4, the net input current at A5's summing point is equal to, but opposite, the current through R2. A5 now operates as a summing inverter, and yields a positive output. (R6 functions simply to reduce output errors due to input offset currents.) Thus, the positive and negative portions of the DMM's AC voltage input both yield positive DC outputs from A5. With C2 connected across R5 as shown, the circuit becomes an averaging filter. As already mentioned, the tap on R5 is set so that the circuit's DC output is equivalent to the rms value of the DMM's AC voltage input, which is the value converted and displayed by the ADD3501.

DC Current Measurement

To make a DC current measurement, the user inserts the DMM's probes in series with the circuit current to be measured and selects a suitable scale. On any scale range, the DMM loads the measured circuit with a 2-V drop for a full-scale input. (This drop may be reduced to 200 mV; refer to the last section of this application report.) The ADD3501 simply converts and displays the voltage drop developed across the DMM's current-sensing resistor.

AC Current Measurement

AC current measurements are made in a way similar to DC current measurements. The DMM is switched to its AMPS and AC settings. The in-circuit current is again measured by a drop across the DMM's current-sensing resistor, but now the AC voltage developed across this resistor is processed by A3, A4, and A5, exactly as described for AC voltage measurements, before being transferred to the ADD3501. Again, the DMM displays an rms value appropriate for the AC signal current being measured.

Resistance Measurement

This DMM measures resistance in the same way as do most multimeters: it measures the voltage drop developed across the unknown resistance by forcing a known, constant-current through it. Suitable scale calibration translates the voltage drop to a resistance value.

The resistance measurement requires the generation of a constant-current source that is independent of changes in V_{CC} , using the 2V, ground-referenced reference voltage. The circuit of [Figure 3](#) accomplishes this.

In [Figure 3](#), A1 establishes a constant-current sink by forcing node A to V_{REF} , the voltage level at A1's non-inverting input. With node A held constant at V_{REF} (2.000V), current through R2 is also fixed, since Q1's collector current is determined by the αI_E product, thus establishing V1 as:

$$V1 = V_{CC} - \alpha(V_{REF}/R1)R2 \quad (1)$$

Note that V_{REF} is derived from the LM336, a precision voltage source. [Equation 1](#) shows that (all else remaining constant) V1 varies directly with changes in V_{CC} ; that is, V1 tracks V_{CC} . The A1/Q1 pair thus establishes a voltage across R2 that floats, independent of changes in the ground-referenced potentials (V_{CC} and V_{REF}) that define it. Now look at the A2/Q2 circuitry. The closed-loop operation of A2 tries to maintain a zero differential voltage between its input terminals. A2's non-inverting input is held at V1; thus, A2's inverting input is driven to V1. The current through RL (Q2's emitter current) is therefore $(V_{CC} - V1)R_L$. Since V1 tracks V_{CC} , then $(V_{CC} - V1)$, the voltage drop across R_L , is constant, thus producing I_{SOURCE} ([Figure 3](#)), the constant source current needed for the resistance measurement.

Note, that varying R_X will not affect I_{SOURCE} so long as the voltage drop across R_X is less than $(V1 - V_{BE2})$. Should V_{RX} exceed $(V1 - V_{BE2})$, Q2 would saturate, invalidating the measurement. The ADD3501 eliminates this worry, however, because as soon as the drop across R_X equals or exceeds the 2V full-scale input voltage the ADD3501 will display an OFL condition.

Finally, SW1 ([Figure 3](#)) is required as part of the VOLTS/AMPS/OHMS mode selection circuitry; in the VOLTS/AMPS position it prevents Q2's base-emitter junction pulling the V- supply to ground through A2.

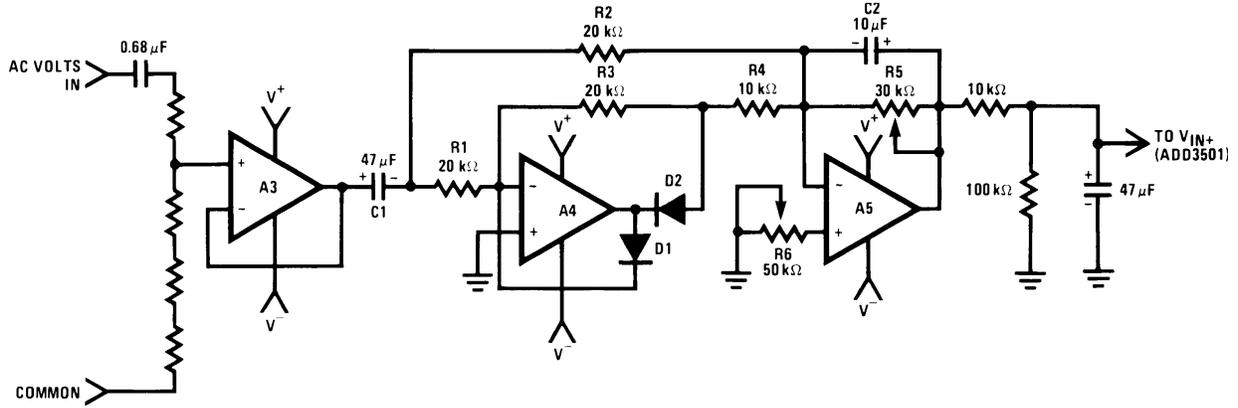


Figure 2. AC/DC Converter

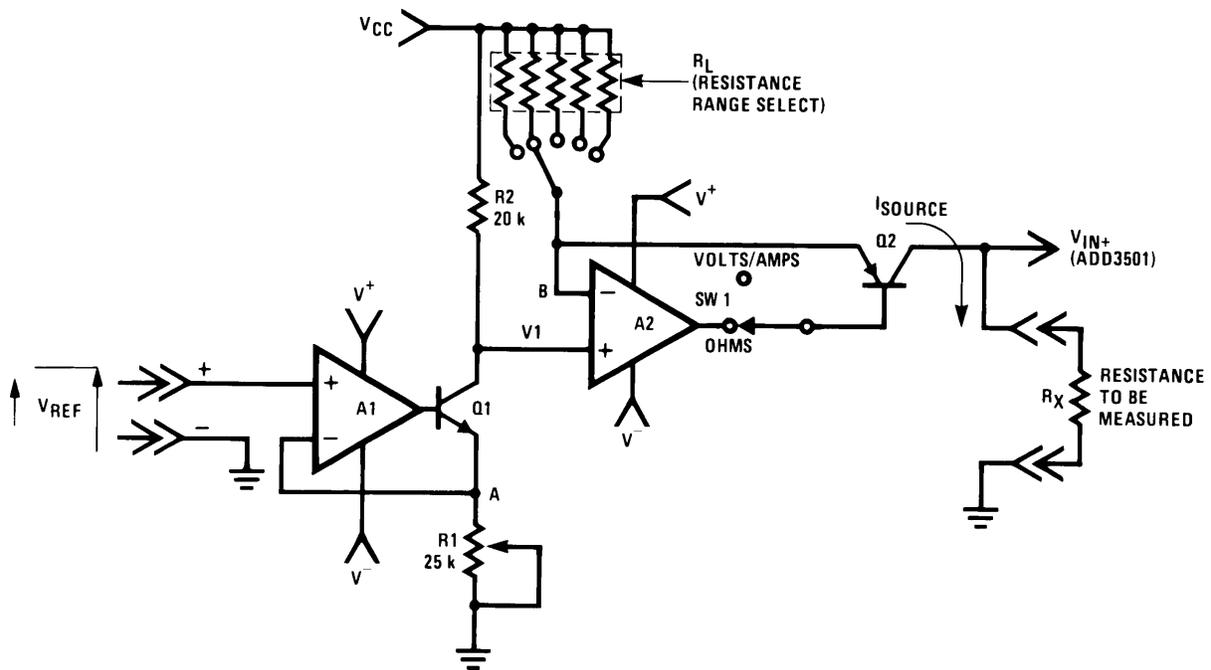


Figure 3. Constant-Current Source

Calibration

Calibrate the DMM according to the following sequence of operations:

1. Adjust P1 until the cathode voltage of the reference diode, LM336, equals 2.49 V. This reduces the diode's temperature coefficient to its minimum value.
2. DC Volts 2-V Range: Short the (+) and (-) probe inputs of the ADD3501 and adjust P2 until the display reads 0000.
3. DC Volts 2-V Range: Apply 1.995 volts across the (+) and (-) probe inputs and adjust P3 until the display reads 1.995.
4. Ohms 2-M Ω Range: Select a precision resistor with a value near full-scale or the 2-M Ω range, and adjust P4 until the appropriate value is displayed.
5. AC Volts 2V Range: Apply a known 1.995V_{rms} sinewave signal to the DMM and adjust.

PC Board Layout

It is imperative to have only one, single-point, analog signal ground connection for the entire system. In a multi-ground layout, the presence of ground-loop resistances will cause the op amps' offset currents and AC response to have a devastating effect on system gain, linearity, and display LSD flicker. Similar precautions must also be taken in the layout of the analog and high-switching-current (digital) paths of the ADD3501.

A Final Note

The digital multimeter described in this application report was developed with the goals of accuracy and low cost. For the high-end DMM market segments, however, improvements to the basic circuit of [Figure 1](#) are possible in the following areas:

1. Expand the VOLTS mode to include a 200 mV full-scale range.
2. Decrease the full-scale current-measurement loading voltage from 2V to 200 mV.
3. Provide a true-rms measurement capability.
4. Increase resolution by substituting the ADD3701 3 3/4-digit DVM chip, which is interchangeable and provides a maximum display count of 3.999.

The first two improvements involve a dividing down of the ADD3501 feedback loop by a ratio of 10:1, which reduces the 2 V full-scale input requirement to 200 mV. This not only allows a 200 mV signal between the ADD3501's V_{IN+} and V_{IN-} inputs to display a full-scale reading, but implies that the maximum voltage dropped across the current-measuring-mode resistance also will be 200 mV. Note, though, that the values of the current-measurement resistors must be scaled down by a factor of 10.

Additionally, a 200 mV full-scale input implies a resolution of 100 μ V/LSD. At such low input levels, the DMM may require some clever circuitry to eliminate the gain and linearity distortions that can arise from the offset currents in the AC-to-DC converter.

The third possible improvement, the reading of true-rms values, can be implemented by replacing the AC-to-DC converter of [Figure 2](#) with Texas Instruments LH0091, a true-rms-to-DC converter, and appropriate interface circuitry.

References

1. ADD3501 Data Sheet
2. *AN-20 An Applications Guide for Op Amps Application Report* ([SNOA621](#))
3. *LH0091 True RMS to DC Converter* ([SNOSB14](#))
4. ADD3701 Data Sheet
5. LM336 Data Sheet ([SNVS749](#))

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

This revision history highlights the technical changes made to the AN-202 Digital Multimeter document

AN 202 Revision History

REVISION	SEE	ADDITIONS/MODIFICATIONS/DELETIONS
B	Circuit Description	Added images -- Figure 1 , Figure 2 , and Figure 3
C		Updated formatting.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com