

# ***Stopping Reverse Current Flow in Standard Hot Swap Applications***

*Mike Hartshorne*

*SVA Infrastructure Power*

## **ABSTRACT**


This report provides a solution to stop reverse current flow in hot swap controller applications. The proposed circuit uses an inexpensive operational amplifier to sense the condition of the output voltage exceeding the input voltage, and subsequently disable the hot swap controller, stopping the flow of reverse current (current flow from the output (load) into the input (supply)). The device used for testing this method is the LM5069, configured to provide hot swap control of input voltages from 11V to 22V to a load capacitor of 220  $\mu$ F. A schematic of the solution and results are provided.

## **INTRODUCTION**

Hot Swap controllers have become popular choice for system protection at the front end of many power supplies. They help increase reliability by providing inrush current protection, over- and under-voltage control, current limit, and circuit breaker functionality. However, most hot swap controllers do not provide any protection from reverse current flow (current flow from the load to the input supply). Maintaining the charge stored on the load capacitance in the event of an input supply collapse or removal is critical in many applications, such as Solid State Drives (SSD). In these applications, reverse current flow results in unnecessary energy loss from the load capacitance. A diode can easily provide this function but consumes power during forward current flow. This paper offers a solution for the reverse current flow problem with the addition of a FET and a low-cost operation amplifier to the standard hot swap configuration.

## **BLOCKING REVERSE CURRENT WHEN THE HOT SWAP IS DISABLED**

Adding a single FET in series to the standard pass FET blocks reverse current flow when the gate of the pass FET is off. Figure 1 shows a standard hot swap circuit using the LM5069, with the addition of a reverse blocking FET (Q2) that is oriented with the source connected to the pass FET (Q1) source. The gates are tied together such that when the GATE pin is low, the pass FET stops current flow from the input to output and the blocking FET stops current flow from output to input.

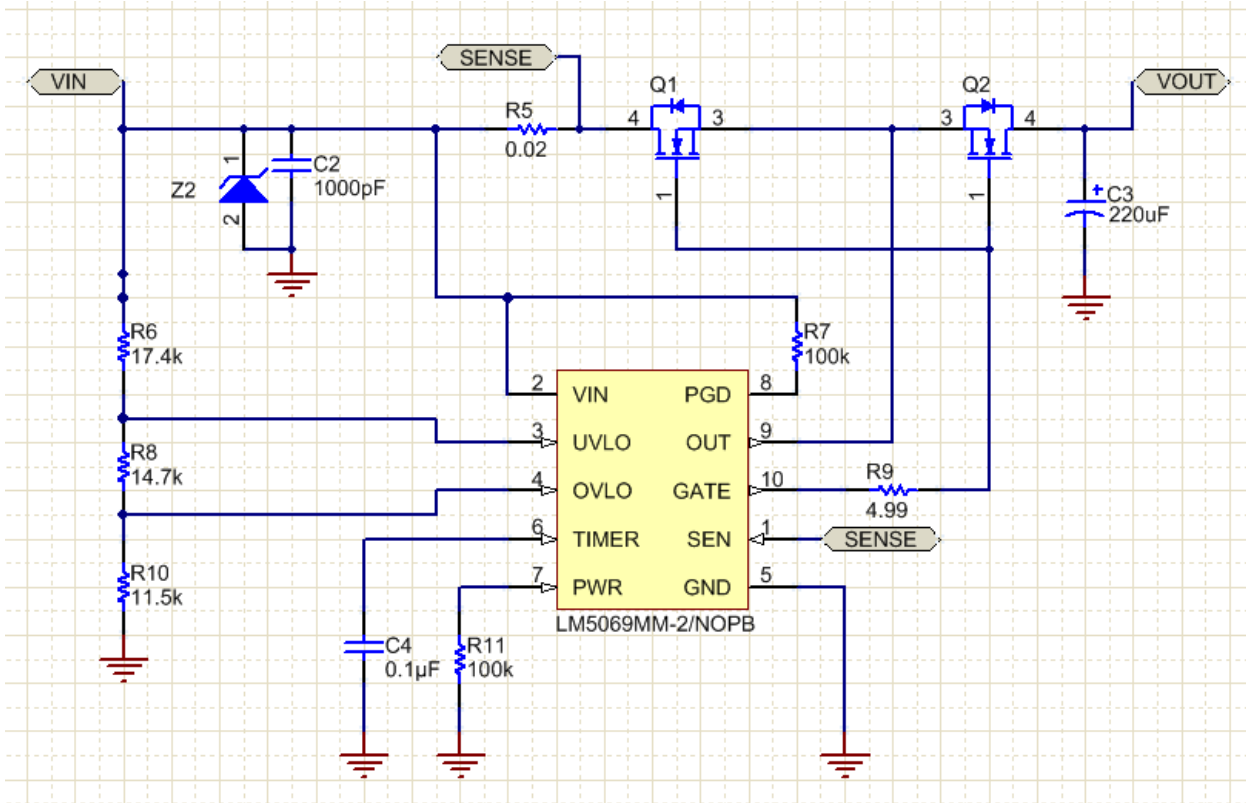

**Figure 1. Reverse Current Blocking with the LM5069 When Device is Disabled**


This addition can provide reverse current blocking in situations where the load can encounter positive voltages while the hot swap controller is in its insertion delay period, or if it has been shut off during a fault condition. The problem with this solution, though, is that once the gate is enabled, the hot swap controller does not react to a negative sense voltage. Therefore, if the input supply is lowered or removed, there is no mechanism to stop the flow of current from VOUT to VIN, and VOUT will track VIN until the hot swap controller's under-voltage threshold (UVLO) is crossed. Additionally, any external voltage impressed on the load can result in large current flow from the load to the input, limited only by the on-resistance of the pass FET, the sense resistance, and the internal impedance of the input supply.

## BLOCKING REVERSE CURRENT WHEN THE HOT SWAP IS ENABLED

Active reverse current protection can easily be incorporated into the standard hot swap configuration with the use of a low-cost operational amplifier, the additional FET, and a handful of passive components. The premise is simple: detect a negative voltage from the input to the output, and disable the hot swap such that the gate of both the pass FET and the blocking FET are low. This condition can be maintained until the output falls back down to the input voltage or the system is disabled. The circuit in Figure 2 provides this function: when VOUT goes 3.5 mV above VIN, the operational amplifier U1 will swing its output from the negative rail created by Z1 to the positive rail, or VIN. When this happens, the transistor connected to the UVLO and OVLO resistor network will shut off. This causes the UVLO voltage to fall to ground, and the LM5069 in turn shuts off the gates of the pass and blocking FETs. This shut down state is reversed when the output voltage decreases to equal the input voltage, at which point the output of U1 will go to the negative rail and enable the hot swap.





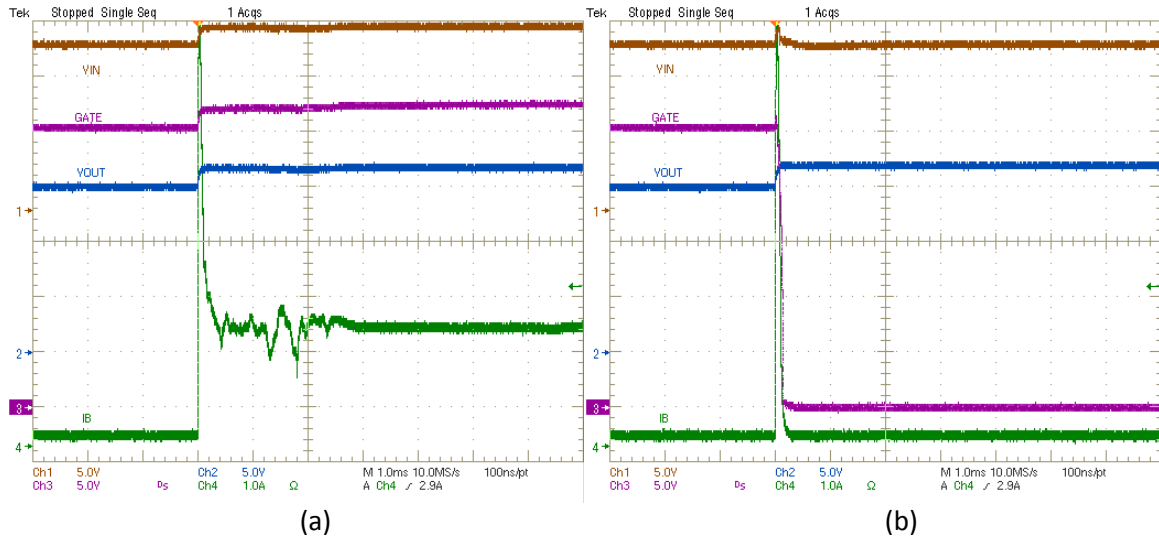

**Figure 4. Hot swap Gate Response with the Reverse Blocking Circuitry Disabled (a) and Enabled (b)**

## CONCLUSION

A simple, inexpensive circuit addition to the standard hot swap controller configuration has been proposed to add active reverse current blocking capability. This functionality can be useful in applications that already use a hot swap and cannot tolerate current flow from the output to the input. While the response to reverse current conditions is not as fast as what is possible with a stand-alone diode, it offers improved efficiency due to minimal voltage drop during forward current flow.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2012, Texas Instruments Incorporated