

AN-1806 LMV232 Evaluation Board

1 General Description

This board, the LMV232TLEVAL, can be used to evaluate the Texas Instruments LMV232 dual-channel mean square power detector. The LMV232 mean square power detector is particularly suited for accurate power measurement of RF modulated signals that exhibit large peak to average ratios, that is, large variations of the signal envelope. Such noise-like signals are encountered in applications such as CDMA and wideband CDMA cellphones.

2 Basic Operation

The LMV232 power detector provides an accurate power measurement for arbitrary input signals, low and high peak-to-average ratios and crest factors. This is because its operation is not based on peak detection, but on direct determination of the mean square value. The single supply, ranging from 2.5V to 3.3V, can be applied through connectors P₅ and P₆ of the evaluation board. The device has two digital interfaces. The signal connected to P₃ (SD) puts the device in an active mode or a shutdown mode. When SD = HIGH, the device is in shutdown, if SD = LOW the device is active. The signal connected to P₄ (BS) selects the active RF input signal. When BS = HIGH, RF_{IN1} is active (P₁). When BS = LOW, RF_{IN2} is active (P₂). The output voltage is measured through connector P₈. Connector P₇ can be used to monitor the voltage on the FB pin of the LMV232 when a 0Ω resistor is placed in R₂. Further details can be found in the Application Notes section of *LMV232 Dual-Channel Integrated Mean Square Power Detector for CDMA & WCDMA* ([SNWS017](#)).

The LMV232 conversion gain and bandwidth can be configured by a resistor and a capacitor. Resistor R₁ sets the conversion gain from RF_{IN} to the output voltage. A higher resistor value will result in a higher conversion gain. The maximum dynamic range is achieved when the resistor value is as high as possible, i.e. the output signal just doesn't clip and the voltage stays within the baseband ADC input range. The filter bandwidth is adjusted by capacitor C₄. The capacitor value should be chosen such that the response time of the device is fast enough and modulation on the RF input signal is not visible at the output (ripple suppression). The -3 dB filter bandwidth of the output filter is determined by the time constant R₁*C₄. Generally a capacitor value of 1.5 nF is a good choice.

3 Schematics

The schematic of the evaluation board is shown in [Figure 1](#).

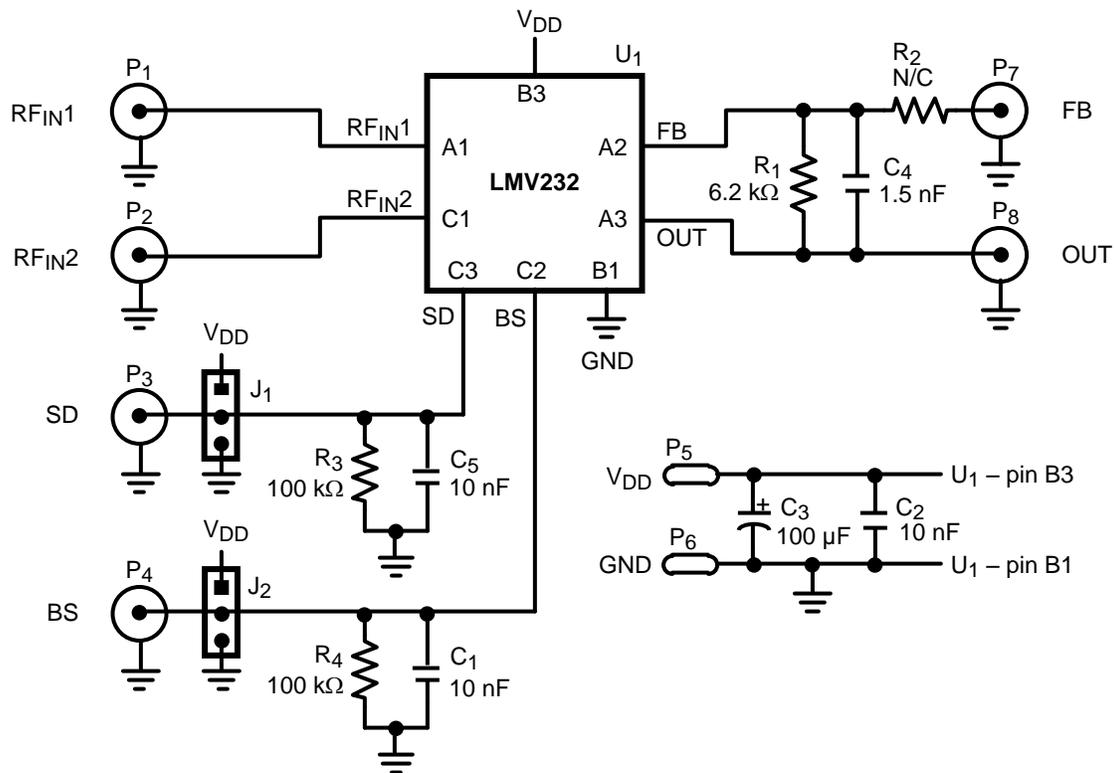


Figure 1. Schematic of the Evaluation Board

4 Bill of Materials

The bill of material (BOM) of the evaluation board is listed in [Table 1](#).

Table 1. Bill of Materials of the Evaluation Board

| Designator | Description | Comment |
|----------------|------------------|---------------|
| C1, C2, C5 | 0603 Capacitor | 10 nF |
| C3 | Case_C Capacitor | 100 μF |
| C4 | 0603 Capacitor | 1.5 nF |
| J1, J2 | Header 1 × 3 | For Jumper |
| P1, P2 | Connector | SMA |
| P3, P4, P7, P8 | Connector | BNC |
| P5, P6 | Connector | Banana |
| R1 | 0603 Resistor | 6.2 kΩ |
| R2 | 0603 Resistor | Not Connected |
| R3, R4 | 0603 Resistor | 100 kΩ |
| U1 | DSBGA | LMV232 |

5 Layout

The layout of the evaluation board is shown in [Figure 2](#).

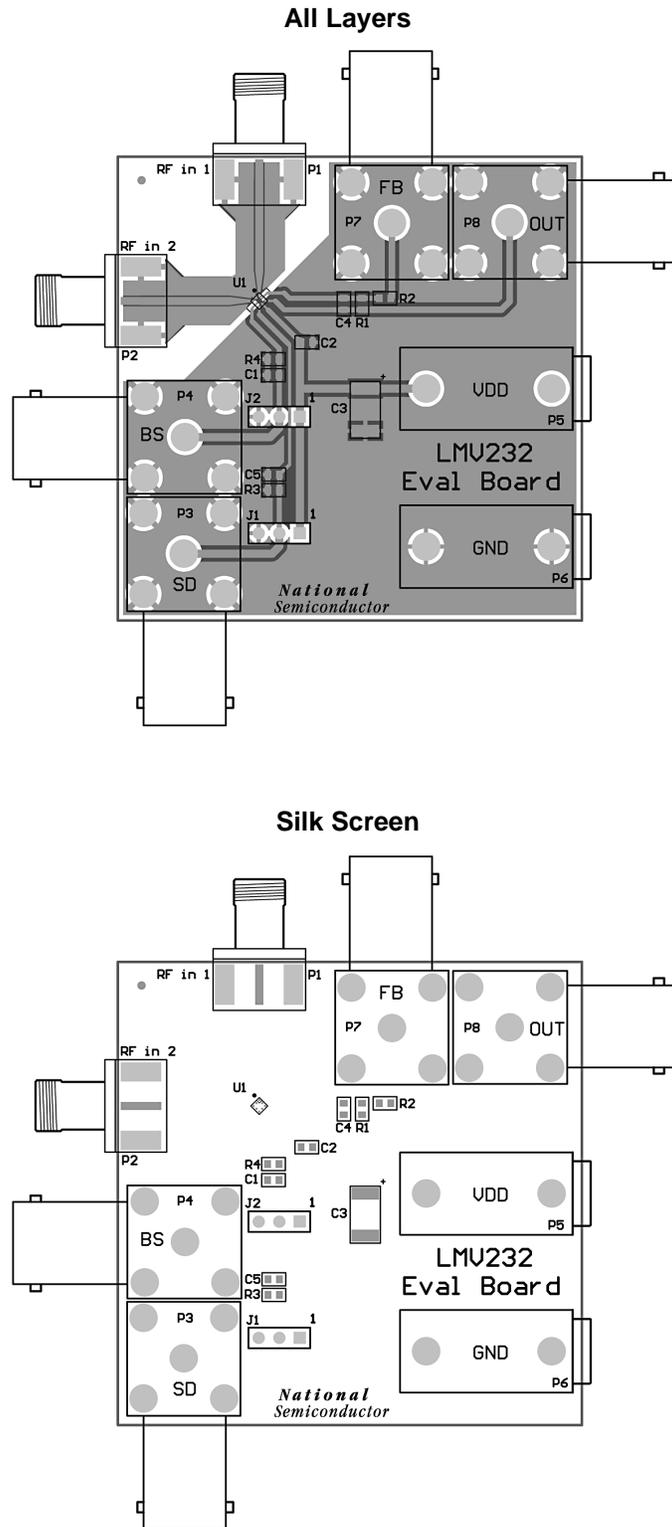


Figure 2. Layout of the Evaluation Board

6 Measurement Procedure

The performance of the LMV232 can be measured with the setup given in Figure 3.

In this measurement example a supply voltage of 2.7V is applied by the power supply. The LMV232 is set in active mode by connecting SD (P₃) to GND, while RF_{IN1} is selected by connecting BS (P₄) to 2.7V. Both RF_{IN2} (P₂) and FB (P₇) can be left unconnected. The resulting DC output voltage is measured with a multimeter connected to OUT (P₈).

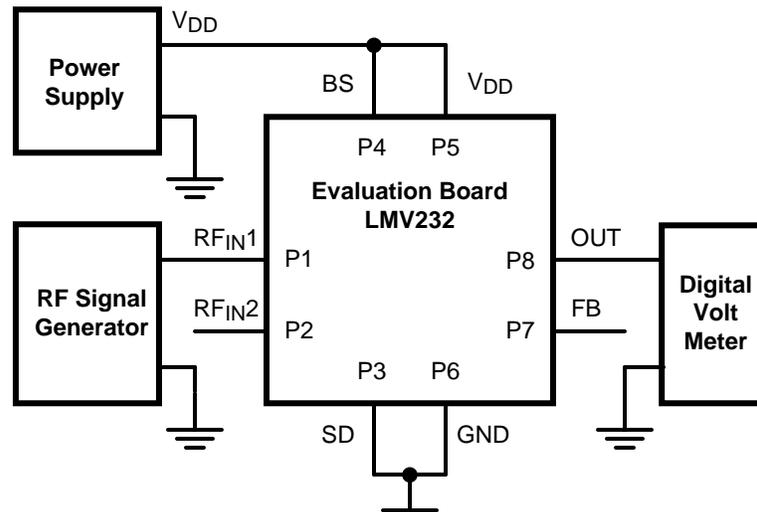


Figure 3. Measurement Setup

7 Measurement Results

Figure 4 and Figure 5 show the measurement results for the LMV232. The power is swept at 900 MHz for different temperatures (Figure 4). The resulting error with respect to an ideal fitted curve is shown in Figure 5.

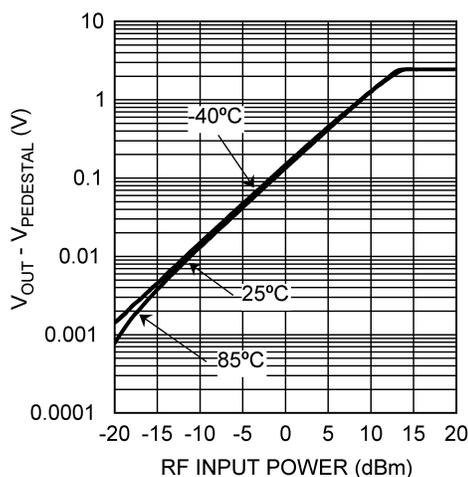


Figure 4. $V_{OUT} - V_{PEDESTAL}$ vs. RF Input Power at 900 MHz

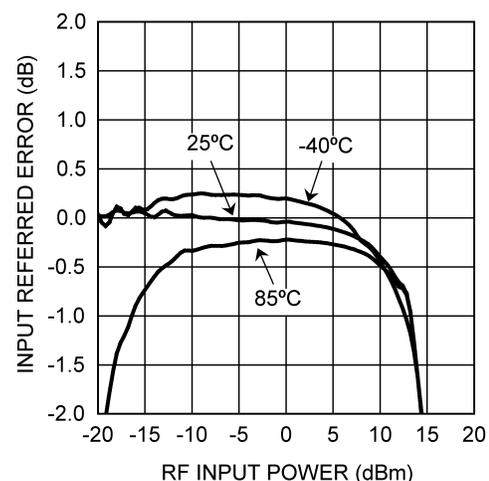


Figure 5. Input Referred Error vs. RF Input Power at 900 MHz

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

| | |
|------------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Applications Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Automotive and Transportation | www.ti.com/automotive |
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Video and Imaging | www.ti.com/video |

TI E2E Community

e2e.ti.com