

# Adapting Qi-compliant wireless-power solutions to low-power wearable products

By **Bill Johns**, *Senior Applications Engineer*  
**Kalyan Siddabattula**, *System Engineer*  
**Upal Sengupta**, *Applications & Marketing Manager*

## Introduction

A large number of low-power wearable devices such as smart watches, fitness wrist bands and headphones have been introduced to the market (Figure 1). This new family of electronic products is expected to grow and expand rapidly over the next few years. These devices are typically small and thin, with varying form factors and industrial design. Battery sizes might range from 100- to 300-mAh capacity, which determines the required charge rates.

The plug-and-jack style or micro-USB types of connectors have been the traditional way to charge such devices. But even these relatively small connectors are now too large for some of the new ultra-thin wearable applications. Connector contamination is an even greater problem due to the outdoor wearable environment.

Wireless charging is a solution to these problems and offers additional opportunities to designers. Existing semiconductor devices used for the Qi standard established by the Wireless Power Consortium (WPC) can be easily adapted for this lower-power application. The technology uses two planar coils to transfer power through a sealed case. For low-power wearable devices, a small, thin low-power receiver coil easily could fit into the back of the case or wristband area. Qi-compliant devices are a mature solution that can shorten development time, and the products are supported by the existing WPC infrastructure.

**Figure 1. Smart watch with wireless charging**




Used with permission from Secret Labs. LLC

## Qi-compliant wireless-power system

The typical wireless power system (Figure 2) has a receiver (Rx) in the portable device that provides energy to charge the battery. The transmitter (Tx) is located in a fixed base and is connected to a wall power supply. Input power to the transmitter is converted to AC, then magnetically coupled through the transmitter coil to the receiver coil when they are in close proximity. Output from the receiver is typically 5 V at up to 1 A, which provides input power to a battery charger IC inside the portable device.

**Figure 2. Block diagram of a Qi-compliant system**

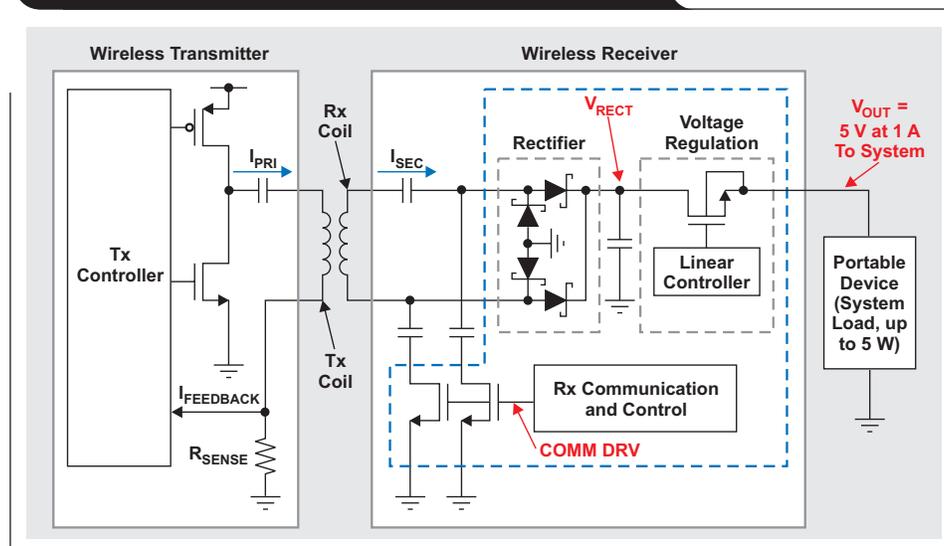

Transmitter operation in this system is controlled by the receiver chip using feedback in the form of digital communications packets sent back over the same magnetic coupling path. The Qi-compliant receiver communicates with the transmitter using load modulation to send information in data packets across the two coils. The transmitter-coil voltage and current are modulated at a 2-kHz rate that is decoded by the transmitter and used for control. The receiver can send several types of packets to the transmitter for control and information purposes. Also, a loss of communications terminates any power transfer.

The Qi-standard's *identification-and-configuration* command packets are very useful to assure that power is only transferred to the correct device, avoiding potentially hazardous situations. *Charge-complete* and *end-power-transfer* packets are also useful commands that stop power transfer when the battery is charged, or when other conditions require that power transfer be stopped.<sup>1</sup> These features assure safe power transfer between the transmitter and receiver using an existing, well-known standard.

## Low-power wireless systems

An available Qi-compliant receiver and transmitter can be optimized for a low-power wireless system by carefully tailoring the coil sizes and external component values to match the smaller application. Coils for both the transmitter and receiver can be reduced in size to fit the smaller form factor. Power-section components, in particular for the transmitter, can have reduced power specifications.

The typical WPC-1.1, Qi-compliant system supports up to 5-W output loads, typically 5 V at 1 A. A low-power system for a wearable-device application, on the other hand, might have output power in the range of 5 V at 100 to 250 mA.

Most Qi-compliant features can be used without impact on size or performance. Foreign-object detection (FOD) is an optional feature that protects against power transfer to stray metal objects in the charging area. In a low-power system with FOD, total output power is reduced by more than 50%. Along with reduced charging area, the possibility of introducing an object into the field that will heat up enough to present a problem is greatly reduced. The criticality of the FOD function may depend primarily on the mechanical design of the charging pad or charging cradle for a wearable device. Table 1 summarizes some of the key functions available when using the WPC-1.1 Qi standard

**Table 1. Qi-compliant standard versus wearable solution**

FEATURE	QI-COMPLIANT?	WEARABLE?
Identify Rx before power transfer	Yes	Yes
Stop power transfer on Rx command	Yes	Yes
Charge complete indications	Yes	Yes
Foreign object detection	Yes	Optional
Power transfer up to 5 W	Yes	Optional
Inter-operability with other devices	Yes	Optional

that may or may not be required in a customized wearable application.

## Low-power system coils

Coils can be reduced in size to a point, but must still transfer power and communicate with the transmitter. Typical coil construction is a round planar coil made of copper wire on a shield. Alternate configurations are PCB or flex-circuit coils. Typically, these alternates could have higher DC resistance (lower efficiency) but can be very thin, a desirable feature for small, low-power applications. The shield prevents AC fields from entering the electronics and battery, which also can improve coil performance.

Assuming that the Rx and Tx coils are aligned in the x-y plane, there are two key factors that determine the coupling factor,  $k$ . The first is coil-to-coil ( $z$ ) distance, and the second is the ratio of diameters of the two coils. The best coupling (highest  $k$ ) results when the coils are closer together and matched in diameter.<sup>2</sup> To ensure close x-y alignment from the start, the mechanical design of the charging base or cradle for a wearable device should include a physical means of aiding proper placement of the device in the cradle. Because the receiver coils are very small in this application, a slight misalignment between the Rx and Tx coils can result in a significant reduction in coupling factor and very poor power-transfer efficiency.

In a coupled-inductor system such as WPC/Qi, the coupling coefficient ( $k$ ) between the primary and secondary coil generally is in the range of 0.5 to 0.7. A typical transformer can have a much higher  $k$ , such as 0.99. When the coupling factor is low, a higher inductance value is required on the secondary (receiver) side to ensure that the output power demands can be met. As a result, small low-power devices that may have low coupling actually require a larger secondary inductance than the standard 5-W designs.<sup>3</sup> A higher-inductance receiver coil with more turns and larger shield may be needed to achieve the required voltage gain.

## Coil design

Design trade-offs of the receiver coil size include the wire diameter, shield size and thickness. Coil DC-resistance shows up as a reduction in receiver efficiency. The receiver coil design requires a specific number of turns to achieve the desired inductance. As previously noted, the required inductance of a small coil will be higher than a large coil due to a decrease in coupling factor. As the number of turns increases to achieve the higher inductance value in a smaller space, the wire diameter decreases. The combined effect of smaller wires and more turns will drive the DC-resistance higher and lower efficiency.

The shield provides a low-impedance path for the magnetic flux and increases coil inductance. Also the shield prevents the AC field from entering the battery and surrounding metal in the receiver. A larger and thicker shield is better because thinner shields run the risk of saturation in high-flux fields. Transmitter coil designs have fewer

physical restrictions. The coil can be larger and have lower inductance.

A typical coil used for standard 5-W WPC applications is the A11 coil type. This circular coil is approximately 50-mm in diameter and has a thick ferrite shield behind it. While this coil has been tested in a wide range of applications with many types of receivers, it works best for the higher power levels (3 to 5 W). For lower-power and reduced-range receivers, many coil dimensions can be reduced.

Typical inductance of the A11 coil is 6.3  $\mu$ H. This value should be maintained for best performance. Wire diameter can be reduced to allow a smaller coil size, however, this increases DC-resistance losses. Further size reduction can be achieved with a reduction in shield thickness. Several types of shields are available that provide good performance.

Tests with a 30-mm round transmitter coil have been conducted with good results (Figure 3). Smaller solutions are possible, but the designer must take care that the DC resistance is not increased significantly. In the case of the resonant-converter architecture used in most WPC transmitters, current flows in the primary coil even at minimal loads. To avoid excessive power loss, the DC resistance of the Tx coil must be as low as is practically possible, given the size constraints of the product.

### Low-power receiver

The bq51003 is one device in the TI bq51xxx family of wireless-power receivers that is adapted specifically for lower-power applications. The key change in the device is optimizing the behavior of a few features for lower output current.

This family of devices features Dynamic Rectifier Control™ to improve load-transient behavior. The Qi standard has a relatively slow global feedback loop and may require up to 100 ms to change the operating point. This means that a load-step can reduce output voltage and result in system resets. To provide enough voltage to operate though a transient, the  $V_{RECT}$  operating point is set high at low loads. This feature helps with load-step, but reduces light-load efficiency. To solve this problem, Dynamic Efficiency Scaling™ is used to tailor the light-load voltage to maximum output load. Maximum output current is set using a resistor.

**Table 2. Dynamic Rectifier Control for wireless receiver (bq51003)**

OUTPUT CURRENT PERCENTAGE	$R_{ILIM} = 1116 \Omega$ $I_{MAX} = 250 \text{ mA}$	$R_{ILIM} = 488 \Omega$ $I_{MAX} = 500 \text{ mA}$	$V_{RECT}$
0 to 10%	0 to 25 mA	0 to 50 mA	7.08 V
10 to 20%	25 to 50 mA	50 to 100 mA	6.28 V
20 to 40%	50 to 100 mA	100 to 200 mA	5.53 V
>40%	>100 mA	>200 mA	5.11 V


Due to the reduced PCB area for power dissipation, thermal paths also should be taken into consideration. Since the typical application requires charging a small battery with reduced charge current, power dissipation can be managed.

**Figure 3. Standard transceiver coil and 30-mm, low-power coil**





Figure 5. Low-power transmitter

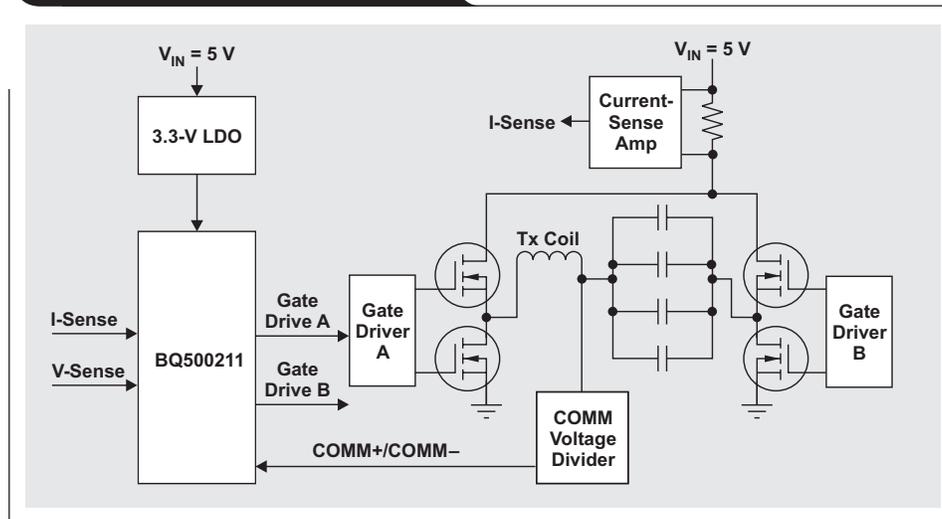

USB port or small adapter. This works very well with low-power receivers with low current demand. A block diagram example is shown in Figure 5. Input current is sensed across a resistor and amplified through a current-sense amplifier. The power section uses power-stage MOSFETS with integrated drivers. But independent drivers and low-loss MOSFETS could be used to reduce cost. As discussed earlier, at lower output power, FOD protection may be optional; the circuit shown does not have the FOD feature implemented. Also, for simplicity and cost reduction, the design in Figure 5 does not show the optional circuitry for low-power standby mode. Reference 4 has more information about this design.

## Conclusion

Implementing wireless inductive charging in a low-power, wearable design is possible now using existing off-the-shelf devices. Among the key factors to design a working solution in the 500- to 1500-mW power range is optimization of the magnetic components—specifically, matching the smaller-size receiver coils to correspondingly smaller transmitter coils to maintain the best coupling factor. Also important is implementation of appropriate external circuit modifications with the bq500211 transmitter and bq51003 low-power receiver to minimize system power losses.

## References

1. Bill Johns, "An Introduction to the Wireless Power Consortium standard and TI's compliant solutions," *Analog Applications Journal* (1Q 2011). Available: [www.ti.com/2q14-slyt401](http://www.ti.com/2q14-slyt401)
2. E. Waffenschmidt and Toine Staring, "Limitation of inductive power transfer for consumer applications," *13th European Conference on Power Electronics and Applications (EPE2009)*, Barcelona, Spain, 8-10 Sept 2009, paper #0607.
3. Bill Johns, Tony Antonacci and Kalyan Siddabattula. "Designing a Qi-compliant receiver coil for wireless power systems," *Analog Applications Journal* (3Q 2012). Available: [www.ti.com/2q14-slyt479](http://www.ti.com/2q14-slyt479)
4. Bill Johns, "Low Power Transmitter Reference Design, bq500211," Reference Design (April 2014). Available: [www.ti.com/2q14-slua705](http://www.ti.com/2q14-slua705)

## Related Web sites

Wireless power products:

[www.ti.com/2q14-wireless](http://www.ti.com/2q14-wireless)

[www.ti.com/2q14-bq51003](http://www.ti.com/2q14-bq51003)

[www.ti.com/2q14-bq500211](http://www.ti.com/2q14-bq500211)

[www.ti.com/2q14-bq24232](http://www.ti.com/2q14-bq24232)

Subscribe to the AAJ:

[www.ti.com/subscribe-aaj](http://www.ti.com/subscribe-aaj)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

**Americas** Phone +1(512) 434-1560

**Brazil** Phone 0800-891-2616

**Mexico** Phone 0800-670-7544

Fax +1(972) 927-6377  
Internet/Email [support.ti.com/sc/pic/americas.htm](http://support.ti.com/sc/pic/americas.htm)

### Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS  
(00800 275 83927)  
International +49 (0) 8161 80 2121  
Russian Support +7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +(49) (0) 8161 80 2045  
Internet [www.ti.com/asktexas](http://www.ti.com/asktexas)  
Direct Email [asktexas@ti.com](mailto:asktexas@ti.com)

### Japan

Fax International +81-3-3344-5317  
Domestic 0120-81-0036  
Internet/Email International [support.ti.com/sc/pic/japan.htm](http://support.ti.com/sc/pic/japan.htm)  
Domestic [www.tij.co.jp/pic](http://www.tij.co.jp/pic)

### Asia

Phone Toll-Free Number

**Note:** Toll-free numbers may not support mobile and IP phones.

Australia 1-800-999-084  
China 800-820-8682  
Hong Kong 800-96-5941  
India 000-800-100-8888  
Indonesia 001-803-8861-1006  
Korea 080-551-2804  
Malaysia 1-800-80-3973  
New Zealand 800-446-934  
Philippines 1-800-765-7404  
Singapore 800-886-1028  
Taiwan 0800-006800  
Thailand 001-800-886-0010

International +86-21-23073444  
Fax +86-21-23073686  
Email [tiasia@ti.com](mailto:tiasia@ti.com) or [ti-china@ti.com](mailto:ti-china@ti.com)  
Internet [support.ti.com/sc/pic/asia.htm](http://support.ti.com/sc/pic/asia.htm)

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A021014**

Dynamic Efficiency Scaling, Dynamic Rectifier Control, E2E and OMAP are trademarks and DLP is a registered trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)