

# EXTERNAL SYNCHRONIZATION OF THE DCP01/02, DCR01/02, AND DCV01 SERIES OF DC/DC CONVERTERS

By D. McIlroy

The DCP01/02, DCR01/02, and DCV01 (referred to only as the *DCP01, 02* in this document) are a family of miniature DC/DC converters providing both step-up and step-down voltage conversions within the 1W and 2W power range. These converters are approved to UL1950 and are available in through-hole and surface-mount packages.

The DCP01, 02s have the facility to be synchronized to an external frequency. This has the benefit of eliminating beat frequencies caused by two or more devices operating at frequencies that are close to one another. Additionally, with all the DCP01, 02s operating at the same frequency, any EMC emissions generated will have a similar spectral density, making it easier to design circuits with high EMC immunity.

There are several methods that can be used to externally synchronize the DCP01, 02 family. The following describes how to interface external circuits to the DCP01, 02, and how to derive a clock pulse for synchronization.

## CIRCUIT DESCRIPTION

Each DCP01, 02 has an onboard oscillator that runs at a nominal 800kHz. The internal oscillator operates by charging an internal timing capacitor from a constant current of 75μA. This voltage appears on the SYNC<sub>IN</sub> pin in the form of a ramp. When the ramp exceeds the upper threshold, the internal discharge circuit discharges the capacitor to the lower threshold and the process repeats, as shown in Figure 1.

The oscillator frequency is divided by 2 before being used to drive the power stages. Both the internal oscillator and the

 


FIGURE 1. Internal Oscillator Timing.

divide by 2 circuits are controlled from comparator outputs with a lower input threshold value of 0.4V and an upper input threshold of 2.1V, as shown in Figure 2.

The internal oscillator may be overridden by the application of an external signal that exceeds the comparator thresholds. Typically, the signal should be 0.3V to 2.5V with a maximum peak voltage of 3.0V, and with a frequency between 720kHz to 880kHz.

## EXTERNAL INTERFACE CIRCUITS

Two methods can be deployed in interfacing external circuitry to the DCP01, 02. Either a signal may be applied to ensure that the internal circuits operate in phase with the external signal, thus synchronizing all the devices to a common frequency, or the internal oscillator may be disregarded by driving from an external source.

 


FIGURE 2. Internal Oscillator Circuit.

## SYNCHRONIZATION USING AN EMITTER-FOLLOWER CIRCUIT

Synchronization can be achieved by the injection of a positive pulse into the SYNC<sub>IN</sub> pin during a charge cycle, thus rapidly charging the internal capacitor. This forces the SYNC<sub>IN</sub> pin above the upper threshold and initiates a discharge cycle. By injecting this pulse simultaneously onto the SYNC<sub>IN</sub> pins of all other DCP01, 02s, they will also synchronize to this external frequency.

Figure 3 shows an emitter-follower configured for operation from a +5V power supply to give a 3.0Vpk signal output capable of driving eight DCP01, 02 devices.

 


FIGURE 3. DCP01 Series, Emitter-Follower Interface.

The peak output voltage is set by the resistor ratio,  $R_3:R_4$ , less the forward voltage drop,  $V_{BE}$ , of the transistor,  $Q_2$ .

$$\text{Output Voltage} = V_{CC} \cdot R_4 / (R_3 + R_4) - 0.6$$

where  $V_{CC} = 5$  in the above example.

The driving signal,  $V_{IN}$ , is fed to transistor  $Q_1$ , which is used to switch off transistor  $Q_2$ , allowing the DCP01, 02 to run freely in the charge cycle. Before completion of the charge cycle,  $V_{IN}$  goes low, switching off  $Q_1$ . Consequently  $Q_2$  is turned on rapidly, charging the internal timing capacitor. The internal discharge cycle is delayed until  $Q_2$  is turned off. When the discharge cycle is complete, a charge cycle is initiated automatically.

The choice of  $Q_1$  will depend upon the available driving source; however, most readily available logic levels can be accommodated by careful choice of values for  $R_1$  and  $R_2$ .  $Q_1$  can be replaced with a FET with an appropriate gate threshold voltage. Caution must be exercised to ensure that  $Q_1$  is not driven into heavy saturation, necessitating a long recovery time, as this would prevent the circuit from running. Likewise, a FET with a low capacitance should be chosen if being driven from a high impedance source. Capacitor  $C_1$  is provided for power-supply filtering.

The duty cycle of the driving signal is not critical. A value within the range of 20% to 60% will ensure correct operation, as shown in Figure 4.

 


FIGURE 4. Emitter Follower Output Waveform  $V_S$  and  $V_{IN}$ .

**Important Note:** The frequency of the internal oscillator depends on the internal capacitor. This signal has a value of approximately 34pF at the SYNC<sub>IN</sub> pin. Therefore, using an oscilloscope probe to monitor this signal places additional capacitance in parallel with the internal capacitance, and reduces the frequency of oscillation. If it is required to view the waveform at this point, a low capacitance probe must be used (i.e., x100), and caution must be exercised to ensure that the frequency is not taken outside operational limits. Otherwise, damage to the device may occur.

The frequency of the internal oscillator can be measured accurately on the DCP01s by monitoring the SYNC<sub>OUT</sub> pin and multiplying the frequency obtained by 2. This method ensures that the oscillator circuit is not loaded.

## INTERFACING THE DCP01, 02 SERIES USING HCMOS LOGIC

The ready availability and flexible operating supply voltage of the standard 74HCMOS logic family provide a suitable interface to the DCP01, 02 series. If a 3.0V supply is available, the HCMOS logic family can be powered directly. Otherwise, the supply will have to be regulated.

The digital output of the HCMOS is used to force the SYNC<sub>IN</sub> pin high by charging the internal timing capacitor at a faster rate than internal constant current, thereby reaching the upper threshold more rapidly. The internal discharge cycle is initiated, but prevented from discharging the internal capacitor until the HCMOS logic output is low, whereby the internal discharge circuit and the HCMOS logic discharge the internal capacitor together. Although a charge cycle is initiated internally, the voltage is held low until the HCMOS logic goes high again. Therefore, the DCP01, 02 oscillator is overridden by the external logic signal, as shown in Figure 5.

 


FIGURE 5. 74HC245 O/P Drive Waveform.

The maximum load presented to the HCMOS device is the charging ramp current of  $75\mu\text{A}$ , as seen by the HCMOS device when its output is low, and the discharge current of  $1.5\text{mA}$  (maximum) when the HCMOS device is still trying to hold its output high.

The choice of the 74HC245 (an octal bus transceiver) ensures that there is sufficient current output to drive a total of three DCP01, 02  $\text{SYNC}_{\text{IN}}$  pins connected in parallel from each 74HC245 output, giving a total capability of synchronizing 24 DCP01, 02 devices, as shown in Figure 6.

If  $V_{\text{IN}}$  is incapable of driving all eight inputs simultaneously, one input can be driven from  $V_{\text{IN}}$  and its output used to drive the remaining inputs. Capacitor  $C_1$  is for power-supply filtering, and  $V_{\text{CC}}$  is  $3.0\text{V}$ .

 


FIGURE 6. DCP01 Series HCMOS Interface.

## GENERATION OF A SYNCHRONIZATION CLOCK SIGNAL

In the absence of a suitable clock signal to synchronize the DCP01, 02 devices, a clock signal can be derived from one of the DCP01, 02 devices. This presents a master-slave situation, whereby all the slave devices are locked onto the frequency of the master device.

The  $\text{SYNC}_{\text{IN}}$  pin of the master device is used to drive a comparator whose reference is set to approximately  $1\text{V}$  (midpoint of the waveform). A pulse train is then obtained from the comparator that can be used to drive the HCMOS driver. The comparator must exhibit a low-input capacitance, as this is connected directly in parallel with the internal timing capacitor of approximately  $34\text{pF}$ . The frequency of oscillation is lowered, approximately, by the ratio of external to internal capacitance, (i.e.,  $3.3\text{pF}$  will produce approximately 10% reduction in oscillator frequency). An input capacitance of  $1\text{pF}$  to  $2\text{pF}$  is ideal. The response time of the comparator must be small enough not to affect the operation of the circuit; ideally, less than  $100\text{ns}$ . The use of a single-supply comparator will give a unipolar output, making it easier to interface with the HCMOS devices.

Figure 7 shows an application using a comparator to derive a synchronizing clock pulse capable of driving a single input to the 74HC245, one of the outputs being used to drive all the other inputs.

With a supply voltage of  $5.0\text{V}$ , the comparator reference is set to a nominal  $1\text{V}$ , with  $C_3$  acting as a bypass filter. Resistors  $R_3$  and  $R_4$  provide  $0.1\text{V}$  of hysteresis (this is necessary, as the charging ramp is changing relatively slowly). If the DCP01, 02 is being operated over the specified range of input supply voltages, this will have a direct effect on the comparator reference voltage. This may be overcome by using a semiconductor voltage reference in place of  $R_2$ .

 


FIGURE 7. Comparator Generated Timing Pulses.

The split supplies are used to provide 5V for the comparator, and 3V for the 74HC245. This allows the HCMOS output to be connected directly to the DCP01, 02 devices.  $R_5$  is provided to limit the current from the comparator to the HCMOS part, when its output is greater than 3V.

The circuit was evaluated using a Linear Technology (LT1016) comparator whose input capacitance was given as 3.5pF. This value, plus an allowance of 3.5pF (measured with an LCR bridge) for the tracking, gives a total additional capacitance of 7pF.

In order to accommodate the additional capacitance, a bleed resistor,  $R_B$ , has been added. The current through this resistor should be sufficient to compensate for the additional capacitance, thereby making it transparent to the internal oscillator circuit (see "Connecting a Bleed Resistor to the SYNC<sub>IN</sub> Pin").

The voltage across the resistor is taken as the nominal, or supply voltage minus half the peak ramp voltage.

With  $R_B$  equal to 270k $\Omega$ , the circuit was tested using the DCP01 series with the SYNC<sub>OUT</sub> pin monitored before and after the comparator circuit was added. The change in the frequency of the output signal was less than +3%.

The output waveform of the comparator switched from a low of 0.3V to a high of 4V. The output from the 74HC245 switched from 0V to 3.0V with a load of 3 SYNC<sub>IN</sub> pins, as shown in Figure 8.

Capacitors  $C_1$  and  $C_2$  are power-supply decoupling capacitors.

 


FIGURE 8. Comparator-Generated Timing Pulses.

### GENERATING A CLOCK SIGNAL FROM A CRYSTAL

See Figure 9 for an alternative circuit for generating a clock signal. U1 is an Intersil HA7210 crystal driver circuit capable of being driven by a wide range of crystal frequencies. U2 is a standard HCMOS decade counter from which the carry-out pin has been used, as this gives an equal mark-to-space ratio. The crystal frequency is 8.0MHz. Therefore, the drive to the 74HC245 is 800kHz. This output is capable of driving all 8 inputs of the 74HC245 simultaneously.

 


FIGURE 9. Crystal-Generated Clock Signal.

## CONNECTING A BLEED RESISTOR TO THE SYNC<sub>IN</sub> PIN

The effects of additional capacitance loading on the SYNC<sub>IN</sub> pin can be nulled by the addition of a bleed resistor. This is connected between V<sub>IN</sub> and SYNC<sub>IN</sub>, and its purpose is to supply additional charging current to accommodate the extra capacitance connected in parallel with the internal timing capacitor, therefore, making the additional capacitance transparent to the oscillator, as shown in Figure 10. C<sub>EXTRA</sub> represents the additional capacitance due to tracking, etc.

With no additional capacitance connected, the voltage on the SYNC<sub>IN</sub> pin is changing at a rate of:

$$\begin{aligned} \text{Oscillator} \Rightarrow \frac{dv}{dt} &= \frac{\text{Constant Charge Current}}{\text{Internal Capacitance}} \\ &= \frac{75 \cdot 10^{-6}}{34 \cdot 10^{-12}} \\ &= 2.2\text{V}/\mu\text{s} \end{aligned}$$

Nominal charge time = 1.1μs gives a peak voltage of approximately 2.4V.

To maintain this rate with the additional capacitance, the charging current has to be increased. This is now made up of the constant current plus the bleed resistor current, I<sub>B</sub>:

$$\text{Oscillator Ramp} = \frac{\text{Charge Current} + \text{Bleed Current}}{\text{Total Capacitance}}$$

Or rearranging to give:

$$\begin{aligned} \text{Bleed Current} &= (\text{Oscillator Ramp} \cdot \text{Total Capacitance}) - \text{Charge Current} \\ &= (2.2 \cdot 10^6 \cdot 41 \cdot 10^{-12}) - 75 \cdot 10^{-6} = 15.2\mu\text{A} \end{aligned}$$

$$\text{Bleed Resistor} = \frac{\text{Nominal Voltage } R_B}{\text{Bleed Current}} = \frac{5 - 1.2}{15.2\mu\text{A}} = 250\text{k}\Omega$$

The above gives a good guide to the value of the bleed resistor; however, because PCB layouts vary considerably, a value of resistor may be found empirically using the above as a starting point.

The maximum value of additional capacitance using the bleed method is 10pF, as this gives rise to a non-linear ramp due to the varying voltage across the bleed resistor (this decreases as the capacitor charges).

## CIRCUIT CHOICE

Each circuit has its own merits and the correct solution will ultimately depend upon the specific application; however, a brief comparison can be made between the circuits.

### Emitter Follower (Figure 3)

Advantages: low cost; can accept a wide variation of supply voltages; able to drive many channels.

Disadvantages: requires a logic signal at 800kHz for synchronization.

### HCMOS Interface (Figure 6)

Advantages: low-cost, single-chip solution with capability of driving up to 24 DCP01, 02s.

Disadvantages: requires a low-voltage supply, and a logic signal at 800kHz for synchronization.

### Comparator Derived Clock Signal (Figure 7)

Advantages: self-generated clock from single DCP01, 02 for synchronization to other DCP01, 02s.

Disadvantages: requires fast comparator.

### Crystal Generated Clock Signal (Figure 9)

Advantages: crystal-controlled clock frequency, low-component count, and capability of driving up to 24 DCP01, 02s.

Disadvantages: requires low-voltage supply.

## REMOTELY CONTROLLING THE DCP01, 02

The output from the DCP01, 02 may be remotely controlled by pulling the SYNC<sub>IN</sub> pin LOW. This halts the internal oscillator by preventing the internal capacitor from charging. The watchdog detects the stopped oscillator and tri-states the driver transistors, shutting down the DCP01, 02; this pin must not be taken HIGH in order to stop the oscillator.

When the SYNC<sub>IN</sub> pin is released, the oscillator runs freely and can re-establish the output voltage.

 


FIGURE 10. Connecting a Bleed Resistor.

One simple method of implementing the above is to use an open drain or collector transistor configuration, as shown in Figure 11. With the transistor always connected to the SYNC<sub>IN</sub> pin, it must have a very low capacitance to minimize the effect on the oscillator.

Transistor Q<sub>1</sub> is an Infineon BFR180 whose combined capacitance on the collector is less than 1pF (collector-to-base plus collector-to-emitter). When tested, this reduced the frequency of the internal oscillator by approximately 5kHz.

It should be noted that the collector was connected to the SYNC<sub>IN</sub> pin as close as physically possible. Even a short length of PCB trace would have affected the oscillator more than the transistor. Resistors R<sub>1</sub> and R<sub>2</sub> are 22kΩ each. This allows the DCP01, 02 to be controlled from +5V (shutdown) and 0V signal.

Q<sub>1</sub> was replaced by Infineon transistor BRS17P. This device has a higher capacitance (approximately 2.5pF) and subsequently the frequency of the oscillator fell by 20kHz. A bleed resistor of 1MΩ (R<sub>B</sub>) was fitted and the frequency of the oscillator was measured at approximately 5kHz higher than the unloaded oscillator frequency.

In the above tests the oscillator frequency was monitored at the SYNC<sub>OUT</sub> pin on the DCP01, as this presents no loading to the oscillator. The frequency at this point is half that of the internal oscillator.

## CIRCUIT LAYOUT CONSIDERATIONS

Careful consideration should be given to the track layout of the DCP01, 02 series, and in particular the 5V input version, due to the presence of high switching currents. Ideally, ground and power planes should be used on the input side. If this is not possible, then the input supply and ground must be connected in a star formation. Otherwise, large start up currents may cause the input voltage to fall below the minimum input voltage specification, and the DCP01, 02 may not operate. A 2.2μF low-ESR ceramic capacitor connected across the input voltage and mounted close to the device will ensure start up on full load over the specified input voltage range. The output voltage ripple will depend on the load, the value of filter capacitor, and its value of ESR. A minimum value of 1μF is recommended.

When using the SYNC<sub>IN</sub> pin to generate a synchronizing clock pulse, it is important to note that the internal timing capacitor is 34pF and is highly susceptible to stray capacitance at the SYNC<sub>IN</sub> pin, which will reduce the oscillator frequency. Therefore, the tracking from the SYNC<sub>IN</sub> pin to the comparator must be kept as short as possible. Avoiding any tracks on adjacent layers within this area will ensure a minimum capacitance (including ground and power planes).

It should be observed that connecting an oscilloscope probe to the SYNC<sub>IN</sub> pin places a relatively large capacitance in parallel with the internal timing capacitor, consequently decreasing the frequency of oscillation. If the oscillator frequency is substantially reduced, damage may result to the device. Therefore, a low-capacitance oscilloscope probe must always be used (x100).

 


FIGURE 11. External Control of the DCP01, 02.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated