

# Class-D Output Snubber Design Guide

The design for a class-D audio system sometimes requires a snubber circuit on the output. This design guide includes what a snubber circuit does and how to design one if needed.

## Contents

1	What Is an Output Snubber? .....	1
2	System-Level Impact of Ringing and Overshoot .....	1
3	Designing an Output Snubber.....	1

## List of Figures

1	One-Half of the Typical H-Bridge Output Stage With Snubbers.....	2
---	--	---

## 1 What Is an Output Snubber?

An output snubber is an RC network placed at the output of a switching audio amplifier. The snubber dampens any ringing or overshoot on the PWM output waveform. The stray inductance in the IC leads, IC bond wires, and PCB traces causes the overshoot and ringing. Having an output snubber provides a low-impedance drainage path to ground for the energy stored in these inductances. Without a provided path, the stored current finds a path through parasitic capacitance on the PCB and causes the overshoot and ringing.


## 2 System-Level Impact of Ringing and Overshoot

Overshoot can stress the output MOSFETs of a class-D device by overvoltage. The overshoot and ringing are also potential sources of EMI. The snubber also improves the total harmonic distortion (THD) of the amplifier. The overshoot and ringing at the output are present in the feedback signal to the amplifier. The amplifier must then try to eliminate this overshoot and ringing from the signal. The amplifier cannot completely remove this signal, which is then present on the output as distortion.

## 3 Designing an Output Snubber

To design the proper output snubber, measure the voltage spike at the output pin. Use Section 4 in *Voltage Spike Measurement Technique and Specification*, [SLEA025](#), as a reference in performing this measurement.

**Figure 1** shows the basic output circuit. Inclusion of a bypass capacitor,  $C_{(BYPASS)}$ , is necessary in the design because it is part of the current path for snubbing the inductance of the high-side FET. The terminals of  $C_{(BYPASS)}$  must be close to the power pins and the ground pins of the IC.  $R_{(x)}$  and  $C_{(x)}$  should be close to the output pin and the ground pins of the IC. This is necessary to reduce the series inductance of the PCB traces. **Figure 1** has labels of *High-side FET current-loop* and *Low-side FET current-loop* for the current loops formed by  $R_{(x)}$  and  $C_{(x)}$ . If  $R_{(x)}$  and  $C_{(x)}$  are not present, the current stored in the drain, source, and lead inductances has no place to sink during dead time. This current then flows through parasitic capacitances on the PCB and appears on the waveform as ringing. Good control of the high-side and low-side current loops is necessary for good protection from overvoltage spikes and for good EMI results.

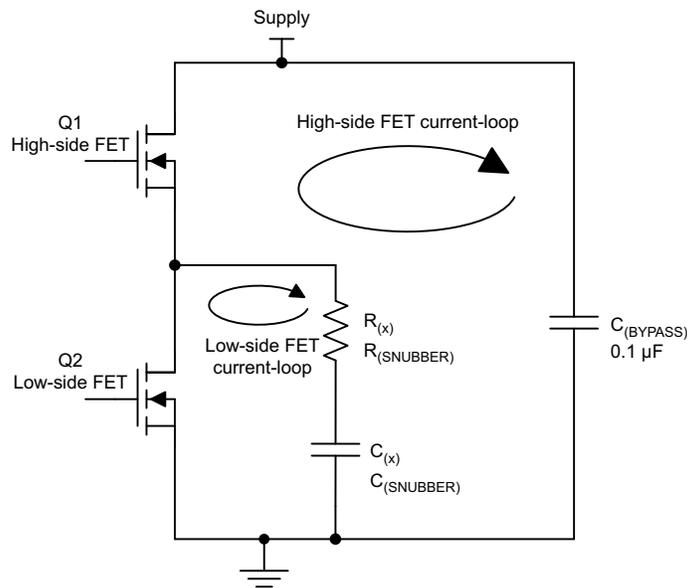

**Figure 1. One-Half of the Typical H-Bridge Output Stage With Snubbers**

For  $R_{(x)}$  start with a value of  $10\ \Omega$  and use a surface-mounted device (SMD) to keep the series inductance (ESL) low. For  $C_{(x)}$  select a small value of  $470\ \text{pF}$  to  $1000\ \text{pF}$ , and also an SMD. Use the techniques listed in [SLEA025](#) to measure the spike and the associated ringing. Measure the frequency of the ringing. If there is no ringing, use a higher value resistor for  $R_{(x)}$  or a smaller capacitor for  $C_{(x)}$ . The final  $C_{(x)}$  should be labeled as  $C_{(1)}$  and the ringing frequency is  $f_{(1)}$ .

Change  $C_{(x)}$  to a value that is about 1.5 to 2 times the previous value. Keep  $R_{(x)}$  the same. Again, measure the frequency of the ringing on the waveform. If no ringing is available to measure, change  $C_{(x)}$  to a slightly smaller value. Label the value of  $C_{(x)}$  as  $C_{(2)}$  and the ringing frequency as  $f_{(2)}$ .

Use [Equation 1](#) to calculate the value for  $L$ .

$$L = \left[ \frac{1}{(C_{(2)} - C_{(1)}) \times 4 \times \pi^2} \right] \left[ \frac{1}{f_{(2)}^2} - \frac{1}{f_{(1)}^2} \right] \quad (1)$$

where  $L$  is the value of the stray inductance that requires snubbing.

$L$  is a bulk inductance and is not any individual inductance.

Find the appropriate values of  $C_{(x)}$  and  $R_{(x)}$ . Use [Equation 2](#) to calculate the appropriate  $R_{(x)}$ .

$$R_{(x)} = 2 \times \pi \times f_{(x)} \times L \quad (2)$$

The ringing frequency  $f_{(x)}$  is for a given  $C_{(x)}$ . If the application is to use  $C_{(1)}$  for the snubber capacitor then use  $f_{(1)}$  in the equation to calculate the proper  $R_{(x)}$  (or use  $C_{(2)}$  and  $f_{(2)}$ ).

To account for tolerances and differences in production units, use a value that is 0.7 to 0.8 of the calculated  $R_{(x)}$ . Too high a value for  $R_{(x)}$  could allow for a spike, but too low a value for  $R_{(x)}$  could cause the snubber to draw excessive current and overheat. Use [Equation 3](#) to calculate the power loss in the resistor.

$$P = C_{(x)} \times V^2 \times f_{(S)} \quad (3)$$

where:

- $V$  is the supply voltage
- $f_{(S)}$  is the switching frequency

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)