

C2000™ Dual Sync Buck/Boost Converters

Vieri Xue/Liwin Shu

Contents

| | | |
|----------|---|-----------|
| 1 | Basics | 3 |
| 2 | MCU Solution for Multiconverters | 4 |
| | 2.1 C2000 Piccolo A MCU Overview | 4 |
| | 2.2 C2000 MCU Solution | 4 |
| 3 | Hardware Design | 5 |
| | 3.1 Power Stage | 5 |
| | 3.2 Auxiliary Power Supply | 5 |
| | 3.3 Detection Circuits | 5 |
| | 3.4 MCU Functions | 6 |
| | 3.5 PCB Layout Design | 6 |
| 4 | Firmware Design | 6 |
| | 4.1 Firmware Tasks | 6 |
| | 4.2 The Status Machine | 8 |
| | 4.3 The Key and LED Specification | 9 |
| | 4.4 The Interrupt Service Routine | 9 |
| | 4.5 The Algorithms | 10 |
| | 4.5.1 The Voltage Mode | 10 |
| | 4.5.2 The Average Current Mode | 11 |
| | 4.5.3 Peak Current Mode | 12 |
| 5 | How the System Works | 13 |
| | 5.1 System On | 13 |
| | 5.2 Control Mode | 13 |
| | 5.3 Power Dissipations | 14 |
| | 5.4 System Off | 15 |
| 6 | Measurements | 15 |
| | 6.1 Startup Waveform | 15 |
| | 6.2 Transient Load | 16 |
| | 6.3 Output Ripple Voltage | 17 |
| 7 | Fault Management | 18 |
| 8 | References | 18 |

Figures

Figure 1. Buck and Boost Converter..... 3
 Figure 2. Block Diagram of Dual Sync Buck/Boost Converters 4
 Figure 3. PCB Layout Design 6
 Figure 4. Background Structure..... 7
 Figure 5. Status Machine Flow Chart 8
 Figure 6. The ISR Flow Chart..... 10
 Figure 7. Voltage Mode Control Block Diagram 10
 Figure 8. Current Mode Block Diagram..... 11
 Figure 9. Control Block Diagram 12
 Figure 10. Block Diagram of the Implementation..... 13
 Figure 11. Startup Waveforms 15
 Figure 12. Buck 1 Transient Load 16
 Figure 13. Buck 2 Transient Load 16
 Figure 14. Boost 1 Transient Load..... 17
 Figure 15. Boost 2 Transient Load..... 17
 Figure 16. Output Ripple Voltage 18

Tables

Table 1. Comparison of Some Methods 3
 Table 2. Some Pinouts of This Solution 5
 Table 3. Key Definition 9
 Table 4. LED Flashing Specification..... 9

1 Basics

Buck/Boost is a very normal topology in current power supply equipment.

Buck and Boost are very similar topologies. They have two MOSFETs and diodes and one power inductor. But the I/O ports are symmetrical.

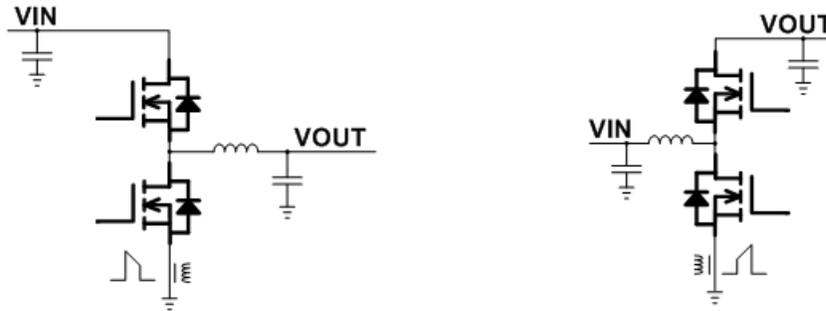


Figure 1. Buck and Boost Converter

Usually, we used a special analog controller to control the power stage before. Unfortunately, this analog controller can do very limited tasks. When this power supply is placed in a large system, it might be required to report some running information, or it might be controlled by the upper machine. A digital controller can fulfill all complex tasks and satisfy all kinds of requirements.

Table 1. Comparison of Some Methods

| | | Advantages | Disadvantages |
|-----------------------|---------------------|--|---|
| Analog versus Digital | Analog Control | Widely used before | Special part for application Difficult to optimize |
| | Digital Control | Good platform for all kinds of topologies Less external components SCI/PMBUS interface | Need software engineer Need 3.3-V auxiliary power |
| Nonsync versus Sync | Nonsync Rect. | Less expensive | Lower efficiency under heavy load |
| | Sync Rect. | Higher efficiency and lower temperature rise, higher output ability | Expensive |
| Current Sensing | Current transformer | Higher efficiency | Cannot sample dc signal |
| | Shunt Resistor | Can sample ac or dc signal | Lower efficiency Need an expensive amplifier. |

2 MCU Solution for Multiconverters

In this application note, we will show how to control a synchronous buck/boost converter and how one C2000 microcontroller unit (MCU) can handle multichannel buck/boost converters.

2.1 C2000 Piccolo A MCU Overview

The features of the C2000 Piccolo A MCU are:

- High-efficiency 32-bit CPU of 60 MIPS
- Low cost of device and system
- Enhanced pulse width modulator (ePWM) module
- High-resolution PWM (HRPWM) module
- Enhanced capture (eCAP) module
- Analog-to-digital converter (ADC); up to 13 channels and 4.6 MSPS
- On-chip temperature sensor
- Comparator supports all peripheral interrupts
- Independent 16-bit timer in each ePWM module

2.2 C2000 MCU Solution

Figure 2 shows the block diagram of the dual sync buck/boost converters.

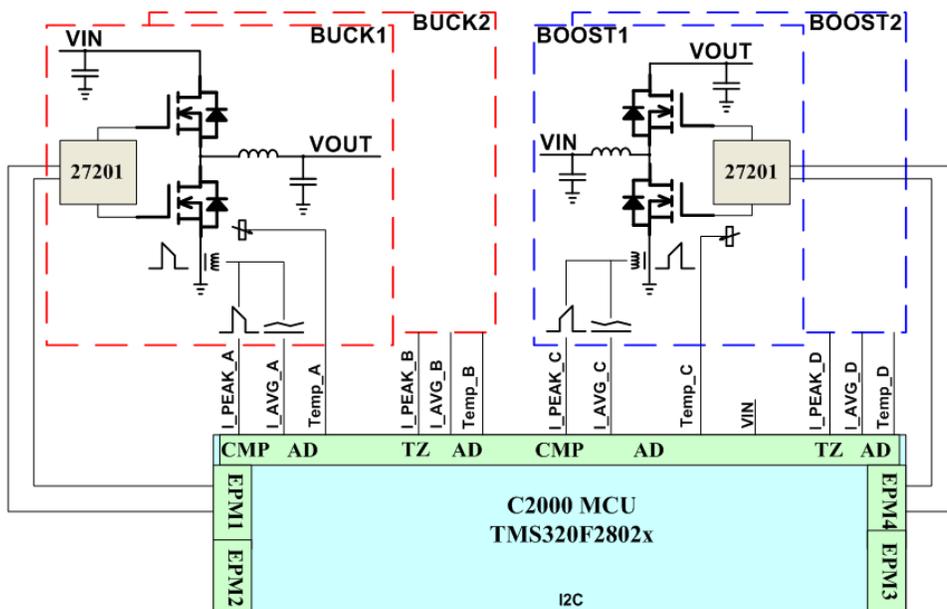


Figure 2. Block Diagram of Dual Sync Buck/Boost Converters

In our solution, we use the powerful ADC/comparator/calculation functions of C2000 Piccolo A MCU to control dual sync buck/boost converters.

3 Hardware Design

3.1 Power Stage

The power stage is standard buck/boost circuit, which would be compatible between a synchronous rectifier and a nonsynchronous rectifier.

3.2 Auxiliary Power Supply

The auxiliary power supply is connected to an input port and supplies +12 V or +3.3 V power for MOSFET drivers and MCU and other ICs.

3.3 Detection Circuits

The most important feedback is the current signal which sends the MCU an image of the current flowing through the upper and lower MOSFET. This signal is used to monitor the current amplitude and the average value, and to protect the converter from OCP damage.

Table 2. Some Pinouts of This Solution

| PORT | ADC/CMP | PORT NAME | Function |
|------|-----------|-----------|-----------------------------------|
| A0 | ADC | VAO | Buck1 output voltage sampling |
| A1 | ADC | IAAD | Buck1 output current sampling |
| A2 | CMP | IACMP | Buck1 peak current protection |
| A3 | ADC | TEMPA | Buck1 and 2 temperature sampling |
| A4 | CMP | ICOMP | Boost1 peak current protection |
| A6 | ADC | ICAD | Boost1 output current sampling |
| A7 | ADC | VCO | Boost1 output voltage sampling |
| | | | |
| B1 | ADC | IBAD | Buck2 output current sampling |
| B2 | ADC | VBO | Buck2 output voltage sampling |
| B3 | ADC | IDAD | Boost2 output current sampling |
| B4 | ADC | VDO | Boost2 output voltage sampling |
| B6 | ADC | TEMPD | Boost1 and 2 temperature sampling |
| B7 | ADC | VIN_R | Input voltage sampling |
| | | | |
| TZ1 | Trip zone | TZB | Buck2 peak current protection |
| TZ2 | Trip zone | TZD | Boost2 peak current protection |

3.4 MCU Functions

The C2000 MCU samples the I/O voltage and current value with a 4.6-MSPS high-speed ADC converter and quickly calculates the duty ratio of each converter with 60 MIPS high-speed calculation unit and then sends out PWM signals to control all four channel converters.

PWMH (HRPWM) is for the main switch, and PWML is for the auxiliary switch.

3.5 PCB Layout Design

The four converters, shown in Figure 3, have the same 24-V input power supply.

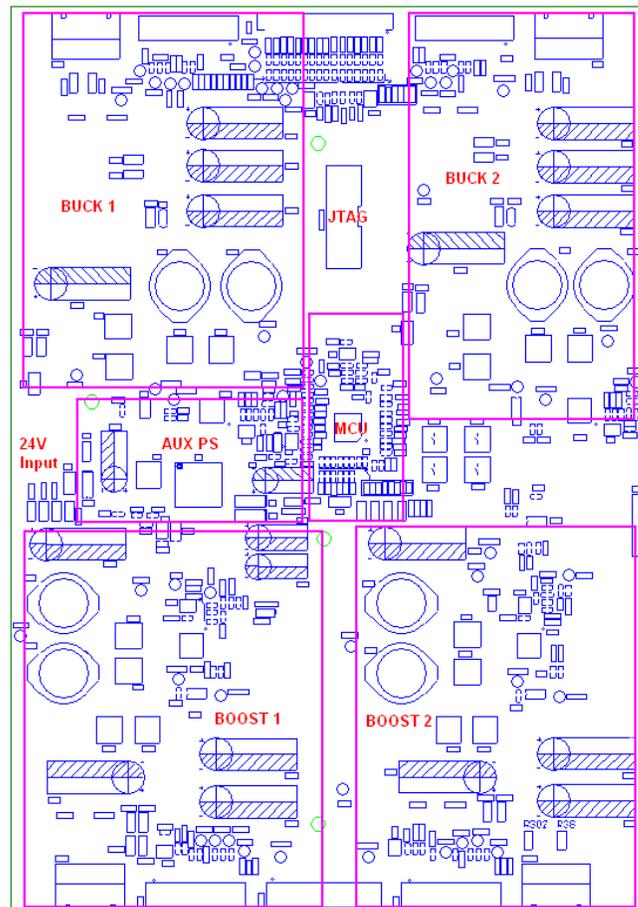


Figure 3. PCB Layout Design

4 Firmware Design

4.1 Firmware Tasks

The entire firmware system is a forward-background system. Figure 4 shows the background structure.

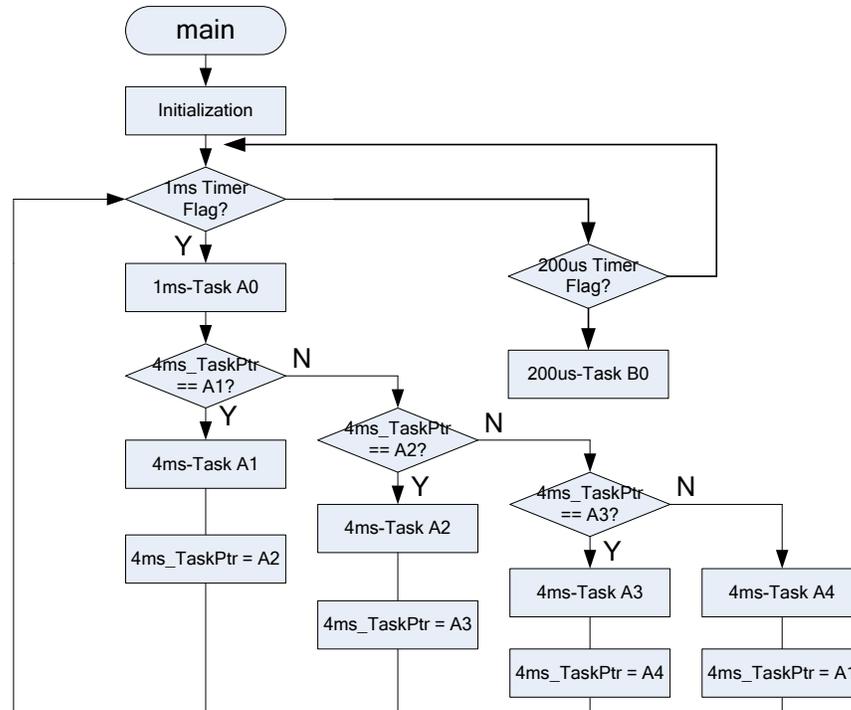


Figure 4. Background Structure

- **200 μ s – Task B0:** The 200- μ s task deals with the protection.
- **1ms – Task A0:** The 1-ms periodical task. The soft-start process is performed in this task.
- **4ms – Task A1:** The task deals with the status machine of the system.
- **4ms – Task A2:** The task deals with the ADC calibration in the power on stage, and it also execute the SFO function periodically, which is used by the HRPWM module.
- **4ms – Task A3:** The task detects the key operation, finishes the auto-restart detection, and sends the command.
- **4ms – Task A4:** The task detects the input voltage range. When the input voltage is out of range, it generates a fault status.

4.2 The Status Machine

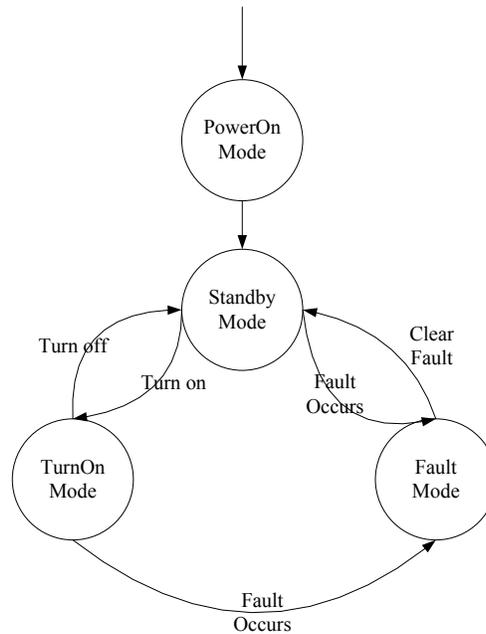


Figure 5. Status Machine Flow Chart

There are four running modes in this system:

- Power-on
- Standby
- Turn-on
- Fault

When the power is on, the MCU starts to work. First, it gets into power-on mode. In this mode, the system deals with the initializations. When the initialization is finished, the system goes automatically to standby mode.

In standby mode, the system responds to a command only when the user presses the appropriate key. When a turn-on command exists, the corresponding buck or boost converter turns on its PWM, and soft-starts the reference voltage, after which the system enters turn-on mode.

In turn-on mode, only some of the converters may be working. If a converter is not working, the converter also can be turned on by the user. If one of the converters contains a fault, the fault status of that converter is recorded while the remaining converters continue to run.

When all the converters have faults, the system goes to fault mode, and all the PWMs turn off. Fault mode can be cleared by powering on again or by pressing and holding any key for more than 1 second. When the fault is cleared, the system returns to standby mode.

4.3 The Key and LED Specification

There are four user keys on the board. Table 3 summarizes the key functions.

Table 3. Key Definition

| | SW1 | SW2 | SW3 | SW4 |
|--------|-------------|-------------|-------------|-------------|
| BUCK1 | Turn ON/OFF | X | X | X |
| BUCK2 | X | Turn ON/OFF | X | X |
| Boost1 | X | X | Turn ON/OFF | X |
| Boost2 | X | X | X | Turn ON/OFF |

When the system is in fault mode, pressing and holding any key for more than 1 second clears the fault.

If there is an LED in this system, the LED flashes follow the rules defined in Table 4.

Table 4. LED Flashing Specification

| | Power On Mode | Standby Mode | Turn On Mode | Fault Mode |
|---------------|----------------------|------------------------------|-------------------------------|-------------------|
| LED1 flashing | Always OFF | Flashing in every 0.6 second | Flashing in every 1.2 seconds | Always ON |

4.4 The Interrupt Service Routine

All the algorithms execute in the interrupt service routine (ISR), which is triggered by the EOS of the ADC. In the MCU initialization, the ADC sampling is triggered in every three switching cycles. To handle the four converters, the ISR must execute the different calculation task in a specified time slot.

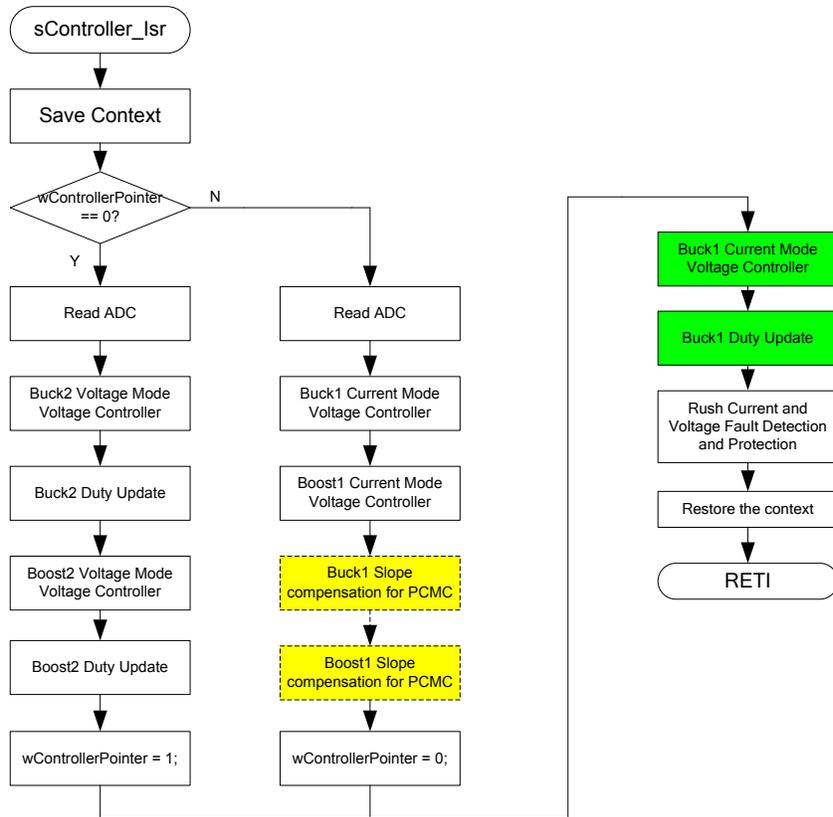


Figure 6. The ISR Flow Chart

The ISR is divided into two time slots: the first interrupt deals with the voltage mode controller calculation and the second interrupt deals with the current mode voltage loop. The duty cycle is updated in every interrupt.

4.5 The Algorithms

4.5.1 The Voltage Mode

Voltage mode control controls the output voltage by a single output voltage loop, and the controller simply regulates the duty cycle in different running conditions. For example, consider the buck topology (see Figure 7 for the voltage mode closed-loop block diagram).

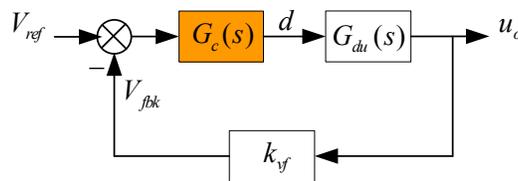


Figure 7. Voltage Mode Control Block Diagram

Equation (1) shows the open-loop transfer function:

$$G_{open} = G_c(s)G_{du}(s)k_{vf} \quad (1)$$

$G_c(s)$ is the closed-loop controller, and k_{vf} is the voltage sampling ratio.

From Equation (1), we can see that $G_{du}(s)$ has a low-frequency pole that greatly affects the frequency response of the system by slowing down the bandwidth and reducing the phase margin. To reduce the effect of this pole, we need a zero to offset the pole.

Therefore, it is better to choose a controller as shown in Equation (2):

$$G_c(s) = \frac{K(s+a)(s+b)}{s(s+c)} \quad (2)$$

$a = \frac{1}{RC}$ is an offset zero to the pole of $G_{du}(s)$.

b is a high-frequency zero to compensate the phase, and c is a high-frequency pole to reduce the high-frequency noise. Besides, we need an integral element to reduce the static difference of the controller.

For the detail controller design, see the reference documentation in Section 8, *References*.

4.5.2 The Average Current Mode

Current mode control means to regulate the output voltage by internal current loop and an external voltage loop controller. The inductor current and the output voltage are controllable in an external voltage loop controller. Figure 8 shows the current mode control block diagram.

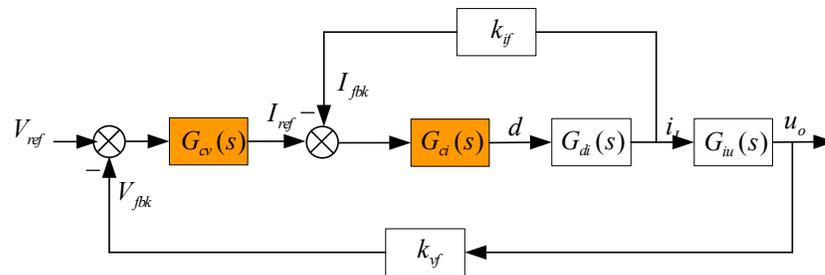


Figure 8. Current Mode Block Diagram

When designing the multiloop system, the most important factor is the design of the current loop controller for the system. Also, the internal loop must be designed first. From Figure 8, we can get the internal open-loop transfer function is:

$$G_{open_i} = G_{ci}(s)G_{di}(s)k_{if} \quad (3)$$

The internal loop object is the transfer function from the duty cycle to the inductor current $G_{di}(s)$. From the preceding analysis, this object is integral. To regulate this kind of object, the PI controller can be used.

Equation (4) reflects a PI controller that adds a high-frequency pole, which can reduce the high-frequency noise of the system.

$$G_{ci}(s) = \frac{K(s + b)}{s(s + a)} \tag{4}$$

If the design of the internal loop is fast enough, the internal loop of the system can be considered as a gain, so the external loop object is similar to the integral, and the PI controller can be used for the external loop.

$$G_{cv}(s) = \frac{K(s + b)}{s(s + a)} \tag{5}$$

To ensure the stability of the system, the internal loop must be much faster than the external loop. Therefore, it is necessary to choose the proper bandwidth for both current loop and voltage loop. In the 300-kHz switching frequency application, a 60-MHz MCU cannot execute a 1-cycle controller algorithm because the CPU speed is not fast enough to finish the calculation for the controller in 3.3 μ s. In addition, the sampling delay in the closed loop, which greatly reduces the phase margin of the system, cannot be neglected. So, we must reduce the sampling rate and the controller execution rate to reduce the CPU load and the effect of the sampling delay.

For the detail design for the controller, see the reference documentation in Section 8, *References*.

4.5.3 Peak Current Mode

The control block diagram of the peak current control is nearly the same as the block diagram of the average current control mode. The difference is that the internal comparator does the internal loop of the peak current mode.

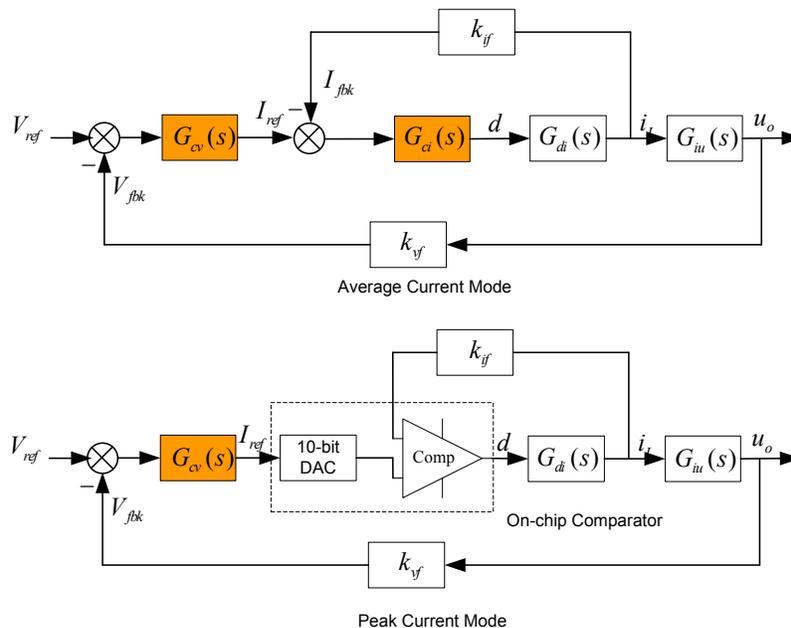


Figure 9. Control Block Diagram

For the peak current mode control, as with average current mode, only a voltage loop controller must be designed.

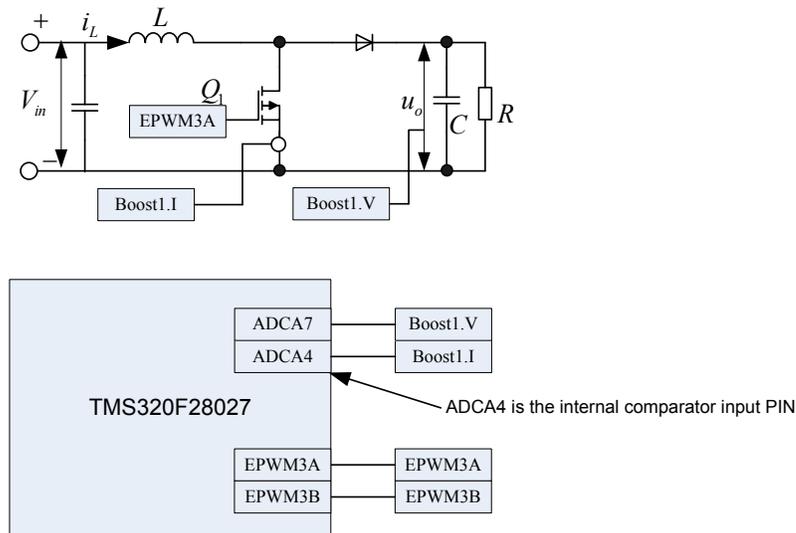


Figure 10. Block Diagram of the Implementation

Using the Piccolo A MCU as the main controller, the EPWM3A is the PWM output pin and the IGBT current is sampled as the inductor current. Also, the output voltage is sampled to design the voltage loop.

In peak current mode, software only needs to calculate the voltage loop, after which the reference current is determined. The reference current is written to the internal 10-bit DAC to let the comparator finish the current loop process. At the same time, the RAMP ratio must be updated when the reference current is changed.

The voltage loop and the slope compensation are executed every three switching cycles in the ISR.

5 How the System Works

5.1 System On

The converter is turned on by pressing the respective ON/OFF button.

5.2 Control Mode

To show the performance of our demo, the four converters run in different modes.

- Buck 1 is in average voltage mode.
- Buck 2 is in average current mode.
- Boost 1 is in peak current mode.

- Boost 2 is in average current mode.

5.3 Power Dissipations

Buck converter is an example.

The calculation for power loss in the lower MOSFET is simple, because virtually all of the loss in the lower MOSFET is due to current conducted through the channel resistance ($R_{ds(on)}$).

$$P_{low_on} = I_{out}^2 \times R_{ds(on)} \times (1 - D) \quad (6)$$

In Equation 6, I_{out} is the average output current and D is the duty cycle (V_{out}/V_{in}).

An additional term can be added to the loss equation of the lower MOSFET to account for additional loss accrued during the dead time when inductor current is flowing through the body diode of the lower MOSFET. This term is dependent on the diode forward voltage (V_d) and the switching frequency, F_s , and the length of dead times.

$$P_{low_off} = \frac{1}{6} \times V_d \times I_{out} \times F_s \times (t_{d1} + t_{d2}) \quad (7)$$

In addition to $R_{ds(on)}$ losses, a large portion of the upper MOSFET losses are due to currents conducted across the input voltage (V_{in}) during switching. Because a substantially higher portion of the upper MOSFET losses are dependent on switching frequency, the power calculation is more complex.

$$P_{up_on} = I_{out}^2 \times R_{ds(on)} \times D \quad (8)$$

When the upper MOSFET turns off, the lower MOSFET does not conduct any portion of the inductor current until the voltage at the phase node falls below ground. Once the lower MOSFET begins conducting, the current in the upper MOSFET falls to zero as the current in the lower MOSFET ramps up to assume the full inductor current. At turn on, the upper MOSFET begins to conduct and this transition occurs over a time, t_2 . The approximate power loss is P_{up_off} .

$$P_{up_off} = \frac{1}{6} \times V_{in} \times I_{out} \times F_s \times (t_1 + t_2) \quad (9)$$

The total power dissipated by the upper MOSFET at full load can now be approximated as the summation of the results from Equations (8) and (9).

The output inductor is another key loss. DCR is the DC resistance of the output inductor and P_{fe} is the ferrite core loss.

$$P_l = I_{out}^2 \times DCR + P_{fe} \quad (10)$$

The total dissipation P_d is:

$$P_d = P_{low_on} + P_{low_off} + P_{up_on} + P_{up_off} + P_l \quad (11)$$

Because the power equations depend on MOSFET parameters, choosing the correct MOSFETs can be an iterative process involving repetitive solutions to the loss equations for different MOSFETs and different switching frequencies.

Also, the dead time of the two PWM signals would affect the total efficiency. It is very easy to optimize the dead time with a C2000 MCU emulator.

5.4 System Off

The converter is turned off by pressing the respective ON/OFF button again.

6 Measurements

6.1 Startup Waveform

In demo board, there are four switches for four converters to power on/off them. After pressed the "ON/OFF" button, C2000 MCU would power on the respectively channel. We can see the startup waveform is very smooth and no overshoot.

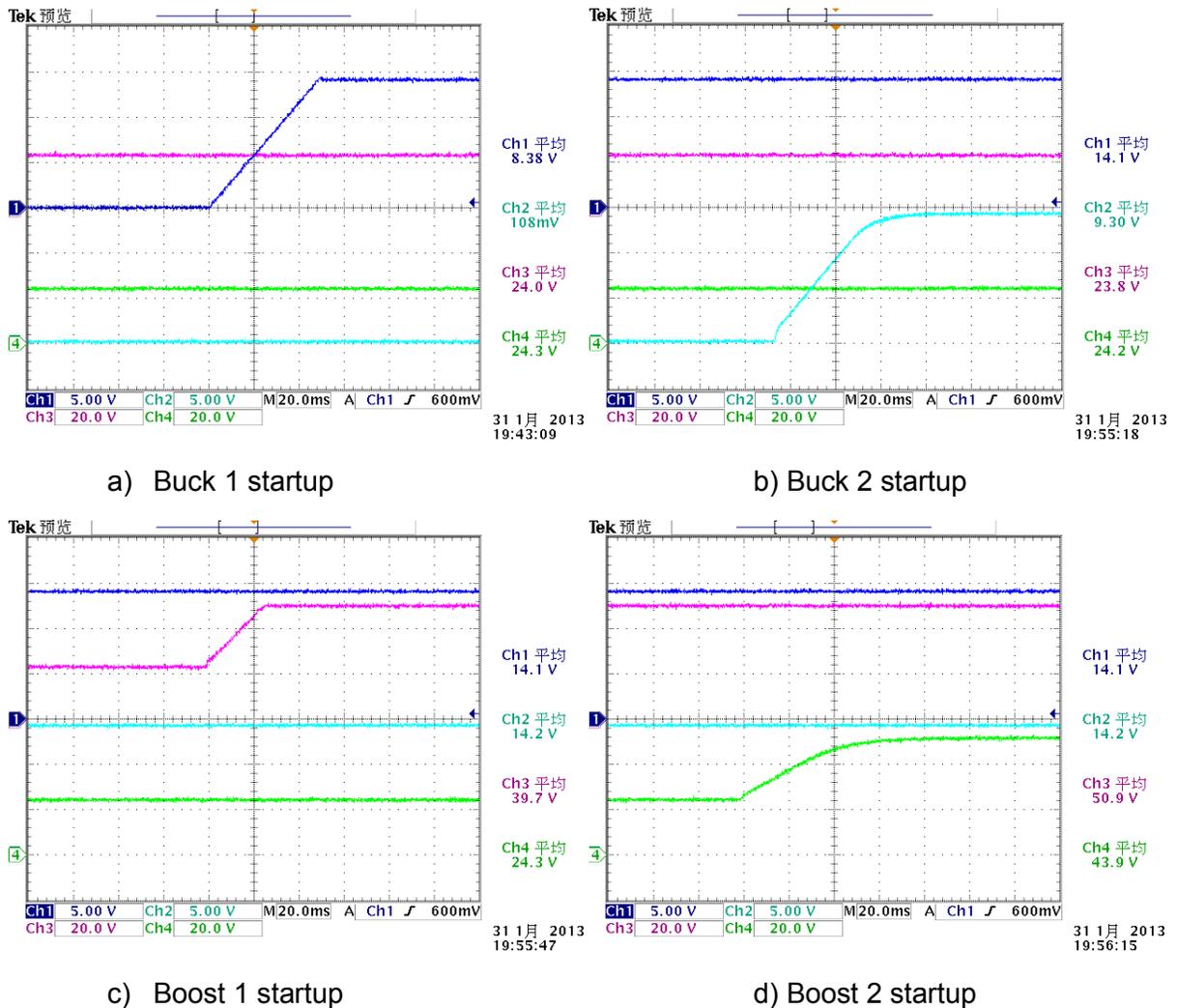


Figure 11. Startup Waveforms

6.2 Transient Load

Figures 12 through 15 show the test condition of transient load:

- 0% to 100% with approximately 0 load
- 1A/uS slew rate

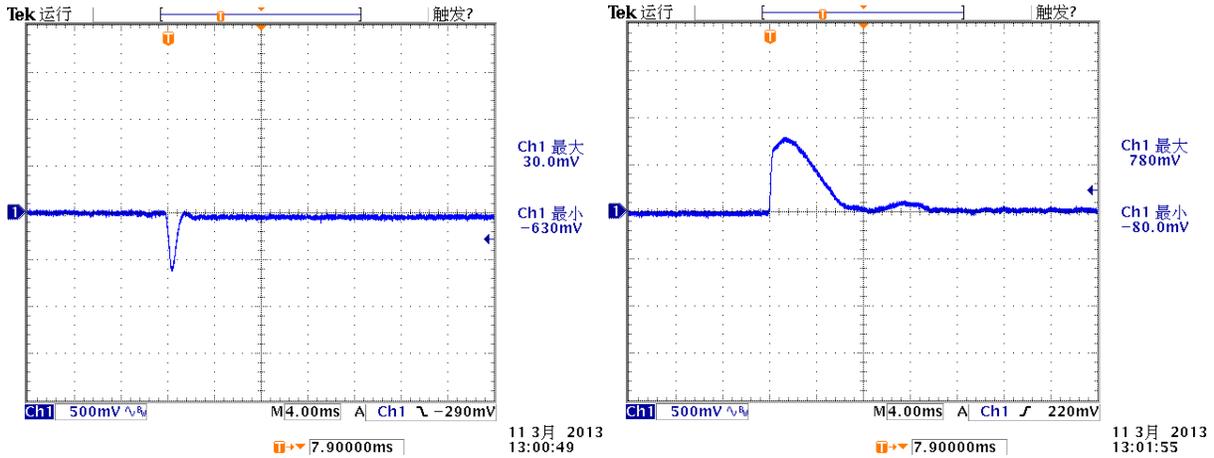


Figure 12. Buck 1 Transient Load

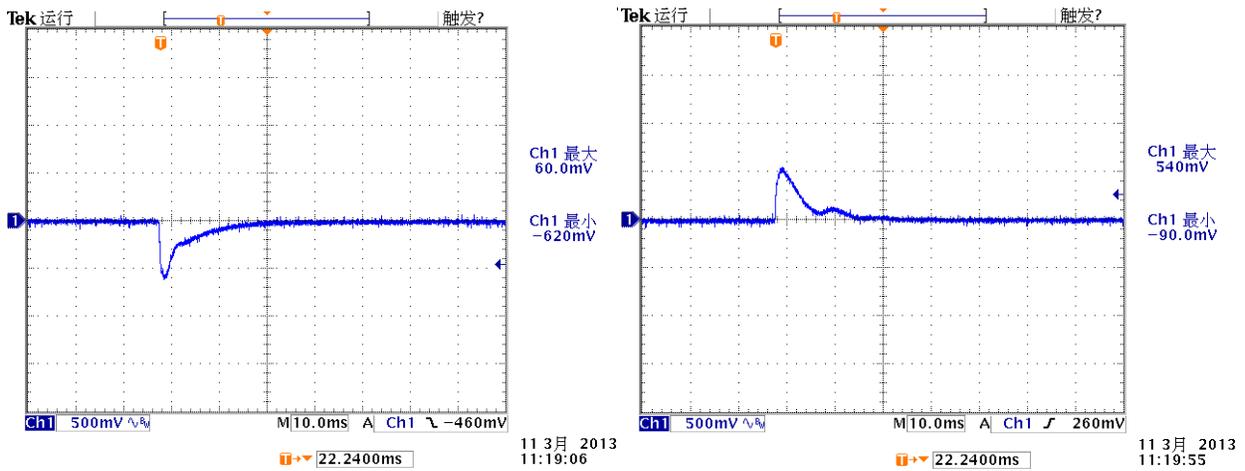


Figure 13. Buck 2 Transient Load

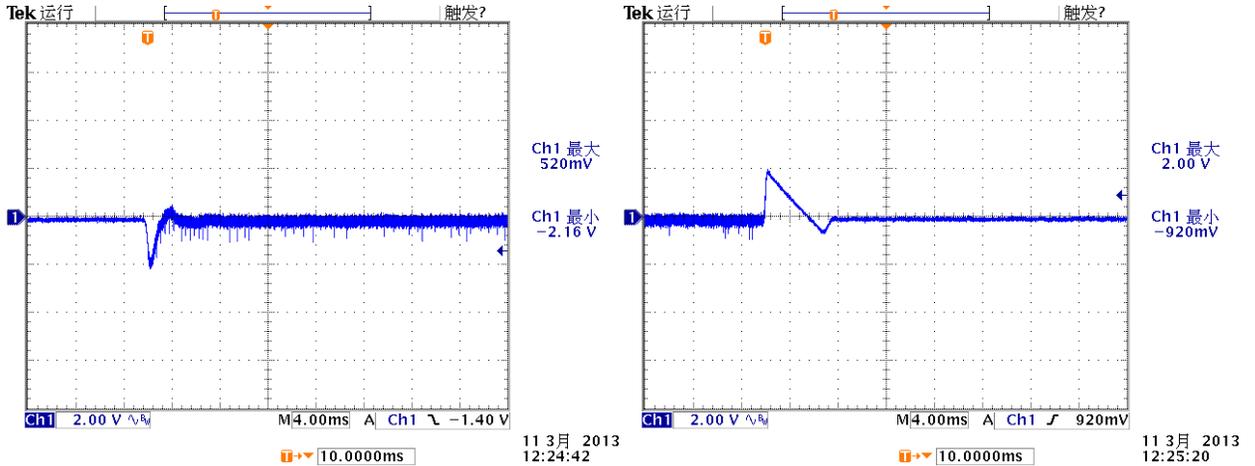


Figure 14. Boost 1 Transient Load

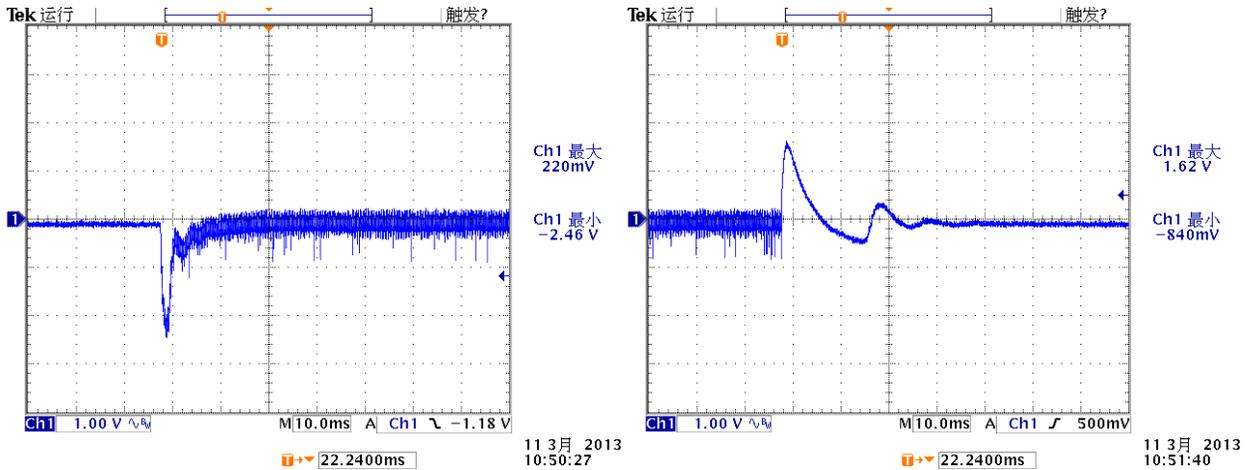


Figure 15. Boost 2 Transient Load

We received a good transient load response, which is approximately 5% to 6% of output voltage.

6.3 Output Ripple Voltage

Figure 16 shows the test results of output ripple voltage. The ripple voltage is the same because we used synchronous rectify technology.

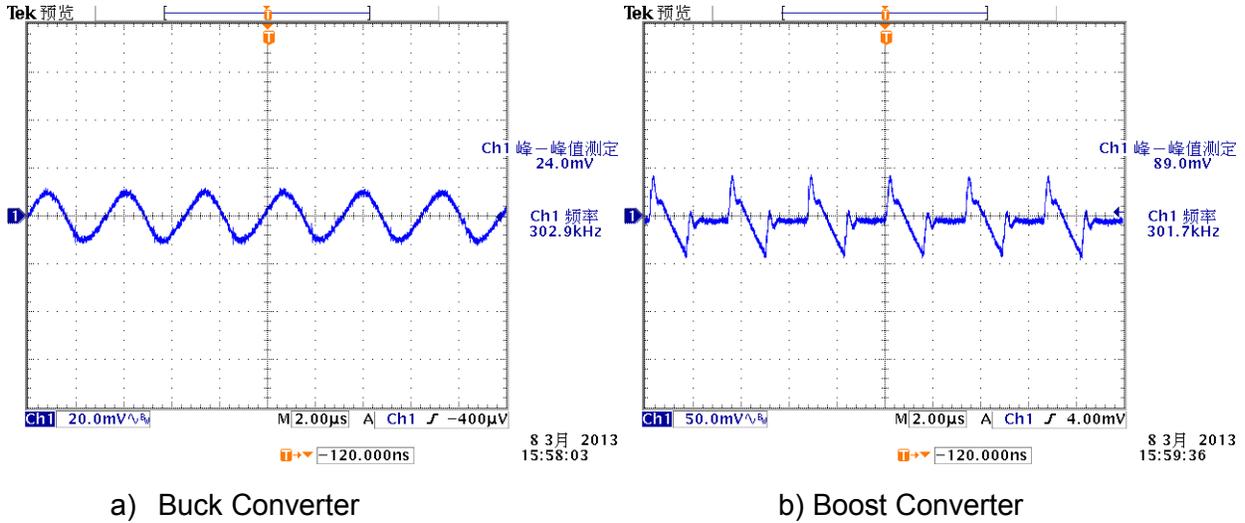


Figure 16. Output Ripple Voltage

7 Fault Management

When input UVP/OVP occurs, the output shuts down.

When output OVP occurs, the output latches off.

When output OCP occurs, the converter goes into hiccup mode (that is, the converter shuts off the power supply for a given time and then tries to restart the power).

8 References

1. *TMS320F28027/28026/28023/28022/28021/28020/280200 Piccolo Microcontrollers (Rev. I) Datasheet, SPRS523I*

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

| | |
|------------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Applications Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Automotive and Transportation | www.ti.com/automotive |
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Video and Imaging | www.ti.com/video |

TI E2E Community

e2e.ti.com