

Module 2

Introduction: Voltage, Current and Power



Introduction: Voltage, Current and Power

Educational Objectives:

REVIEW Electric circuits with resistors, capacitors and inductors UNDERSTAND Voltage, current, and power EXPLORE Behavior of resistors, capacitors, and LEDs LEARN How to use an oscilloscope MEASURE Voltage and current in resistors, capacitors and LED

Prerequisites (Module 1)

Running code on the LaunchPad (Module 1)

Recommended reading materials for students:

Volume 1 Section 1.1,
Embedded Systems: Introduction to the MSP432 Microcontroller
ISBN: 978-1512185676, Jonathan Valvano, copyright (c) 2017

10

Volume 2 Sections 8.1, 8.3.1, and 9.1
Embedded Systems: Real-Time Interfacing to the MSP432
Microcontroller, ISBN: 978-1514676585, Jonathan Valvano, copyright (c) 2017

This module serves as a brief overview of the electrical engineering terms used in the circuits of this class. As a prerequisite of this course, we expect the students to have basic understanding of resistors, capacitors, and inductors. The electrical circuits for the robot explorer are either given or very simple, so this course does not entail circuit design. However, students will need to understand voltage, current, and power as they apply to these circuits. This module presents formal definitions of voltage, current, and power. The lab provides a simple means to discover these parameters for resistors, capacitors, and LEDs.

Current (I) is defined as the movement of electrons. Current is directional and measured at one point as the number of electrons travelling per second. Current has amplitude and a direction. Because electrons are negatively charged, if the electrons are moving to the left, we define current as flowing to the right.

Voltage (V) is an electrical term representing the potential difference between two points. The units of voltage are volts (V), and it is always measured as a difference. Voltage is the electromotive force or potential to produce current.

Another important parameter occurring when current flows through a device is **power**. The power (P in watts) dissipated in a device can be calculated as the product of voltage (V in volts) times current (I in amps). Interestingly, although voltage has a polarity (+ and –) and current has a direction, power has neither a polarity nor a direction. Resistors, capacitors, LEDs, and motors dissipate power in different ways.

The **energy** (E in joules) stored in a battery can be calculated from voltage (V in volts), current (I in amps), and time (t in seconds). Energy has neither polarity nor direction.

An **oscilloscope**, or scope, graphically displays information about an electronic circuit, where the voltage amplitude versus time is displayed. A scope has one or more channels, with many ways to trigger or capture data. A scope is particularly useful when interfacing sensors and actuators to the robot explorer.

A **signal generator** is a device that creates a voltage versus time output. Example waveform shapes are square waves, pulses and sine waves. Some generators allow you to control frequency and voltages of these waves.

In the lab associated with this module, you will build some simple circuit with resistors, capacitors, and LEDs. Using a voltmeter and current meter, you will study the steady state response (direct current, **DC**) of resistor and LED circuits. In this way, you can discover voltage, current and power. Using a signal generator and an oscilloscope, you will study the transient response (alternating current, **AC**) of the resistor/capacitor circuits.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products http://www.ti.com/sc/docs/stdterms.htm), evaluation modules, and samples (http://www.ti.com/sc/docs/sampterms.htm).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2018, Texas Instruments Incorporated