



Module 8

Activity: Interfacing Input and Output




Activity: Interfacing input and output devices using LEDs and Switches

Question 1

You are given a double-pole switch that has three pins, labeled 1, 2, and 3. If the switch is not pressed, pins 1 and 2 are connected (0Ω resistance) and pins 2 and 3 are not connected (infinite resistance). If the switch is pressed, pins 2 and 3 are connected (0Ω resistance) and pins 1 and 2 are not connected (infinite resistance). Pins 1 and 3 are never connected (it is a break-before-make switch). Interface this switch to the microcontroller, such that input pin is high (3.3V) if the switch is pressed and input pin is low (0V) if the switch is not pressed.

You do not need to debounce the switch. Label all chip numbers and resistor values. No software is required. The best solution will not require any resistors.

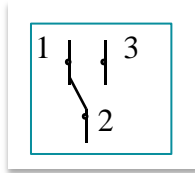

Question 2

Interface a positive logic switch to P1.5 without an external resistor. Write code to configure Port 1 bit 5 as needed. Write code that waits for the switch to be touched, and then released.

- Part a) Develop a solution assuming the switch does not bounce.
- Part b) Develop a solution assuming there is 2ms of switch bounce

Question 3

Interface a negative logic switch to P2.6 without an external resistor. Write code to configure Port 2 bit 6 as needed. Write code that waits for the switch to be touched, and then released.

- Part a) Develop a solution assuming the switch does not bounce.
- Part b) Develop a solution assuming there is 2ms of switch bounce.

Question 4

Interface an LED that requires 1 mA at 2.5 V. A digital output high on the microcontroller turns on the LED. Assume $V_{OH} = 3.2V$. I.e., this interface is positive logic.

Question 5

Interface an LED that requires 2 mA at 2.0 V. A digital output low on the microcontroller turns on the LED. I.e., this interface is negative logic. Because of the direct connection to the microcontroller, you should use 3.3V to power the LED (and not 5V). Assume $V_{OL} = 0.3V$.

Question 6

Interface an LED that requires 15 mA at 2.5 V. Use a LM7405 driver and a current limiting resistor. A digital output high on the microcontroller turns on the LED as this interface is positive logic. The LM7405 output voltage V_{OL} is 0.5V. At this current you can safely use either 3.3V or 5V to power the LED.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated