

**Power Supply Design Seminar**

# Introduction to the Trans-Inductor Voltage Regulator (TLVR)

---



Reproduced from  
2024 Texas Instruments Power Supply Design Seminar  
SEM2600  
Topic 3  
Matthew Schurmann and Mohamed Ahmed  
Literature Number: SLUP413


Power Supply Design Seminar resources  
are available at:  
[www.ti.com/psds](http://www.ti.com/psds)

**Introduced in 2019, the trans-inductor voltage regulator (TLVR) topology offers major transient response, power density and solution cost improvements (a >40% capacitor reduction for the design example reviewed in this topic) versus the traditional multiphase buck voltage regulator topology. This topic covers the operating principles of the TLVR topology, performance and cost improvements over traditional voltage regulators, design equations, and guidelines.**


## Introduction

Load transient regulation performance continues to be an important challenge in the design of voltage regulators for modern computing devices such as microprocessors, graphics processors, application-specific integrated circuits and field-programmable gate arrays. Technology trends in the development of these computing devices, such as rapidly increasing complexity, silicon process-node evolution, physical limitations of transistor scaling and chiplet architectures continue to accelerate the demands placed on the voltage regulators powering them. In some cases, high-end core-rail voltage regulators have thermal design currents greater than 1,000 A, peak currents greater than 2,000 A, rise times in the nanosecond range, and regulated output voltages of 0.7 V,  $\pm 3\%$ .

The TLVR topology is derived from the multiphase half-bridge buck converter topology, but replaces the single-winding inductor of each phase with a two-winding coupled inductor, as shown in **Figure 1** and **Figure 2**. Similar to the multiphase buck converter, the primary side of each coupled inductor is connected between the switch node of each phase and the converter output voltage. The added secondary windings are connected in a series loop, with an additional inductor known as the compensating inductor ( $L_C$ ). In the following sections, we'll discuss the limitations of the multiphase buck converter in terms of load transient response, fundamental operating principles of the TLVR topology, trade-offs and practical considerations.

 

**Figure 1.** Multiphase buck topology.

 


**Figure 2.** TLVR topology.

## Converter Transient Response


**Figure 3** shows a simple block diagram of a voltage regulator system subject to a load transient condition.  $I_{SUM}$  represents the sum of the individual inductor currents from each phase in the converter.  $I_{LOAD}$  represents the actual load current drawn by the load device. Any time  $I_{LOAD}$  changes, the voltage regulator responds by changing the effective duty cycle of switching in each phase in order for the  $I_{SUM}$  to ramp up or down to track the new  $I_{LOAD}$  value.

The output filter of the converter – in particular, the filter inductance – limits how quickly  $I_{SUM}$  can ramp to the new  $I_{LOAD}$  value. During the time when  $I_{SUM}$  is ramping up or down, the filter capacitors must supply the difference between them over time; this is known as the charge  $\Delta Q$ . The output voltage of the converter will undershoot or overshoot during this time, and the only ways to limit the voltage deviation ( $\Delta V$ ) are to either increase the rate at which  $I_{SUM}$  can ramp (by reducing the filter inductance, for example) or to increase the total output capacitance ( $C_{OUT}$ ) of the filter.

 

**Figure 3.** Converter load transient block diagram.

**Figure 4** shows the typical  $I_{SUM}$  and output voltage waveforms in a traditional multiphase buck converter.

 

**Figure 4.** Buck converter load transient.

**Equation 1** shows the relationship between the total output deviation  $\Delta V$ ,  $C_{OUT}$ , and the rate (slope) at which the converter can ramp its current up or down:


$$\Delta V = \frac{\Delta Q}{C_{out}} = \frac{\frac{1}{2} \times t_{resp} \times I_{step}}{C_{out}} = \frac{\frac{1}{2} \times \frac{I_{step}^2}{Slope}}{C_{out}} \quad (1)$$

For the traditional multiphase buck converter, this slope is directly related to the output filter inductance used for each phase. Reducing the inductance value would indeed improve the transient response of the converter.

Simply reducing the output inductance of each phase has unintended consequences for the converter's power losses and its steady-state ripple, however. Reducing the inductance value leads to a higher inductor current ripple and consequently a higher voltage ripple on the output of the converter, which typically also has stringent requirements. It also increases the root-mean-square (RMS) current in each phase, reducing overall converter efficiency.

In a multiphase buck converter topology, the inductance value is a constant, in both steady state and during transient events. Therefore, the selection of an inductance value is a balanced trade-off between transient response, power loss, and voltage ripple and current ripple. It is not practical to make the inductance very small; thus, a large amount of  $C_{OUT}$  may be required to limit  $\Delta V$  in order to meet the specifications.

The TLVR topology addresses this problem by allowing a different effective filter inductance in different conditions. A high effective value of filter inductance during steady-state operation limits the converter ripple and RMS power losses. A low effective inductance value during transient conditions dramatically reduces the amount of  $C_{OUT}$  required to meet a given transient regulation specification. **Figure 5** shows the typical load transient response of a TLVR converter, having a much higher  $I_{SUM}$  slope during the converter response.

 

**Figure 5.** TLVR load transient.

It is possible to achieve a further reduction in capacitance with either the multiphase buck or TLVR topology using DC load line (DCLL), also known as adaptive voltage positioning. **Figure 6** demonstrates the concept. This technique applies to either the multiphase buck converter or TLVR topology and does not change fundamentally.

Given a specification, in terms of a load step size and minimum and maximum allowable output voltage, the converter typically regulates the output voltage to a constant value regardless of the load current – this is known as zero load line,  $R_{LL} = 0 \text{ m}\Omega$ . Then the allowed output voltage overshoot ( $\Delta V_{\text{overshoot}}$ ) and undershoot ( $\Delta V_{\text{undershoot}}$ ) each become equal to 50% of the total voltage specification window.

For a non-zero-load-line design, configure the converter to set its output voltage as a function of the sensed load current. The voltage at zero load ( $V_0$ ) is configured to a value near the maximum allowed output voltage.

**Equation 2** describes the output voltage when using the load line:

$$V_{\text{OUT}}(I_{\text{OUT}}) = V_0 - R_{LL} \times I_{\text{OUT}} \quad (2)$$


**Equation 3** defines the  $R_{LL}$  value in terms of the allowed voltage change  $\Delta V_{\text{DROOP}}$ :

$$R_{LL} = \frac{\Delta V_{\text{DROOP}}}{\Delta I_{\text{STEP}}} \quad (3)$$

**Equation 4** and **Equation 5** express the effect of  $R_{LL}$  on the required  $C_{\text{OUT}}$  of the converter:

$$C_{\text{OUT}}(\text{min, step up}) = \frac{\Delta Q_{\text{under}}}{\Delta V_{\text{under}}} = \frac{\frac{1}{2} \times \frac{I_{\text{STEP}}^2}{\text{Slope}}}{\Delta V_{\text{ac}} + R_{LL} \times I_{\text{step}}} \quad (4)$$

$$C_{\text{OUT}}(\text{min, step down}) = \frac{\Delta Q_{\text{over}}}{\Delta V_{\text{over}}} = \frac{\frac{1}{2} \times \frac{I_{\text{step}}^2}{\text{Slope}}}{\Delta V_{\text{ac}} + R_{LL} \times I_{\text{step}}} \quad (5)$$

 

**Figure 6.** DC load line, or adaptive voltage positioning.


## Magnetics

Because the TLVR topology achieves its transient benefits by allowing different effective inductance values in steady-state and transient conditions, it is helpful to explore the behavior of the coupled inductor structure that it uses. This concept is not entirely unique to the TLVR topology.

**Figure 7** shows a traditional two-phase coupled inductor structure in which the windings for individual phases in the converter share a common magnetic core. Current in one winding directly induces current in the others, as the magnetic flux in the core is additive. During a load transient, a current change in one phase (one winding) directly causes a change in the same direction in the other phases. This behavior allows the total converter  $I_{\text{SUM}}$  to ramp up or down to meet the load current demand more quickly than if the phases were uncoupled.

The coupling coefficient ( $K$ ) between different windings of this structure will typically be between 0.4 and 0.7. This coupling is well controlled by the core design (in **Figure 7**, by the air gap in the middle leg). Very high coupling

 ( $K \cong 1.0$ ) is not beneficial, as it increases the current ripple of the converter in steady state. Very low coupling simply reduces the transient benefits achievable.




Source: Eaton

**Figure 7.** Traditional two-phase inverse-coupled inductor.

Adoption of the traditional coupled inductor for high-phase-count designs (more than four phases) has been limited for several reasons. Extending it to higher phase counts requires a complex core geometry to maintain coupling symmetry. This structure also requires more customization of inductors for different designs, limiting scalability; for example, you would need a different inductor for two- and three-phase designs. Additionally, until recently, aggressive patent protection limited multisourcing options; no such limitation exists for the TLVR topology.

The TLVR topology relies on a similar principle but with a different magnetic structure, known as an indirect-coupled inductor, shown in **Figure 8**. Each phase inductor has its own physical core with two windings, so this structure is easily scalable to higher phase counts simply by adding more cores. The magnetizing inductance ( $L_M$ ) of each coupled inductor provides energy storage and filtering. The  $K$  between two windings on one core can be very high. Passing the same

 secondary-side current to all phases achieves coupling between cores (the phases), as they are connected in a loop.




A. Primary side (connect to power stage)

B. Secondary side (provides coupling)

**Figure 8.** Indirect-coupled two-phase inductor.


Similar to a traditional coupled inductor, it is beneficial to have the coupling coefficient ( $\alpha$ ) between phases in the range of 0.4 to 0.7. The secondary loop controls this coupling. The inductance in the secondary loop may be very low, leading to high coupling (and thus a large steady-state current ripple) or simply not well-controlled, as a result of interconnect and physical construction tolerances.

To control the coupling between phases, the TLVR topology often uses a separate physical inductor on the secondary side,  $L_C$ , shown in **Figure 9**. If the leakage inductance in the secondary-side loop is large enough compared to the magnetizing inductance of the individual coupled inductors, and can be well-controlled by manufacturing, a separate physical  $L_C$  is not needed, especially in high-frequency designs switching at higher than 1 MHz per phase.

 

**Figure 9.** Indirect-coupled two-phase inductor with a physical compensating inductor.

**Figure 10** shows the typical construction of a TLVR inductor. The inductor size and shape are similar to traditional high-current ferrite core inductors for multiphase buck converters, with the secondary winding inside the primary winding. The land pattern on the bottom of the package enables co-layout with both TLVR and non-TLVR designs on the same physical printed circuit board (PCB).

 

- A. Primary winding
- B. Secondary winding

Source: Eaton

**Figure 10.** Typical TLVR inductor construction.

## TLVR Topology Operating Principles


### Steady-State Operation

**Figure 11** shows a typical TLVR converter schematic, with important nodes, voltages and currents labeled.

**Figure 12** illustrates the steady-state operating waveforms of a TLVR converter, with four phases shown. In this example, the pulses from adjacent phases do not overlap in time. There is no maximum duty-cycle requirement for the TLVR topology. The same principles apply for higher-duty-cycle applications where pulses do overlap in time.


**Figure 12** shows the voltage and current waveforms of the  $L_C$  of the secondary-side loop, switch nodes of all four phases, and the primary-side current of phase 4 ( $I_{PRI4}$ ). For clarity, this figure includes labels for the three distinct states of operation.

 The most important relationships are those of the  $L_C$  loop and its influence on  $I_{PRI}$  and  $I_{SUM}$ .



Four-phase example, no pulse overlap

**Figure 11.** Steady-state topology.

 

Four-phase, no pulse overlap

**Figure 12.** Steady-state waveforms.

The magnetizing voltage for each phase is similar to that of a buck converter. Equation 6 applies to phase on, and Equation 7 applies to phase off. The magnetizing inductance always follows the fundamental inductor relationship shown in Equation 8:

$$\Delta V_{Lm,i} = V_{IN} \quad (6)$$

$$\Delta V_{Lm,i} = V_{IN} - V_{OUT} \quad (7)$$

$$I_{LM} = \frac{\Delta V_{Lm}}{L_m} \quad (8)$$

The voltage across the  $L_C$  is always equal to the sum of the magnetizing voltages across all phases, as shown in Equation 9.  $L_C$  itself always follows the fundamental inductor relationship, expressed by Equation 10:

$$\Delta V_{LC} = V_{Lm1} + V_{Lm2} + \dots \quad (9)$$

$$I_{LC} = \frac{\Delta V_{LC}}{L_C} \quad (10)$$

The  $I_{PRI}$  for each phase is equal to the sum of its magnetizing current and  $I_{LC}$ , expressed in Equation 11.  $I_{SUM}$  is the sum of the primary currents from all phases, expressed by Equation 12:

$$I_{PRI,i} = I_{Lm,i} + I_{LC} \quad (11)$$

$$I_{SUM} = I_{PRI1} + I_{PRI2} + \dots \quad (12)$$

**Table 1** summarizes the state of each of the relevant voltages and currents shown in Figure 12, with respect to the derivation of  $I_{PRI4}$  shown in the plot.

Parameter	State 1 Phase 4 on, phases 1, 2 and 3 off	State 2 All phases off	State 3 Phase 4 and two others off, one of the other phases is on
$V_{SW1}$	0 V	0 V	One phase is equal to $V_{IN}$ and the other two are equal to 0 V.
$V_{SW2}$	0 V	0 V	
$V_{SW3}$	0 V	0 V	
$V_{SW4}$	$V_{IN}$	0 V	$-V_{OUT}$
$\Delta V_{Lm1}$ <sup>(1)</sup>	$-V_{OUT}$	$-V_{OUT}$	One phase is equal to $V_{IN} - V_{OUT}$ and the other two are equal to $-V_{OUT}$
$\Delta V_{Lm2}$ <sup>(1)</sup>	$-V_{OUT}$	$-V_{OUT}$	
$\Delta V_{Lm3}$ <sup>(1)</sup>	$-V_{OUT}$	$-V_{OUT}$	
$\Delta V_{Lm4}$	$V_{IN} - V_{OUT}$	$-V_{OUT}$	$-V_{OUT}$
$I_{Lm4}$	Increasing <sup>(2)</sup>	Decreasing <sup>(2)</sup>	Decreasing <sup>(2)</sup>
$\Delta V_{LC}$	Sum of $V_{SW1}$ to $V_{SW4}$ <sup>(5)</sup>	Sum of $V_{SW1}$ to $V_{SW4}$ <sup>(5)</sup>	Sum of $V_{SW1}$ to $V_{SW4}$ <sup>(5)</sup>
$I_{LC}$	Increasing <sup>(3)</sup>	Decreasing <sup>(3)</sup>	Increasing <sup>(3)</sup>
$I_{PRI4}$	Increasing <sup>(4)</sup>	Decreasing faster <sup>(4)</sup>	Decreasing slower <sup>(4)</sup>

**Table 1.** Four-phase example, steady-state voltages and currents.

- (1) Not in Figure 12.
- (2)  $\Delta V_{Lm4}/L_m$
- (3)  $\Delta V_{LC}/L_C$
- (4)  $I_{Lm4} + I_{LC}$
- (5)  $V_{IN} - 4 \times V_{OUT}$

## Load Transient Step-Up

Figure 13 and Figure 14 show a simulated comparison between a multiphase buck converter and a TLVR design under the same load step-up condition. Table 2 summarizes the simulation parameters. These are closed-loop simulations using the TI TPS536C9T DCAP+™ constant on-time controller.

A few observations about Figure 13 and Figure 14:

- The TLVR design responds to the transient ( $I_{SUM}$  catches up to  $I_{LOAD}$ ) much more quickly because the  $I_{SUM}$  rises at a faster rate. As a consequence, the output voltage deviation is significantly lower.



- During the transient response, the multiphase buck converter design required many more pulses to respond than the TLVR design, meaning that the TLVR design delivers more energy per pulse during the transient event.
- Given the nature of constant-on-time control, pulses overlapped during the transient response. The  $L_C$  voltage increased to a level significantly higher than the input voltage during pulse overlap operation, then returned to normal operation at steady state.

 


Figure 13. Multiphase buck converter.

 


Figure 14. TLVR.

Parameter	Description	Value
$V_{IN}$	Input voltage	12 V
$V_{OUT}$	Output voltage	0.8 V
$N_{TOTAL}$	Total operating phase number	4 phases
$f_{SW}$	Switching frequency per phase	600 kHz
$I_{STEP}$	Load step size	25 A to 325 A, instantaneous
$L_M/L_{BUCK}$	Magnetizing inductance $L_M$ for TLVR, filter inductor $L_{BUCK}$ for buck	150 nH/150 nH
$L_C$	$L_C$ value for TLVR	180 nH
$C_{OUT}$	Output capacitance	5.0 $\mu$ F, idealized

Table 2. Simulation parameters for transient load step-up and step-down examples.

Following the relationships described in the **Steady-State Operation** section, it is evident why the TLVR is able to ramp its  $I_{SUM}$  up more quickly than the buck converter, and why its transient response was superior.

$I_{SUM}$  for the buck converter is simply the sum of its individual inductor currents, as shown in **Equation 13**. For the TLVR design,  $I_{LC}$  gets added once for each phase, in addition to each magnetizing current ( $I_{LM}$ ), as shown in **Equation 14**:

$$I_{SUM(buck)} = I_{L1} + I_{L2} + \dots \quad (13)$$

$$I_{SUM(TLVR)} = I_{PRI1} + I_{PRI2} + \dots = (I_{LM1} + I_{LC}) + (I_{LM2} + I_{LC}) + \dots \quad (14)$$

All inductors in the system follow the fundamental inductor relationship. During the transient response to the load step-up, the converter turns on  $N_{ON}$  phases simultaneously. For various reasons, it may not be possible to turn on all phases at once, so also consider that  $N_{OFF}$  phases remain off at any one time. **Equation 15** and **Equation 16** show the rising  $I_{SUM}$  slope for the multiphase buck converter. These equations do not account for the controller response time, but show only the limitation from the converter topology.

$$\uparrow \text{Slope}_{(buck)} = \frac{\Delta V_{L1}}{L} + \frac{\Delta V_{L2}}{L} + \dots \quad (15)$$

$$\uparrow \text{Slope}_{(buck)} \cong N_{ON} \left( \frac{V_{IN} - V_{OUT}}{L} \right) - N_{OFF} \left( \frac{V_{OUT}}{L} \right) \quad (16)$$



**Equation 17** and **Equation 18** show the rising  $I_{SUM}$  slope for the TLVR design, assuming that the TLVR magnetizing inductance  $L_M$  was equal to the buck filter inductor  $L$  for comparison purposes:

$$\uparrow \text{Slope}_{(TLVR)} = \left( \frac{\Delta V_{L1}}{L_M} + \frac{\Delta V_{LC}}{L_C} \right) + \left( \frac{\Delta V_{L2}}{L_M} + \frac{\Delta V_{LC}}{L_C} \right) + \dots \quad (17)$$

$$\uparrow \text{Slope}_{(TLVR)} \cong \uparrow \text{Slope}_{(buck)} + N_{TOTAL} \times \left( \frac{N_{ON} \times V_{IN} - N_{TOTAL} \times V_{OUT}}{L_C} \right) \quad (18)$$


Written in this way, the additional terms clearly show the influence of  $L_C$  in enabling the TLVR design to respond more quickly to transients than a traditional multiphase buck design.

### Load Transient Step-Down


**Figure 15** and **Figure 16** show a simulated comparison between a multiphase buck converter and a TLVR design under the same load step-down condition. This simulation uses the same parameters as those in **Table 2**.

A few observations about **Figure 15** and **Figure 16**:

- The TLVR design responds to the transient ( $I_{SUM}$  catches up to  $I_{LOAD}$ ) much more quickly because the  $I_{SUM}$  is falling at a faster rate. As a consequence, the output voltage deviation is significantly lower.
- In this case, both designs had the same number of phases off, but the TLVR design ramped down the  $I_{SUM}$  at a faster rate.

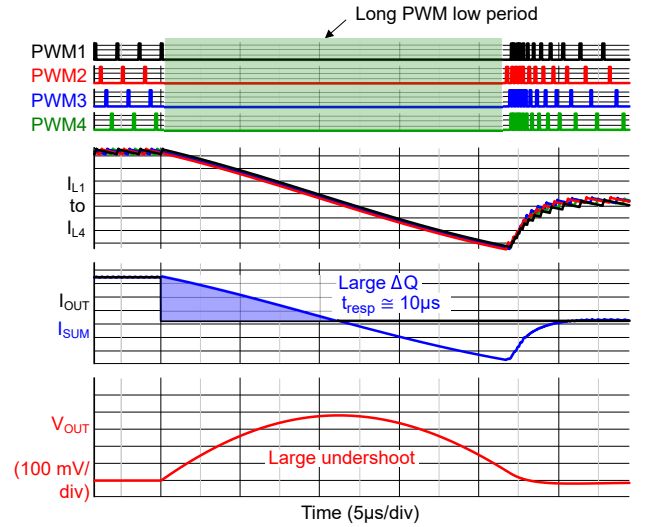

**Figure 15.** Multiphase buck converter.

 

**Figure 16.** TLVR.

Again, the relationship of  $I_{LC}$  to  $I_{SUM}$  explains the superior transient response of the TLVR design. And again, all inductors in the system follow the fundamental inductor relationship. During the transient response to the load step-down, the converter turns off all phases,  $N_{TOTAL}$ , simultaneously. **Equation 19** shows the falling  $I_{SUM}$  slope for the multiphase buck converter:

$$\downarrow \text{Slope}_{(buck)} = - N_{TOTAL} \left( \frac{V_{OUT}}{L} \right) \quad (19)$$

Using a similar analysis, [Equation 20](#) shows the falling  $I_{SUM}$  slope for the TLVR design, assuming that the TLVR magnetizing inductance  $L_M$  is equal to the buck filter inductor  $L$  for comparison purposes. The TLVR design ramps down its  $I_{SUM}$  faster given the factor from the  $L_C$  loop, which decreases proportionally to the square of the number of phases,  $N_{TOTAL}$ .

$$\downarrow \text{Slope}_{(TLVR)} \cong \downarrow \text{Slope}_{(buck)} - N_{TOTAL} \times \left( \frac{N_{TOTAL} \times V_{OUT}}{L_C} \right) \quad (20)$$

## L<sub>C</sub> Inductor Selection

The  $L_C$  has somewhat unique requirements compared to other inductors in a typical DC/DC design. The inductance of  $L_C$  is a trade-off between current ripple and transient response benefits. Typically, start with  $L_C = L_M$  as a balanced trade-off. Values between 0.8 to 1.5 times  $L_M$  are common with discrete designs. Lower values may be more common in highly integrated designs, such as power modules.

At steady state,  $L_C$  carries no DC current – only a small AC current ripple – because it is switching at a high frequency (at least  $N_{TOTAL} \times f_{SW}$  when there is no pulse overlap). Its current ripple dominates its RMS current at steady state, described in [Equation 21](#). Consider low core-loss materials, such as ferrite cores, because of the high  $f_{SW}$ . Another option to further improve transient response may be soft-saturating cores.


$$I_{rms}(L_C) \approx \frac{\Delta I_{LC}}{\sqrt{3}} \quad (21)$$

However,  $L_C$  can continue to build large amounts of current during transient events, as expressed by [Equation 22](#), where  $t_{RESP}$  is the response time of the controller, as highlighted in [Figure 15](#) and [Figure 16](#). Therefore, size the  $L_C$  with a high saturation current, similar to the coupled inductors used in each phase.


$$I_{SAT}(L_C) \gg t_{RESP} \times \left( \frac{N_{ON(step)} \times V_{IN} - N_{TOTAL} \times V_{OUT}}{L_C} \right) \quad (22)$$

After building up a large current, the  $L_C$  current naturally decays to zero, with a relatively high time constant,  $\tau_{LC}$ , as described in [Equation 23](#), formed by the  $L_C$  and the resistances in the  $L_C$  loop. During high-frequency repetitive transients,  $I_{LC}$  may not settle fully but will not saturate, as load steps up and down push  $I_{LC}$  in different directions. [Figure 17](#) and [Figure 18](#) show a simulation of this behavior:

$$\tau_{LC} = \frac{L_C}{R_{DCR, L_C} + N_{total} \times R_{DCR, secondary} + R_{routing}} \quad (23)$$

 

**Figure 17.** Low-frequency transient event.

 

**Figure 18.** High-frequency transient event.

The voltage across the  $L_C$ ,  $\Delta V_{LC}$ , can exceed the input voltage,  $V_{IN}$ , during a load step response. Assuming that a controller turns on  $N_{ON}$  phases in response to the load step, Equation 24 calculates  $\Delta V_{LC}$ :

$$\Delta V_{LC(max)} = N_{ON(step)} \times V_{IN} - N_{TOTAL} \times V_{OUT} \quad (24)$$

Creepage is not generally a concern, as the high voltage is not sustained for a long period of time. But the high transient voltage across  $L_C$  may be important to know for application safety and component reliability in some cases.

### Steady-State Ripple

TLVR-based designs tend to have larger output voltage ripple than their multiphase buck converter counterparts. Normally, multiphase converters have low voltage ripple caused by interleaving and ripple cancellation. The converter achieves optimum ripple cancellation when each inductor current has a phase offset of  $360$  degrees/ $N_{TOTAL}$  with respect to each other. For TLVR designs, however,  $I_{LC}$  gets added once to  $I_{SUM}$  for each phase offset. So while the  $I_{SUM}$  contribution from each magnetizing inductance  $L_M$  does cancel because of interleaving, the contribution from  $I_{LC}$  does not, as expressed by Equation 25:

$$I_{SUM(TLVR)} = (I_{Lm1} + I_{LC}) + (I_{Lm2} + I_{LC}) + \dots \quad (25)$$

Figure 19 illustrates the relationship between the ripple on  $I_{SUM}$  and the ripple on the converter output voltage. Typically, the converter and load are separated by a power distribution network (PDN).  $I_{SUM}$  is generated by the converter in one location and fed to the PDN, at some distance. The impedance of the PDN (including output capacitors) then determines the output voltage ripple. For this reason, the additional  $I_{SUM}$  ripple in TLVR designs translates directly to a larger output voltage ripple.

An example in Figure 20 demonstrates the influence of the converter duty cycle. The  $I_{LC}$  ripple can still become very small at certain duty cycles, when phases overlap

perfectly (with  $N_{TOTAL} \times D = 1, 2, \dots$ ). However, for typical applications (highlighted in Figure 20 for typical output voltages of 1.0 V, 1.2 V and 1.8 V), TLVR designs typically have a 25% to 50% larger  $I_{SUM}$  ripple, and consequently, a 25% to 50% larger output voltage ripple. For many cases this will not be an issue, because the  $C_{OUT}$  required to meet the transient requirement is much larger than the capacitance required to meet the design's ripple requirement.

 


Figure 19. Model for output voltage ripple.



 


Figure 20. Output voltage ripple.

A common technique to reduce the voltage ripple of a TLVR design is to use more than one  $L_C$  loop. Figure 21 shows an example with two  $L_C$  loops. The phase-fire order for each phase is such that the  $I_{LC1}$  and  $I_{LC2}$  currents are 180 degrees out of phase, allowing the  $I_{LC1}$  and  $I_{LC2}$  current ripple to cancel.

 

**Figure 21.** Interleaved TLVR design.

 

**Figure 22.** Two-loop interleaved TLVR waveforms.

Interleaving is also common in cases where space constraints on the board layout prevent placing phases near each other. Phases on each  $L_C$  loop are co-located with each other, but the  $L_C$  loops may be separated by some distance, sometimes even on different sides of the load device. While less beneficial in terms of output voltage ripple, TLVR designs with asymmetric phase numbers on each  $L_C$  loop are also possible.

## Power Loss and Efficiency


**Figure 23** compares the power efficiency between a multiphase buck converter and TLVR when designed with the same component values. The curves are already quite similar, but the TLVR design is a small amount lower (0.1 %) in terms of efficiency.

While this plot is useful for demonstration purposes, typically, multiphase buck and TLVR designs will not have the same inductance values. The buck converter will require a lower inductance value to meet the same transient specifications, which further reduces its power efficiency. In practice, when designing two converters to the same specifications, the multiphase buck and TLVR converters have approximately equivalent efficiency. In some cases, TLVR designs can have slightly higher efficiency.

Two loss mechanisms differentiate the TLVR design from the multiphase buck converter. Most obviously the  $L_C$  loop losses are present only in TLVR designs. Earlier, **Equation 21** showed the RMS current in the  $L_C$  loop, as a result of its current ripple. Thus, the losses in the  $L_C$  loop have a component of RMS conduction losses, as well as core losses, which may be significant given the high switching frequency of the  $L_C$ . Equation 25 estimates the power losses in the  $L_C$  loop:


$$P_{L_C} \cong I_{\text{rms}(L_C)}^2 \times (R_{\text{DCR}, L_C} + N_{\text{TOTAL}} \times R_{\text{DCR}, \text{secondary}} + R_{\text{routing}}) + P_{\text{core}(L_C)} \quad (26)$$

Additionally, consider that the additional ripple from  $I_{L_C}$  will increase the RMS current in each power stage, and thus the conduction losses. **Figure 24** demonstrates how the addition of  $I_{L_C}$  increases the peak-to-peak current ripple,  $\Delta I_{\text{pp}}$ , in the low-side switch of each phase. As the  $I_{L_C}$  current ripple increases with lower phase numbers, this additional component can become significant. That is one reason why TLVR designs are typically reserved for high-power, high-phase-count (greater than six phase) designs.

 

$V_{IN} = 12 \text{ V}$                        $V_{OUT} = 1.80 \text{ V}$   
 $f_{SW} = 600 \text{ kHz}$                  $R_{LL} = 0.5 \text{ m}\Omega$   
 $L_M = L_{BUCK} = 120 \text{ nH}$          $L_C = 120 \text{ nH}$   
 Excludes PDN conduction losses

**Figure 23.** Efficiency vs. output current.

 

**Figure 24.** Addition of  $I_{LC}$  to low-side metal-oxide semiconductor field-effect transistor (MOSFET) current.

To understand this loss mechanism, [Equation 27](#) expresses the relationship between the current ripple and low-side MOSFET RMS current for a typical buck converter design. An exact equation for the TLVR design is more complex, but the buck converter equation demonstrates the influence of  $\Delta I_{PP}$ .


$$I_{RMS(LSFET)} = I_{OUT} \times \sqrt{1-D} \times \sqrt{1 + \frac{1}{3} \times \left( \frac{\Delta I_{PP}}{2 \times I_{OUT}} \right)^2} \quad (27)$$

It is also common to use dynamic phase shedding (DPS) in high-phase-count designs to improve light-load efficiency. Switching a fewer number of phases when the total output current is low enough to be supported without all phases active reduces switching losses. Phases can be in one of three states: high-side MOSFET on, low-side MOSFET off; high-side MOSFET off, low-side MOSFET on; or both MOSFETs off. Typically, nonlinear control techniques add or drop phases quickly during load transient events, so the impact on the load transient response is minimal. [Figure 25](#) shows the current flow in each state.


In a TLVR design, the  $L_C$  loop continues to conduct current through the body-diode phases in the third state (both MOSFETs off), which are not switching. There will be additional power losses from nonswitching phases caused by the voltage drop of the body diodes,  $V_{diode}$ . Therefore, for phase shedding to make sense, the switching losses saved by not switching a phase must be greater than that created by the body-diode losses. [Equation 28](#) describes the power losses in nonswitching phases:

$$P_{cond, HiZ} = I_{LC(rms)} \times V_{diode} \quad (28)$$

A measured plot of the same design with phase shedding on and off, shown in [Figure 26](#), demonstrates the TLVR design efficiency improvement at light load.

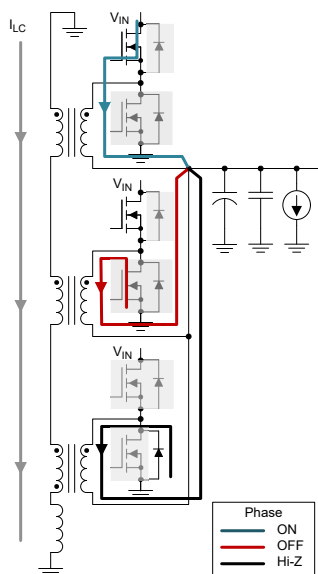

**Figure 25.** Dynamic phase shedding.

 


$V_{IN} = 12\text{ V}$	$V_{OUT} = 1.80\text{ V}$
$f_{SW} = 90\text{ kHz}$	$L_M = L_C = 100\text{ nH}$
8 phases	Dual-side layout
TLVR	CSD08860 (90-A SPS)

**Figure 26.** Efficiency vs. output current.

## Phase Multiplication

As power requirements continue to increase rapidly, it is often necessary to design very high phase-count (more than 16 phase) designs using controller devices that do not have enough independent pulse-width modulation (PWM) outputs to control each phase individually. It has become common to phase double or phase multiply – that is, to drive more than one power stage with the same controller PWM output. This practice enables easy scalability of multiphase designs – buck converter or TLVR – to high power levels.

**Figure 27** shows the connections of the  $L_C$  loops in an interleaved, phase-doubled TLVR design. Such a design could, for example, extend a 12-phase design to 24 or 36 phases, without requiring a different controller device. For all phases (doubled or not) in the same  $L_C$  loop, the secondary sides are connected in series. The current feedback lines from each phase (not shown in **Figure 27**) can be resistor-averaged for power stages with voltage-source-output current sensing, or simply added for power stages with current-source-output current sensing. It is possible to connect temperature sense outputs from each power stage (also not shown in **Figure 27**) together, regardless of which  $L_C$  loop the power stages are in.

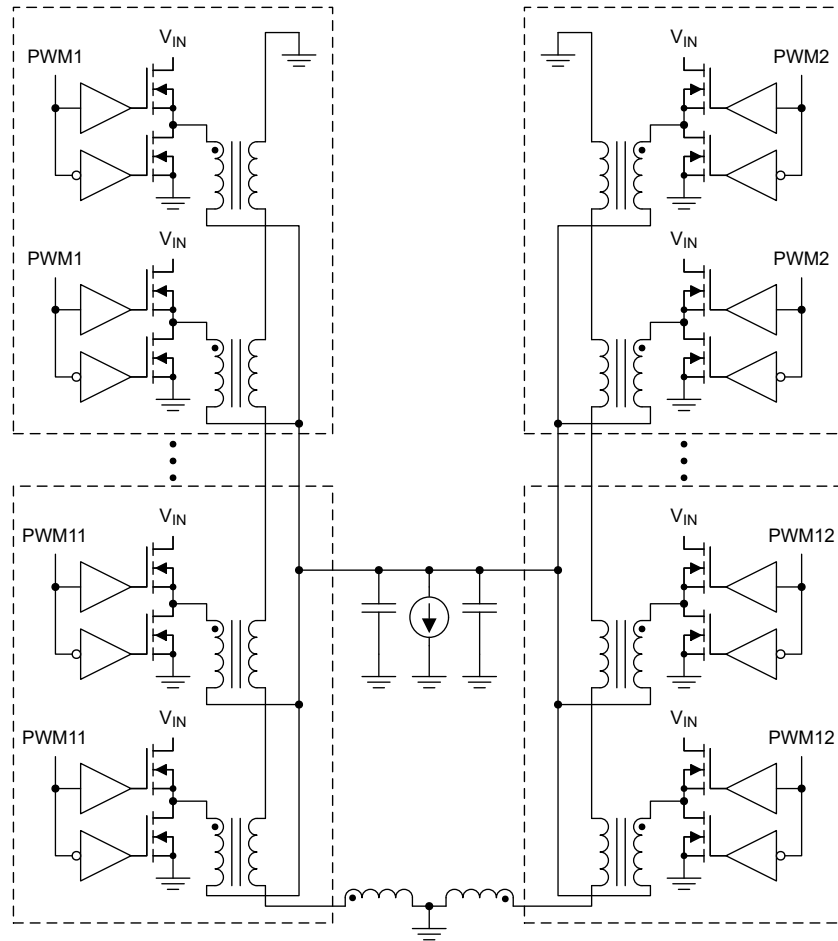

**Figure 27.** Interleaved phase-doubling TLVR topology.



## PCB Layout

**Figure 28** shows an example circuit board layout and component placement for a TLVR design powertrain. This design uses 4-mm-by-6-mm power-stage devices and co-layout-compatible TLVR inductors, enabling similar placement to a typical multiphase buck design.


The  $L_C$  loop runs through the middle of the primary-side pads. The secondary-winding pads of the TLVR inductor enable the running of this loop to occur on the top layer, without requiring many vias or wide traces. Because the  $L_C$  loop can conduct high current during transient events, the traces are as wide as the clearance rules allow, but multilayer planes are not required. Inner ground planes close the  $L_C$  loop from one side of the powertrain to another. Sensitive circuitry should have a wide clearance to the  $L_C$ , and  $L_C$  loop traces to avoid noise coupling and interference.

The  $L_C$  inductor is placed to the side of the power stages. Because the  $L_C$  can be subjected to voltages higher than  $V_{IN}$  and will be switching at a high frequency, high transient voltages and electromagnetic interference may become a concern as well. One possibility to mitigate this (not shown in **Figure 28**) is to split the  $L_C$  into two physical inductors – each with an inductance of one-half  $L_C$  – and place them symmetrically on either side of the power stages. This lowers the maximum voltage across each  $L_C$  during transient events.


Placing the phases as close to each other as possible saves space. However, the phase-fire order is not sequential. Changing the phase-fire order helps to reduce crosstalk issues between phases by spreading their switching nodes out from each other in the time domain.

**Figure 29** is a zoomed-out example of a high-phase-count layout design that uses two  $L_C$  loops, placing doubled phases next to one another and in the same  $L_C$  loop. The phases and  $L_C$  in each loop follow the example in **Figure 28**. The loops are placed on opposite sides (sometimes referred to as cardinal directions, east and west) of the load to minimize the PDN routing between the output of each inductor and the pins of the load device. Two sides of the load device remain open, on the top side, for high-frequency signal routing, as needed by the design.

Decoupling capacitors (not shown in **Figure 29**) are under and, if possible, inside the footprint of the load device. There are placeholders for polymer bulk capacitors, but some designs will not need them. Placing the controller device far away from the powertrain avoids noise issues, with long traces connecting it to the power stages in each  $L_C$  loop. As with any high-power design, it's important to maintain good signal integrity on the PWM outputs, current-sense inputs and voltage-sense lines for the controller.

 

**Figure 28.** Example TLVR powertrain layout.

 

**Figure 29.** Example phase-doubled interleaved TLVR layout.

## TLVR-Optimized Components

Recently, semiconductor vendors such as Texas Instruments (TI) have begun to offer multiphase controllers and power stages optimized for TLVR designs.

Smart power stages optimized for TLVR designs require higher-bandwidth current-sensing architectures because of the high-speed nature of the TLVR topology. The IOUT pin waveform of a TI smart power stage, for example, tracks even the induced current ripple from the  $L_C$  loop in a TLVR design. This requires current-sensing bandwidth at least an order of magnitude higher than the  $f_{SW}$  of the design on a per-phase basis. The TLVR topology also increases the bandwidth requirements for high-speed overcurrent protection.

Smart power stages optimized for TLVR designs must also be rated for increasingly high RMS currents and be able to support peak current pulses nearly two times their RMS rating for short durations, thermally as well as electrically.

Controllers generally do not need re-architecting. TLVR designs use the same control schemes designed for multiphase buck designs. TI controllers continue to use

the DCAP+ control architecture, a form of constant on-time valley current-mode control. They may still require second-order optimizations such as new gain and compensation parameters suited to the TLVR powertrain. Higher-strength PWM output drivers are often needed to support longer distances between multiple  $L_C$  loops while maintaining good signal integrity. The implementation of a new protection mechanism for an open or shorted  $L_C$  loop should ease manufacturability concerns.

**Table 3** and **Table 4** summarize TLVR-optimized components available from TI at the time of this writing, with more under development.

Part number	Current rating	Package size (mm)	$I_{MON}$
CSD95440	80-A peak, 40-A RMS	5 × 6	Voltage
CSD95510	90-A peak, 50-A RMS	4 × 6	Voltage
CSD95560	90-A peak, 50-A RMS	4 × 6	Current
CSD95520	60-A peak, 30-A RMS	4 × 5	Voltage
CSD95570	60-A peak, 30-A RMS	4 × 5	Current

**Table 3.** TLVR-optimized smart power stages.

Part number	Phases	Package size (mm)	Interface
TPS53685	8	5 × 5	AMD
TPS536C5	12	6 × 6	AMD
TPS53689T	8	5 × 5	Intel
TPS536C9T	12	6 × 6	Intel

**Table 4.** TLVR-optimized controllers.

## Example Side-by-Side Design

The examples in earlier sections demonstrated the difference between a multiphase buck design and a TLVR design with the same external components. This comparison is not often practical, however, because the requirements of the load do not change – it


is the design that must change to meet the load requirements. As we've discussed, TLVR inductors are footprint-compatible with standard single-winding inductors, enabling the testing of both designs with the same physical PCB layout.

**Table 5** summarizes one such example. The TLVR design met the same specifications as the multiphase buck converter design with almost no impact on overall power losses, and an over 40% reduction in  $C_{OUT}$  required.


**Figure 30** and **Figure 31** illustrate the worst-case overshoot waveforms for this design.

Parameter	Multiphase buck	TLVR
Controller/standby power supply	TPS53689, CSD95440	
Input voltage ( $V_{IN}$ )	12 V	
Output voltage ( $V_{OUT}$ )	1.8 V	
Minimum output voltage ( $V_{MIN}$ )	1.59 V	
Maximum output voltage ( $V_{MAX}$ )	1.85 V	
Number of phases	8	
Switching frequency	900 kHz	
Load step	60 A-430 A, 1,000 A/μs, 1 kHz-1 MHz	
Load line	0.5 mΩ	
$L_M/L_{BUCK}$	70 nH	120 nH
$L_C$	N/A	100 nH
$C_{BULK}$ (polymer)	5 × 470 μF	0 × 470 μF
Multilayer ceramic capacitors (MLCCs)	80 × 22 μF, 0402	80 × 22 μF, 0402
	45 × 47 μF, 0805	56 × 47 μF, 0603
	15 × 100 μF, 0805	0 × 100 μF, 0805
	8 × 0.1 μF, 0402	8 × 0.1 μF, 0402
Peak power efficiency ( $\eta_{PEAK}$ )	94.0%	93.9%
Full load efficiency ( $\eta_{FULL}$ )	88.1%	88.1%
$V_{MIN}$ measured (worst case)	1.600 V (+10-mV margin), dominated by $R_{LL}$	1.600 V (+10-mV margin), dominated by $R_{LL}$
$V_{MAX}$ measured (worst case)	1.846 V (+4-mV margin)	1.839 V (+11-mV margin)
Total output capacitance ( $C_{OUT}$ )	7.7 mF	4.4 mF

**Table 5.** Design parameters.

 

**Figure 30.** Worst-case overshoot (multiphase buck converter).

 

**Figure 31.** Worst-case overshoot (TLVR).

## Summary

The TLVR topology is an evolution of the traditional multiphase buck converter design for high-phase-count, low-voltage nonisolated designs. It offers significant output capacitor savings and has become increasingly popular. In this paper, we introduced the concepts, operating principles, trade-offs, results from example designs, and practical considerations for TLVR designers.

## Additional Resources

- Technical Disclosure Commons. “**Fast Multi-Phase Trans-Inductor Voltage Regulator.**” Technical Disclosure Commons Defensive Publications Series, May 9, 2019.
- Radhakrishnan, Kaladhar, and Jonathan Douglas, “Microprocessor Power Delivery Challenges.” APEC 2022, March 22, 2022.
- Parisi, Carmen. “**Multiphase Buck Design From Start to Finish (Part 1).**” Texas Instruments application report, literature No. SLVA882B, April 2021.
- Dong, Yan. 2009. “**Investigation of Multiphase Coupled-Inductor Buck Converters in Point-of-Load Applications.**” Ph.D. dissertation, Virginia Polytechnic Institute and State University.
- Qiu, Yang. 2007. “**Coupled Inductors for Power Supplies: Advantages and Compromises.**” EETimes, June 2007.
- Lu, Zengyi, and Wei Chen. “Multi-Phase Inductor Coupling Scheme with Balancing Winding in VRM Applications.” Published in Proceedings of the 22nd Annual IEEE Applied Power Electronics Conference and Exposition, Feb. 25-March 1, 2007, pp. 680-684.
- Zhu, Feiyang. “Multi-Phase Coupled Inductor Analysis for Multi-Phase Voltage Regulators.” Center for Power Electronics Systems PMC Review, June 2021.
- Jiang, Shuai, Xin Li, Mobashar Yazdani, and Chee Chung. “Driving 48V Technology Innovations Forward – Hybrid Converters and Trans-Inductor Voltage Regulator (TLVR).” Published in 34th Annual IEEE Applied Power Electronics Conference and Exposition, March 15-19, 2020.
- Erickson, Robert W., and Dragan Maksimovic. 2020. “Fundamentals of Power Electronics, Third Edition.” New York: Springer AG.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated