

TMS320DM335/DM355 DSP Power Reference Design PR742

1 Features

- Provides sequenced core and input/output voltages from 2-V to 5.5-V input voltages
- Suitable for Li-ion and 3 AA battery inputs
- RESET delay fixed at 20 ms, but can be adjusted
- Optimized for cost and efficiency

2 Introduction

This reference design is for the TMS320DM335/DM355 digital signal processor (DSP) and accounts for voltage, current, and sequencing requirements. The operating input voltage ranges from 2 V to 5.5 V for Li-ion batteries and 3 AA batteries. This design also can work with 2 AA batteries with some limitations. The design is optimized for efficiency over the full range of operation and low overall cost.

3 Requirements

The TMS320DM335/DM355 DSP requires three input rails, which are outlined in [Table 1](#).

Table 1. Voltage Input Requirements

Power Rail	Voltage (V)	Current (mA)	Power-up Sequence	Power-down Sequence
Vout 1	1.3	210	First	Second or third
Vout 2	1.8	30	Second	Second
Vout 3	3.3	95	Second or third	First

To avoid corrupting data or damaging the DSP, the rails must power up and power down in the proper order. On power up, the 1.3 V comes up first, then 1.8 V and 3.3 V together, or 1.8 V, then 3.3 V. Power down is the exact opposite sequence. The 1.8 V and 3.3 V come down together, then 1.3 V, or in the order 3.3 V, 1.8 V, and then 1.3 V.

4 Implementation

This design achieves the three voltages needed to power the TMS320DM335/DM355 with the correct sequencing using two switching converters (TPS62240 and TPS63001), one low dropout (LDO) linear regulator (TPS72118), and two supply voltage supervisors (SVS) (TPS3808-01 and TPS3808G33). The block diagram of the design is shown in [Figure 1](#). See the schematic for further detail.

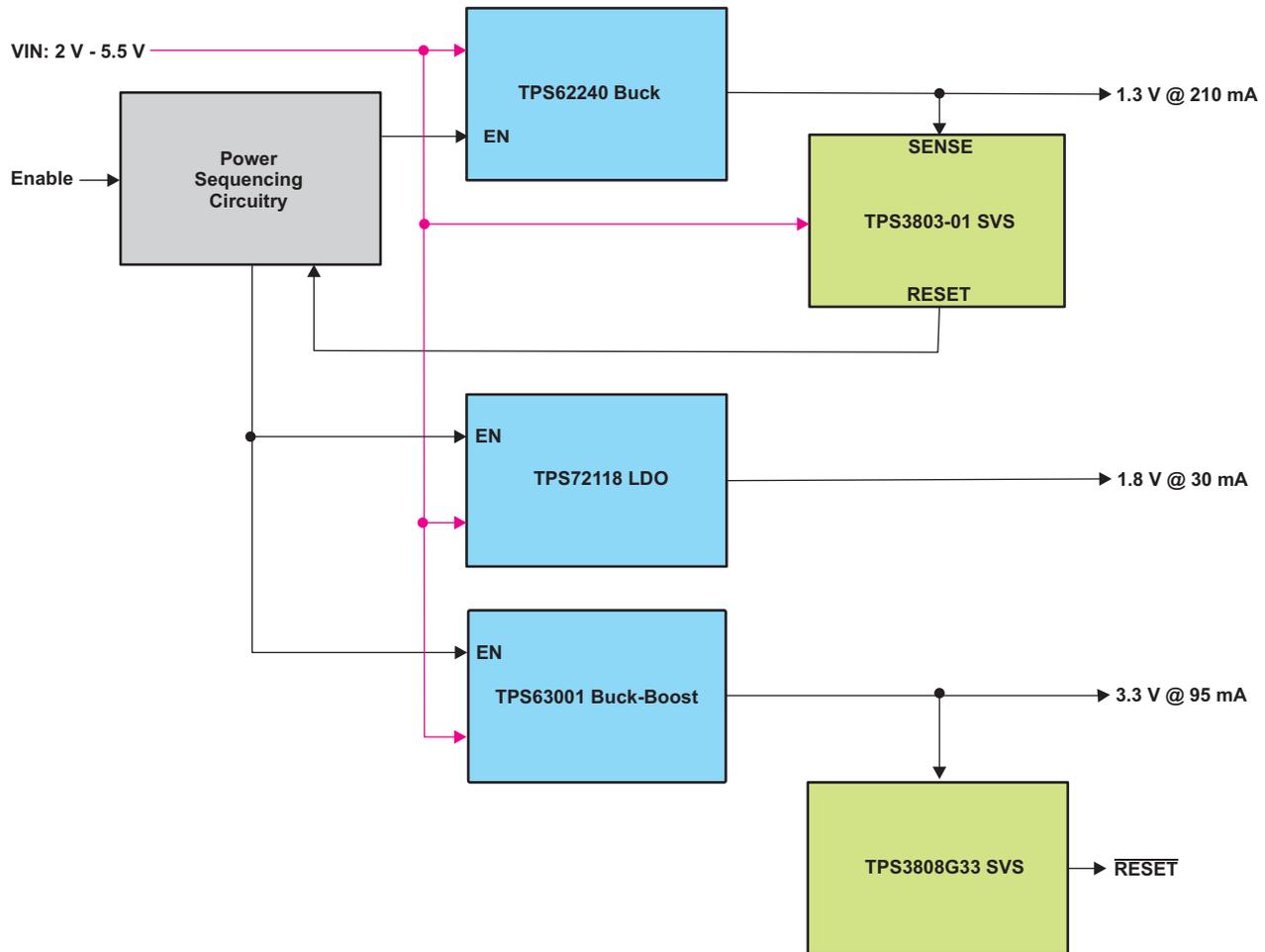


Figure 1. Block Diagram of Power Design

4.1 Power Up

When *ENABLE* goes high (high is considered 1 V to V_{IN}), the TPS62240 is enabled first and the 1.3-V rail comes up. Once the 1.3 V goes above the 1.226-V voltage threshold of the TPS3808-01 SVS, the open-drain *RESET* pin is pulled up to V_{IN} . This pulls the *ENABLE* pins high on the TPS72448 and TPS63001. The 1.8-V rail comes up first and then the 3.3-V rail. The TPS2808G33 SVS is placed on the 3.3-V rail because it is the last rail to come up. The threshold voltage for the TPS2808G33 is 3.07 V, and the delay is set to 20 ms in this design.

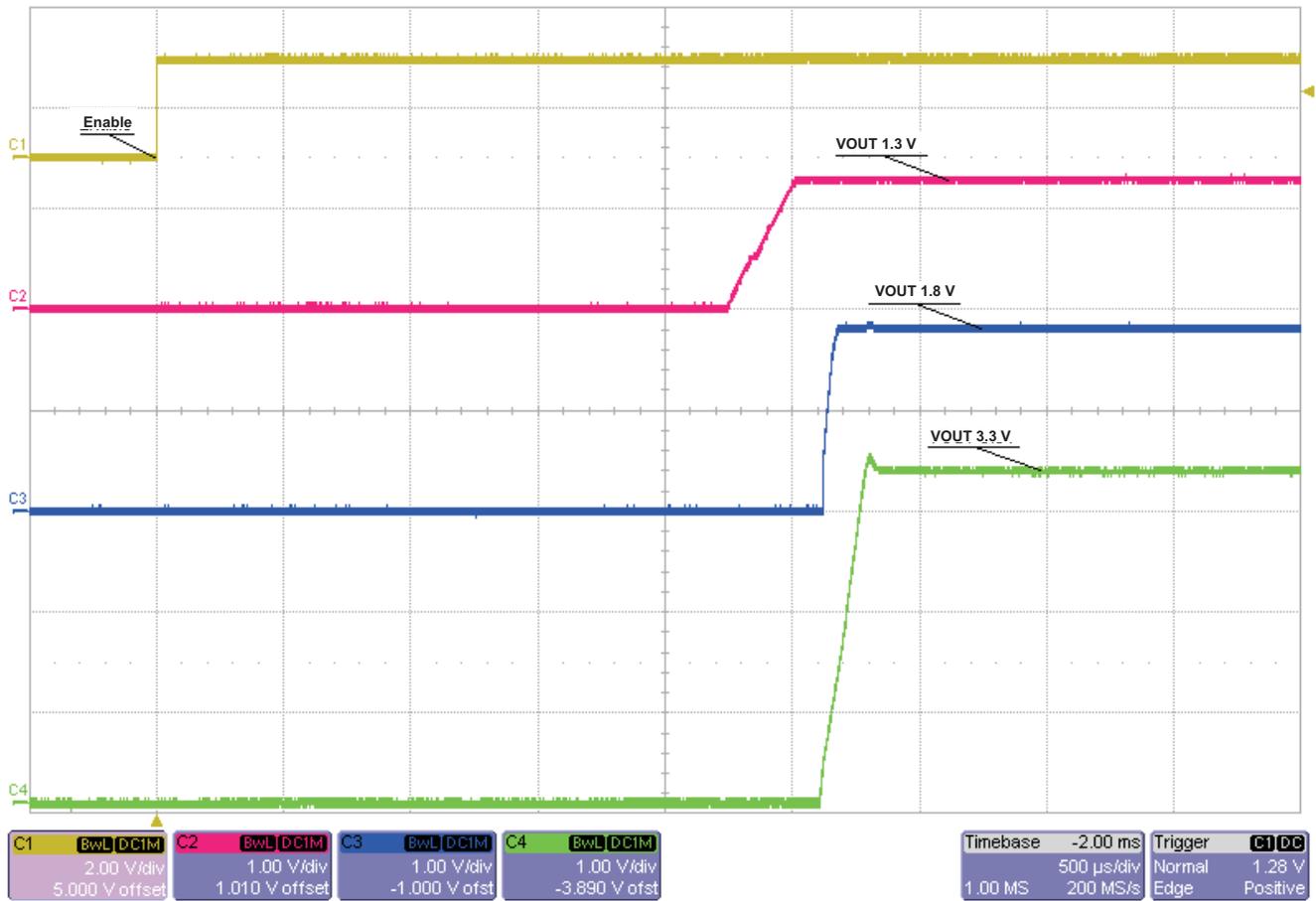


Figure 2. Power Up With 2-V Input and ENABLE Voltage

Once ENABLE is pulled high, the 1.3-V rail comes up and the 1.8 V and 3.3 V come up together 200 ns later.

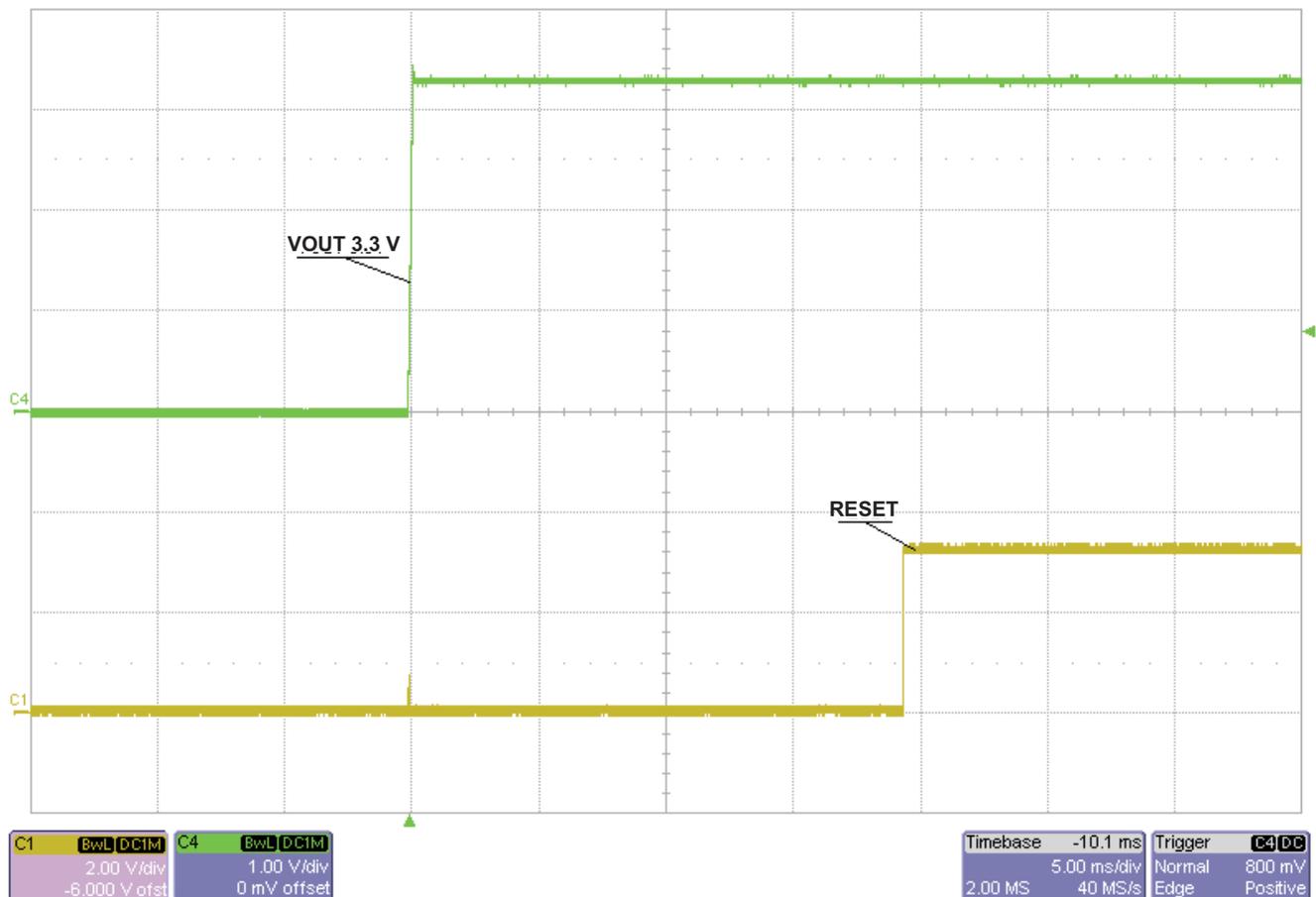


Figure 3. $\overline{\text{RESET}}$ Pin of TPS3808G33 Pulled High

The $\overline{\text{RESET}}$ pin of TPS3808G33 that supervises the 3.3-V rail is pulled high about 20 ms after the 3.3-V rail is up. Input and ENABLE voltages are 2 V.

4.2 Power Down

When ENABLE is pulled low (low is considered 0 V to 0.4 V), the ENABLE pins on the TPS72118 and TPS63001 are pulled low immediately, letting the 1.8-V and 3.3-V rails fall first. An RC circuit with a 5-ms time constant on the ENABLE of the TPS62240 keeps the 1.3-V rail up longer. The delay between ENABLE going low and the 1.3-V rail falling depends on the ENABLE voltage. With the ENABLE voltage between 1 V and 5.5 V, it is 513 ms.

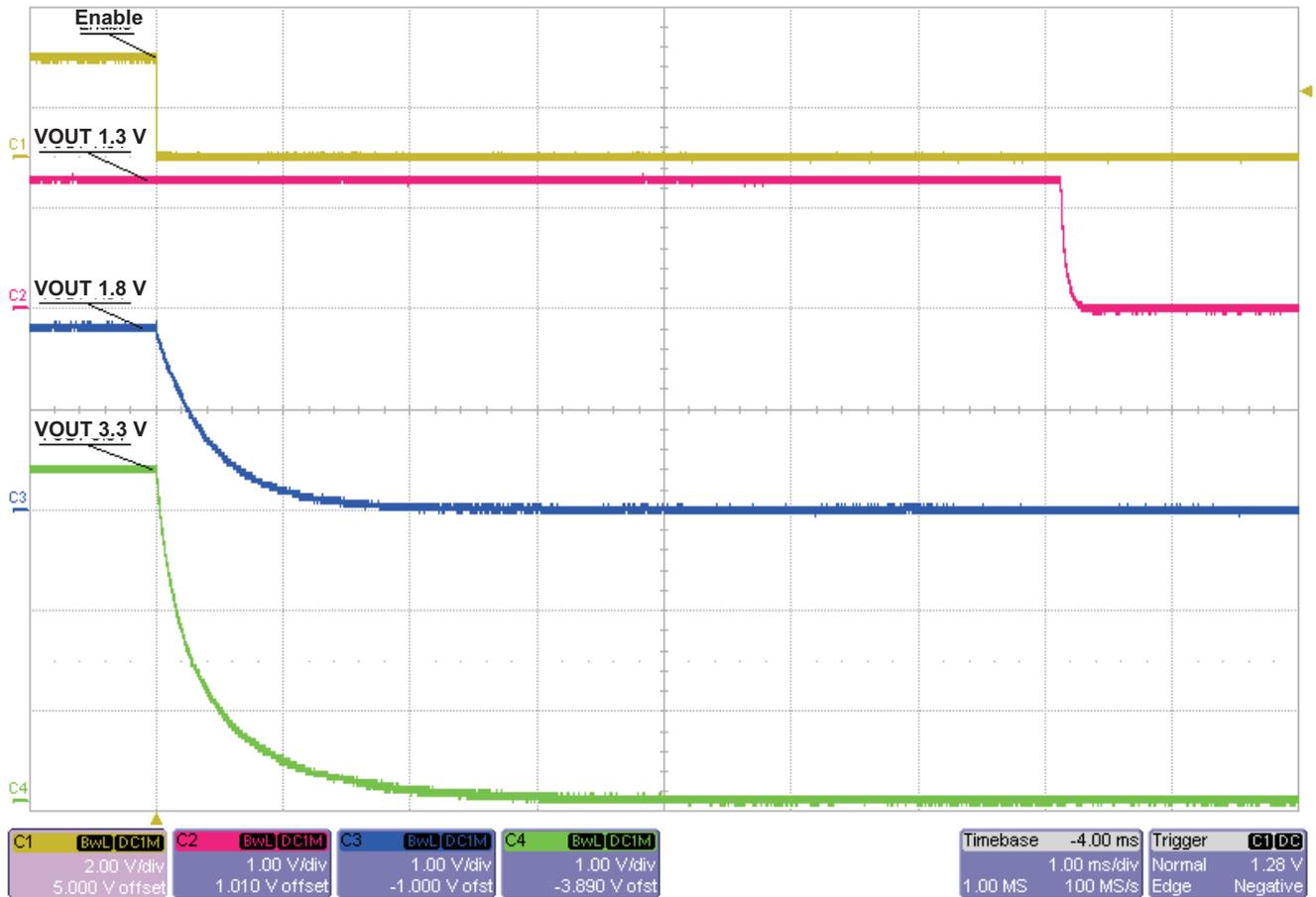


Figure 4. Power Down With 2-V Input and ENABLE Voltage

Once ENABLE is pulled low, the 1.8 V and 3.3 V come down together and the 1.3-V rail comes down 7 ms later.

4.3 Output Current

Depending on the DSP and application needs, you may need more or less current than the values given in the requirements. The maximum output currents for each rail are shown in [Table 2](#).

Table 2. Maximum Output Current

Output Voltage (V)	System Input Voltage (V)	Maximum Output Current (mA)
1.3	2 - 2.3	150
	2.3 - 5.5	300
1.8	2 - 5.5	150
3.3	2 - 3.3	800
	3.3 - 5.5	1200

Note that with VIN between 2 V and 2.3 V, only 150 mA can be attained from the 1.3-V source. However, tests at VIN = 2 V met the current and sequencing requirements outlined in the requirements section. If you plan to run the system off 2 AA batteries (1.8-V to 3-V range), consider using 3 AAA batteries (2.7-V to 4.5-V range) or Li-ion batteries (3-V to 4.2-V range). Otherwise, additional testing will be required.

4.4 Reset Delay Time

The reset delay time in this design is set to 20 ms, but the TPS3808G33 has a programmable delay time that can be programmed anywhere between 1.25 ms and 10 s. See the *TPS3808G33* data sheet for a detailed explanation.

5 Additional Waveforms

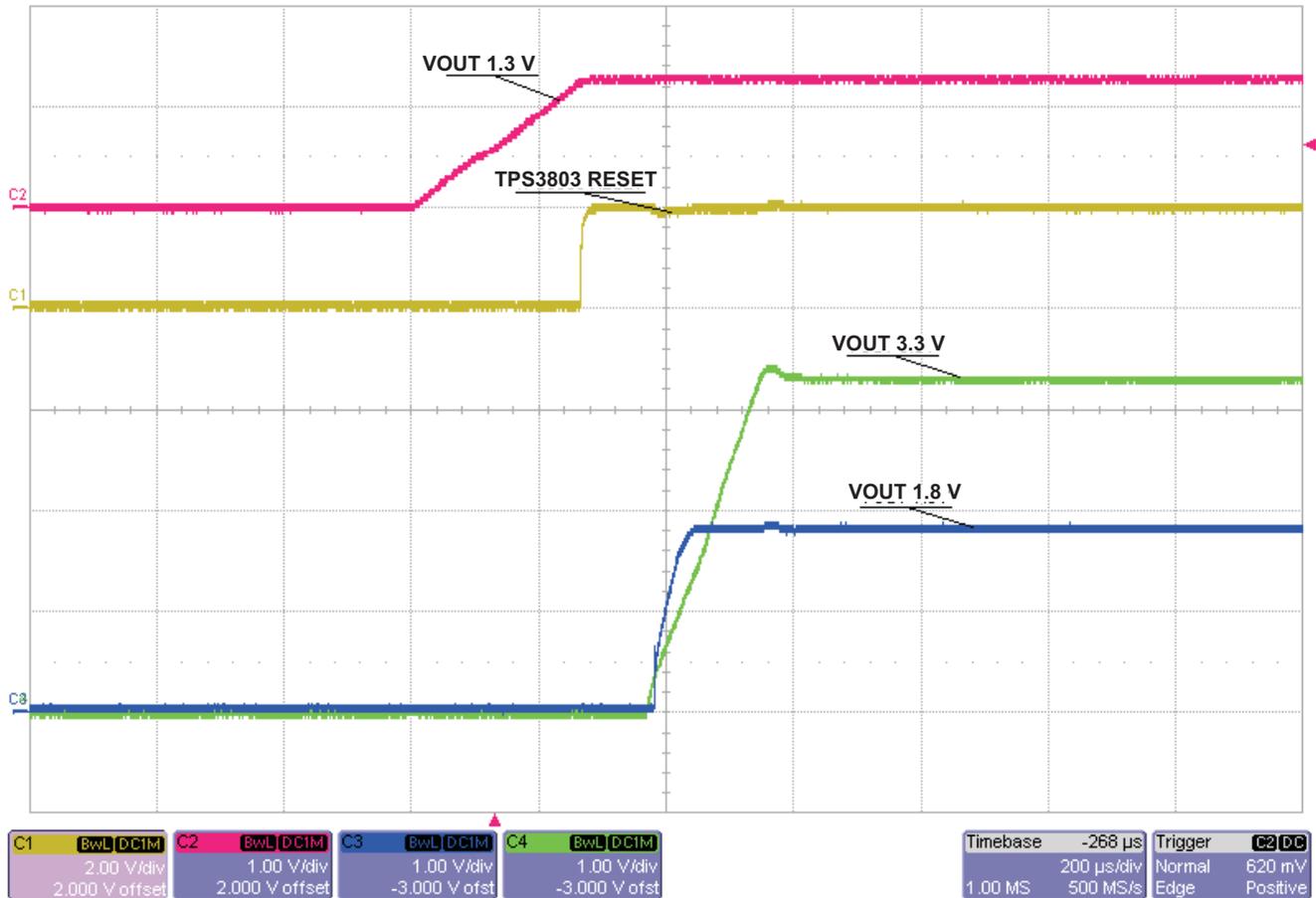


Figure 5. Power-Up Sequence Showing TPS3803-01 RESET Signal

In the power-up sequence of [Figure 5](#), the TPS380-01 RESET signal enables the 1.8-V and 3.3-V rails. The input and ENABLE voltages are 2 V.

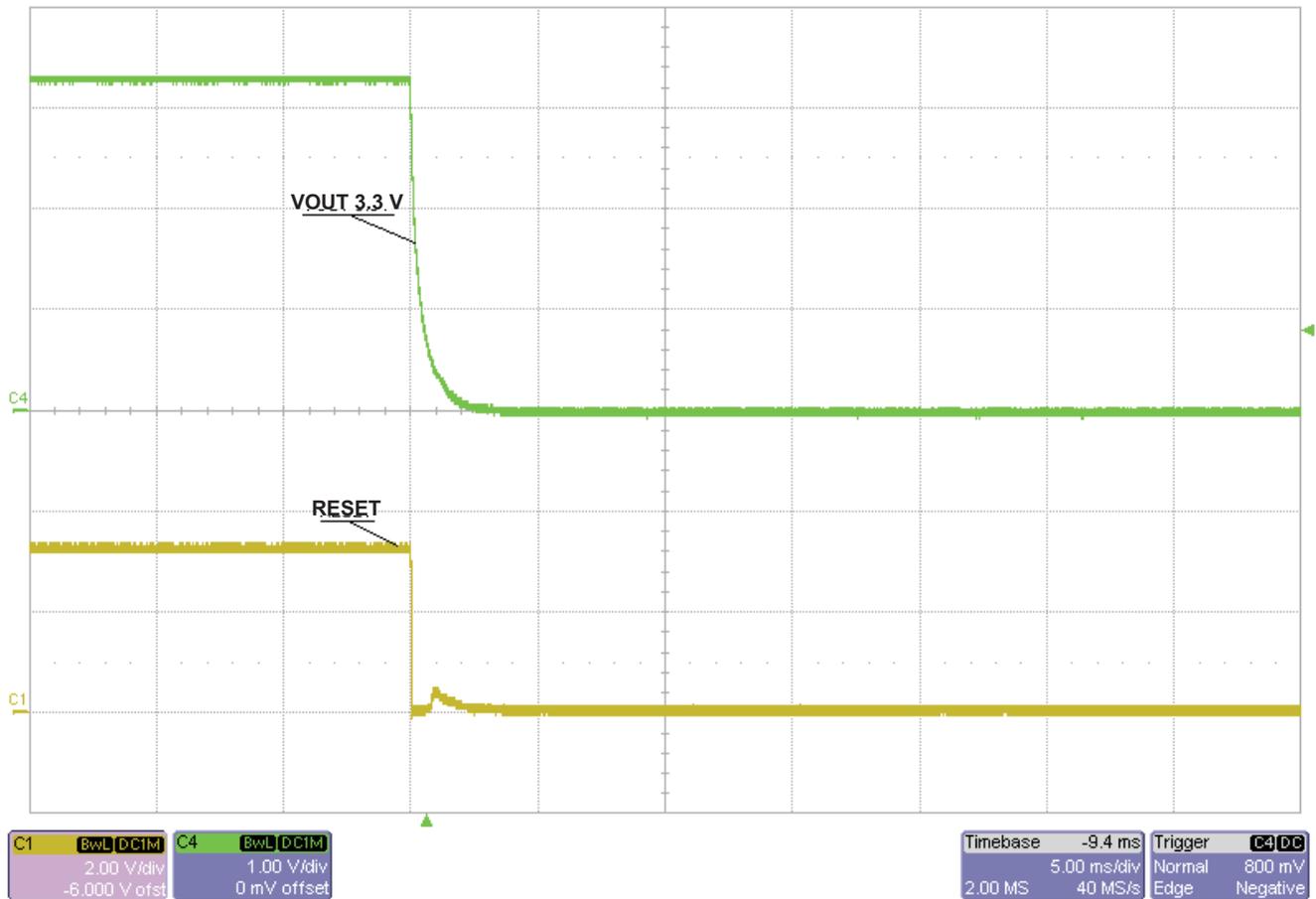


Figure 6. Power-Down Sequence Showing TPS3808G33 RESET Pin Signal

In Figure 6, the input and ENABLE voltages are 2 V.

6 Data Sheet Web Links

Part Number	Datasheet Web Link
TPS62240	http://www.ti.com/lit/gpn/tps62240
TPS3803-01	http://www.ti.com/lit/gpn/tps3803-01
TPS72118	http://www.ti.com/lit/gpn/tps72118
TPS63001	http://www.ti.com/lit/gpn/tps63001
TPS3808G33	http://www.ti.com/lit/gpn/tps3808g33

7 Schematic and Bill of Materials

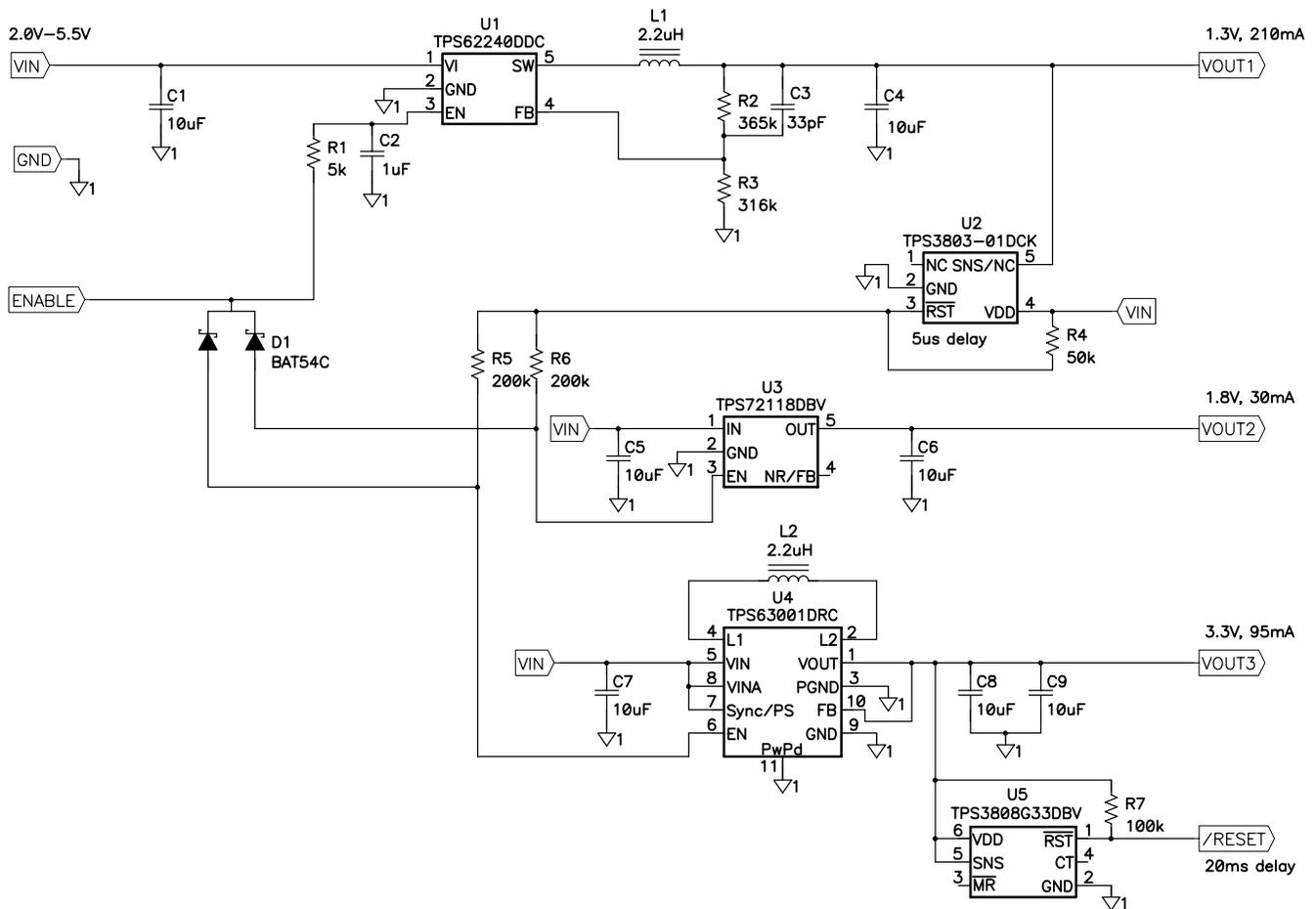


Figure 7. Schematic

Table 3. Bill of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR
7	C1, C4C9	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0603	GRM188R60J106ME47D	Murata
1	C2	1 F	Capacitor, Ceramic, 50V, C0G, 5%	0603	C1608C0G1H220J	TDK
1	C3	33 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	C1608C0G1H220J	TDK
1	D1		Diode, Dual Schottky, 200-mA, 30-V	SOT23	BAT54C	Vishay-Liteon
2	L1, L2	2.2 H	Inductor, SMT, 1.5A, 110 milliohm	0.118 0.118	LPS3015-222ML	Coilcraft
1	R1	5k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
1	R2	365k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
1	R3	316k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
1	R4	50k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
2	R5, R6	200k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
1	R7	100k	Resistor, Chip, 1.16W, 1%	0603	Std	Std
1	U1		IC, 2.25 MHz, 600 mA Step-Down Converter	SOT23-5	TPS62240DDC	TI
1	U2		IC, Voltage Detector	SOP-5 (DCK)	TPS3803-01DCK	TI
1	U3		IC, 150mA, Low Iq, Wide Bandwidth, LDO Linear Regulators	SC70	TPS71718DBV	TI
1	U4		IC, High Efficiency Single Inductor Buck-Boost Converter with 1.2A Switches	QFN10	TPS63000DRC	TI
1	U5		IC, Low Quiescent Current, Programmable vv-V, Delay Time: 1.25ms to 10s	SOT23-6	TPS3808G33DBV	TI

Table 3. Bill of Materials (continued)

Count	RefDes	Value	Description	Size	Part Number	MFR
Notes: 1. These assemblies are ESD sensitive, ESD precautions shall be observed. 2. These assemblies must be clean and free from flux and all contaminants. Use of no clean flux is not acceptable. 3. These assemblies must comply with workmanship standards IPC-A-610 Class 2. 4. Ref designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG's components.						

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated