

AN-2170 LMR24210/20 Evaluation Board

1 Introduction

The LMR24210/20 Step Down Switching Regulator features all required functions to implement a cost effective, efficient buck power converter capable of supplying up to 1.0A or 2.0A. The Constant On-Time (COT) regulation scheme requires no loop compensation, results in a fast load transient response and simple circuit implementation, this allows low component count, and consequently very small overall board space. The regulator can function properly even with an all ceramic output capacitor network, and does not rely on the output capacitor's ESR for stability.

The LMR24210/20 has a wide input range from 4.5V-42V, making it suitable for a variety of applications from automotive to power conditioning of unregulated sources. The LMR24210/20 Evaluation Board is designed to provide the design engineer with a fully functional power converter to evaluate the LMR24210/20 series of buck regulators.

2 Features

- 4.5V to 42V Input Voltage Range
- 3.3V Output Voltage (default setting)
- Up to 2000 mA Output Current (LMR24220)
- Up to 1000 mA Output Current (LMR24210)
- Switching Frequency of 500 KHz (default setting)
- PCB size: 46.8mm x 27.4mm

3 Enable Option

Install R4, R5 and D1 to enable the part at a desider input voltage. A voltage higher than 1.26V on the EN pin will enable the device. Use the EN post to disable the device by pulling this node to GND. A logic signal may be applied, to the post, to test startup and shutdown of the device. Leaving the EN pin open will enable the device at internal UVLO level.

4 Adjusting the Output Voltage

The output voltage can be changed from 3.3V to another voltage by adjusting the feedback resistors using Equation 1:

$$V_{OUT} = V_{FB}(1+(R1/R2))$$

(1)

1

Where V_{FB} is 0.8V.

For more information on component selection and features, see the LMR24210 SIMPLE SWITCHER® 42Vin, 1.0A Step-Down Voltage Regulator (SNVS738) and LMR24220 SIMPLE SWITCHER 42Vin, 2.0A Stp-Dwn V-Reg in micro SMD (SNVS737) data sheets.

SIMPLE SWITCHER is a registered trademark of Texas Instruments. All other trademarks are the property of their respective owners.



Adjusting the Output Voltage

www.ti.com



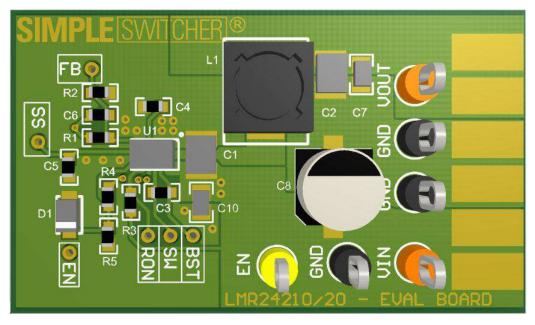


Figure 1. Top View

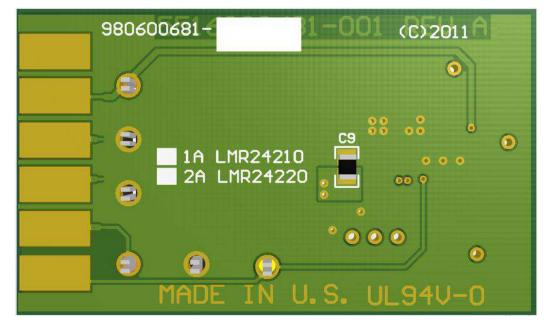

Bottom View

 



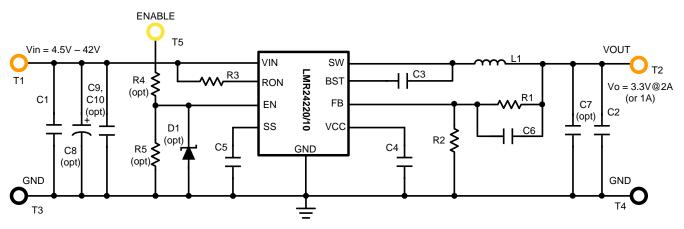


Figure 3. LMR24210/20 Evaluation Board Schematic

Designation	Description	Size	Manufacturer Part #	Vendor
C1	Cap 10µF 50V X5R	1210	UMK325BJ106MMT	Taiyo Yuden
C2	Cap 47µF 10V X5R	1210	GRM32ER61A476KE20L	Murata
C3,C5,C6	Cap 0.01µF 100V X7R	0603	06031C103MAT2A	AVX
C4	Cap 1µF 10V X5R	0603	C0603C105K8PACTU	Kemet
R1	RES, 31.6k ohm, 1%, 0.1W	0603	CRCW060331K6FKEA	Vishay
R2	RES, 10.2k ohm, 1%, 0.1W	0603	CRCW060310K2FKEA	Vishay
R3	RES, 49.9k ohm, 1%, 0.1W	0603	CRCW060349K9FKEA	Vishay
L1	Shielded Inductor 8.2µH 2.53A		DR74-8R2-R	Colitronics
U1	IC LMR24210/20	28-ball DSBGA	LMR24210/20	TI
R4,R5	optional			
C7,C8,C9,C10	optional			
D1	optional			
T1,T2	test point (orange)	Keystone5013		
T3,T4	test point (black)	Keystone5011		
T5	test point (yellow)	Keystone5014		

Table 1. Bill of Materials (BOM) LMR24210/20

5 Optional components

R4,R5 set the input voltage level at which the device is enabled.

D1 is a zener diode that clamps the voltage on the EN pin. A 5.1V zener is suggested.

C7 is an additional output capacitor.

C8 is an input bulk capacitor. The bulk capacitor should be located near the Power-supply connection point. The purpose of the bulk capacitor is to overcome the inductive effects of bench wiring.

C9,C10 are additional input capacitors.



Test Setup


6 Test Setup

Step	Description	Notes
1	Connect a power supply to V _{IN} terminals	V _{IN} range: 4.5V to 42V
2	Connect a load to V _{OUT} terminals	I _{OUT} range: 0A to 2.0A (or 1A)
3	EN should be left floating for normal operation. Short this to ground to shutdown the part	
4	Turn on V_{IN} with 0A load applied, check V_{OUT} with a voltmeter	Nominal 3.3V
5	Apply a 2.0A (or 1A) load and check V_{OUT}	Nominal 3.3V


Table 2. Demonstration Board Quick Setup Procedures



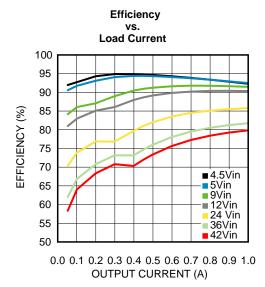
7 Typical Performance Characteristics for LMR24210




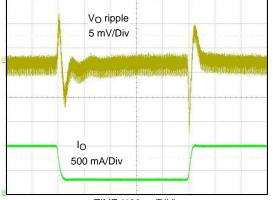Load Transient Waveforms 300mA to 1A, 12V_{IN}




TIME (100 µs/DIV)

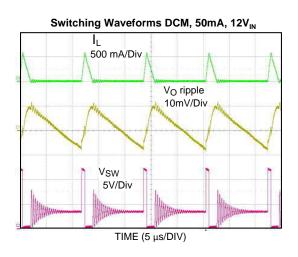

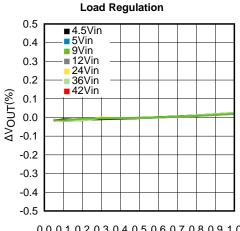


0.0 0.1 0.2 0.3 0.4 0.5 0.6 0.7 0.8 0.9 1.0 **OUTPUT CURRENT (A)**

Switching Waveforms CCM, 1A, 12V_{IN}

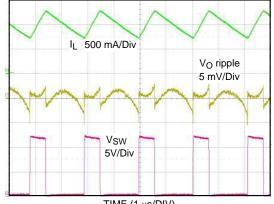


TIME (1 µs/DIV)

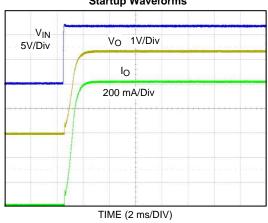


Startup Waveforms

SNVA495A-November 2011-Revised April 2013 Submit Documentation Feedback

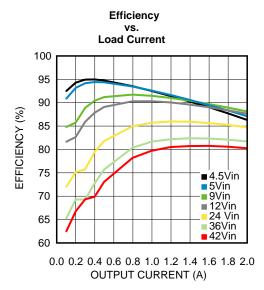
8 Typical Performance Characteristics for LMR24220



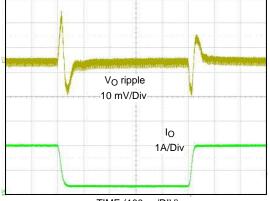
Load Transient Waveforms 300mA to 2A, 12V_{IN}




TIME (100 µs/DIV)

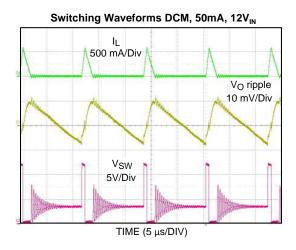


AN-2170 LMR24210/20 Evaluation Board

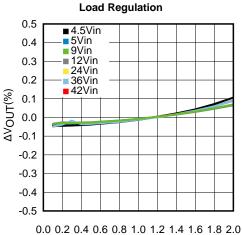

OUTPUT CURRENT (A)

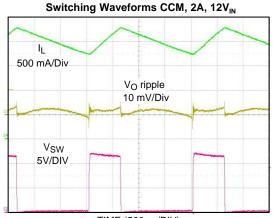

TIME (500 ns/DIV)

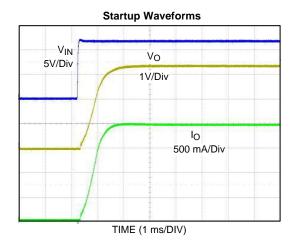



9 Layout

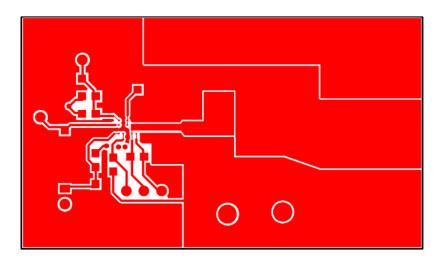


Figure 4. Top Layer

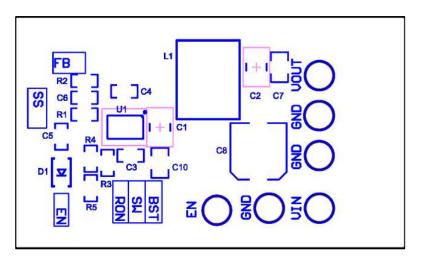


Figure 5. Top Silkscreen

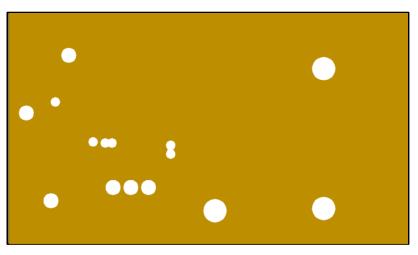


Figure 6. Mid Layer 1



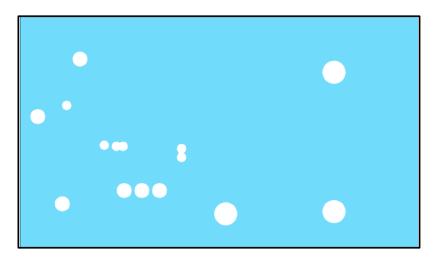


Figure 7. Mid Layer 2

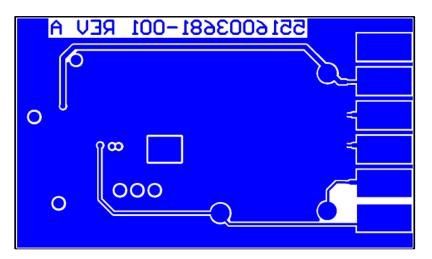


Figure 8. Bottom Layer

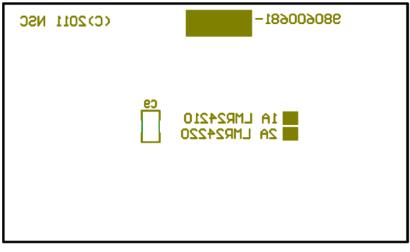


Figure 9. Bottom Silkscreen

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications		
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive	
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications	
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers	
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps	
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy	
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial	
Interface	interface.ti.com	Medical	www.ti.com/medical	
Logic	logic.ti.com	Security	www.ti.com/security	
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense	
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video	
RFID	www.ti-rfid.com			
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com	
Wireless Connectivity	www.ti.com/wirelessconnectivity			

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2013, Texas Instruments Incorporated