

LP3970

Powering Applications Processors with a Multifunction Integrated Power Solution



Literature Number: SNVA546

Technology Edge

Powering Applications Processors with a Multifunction Integrated Power Solution

Alan Moore, Marketing Engineer, Portable Power Systems

Power consumption and battery life are major obstacles that system designers have to consider when designing for portable battery-operated systems. One system that requires sophisticated power management to achieve maximum battery life is one that incorporates a high-performance applications processor. An example is Intel's PXA27x XScale® applications processor. This device requires up to 12 different power domains for the processor, IOs and internal subsystems to function with peak performance and optimized efficiency. Intel's PXA27x processor has multiple power-supply inputs which can be turned on and off as demanded by the CPU's power management software. Its flexible power management architecture controls the selection of the internal and external peripherals that can be powered at any given time.

Flexible Integration

National has developed an integrated power solution, the LP3970 Flexible Power Management Unit, for Intel's XScale high-performance power architectures. The LP3970 provides an integrated power management solution that can supply power to support 10 independent low-noise, lowdropout LDOs, two DC-DC buck regulators, a backup battery charger for both Lithium-Ion (Li-Ion) and Lithium Manganese (Li-Mn) coin-cell batteries, and a dedicated regulator for the real-time clock (RTC) function - all integrated in a single 48-pin, thermally enhanced Leadless Lead-frame Package (LLP). The LP3970 automatically switches from main to backup battery when the preset battery empty voltage is reached. And, the LP3970 interfaces with the PXA27x processor via the simple two-wire I2C-compatible bus and four additional General Purpose Outputs (GPOs).

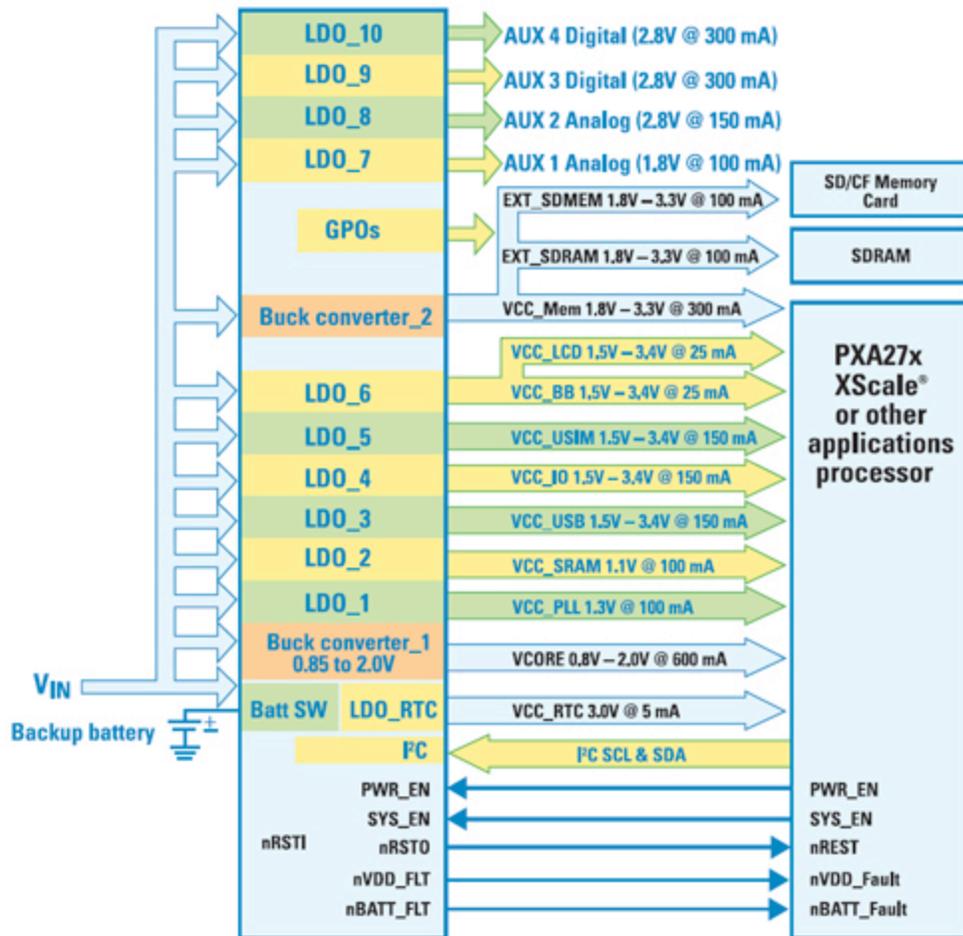


Figure 1. LP3970 Application diagram

Variable-Controlled Voltage Buck Regulators

One major feature integrated into Intel's PXA27x is their dynamic voltage management (DVM). Intel's DVM and dynamic frequency management allow continuous changes to system voltage and frequency, depending on the core load requirements, without interrupting the CPU. Thereby, additional tools are provided in the developer's library to achieve better balance between performance and battery life. For the LP3970 to achieve dynamic voltage management within the PXA27x processor, Buck converter_1 of the two programmable buck regulators will drive the dynamic input for the processor core, which needs an input varying from 0.85V to 1.7V. The internal power manager programs the required core voltage for the specified frequency. The step-size increment of 50 mV can then be programmed via the I2C-compatible bus. Buck converter_2 meets the power requirements of internal peripheral logic blocks such as the memory controller, LCD controller, digital audio, and the serial ports for the PXA27x. The programmable voltage range for Buck converter_1 is 0.8V to 2V, which should provide power for a wide range of applications. Buck converter_2, with its programmable output voltage range of 1.8V to 3.3V, is designed for other high-current peripherals (i.e. internal processor memory, external SRAM, etc.). Programming can be initiated by the PXA27x host processor via the I2C-compatible bus with a series of commands to the LP3970, running at either at 40 kHz (standard mode) or at 400 kHz (fast mode) using the standard 7-bit addressing.

Additional Buck Features

The buck regulators can deliver up to 650 mA each, depending upon the external inductor, and the input and output voltages by using synchronous rectification with the internal FETs and voltage mode control. Each buck regulator can also operate up to a 100% duty cycle for low-dropout control of the output voltage. As a result, power efficiency of 90% or higher is achieved. Additional features for the buck regulators include softstart and both current and thermal overload protection. The buck regulators operate in PWM mode when the current loads are 70 mA or greater. With lighter current loads, the buck regulators automatically switch to PFM mode when the following two conditions occur. These two conditions are when the inductor becomes discontinuous and when the PMOS switch current drops below the current level of less than (66 mA +

VIN/160W).

The PXA27x processor outputs two hard-wired power control signals directly to the PMIC. The two control signals are system enable (SYS_EN), which controls the high-voltage supplies, and power enable (PWR_EN), which controls the low-voltage supplies from the LP3970 to the PXA27x. Installation of a backup battery for the first time begins the initial cold-start, power-up sequence, which enables its internal power management unit and one oscillator.

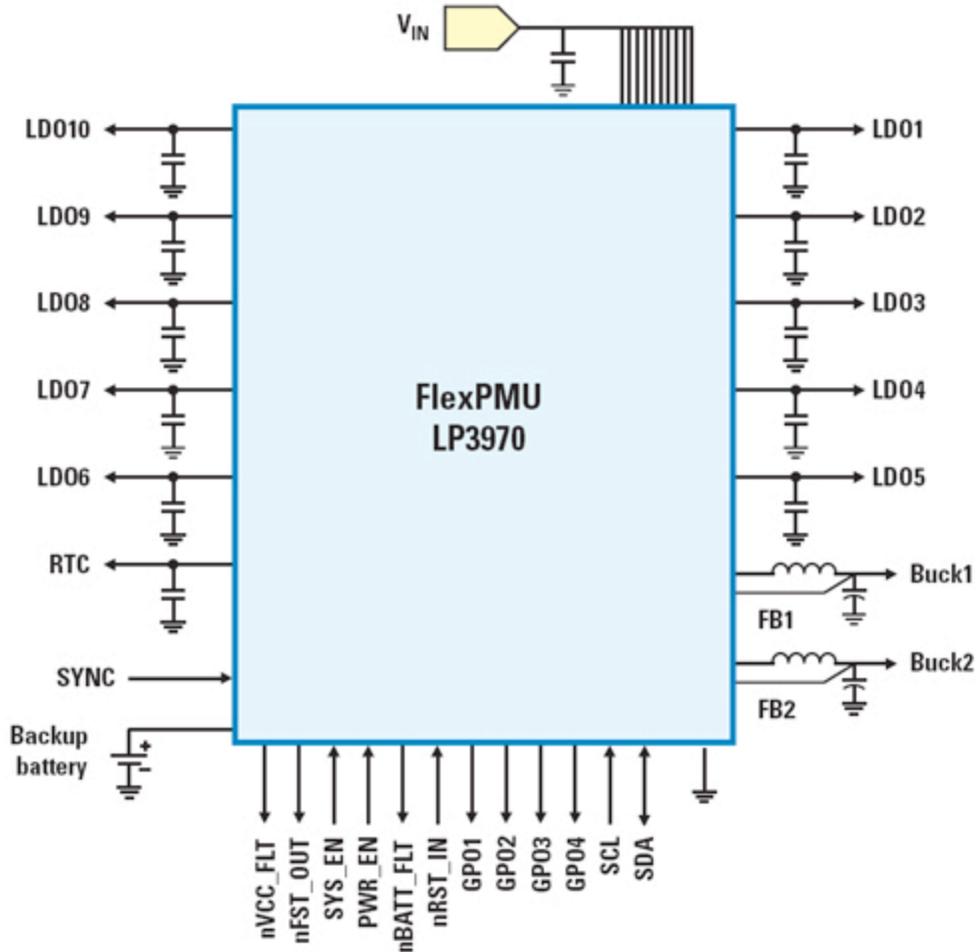


Figure 2. LP3970 functional schematic

Backup Battery Charger

With the integrated backup battery charger, the LP3970 automatically switches from the main battery to a backup coin-cell battery or super capacitor. Further, the switch happens when the main battery is removed or its voltage is too low. The backup battery continues to power the LDO_RTC until the main battery is recharged or replaced. When the main battery is available, the battery switch connects the main battery to the LDO_RTC and the backup battery charger starts charging the backup battery when the system voltage is above 3.4V. The battery charging current can be programmed via the I2C-compatible interface.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated