

How Much Loading Can an Auto-polarity RS-485 Bus Support?



The RS-485 interface is popular because of its robustness; the use of differential signaling effectively rejects common-mode noise on the bus. To make the communication work, the transceiver and receiver have to match the pins: A to A and B to B. In some RS-485 applications, however, the bus polarity information might not be available on the receiver ends or the polarity could be mistaken.

Auto-polarity RS-485 transceivers like the SN65HVD888 and THVD1505 can detect the bus polarity automatically so that the two bus wires can be connected during installation either way. For example, the A pin of the device can be connected to any one of the two bus wires and B pin can be connected to the other wire. Using this configuration reduces costs and helps increase system reliability. The bus polarity feature could be beneficial for systems with high installation rates, such as IP cameras, E-meter, air conditioning and lighting. In the event that the RS-485 connection is installed backwards, the device can self correct the polarity instead of requiring an installation team to revisit the site and correct the error.

The mechanism of auto-polarity detection relies on generating enough voltage difference on the idle bus in the system using bias resistors, R_{FS} and R_{T2} , shown in [Figure 1](#).

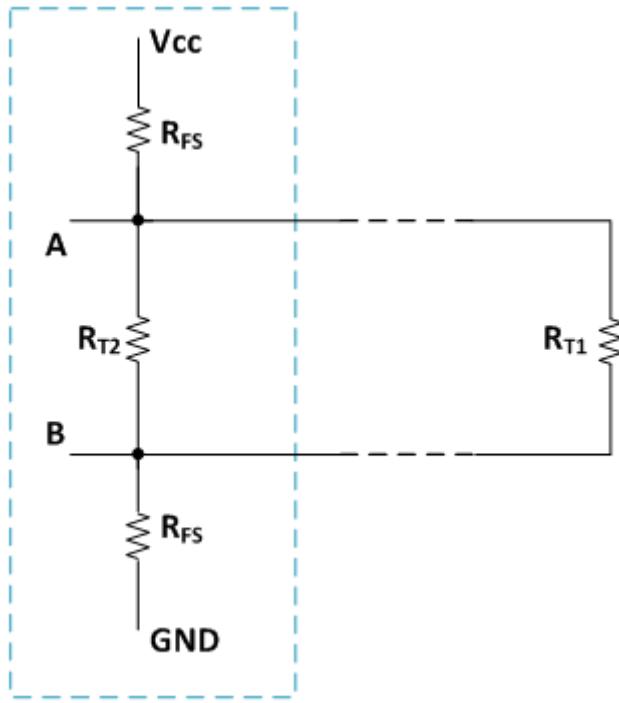


Figure 1. Auto-polarity RS-485 Bus Network

Because designing this bias (fail-safe) network is sometimes not as straightforward as it looks, in this post I'll apply two equations to make the calculations. After the resistor values are fixed, I will show the network's impact on the loading condition of the system.

To design a proper fail-safe network, you need to meet two fundamental conditions. First, the equivalent resistance of the network, R_{FS} and R_{T2} , needs to be equal to the characteristic impedance of the cabling. In this setup, this value is presented by the termination resistor value of the bus, R_{T1} . Secondly, the voltage

generated on the idle bus should be bigger than the input threshold voltage, V_{it} , of the receiver. Provided with the first condition, the voltage drop on R_{T2} from the network itself should be twice the voltage required. In other words, the calculation is only based on the resistors in the dotted blue box of [Figure 1](#), excluding R_{T1} .

From the first condition, you can redraw the network by connecting the virtual ground, V_{cc} and GND, of R_{FS} together ([Figure 2](#)).

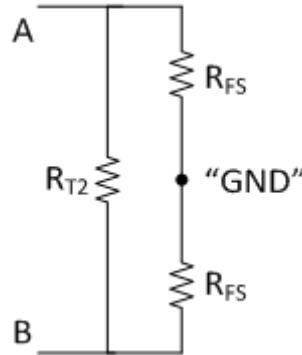


Figure 2. Equivalent Circuit of a Fail-safe Network

By doing this, you can easily calculate the equivalent resistance using Equation 1:

$$R_{T1} = \frac{1}{\frac{1}{R_{T2}} + \frac{1}{2R_{FS}}} \quad (1)$$

From the second condition, suppose that the minimum V_{cc} is 4.5 V and V_{it} is 100 mV. You can also include 50 mV of noise margin on top of V_{it} (Equation 2):

$$2(V_{it} + V_{noise}) = V_{cc} \frac{R_{T2}}{R_{T2} + 2R_{FS}} \quad (2)$$

Now that you have two equations with two variables, you can put them together using Equation 3:

$$R_{FS} = R_{T1} \frac{V_{cc}}{4(V_{it} + V_{noise})} = 120 \frac{4.5}{4 * 0.15} = 900\Omega \quad (3)$$

From here, it's easy to deduce the value of R_{T2} . In this example, it is 128 Ω .

After you have obtained all resistor values, you can evaluate their impact on the system. In the RS-485 standard, 375 Ω represents the maximum loading of the bus (R_{INEQ} in [Figure 3](#)), or (1/375) S in conductance. Assume the bus voltage is 1 V. This means that the most leakage current the bus can take is about 2.67 mA single-ended.

RS-485 specifies a term of unit load (UL) to represent a load impedance of approximately 12 k Ω . If each node has a 96 k Ω input resistance (1/8 UL), it would take 256 nodes to generate equivalent leakage. 900 Ω R_{FS} takes 1.11 mA away from the total current budget (the blue arrow in [Figure 3](#)). Therefore, the nodes on the bus can have a maximum leakage of 1.56 mA (the red arrow in [Figure 3](#)). 1.56 mA divided by 104 μ A (1 V/96k Ω) is equal to 149 nodes.

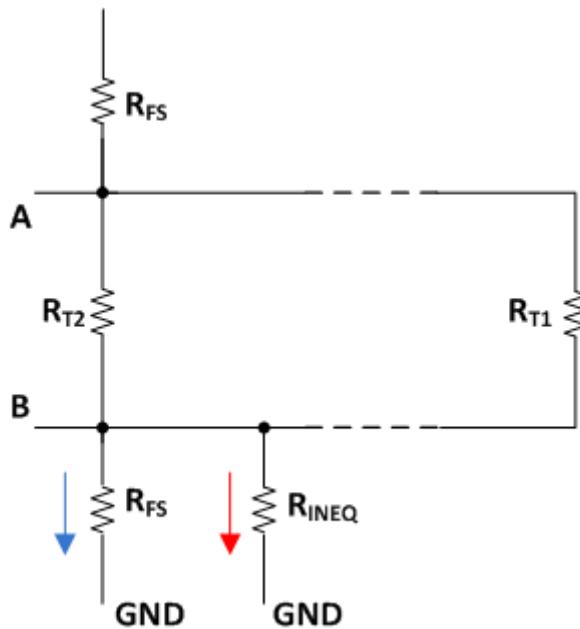


Figure 3. Auto-polarity RS-485 Bus Network Showing Loading Conditions

A proper fail-safe network for SN65HVD888 shows that the bus can support up to 149 1/8UL nodes with the network.

Additional Resources

- Read the Analog Design Journal article, “[RS-485: Passive failsafe for an idle bus](#).”

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated