

Ripple Reduction Techniques for Sensitive and Dynamic Rails in Automotive Camera Modules



Luis Cordova

When you test the video feed from your newly designed camera module, have you ever noticed slow-moving bars, discoloration or flickering in your video, or no video at all?

There can be many different reasons for video issues like these: switching noise from a switcher, voltage ripple during frames or rows, elevated system temperature, or even damage to an imager. In this blog post, I will address three design techniques that reduce voltage ripple caused by load steps from an imager and image signal processor (ISP) using the [Automotive 1MP Camera Module Reference Design with YUV422 Output, FPD-Link III and Power Over Coax](#) and [Automotive 1MP Camera Module Reference Design with YUV422, FPD-Link III and 4V-36V Power Over Coax](#). Below is the block diagram for the 4-36V Power Over Coax camera module reference design. Previous design approaches for camera modules only included considerations for just the imager. However, introducing an ISP created a new set of challenges.

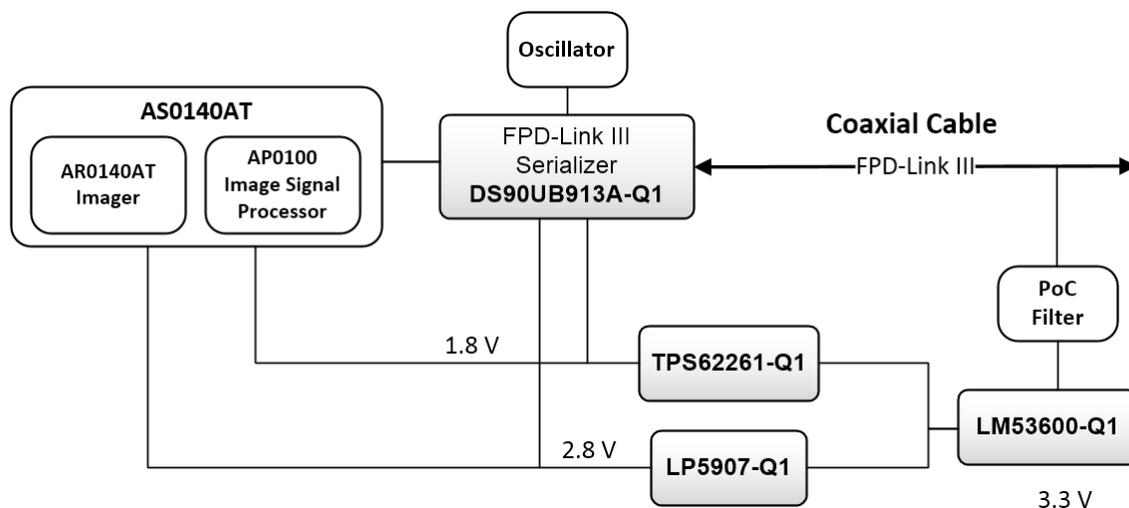


Figure 1. Automotive 4V-36V Power over Coax Reference Design Block Diagram

Because of frame and row transitions, the dynamic loading of both the imager and ISP can create considerable voltage ripple on the analog rails. For example, during the transition to a new frame or row, the current draw resembles a load step, requiring 100-200mA during a row or frame and 10-20mA during row or frame dead time. [Figure 2](#) shows the actual 2.8V rail load current waveform in yellow, and the 2.8V rail voltage ripple in pink. [Figure 2](#) was taken on the first revision. I had to address this unexpected ripple.

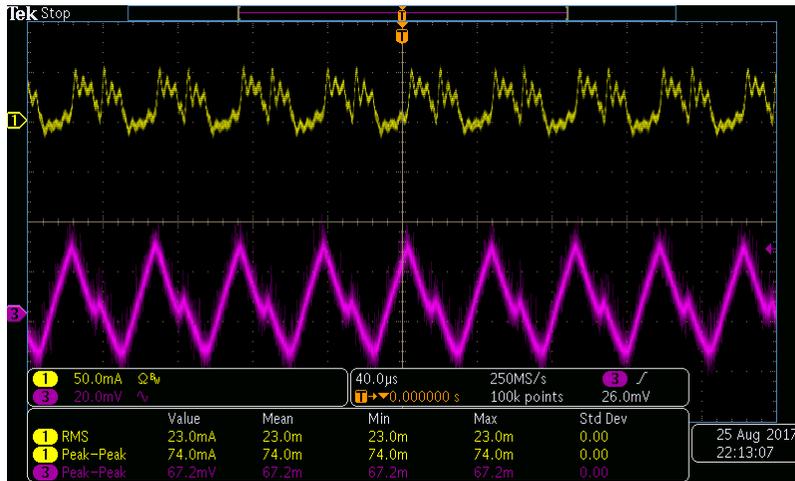


Figure 2. 60mV_{P-P} Voltage Ripple Caused by the Dynamic Loading of a 2.8V Rail

Figure 3 and Figure 4 are oscilloscope screenshots that show the fast Fourier transform (FFT) of the load-current waveforms for 2.8V and 1.8V rails, respectively. I measured the load current waveforms by replacing ferrite beads between the supply and rail decoupling capacitors with a loop of wire, and then placing a grounded current probe on that wire.

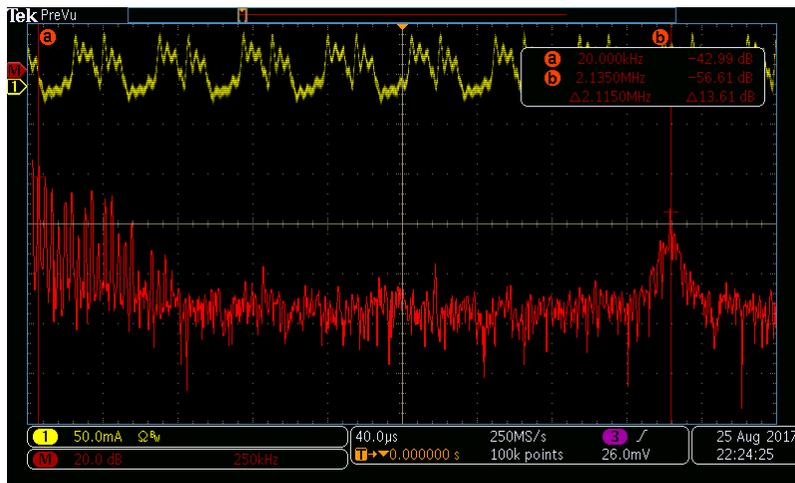


Figure 3. FFT of a 2.8V Load Current



Figure 4. FFT of a 1.8V Load Current

Note the differences in magnitude of frequency content close to DC, spanning up into the 400kHz range, between the 2.8V load-current waveform in [Figure 3](#) and the 1.8V load-current waveform in [Figure 4](#). The spike around 2MHz comes from the switching frequency of the buck converters.

The first approach I'll discuss will be the use of ferrite beads. While you probably already know that ferrite beads are used to isolate noise or reduce high frequency noise, there are some cases where ferrite beads between the voltage rail and supply can exacerbate voltage ripple, in some cases doubling the voltage ripple at the imager.

Row and frame rates occur at frequencies closer to DC (22.4-44.8kHz, 30-60Hz typical, respectively), and the loading within each row and frame requires fairly dynamic currents. These load steps occur so quickly that practical power supplies cannot recover before the next load step. Even in testing, common programmable load test equipment can only provide load steps as fast as 15kHz. The originally recommended ferrite bead had a considerable DC resistance of 500mΩ. The dynamic load current through this resistance will create voltage that is closely predicted by $V = IR$, and may resemble something like [Figure 5](#). If a ferrite bead is used, it should have low DCR to most effectively reduce this low frequency voltage ripple while mitigating high frequency noise as originally intended.

[Figure 5](#) and [Figure 6](#) are oscilloscope shots that show the effect of ferrite-bead removal on the 2.8V analog rail.



Figure 5. 2.8V Voltage Ripple with Ferrite Bead – 35.2mV_{P-P}



Figure 6. 2.8V Voltage Ripple without Ferrite Bead – 11.2mV_{P-P}

The second approach is to ensure tight current loops between the power supplies and the imager rails, which reduces ripple by minimizing current-loop and parasitic trace inductance.

In order to benefit from this approach, place supplies as close to the imager rails as practically possible. Unless vias for both power and ground paths are in close proximity and viewed as a pair, the loop inductance can be

much higher and introduce a larger-than-normal voltage ripple. [Figure 7](#) shows the recommended vias in the PCB view of the camera module design. These vias are circled.

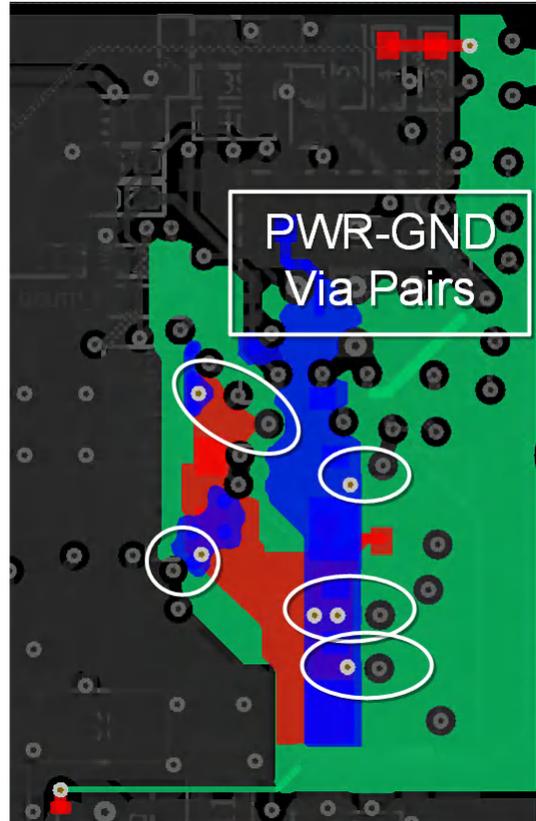


Figure 7. Example of Power-ground via Pairs from the Automotive 4V-36V Power over Coax Reference Design

When mechanical housings or form-factor requirements limit power-supply placement, carefully consider the layer stack up. Placing the load and power layers close together will keep the current loop as small as possible in the z-direction between load and supply.

Like tight current loops, using power and ground planes also reduces current-loop inductance and parasitics. As camera modules get increasingly smaller, you must give power planes extra attention. When routing the many video and control signals through vias, PCB editing software automatically removes copper from power or ground planes in order to make room for these vias. Staggering signal vias and reducing the hole diameter automatically created by the software can drastically improve the continuity of power and ground planes, and in turn reduce loop inductance. [Figure 8](#) and [Figure 9](#) show the early ground plane compared to the improved ground plane.

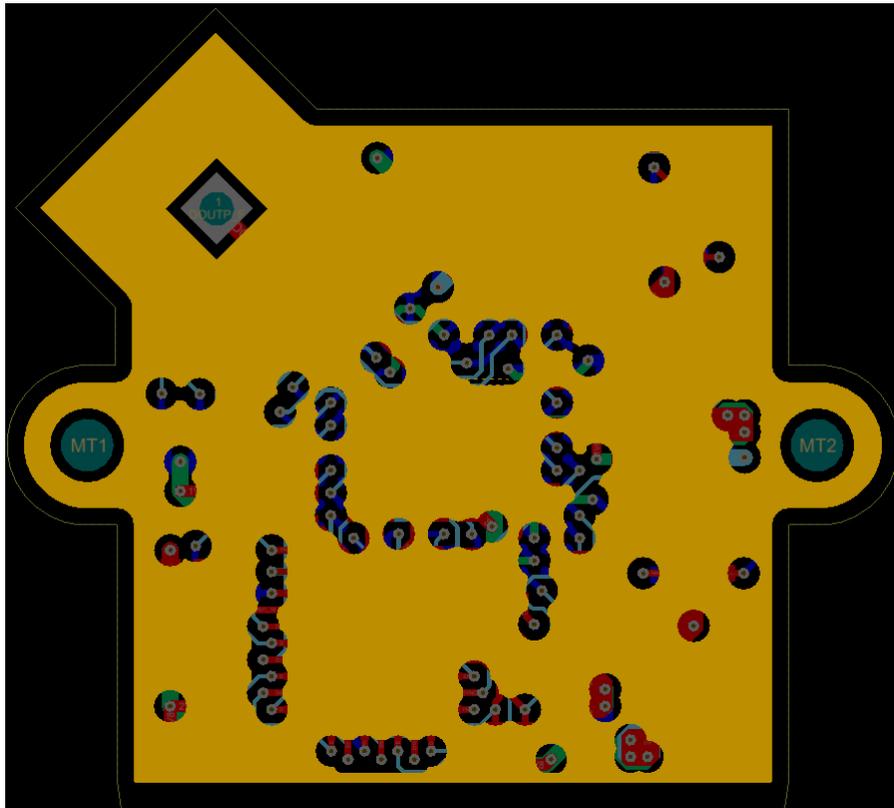


Figure 8. Revision 1 GND Layer

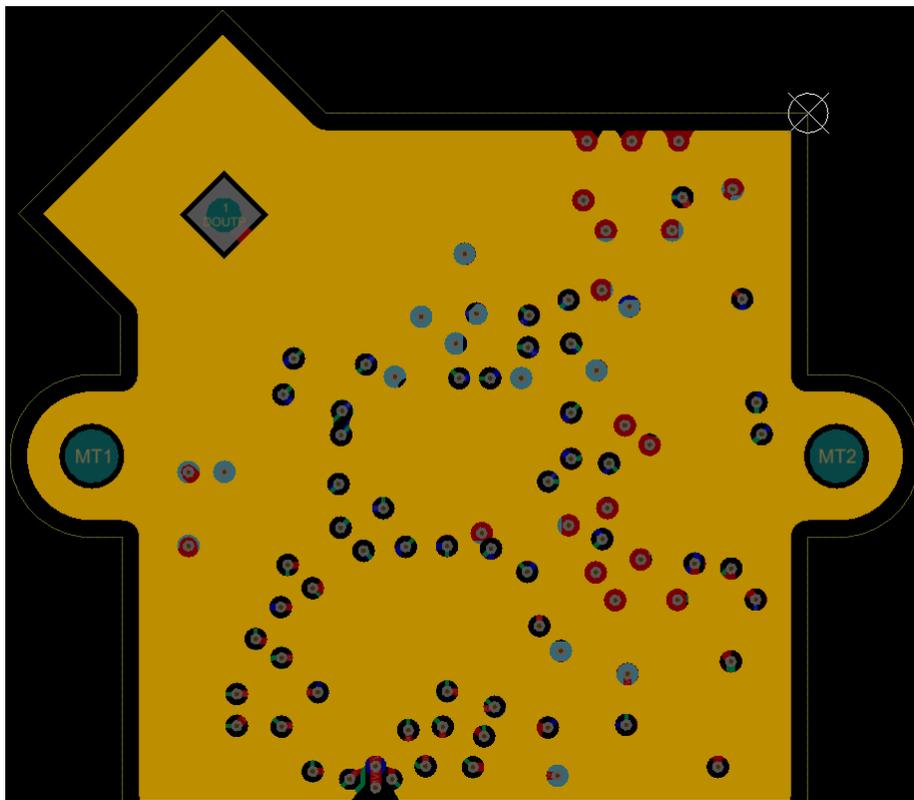


Figure 9. Final Revision GND Layer

The third and final approach is to optimize decoupling capacitors. For imager decoupling, I recommend using larger bulk capacitors such as 10 μ F, 22 μ F or 47 μ F, as these have the lowest impedance around frequencies shown in [Figure 3](#) and [Figure 4](#) with the FFT. I tested different decoupling capacitor combinations for these designs, but they were not implemented in the final revisions.

[Figure 10](#) and [Figure 11](#) show the voltage ripple on the 2.8V rails for the final revisions of both the Automotive Power Over Coax and Automotive 4V-36V Power Over Coax reference designs.

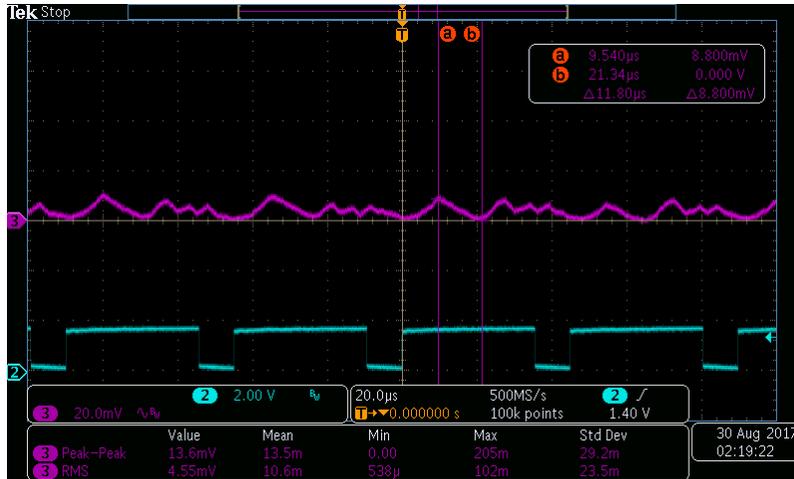


Figure 10. Automotive Power over Coax Reference Design Final 2.8V Voltage Ripple

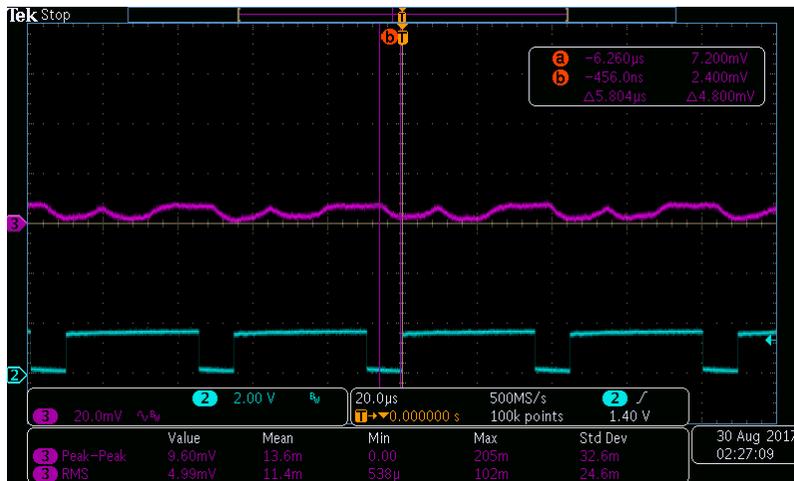


Figure 11. Automotive 4V-36V Power over Coax Reference Design Final 2.8V Voltage Ripple

The voltage ripple dropped from roughly 40-60mV_{P-P} to 5-8mV_{P-P}, improving by a factor of 8 to 10 by using these design techniques:

- Ferrite bead DCR reduction or removal
- Current loop reduction between dynamic load and supply
- Decoupling capacitor optimization

Additional Resources:

- Learn more about TI's ADAS reference designs
- Learn more about [automotive rear view camera module with integrated image processing](#)
- Learn more about [automotive front camera module with integrated image processing](#)
- Learn more about FPD-Link™ in the [Learning Center](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated