

How to Extend a Controller's Output-voltage Range



Terry Allinder

A controller is capable of regulating a maximum output voltage: for example, the [LM5140-Q1](#) regulates a maximum output voltage of 15V. Still, there are many applications where a design engineer would need a regulated voltage above this level, such as for an industrial application where the standard operating bus that provides power for programmable logic controller (PLC) and factory automation equipment is 24V.

In this post, I'll describe how to design a power supply using the LM5140-Q1 for industrial applications with a 24V output supplying 3A of load current. The LM5140-Q1 was designed for automotive applications where the required regulated output voltages are typically under 8V. With the addition of a few external components, you can use the LM5140-Q1 in industrial applications.

Before beginning the design, the following items should be considered:

- The LM5140-Q1 requires an external 5V bias supply that connects to VCCX.
- An OR'd diode configuration to the buffer amplifier is required to ensure functional operation at startup.
- The absolute maximum VCCX voltage is 6.5V.
- The VOUT pin requires a low impedance input. A resistor voltage divider with a low enough impedance may draw sufficient current that it will affect the system efficiency.
- The LM5140-Q1 internal slope compensation governs the selection of inductor and R_{SENSE} .

[Figure 1](#) shows how to configure the LM5140-Q1 to regulate voltages greater than 15V. Set V_{O1} to 5V and connect to VCCX. This disables the LM5140-Q1's internal regulator, reducing the controller's power dissipation.

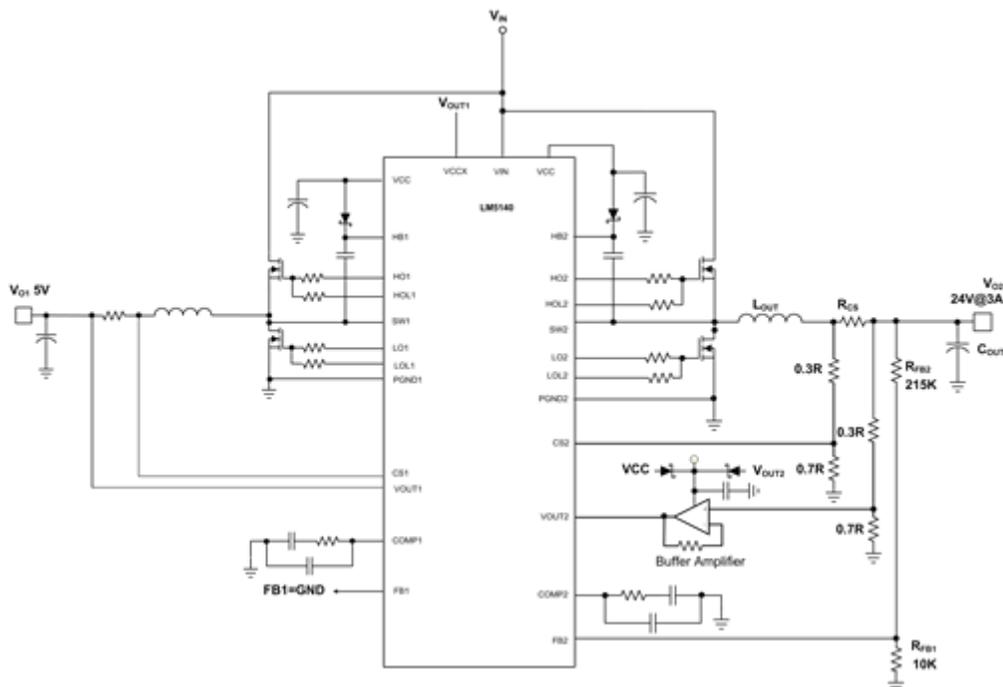


Figure 1. Schematic, LM5140-Q1 with Extended Output Range External Components

You can configure the LM5140-Q1 with adjustable output voltages using feedback resistors, or with two fixed-output voltage options without using feedback resistors. See the [LM5140-Q1 data sheet](#) for additional details.

Using Equation [Figure 2](#), set the output voltage to 24V:

$$R_{FB2} = \left(\frac{V_{O2}}{V_{REF}} - 1 \right) \times R_{FB1} \quad (1)$$

Figure 2. (1)

where: $V_{REF} = 1.2V$. See the schematic in [Figure 1](#).

I recommend a starting point for R_{FB1} between 10k Ω and 20k Ω (Equation [Figure 3](#)):

$$R_{FB2} = \left(\frac{24V}{1.2V} - 1 \right) \times 10k\Omega = 218k\Omega \quad (2)$$

Figure 2. (2)

218 k Ω is not a standard 1% resistor value so use: 215k Ω

You'll need two identical voltage dividers for sensing the differential voltage across the current-sense resistor, R_{CS} , and V_{O2} . The input to the buffer amplifier is high-input impedance and will not affect the power-supply efficiency, and the output of the amplifier is low-input impedance capable of driving the V_{OUT2} pin of the LM5140-Q1.

The LM5140-Q1 CS pin has an absolute maximum voltage rating of 15V. In order to prevent violation of the absolute maximum rating, you'll use a resistor divider network to reduce the voltage at the CS pin. Use the same divider ratio to reduce the voltage sensed at the input to the buffer amplifier to ensure that the same voltage is sensed at V_{O2} . The common-mode voltage of the buffer amplifier needs to be rated above the voltage seen at its inputs with respect to ground. In this case, the common-mode voltage needs to be above $(0.7R/1R) \times 24V = 16.8V$.

Either V_{O1} or V_{O2} – or both – can use the external circuit described. Use an external bias supply to provide power to the LM5140-Q1 VCCX pin.

To calculate the output inductor, L_{OUT} , use the following design steps starting with Equation [Figure 4](#), which assumes a 30% inductor-ripple current:

$$L_{OUT} = \frac{F_{SW}}{LX} \quad (3)$$

$$L_{OUT} = \frac{24V}{440kHz \times 1} = 54.5\mu H$$

Figure 2. (3)

where LX is 1.0 +/-0.25 and F_{SW} is the LM5140-Q1's oscillator frequency (440kHz).

Thus, I selected a 55 μH inductor for this application.

Lower inductor values increase the peak-to-peak inductor current, minimize size and cost, and improve transient response. However, lower inductor values reduce efficiency due to higher root mean square (RMS) currents.

Higher inductor values decrease the peak-to-peak inductor current and increase efficiency. You may need larger output capacitors to meet a given transient-response requirement.

$$D = \frac{V_{O2}}{V_{IN}} = \frac{24V}{48V} = 0.5 \quad (4)$$

$$\Delta I = \frac{V_{IN} - V_{O2}}{L_{OUT}} \times \frac{D}{F_{SW}} \quad (5)$$

$$\Delta I = \frac{48V - 24V}{55\mu H} \times \frac{0.5}{440kHz} = 0.496 A$$

$$I_{pk} = I_{OUT} + \frac{\Delta I}{2} \quad (6)$$

$$I_{pk} = 3A + \frac{0.496}{2} = 3.248 A_{pk}$$

Current-sense Resistor

To calculate the current-sense resistor value, multiply the maximum output current (I_{OUT}) by 120% to ensure that the current limit does not affect full load operation: 120% of 3.248 ampere's peak (A_{pk}) is 3.89A_{pk}.

The voltage dividers attenuate the differential voltage between the CS pin and V_{OUT} pin. This affects the internal slope compensation and current-limit set point. For a 24V output, the external resistors used in the voltage dividers have a ratio of 0.7. Equation [Figure 5](#) accounts for this attenuation:

$$R_{CS} = \frac{V_{CS}}{I_{pk} \times A} \quad (7)$$

$$R_{CS} = \frac{75mV}{3.89A_{pk} \times 0.7} = 27m\Omega$$

Figure 2. (7)

where V_{CS} is the current-limit set point, which for the LM5140-Q1 is 75mV, and A is the resistive divider network attenuation factor, which is 0.7.

The LM5140-Q1 was designed for automotive applications where the required regulated output voltages are typically under 8V. With the addition of a few external components, and by using the design approach detailed in this blog, you can use the LM5140-Q1 controller in industrial applications that require higher output voltages exceeding the absolute maximum voltage ratings of the CS and V_{OUT} pins.

Additional Resources

- Open the [“LM5140-Q1 Evaluation Module User's Guide.”](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated