

Texas Instruments

FB PS LLC Test Report

HVPS SYSTEM AND APPLICATION TEAM

REVA

12/05/2014

1 General


1.1 PURPOSE

Provide the detailed data for evaluating and verifying the FB-PS-LLC.

The FB-PS-LLC is a Full bridge Phase Shift LLC reference design realized by UCD3138. The topology is same as full bridge LLC. Full bridge LLC is always selected in high power level AC/DC application, and for output voltage in control under light load, PWM mode is always selected. But there is some disadvantages in PWM mode for LLC, like hard switch, high switch frequency and high power loss. The purpose of this reference design is to find a high efficiency method for LLC under light load. Select Phase shift mode replace of PWM mode under light load is a good method.

For testing applications, cooling airflow is required.

Block Diagram

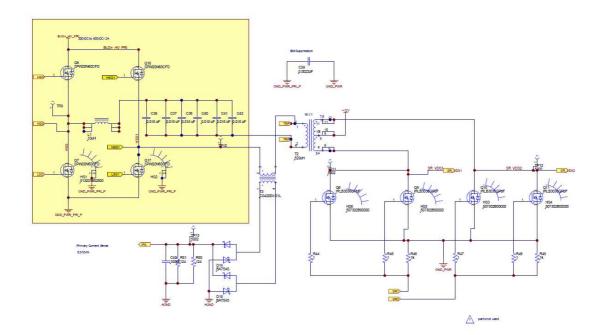

Board Photo




1.3 <u>TEST EQUIPMENTS</u>
Multi-meter:
AC Source: Chroma 61503 Load: Chroma 63202 Power Meter: WT210


Ambient Temperature at 25DegC, with Fan cooling

2 INPUT & OUTPUT CHARACTERISTICS

2.1 **Efficiency comparison**

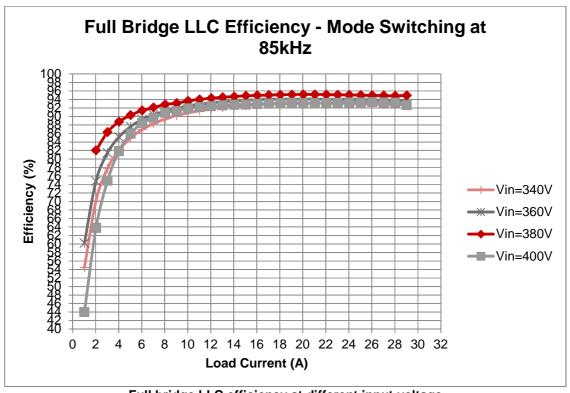


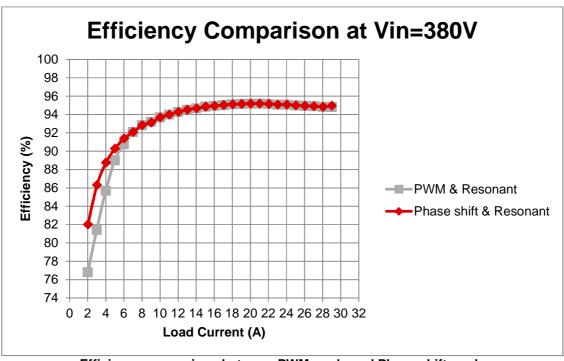
Full bridge LLC efficiency at different input voltage





Efficiency comparison between PWM mode and Phase shift mode

2.2 The ramp up waveform

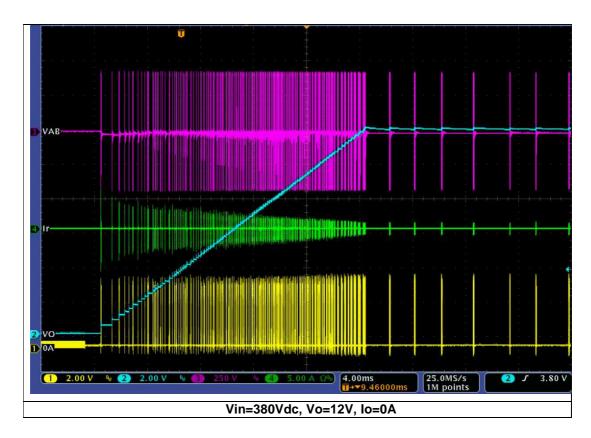

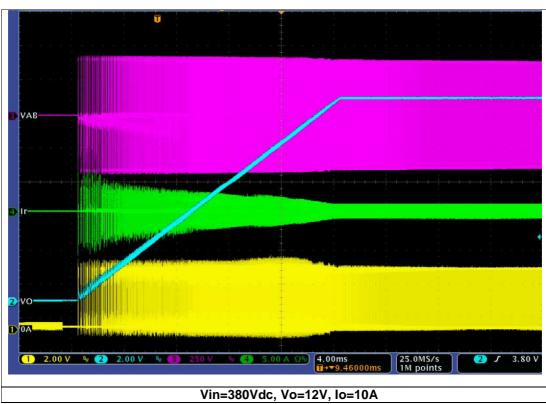


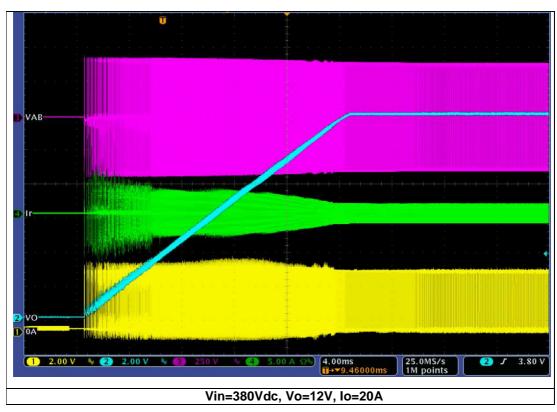

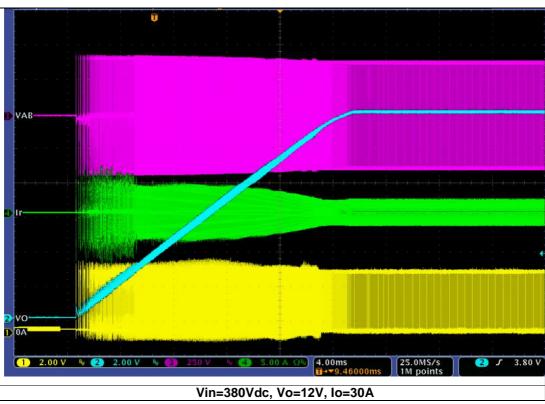




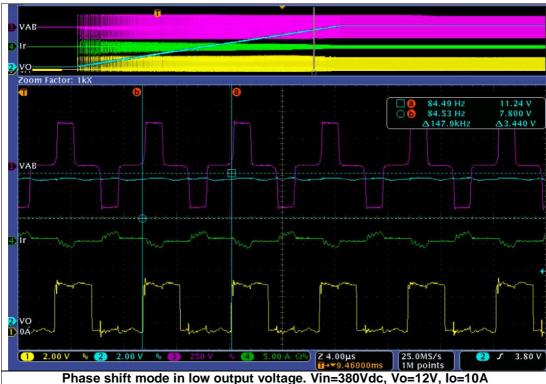
Phase shift mode in low output voltage. Vin=380Vdc, Vo=12V, Io=10A
Phase angle is very small, switch frequency is 150kHz (maximum switch frequency)




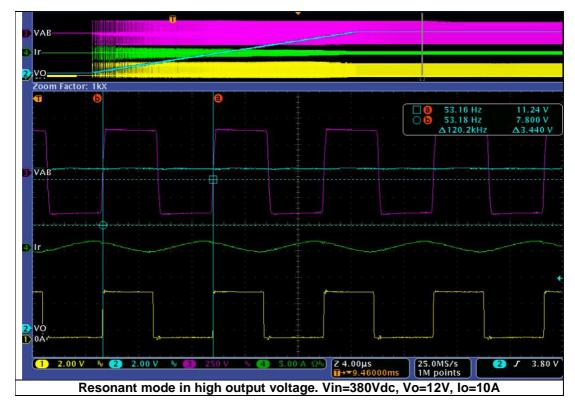
Phase shift mode in low output voltage. Vin=380Vdc, Vo=12V, Io=10A
Phase angle is increased, switch frequency is 150kHz (maximum switch frequency)





2.4 The load dynamic response Waveforms

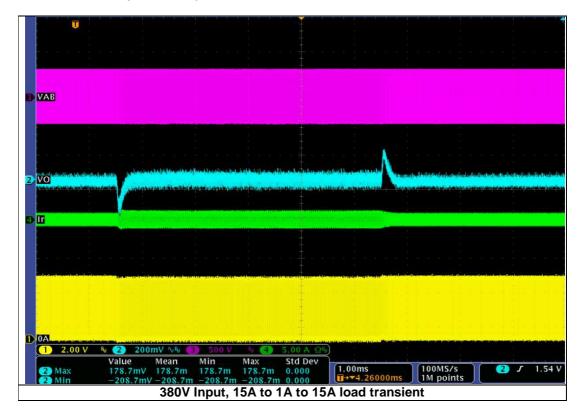


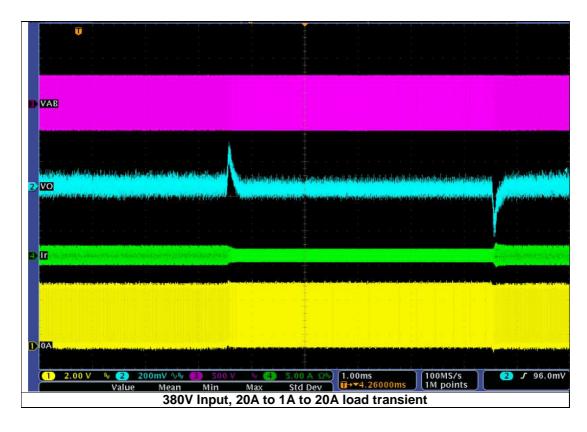


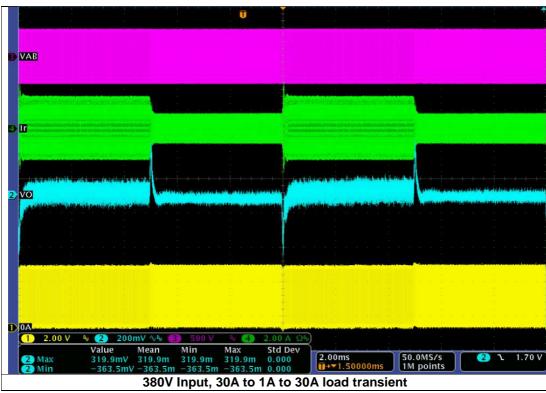

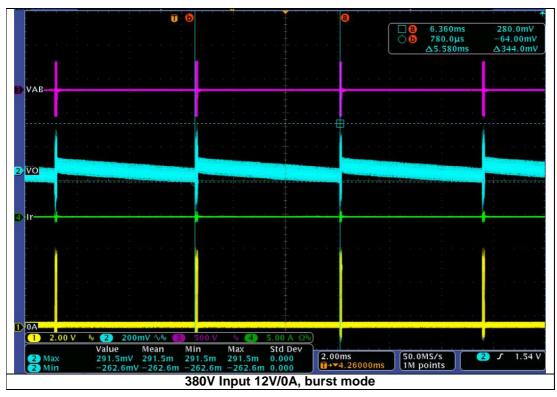

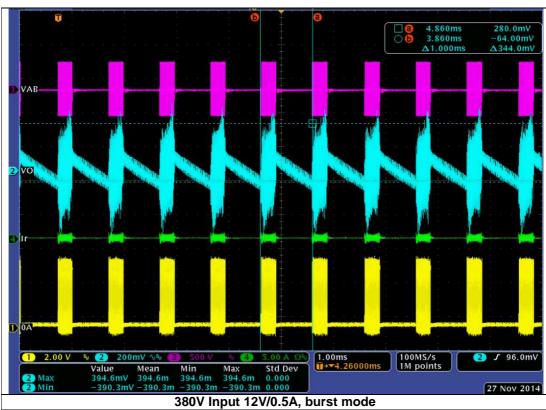

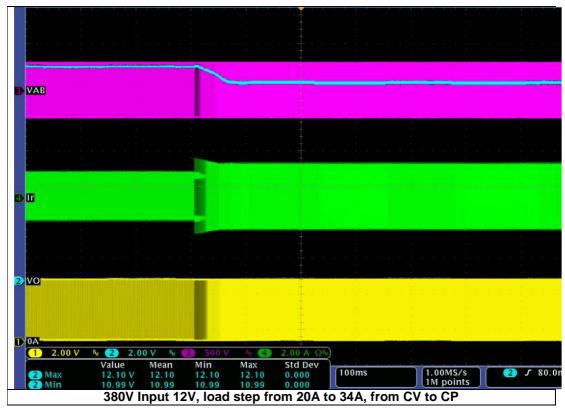

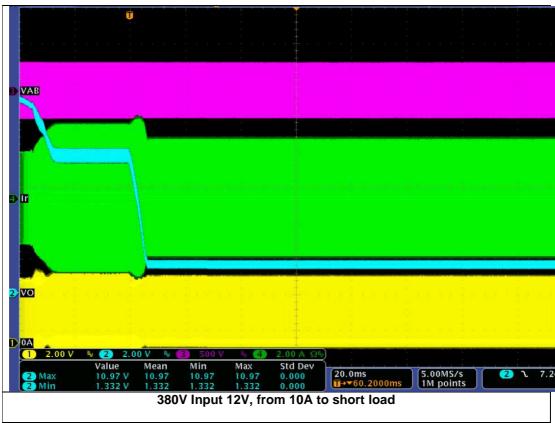



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated