



# PMP10979 4-Phase Synchronous Buck Converter Test Report 3/23/15


#### The tests performed were as follows:

- A. LM5119(x2)
  - 1. Startup
  - 2. Shutdown
  - 3. Switch
  - 4. Output Voltage Ripple (No Load and Full Load)
  - 5. Transient Response (0A to 50A Load Step)
  - 6. Efficiency
  - 7. Load Regulation
  - 8. Board Photos
  - 9. Thermal Images



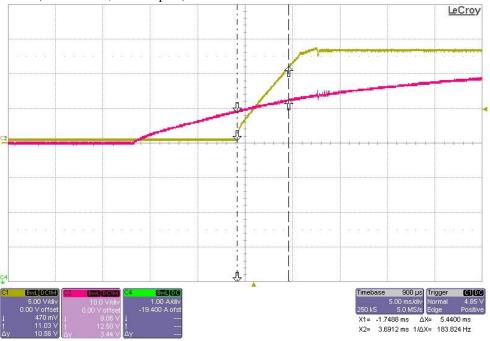
#### 1 Startup

The photos below show the startup waveforms. The input voltage is varied from 0-19V and the output is not loaded. Channel 1 – Yellow: Vout (13.5V) – (5V/Division; DC Coupled) (5msec/div) Channel 2 – Pink: Vin–(5V/Division; DC Coupled)



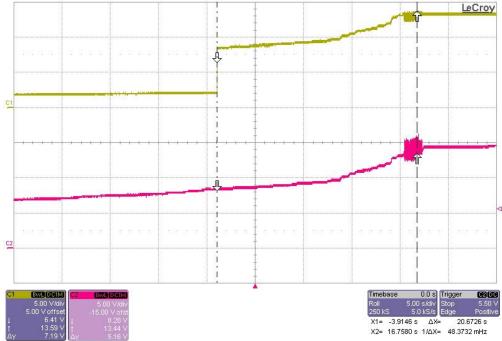13.5V Output showing rise time from 0V-11V is less than 20msec

Channel 1 – Yellow: Vout (13.5V) – (5V/Division; DC Coupled) (5msec/div) Channel 2 – Pink: Vin–(5V/Division; DC Coupled)




13.5V Output showing Vout rising with Vin.


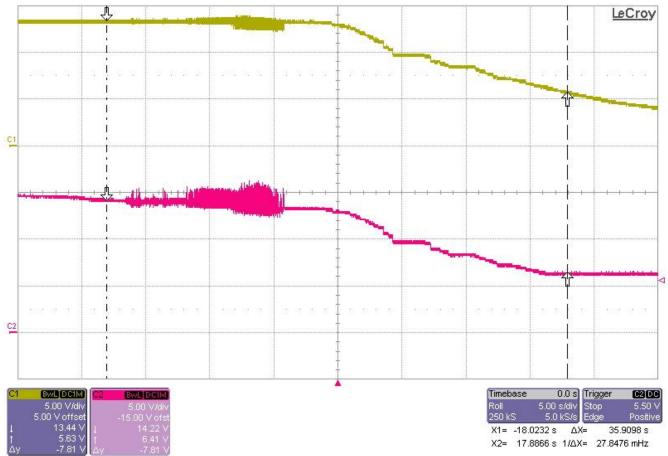
#### 2 Shutdown

The photos below show the Shutdown waveforms. The input voltage is decreased from 15V to 0V and the output is not loaded.

Channel 1 – Yellow: Vout (13.5V) – (5V/Division; DC Coupled) (5sec/div) Channel 2 – Pink: Vin–(5V/Division; DC Coupled)



13.5V Output showing Vout decreasing with Vin.




### 3 Switch Node

The pictures below show the switching waveform for the converter at full load. The input voltage is 26V.

Channel 1 – Yellow: Switch Node Phase 1 – (10V/Division; DC Coupled) (5usec/div)

- Channel 2 Pink: Switch Node Phase 2 (10V/Division; DC Coupled)
- Channel 3 Blue: Switch Node Phase 3 (10V/Division; DC Coupled)

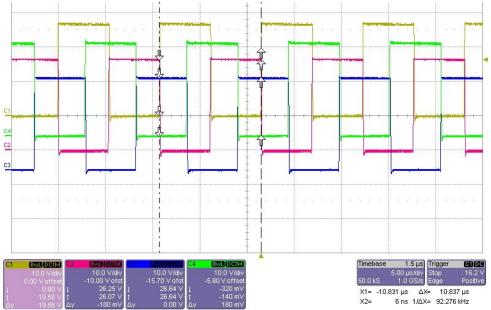
Channel 4 – Green: Switch Node Phase 4 – (10V/Division; DC Coupled)



4Phase operation; 90 deg phase shift at 50% DC;  $F_{sw} = \sim 100 KHz$ 

- Channel 1 Yellow: Switch Node Phase 1 (10V/Division; DC Coupled) (5usec/div)
- Channel 2 Pink: Switch Node Phase 2 (10V/Division; DC Coupled)
- Channel 3 Blue: Switch Node Phase 3 (10V/Division; DC Coupled)

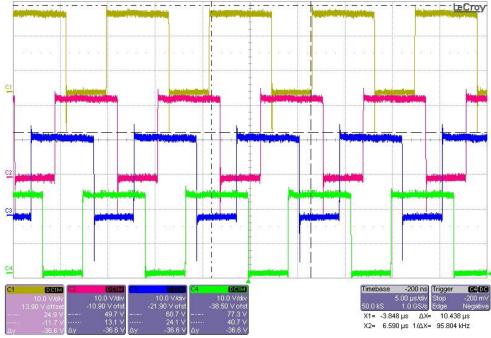Channel 4 – Green: Switch Node Phase 4 – (10V/Division; DC Coupled)




Full BW showing 36.6V pk to pk Vsw. 24Vin



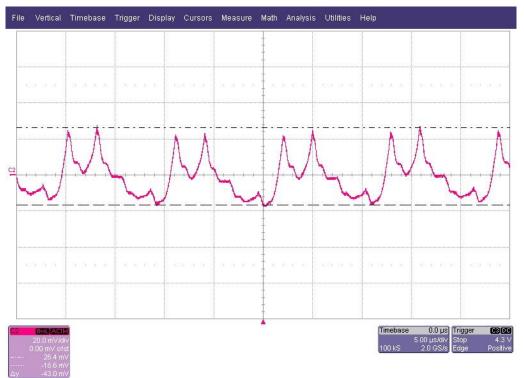
## 4 Output Voltage Ripple

The output voltage ripple of the converter is shown in the figures below. The input voltage is 24V. The time-base is set to

Channel 2 – Pink: Output Voltage – (20mv/Division; AC Coupled) (5us/div)



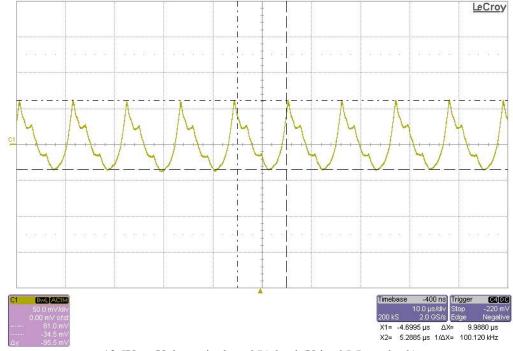13.5Vout Voltage ripple at 0A load (Vrip=43mv pk-pk) Channel 1 – Yellow: Output Voltage – (50mv/Division; AC Coupled) (5us/div)




13.5Vout Voltage ripple at 95A load (Vrip=95.5mv pk-pk)



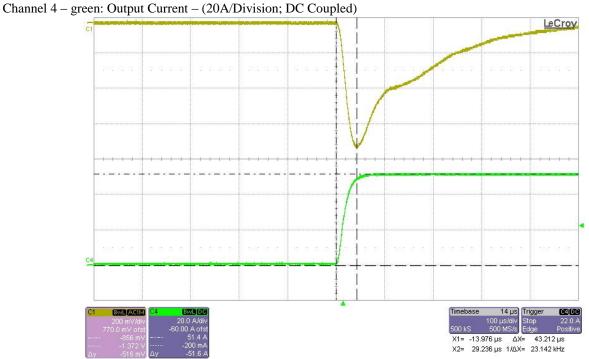
### 5 Transient Response


The transient response of the converter is shown in the figures below. The input voltage is 24V. The load is stepped from 0A to 50A. Channel 1 – Yellow: Output Voltage (AC Coupled) (100us/div)



 13.5Vout transient response showing 0A-50A load step




C1 EXERCISE C2 200 AVX -700 MV C4 -700

 


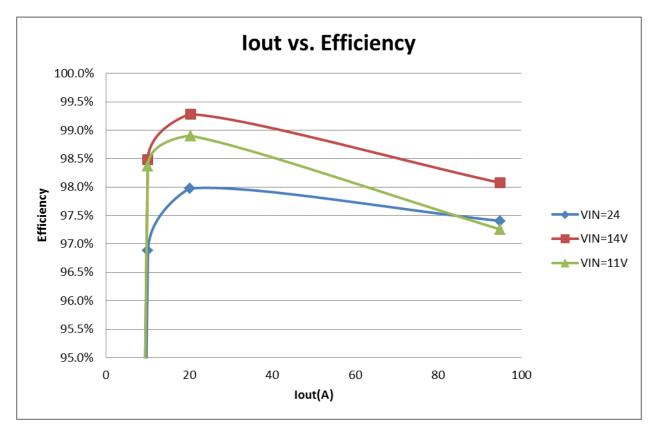
# 6 Efficiency

The efficiency of the board at its two outputs is shown in the figures below.




Vin(V)	lin(A)	Vout(V)	lout(A)	Eff(%)
23.99	0.15	13.48	0	0.00%
23.9	5.88	13.48	10.1	96.88%
23.76	11.70	13.47	20.22	97.97%
23.15	56.75	13.47	95	97.40%
14.5	0.1	13.47	0	0.00%
14.5	9.49	13.47	10.06	98.47%
14.1	19.61	13.47	20.38	99.28%
14.26	91.5	13.47	95	98.07%
11	0.1	10.82	0	0.00%
11	9.92	10.67	10.06	98.36%
10.65	19.91	10.29	20.38	98.90%
11.04	92.55	10.46	95	97.25%


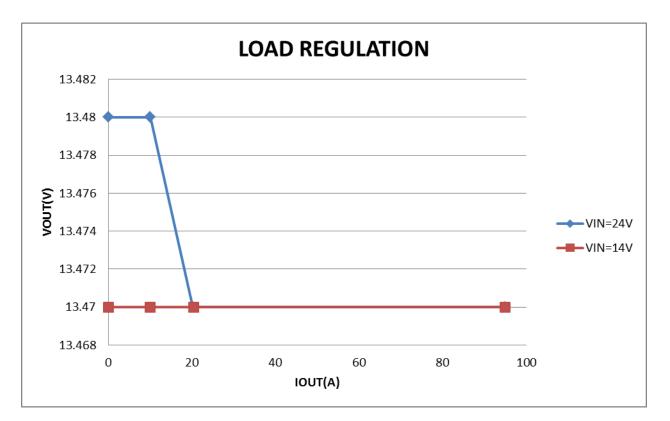
# 7 Load Regulation – (LM5119)

The load regulation of the board measured at both of the outputs with a 24V input is shown below.



Vin	Vout	lout
23.99	13.48	0
23.9	13.48	10.1
23.76	13.47	20.22
23.15	13.47	95
14.5	13.47	0
14.5	13.47	10.06
14.1	13.47	20.38
14.26	13.47	95




#### 8 Board Photo

The photos below show the PMP10979 board that is used.



Top Side

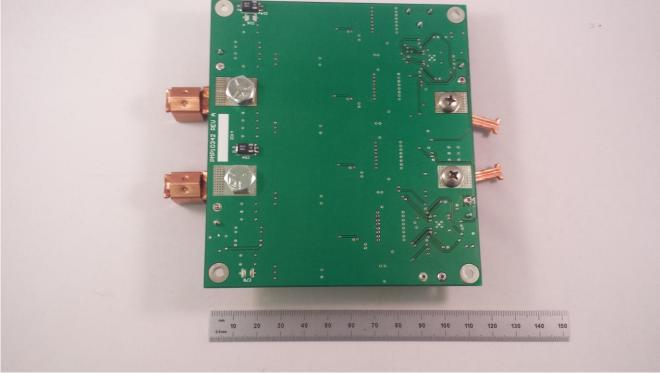


Bottom Side

9


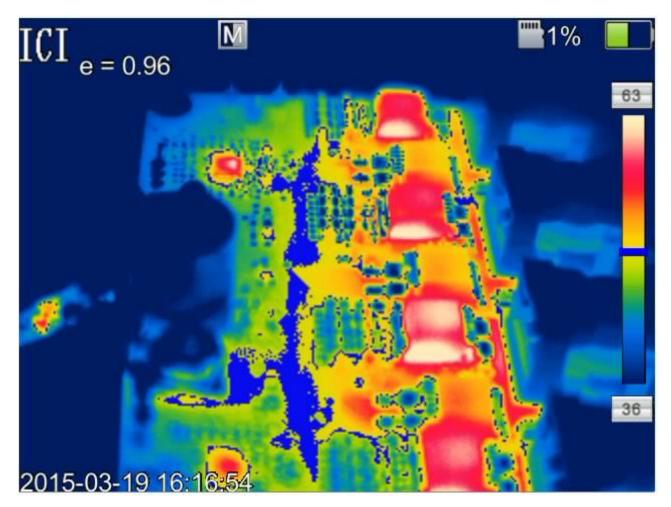
#### Thermal Images

The images below show the thermal performance of the design.



#### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated