

PMP8730RevB Test Results

1	Startup	2
2	Shutdown	3
3	Efficiency	4
4	Output Ripple Voltage	5
5	Input Ripple Voltage	5
6	Control Loop Frequency Response	6
7	Miscellaneous Waveforms	8
7.1	150R Load	8
7.2	LED Load	11
8	Thermal Image	13


Topology: LED Boost
 Device: TPS40210, for reuse go for TPS40211 and set sense resistor to 1.3 Ohm
 (here TPS40210 on customers demand)

Unless otherwise mentioned, the measurements were done with synchronization to Fsw 348kHz and the load was resistive 150Ohm, resulted in Vout 30V.


For crosschecking LED array was used, resulted in Vout approx. 20V

1 Startup

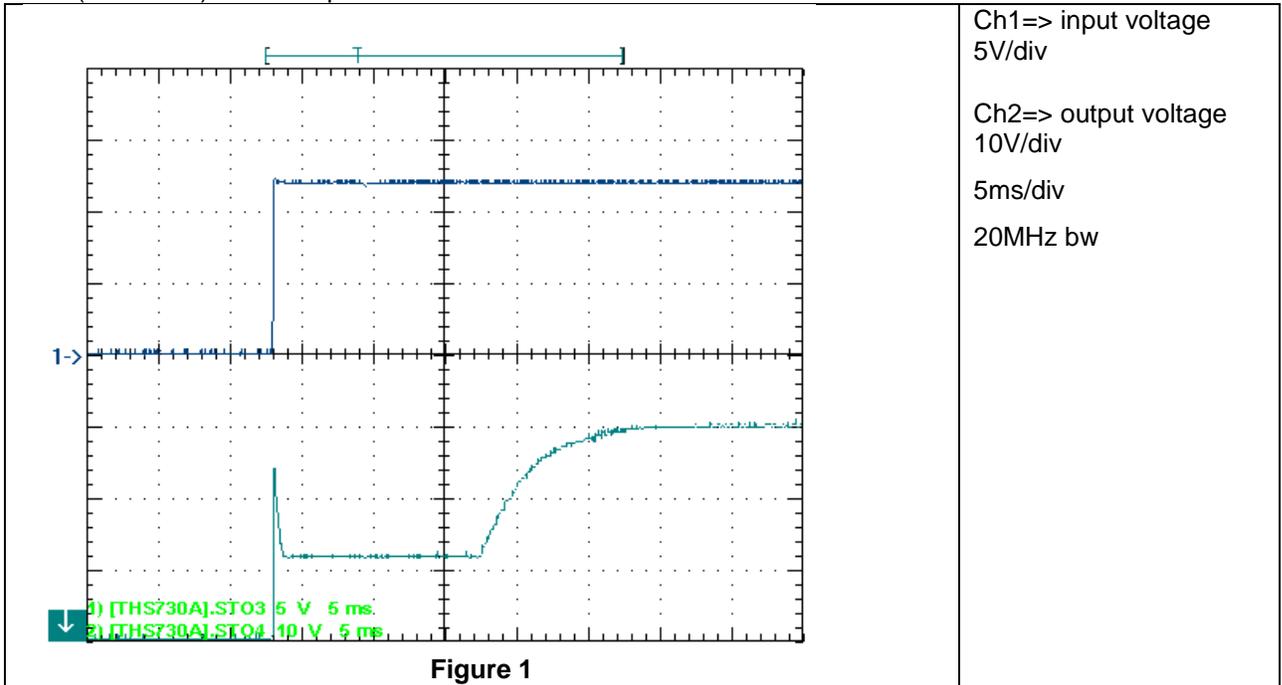The startup waveform is shown in the Figure 1. The input voltage was set at 12V, with resistive load (150Ohms) at the output.




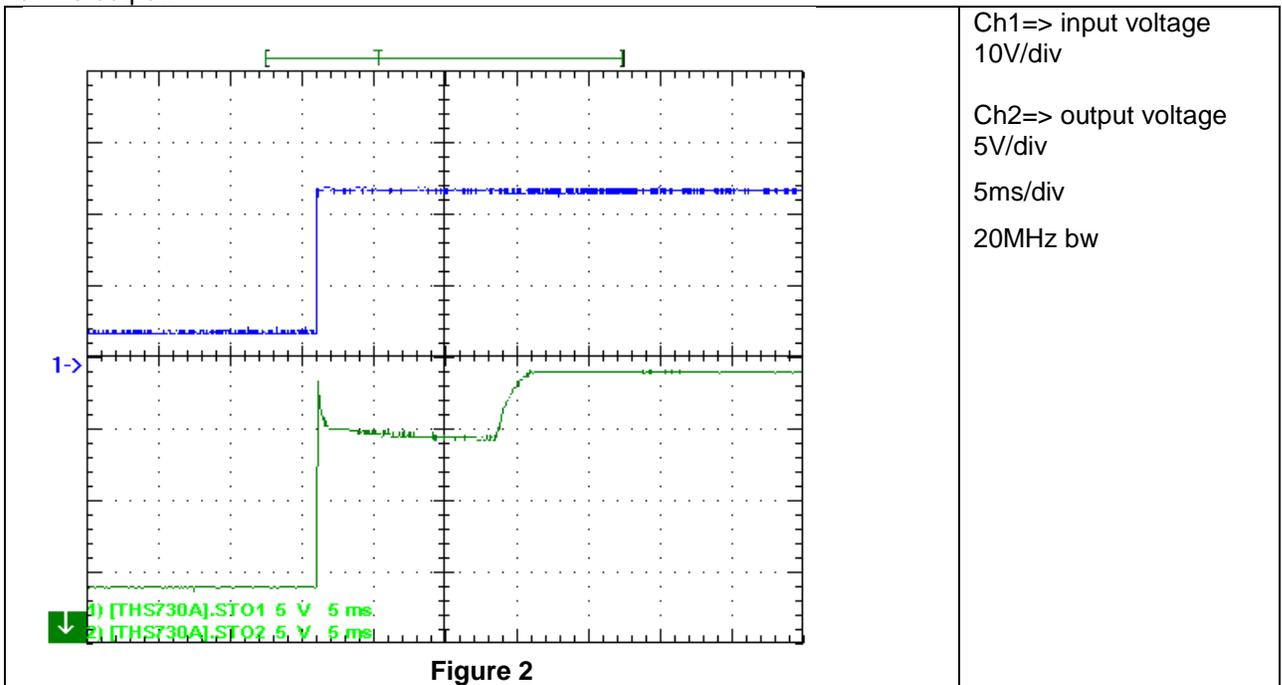The startup waveform is shown in the Figure 2. The input voltage was set at 12V, with LED load at the output.




2 Shutdown

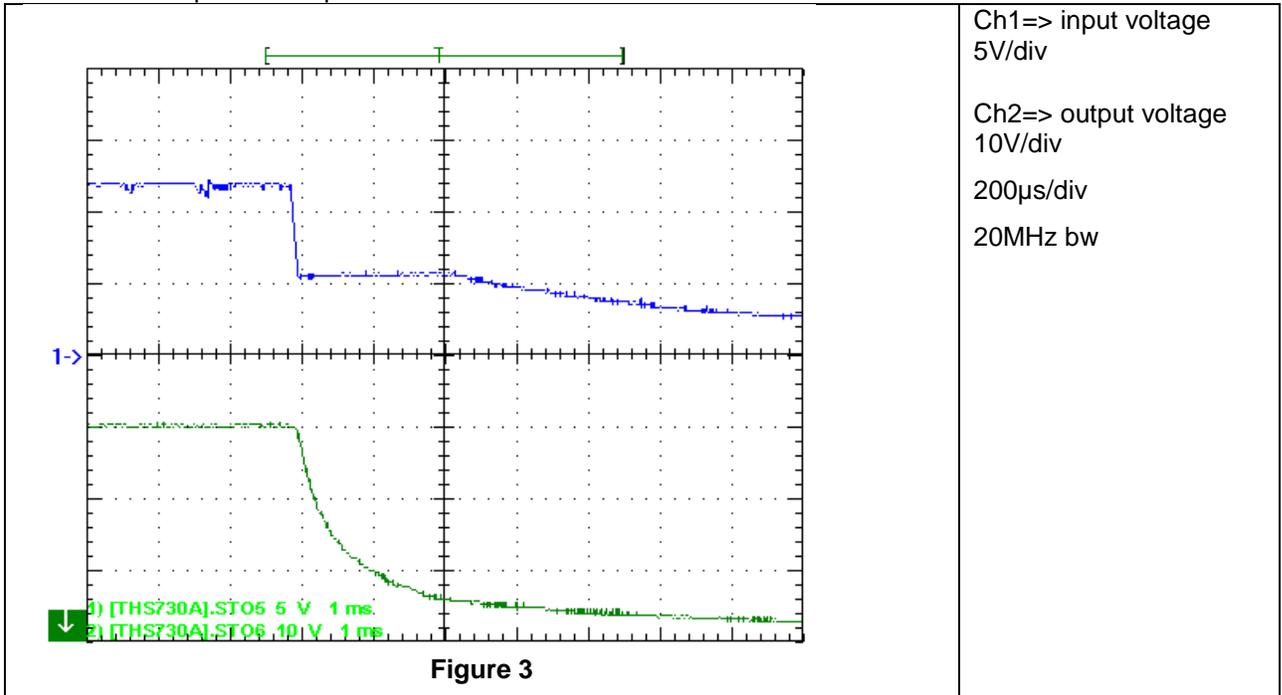The shutdown waveform is shown in the Figure 3. The input voltage was set at 12V, with resistive load on the output. One input cable was disconnected.



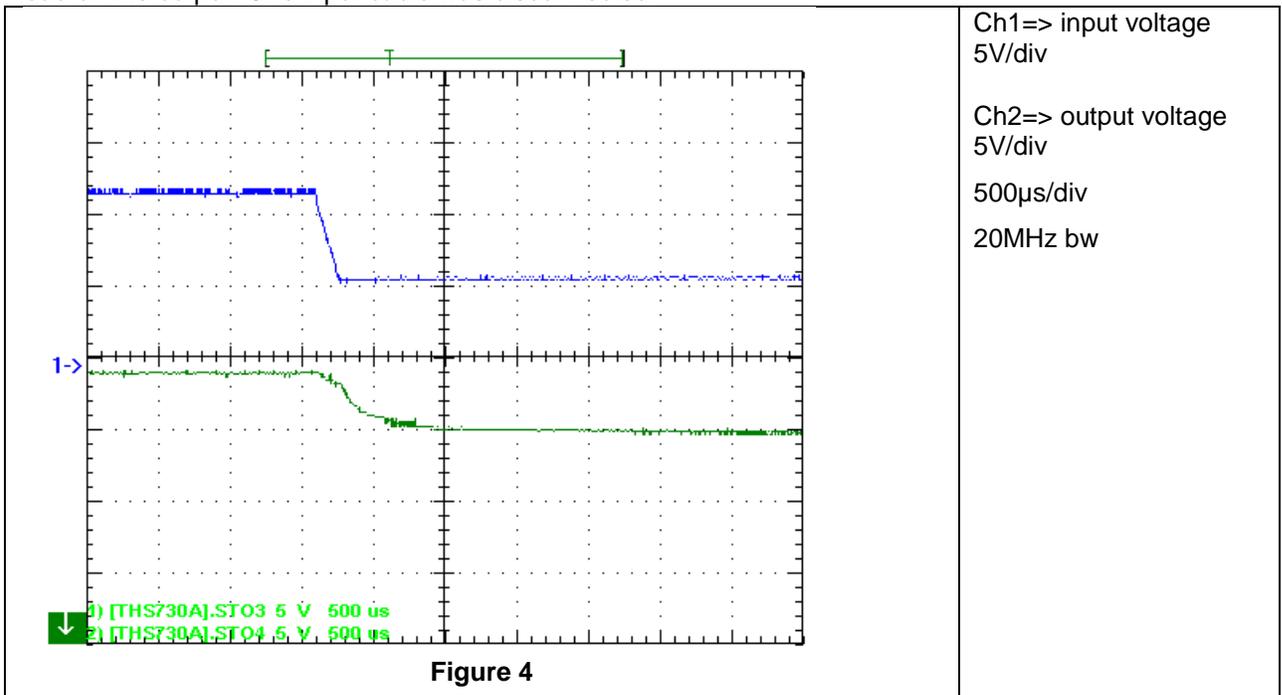The shutdown waveform is shown in the Figure 4. The input voltage was set at 12V, with LED load on the output. One input cable was disconnected.




3 Efficiency

The efficiencies are shown in the table below. The input voltage was set to 6V, 12V and 18V. Also measurements with and without synchronization were done.

sync R-load						
<i>V_{in}</i>	<i>I_{in}</i>	<i>V_{out}</i>	<i>I_{out}</i>	<i>P_{in}</i>	<i>P_{out}</i>	<i>Effcy</i>
6.40	1.0988	30.618	0.2000	7.03	6.12	87.07%
12.01	0.5417	30.348	0.1986	6.50	6.03	92.67%
18.00	0.3624	30.492	0.1992	6.52	6.07	93.12%
free running R-load						
<i>V_{in}</i>	<i>I_{in}</i>	<i>V_{out}</i>	<i>I_{out}</i>	<i>P_{in}</i>	<i>P_{out}</i>	<i>Effcy</i>
6.40	1.0958	30.622	0.2000	7.01	6.13	87.33%
12.00	0.5417	30.359	0.1987	6.50	6.03	92.78%
18.00	0.3623	30.507	0.1992	6.52	6.08	93.20%
sync LED						
<i>V_{in}</i>	<i>I_{in}</i>	<i>V_{out}</i>	<i>I_{out}</i>	<i>P_{in}</i>	<i>P_{out}</i>	<i>Effcy</i>
12.00	0.3449	19.064	0.1985	4.14	3.78	91.40%
free-running LED						
<i>V_{in}</i>	<i>I_{in}</i>	<i>V_{out}</i>	<i>I_{out}</i>	<i>P_{in}</i>	<i>P_{out}</i>	<i>Effcy</i>
12.01	0.3446	19.061	0.1987	4.14	3.79	91.55%


4 Output Ripple Voltage

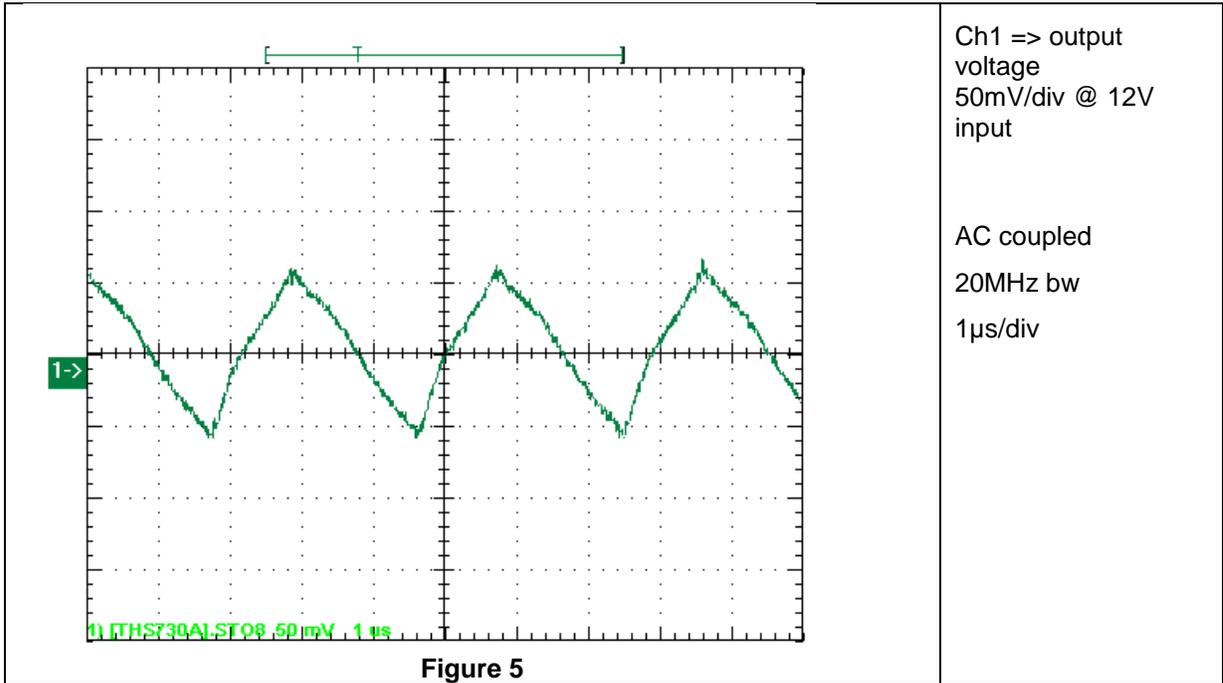The output ripple voltage is shown in Figure 5, here around 120mVpp.



5 Input Ripple Voltage

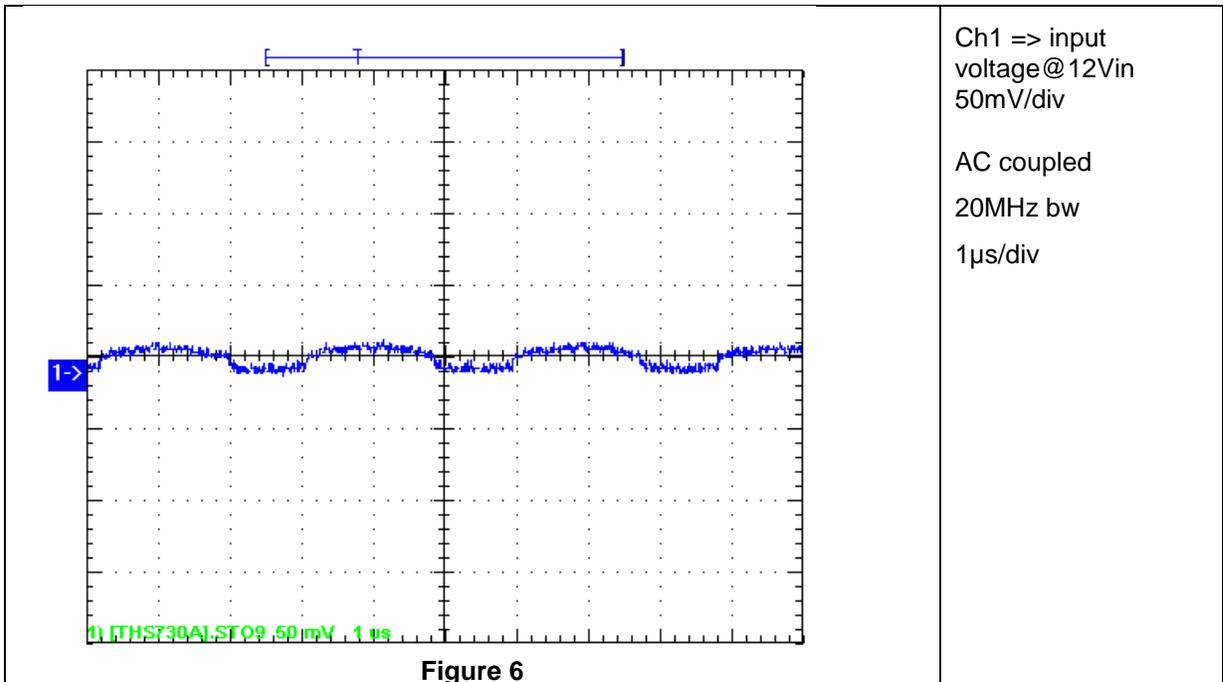The output ripple voltage is shown in Figure 6, here 20mVpp.



6 Control Loop Frequency Response

Figure 7 shows the loop response. 150Ohm-resistor were connected. The input voltage was set to 6V.(not synchronized), RHPZ around 10kHz (duty cycle 80%)

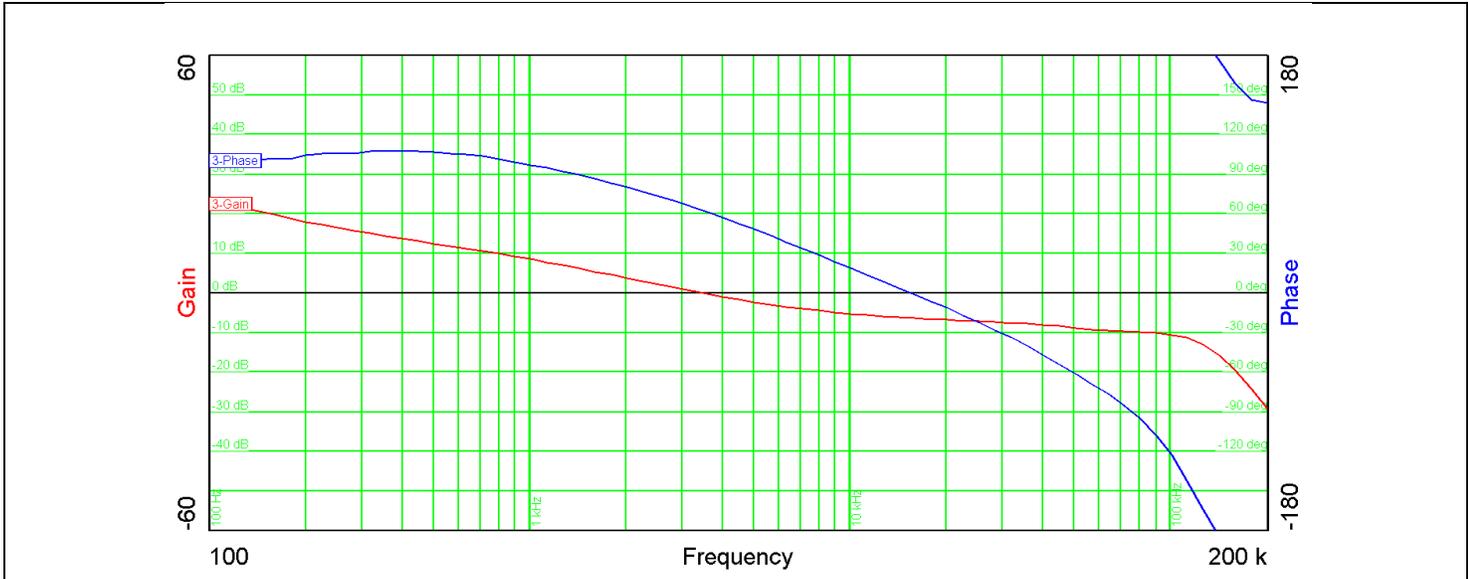


Figure 7

Figure 8 shows the loop response. 150Ohm-resistor were connected. The input voltage was set to 12V. (not synchronized)

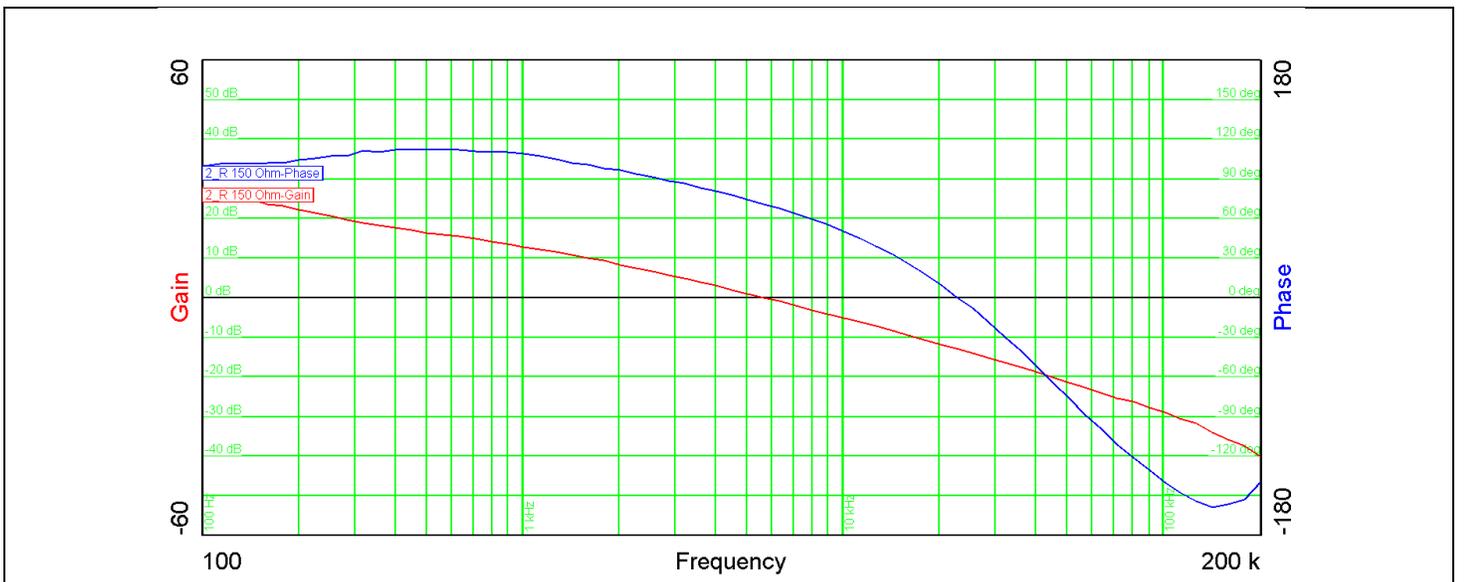


Figure 8

Figure 9 shows the loop response. LED was connected as nonlinear load. The input voltage was set to 12V.

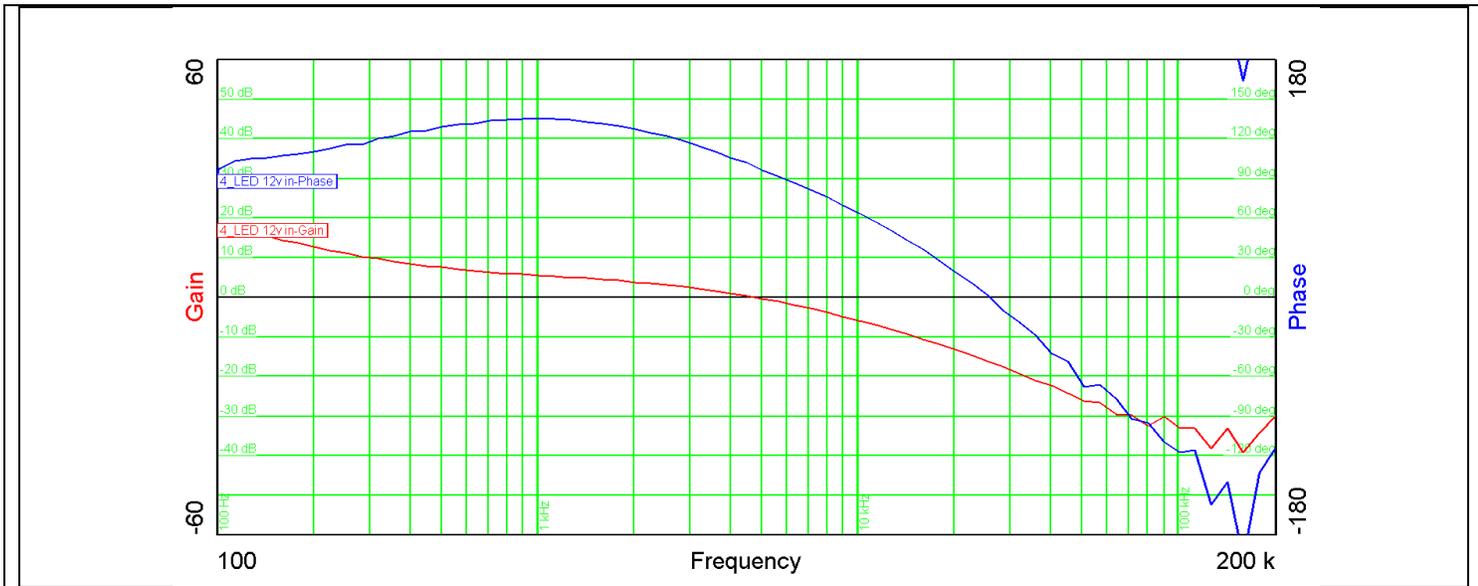


Figure 9

Table 1 summarizes the results from Figure 7 Figure 8 and Figure 9.

Vin	6V	12V	12V LED
Bandwidth (kHz)	3.43	5.63	4.76
Phase margin	63°	71	99
slope (20dB/decade)	-0.74	-1.03	-0.73
gain margin (dB)	-6.35	-13	-16.4
slope (20dB/decade)	-0.23	-1.16	-1.55
freq (kHz)	15.4	22.8	25.7

Table 1

7 Miscellaneous Waveforms

7.1 150R Load

The waveform of the voltage on Q1 (Drain-Source) is shown in Figure 10. Input voltage was set to 12V and 150Ohm as load.

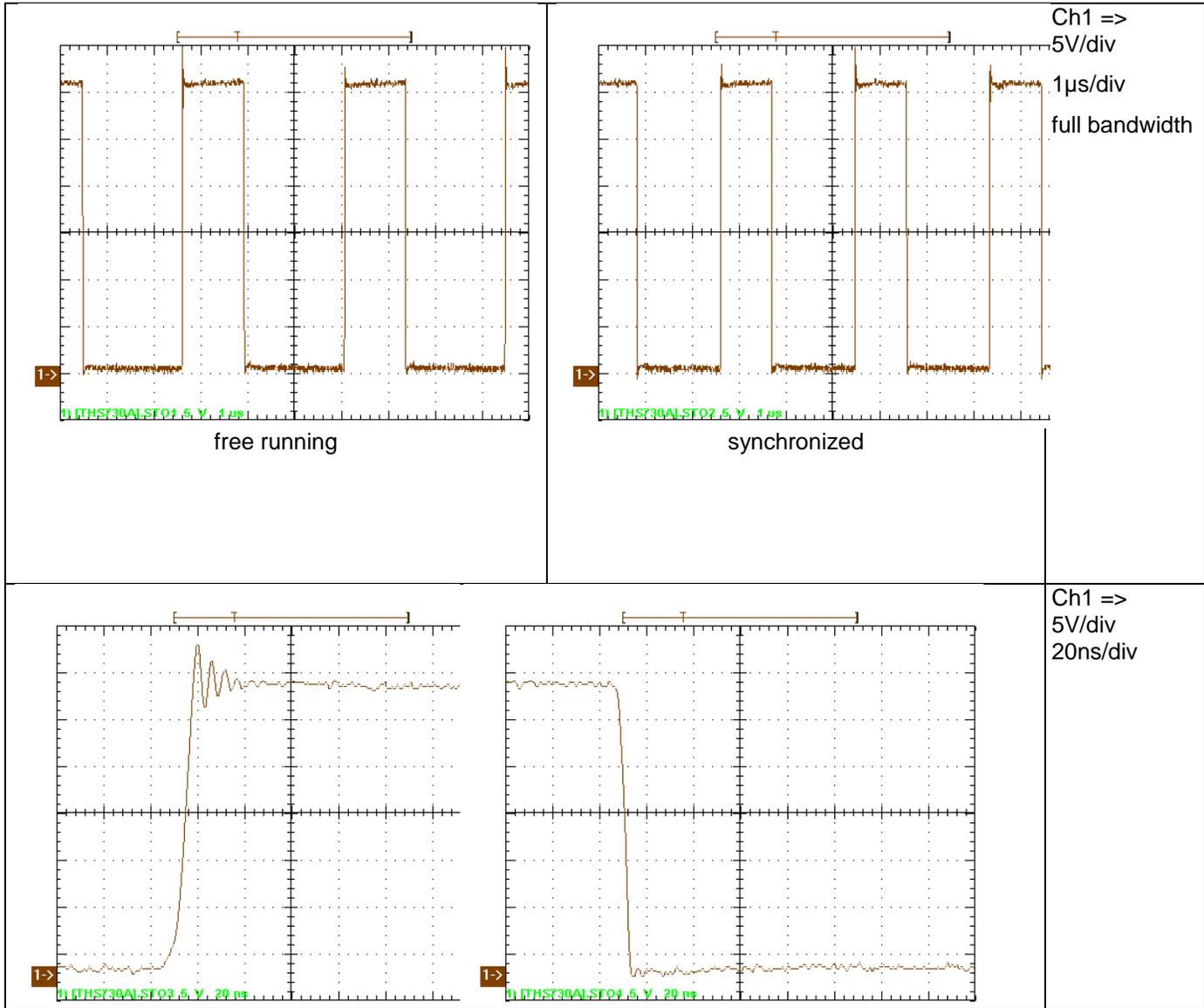


Figure 10

The waveform of the voltage on the gate to source is shown in Figure 11. Input voltage was set to 12V and 150Ohm as load.

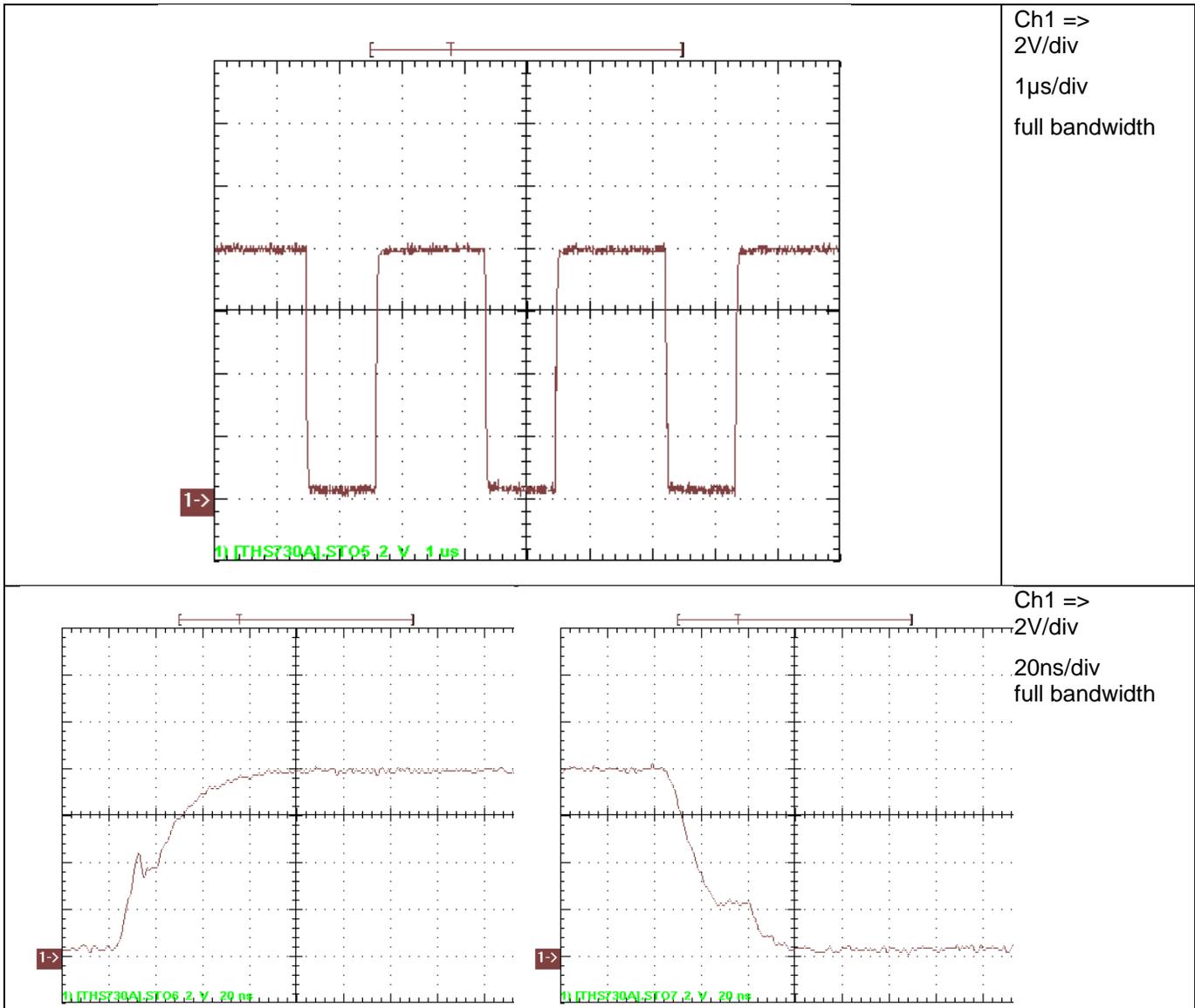


Figure 11

The waveform of the voltage on diode (referenced to Vout) is shown in Figure 12. Input voltage was set to 12V and 150Ohm as load.

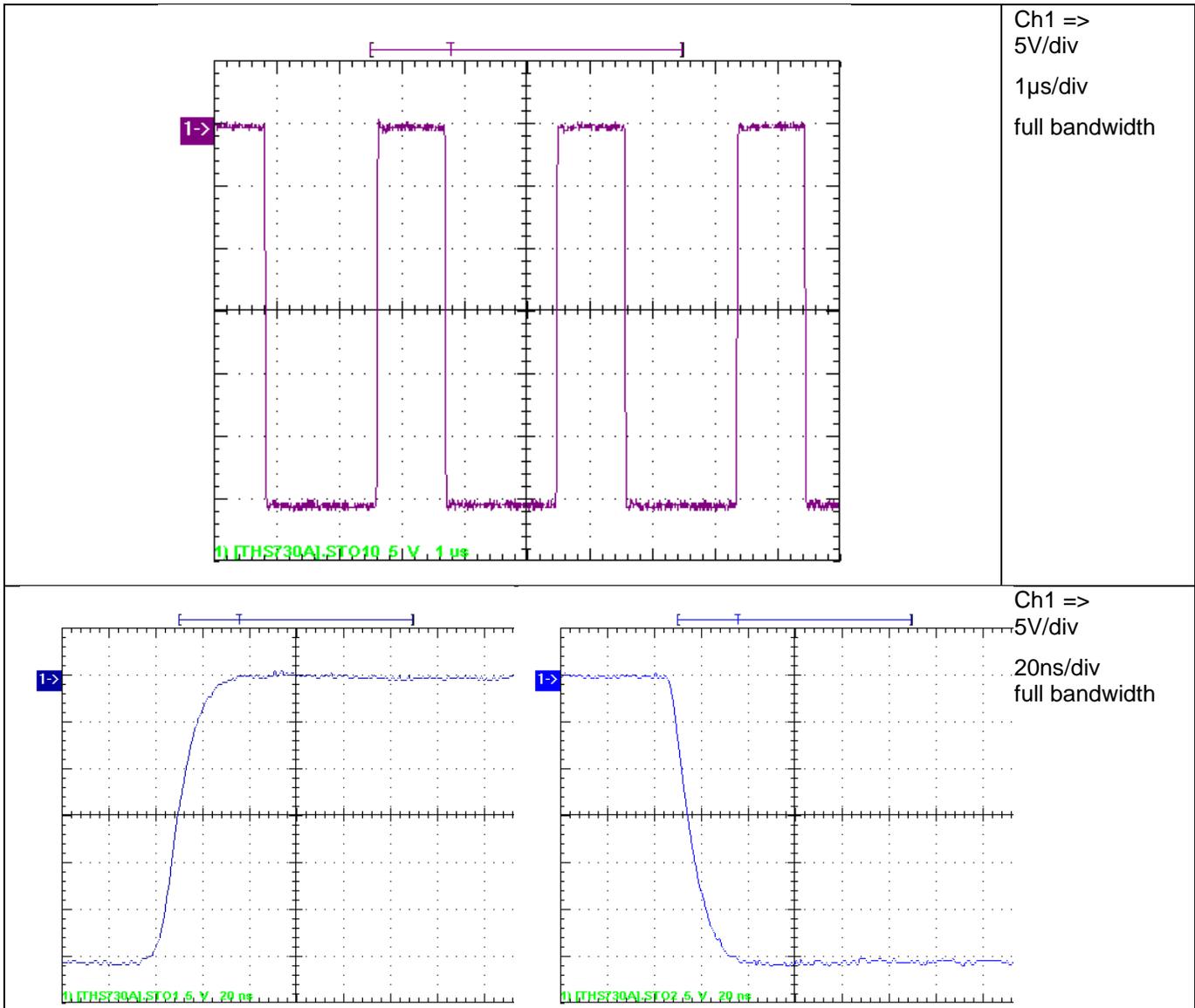


Figure 12

7.2 LED Load

The waveform of the voltage on Q1 (Drain-Source) is shown in Figure 13. Input voltage was set to 12V and LED-load

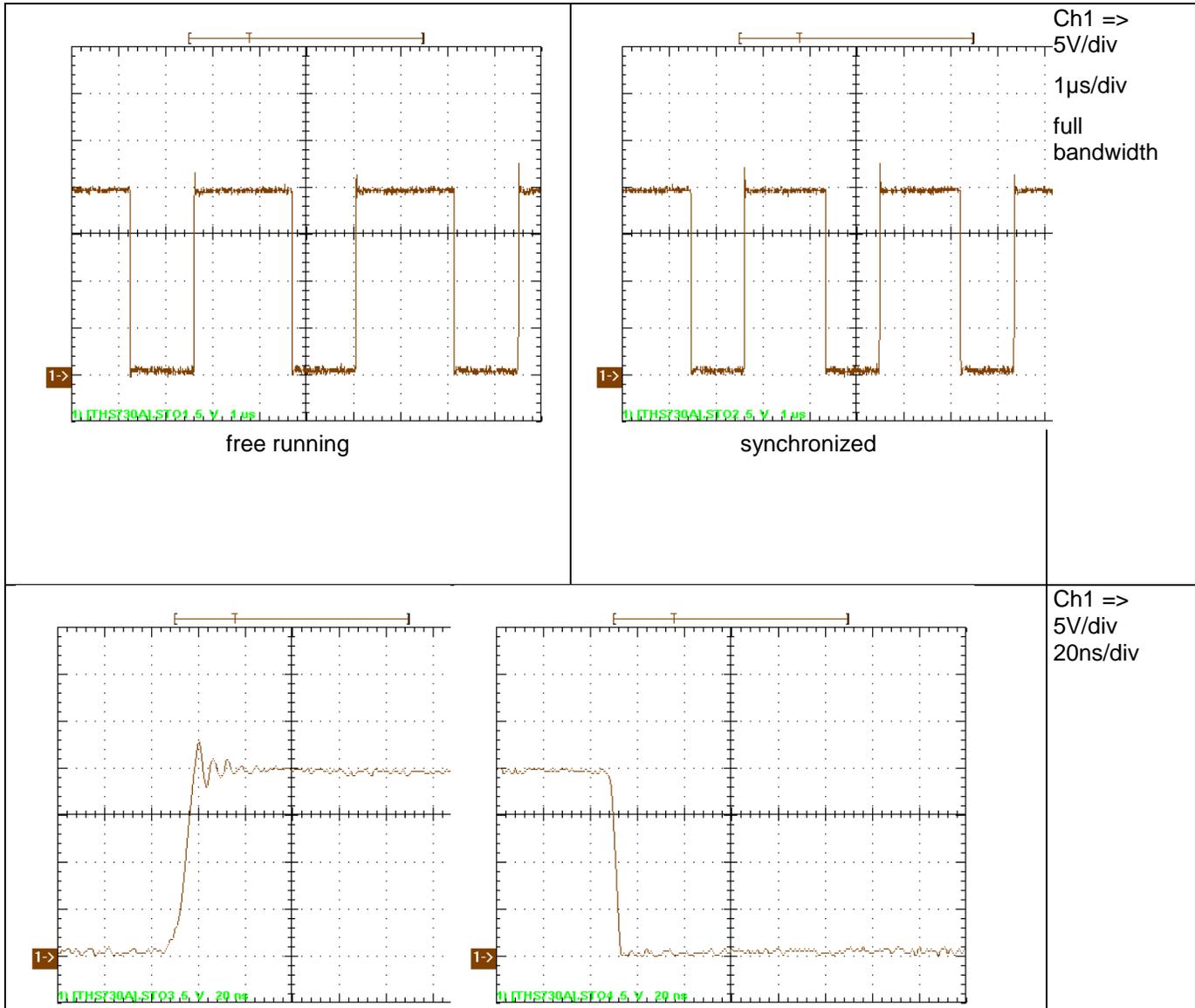


Figure 13

The waveform of the voltage on the gate to source is shown in Figure 14. Input voltage was set to 12V and LED-load.

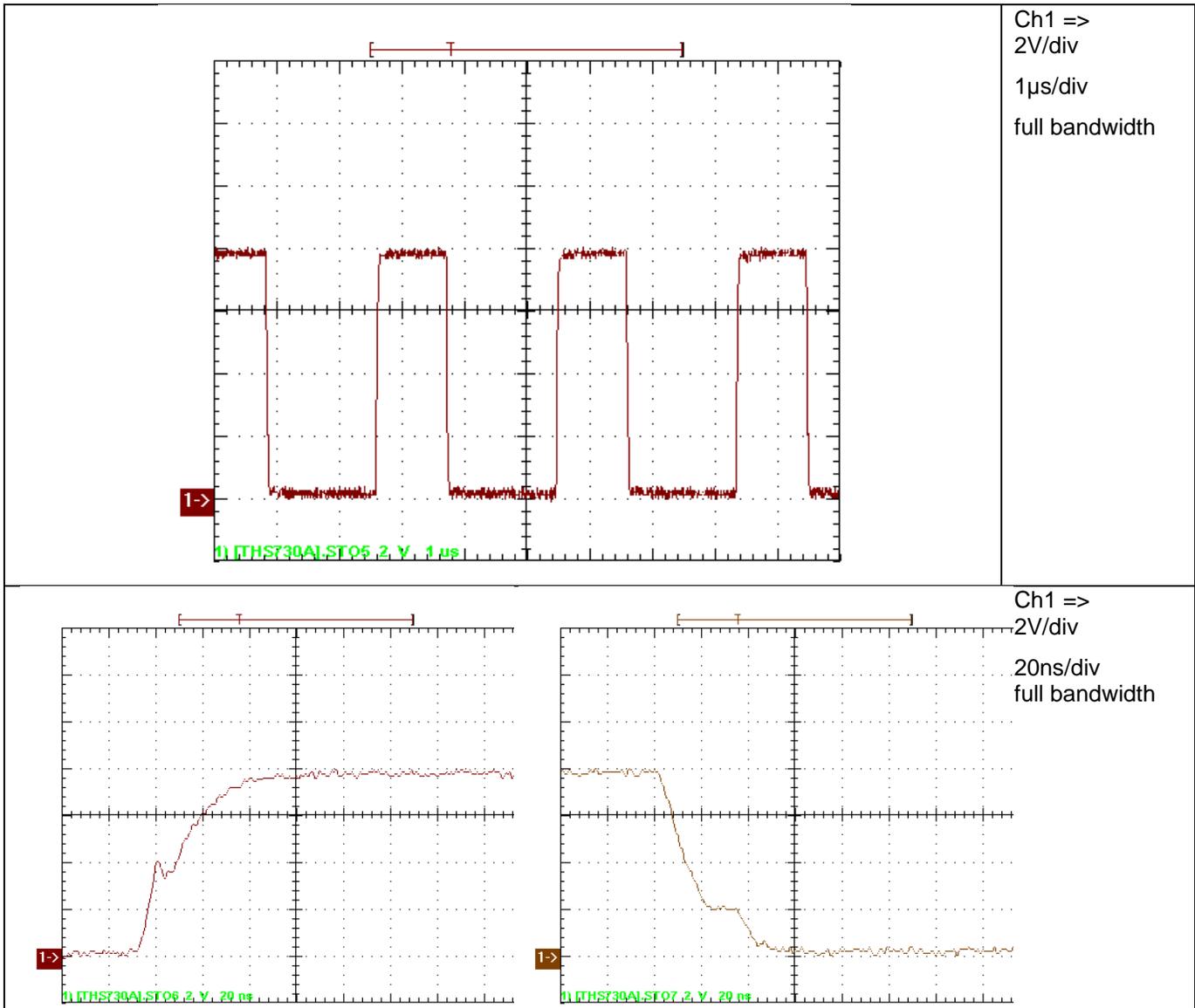


Figure 14

8 Thermal Image

Figure 15 shows the thermal image at 12V input voltage and 150R output (30V)

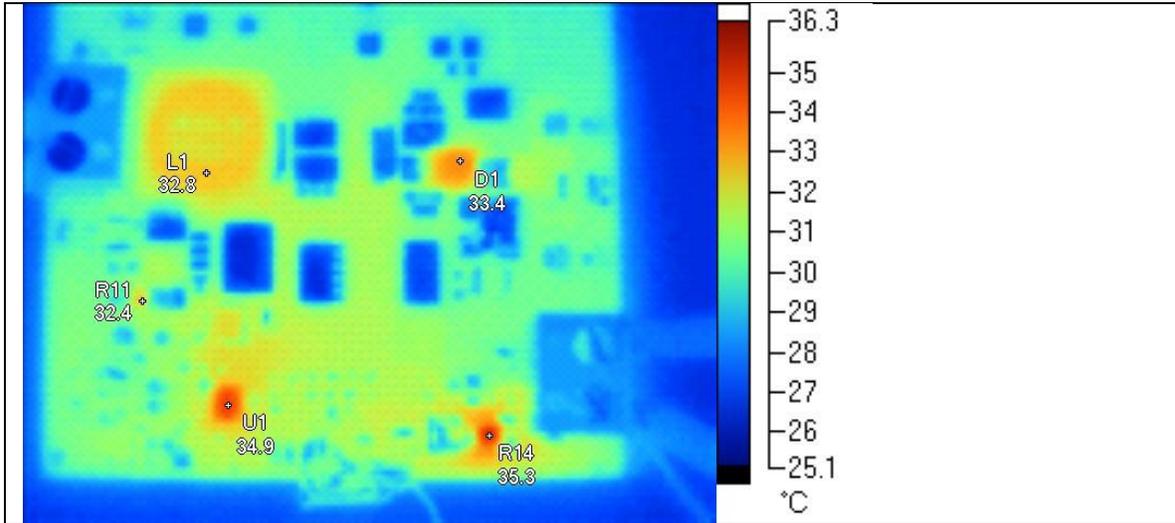


Figure 15

Name	Temperature
R14	35.3°C
D1	33.4°C
U1	34.9°C
R11	32.4°C
L1	32.8°C

Figure 16 shows the thermal image at 6.2V input voltage and 150R output (30V).

The design itself is fine for continuous operation at 6V input, so max. boost factor.

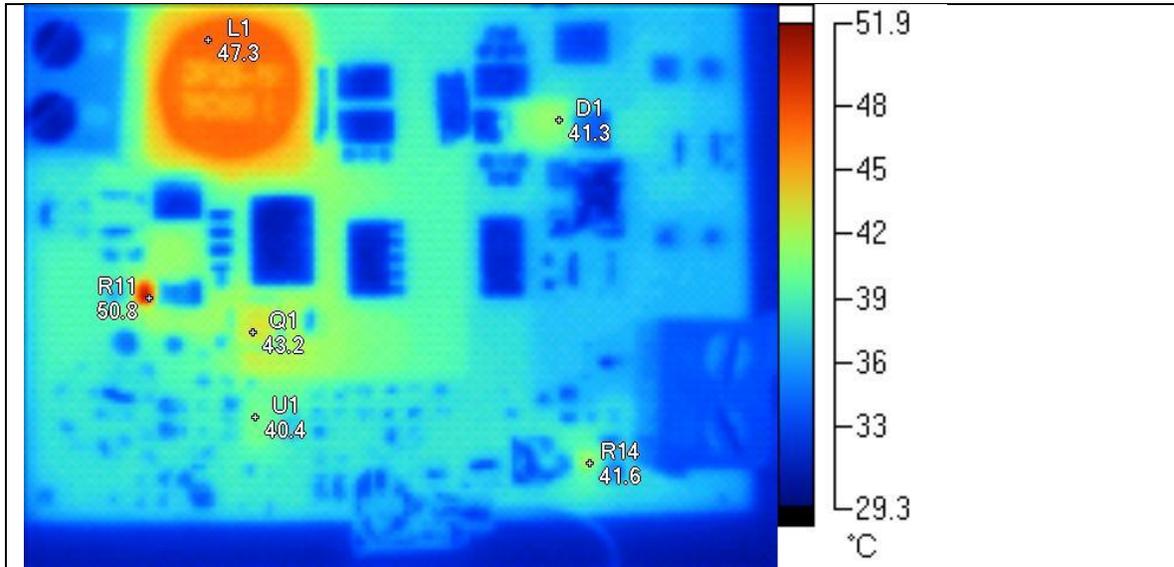


Figure 16

Name	Temperature
R11	50.8°C
R14	41.6°C
D1	41.3°C
L1	47.3°C
Q1	43.2°C
U1	40.4°C

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated