

TI Designs: TIDA-01419

Four-Phase, 150-A Reference Design for Intel® Arria® 10 GX FPGAs Using TPS53647



Description

This reference design focuses on providing a compact, high-performance, multiphase solution suitable for powering Intel® Arria® 10 GX field-programmable gate arrays (FPGAs) with a specific focus on the 10AX115U1451VG variant. Integrated PMBus™ allows for easy output voltage setting and telemetry of key design parameters. The design enables programming, configuration, smart VID adjustment, and control of the power supply, while providing monitoring of input and output voltage, current, power, and temperature. TI's Fusion Digital Power™ Designer is used for programming, monitoring, validation, and characterization of the FPGA power design.

Resources

TIDA-01419	Design Folder
TPS53647	Product Folder
CSD95472Q5MC	Product Folder
Fusion Digital Power Designer	Product Folder




[ASK Our E2E Experts](#)

Features


- All Ceramic Output Capacitors
- D-CAP+™ Modulator for Superior Current-Sharing Capabilities and Transient Response
- Peak Efficiencies of 89% ($V_{OUT} = 0.8\text{ V}$) and 90% ($V_{OUT} = 0.9\text{ V}$) at 600 kHz
- Excellent Thermal Performance Under No Airflow Conditions
- Overvoltage, Overcurrent, and Overtemperature Protection
- PMBus Compatibility for Output Voltage Setting and Telemetry for V_{IN} , V_{OUT} , I_{OUT} , and Temperature
- PMBus and Pinstrapping Programming Options

Applications

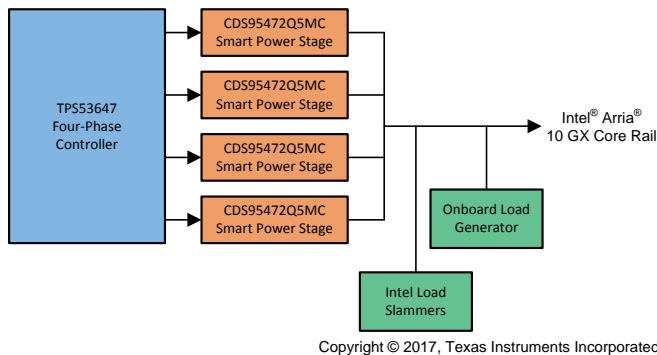- FPGA Core Rail Power
- Ethernet Switches
- Firewalls and Routers
- Telecom Base Band Units
- Test and Measurement



 Copyright © 2017, Texas Instruments Incorporated



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

The TIDA-01419 is a high-efficiency, power-dense design featuring a four-phase buck controller and TI's proprietary Smart Power Stages optimized for use in Intel® Arria® 10 GX FPGA core rail applications. These FPGAs are typically used in enterprise switching, telecom infrastructure, test and measurement, and cloud computing infrastructure environments with high utilization percentages that call for the high current and fast transient response that this design provides.

A 600-kHz switching frequency is used to minimize the size and number of output filter components while maintaining a thermal design current efficiency of 88.0%. The TPS53647 controller uses the D-CAP+™ multiphase modulator for fast transient response capabilities and tight regulation of the output voltage. The D-CAP+ modulator offers reliable current balancing between the four phases of the design that provides stability over a wide range of operating conditions and simple Type II compensation of the control loop. Additionally, the TPS53647 is compatible with TI's Smart Power Stages, like the CSD95472 used in this design, which offer optimized driver-FET solutions for high efficiency and integrated current-monitoring circuitry, that saves layout area and eliminates the requirement for external current sensing components.

Design modifications can be done in WEBENCH® Designer if a lower-power Altera 10 GX FPGA is used, or a different output capacitor mix is desired.


1.1 Key System Specifications

Table 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input supply	12 V \pm 5%
Nominal output voltage	0.9 V
DC regulation	<1.2%
DC ripple	2% max
AC ripple	\pm 5%
Max output current	150 A
Typical output current	100 A
Max load step	75 A at 500 A/ μ s
Number of phases	4
Switching frequency	600 kHz

2 System Overview

2.1 Block Diagram

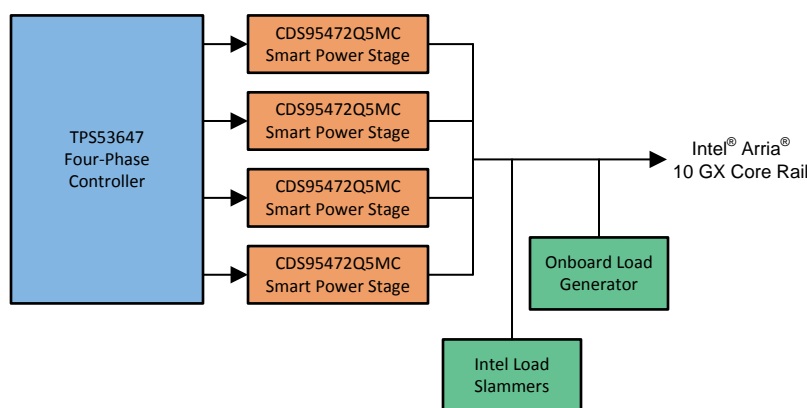

Copyright © 2017, Texas Instruments Incorporated

Figure 1. TIDA-01419 Block Diagram

2.2 Highlighted Products

2.2.1 TPS53647 – Four-Phase, D-CAP+™ Step-Down Buck Controller With NVM and PMBus™ Interface for ASIC Power and High-Current Point-of-Load

Features:

- 8-bit selectable boot voltage through pinstrap or non-volatile memory (NVM)
- One-, two-, three-, or four-phase operation
- 1.8-V or 3.3-V compatible PMBus™ system interface for fault monitoring and voltage, current, power, and temperature telemetry
- D-CAP+ modulator and eight independent levels of overshoot and undershoot reduction for excellent transient response
- Adjustable voltage positioning
- Dynamic phase shedding with programmable current threshold
- 6x6-mm, 40-pin, QFN PowerPAD™ integrated circuit package

2.2.2 CSD95472Q5MC – 60-A Synchronous Buck NexFET™ Smart Power Stage With DualCool™ Package

Features:

- 60-A continuous current capability
- Low power loss of 2.3 W at 30 A
- High-frequency operation up to 1.25 MHz
- 3.3-V and 5-V pulse-width modulation (PWM) compatible
- Temperature-compensated bidirectional current sense
- Analog temperature output
- Integrated bootstrap diode and optimized deadtime
- 5-mm x 6-mm SON, low inductance, DualCool™ packaging

4 Test Results

4.1 Efficiency and Power Loss

Peak efficiencies of 89% ($V_{OUT} = 0.8\text{ V}$) and 90% ($V_{OUT} = 0.9\text{ V}$) were measured for this design. At the thermal design current (TDC) of 100 A, the efficiencies were 87% and 88% for 0.8 V and 0.9 V, respectively. When the load current was set to the maximum current of 150 A the efficiency was 83% for $V_{OUT} = 0.8\text{ V}$ and 84% for $V_{OUT} = 0.9\text{ V}$. The curves also include the losses associated with the 5-V power stage VDD rail.

 


Figure 3. TIDA-01419 Efficiency Curves – $V_{IN} = 12\text{ V}$, 600 kHz

 


Figure 4. TIDA-01419 Power Loss Curves – $V_{IN} = 12\text{ V}$, 600 kHz

4.2 Steady-State Regulation

Steady-state stability, switching frequency, and DC ripple were tested at the 100-A TDC current for output voltages of 0.8 V and 0.9 V. No abnormalities were seen during testing. Care should be taken to ensure that the noise floor of the output voltage differential probe does not impact the results causing false failures in output ripple or stability. TI recommends to monitor a phase node as well to check against any possible questions regarding stability that may be attributed to a noisy differential probe. The design is likely stable if the switching frequency is consistent between phase pulses and varies within the TPS53647 datasheet limits.

Load regulation and the PMBus output voltage setting feature were also tested and found to comply with the specifications of the design. Note that the voltages steps in [Figure 6](#) are exaggerated to be easily seen through the Fusion Digital Power™ graphical user interface (GUI) monitoring software. The actual application keeps the output voltage between 0.8 V and 0.9 V.

 


Figure 5. Steady State: 0.8 V, 100 A

 


Figure 6. Steady State: 0.9 V, 100 A

 


Figure 7. TPS53647 Load Regulation – V_{IN} = 12 V, 600 kHz

 


Figure 8. FPGA Core Smart VID Adjustment Using PMBus™ Commands

4.3 Thermal Performance

The design was placed under 25-A, 50-A, and 100-A loads at an output voltage of 0.9 V for five minutes before measurements were taken of the power stages and inductors using an infrared camera. During testing, the ambient temperature was 25°C with no airflow across the board or heatsinks placed on the CSD95472 power stages.

 


Figure 9. CSD95472 Temperature: 25-A Load

 


Figure 10. CSD95472 Temperature: 50-A Load

 


Figure 11. CSD95472 Temperature: 100-A Load

4.4 Transient Response

A load step of 75 A was applied to the TPS53647 regulator under two test conditions. The first test condition being from 50 A to 125 A and the second from 75 A to the maximum load of 150 A. Under both conditions the duty cycle was swept from 10% to 83% to check for stability under a wider range of operational corners. With no DC load line and an AC tolerance of $\pm 5\%$, a peak-to-peak voltage swing of 90 mVpp is allowed at the nominal output voltage of 0.9 V. No stability issues were seen during testing and the output voltage remained within the regulation window.

 


Figure 12. 50-A to 125-A Transient, 10% Duty Cycle

 


Figure 13. 50-A to 125-A Transient, 10% to 83% Duty Cycle Sweep

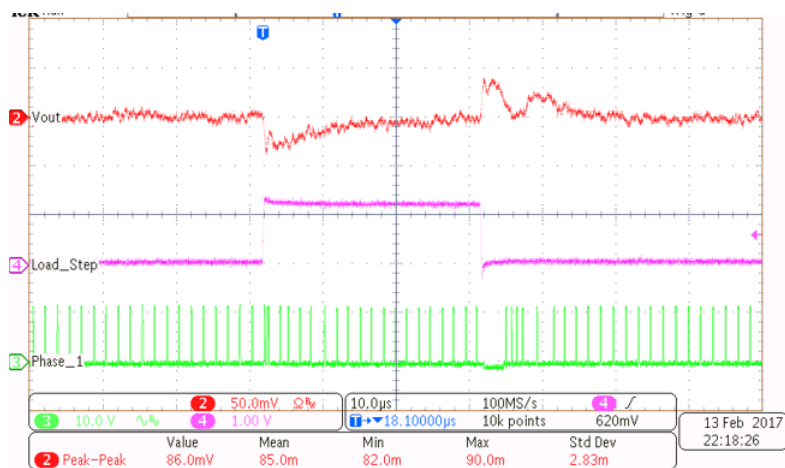


Figure 14. 75-A to 150-A Transient, 10% Duty Cycle

 


Figure 15. 75-A to 150-A Transient, 10% to 83% Duty Cycle Sweep

Table 2. Transient Response Validation Results

LOAD STEP	TRANSIENT SPECIFICATION AT NOMINAL OUTPUT VOLTAGE	VALIDATION RESULTS
75 A to 125 A	90 mVpp (± 45 mV)	83.8 mVpp
100 A to 150 A	90 mVpp (± 45 mV)	84.2 mVpp

4.5 Start-Up and Shutdown

Start-up and shutdown waveforms were taken at 10-A and 25-A loads while monitoring the enable, output voltage, and main phase node.

 


Figure 16. 10-A Start-Up

 


Figure 17. 10-A Shutdown

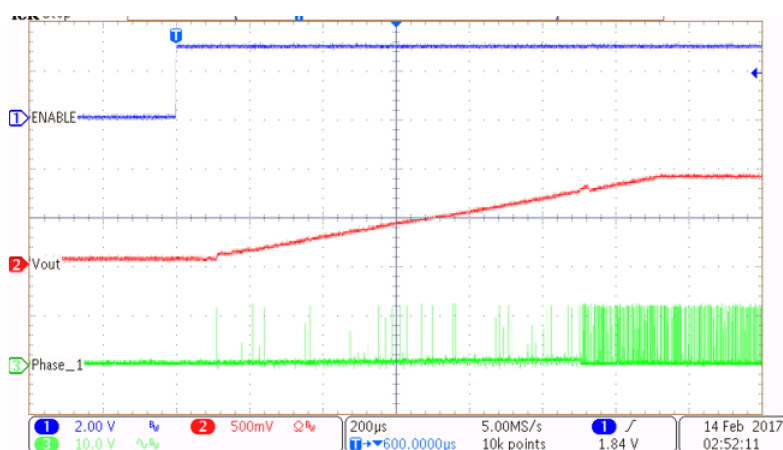


Figure 18. 25-A Start-Up

 


Figure 19. 25-A Shutdown

4.6 Protection Circuitry

When testing the protection circuit for this application, the TPS53647 device also performed admirably. The overcurrent and overtemperature protection features worked as intended when triggered, preventing the load and power field-effect transistors (FETs) from damage. Upon hitting the overcurrent limit, the controller went into hiccup mode and attempted to restart. Successful power-up only occurred after the high current was removed. After the overtemperature threshold was crossed, the phase node was tri-stated and the output voltage decayed to 0 V (according to the load current) until the part had cooled off.

 


Figure 20. Overcurrent Shutdown Event With Hiccup Mode

 


Figure 21. Overcurrent Event as Seen in Fusion GUI

 


Figure 22. Overtemperature Shutdown Event

 


Figure 23. Overtemperature Event as Seen in Fusion GUI

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01419](#).

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01419](#).

5.3 PCB Layout Recommendations

Follow all the layout instructions as specified in the respective datasheet for each part when laying out a design using the TPS53647 controller and CSD95472 Smart Power Stage. Some other guidelines to consider include:

- Keep the layout for all four phases identical to ensure optimal current balancing and thermal performance between phases.
- Route noisy traces such as PWM and the PMBus lines on a separate layer than the sensitive analog sense lines such as VSP, VSN, COMP, IMON, and so forth.
- Use quality capacitors for both the input and output decoupling to obtain the maximum performance possible with respect to DC ripple and transient response. Capacitors must be voltage rated to at least 16 V on V_{IN} and 2.5 V on V_{OUT} with a dielectric rating of X5R or better.
- Ensure that the VOUT and GND nodes are routed on multiple layers of copper and connected with enough vias to handle the current requirements for the best thermal performance. Following this guideline allows for a maximum amount of heat to flow out of the power stages and inductors into the board.

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01419](#).

5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01419](#).

5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01419](#).

5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01419](#).

6 Software Files

To download the Fusion Digital Power Designer software, see the following [tool folder](#).

7 Related Documentation

1. Texas Instruments, [TPS53647 4-Phase, D-CAP+, Step-Down, Buck Controller with NVM and PMBus™ Interface for ASIC Power and High-Current Point-of-Load](#), TPS53647 Datasheet (SLUSC39)
2. Texas Instruments, [CSD95472Q5MC Synchronous Buck NexFET™ Smart Power Stage](#), CSD95472Q5MC Datasheet (SLPS599)
3. Intel, [Intel® Arria® 10 GX, GT, and SX Device Family Pin Connection Guidelines](#), PCG-01017 (https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/dp/arria-10/pcg-01017.pdf)
4. Intel, [Power Reduction Features in Arria 10 Devices](#), AN-711 (https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/an/an711.pdf)
5. Intel, [SmartVID Controller IP Core User Guide](#), UG-SVID (https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/ug/ug_smartvid.pdf)
6. Intel, [25A Mini Slammer](#), Product Page (https://designintools.intel.com/25A_Mini_Slammer_p/q6uj9a00ms25.htm)

7.1 Trademarks

Fusion Digital Power, D-CAP+, PowerPAD, NexFET, DualCool are trademarks of Texas Instruments. WEBENCH is a registered trademark of Texas Instruments. Intel, Arria are registered trademarks of Intel Corporation. PMBus is a trademark of SMIF, Inc. All other trademarks are the property of their respective owners.

8 About the Author

CARMEN PARISI is a Senior Applications Engineer working in the Multiphase and Control Solutions (MCS) group at TI developing reference designs and application notes. He has six years of experience in power electronics working on mobile, desktop, and server V_{CORE} applications; battery chargers; and system PMICs. Carmen earned a combined BS/MS degree in electrical engineering from the Rochester Institute of Technology.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated