

## Multiphase 101 FAQs

Carmen Parisi, November 20, 2017

### When should I look to make the switch from a single phase converter to a multiphase one?

It varies based on the exact design parameters but in general switching to a multiphase design makes sense when thermal design currents are around 25-30A. A multiphase converter will offer better thermal performance, higher efficiency, lower DC ripple, and lower output voltage swings on transients over their single phase counterparts.

### What are the drawbacks of using a multiphase switching regulator?

While there are many benefits of multiphase converters they come at the potential expense of PCB area, BOM cost, and circuit complexity. PCB area can grow as phases are added which requires adding FETs, inductors, and a few passive components. BOM cost will likely increase as the phase count grows but could also drop if the cost of using more, lower current rated components is less than using fewer higher current rated components.

Circuit complexity will always increase as phase increases due to the issue of phase management. All multiphase switchers need some form of current feedback to the controller in order to properly balance current between all phases. Without this feedback stability issues appear and DC regulation suffers. In a worst case scenario FETs, inductors, or possibly the load device could be damaged if the phase management circuitry cannot maintain control of the regulator.

### What if I only need two or three phases of a four phase controller? Are TI's parts easy to configure?

TI's controllers are extremely easy to adapt to lower phase count designs. Typically all that is required is tying the current sense lines of unused phases to the controllers +3.3V supply and leaving unused PWM pins open. Be sure to check the datasheet for any additional requirements.

### One of the benefits of multiphase converters is fewer input and output capacitors for a given set of design conditions. How many caps can I really save?

When it comes to output capacitors the short answer is a lot. The easiest way to verify this claim though is to run the numbers. Let's look at some generic specs for a high powered FPGA core rail:

<b>VIN</b>	12	<b>V</b>
<b>VOUT</b>	1.0	<b>V</b>
<b>D</b>	0.083	
<b>IMAX</b>	120	<b>A</b>
<b>fsw</b>	600	<b>kHz</b>
<b>ΔVOUT</b>	0.05	<b>V±</b>
<b>ΔVIN</b>	1.2	<b>Vpp</b>
<b>L</b>	0.22	<b>μH</b>
<b>ΔIOUT</b>	60	<b>A</b>

Using these specs we can figure out how many capacitors we would need to meet the DC input ripple, RMS input current, and output over/undershoot specs for single and multiphase options. The chart below shows those results and highlights the number of caps need for CIN and COUT in green for each case.

Design Parameter	Number of Phases			
	1	2	4	6
<b>RMS Input Current (Arms)</b>	33.17	22.36	14.14	10.00
<b># of Input Caps - RMS Current</b>	4	3	2	2
<b>CIN (μF) - Vin Ripple</b>	41.67	20.83	10.42	6.94
<b># of Input Caps - Ripple Spec</b>	5	3	2	1
<b>Undershoot COUT (μF)</b>	780	420	240	180
<b># of Output Caps - Undershoot</b>	8	5	3	2
<b>Overshoot COUT (μF)</b>	7980	4020	2040	1380
<b># of Output Caps - Overshoot</b>	80	41	21	14
Assumes 10μF, 1206 Input Caps rated to 8.66Arm and 100μF Output Caps				

Switching to a multiphase design can cut down the number of input ceramic capacitors by half but the real savings are found when looking at the output capacitance. Simply going from one phase to two cuts the COUT requirements in half! Jumping to four phases requires only a quarter of the output capacitance that a single phase design would need thanks a lower equivalent inductance. From these results we can also see that adding more than four phases wouldn't results in saving too many more capacitors and the cost of additional FETs, inductors, and PCB area would probably outweigh the savings. Always be sure to find your ideal phase count before committing to a design.


## How much does adding phases to a design affect thermal performance?

Once again, let's let the test results speak for themselves. The following thermal images were captured for the following conditions:

12VIN, 1VOUT, 600kHz, 25A Load

20°C Ambient, 5 minute soak at load, no airflow

Single and Dual Phase Configurations

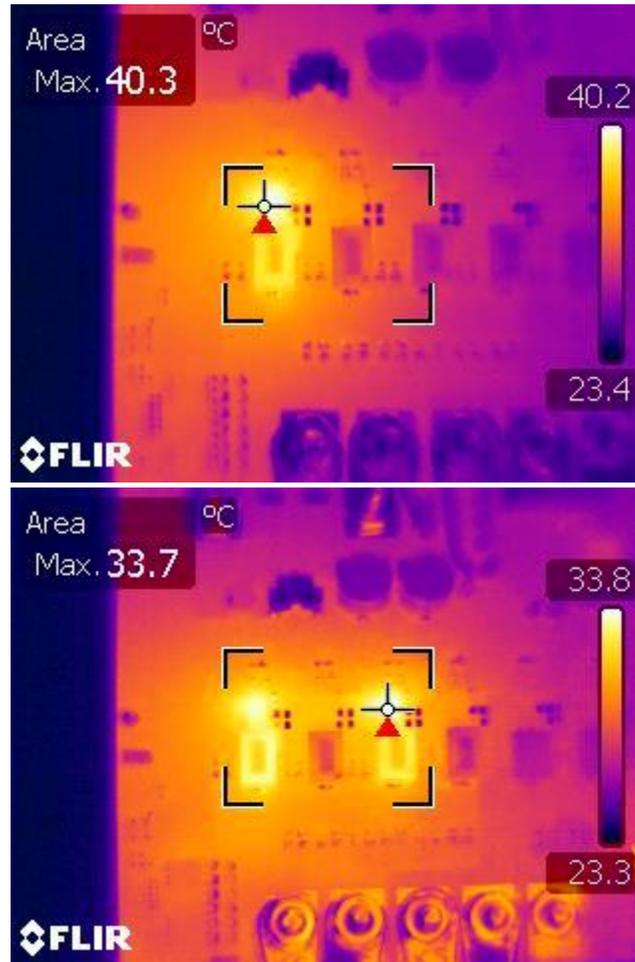

The single phase solution is running almost 7°C hotter than the dual phase configuration for the same conditions! Multiphase thermal performance will only improve as the load current increases to 30A and beyond. Sticking with single phase for such high currents quickly leads to a complicated thermal design as heftier heatsinks and more airflow is required to keep the FETs at a safe operating temperature.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated