

High-Performance Analog Products

Analog Applications Journal

First Quarter, 2014



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as “components”) are sold subject to TI’s terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI’s terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers’ products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers’ products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI’s goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or “enhanced plastic” are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer’s risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP™ Applications	
Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E™ Community**e2e.ti.com**

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

SSZZ022H

Contents

Introduction	4
Power Management	
Split-rail approaches extend boost-converter input-voltage ranges	5
Wide-input-range DC/DC controllers usually have built-in UVLO circuits that set the lower input-voltage limits in single-rail configuration, preventing the controllers from working with input voltage lower than their UVLO thresholds. This article presents several split-rail approaches to extend boost-converter input-voltage ranges, enabling the use of these controllers with input voltage lower than their UVLO thresholds. Design examples along with test results are provided to validate these approaches.	
Low-cost flyback solutions for 10-mW standby power	9
The simplicity and cost-effectiveness of the flyback topology have made it the preferred choice for the many low-power AC/DC designs powering consumer electronics. The standby-power consumption of the flyback converter is being heavily scrutinized to minimize the overall power drain when it seems the converter is doing nothing. This article provides insights into achieving the same performance at lower cost or improved performance at the same cost. It also discusses how the cost of a power-supply solution can be addressed with the smart choice of a power-efficient controller.	
Accurately measuring efficiency of ultralow-I_Q devices	13
There are many important nuances that must be considered when measuring the efficiency of a device with ultralow quiescent current (I_Q). For a device that consumes less than 1 μ A, the circuit's currents are very small and difficult to measure. This article reviews the basics of measuring efficiency, discusses common mistakes in measuring the light-load efficiency of ultralow- I_Q devices, and demonstrates how to overcome them in order to get accurate efficiency measurements.	
Data Converters	
When is the JESD204B interface the right choice?	18
Anyone involved in high-speed data-capture designs that use an FPGA has probably considered the JESD204B standard because it supports interface speeds of up to 12.5 Gbps. So what is the JESD204B interface all about? This article discusses the evolution of the JESD204B standard and what it means to a systems design engineer.	
Interface	
CAN bus, Ethernet, or FPD-Link: Which is best for automotive communications? . . .	20
The CAN bus currently reigns supreme for low-speed, low-cost control applications. However, when higher bandwidths are required, Ethernet or FPD-Link can step in as an enhanced interface. This article examines three automotive communications standards—the CAN bus, Ethernet, and FPD-Link—and explores which interface best suits which system.	
New-generation ESD-protection devices need no V_{CC} connection	23
Discrete ESD-protection diodes have become necessary in many applications to guarantee sufficient system-level ESD protection. In the past, the V_{CC} connection was added to diodes to reduce their junction capacitance. With the advent of new diode technology, this is no longer required. This article explains the V_{CC} connection's necessity in the past and the advantages of not having to use it in the present.	
Index of Articles	27
TI Worldwide Technical Support	34

To view past issues of the
***Analog Applications Journal*, visit the Web site:**
www.ti.com/aaj

Subscribe to the AAJ:
www.ti.com/subscribe-aaaj

Introduction

The *Analog Applications Journal* is a digest of technical analog articles published quarterly by Texas Instruments. Written with design engineers, engineering managers, system designers and technicians in mind, these “how-to” articles offer a basic understanding of how TI analog products can be used to solve various design issues and requirements. Readers will find tutorial information as well as practical engineering designs and detailed mathematical solutions as they apply to the following product categories:

- Data Converters
- Power Management
- Interface
- Amplifiers
- Low-Power RF
- General Interest

Analog Applications Journal articles include many helpful hints and rules of thumb to guide readers who are new to engineering, or engineers who are just new to analog, as well as the advanced analog engineer. Where applicable, readers will also find software routines and program structures.

Split-rail approaches extend boost-converter input-voltage ranges

By Haifeng Fan
Systems Engineer


Introduction

Wide-input-range DC/DC controllers usually have built-in undervoltage lockout (UVLO) circuits to prevent the converters from misoperating when the input voltage is below the UVLO threshold. However, the UVLO circuit might also cause undesirable shutdown in the event of a load transient or a supercapacitor discharge in applications where input voltage is above the UVLO threshold at start-up but later may drop below this threshold. In addition, these controllers normally cannot be used in applications where the input voltage is always under the UVLO threshold. This article presents several split-rail approaches to extend boost-converter input-voltage ranges, enabling the use of these controllers with input voltage lower than their UVLO thresholds. Design examples along with test results are provided to validate these approaches.

Minimum input voltage of a boost converter

Figure 1 shows typical boost converters with a single input supply (V_{IN}) that provides the input voltage to the power stage and the bias voltage to the controller. The minimum bias voltage to the controller at the V_{IN} pin is set by the controller's input UVLO threshold. To guarantee functionality of boost converters with high-side current sensing (Figure 1a), the minimum input voltage to the power stage is defined by the minimum common-mode voltage of the current-sense comparator. This is because the input voltage is also connected with the non-inverting input of the current-sense comparator. The minimum common-mode voltage of the current-sense comparator often is less than the controller's input UVLO threshold. For the boost converter with low-side current sensing (Figure 1b), the input voltage to the power stage is not directly connected to the current-sense

Figure 1. Boost converters in single-rail configuration

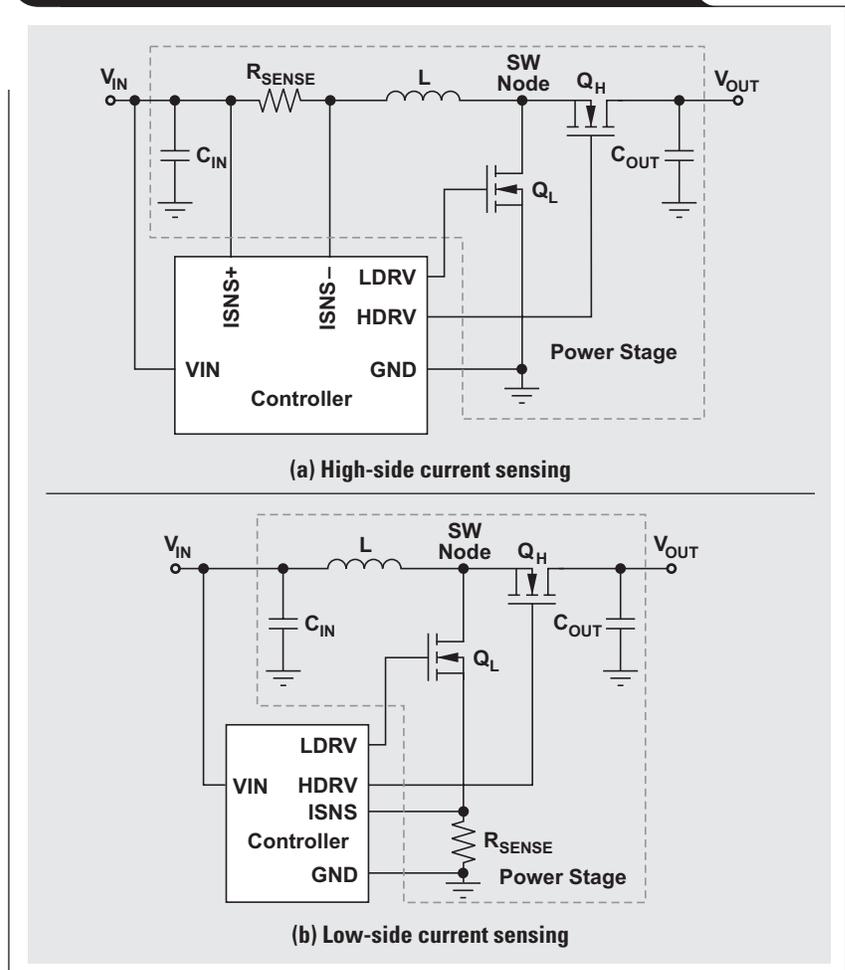

comparator. Therefore, it is not required to match the minimum common-mode voltage. Consequently, in the single-rail configuration where the input voltage to the power stage and the bias voltage to the controller are tied together, the controller's input UVLO threshold imposes a constraint on how low the input voltage to the boost power stage can go.

As shown in Figure 2, the input supply to the boost converter can be split into two rails: the power-stage input rail (V_{IN}) and the controller's bias input rail (V_{BIAS}). In the split-rail configuration, although V_{BIAS} is still required to be above the controller's UVLO threshold to turn on the controller, V_{IN} can go below the UVLO threshold. Since V_{BIAS} needs to supply only a very small amount of power, it can be generated by a charge pump or even share another voltage rail already existing in the system. As a result, the voltage range of the power rail (V_{IN}) can be extended.

This article will discuss several approaches to implementing the split-rail configuration. The TPS43061 synchronous boost controller from Texas Instruments (TI) will be used to elaborate on the split-rail concept and to validate the presented approaches. This boost controller has a high-side current-sense comparator and an internal input UVLO circuit at the bias-supply input (V_{IN}) pin.

Figure 3 shows the turn-off waveforms of the boost converter in the single-rail configuration shown in Figure 1a. The converter stops switching once V_{IN} falls below 3.9 V, which is the controller's UVLO turn-off threshold. The boost converter can be turned on only when V_{IN} rises above the UVLO turn-on threshold of 4.1 V.

Extending input-voltage range after start-up

In some applications with only one input supply, the input-supply voltage is greater than the controller's UVLO turn-on threshold at start-up. However, it might fall below the input UVLO threshold afterwards, leading to undesired shutdown. For example, in power systems using a photovoltaic panel combined with a supercapacitor as an input supply, the input voltage may drop below the controller's UVLO turn-off threshold due to discharge. Another example is a power system powered by a USB power cable where the voltage drops significantly during a load transient, resulting in an unexpected system shutdown.

Figure 2. Boost converters in split-rail configuration

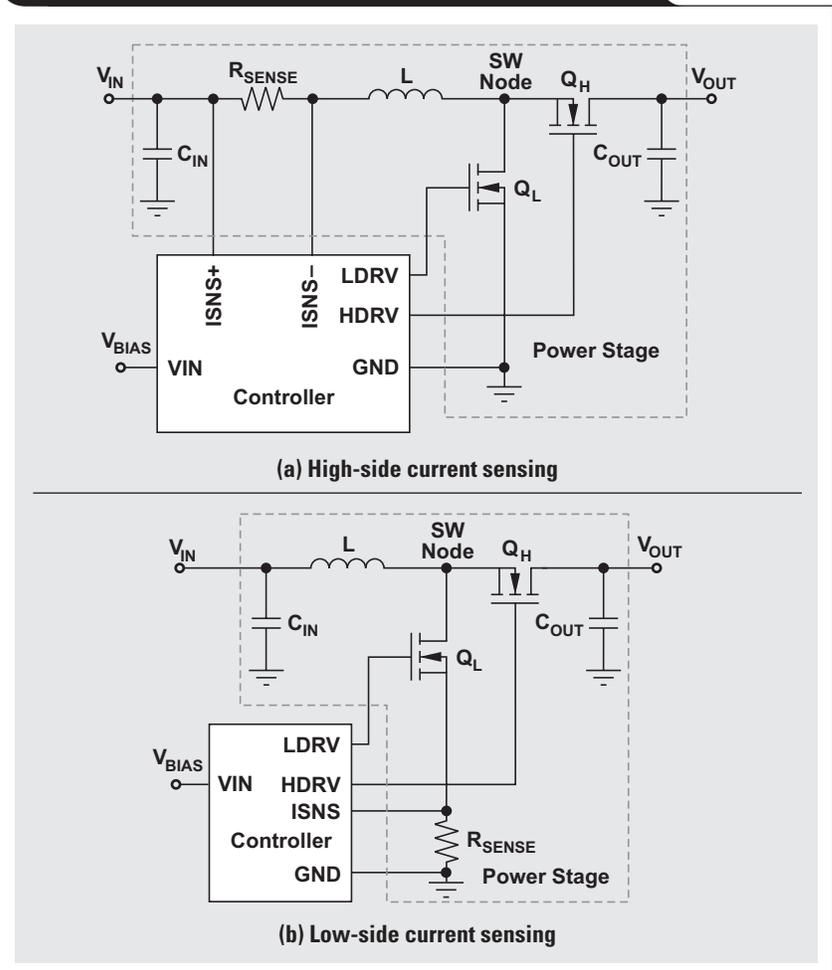


Figure 3. Turn-off waveforms of boost converter in single-rail configuration


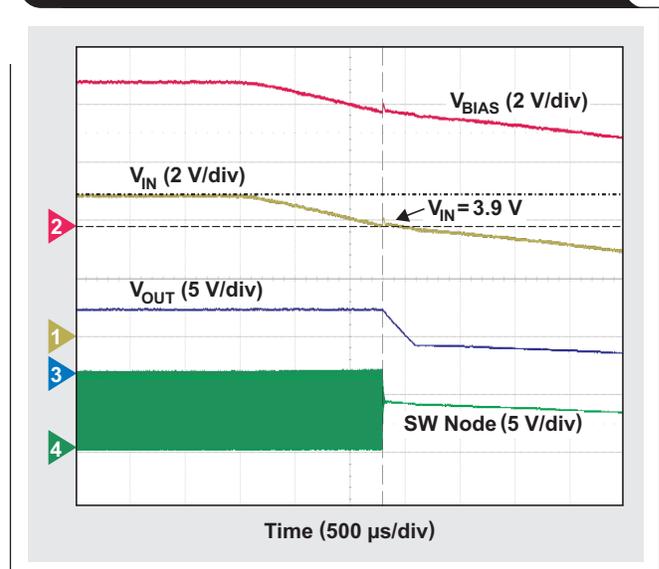


Figure 4. Split-rail approach feeding V_{OUT} back as bias supply

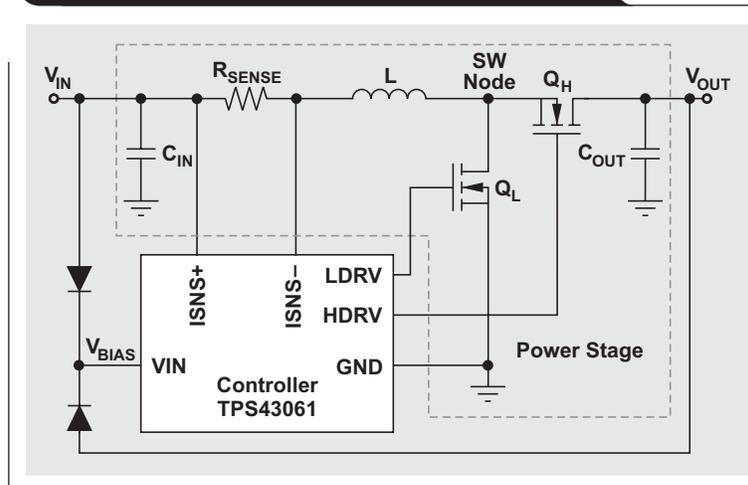


For these applications, if V_{OUT} is within the V_{BIAS} specification range, which is always higher than the UVLO turn-on threshold, V_{OUT} can be fed back as the bias supply (V_{BIAS}) via a diode (Figure 4). After start-up, V_{BIAS} is clamped to V_{OUT} rather than V_{IN} and stays above the UVLO threshold even if V_{IN} drops below this threshold. The boost converter can maintain normal operation as long as V_{IN} can meet the current-sense comparator's requirement for the minimum common-mode voltage.

Figure 5 shows the turn-off waveforms of the boost converter shown in Figure 4, where V_{OUT} is set as 6 V and fed back as the bias supply. With diode's forward voltage drop neglected, the bias-supply voltage (V_{BIAS}) is clamped to V_{OUT} rather than V_{IN} when V_{OUT} is higher than V_{IN} after start-up. Hence, V_{BIAS} stays above the 3.9-V UVLO turn-off threshold to avoid the undesired turn-off when V_{IN} falls below 3.9 V. V_{OUT} stays within regulation until V_{IN} falls below the minimum common-mode voltage of the current-sense comparator, in this example 1.9 V. This means that the minimum input voltage (V_{IN}) has been extended from 3.9 V to 1.9 V after start-up.

Extending the start-up input-voltage range

Lithium-Ion (Li-Ion) batteries are widely used in smartphones, tablet PCs, and other handheld devices. The voltage of a single-cell Li-Ion battery rated at 3.6 V usually ranges from 2.7 V to 4.2 V due to discharge and charge. This is lower than the UVLO threshold of some wide-input-range boost controllers, even before start-up. For these applications, neither a single-rail scheme nor a


Figure 5. Turn-off waveforms of configuration shown in Figure 4

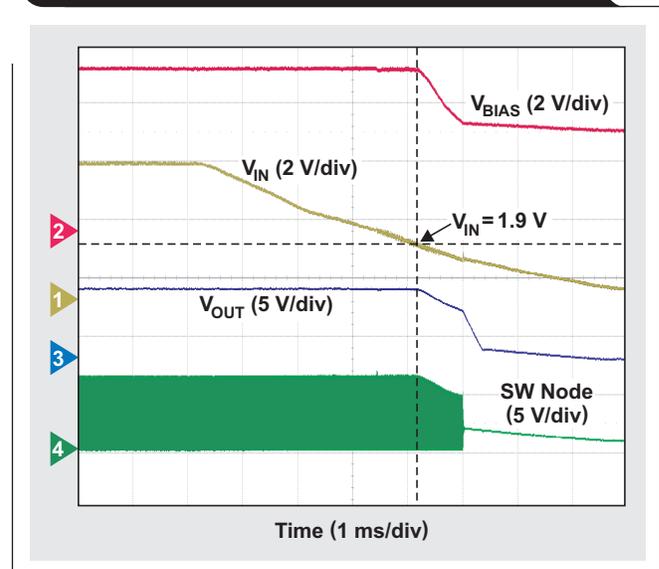

split-rail approach feeding V_{OUT} back as the bias supply works. A separate bias supply different from the battery input is needed.

Fortunately, a bias supply needs to supply only very low power. If there is another supply rail above the UVLO turn-on threshold already available in the system, it can be connected to V_{BIAS} while connecting the power rail (V_{IN})

Figure 6. Split-rail approach using charge pump to produce bias voltage

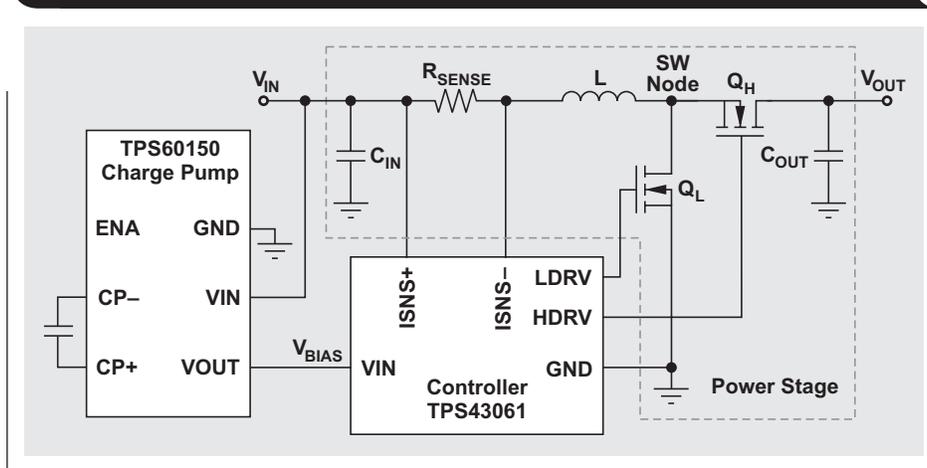

to the battery (Figure 2). If not, a charge pump can be added for a bias supply (Figure 6).

In this example, from the 2.7 V to 4.2 V of battery input, TI's TPS60150 charge pump produces a regulated 5-V supply, which is higher than the UVLO turn-on threshold of the TPS43061 controller, so it can be used as the bias supply. Using a charge pump with the split-rail approach, the boost converter can start up and operate with a single input supply that is lower than the boost controller's UVLO turn-on threshold.

Figure 7 shows the start-up waveforms of the boost converter shown in Figure 6. The converter can start up and operate with a single 2.7 V of supply since V_{BIAS} is regulated at 5 V, although V_{IN} is only 2.7 V. By using this split-rail approach, the boost converter's minimum operating input voltage is extended from 4.1 V to 2.7 V.


Conclusion

Two inputs are usually required for a boost converter to operate: the input supply to the power stage and the bias supply to the controller. The controller's UVLO threshold sets the low limit of the bias supply. It also places a constraint on the input supply to the power stage, if these two rails are connected to share one input supply. Split-rail approaches separate the power rail from the bias supply rail to eliminate the constraint on the minimum operating voltage of the power rail. This extends the input-voltage range of boost converters.

References

1. "Low quiescent current synchronous boost DC-DC controller with wide V_{IN} range," TPS43060/61 Datasheet. Available: www.ti.com/slvsbp4-aaj
2. "TPS60150 5V/140mA charge pump device," TPS60150 Datasheet. Available: www.ti.com/slvs888-aaj

Figure 7. Start-up waveforms of configuration shown in Figure 6

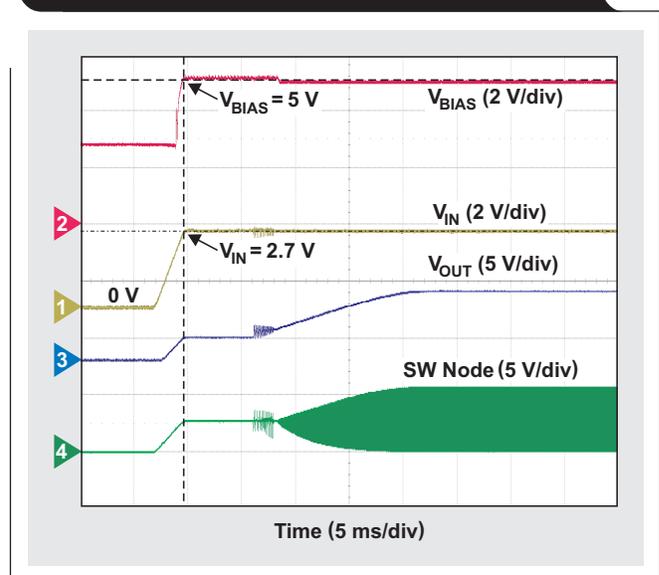

Related Web sites

- Power Management:
www.ti.com/power-aaj
www.ti.com/tps43060-aaj
www.ti.com/tps43061-aaj
www.ti.com/tps60150-aaj
 Subscribe to the AAJ:
www.ti.com/subscribe-aaj

Low-cost flyback solutions for 10-mW standby power

By Adnaan Lokhandwala

Product Manager

For low-power AC/DC conversion, flyback topology remains the preferred choice due to its simplicity and low cost. Using a small number of external components, this topology can provide one or more outputs for a very wide input-voltage range. It is used in isolated and non-isolated forms to cover a broad range of applications, such as battery chargers in smartphones and tablets; auxiliary power supplies in TVs, desktop computers, and home appliances; AC adapters for portable computing, set-top boxes, and networking; and many more. Figure 1 shows the typical power levels in some of these applications. The wide-spread applicability and use of the flyback topology in high-volume consumer markets (estimated 2012 worldwide shipments for the markets shown in Figure 1 alone exceeded a few billion units) make it a perfect candidate for optimizing every possible performance specification, such as cost, efficiency, and standby power.


In most applications, flyback converters are stand-alone external power supplies in wall chargers/adapters. In some cases they are powering either a portion of larger equipment or providing standby power to maintain system functions like the user display and remote control when the equipment is not performing its primary function. In all cases, the standby-power consumption of the flyback

converter is being heavily scrutinized to minimize the overall power drain when it seems the converter is doing nothing. For example, a flyback power supply used in an AC wall charger may have a mass-production specification of less than 30 mW. If the actual supply consumes only 10 mW of standby power, the 20-mW difference can allow a higher margin for leaky circuit components such as input filters, capacitors, and bias components, reducing overall solution cost. Similarly, a flyback converter with low standby-power consumption can allow more system functions to be active in standby mode while keeping the end equipment's total power consumption to a minimum.

The push towards green power

There is an array of initiatives and directives in the power industry addressing efficiency and standby power that vary by end equipment, power level, and governing authority. In the U.S., these include the California Energy Commission and the Environmental Protection Agency's ENERGY STAR[®],¹ and in Europe, the European Union's Standby Initiative, to name a few. After a quick glance at many of these energy-conservation initiatives, it is clear that they all have a common theme—driving minimal power loss at light loads and no-load/standby. Many

Figure 1. Typical power levels for AC/DC flyback-converter designs

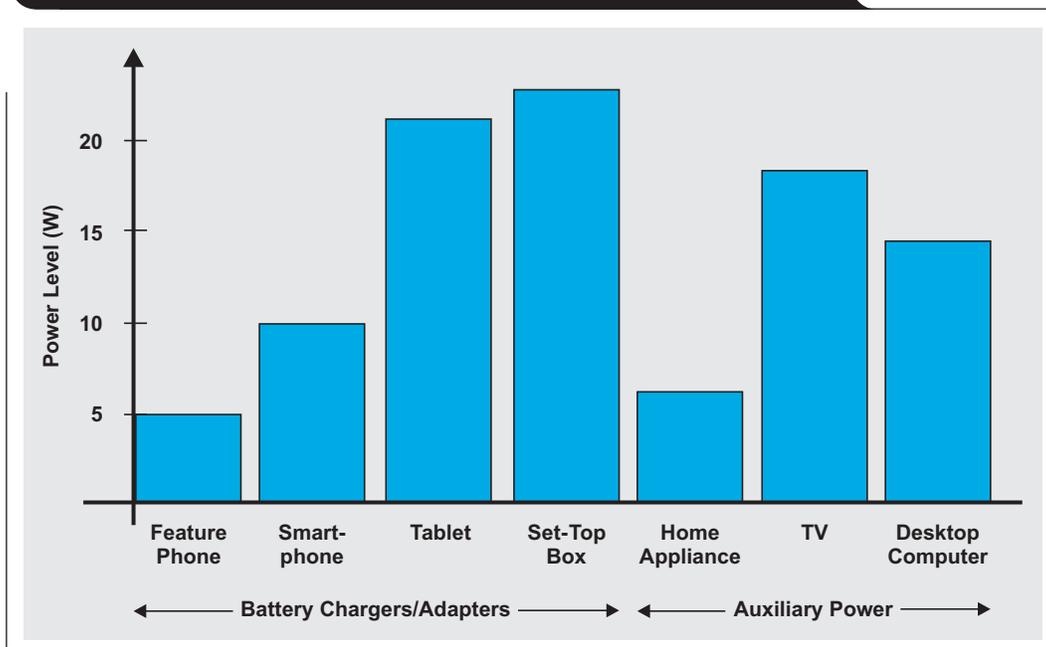

regions in the world are also introducing mandatory and voluntary limits for standby-power consumption and light-load operating efficiency of external power supplies.

In the U.S., the California Energy Commission adopted for its own state a battery-charging efficiency standard that became effective in February 2013. Additionally, the U.S. Department of Energy is finalizing a draft that will affect current regulations for power-supply efficiency worldwide. Similarly, the Joint Research Centre of the European Commission (EC) published the final draft of Version 5 of its Code of Conduct on Energy Efficiency of External Power Supplies in October 2013. These new voluntary specifications, which propose tightening of active-mode efficiency and no-load power consumption, are tougher to meet than the mandatory specifications of the EC's current Ecodesign Directive.

To ensure that the external supply is efficient in the idle and standby modes of some applications, the EC has added an additional efficiency requirement at 10% load beyond the four-point active-mode average-efficiency requirement. The EC also has added an additional classification for mobile handheld battery-driven external supplies of less than 8 W that must limit no-load power consumption to less than 75 mW starting in 2014. Finally, the EC's Ecodesign Directive for energy-related products, Lot 6, Tier 2 took effect in January 2013. This part of the directive limits total system standby-power consumption of household and office equipment to less than 0.5 W.

Less than 10 mW of standby-power consumption

The typical architecture for an isolated flyback converter that consumes less than 10 mW of standby power is shown in Figure 2. Four key elements (labeled A through D) in a


flyback that contribute most to its standby-power loss are shown along with their relative cost. Traditionally, this type of converter compares its output voltage with a secondary-side reference. An optoisolator is used to transfer an error signal across the isolation barrier.

There are two fundamental issues with this approach. First, a low-cost reference like the widely used TL431 shunt regulator from Texas Instruments (TI) needs a minimum cathode bias current (~1 mA) independent of converter loading under all conditions. Second, the standard optocoupler configuration is such that it consumes the most current under no-load conditions. Note that in order to achieve standby-power consumption of less than 10 mW, a more expensive reference such as TI's TLV431 shunt regulator with very low bias current may need to be used for feedback control.

One way to address these issues is to use a constant-voltage, constant-current (CVCC) controller with primary-side regulation, such as TI's UCC28710. This type of controller can simplify and improve performance in AC/DC designs. The UCC28710 regulates the flyback output voltage and output current within 5% accuracy without optocoupler feedback. It also processes information from the primary power switch and transformer auxiliary winding for precise output CVCC control.

To reduce its no-load consumption, the controller enters smart sleep modes as the converter load decreases and the controller reduces its average current consumption down to 95 μ A. The control algorithm modulates the converter's switching frequency and the primary current's peak amplitude while maintaining MOSFET valley switching for high conversion efficiency across line and load. Finally, thanks to high-voltage IC technology, the external HV start-up

Figure 2. Conventional AC/DC flyback consumes less than 10 mW of standby power

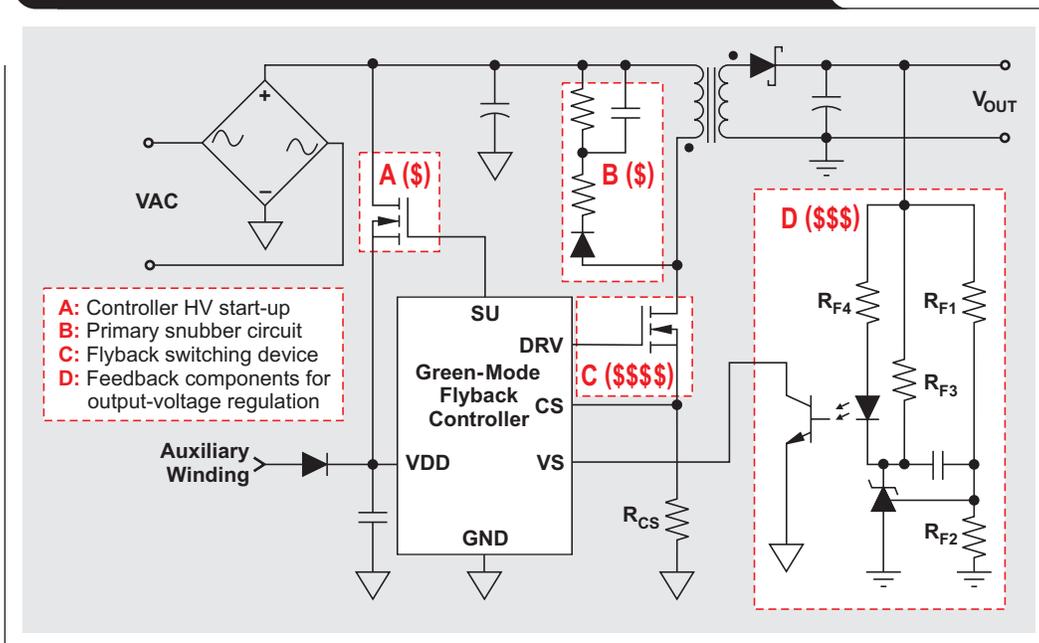

MOSFET is also integrated into the controller to further reduce component count and simplify the solution (Figure 3a).

The choice of a flyback converter switch is very application-specific and performance-driven. In some situations, a bipolar junction transistor (BJT) can be a better choice than a MOSFET. Fundamentally, BJTs cost less than power MOSFETs because their fabrication involves a simpler process with fewer layers, particularly for high-voltage ($\geq 700\text{-V}$) and low-power applications. BJTs with very high voltage ($>900\text{ V}$) are economical options today, making BJT-based designs attractive in off-line power supplies for the industrial market and in regions with widely varying AC utility voltages.

Converters with BJTs can have lower manufacturing cost because they normally have less di/dt and dV/dt switching stress, EMI compliance is easier with no Y capacitor, no common-mode choke is required, and transformer construction is simpler. Also, due to slow di/dt at turn-off, some energy in the transformer's leakage inductance can be dissipated at the BJT turn-off transition, potentially eliminating snubber circuits in some designs. On the flip side, BJTs suffer from higher switching losses, are limited to designs with lower switching frequencies, and require a complex drive scheme.

A highly integrated solution for driving a BJT is shown in Figure 3b. The UCC28720 controller incorporates a driver that dynamically adjusts the base-current amplitude based on the converter load. This ensures that the BJT always operates in optimal switching conditions with minimal switching and conduction losses even for higher-power AC/DC designs.

Figure 3. Simplified flyback schematics


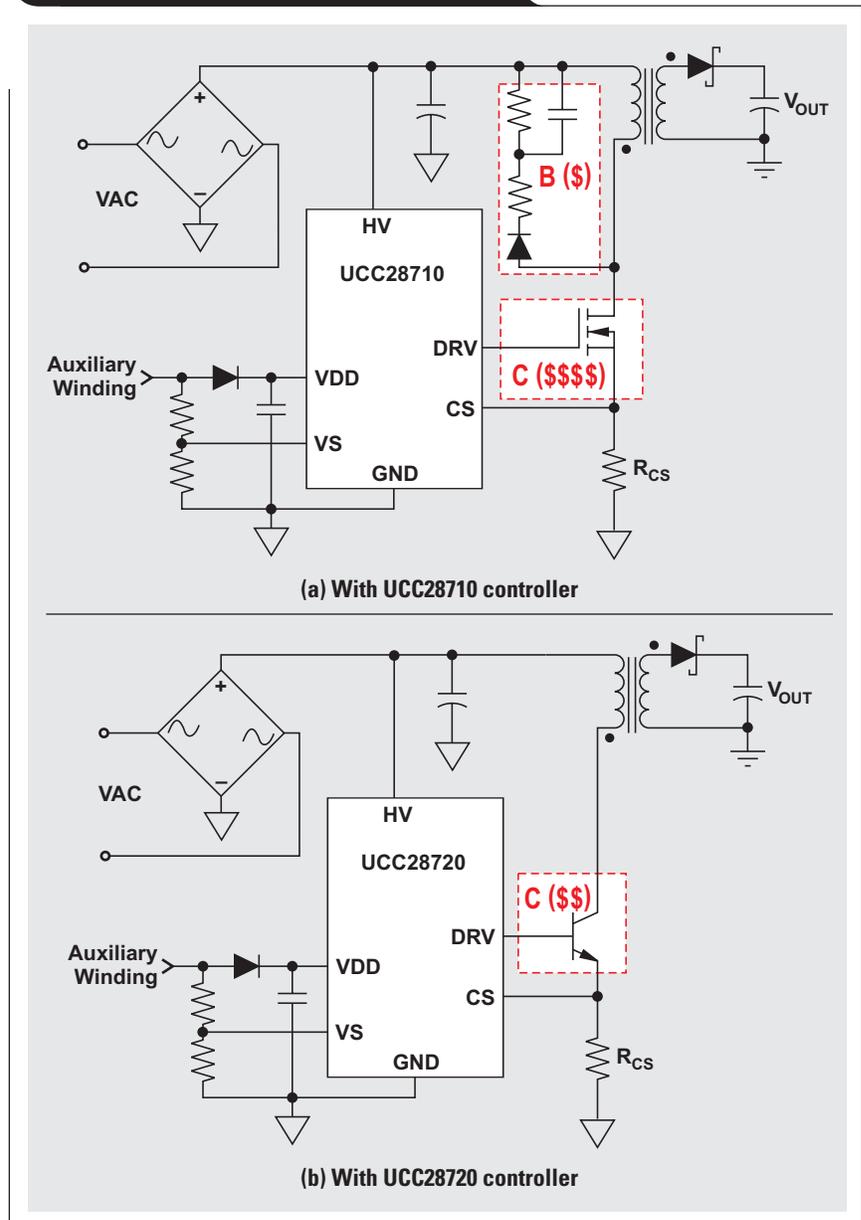


Figure 4. Summary of test data for AC/DC flyback designs with UCC287xx controllers

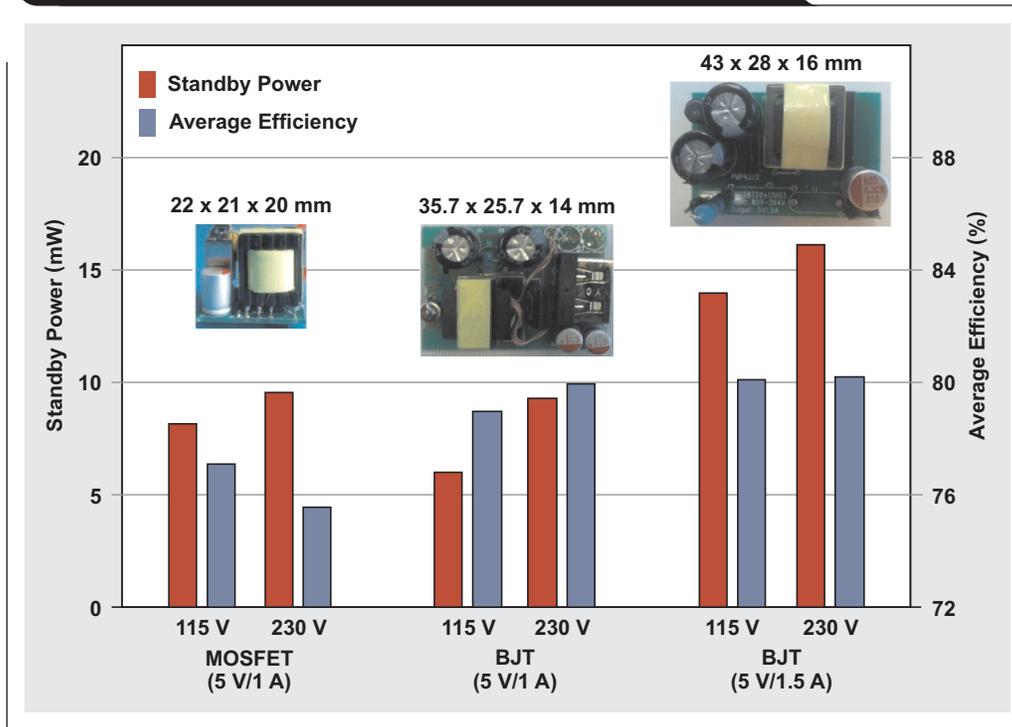

Two 5-V/1-A USB chargers were designed to illustrate some of the preceding points. Their test data are summarized in Figure 4. Note that the controllers enable ultralow standby-power consumption of less than 10 mW. Optimized modulation and drive schemes also facilitate achieving high average efficiency to meet the most stringent worldwide regulations. References 2 and 3 provide links to full test data and a bill of materials for these designs. Test data for a higher-power 5-V/1.5-A design is included in Figure 4 to illustrate that this BJT-based solution can provide an average efficiency of 80+%.⁴

Conclusion

The simplicity and cost-effectiveness of the flyback topology have made it the preferred choice for the many low-power AC/DC designs powering consumer electronics. Power-supply designers are continuously challenged to achieve the same performance at lower cost or improved performance at the same cost. This article has touched on a few of these performance aspects and how the cost of the power-supply solution can be addressed with the smart choice of a power-efficient controller. The UCC28710 and UCC28720 members of TI's 700-V flyback-controller family enable cost-optimal designs with best-in-class standby power and efficiency for compliance with current and future industry standards.

References

1. Adnaan Lokhandwala. (May 20, 2013). "The no-load power crunch: 30 mW and beyond." *Power Systems Design* [Online]. Available: www.powersystemsdesign.com
2. "Universal AC input 5V@1.2A cube charger with <10mW no-load power," Reference Design using UCC28710. Available: www.ti.com/pmp4344-aaj
3. "5V1A low standby power AC charger with low cost BJT solution," Reference Design using UCC28720. Available: www.ti.com/pmp4373-aaj
4. "High efficiency 5V@1.5A adapter using BJT solution," Reference Design using UCC28720. Available: www.ti.com/pmp4372-aaj

Related Web sites

Power Management:

www.ti.com/power-aaj

www.ti.com/tl431-aaj

www.ti.com/tlv431-aaj

www.ti.com/ucc28710-aaj

www.ti.com/ucc28720-aaj

www.ti.com/adapterpower-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Accurately measuring efficiency of ultralow- I_Q devices

By Chris Glaser

Applications Engineer

Introduction

While almost every power-supply engineer intimately knows and understands the lab setup for measuring efficiency, there are many important nuances that must be considered when measuring the efficiency of a device with ultralow quiescent current (I_Q). For a device that consumes less than 1 μA , the circuit's currents are very small and difficult to measure. These measurements may equate to calculated light-load efficiencies that are far lower than what is shown in the datasheet graphs and lower than what would be seen in the real application. This article reviews the basics of measuring efficiency, discusses common mistakes in measuring the light-load efficiency of ultralow- I_Q devices, and demonstrates how to overcome them in order to get accurate efficiency measurements.

Basics of measuring efficiency


Reference 1 details the best setup to accurately measure a device's efficiency with a power-save or pulse-frequency-modulation (PFM) mode. This reference provides an excellent background to the topics covered in this article and should be read first. Generally, and especially in this article, efficiency is defined as

$$\eta (\text{efficiency}) = \frac{\text{Power}_{\text{OUT}}}{\text{Power}_{\text{IN}}} = \frac{V_{\text{OUT}} \times I_{\text{OUT}}}{V_{\text{IN}} \times I_{\text{IN}}}$$

The following summarizes two key points made in Reference 1. The first is that any power-save mode draws relatively large bursts of current from the input supply. These bursts are an AC current from the input. Devices that always operate in continuous-conduction or pulse-width-modulation (PWM) mode draw DC currents from the input supply. Unlike the DC current drawn in PWM mode, the power-save mode's bursts of current create an incorrect RMS-current reading in the input-current meter. Therefore, the proper test setup for measuring efficiency in power-save mode includes sufficient input capacitance after the input-current meter to smooth out the AC currents drawn by the PFM mode in order to present a DC current to the current meter.

The second key point in Reference 1 regards the placement of the voltmeters relative to the current meters. It is critical in both PFM and PWM modes not to include the voltage drops across the current meters in the efficiency calculations. Therefore, each voltmeter should be connected to the input and output voltages on the PCB, ideally at the S+/S- header on most evaluation modules (EVMs). This places the input-current meter out of the circuit and the output-current meter as part of the load. These placements are shown in Figure 1 with the recommended setup for measuring PFM-mode efficiency with the best accuracy.

Figure 1. Recommended setup for measuring PFM-mode efficiency

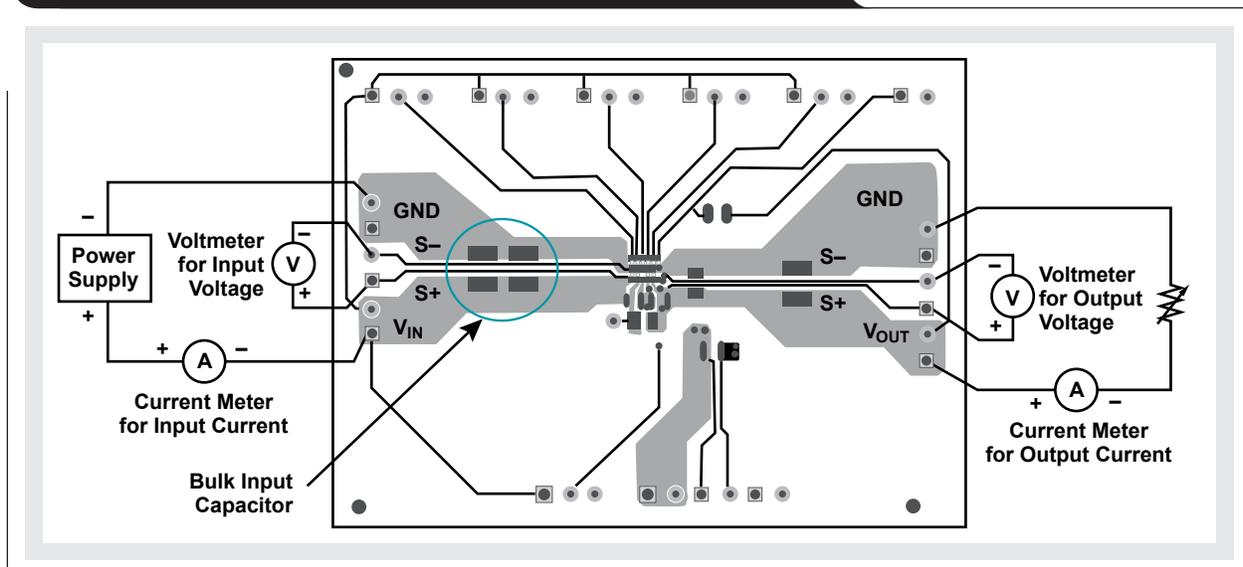

Setup issues in measuring efficiency of an ultralow- I_Q device

Devices with an ultralow I_Q have special considerations for their efficiency-measurement setup. For simplicity, ultralow I_Q can be approximated as less than roughly 10 μA of I_Q . Below this level, the input current drawn by one or both voltmeters, as well as the leakage current of the additional input capacitor, can substantially affect the measured input current and thus the calculated light-load efficiency. Note that if higher-leakage equipment is used, these concerns also would be relevant for higher- I_Q devices. Reference 2 explains I_Q in detail.

Input resistance of the input voltmeter

In the test setup in Figure 1, the two voltmeters have some finite input resistance. For example, the standard handheld, battery-powered Fluke digital multimeter (DMM) has an input resistance of around 10 M Ω . While this certainly seems very large and unlikely to affect the efficiency measurement, calculating how much current it draws when it measures a very common 3.6-V input voltage can be revealing. In this case, when 3.6 V is applied to the DMM's terminals (across its resistance), 0.36 μA of current flows into the meter. This is effectively 360 nA of leakage current that is drawn directly from the input voltage applied to the device and flows through the input-current meter. Just attaching the input voltmeter to the circuit increases the input current by 360 nA. If the measured device has a 20- μA I_Q , then this 360 nA is less than 2% of the input current and is not very significant. But, if a step-down converter like the Texas Instruments (TI) TPS62740 with its 360-nA I_Q is being tested, then this extra current drawn by the voltmeter could be up to half of the input current. This results in quite a large difference in efficiency.

Extra load current through the output voltmeter

A voltmeter connected on the output behaves in the same way. It draws some extra (leakage) current not measured as part of the load's current. This leakage current is not included in the numerator in the efficiency calculation. The output voltmeter creates an extra load, which draws an extra (and measured) input current. With this extra unmeasured load current creating an increased input current, the measured efficiency is lower than the actual efficiency.

High leakage current of the extra input capacitor

Finally, the additional input capacitor used to smooth out the input current might have a sufficiently high leakage to draw substantial current from the input. For example,

some high-capacitance capacitors have maximum leakage currents in the hundreds of microamperes. This leakage may change over time, so it should be checked before any efficiency testing. This extra current, if too high, is sure to throw off the efficiency calculations.


Solutions to measurement-setup issues

There are easy solutions to the three measurement-setup issues just described. The most important point, however, is simply to be aware that the setup used to take efficiency data can cause inaccuracies in the efficiency data collected. This is especially true at light loads, where the currents are very small and difficult to measure.

Overcoming the effects of the input voltmeter's input resistance

There are three methods of accounting for current leakage through the input voltmeter: (1) disconnecting the voltmeter, (2) connecting it in a different location, or (3) compensating for the current into it. The first and simplest method is to record the input voltage with the voltmeter connected as usual and then disconnect the voltmeter from the input terminals before recording the input current. This accurately measures the input voltage without increasing the input current. Minimal measurement inaccuracy is introduced by this method. What is not advisable is to read the input voltage from the display on the input supply (which typically is not calibrated) and use this value for the efficiency calculations. Rather, a high-quality, high-resolution voltmeter should be used to measure the input voltage at the EVM. This overcomes small voltage drops in wires and cabling between the input supply and the EVM.

The second method of accounting for the leakage current is to connect the input voltmeter in a different location. Specifically, the voltmeter's positive lead can be connected to the input-current meter's positive side, while the voltmeter's ground lead remains connected to the same location as before (the S- header on the EVM). In this way, the input voltmeter does not draw any measured current and so does not affect the calculated efficiency. The downside of this method is that the voltage drop across the input-current meter is not accounted for. At very light loads, however, such a drop is usually insignificant. To minimize this inaccuracy at heavier loads, the input voltmeter can be moved to its original location (after the input-current meter) once the measured input current is about 100 times greater than the leakage current into the voltmeter. This allows for a simple setup where the input voltmeter remains connected throughout testing and inaccurate measurement is minimized.

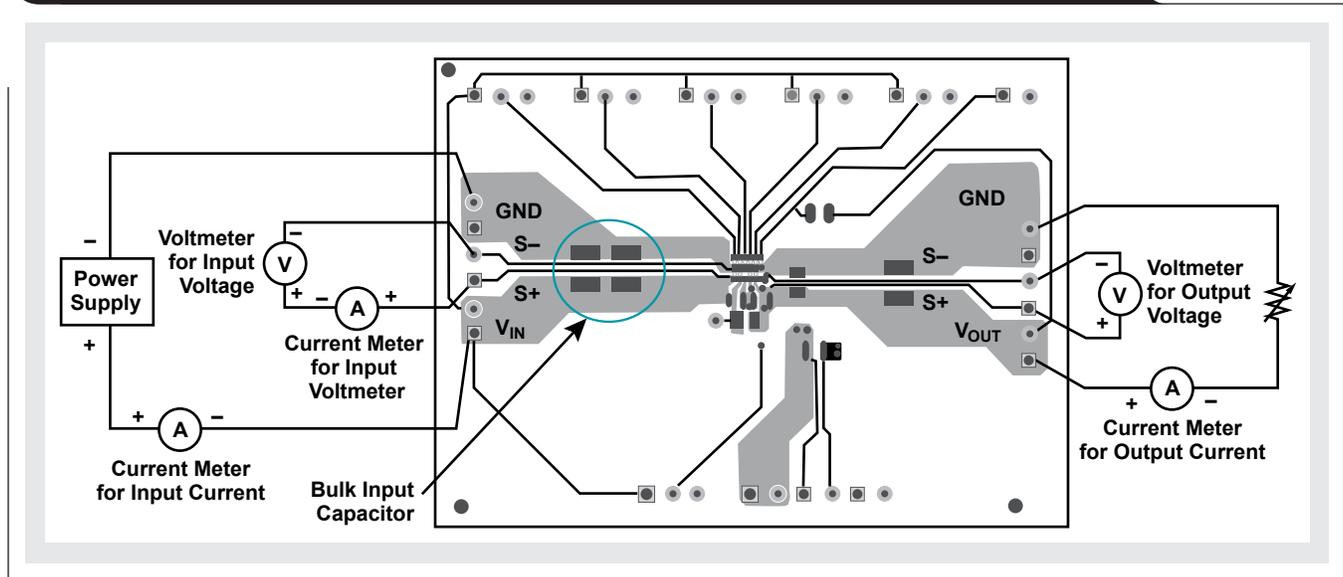Figure 2. Efficiency-measurement setup to compensate for leakage into the input voltmeter

The third method of accounting for the leakage current into the input voltmeter is to measure the current through it with an additional current meter (Figure 2). The current through this new current meter is subtracted from the measured input current. The result is used to compute the efficiency. This is the most accurate way of accounting for the leakage current into the input voltmeter. The computed efficiency is highly accurate because the input voltmeter remains connected where it should be throughout the entire testing. Furthermore, assuming that the input voltage is not varied considerably throughout testing, the leakage current also remains fairly constant. This fact allows for a single measurement of the leakage current to be made at a given input voltage and for this value to be used for all data points in the efficiency testing. In other words, it is not necessary to record the data of this extra multi-meter for all measurement points.

Overcoming the extra load current through the output voltmeter

The leakage current into the output voltmeter can be accounted for in the same three ways as for the input voltmeter. The first method (disconnecting the output voltmeter) can be used in exactly the same way—connecting the voltmeter as usual, reading the output voltage, then disconnecting it and reading the input current. The second method (connecting the voltmeter in a different location) is slightly different for the output voltage. In this method, the output voltmeter should be connected after the output current meter so that its current sums with the load's current to give the total output current. Once the load current is about 100 times greater than the leakage


current into the output voltmeter, the voltmeter can be moved back to its usual location on the S+/S− header. The third method (compensating for the current drawn by the voltmeter) can be used in the same way as for the input voltmeter. Note that for this method the load current used to graph the efficiency data should be the sum of the current into the load and the leakage current into the output voltmeter. Not accounting for this may slightly shift the efficiency graph on the load-current axis.

Of course, the best way to eliminate errors from leakage currents into the voltmeters is to use voltmeters with extremely low leakage currents. For example, the efficiency data in the TPS62740 datasheet³ was taken with Agilent 34410A multimeters. Their 10-G Ω input-resistance setting was used for the voltage measurements, producing a negligible amount of leakage current with no effect on the calculated efficiency.

Minimizing leakage current from the extra input capacitor

Finally, the leakage of the input capacitor is best mitigated by choosing a proper bulk input capacitor. X5R or X7R dielectric ceramic capacitors and their inherent low-leakage currents are recommended for measuring ultralow-power efficiency, as the ceramic technology used in these capacitors produces the lowest leakage currents. If the voltage is too high for a ceramic capacitor, then a low-leakage-current polymer or tantalum capacitor should be used. It is important to consult the datasheet of the chosen capacitor to determine if its leakage might cause measurement errors. It is also important to measure the leakage current of the exact capacitor used in the efficiency testing.

Figure 3. Efficiency comparison of different test setups

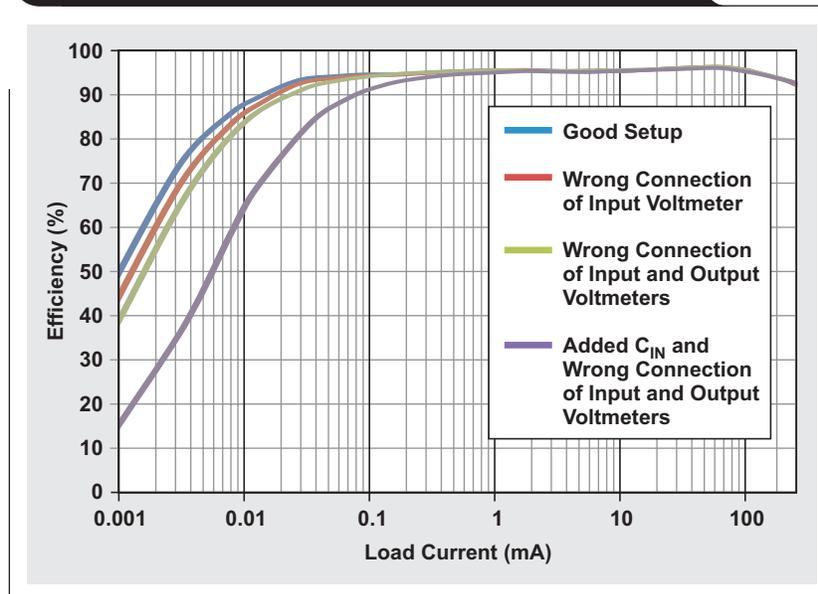

Test results of efficiency-measurement setups

Figure 3 compares the measured efficiency of several different test setups that used the TPS62740EVM-186 evaluation module.⁴ A proper test setup with a 100- μ F ceramic bulk input capacitor was used, with compensation for the leakage current into the input and output voltmeters. This bulk input capacitance was sufficient to produce accurate results, as was evidenced by a DC input current. If longer wires from the input supply with their larger impedance had been used instead, the input-current shape might have changed to be more sinusoidal. This would have produced an inaccurate input-current reading and shows that more bulk input capacitance would have been required for an accurate measurement.

Figure 3 also shows the test results of three improper test setups: the input voltmeter's leakage not accounted for, the output voltmeter's leakage not accounted for, and an extra input capacitor with about 5 μ A of leakage. For the three improper test setups, the wrong configurations build on one another; they are additive. The wrong connection of input voltmeter used the correct input capacitor as well as the correct output voltmeter. The wrong connection of input and output voltmeters used the correct input capacitor. The setup using the leaky input capacitor also used the wrong connection for the input and output voltmeters. As expected, less accurate efficiency measurements were obtained with worse test setups.

Other considerations in measuring efficiency

With an understanding of the impact that measurement setups have on measuring an ultralow- I_Q device's efficiency, there are two final considerations that deserve a mention: the remote-sense lines on the input supply, and the use of external or internal feedback resistors. Though less commonly seen, each of these has an impact on efficiency.

An input-power supply with remote-sense capability is sometimes used in efficiency-measurement test setups to provide a regulated input voltage as the load and voltage drop across the input-current meter change. However, just like the input voltmeter, these remote-sense lines draw current. In many instances, this current is relatively large—sometimes in the hundreds of microamperes. Needless to say, such high currents drawn by the test setup certainly affect the calculated efficiency and produce erroneous results. Therefore, for best results, the remote-sense lines of the input supply should be connected *before*, not after, the input-current meter.

A final consideration in measuring the efficiency of ultralow- I_Q devices is whether to use external or internal feedback resistors to set the output voltage. Most power supplies use two external resistors between the output voltage, FB pin, and ground to set the output voltage. This gives the user full flexibility to set the output voltage at any desired point. However, with external resistors and the highly sensitive external FB pin come more susceptibility

to noise. Any external noise seen at the FB pin is gained up, resulting in an incorrect output voltage. To avoid this, the two feedback resistors typically should have between 1 and 10 μA of current flowing in them to keep them robust against external noise sources. Since this current is not flowing to the load, it should be considered a loss that results in decreased efficiency.

To keep efficiency high, the FB pin and two resistors should be located inside the power supply to remove them from the variable and noisy external environment. In this way, a large resistance with minimal current flow is used for the feedback resistors, and efficiency is not significantly lowered. While internal feedback resistors fix the output voltage inside the power supply and prevent the user from having every possible output voltage available, a step-down converter like the TPS62740 overcomes this limitation. It has four digital input pins that allow the user to choose from among the most common output voltages ranging from 1.8 V to 3.3 V. As well, many other TI TPS62xxx devices internally set the output voltage to be either completely fixed (as in the TPS62091) or adjustable via I²C (as in the TPS62360). These low-I_Q devices are preferred because they do not lower the efficiency with external resistors but still allow sufficient user configurability.

Conclusion

Accurately measuring the efficiency of ultralow-I_Q devices is difficult because the currents in the circuit are very small. The basic efficiency-measurement test setup must be slightly altered to achieve accurate measurement

results that reflect the capability of the real circuit in the final application. Accounting for and/or eliminating the various leakage currents in the measurement equipment is the key to an accurate measurement.

References

1. Jatan Naik, "Performing accurate PFM mode efficiency measurements," Application Report. Available: www.ti.com/slva236-aaj
2. Chris Glaser, "I_Q: What it is, what it isn't, and how to use it," *Analog Applications Journal* (2Q, 2011). Available: www.ti.com/slyt412-aaj
3. "360nA I_Q step down converter for low power applications," TPS62740 Datasheet. Available: www.ti.com/slvsb02-aaj
4. "TPS62740EVM-186 Evaluation Module," User's Guide. Available: www.ti.com/slvu949-aaj

Related Web sites

Power Management:

www.ti.com/power-aaj

www.ti.com/tps62091-aaj

www.ti.com/tps62360-aaj

www.ti.com/tps62740-aaj

www.ti.com/tps62740evm-aaj

www.ti.com/dcs-control-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

When is the JESD204B interface the right choice?

By Sureena Gupta

Worldwide Analog Marketing

Introduction

Anyone involved in high-speed data-capture designs that use an FPGA has probably heard the buzzword for the new JEDEC standard: JESD204B. Recently a lot of engineers have contacted Texas Instruments requesting information on the JESD204B interface, including how it works with an FPGA and how it will make their designs easier to execute. So what is the JESD204B interface all about? This article discusses the evolution of the JESD204B standard and what it means to a systems design engineer.

What led to the JESD204B standard?

About ten years ago, designers of high-speed data converters switched from using the traditional single-ended CMOS interface to using a differential LVDS interface because the latter enabled higher data rates. (The CMOS interface is limited to about 200 Mbps.) The LVDS interface also improved noise coupling on signal lines and power supplies. The drawback of this interface was higher power consumption at lower sampling speeds. This gave the CMOS interface a reason for existence, and it is still being used today.

But with the evolution of analog-to-digital converters (ADCs) requiring faster sampling rates and higher channel density, the industry was demanding a faster, more power-efficient digital interface than parallel LVDS. In order to overcome this challenge, a true serial interface called JESD204 was developed and approved by JEDEC in April 2006. The JESD204 interface is defined as a single-lane, high-speed serial link connecting single or multiple data converters to a digital logic device with data rates of up to 3.125 Gbps. It needs a common frame clock sent to the converter and the FPGA to synchronize the frames.

Supporting only one lane and one serial link, JESD204 was soon viewed as not quite as useful as initially hoped, so in April 2008 the standard was revised to JESD204A. JESD204A extended support for multiple aligned lanes and multipoint links, but the maximum speed was still limited to 3.125 Gbps. This drove the development in July 2011 of JESD204B, which promises to address several different system-design challenges. Besides drastically increasing the supported data rates from 3.125 Gbps to 12.5 Gbps, it also greatly simplifies multichannel synchronization by adding the deterministic latency feature.

What is the JESD204B standard?

JESD204B supports interface speeds of up to 12.5 Gbps, uses a device clock instead of the previously used frame clock, and has three different subclasses. Subclass 0 is backward-compatible with JESD204A except with higher speeds, and it does not support deterministic latency. Furthermore, the SYNC signal has special timing requirements for error reporting (Figure 1). Subclass 1 uses synchronization signal SYSREF to initiate and align the local multiframe clocks across devices (Figure 2). This

Figure 1. JESD204B Subclass 0 interface


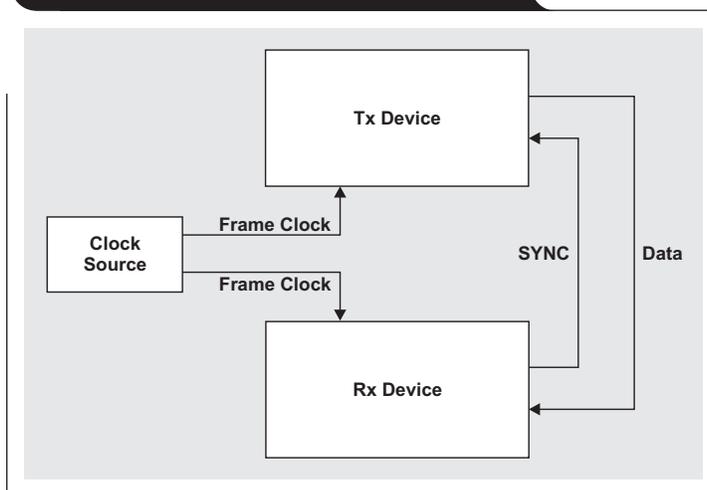


Figure 2. JESD204B Subclass 1 interface

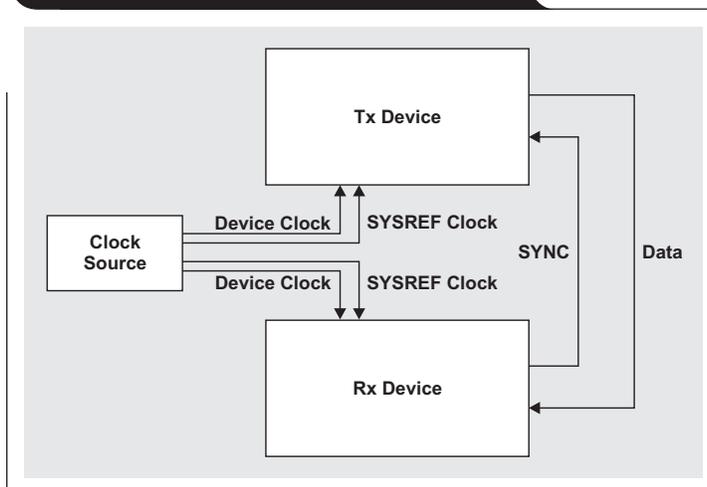

synchronizes data transmission and achieves a known, deterministic latency across the digital link. Subclass 2 uses the SYNC signal for that same purpose (Figure 3). Due to SYNC timing constraints, Subclass 2 typically is employed for data rates lower than 500 MSPS. For speeds higher than 500 MSPS, Subclass 1 with an external SYSREF clock is commonly preferred.

JESD204B-compliant receivers are outfitted with an elastic buffer that is used to compensate for skew across serializer/deserializer (SerDes) lanes, which simplifies board layout. This elastic buffer stores the data until the data from the slowest lane arrives. It then releases the data from all lanes simultaneously for digital processing. This skew management is possible because the data clock is embedded in the serial data stream.

Why care about the JESD204B interface?

Since JESD204B-compliant data converters serialize and transmit output data at a much higher rate than with previous interfaces, the number of pins required on the data converters as well as on processors or FPGAs is drastically reduced, translating to smaller package sizes and lower cost. However, the biggest benefits from the reduced pin count may be a much simpler layout on the printed circuit board (PCB) and easier routing because there are much fewer lanes on the board.

Layout and routing are further simplified by the reduced need for skew management, which is made possible by the data clock now being embedded in the data stream and the presence of the elastic buffer in the receiver. Hence, the need for trace squiggles to match lengths is eliminated. The JESD204B standard also allows longer transmission distances. Relaxed skew requirements enable logic devices to be placed much farther from data converters to avoid any impact on sensitive analog parts.


Additionally, the JESD204B interface is adaptable to different resolutions of data converters. This removes the need for physical redesign of transceiver/receiver (Tx/Rx) boards (logic devices) for future ADCs and digital-to-analog converters (DACs).

Does this mean the end for the LVDS interface?

The CMOS interface provides lower power consumption for data converters with lower data rates, while the JESD204B interface offers a few benefits over the traditional LVDS interface. So does the LVDS interface have any chance of survival?

The simple answer is yes. While the JESD204B standard has simplified multichannel synchronization by using

Figure 3. JESD204B Subclass 2 interface

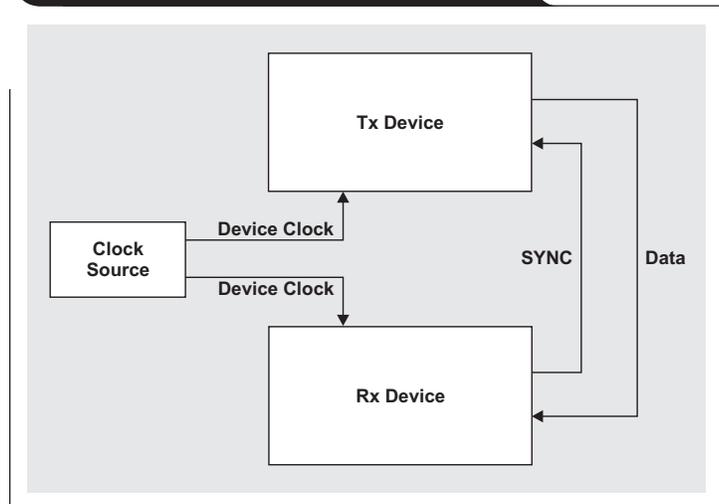

deterministic latency, there are applications that require minimal latency (and, in an ideal world, no latency). These applications (for example, aerospace applications like radar) need an immediate response to an action or detection. Any possible delay must be minimized. For these applications, the LVDS interface should be considered, since the JESD204B-compliant data converter's delay in serializing the data is omitted.

Conclusion

This article has discussed the evolution of the JEDEC JESD204B standard and has explained the many benefits of using this type of interface, including faster data rates, simplified PCB layout, smaller package sizes, and lower cost. It is hoped that the reader now understands the JESD204B-based system a little better.

References

1. "Analog for Altera FPGAs," Texas Instruments. Available: www.ti.com/altera-aj
2. Thomas Neu. (Aug. 2, 2013). "Enabling larger phased-array radars with JESD204B." *RF Globalnet* [Online]. Available: www.rfglobalnet.com

Related Web sites

Interface:

www.ti.com/interface-aj

Subscribe to the AAJ:

www.ti.com/subscribe-aj

CAN bus, Ethernet, or FPD-Link: Which is best for automotive communications?

By Mark Sauerwald

Applications Engineer

Introduction

In 1915 Ford Motor Company introduced electric lights and an electric horn to its Model T automobile. Since then, the dependence on electrical and electronic systems in automobiles has been steadily increasing. The initial systems tended to be local and independent. For example, a switch that controlled the headlights was connected directly to the battery. Today, however, these systems are all interconnected. When a car's headlights are turned on, the dashboard lighting, mirrors, and other systems may all adjust to the new conditions. For this to work properly, the various different systems must communicate with one another. As the automobile has evolved, so have the networks used within it to make this communication possible. As autonomously driven vehicles continue to be developed, there will be an even greater demand for data transport within the vehicle and between vehicles. This article examines three automotive communications standards—the controller area network (CAN) bus, Ethernet, and Flat Panel Display Link (FPD-Link)—and explores which interface best suits which system.

CAN bus


The CAN bus was initially developed by Robert Bosch GmbH in the 1980s. Today it is supported by several manufacturers of integrated circuits and subsystems and

is used in all modern automobiles. The CAN bus allows different controllers or processors on the bus to communicate with one another via messages that are passed on the bus. There is a method for prioritization so that lower-priority messages do not interfere with higher-priority messages. The CAN bus operates at speeds of less than 1 Mbps, and message lengths (CAN frames) are typically 50 to 100 bits in length.

Since a CAN bus can be shared by many different controllers, it is generally not very good for sending messages that might require updates more than approximately 100 times per second. Ideally it is suited for relaying much slower status updates from sensors to the engine-control unit. This includes applications such as communication about other mechanical systems (transmission, braking, cruise control, power steering, windows, door locks, and others) where the amount of data is limited and the bandwidths involved tend to be relatively low.

Further reducing the overall transmission speed is the fact that automotive systems have become more complicated, with more sensors and processors being added to the network. Figure 1 shows a CAN bus being used for both door- and climate-control functions. Since each of these is a low-bandwidth application, there is little concern about one interfering with the other. However, if the same bus is also handling a higher-bandwidth, more critical function

Figure 1. Portion of a CAN-bus implementation

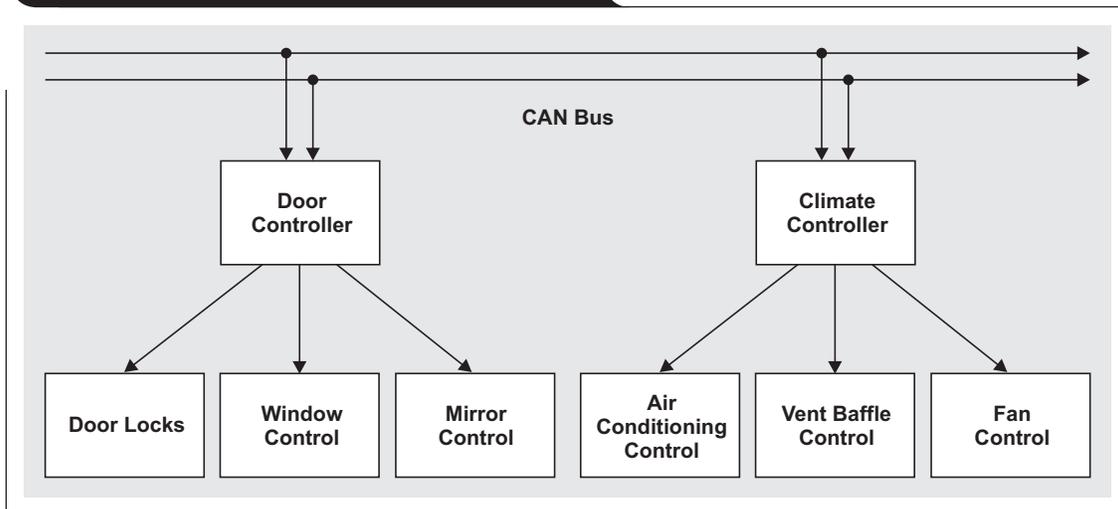

such as engine control, the priorities of door and climate control need to be set low enough so that these functions do not interfere with engine control.

The net result is that the CAN bus is well suited as a communications network between the mechanical sensors and systems within a car, but it is not readily extended to the higher-bandwidth requirements of applications such as entertainment systems or sensors for cameras or radar.

Ethernet

Ethernet is one of the most common high-speed interfaces found in homes and offices, and there are some automobiles where Ethernet is being used to transport a variety of high-speed data. Like the CAN bus, Ethernet is a packetized system, where information is transferred in packets between nodes on various parts of the network. Also like the CAN bus, Ethernet is bidirectional, and the speed possible on any individual link decreases as the number of nodes on the system increases. Still, Ethernet can transport data over a link 100 times faster than a CAN bus.

Ethernet is good for midbandwidth communications in applications such as navigation systems and control. It can be used in much the same way as a CAN bus while providing much more bandwidth. Ethernet would be an ideal choice to replace the CAN bus, but since Ethernet's cost per node is higher, it probably will not replace but rather will augment the CAN bus.

Some cars today are using Ethernet for data-intensive requirements such as backup cameras and entertainment systems. Of particular interest in automotive applications is the DP83848Q-Q1 from Texas Instruments (TI). This is an Ethernet PHY, screened to AEC-Q100 grade 2, and includes a loopback test mode for facilitating system diagnostics.

To transport video over an Ethernet network, even if there is only one video channel being transported, the video must be compressed at its source, then decompressed at the destination to avoid exceeding Ethernet bandwidth limitations. For an application such as a backup camera, this implies that there needs to be a relatively high-power processor in the camera to compress the image sufficiently to get it into the Ethernet network. This in turn means that the camera will be physically larger and more expensive and will have higher power dissipation than a solution that doesn't require much image processing. Another disadvantage of this solution is that video compression and decompression add latency to the link.

If the same Ethernet network is shared by several cameras or other video sources in the car, there is a trade-off between the amount of compression (and corresponding video quality) and the number of video channels that can

be supported. This limitation could be mitigated by setting up multiple networks within the car in a hierarchical configuration. There might be one network that deals only with engine control and diagnostics, a second network that handles backseat entertainment and the audio system, and another network that handles driver-assist functions such as vision-enhancement cameras. In the end, Ethernet provides greater capacity than the CAN bus, at the expense of greater complexity, but still struggles to handle the highest-bandwidth applications such as video.


FPD-Link

FPD-Link is a technology developed for point-to-point transport of high-bandwidth data. It has one forward channel with a very high speed of several gigabits per second and a low-speed back channel. The back channel can be used to transport an I²C bus at 400 kbps or it can control GPIO lines at rates of up to 1 Mbps. FPD-Link was developed to transport video data within the car. For example, it can be used to send uncompressed video to a video display while the back channel sends information from a touch panel on the display screen back to the processor generating the video. The physical layer for FPD-Link is either a twisted-pair or coaxial cable. The wiring is dedicated, so if FPD-Link is used for a backup camera, one cable goes from the backup camera to a processor, and a second cable goes from the processor to the display in the cabin.

The big advantage of using FPD-Link in this application is that both the camera and the display can be much simpler circuits, since compression and decompression are not required. Additionally, since the links are dedicated, the image quality of one video system is independent of what else is going on in the vehicle. The back channel can be used to configure a camera, operate a zoom lens, or send touch-screen information back to a controller without interrupting video flow on the forward channel.

For autonomously driven vehicles, another important factor will be the amount of latency in the link. The processing required to compress and decompress an image adds to this latency. For an application such as backseat entertainment, a delay between reading the data from a DVD and its display on the screen is not important. However, if the image being transported is from a camera looking for pedestrians in the path of the vehicle, latency may have dire consequences.

FPD-Link is perfect for critical links where high bandwidth and low latency are the most important factors. Additionally, with the ability to support a back channel and power over a single twisted-pair or coaxial connection,

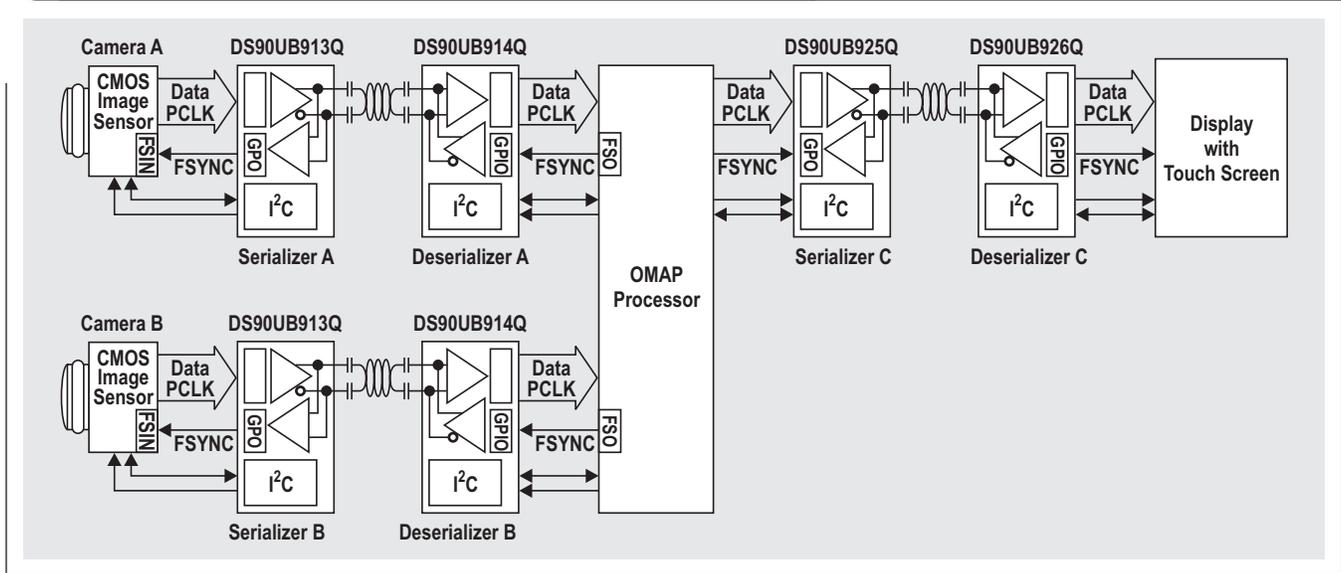Figure 2. Using FPD-Link to connect dual cameras and display


wiring can be simplified. Figure 2 shows an OMAP™ video processor connected to two different cameras, and a display with a single twisted-pair cable going to each peripheral. This twisted-pair cable supports camera video data and touch-screen/camera-setup data. It can also provide power for the display or camera. Since each link is dedicated to one peripheral, there is no risk of interference between the signals from the two cameras.

Conclusion

So which interface is best for automotive communications? They all are—but each for its own purpose. The CAN bus reigns supreme for low-speed control applications where cost is a driving factor. When bandwidth requirements move up, Ethernet can step in as an enhanced interface to support moderate bandwidth requirements. When the

highest bandwidth and lowest-latency link are required, such as for a surround-view camera system providing input to an autonomous vehicle pilot, then FPD-Link is ready to meet the challenge.

Related Web sites

Interface:

www.ti.com/interface-aa

www.ti.com/dp83848qq1-aa

www.ti.com/ds90ub913qq1-aa

www.ti.com/ds90ub914qq1-aa

www.ti.com/ds90ub925qq1-aa

www.ti.com/ds90ub926qq1-aa

Subscribe to the AAJ:

www.ti.com/subscribe-aa

New-generation ESD-protection devices need no V_{CC} connection

By Roger Liang

High Volume Linear

Introduction


As digital and analog ICs grow increasingly sensitive to electrostatic-discharge (ESD) damage due to their shrinking process nodes, discrete ESD-protection diodes have become necessary to guarantee sufficient system-level ESD protection. In the past, the V_{CC} connection was added to diodes to reduce their junction capacitance. With the advent of new diode technology, this is no longer required. This article explains the V_{CC} connection's necessity in the past and the advantages of not having to use it in the present.

ESD is the release of built-up static electricity when two objects of different electric potential come into contact. For example, on a dry winter day, up to 20 kV of ESD can build up simply from packing a printed circuit board (PCB) into a foam-lined box. To ensure that electronic end equipment is immune to everyday ESD events, discrete diodes with more robust ESD ratings than the standard 2-kV human-body model (HBM) are often required. The ESD rating of discrete diodes is directly proportional to the area of the diode's p-n junction; however, the bigger the junction, the larger is the parasitic capacitance. In order not to compromise a diode's ESD rating, adding a V_{CC} connection is one IC design technique that effectively decreases the diode's parasitic capacitance, but at the risk of damaging any other device connected to V_{CC} . However, recent improvements in process technologies have allowed diode designers to remove the V_{CC} connection while still guaranteeing a high ESD rating with low capacitance.

Diode characteristics

A diode is the most basic semiconductor device. It is made from a p-type and an n-type junction and has two terminals: an anode at the p-type end and a cathode at the n-type end (Figure 1). When a large enough voltage is applied from the cathode to the anode (reverse biasing), the diode enters its breakdown region and, in theory, can conduct an infinite amount of current at zero resistance. A voltage applied in the other direction (forward biasing) causes the diode to enter its forward-conducting region. Figure 2 shows the IV curve of a basic


Figure 1. Construction of a diode

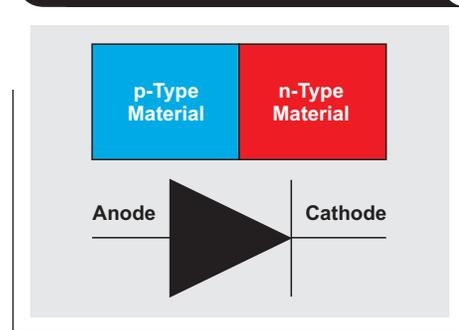

diode with the anode grounded and voltage swept across the cathode. While there are many types of diodes made for different applications, the topic under discussion is ultrafast-response diodes made for ESD-protection applications. These diodes can respond to a high ESD voltage very quickly and clamp thousands of volts to just tens of volts in a matter of nanoseconds by shunting the ESD current to ground.

There are two contributing factors to a diode's parasitic capacitance: junction capacitance (due to charge variation in the depletion layer) and diffusion capacitance (due to excess carriers in the quasi-neutral region). Junction capacitance dominates in the reverse-biased region, which is the

Figure 2. Diode IV curve

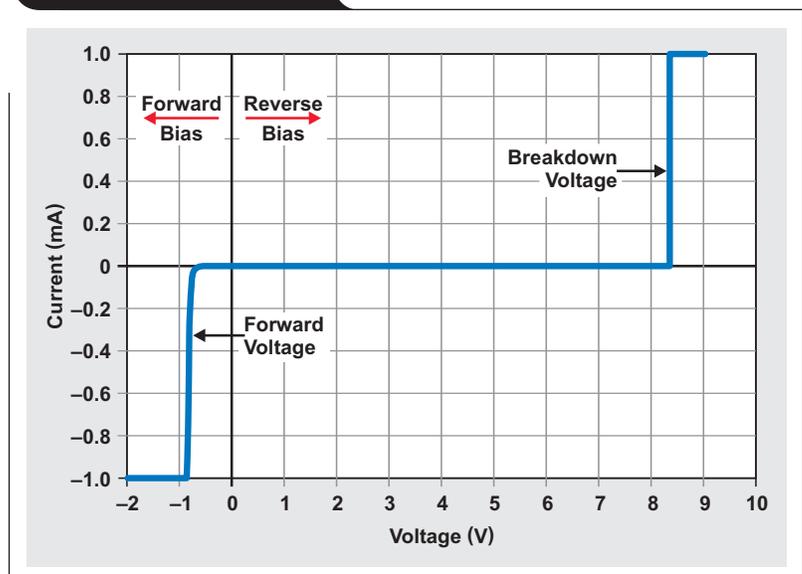

usual application region for ESD diodes. The junction capacitance of a diode is characterized by

$$C_j (V) = A \sqrt{\frac{\epsilon_{Si} q}{2} \left(\frac{N_A N_D}{N_A + N_D} \right)} \left(\frac{1}{\sqrt{\phi_0 - V_A}} \right),$$

with the following definitions:

A is the area of the junction.

ϵ_{Si} is the dielectric constant of silicon.

q is one coulomb charge.

N_A is the acceptor doping concentration.

N_D is the donor doping concentration.

ϕ_0 is the built-in voltage of the junction.

V_A is the bias voltage applied on the junction.

On the application level, the more V_A is applied, the lower the junction capacitance will be (Figure 3). This is the reason why older diode technology required a V_{CC} bias in order to adjust V_A and bring down the parasitic capacitance. Having a V_{CC} connection also allows a systems engineer to add a large capacitor at the V_{CC} node (Figure 4), which serves as a charge reservoir to absorb some extra ESD energy, thus increasing ESD protection incrementally.

Figure 3. TPD4E001 capacitance versus bias voltage

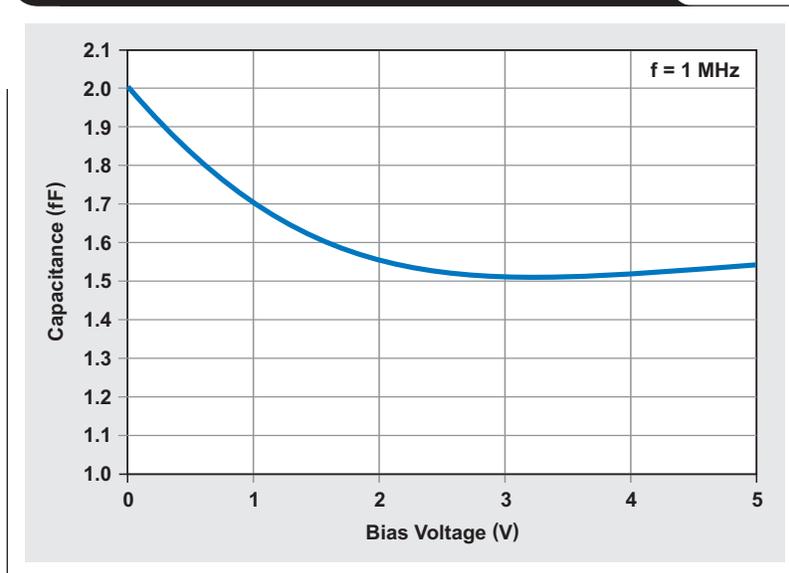


Figure 4. Older diode technology with V_{CC} connection

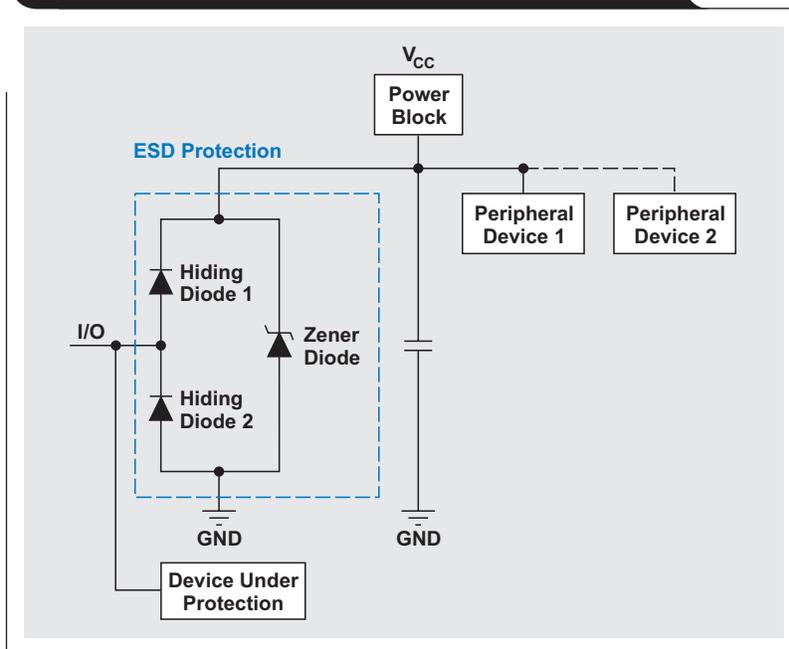


Figure 5. Discharge path of positive ESD strike


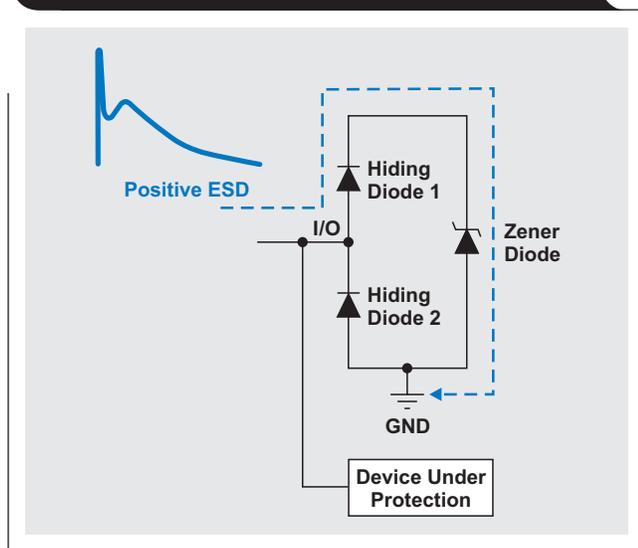


Figure 6. Discharge path of negative ESD strike

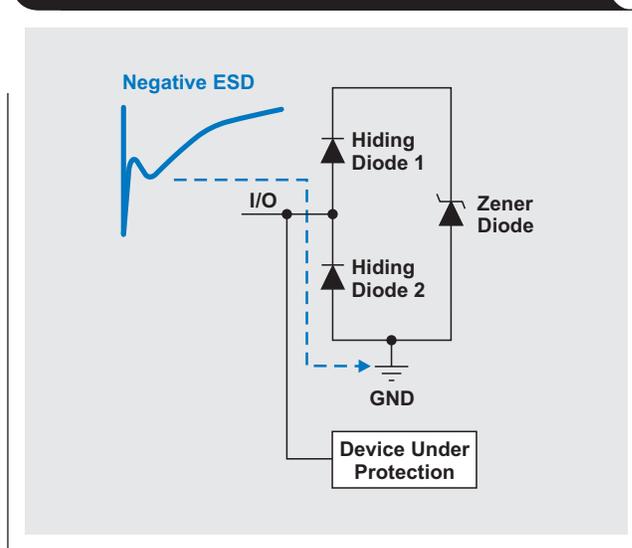

Using high-speed diodes for ESD protection

To design a low-capacitance diode structure with a high ESD rating, a three-diode approach often is used (see Figures 5 and 6), for three reasons:

1. A diode can withstand much more current in the forward-conducting region than in the reverse-breakdown region.
2. Hiding Diode 1 with the Zener diode protects against positive ESD strikes.
3. Hiding Diode 2 protects against negative ESD strikes.

Two smaller *hiding* diodes are connected in series with a larger Zener diode because the hiding diodes' smaller capacitance effectively hides the Zener diode's large capacitance due to the series structure. During a positive ESD event, Hiding Diode 1 enters its forward-conducting region. The Zener diode enters its reverse-breakdown region, creating a path for ESD current to be shunted to ground without entering the device under protection. The size of the larger Zener diode allows it to withstand the large amount of current flow in its breakdown region. During a negative ESD event, Hiding Diode 2 enters its forward-conducting region and channels ESD energy directly to ground. During either event, the hiding diodes can handle the large amount of ESD current flow because they never break down and enter only the forward-conducting region.

Advantages of not using a V_{CC} connection


Diode-fabrication technology has made great improvements over the past few years that have enabled a lower junction capacitance without sacrificing a high ESD rating. These improvements are:

- Moving away from a lateral diode structure to a vertical diode structure
- Increased unit area ESD performance
- Less N_A and N_D doping to reach the same forward and breakdown voltages

These improvements mean a V_{CC} connection is no longer required to bring down the junction capacitance to support high-speed interfaces. Having no V_{CC} connection gives the systems engineer the following three advantages.

1. No current leakage into internal power supply

If a higher-voltage input signal is connected to the ESD diode I/O with a lower V_{CC} level, signal current could leak through Hiding Diode 1 into the V_{CC} and other devices connected on that node (Figure 7). This could damage either

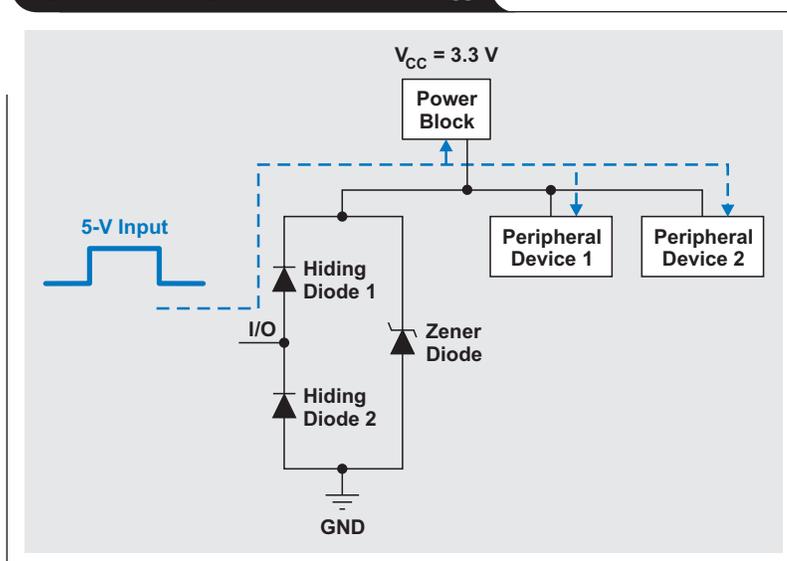Figure 7. Leakage path from I/O to V_{CC} 

the power supply or any device connected to it. If V_{CC} is not connected to the ESD diode, there is no such worry.

2. No ESD damage to internal power supply

During a positive ESD strike, V_{CC} is along the ESD current's discharge path and experiences a voltage level that is one V_F (~0.5 to 0.7 V) drop below the clamping voltage at the I/O. Although the power supply is very robust against ESD due to the shunt capacitor, this raised voltage level could very likely damage any device powered by the V_{CC} (Figure 8). Again, if V_{CC} is not connected to the ESD diode, there is no such worry.

3. No external capacitor necessary

ESD-diode process development at Texas Instruments (TI) is focusing on strengthening the overall p-n structure so it can withstand more ESD voltage. With TI's new generation of ESD-protection diodes rated as high as 30 kV, an extra capacitor can improve the overall ESD rating only marginally. Using one will generally reach a point of diminishing returns. Not having a capacitor reduces the bill of materials count, saves on cost, and allows more PCB space for other critical devices.

Examples of TI's new-generation ESD-protection devices

TI's TPD2E2U06 ESD-protection device is a noteworthy example of the improvements made in diode technology. Unlike its predecessor, the TPD2E001 does not require a V_{CC} connection but maintains the same capacitance, clamps to a lower voltage, and increases the ESD rating threefold. (See Table 1.) Other similar ESD-protection devices from TI include the TPD4E1U06, TPD4E1U06, and TPD4E05U06.


Table 1. Specifications of TPD2E001 versus TPD2E2U06

SPECIFICATIONS	TPD2E001	TPD2E2U06
V_{CC} connection	Recommended	Not required
Contact ESD (kV)	±8	±25
Air ESD (kV)	±15	±30
C_{IN} (pF)*	1.5	1.5
Clamping voltage (V)**	12	9.5

* Capacitance measured at $f = 1$ MHz, $V_{BIAS} = 2.5$ V.

** Clamping voltage measured using TLP curve at 1 A, 100-ns pulse width.

Figure 8. Positive ESD strike can damage V_{CC}

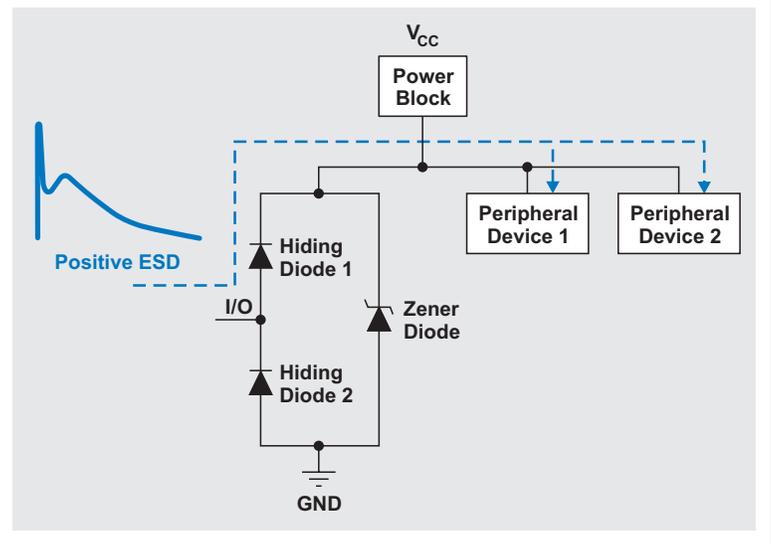

Conclusion

ESD-protection diodes that don't require a V_{CC} connection bring many advantages to the table. No capacitor is needed on the V_{CC} pin to boost the ESD rating; this reduces component count, simplifies layout, and lowers placement cost. Having no V_{CC} connection also guarantees no leakage into the power supply and no ESD damage to any internal nodes that otherwise would be connected to the power supply via V_{CC} .

Related Web sites

Interface:

www.ti.com/interface-aaaj

www.ti.com/tpd2e001-aaaj

www.ti.com/tpd2e2u06-aaaj

www.ti.com/tpd4e001-aaaj

www.ti.com/tpd4e05u06-aaaj

www.ti.com/tpd4e1u06-aaaj

For more information about TI's new-generation ESD-protection devices:

www.ti.com/esd-aaaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaaj

Index of Articles

Title	Issue	Page	Lit. No.
Data Converters			
When is the JESD204B interface the right choice?	1Q, 2014	18	SLYT559
Grounding in mixed-signal systems demystified, Part 2	2Q, 2013	5	SLYT512
Add a digitally controlled PGA with noise filter to an ADC	1Q, 2013	9	SLYT500
Grounding in mixed-signal systems demystified, Part 1	1Q, 2013	5	SLYT499
WEBENCH® tools and the photodetector's stability	4Q, 2012	5	SLYT487
How delta-sigma ADCs work, Part 2	4Q, 2011	5	SLYT438
How delta-sigma ADCs work, Part 1	3Q, 2011	13	SLYT423
Clock jitter analyzed in the time domain, Part 3	3Q, 2011	5	SLYT422
The IBIS model, Part 3: Using IBIS models to investigate signal-integrity issues	2Q, 2011	5	SLYT413
The IBIS model, Part 2: Determining the total quality of an IBIS model	1Q, 2011	5	SLYT400
The IBIS model: A conduit into signal-integrity analysis, Part 1	4Q, 2010	11	SLYT390
Clock jitter analyzed in the time domain, Part 2	4Q, 2010	5	SLYT389
Clock jitter analyzed in the time domain, Part 1	3Q, 2010	5	SLYT379
How digital filters affect analog audio-signal levels	2Q, 2010	5	SLYT375
How the voltage reference affects ADC performance, Part 3	4Q, 2009	5	SLYT355
How the voltage reference affects ADC performance, Part 2	3Q, 2009	13	SLYT339
Impact of sampling-clock spurs on ADC performance	3Q, 2009	5	SLYT338
How the voltage reference affects ADC performance, Part 1	2Q, 2009	5	SLYT331
Stop-band limitations of the Sallen-Key low-pass filter	4Q, 2008	5	SLYT306
A DAC for all precision occasions	3Q, 2008	5	SLYT300
Understanding the pen-interrupt (PENIRQ) operation of touch-screen controllers	2Q, 2008	5	SLYT292
Using a touch-screen controller's auxiliary inputs	4Q, 2007	5	SLYT283
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Using the ADS8361 with the MSP430™ USI port	3Q, 2006	5	SLYT244
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Clocking high-speed data converters	1Q, 2005	20	SLYT075
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129

Title	Issue	Page	Lit. No.
Data Converters (Continued)			
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
Precision voltage references	November 1999	1	SLYT183
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Aspects of data acquisition system design	August 1999	1	SLYT191
Power Management			
Accurately measuring efficiency of ultralow- I_Q devices	1Q, 2014	13	SLYT558
Low-cost flyback solutions for 10-mW standby power	1Q, 2014	9	SLYT557
Split-rail approaches extend boost-converter input-voltage ranges	1Q, 2014	5	SLYT556
Techniques for accurate PSRR measurements	4Q, 2013	19	SLYT547
Dynamic power management for faster, more efficient battery charging	4Q, 2013	15	SLYT546
Low-cost solution for measuring input power and RMS current	4Q, 2013	11	SLYT545
Driving solenoid coils efficiently in switchgear applications	4Q, 2013	5	SLYT544
Improved LiFePO ₄ cell balancing in battery-backup systems with an Impedance Track™ fuel gauge	3Q, 2013	14	SLYT528
Linear versus switching regulators in industrial applications with a 24-V bus	3Q, 2013	9	SLYT527
High-efficiency, low-ripple DCS-Control™ offers seamless PWM/power-save transitions	3Q, 2013	5	SLYT531
Digital current balancing for an interleaved boost PFC	2Q, 2013	19	SLYT517
Designing a negative boost converter from a standard positive buck converter	2Q, 2013	13	SLYT516
Synchronous rectification boosts efficiency by reducing power loss	2Q, 2013	9	SLYT515
How to pick a linear regulator for noise-sensitive applications	1Q, 2013	25	SLYT504
35-V, single-channel gate drivers for IGBT and MOSFET renewable-energy applications	1Q, 2013	22	SLYT503
Power MOSFET failures in mobile PMUs: Causes and design precautions	1Q, 2013	17	SLYT502
Design of a 60-A interleaved active-clamp forward converter	1Q, 2013	13	SLYT501
Simple open-circuit protection for boost converters in LED driver applications	4Q, 2012	21	SLYT490
LDO noise examined in detail	4Q, 2012	14	SLYT489
Harnessing wasted energy in 4- to 20-mA current-loop systems	4Q, 2012	10	SLYT488
Designing a Qi-compliant receiver coil for wireless power systems, Part 1	3Q, 2012	8	SLYT479
Easy solar-panel maximum-power-point tracking for pulsed-load applications	3Q, 2012	5	SLYT478
Design considerations for a resistive feedback divider in a DC/DC converter	2Q, 2012	18	SLYT469
Charging a three-cell nickel-based battery pack with a Li-Ion charger	2Q, 2012	14	SLYT468
Remote sensing for power supplies	2Q, 2012	12	SLYT467
A solar-powered buck/boost battery charger	2Q, 2012	8	SLYT466
Controlling switch-node ringing in synchronous buck converters	2Q, 2012	5	SLYT465
High-efficiency AC adapters for USB charging	1Q, 2012	18	SLYT451
Downslope compensation for buck converters when the duty cycle exceeds 50%	1Q, 2012	14	SLYT450
Benefits of a multiphase buck converter	1Q, 2012	8	SLYT449
Turbo-boost charger supports CPU turbo mode	1Q, 2012	5	SLYT448
Solar lantern with dimming achieves 92% efficiency	4Q, 2011	12	SLYT440

Title	Issue	Page	Lit. No.
Power Management (Continued)			
Solar charging solution provides narrow-voltage DC/DC system bus for multicell-battery applications	4Q, 2011	8	SLYT439
A boost-topology battery charger powered from a solar panel	3Q, 2011	17	SLYT424
Challenges of designing high-frequency, high-input-voltage DC/DC converters	2Q, 2011	28	SLYT415
Backlighting the tablet PC	2Q, 2011	23	SLYT414
I _Q : What it is, what it isn't, and how to use it	2Q, 2011	18	SLYT412
Benefits of a coupled-inductor SEPIC converter	2Q, 2011	14	SLYT411
Implementation of microprocessor-controlled, wide-input-voltage, SMBus smart battery charger	2Q, 2011	11	SLYT410
Fine-tuning TI's Impedance Track™ battery fuel gauge with LiFePO ₄ cells in shallow-discharge applications	1Q, 2011	13	SLYT402
An introduction to the Wireless Power Consortium standard and TI's compliant solutions	1Q, 2011	10	SLYT401
Save power with a soft Zener clamp	4Q, 2010	19	SLYT392
A low-cost, non-isolated AC/DC buck converter with no transformer	4Q, 2010	16	SLYT391
Computing power going "Platinum"	3Q, 2010	13	SLYT382
Coupled inductors broaden DC/DC converter usage	3Q, 2010	10	SLYT380
Designing DC/DC converters based on ZETA topology	2Q, 2010	16	SLYT372
Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter	2Q, 2010	12	SLYT371
Power-supply design for high-speed ADCs	1Q, 2010	12	SLYT366
Li-Ion battery-charger solutions for JEITA compliance	1Q, 2010	8	SLYT365
Fuel-gauging considerations in battery backup storage systems	1Q, 2010	5	SLYT364
Efficiency of synchronous versus nonsynchronous buck converters	4Q, 2009	15	SLYT358
Designing a multichemistry battery charger	4Q, 2009	13	SLYT357
Using power solutions to extend battery life in MSP430™ applications	4Q, 2009	10	SLYT356
Reducing radiated EMI in WLED drivers	3Q, 2009	17	SLYT340
Selecting the right charge-management solution	2Q, 2009	18	SLYT334
Designing a linear Li-Ion battery charger with power-path control	2Q, 2009	12	SLYT333
Taming linear-regulator inrush currents	2Q, 2009	9	SLYT332
Using a portable-power boost converter in an isolated flyback application	1Q, 2009	19	SLYT323
Cell balancing buys extra run time and battery life	1Q, 2009	14	SLYT322
Improving battery safety, charging, and fuel gauging in portable media applications	1Q, 2009	9	SLYT321
Paralleling power modules for high-current applications	1Q, 2009	5	SLYT320
Designing DC/DC converters based on SEPIC topology	4Q, 2008	18	SLYT309
Compensating and measuring the control loop of a high-power LED driver	4Q, 2008	14	SLYT308
Getting the most battery life from portable systems	4Q, 2008	8	SLYT307
New current-mode PWM controllers support boost, flyback, SEPIC, and LED-driver applications	3Q, 2008	9	SLYT302
Battery-charger front-end IC improves charging-system safety	2Q, 2008	14	SLYT294
Understanding output voltage limitations of DC/DC buck converters	2Q, 2008	11	SLYT293
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
TPS6108x: A boost converter with extreme versatility	3Q, 2007	14	SLYT279
Power-management solutions for telecom systems improve performance, cost, and size	3Q, 2007	10	SLYT278
Current balancing in four-pair, high-power PoE applications	2Q, 2007	11	SLYT270
Enhanced-safety, linear Li-Ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Selecting the correct IC for power-supply applications	1Q, 2007	5	SLYT259
Fully integrated TPS6300x buck-boost converter extends Li-Ion battery life	4Q, 2006	15	SLYT256
bq25012 single-chip, Li-Ion charger and dc/dc converter for Bluetooth® headsets	4Q, 2006	13	SLYT255
A 3-A, 1.2-V _{OUT} linear regulator with 80% efficiency and P _{LOST} < 1 W	4Q, 2006	10	SLYT254
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247

Title	Issue	Page	Lit. No.
Power Management (Continued)			
TPS65552A powers portable photoflash.	3Q, 2006	10	SLYT246
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Li-Ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
A better bootstrap/bias supply circuit.	1Q, 2005	33	SLYT077
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
LED-driver considerations	1Q, 2004	14	SLYT084
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2.	4Q, 2003	21	SLYT092
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1.	3Q, 2003	13	SLYT097
Soft-start circuits for LDO linear regulators.	3Q, 2003	10	SLYT096
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down.	3Q, 2003	5	SLYT095
Using the TPS61042 white-light LED driver as a boost converter.	1Q, 2003	7	SLYT101
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Understanding piezoelectric transformers in CCFL backlight applications.	4Q, 2002	18	SLYT107
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
SWIFT™ Designer power supply design program.	2Q, 2002	15	SLYT116
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
Comparing magnetic and piezoelectric transformer approaches in CCFL applications.	1Q, 2002	12	SLYT125
Power control design key to realizing InfiniBand SM benefits.	1Q, 2002	10	SLYT124
Runtime power control for DSPs using the TPS62000 buck converter.	July 2001	15	SLYT131
Power supply solution for DDR bus termination	July 2001	9	SLYT130
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A.	May 2000	14	SLYT171
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Power supply solutions for TI DSPs using synchronous buck converters.	February 2000	12	SLYT177
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Migrating from the TI TL770x to the TI TLC770x.	August 1999	14	SLYT196
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Stability analysis of low-dropout linear regulators with a PMOS pass element.	August 1999	10	SLYT194

	Title	Issue	Page	Lit. No.
Interface				
	New-generation ESD-protection devices need no VCC connection	1Q, 2014	23	SLYT561
	CAN bus, Ethernet, or FPD-Link: Which is best for automotive communications?	1Q, 2014	20	SLYT560
	Correcting cross-wire faults in modern e-metering networks	4Q, 2013	22	SLYT548
	Basics of debugging the controller area network (CAN) physical layer	3Q, 2013	18	SLYT529
	RS-485 failsafe biasing: Old versus new transceivers	2Q, 2013	25	SLYT514
	Design considerations for system-level ESD circuit protection	4Q, 2012	28	SLYT492
	How to design an inexpensive HART transmitter	4Q, 2012	24	SLYT491
	Data-rate independent half-duplex repeater design for RS-485	3Q, 2012	15	SLYT480
	Extending the SPI bus for long-distance communication	4Q, 2011	16	SLYT441
	Industrial data-acquisition interfaces with digital isolators	3Q, 2011	24	SLYT426
	Isolated RS-485 transceivers support DMX512 stage lighting and special-effects applications	3Q, 2011	21	SLYT425
	Designing an isolated I ² C Bus [®] interface by using digital isolators	1Q, 2011	17	SLYT403
	Interfacing high-voltage applications to low-power controllers	4Q, 2010	20	SLYT393
	Magnetic-field immunity of digital capacitive isolators	3Q, 2010	19	SLYT381
	Designing with digital isolators	2Q, 2009	21	SLYT335
	Message priority inversion on a CAN bus	1Q, 2009	25	SLYT325
	RS-485: Passive failsafe for an idle bus	1Q, 2009	22	SLYT324
	Cascading of input serializers boosts channel density for digital inputs	3Q, 2008	16	SLYT301
	When good grounds turn bad— isolate!	3Q, 2008	11	SLYT298
	Enabling high-speed USB OTG functionality on TI DSPs	2Q, 2007	18	SLYT271
	Detection of RS-485 signal loss	4Q, 2006	18	SLYT257
	Improved CAN network security with TI's SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
	Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
	Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
	Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
	The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
	Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
	Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
	The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
	The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
	A statistical survey of common-mode noise	November 2000	30	SLYT153
	Performance of LVDS with different cables	August 2000	30	SLYT163
	LVDS: The ribbon cable connection	May 2000	19	SLYT172
	LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
	Skew definition and jitter analysis	February 2000	29	SLYT179
	Keep an eye on the LVDS input levels	November 1999	17	SLYT188
	TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Amplifiers				
	Designing active analog filters in minutes	4Q, 2013	28	SLYT549
	Exploring anti-aliasing filters in signal conditioners for mixed-signal, multimodal sensor conditioning	3Q, 2013	25	SLYT530
	Using a fixed threshold in ultrasonic distance-ranging automotive applications	3Q, 2012	19	SLYT481
	Source resistance and noise considerations in amplifiers	2Q, 2012	23	SLYT470
	Measuring op amp settling time by using sample-and-hold technique	1Q, 2012	21	SLYT452
	Converting single-ended video to differential video in single-supply systems	3Q, 2011	29	SLYT427
	Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	4Q, 2010	26	SLYT394
	Operational amplifier gain stability, Part 3: AC gain-error analysis	3Q, 2010	23	SLYT383
	Operational amplifier gain stability, Part 2: DC gain-error analysis	2Q, 2010	24	SLYT374
	Precautions for connecting APA outputs to other devices	2Q, 2010	22	SLYT373
	Interfacing op amps to high-speed DACs, Part 3: Current-sourcing DACs simplified	1Q, 2010	32	SLYT368
	Signal conditioning for piezoelectric sensors	1Q, 2010	24	SLYT369
	Operational amplifier gain stability, Part 1: General system analysis	1Q, 2010	20	SLYT367
	Interfacing op amps to high-speed DACs, Part 2: Current-sourcing DACs	4Q, 2009	23	SLYT360
	Using fully differential op amps as attenuators, Part 3: Single-ended unipolar input signals	4Q, 2009	19	SLYT359
	Using the infinite-gain, MFB filter topology in fully differential active filters	3Q, 2009	33	SLYT343
	Interfacing op amps to high-speed DACs, Part 1: Current-sinking DACs	3Q, 2009	24	SLYT342

Title	Issue	Page	Lit. No.
Amplifiers: (Continued)			
Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals	3Q, 2009	21	SLYT341
Using fully differential op amps as attenuators, Part 1: Differential bipolar input signals	2Q, 2009	33	SLYT336
Output impedance matching with fully differential operational amplifiers	1Q, 2009	29	SLYT326
A dual-polarity, bidirectional current-shunt monitor	4Q, 2008	29	SLYT311
Input impedance matching with fully differential amplifiers	4Q, 2008	24	SLYT310
A new filter topology for analog high-pass filters	3Q, 2008	18	SLYT299
New zero-drift amplifier has an I_Q of 17 μ A	2Q, 2007	22	SLYT272
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242
High-speed notch filters	1Q, 2006	19	SLYT235
Getting the most out of your instrumentation amplifier design	4Q, 2005	25	SLYT226
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Full differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128
Audio power amplifier measurements	July 2001	40	SLYT135
An audio circuit collection, Part 3	July 2001	34	SLYT134
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
An audio circuit collection, Part 2	February 2001	41	SLYT145
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
An audio circuit collection, Part 1	November 2000	39	SLYT155
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
The PCB is a component of op amp design	August 2000	42	SLYT166
Fully differential amplifiers	August 2000	38	SLYT165
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Sensor to ADC — analog interface design	May 2000	22	SLYT173
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Single-supply op amp design	November 1999	20	SLYT189
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198

Title	Issue	Page	Lit. No.
Low-Power RF			
Selecting antennas for low-power wireless applications	2Q, 2008	20	SLYT296
Using the CC2430 and TIMAC for low-power wireless sensor applications: A power- consumption study	2Q, 2008	17	SLYT295
General Interest			
Introduction to capacitive touch-screen controllers	2Q, 2013	29	SLYT513
High-definition haptics: Feel the difference!	3Q, 2012	29	SLYT483
Applying acceleration and deceleration profiles to bipolar stepper motors	3Q, 2012	24	SLYT482
Industrial flow meters/flow transmitters.	2Q, 2012	29	SLYT471
Analog linearization of resistance temperature detectors.	4Q, 2011	21	SLYT442
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273
Analog design tools.	2Q, 2002	50	SLYT122
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001.	52	SLYT147

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic (toll-free number)	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A012014

Auto-Track, E2E, FilterPro, Impedance Track, MSP430, OMAP, and SWIFT are trademarks and DLP and WEBENCH are registered trademarks of Texas Instruments. The *Bluetooth* word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. ENERGY STAR is a registered trademark of the U.S. Environmental Protection Agency. I²C Bus is a registered trademark of NXP B.V. Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com