

TI Precision Designs: Reference Design

0-5 A, Single-Supply, 2 kV Isolated Current Sensing Solution



TI Precision Designs

TI Precision Designs are analog solutions created by TI's analog experts. Reference Designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Circuit Description

This single supply isolated current sensing design can be used to monitor currents from 0-5 A with up to 2500 Vrms isolation. The isolated current measurement is accomplished through an isolation amplifier with a fixed gain of 8 V/V. The 5 V power to the isolated side of the isolation amplifier (VDD1) is provided from the user interface power source (VDD2) using a push-pull driver and small isolation transformer.


Design Resources

[Design Archive](#)
[TINA-TI™](#)
[AMC1200](#)
[SN6501](#)

All Design files
 SPICE Simulator
 Product Folder
 Product Folder



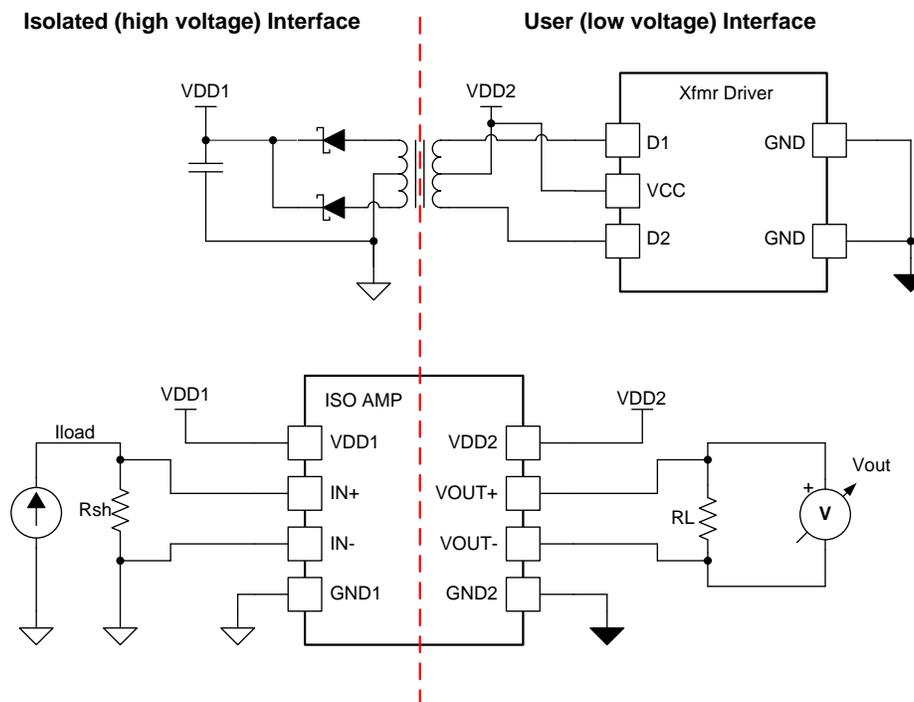[Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Precision Designs Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Design Summary

The design requirements are as follows:

- Generated Isolated Supply Voltage (VDD1): 5.0 Vdc ($\pm 3\%$)
- VDD1 Output Current: 8 mA (max)
- Isolated Sense Current: 0-5 A
- Maximum Shunt Voltage: 250 mV

The design goals and performance are summarized in Table 1. Figure 1 depicts the measured transient response of the design.

Table 1: Comparison of Design Goals and Simulated/Measured Performance

	Goal	Simulated
Offset Voltage	± 2 mV	-957.09 μ V
Current Measurement Error (%FSR)	$\pm 0.5\%$	-0.27%
	Goal	Measured
VDD1 Supply Voltage	$\pm 3\%$	+6-8%

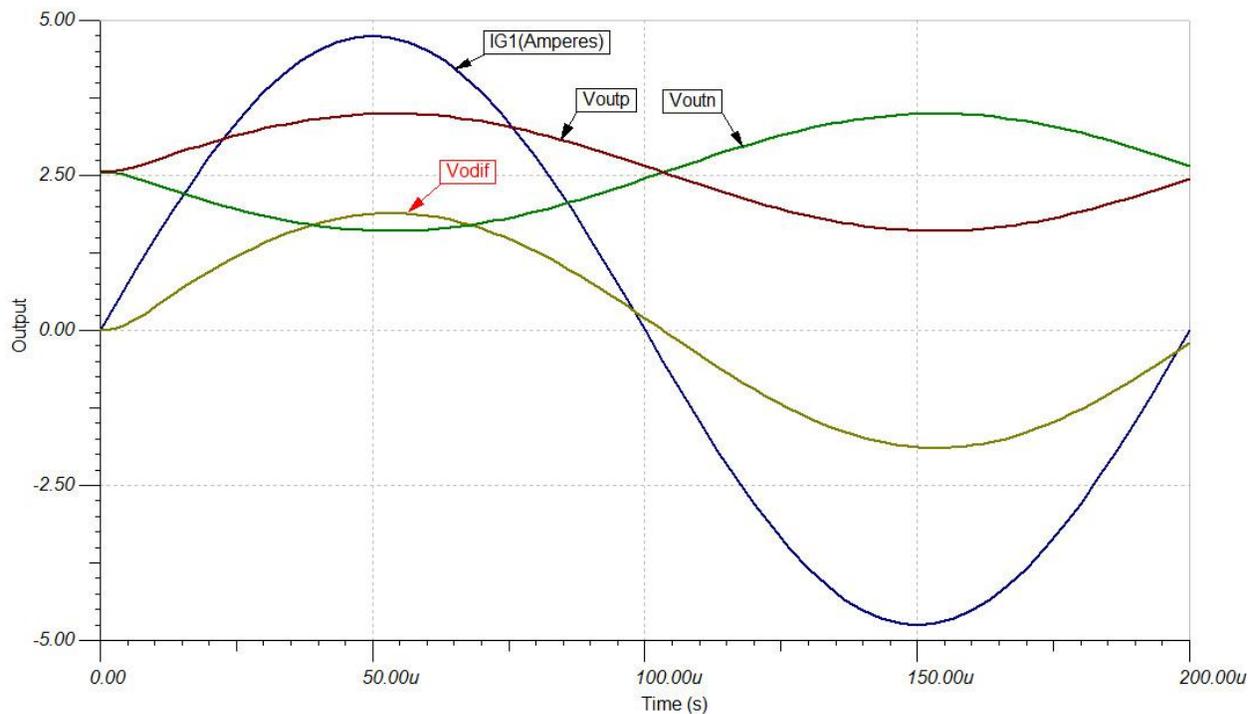


Figure 1: Simulated Transient Response

2 Theory of Operation

The goals of this design are twofold; the primary goal is to be able to show accurate current measurements from 0-5 A from an AC current source. The second goal is to power the isolated side of the current shunt monitor from a 5 V source on the user interface, or output side, of the isolation amplifier.

2.1 Isolated Current Shunt Measurement

The current to be sensed on the isolated side of the circuit (I_{load}) will be fed through a shunt resistor (R_{sh}). I_{load} generates a voltage across the shunt resistor (V_{sh}) that is proportional to the value of the shunt resistor. The differential output voltage of the circuit is the product of the amplifier gain (G) and the voltage across the shunt V_{sh} . The AMC1200 output has a fixed common mode voltage based on the VDD2 rail. When VDD2 is equal to 5 V, the output common-mode voltage is 2.55 V.

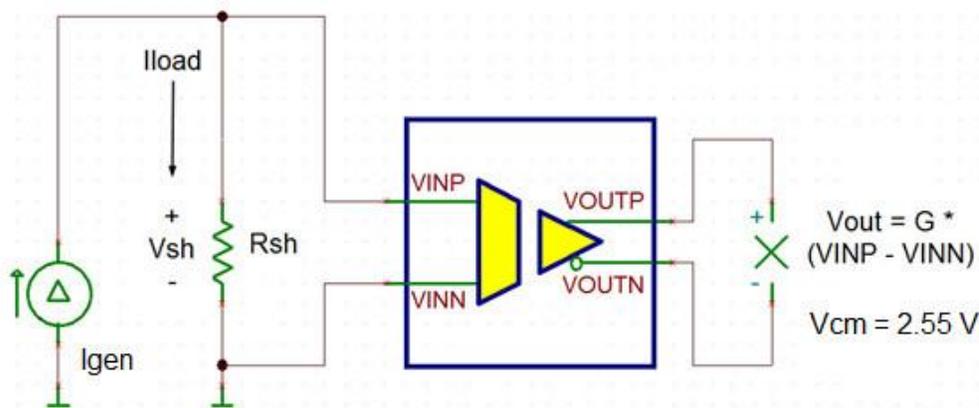


Figure 2: Isolation Amplifier Topology

2.2 Isolated Power Supply

Providing a 5 V high side power supply will be realized using a push-pull driver (the SN6501), a pulse transformer, two rectifiers, and multi-layer ceramic capacitors. Figure 3 depicts the basic transformer circuit which will provide the necessary power to the input side of the isolation amplifier. VDD1 is the 'hot' or isolated, side of the circuit while VDD2 is the user supplied 5 V. The transformer used in this design is rated for 2500 Vrms isolation.

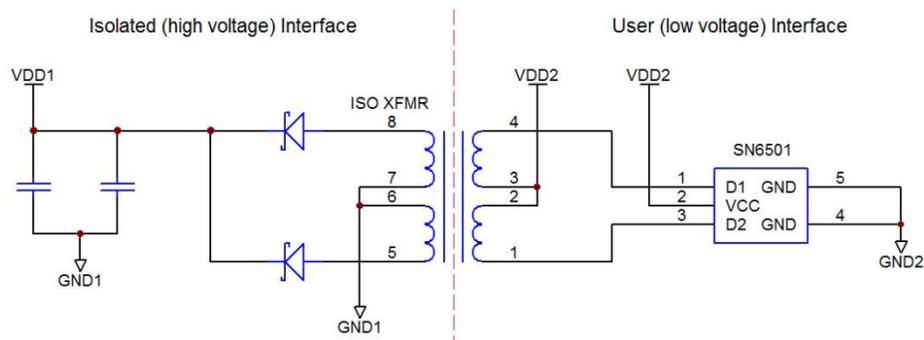


Figure 3: Isolation Transformer Topology

The magnitude of V_{sh} is proportional to the amount of current flowing through the shunt resistor, R_{sh} . The maximum V_{sh} voltage the amplifier can see before clipping is ± 320 mV. To remain in a linear operating region, the specified maximum differential voltage at the input to the amplifier is limited to ± 250 mV. This is going to be the limiting factor on the size of the shunt resistor. The following equation can be used to calculate the value of R_{sh} :

$$R_{sh}(\max) = \frac{250\text{mV}}{5\text{A}} = 0.05\Omega \quad (1)$$

It is recommended to use the maximum shunt resistance possible to provide the widest dynamic range for the system. Using a larger shunt also has the negative effect of increasing the power dissipation in the sense element. As a general rule, use a sense resistor with a power rating of at least 1.5 times the typical power dissipation expected in the circuit to minimize errors induced by self heating. Power through the resistor (PR_{sh}) is the product of the current squared and the shunt resistor value as detailed in equation (2).

$$PR_{sh} = I^2 * R_{sh} = 5\text{A}^2 * 0.05\Omega = 1.25\text{W} \quad (2)$$

The gain in this design is fixed by the isolation amplifier at $G=8$ and can be evaluated using equation (3).

$$G = \frac{V_{out}}{V_{sh}} = \frac{V_{out}}{R_{sh} * I_{load}} = \frac{2.0\text{V}}{0.05\Omega * 5\text{A}} = 8 \frac{\text{V}}{\text{V}} \quad (3)$$

3 Component Selection

3.1 Isolation Amplifier

The AMC1200 was chosen for this application because of its high input bandwidth, the low current drawn on its high-side supply, and its high voltage isolation capability.

3.2 Rectifier Selection

The chosen rectifier diode should possess low-forward voltage to provide as much voltage to the converter output as possible. When used in high-frequency switching applications the rectifier must also possess a short recovery time. Schottky diodes meet both of these requirements. The MBR0520L with a typical forward voltage of approximately 100 mV at 8 mA forward current was used in this low voltage design.

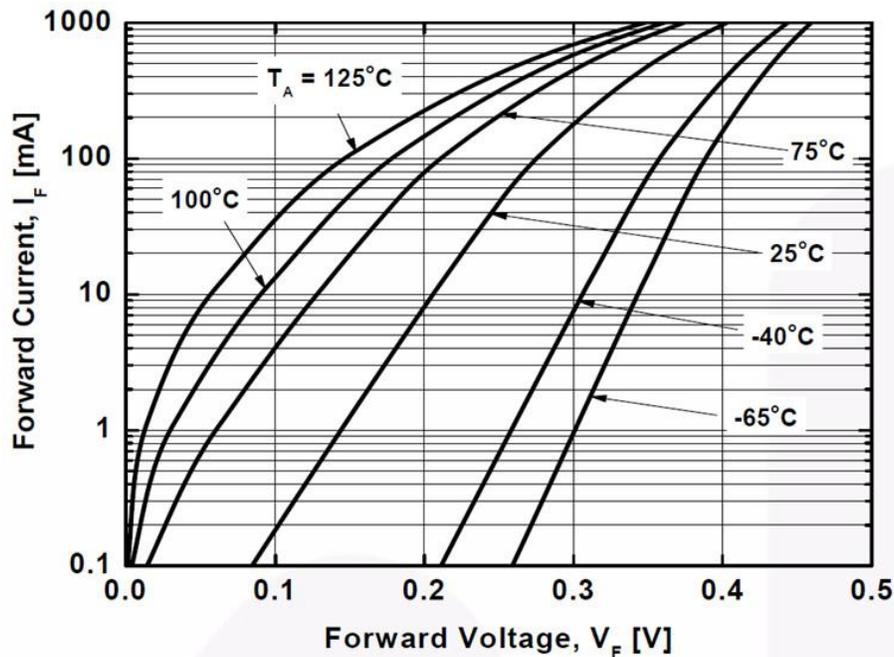


Figure 4: Forward Voltage of the Rectifier

3.3 Transformer Selection

To ensure that a magnetic core does not saturate, the magnetics are designed to dissipate the average stored magnetic flux over each switching cycle of the controller. This is what is known as volt-seconds balance. The average volt-seconds applied to the magnetics during the switch on time must equal the average volt-seconds across the magnetics during the off time. To prevent the isolation transformer from saturating, its volt-seconds (V-t) product must be greater than the maximum volt-seconds product applied by the SN6501. The maximum voltage delivered by the SN6501 is the nominal converter input plus 10%. The maximum time this voltage is applied to the primary is half the period of the lowest frequency at the specified input voltage. The minimum switching frequency of the SN6501 at 5 V operation is 300 kHz. Therefore the transformer's minimum V-t product, as determined by equations (1) and (2) in the [SN6501](#) data sheet, is 9.1 μ s.

When searching for a suitable transformer, it is necessary to determine the minimum turns ratio required that will allow the push-pull converter to operate over the specified current and temperature range. This can be expressed through the ratio of secondary to primary voltage multiplied by a correction factor that takes the transformer's typical efficiency into account. Equations (3) through (8) in the SN6501 data sheet step through the specific requirements for determining the minimum turns ratio for a given application. For this design, Equation (8) from the SN6501 data sheet (assuming no low drop out regulator is needed) is used as a starting point to determine the minimum turns ratio requirement. The turns ratio determination is based on the following equation assuming a forward voltage of 100mV (V_f) across the rectifier with an 8 mA load, the minimum and maximum voltage requirements for the amplifier as noted in design summary, the transformer correction factor, and drain-source on resistance ($R_{DS(on)}$) noted in the SN6501 datasheet, and maximum current listed in the design summary:

$$N_{\min} = 1.031 * \frac{V_f + V_{out \max}}{V_{out \min} - R_{DS(on)} * I_{out}} = 1.031 * \frac{0.1V + 5.15V}{4.85V - 3\Omega * 8.5mA} = 1.12 \quad (4)$$

3.4 Shunt Resistor

The shunt resistor which provides 250 mV with a 5 A load was calculated to be 0.05 Ω . This is a standard value shunt resistor and is available with a tolerance of 1% and a temperature coefficient as low as ± 50 ppm/ $^{\circ}$ C.

3.5 Passive Component Selection

The capacitors in the converter circuit are multi-layer ceramic chip (MLCC) capacitors. As with all high speed CMOS ICs, the SN6501 requires a bypass capacitor in the range of 10 nF to 100 nF. The input bulk capacitor at the center-tap of the primary is 10 μ F, which supports the current into the primary during the fast switching transients. On the secondary side of the transformer, a bulk capacitor of 22 μ F will be used at the rectifier outputs.

4 Simulation

The TINA-TI™ schematic shown in Figure 5 includes the circuit values obtained in the design process.

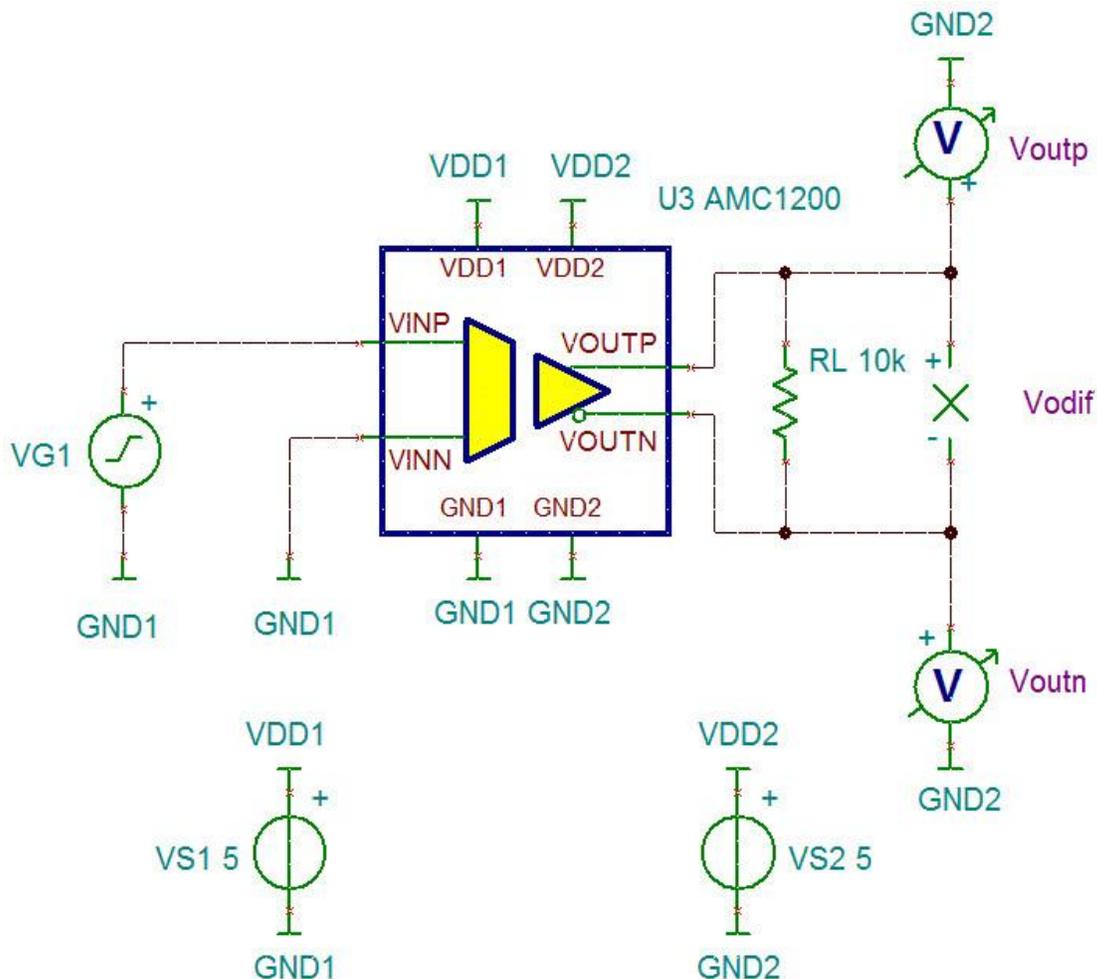


Figure 5: TINA-TI™ Schematic of the Isolation Amplifier

The current source is defined as a sinusoidal current of 5 A at a frequency of 5 kHz. The differential output voltage can be monitored through a standard volt meter or delivered to an analog to digital converter with a differential input. The output voltage range of the AMC1200 is dependent on the applied VDD2. As configured here, the output swing is ± 2 V (differential) with a common mode level of 2.55 V.

4.1 DC Transfer Function

The result of the dc transfer function simulation is shown in Figure 6.

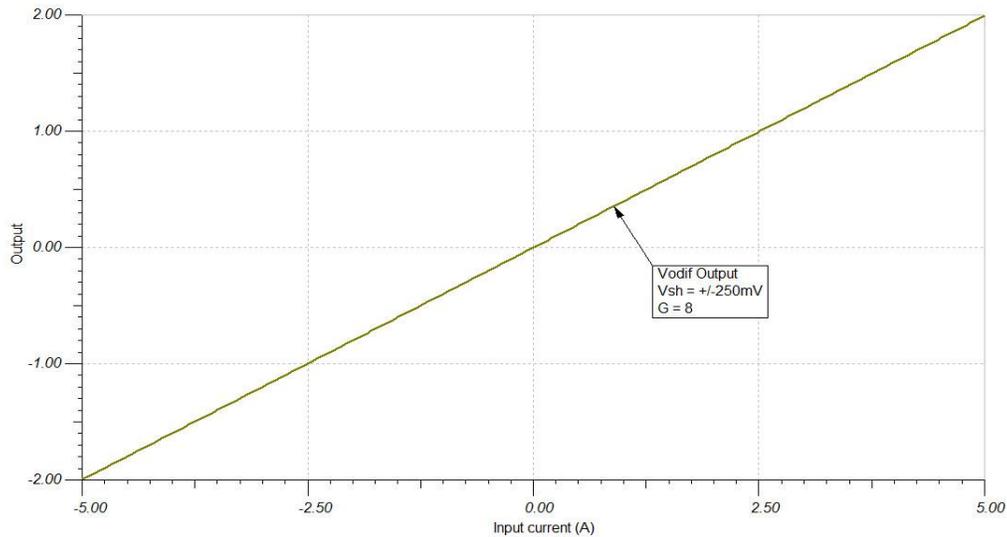


Figure 6: DC Transfer Function

Table 2: Output Voltage versus input Current

Current (A)	Output Voltage
-5	-1.9960 V
0	-957.09 μ V
+5	1.9936 V

4.2 Frequency Response

The AC Transfer Characteristics of the circuit from Figure 5 are shown in Figure 7.

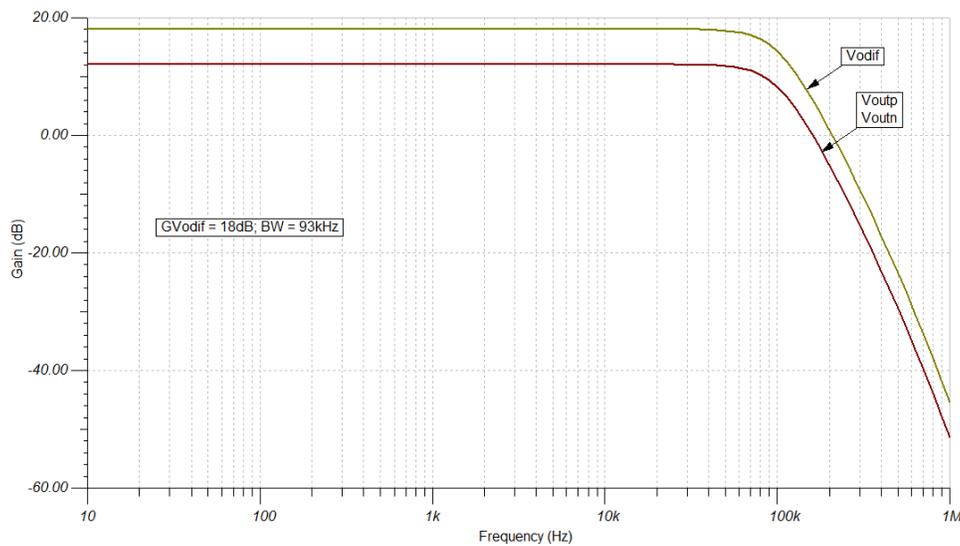


Figure 7: AC Analysis

The bandwidth of the isolation amplifier is 92.98kHz. The dc gain according to the simulation is 18.04dB or 7.97 V/V.

4.3 Error Analysis

A closer analysis of the raw data from figure 6 was used in order to calculate the positive and negative full scale errors as well as the offset of the differential output voltage. At 0A flowing through the load, the differential output voltage was -957.09µV. For positive full scale current, the output voltage was 1.9936V. For negative full scale current, the output voltage was -1.9960. After correcting for the offset voltage, the following equation was used to calculate %FSR.

$$\begin{aligned}
 \%FSR(pos) &= 100\% * \frac{Iload(sim) - Iload(ideal)}{Iload(max) - Iload(min)} & (5) \\
 &= 100\% * \frac{\left(\frac{Vout}{G}\right) * \left(\frac{1}{0.05\Omega}\right) - Iload(ideal)}{5A - 0A} \\
 &= 100\% * \frac{\left(\frac{1.9945}{8}\right) * \left(\frac{1}{0.05\Omega}\right) - 5A}{5A - 0A} = -0.27\%
 \end{aligned}$$

The negative full scale error was 0.25%, which also falls within the original design goals.

4.4 VDD1 Error

The output voltage from the transformer, used for the VDD1 supply on the isolation amplifier, was measured using SN6501 Multi-Transformer EVM. A single AMC1200 draws only 8 mA max, which hampers the efficiency and regulation capabilities of the power supply. Using the curve found in Figure 8 of the SLLU174 document, the estimated voltage applied to the AMC1200 will be between 5.3 and 5.4 V. This deviation from 5 V is approximately two times larger than the design goal of 5 V +/-3%. Measuring directly at the output of the Multi-Transformer EVM, the VDD1 supply was found to be 5.37 V.

Simulating the DC Transfer with 5.4 V applied to VDD1 did show an increase in the offset voltage, but the overall current measurements remained at the 0.27% level.

4.5 Result Summary

Table 2 summarizes the simulated and estimated performance of the design.

Table 3: Comparison of Design Goals and Simulated/Measured Performance

	Goal	Simulated
Offset Voltage	±2mV	-957.09µV
Error (%FSR)	±0.5%	-0.27%
	Goal	Measured
VDD1 Supply Voltage	5 V	5.37 V

5 Modifications

The components selected for this design were based on the design goals outlined at the beginning of the design process. Introducing an LDO at the output of the transformer will provide a more stable VDD1 rail, but this comes at the additional costs associated with board space, component count, and perhaps a different transformer depending on the number of current sensing channels needed in the design.

Adding an LDO to the secondary side of the transformer would require the circuit designer to account for the minimum voltage needed at the LDO input to maintain the desired output voltage. Using the TPS76350 as an example, the regulator needs 75 mV (max) of headroom to maintain 5.0 V out with a 50 mA load. This would provide enough power to drive up to five AMC1200 devices.

A second potential modification to this design would be to replace the 5 V VDD2 source with a 3.3 V supply. With a slightly larger turns ratio on the transformer, the 5 V necessary for the VDD1 rail on the AMC1200 could be realized (with or without an LDO). This would provide a ± 2 V differential output voltage from the AMC1200 centered at 1.29 V.

6 Acknowledgements & References

1. *SN6501 Multi-Transformer EVM Users Guide (SLLU174)*

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com