

AN-1618 LMH1980 Evaluation Board Instruction Manual

1 General Description

The LMH1980 evaluation board can be used to test the LMH1980 auto-detecting SD/HD/PC video sync separator and as a reference for printed circuit board (PCB) layout design.

2 Power Supply

The board can be powered using a clean supply voltage, between 3.3 V and 5.0 V, connected to $V_{\rm CC}$ (J1) and GND (J2) via banana jacks. The LMH1980 supply voltage should be regulated within ±10% variation of the voltage range and should not be shared directly with other digital circuitry.

3 Video Input

A clean, 75 Ω video source can be connected to the board via the video input BNC (J3), which is terminated with a 75 Ω load resistor on the board. Because the input can accept either SD or HD video inputs, a switch-controlled chroma filter, consisting of R_9 and C_2 , is provided on the board. If a PC video input is used, C_2 should be removed to disable the chroma filter.

4 Input Filtering

When an HD tri-level sync input signal is applied, the $\overline{\text{HD}}$ flag (pin 5) will output logic low (following a brief delay for auto format detection) and Q1 will turn off, disabling the SD video chroma filter. When an SD bilevel sync input signal (NTSC/PAL) is applied, $\overline{\text{HD}}$ will output logic high and Q1 will turn on, enabling the chroma filter. When enabled, this low-pass filter will attenuate any chroma subcarrier amplitude extending near the sync pulse so it does not interfere with sync separation. The filter will also improve the input signal-to-noise ratio. The filter cutoff frequency (f_{CO}), set by R_{g} and C_{g} , can be changed depending on the attenuation needed for the SD video signal. Keep in mind that as f_{CO} decreases, the LMH1980 output propagation delays increase, which will affect the timing relationship between the sync and video signals.

Important: If f_{CO} is set too low and HD video is applied, the filter can severely roll off and attenuate the input's high-bandwidth tri-level sync pulses such that the LMH1980 cannot detect a valid HD input signal. If the LMH1980 cannot detect a valid HD input, then the $\overline{\text{HD}}$ flag will never change from logic high to low and the switch-controlled filter will never be disabled via Q1. In other words, f_{CO} should not be set so low that the filter impairs the LMH1980's ability to detect a valid HD input. The values of R_9 and C_2 shown in Figure 1 give $f_{CO} = 2.79$ MHz (about -4 dB at 3.58 MHz NTSC subcarrier frequency) and does not impair auto format detection.

If a PC video input is to be used, C_2 should be removed to disable chroma filtering. This is necessary because $\overline{\text{HD}}$ will output logic high (as in the SD video input case) and enable the filter. A chroma filter could severely band-limit a high-bandwidth PC video signal, which could roll-off and attenuate the sync pulses such that the LMH1980 cannot detect a valid input signal.

If some high-frequency noise filtering is needed for all video signal inputs, a small capacitor may be optionally placed at C_1 . The RC filter formed by R_9 and C_1 is always connected regardless of Q1's switch state. When Q1 is turned on, C_1 and C_2 will be connected in parallel (C_1+C_2).

5 Test Points

Test points and ground points are provided to measure the input and output signals using 10 $M\Omega$ oscilloscope probes with 10 pF load capacitance.

All trademarks are the property of their respective owners.



Board Schematic www.ti.com

6 Board Schematic

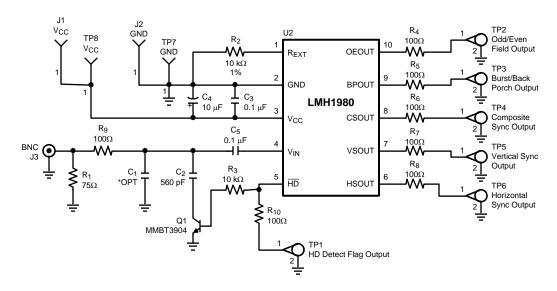


Figure 1. LMH1980 Eval Board 870013153-200 Rev A

7 Board Layout

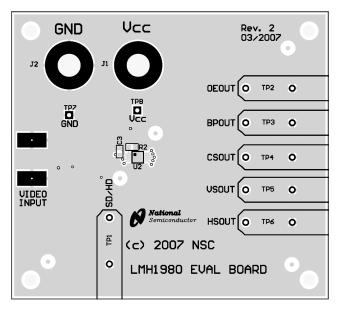


Figure 2. Top Side



www.ti.com Bill of Materials

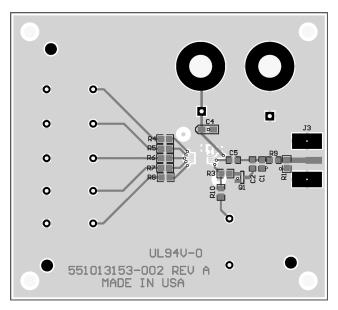


Figure 3. Bottom Side

8 Bill of Materials

Item	Part Number	Part Description	Qty	Ref Designator	Remark
1	LMH1980		1	U2	
2	MMBT3904	NPN Transistor, SOT-23	1	Q1	
3	Digi-key PCC1762CT- ND	Capacitor Ceramic 0.1 µF, X7R, 0603, 16V	1	C ₃	
4	Digi-key PCC1828CT- ND	Capacitor Ceramic 0.1 µF, X7R, 0805, 25V	1	C ₅	
5	Digi-key PCC561BNCT- ND	Capacitor Ceramic 560 pF, NPO, 0805, 50V	1	C ₂	
6	Digi-key PCC561BNCT- ND	Capacitor Ceramic 560 pF, NPO, 0805, 50V	1	C ₄	
7	Digi-key P10.0KHCT-ND	Resistor, 10 kΩ, 1%, 1/10W 0603	1	R ₂	Must be 1% or better
8	Digi-key P10.0KCCT-ND	Resistor, 10 kΩ, 1%, 1/8W 0805	1	R ₃	
9	Digi-key P75.0CCT-ND	Resistor, 75Ω, 1%, 1/8W 0805	1	R ₁	
10	Digi-key P100CCT-ND	Resistor, 100Ω, 1%, 1/8W 0805	7	R_4 , R_5 , R_6 , R_7 , R_8 , R_9 , R_{10}	
11	MOUSER 16BJ381	Banana Jack, Red	1	J1	
12	12 MOUSER 16BJ382	Banana Jack, Black	1	J2	
13	Newark 22C4690	EDGE-MOUNT BNC	1	J3	Trompeter UCBJE20-1
14	Digi-key 5001K-ND	Test Point, Black	1	TP7	
15	Digi-key 5000K-ND	Test Point, Red	1	TP8	
16	Digi-key 5001K-ND, 5004-ND	Test Points, Black and Yellow	6	TP1, TP2, TP3, TP4, TP5, TP6	Use black for GND points

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products Applications

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security

Power Mgmt power.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID <u>www.ti-rfid.com</u>

OMAP Applications Processors www.ti.com/omap TI E2E Community e2e.ti.com

Wireless Connectivity <u>www.ti.com/wirelessconnectivity</u>