

AN-2197 LMR62421 Demo Board

1 Introduction

The Texas Instruments LMR62421 is a high frequency switching boost regulator which offers small size and high power conversion efficiency. The part operates at a 1.6MHz switching frequency. It provides all the active functions to provide local DC/DC conversion with fast-transient response and accurate regulation in the smallest PCB area capable of supplying up to 2.1A of switch current. The LMR62421 is internally compensated, so it is simple to use, and requires few external components. The LMR62421 uses current-mode control to regulate the output voltage in a range from 3V to 24V. Additional features include internal soft start which helps reduce inrush current and thermal shutdown. This application note describes the demo board supplied to demonstrate the operation of this part and give information on its usage.

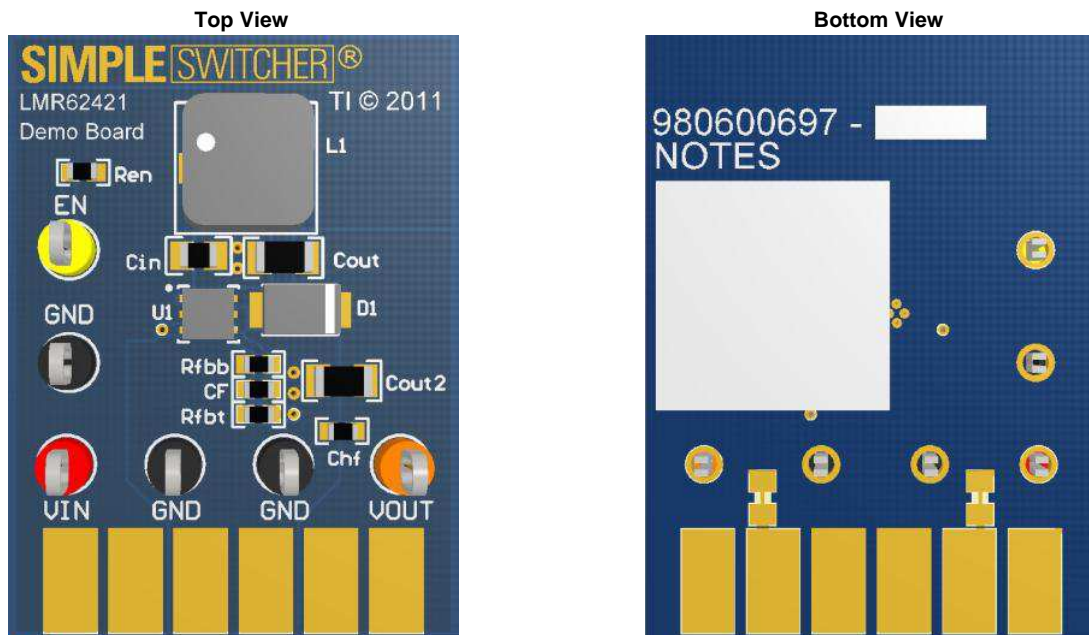


Figure 1. LMR62421 Demo Board

2 Features

- 2.7V to 5.5V Input Voltage Range
- 12V Output Voltage (default setting)
- 500mA Output Current from 3.5V input supply
- 300mA Output Current from 2.7V input supply
- Switching Frequency of 1.6 MHz
- Low Component Count
- PCB size: 27.5mm × 36.9mm

3 Shutdown Operation

The demo board includes a pull-up resistor R3 to enable the device once V_{IN} has exceeded 1.8V. Use the EN post to disable the device by pulling this node to GND. A logic signal may be applied to the post to test startup and shutdown of the device.

4 Adjusting the Output Voltage

The output voltage can be changed from 12V to another voltage by adjusting the feedback resistors using the following equation:

$$V_{OUT} = V_{FB}(1 + (R1/R2)) \quad (1)$$

Where V_{FB} is 1.255V.


5 Feedforward Compensation

The feedforward capacitor CF should be selected to set the compensation zero at approximately 8 kHz. The value of CF is calculated using:

$$CF = 1 / (2 \times \pi \times 8k \times R1) \quad (2)$$

The value of CF is calculated after R1 is selected for the output voltage needed for the specific application.

For more information on component selection and features, see *LMR62421 SIMPLE SWITCHER 24Vout, 2.1A Step-Up Voltage Regulator in SOT-23* ([SNVS734](#)).

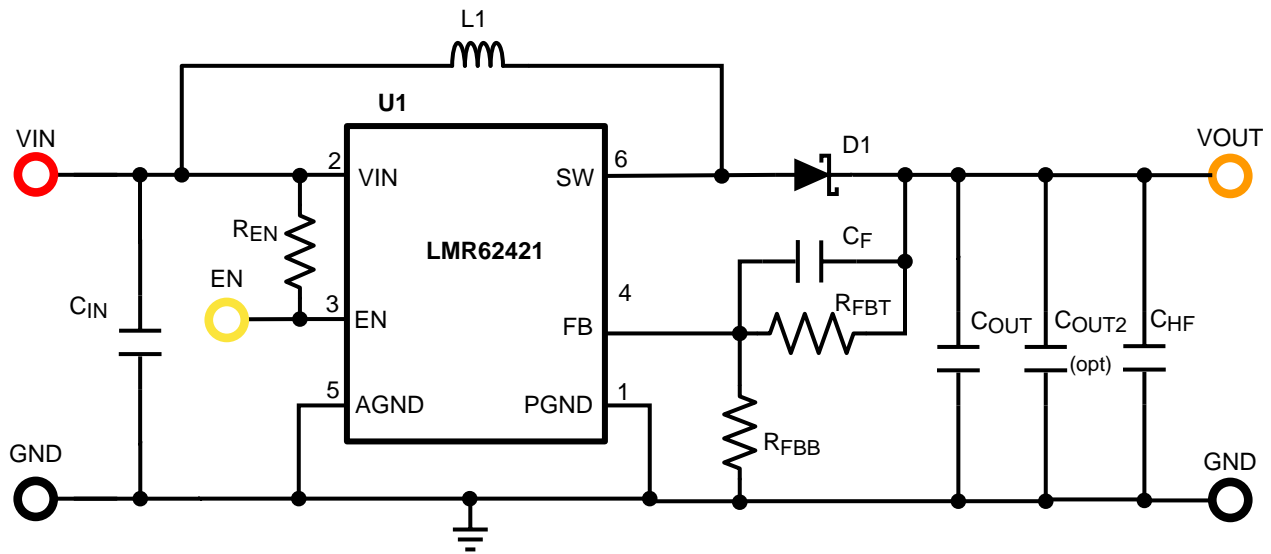6 LMR62421 Demo Board Schematic

Figure 2. LMR62421 Demo Board Schematic
Table 1. Bill of Materials LMR62421

ID	Part Number	Type	Size	Parameters	Vendor
U1	LMR62421	1.6MHz - Space-Efficient Boost	6-pin WSON		Texas Instruments
L1	7447779006	Inductor		Shielded Inductor, 6.8μH, 2.91A	Würth
D1	B220A-13-F	Diode	SMA	Schottky, 20V, 2A	Diodes Inc.
Cin	GRM21BR71A106KE51L	Capacitor	0805	Ceramic, 10μF, 10V, X7R	Murata
Cout	GRM31CR71E106KA12L	Capacitor	1206	Ceramic, 10μF, 25V, X7R	Murata
Cout2	optional		1206	additional output cap	
CF	C0603C221J5GACTU	Capacitor	0603	Ceramic, 220pF, 50V, C0G/NP0	Kemet
CHF	GRM188R71H223KA01D	Capacitor	0603	Ceramic, 0.022μF, 50V, X7R	Murata
Rfbt	CRCW060386K6FKEA	Resistor	0603	86.6 kΩ	Vishay
Rfbb	CRCW060310K2FKEA	Resistor	0603	10.2 kΩ	Vishay
Ren	CRCW06031M00JNEA	Resistor	0603	1.0 MegΩ	Vishay
EN	5014	Test Point Loop		Yellow	Keystone
VIN	5010	Test Point Loop		Red	Keystone
VOUT	5013	Test Point Loop		Orange	Keystone
GND	5011	Test Point Loop		Black	Keystone

7 Quick Setup Procedures

Step 1: Connect a power supply to V_{IN} terminals. V_{IN} range: 2.7V to 5.5V

Step 2: Connect a load to V_{OUT} terminals. I_{OUT} range: 0mA to 500mA

Step 3: Do not allow the EN pin to float or be greater than $V_{IN} + 0.3V$. EN pin must be connected to V_{IN} by means R3 for normal operation. Short this to ground to shutdown the part.

Step 4: Turn on V_{IN} with 0A load applied, check V_{OUT} with a voltmeter. Nominal 12V

Step 5: Apply a 500mA load and check V_{OUT} . Nominal 12V

8 Measurements

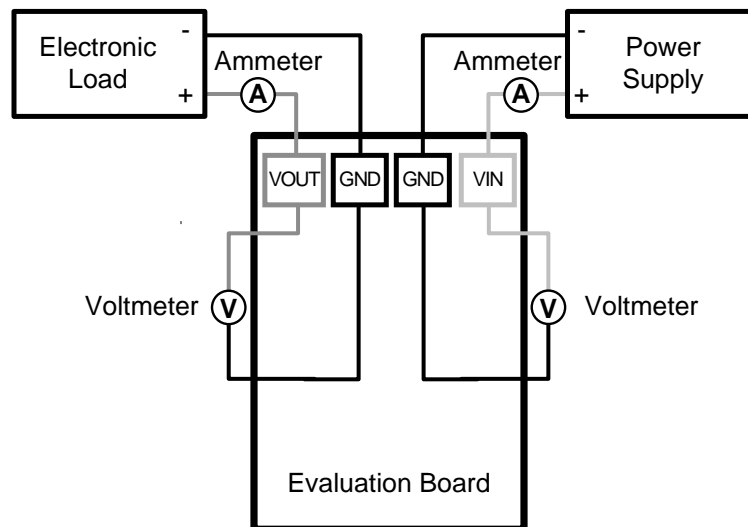


Figure 3. Efficiency Measurements

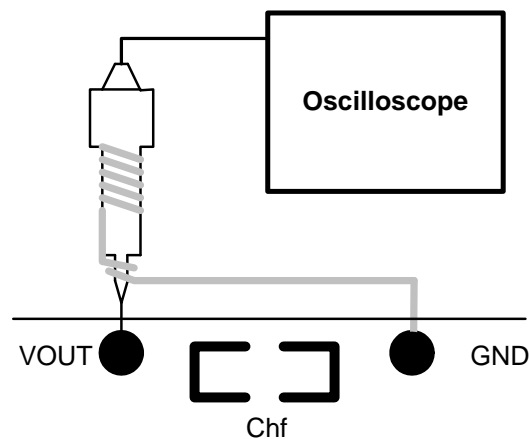


Figure 4. Voltage Ripple Measurements


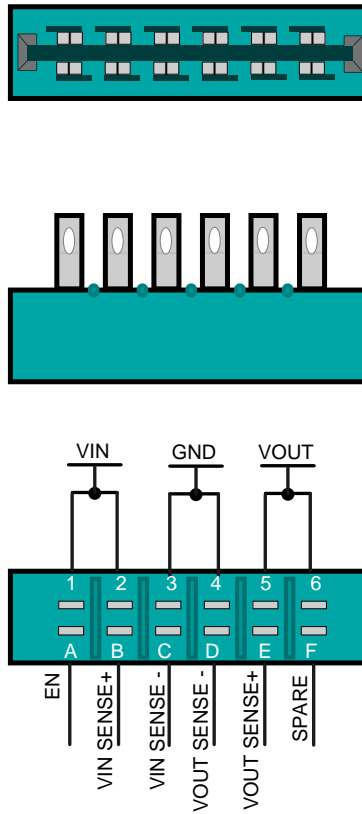



Figure 5. Edge Connector Schematic

9 Typical Performance Characteristics

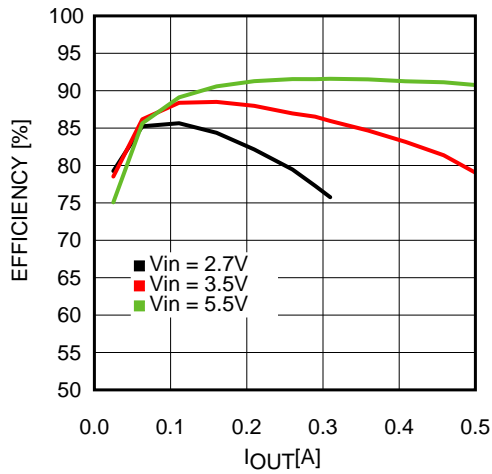
Efficiency vs. Load Current LMR62421, $V_{OUT} = 12V$




Load regulation, $V_{OUT} = 12V$

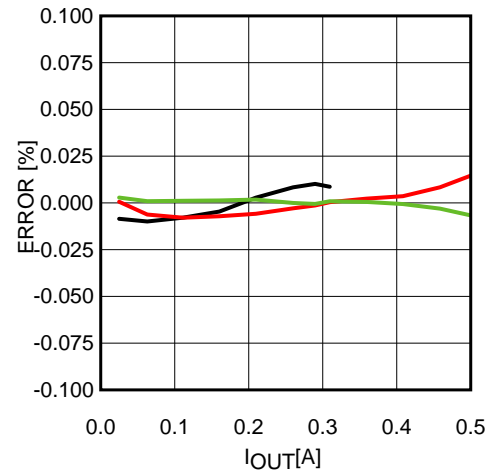

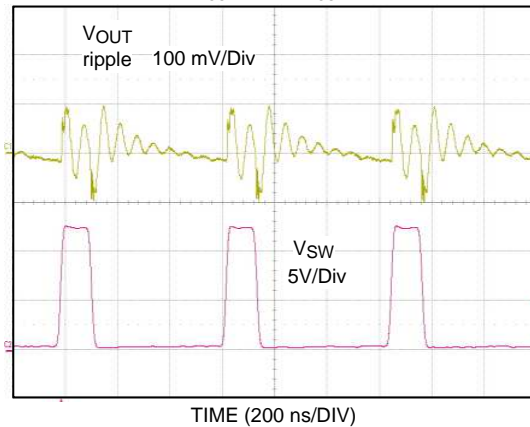
Output Voltage Ripple and Switching Waveform, $V_{IN} = 2.7, V_{OUT} = 12V, I_{OUT} = 300mA$



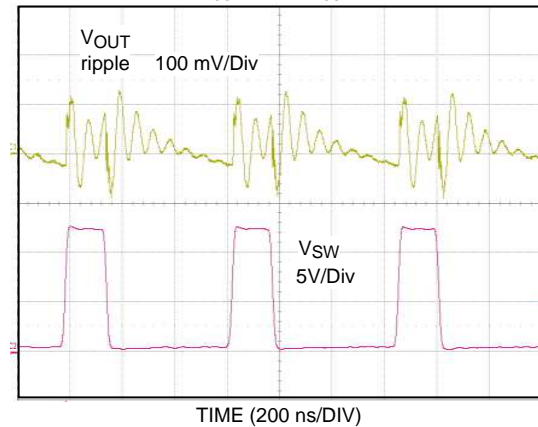
Output Ripple and Switching Waveform, $V_{IN} = 3.5, V_{OUT} = 12V, I_{OUT} = 500mA$



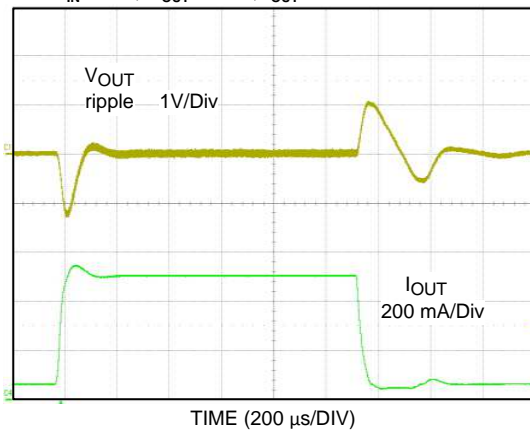Load Transient $V_{IN} = 5.5, V_{OUT} = 12V, I_{OUT} = 50mA$ to $500mA$



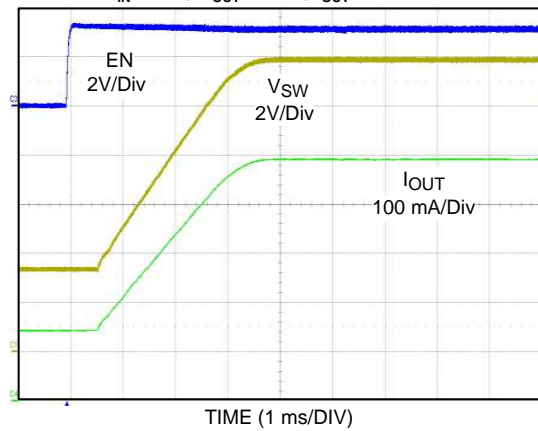Start Up with Enable $V_{IN} = 3.5, V_{OUT} = 12V, I_{OUT} = 500mA$



10 Layout

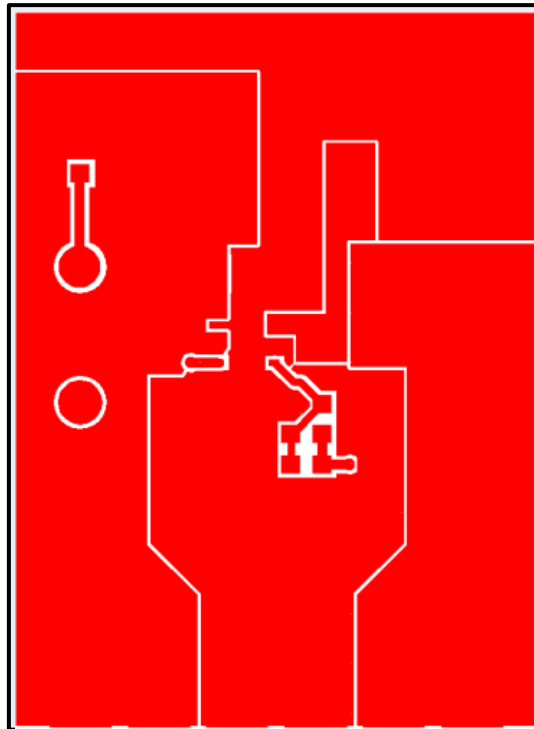


Figure 6. Top Layer

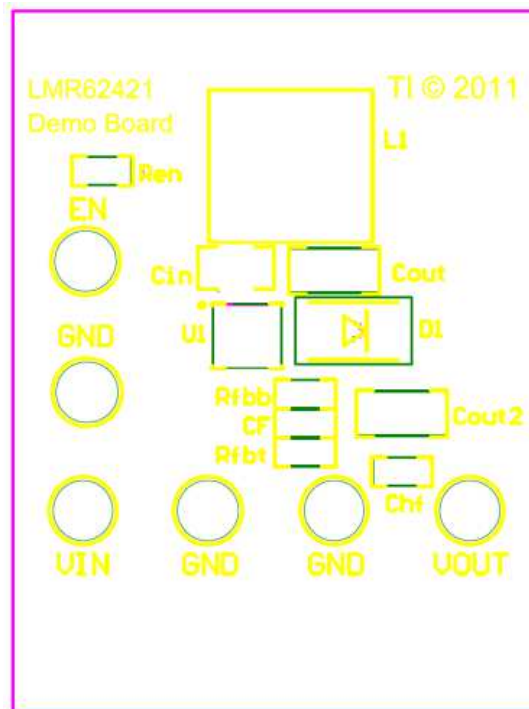


Figure 7. Top Overlay

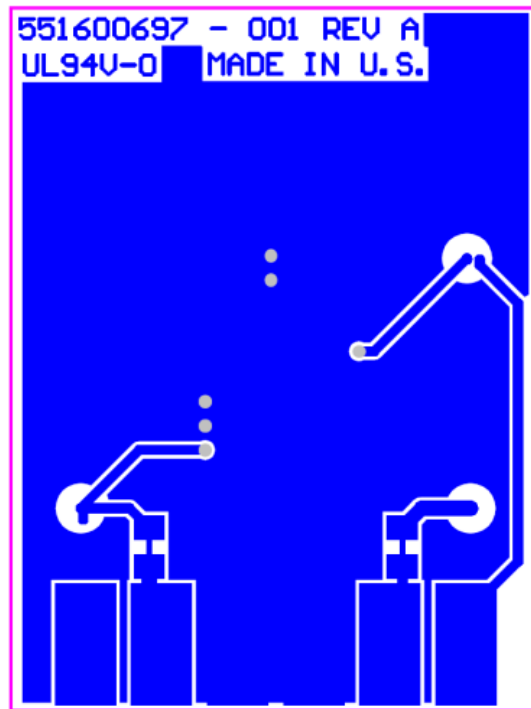


Figure 8. Bottom Layer

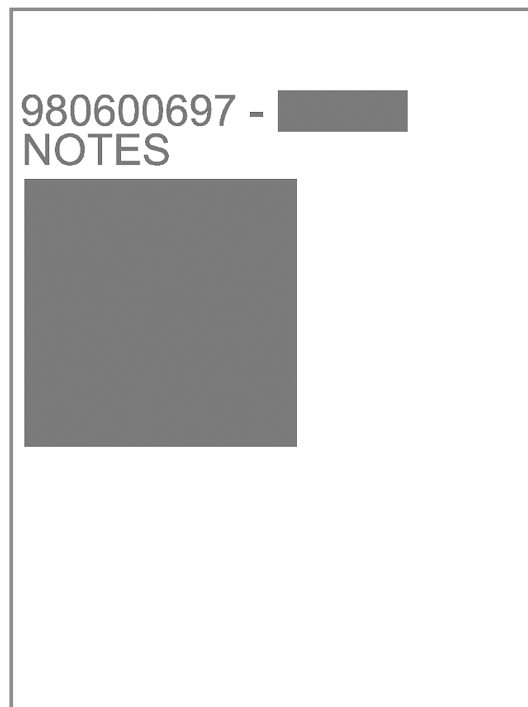


Figure 9. Bottom Overlay

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com