

TIDA-00334 Test Report

Bill Johns

BMS/WLPC

Abstract

TI design TIDA-00334 wireless power supply transmitter is an application of the bq500212A IC in a small form factor design targeted at low power wearable devices. Input voltage to the unit is 5V from a Micro USB connector. The low power design will support output power at the receiver up to 2.5W.

All key transmitter circuits are laid out in a 30mm area which matches the diameter the Würth coil P/N 760308101103. This area is slightly larger than a US Quarter or 2 Euro coin. PCB is 38mm X 76mm (1.5" X 3.0") but area for the circuit is inside the 30mm coil diameter is about 700mm².

The design is based on Qi standard components and will operate with Qi compliant receivers but due to the reduced power level is not certifiable to the standard.

The TIDA-00334 is derived from the application design PR2186, both numbers may appear in documentation but refer to a single design.

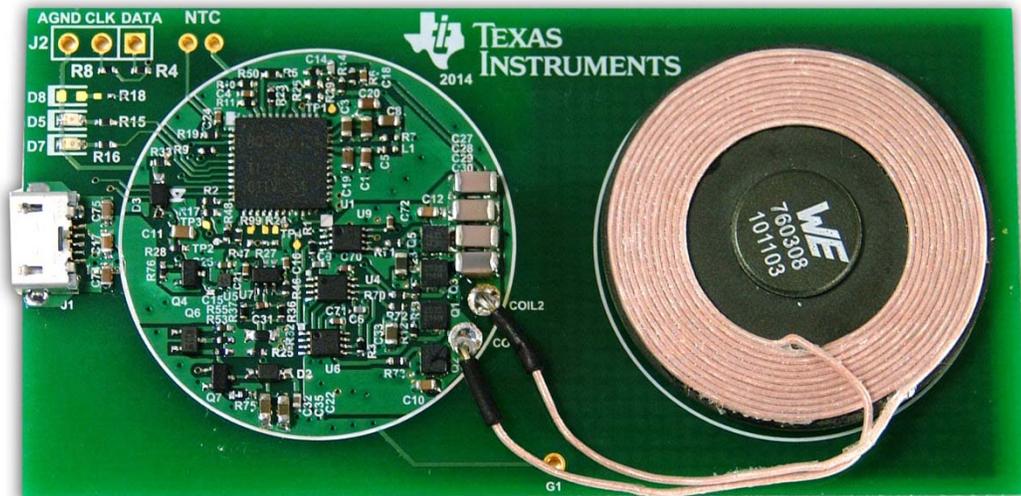


Figure 1. TIDA-00334 Photo

WARNING: EXPORT NOTICE

Recipient agrees to not knowingly export or re-export, directly or indirectly, any product or technical data (as defined by the U.S., EU, and other Export Administration Regulations) including software, or any controlled product restricted by other applicable national regulations, received from Disclosing party under this Agreement, or any direct product of such

technology, to any destination to which such export or re-export is restricted or prohibited by U.S. or other applicable laws, without obtaining prior authorization from U.S. Department of Commerce and other competent Government authorities to the extent required by those laws. This provision shall survive termination or expiration of this Agreement.

According to our best knowledge of the state and end-use of this product or technology, and in compliance with the export control regulations of dual-use goods in force in the origin and exporting countries, this technology is classified as follows:

US ECCN: 3E991

EU ECCN: EAR99

And may require export or re-export license for shipping it in compliance with the applicable regulations of certain countries.

bq51003 EVM / Receive Coil

- The bq51003 wireless power receiver is optimized for low power application. The TDK WR222230 is smaller coil that is half the size of the standard EVM coil. The combination of the bq51003 and WR222230 are an example of a small low power receiver solution. Test data is shown with this receiver configuration. Also see TIDA-00318 and TIDA-00329 compact receiver designs. They will work well with this transmitter and are good companion designs.

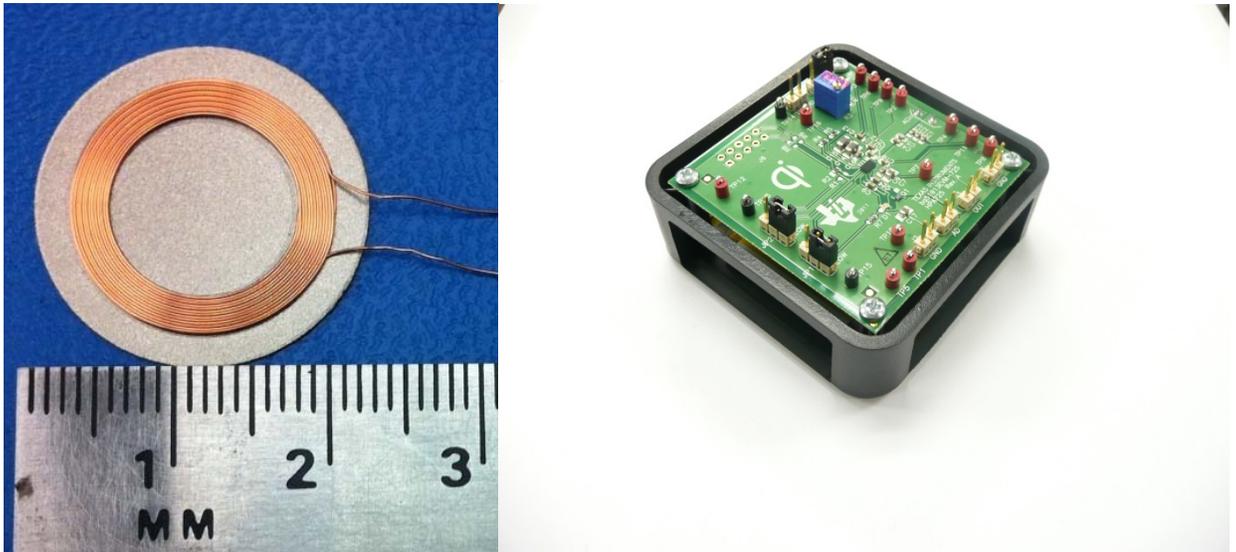


Figure 2 Test Receiver Coil and bq51003 EVM

Block Diagram

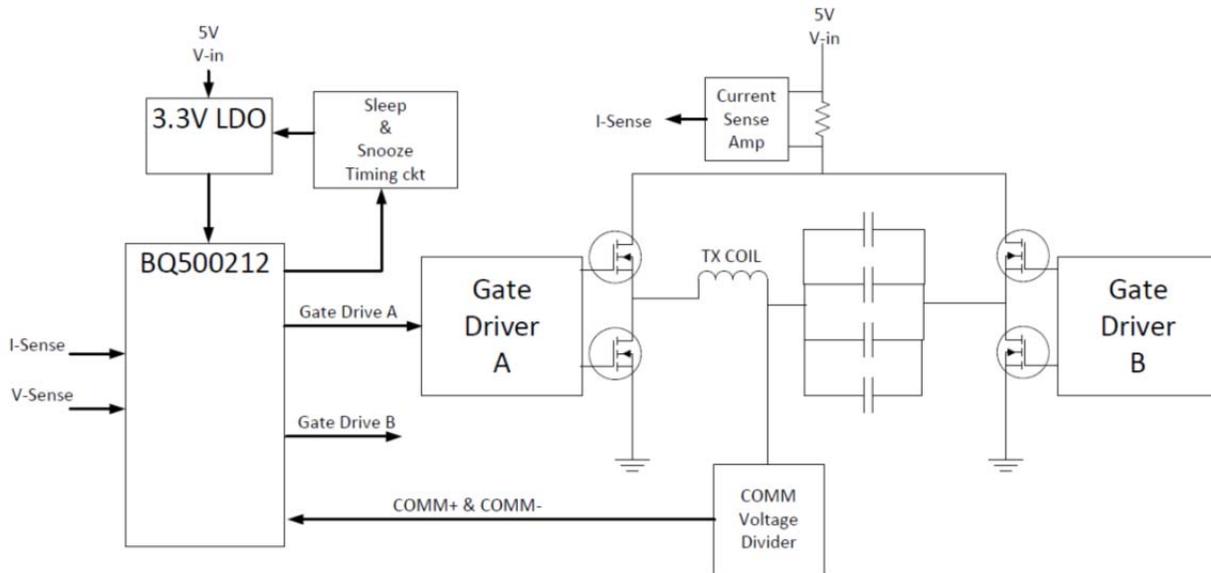


Figure 3 Block Diagram

Schematic

- The TIDA-00334 power schematic shown in figure 4 and bq500212A section schematic is shown in figure 5.

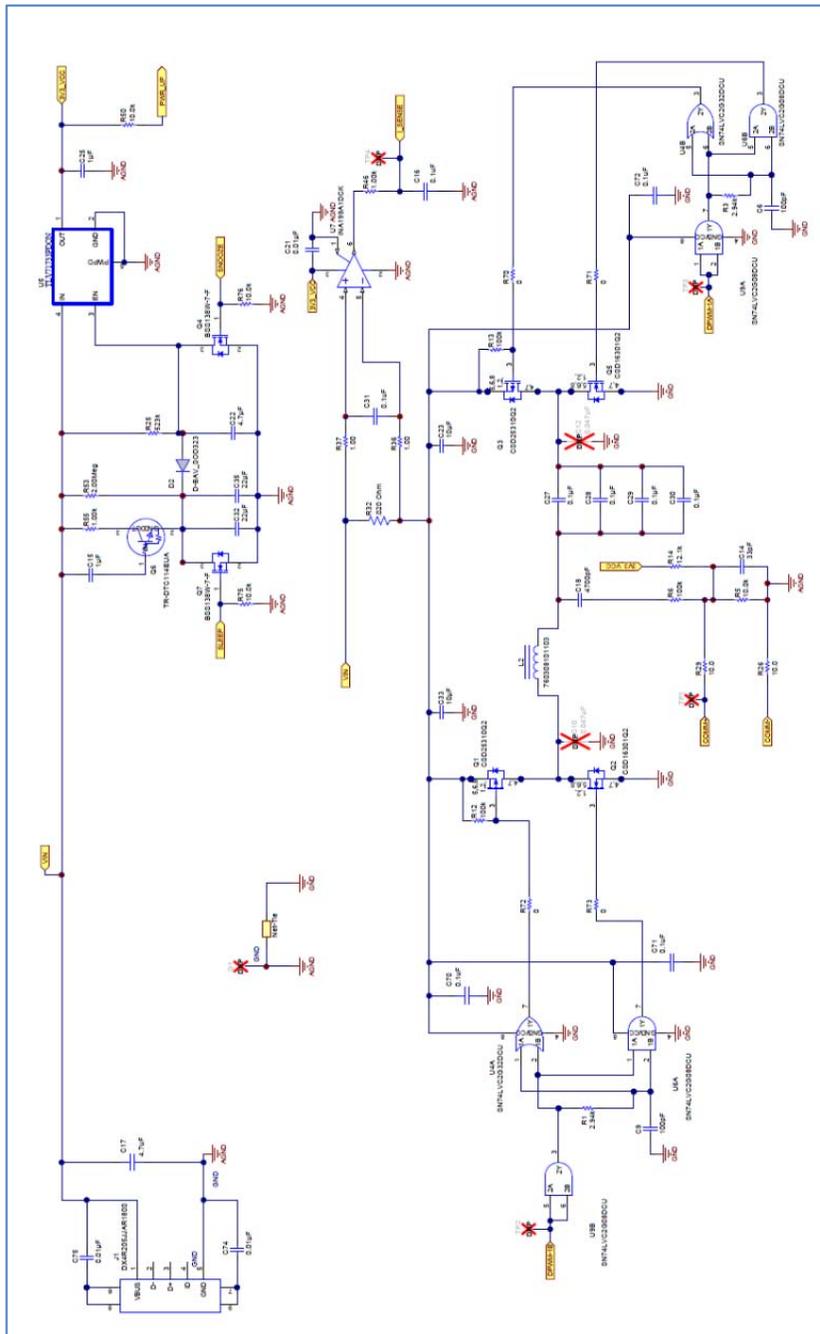


Figure 4 Schematic Power Section

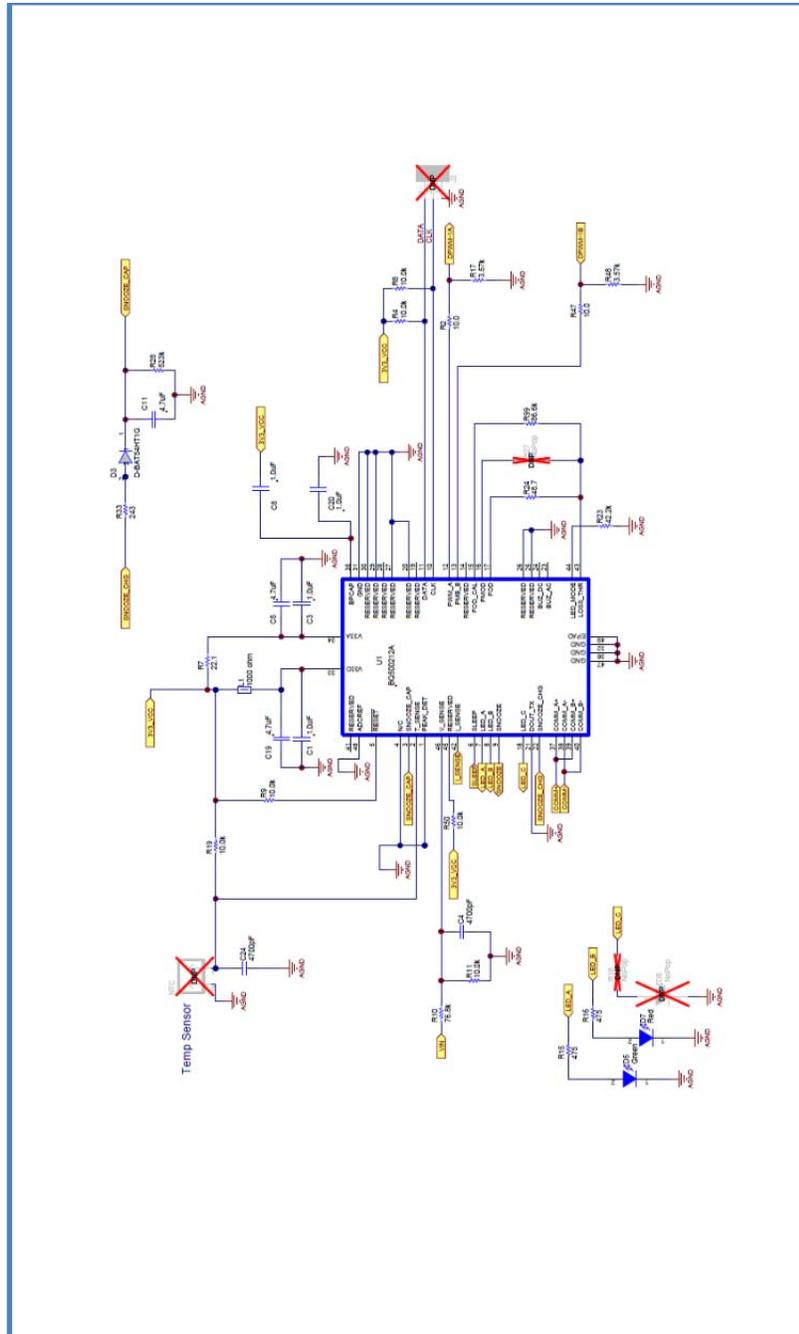


Figure 5 Schematic bq500212A Section

Configuration Options

LED Mode – Resistor R23 controls the behavior of status LED D5, D7 and D8. The standard value is 42.2k Ω for control option 1, see data sheet for additional settings.

NTC- Connector provides the option for connecting a negative temperature coefficient (NTC) sensor for thermal protection, see data sheet for additional settings.

DATA / CLK / AGND – I²C interface to the bq500212A can be used with software tools to monitor device operation. Consult datasheet for more info.

FOD / PMOD – Protection feature that is enabled and disabled using resistor R24 & R99 for FOD and R27 for PMOD. Recommend disabling the feature for initial evaluation, remove R24, R99 and R27. If feature is used a calibration procedure needs to be run on final production unit to determine values, see datasheet for additional settings.

Power Section Configuration

The coil is driven by a full H-Bridge under logic control of the bq500212A. The H-Bridge configuration used for TIDA-00334 is one of several that can be used.

- 1.) Low cost logic drive used on the TIDA-00334. The MOSFET driver is replaced by a logic circuit that drives a P & N-type MOSFET switch configuration.
- 2.) Small integrated solution using power stage device, CSD97376CQ4M. This device will integrate the MOSFETs and Driver into one small package. Design used on the bq500212A EVM and can be used here also.
- 3.) MOSFET Drive solution using TPS28225. This driver or similar devices can driver any number of external N-type MOSFETs can be used. Design used on the bq500211 EVM and can also be used here.

Key requirements to keep in mind while designing the power section. Current in the TX Coil and Resonant Capacitor (C27, 28, 29 and 30) is high even with no load, about 1A. MOSFETs with low RDSon should be used, typically 10m to 30m Ω. Propagation time though the driver will impact communication and should be kept low.

Test Results

- Figure 6 shows a typical start up behavior for the TX and RX as the RX is placed on a TX in standby. The TX can be seen transitioning from standby with digital ping every 500ms to power transfer.



Figure 6 Start Up into 100mA load

- Figure 7 shows the TX and RX behavior during Charge Complete, EPT 01. The bq51003 is configured to send EPT 01. In response TX will end power transfer and not ping for about 2.5 seconds.

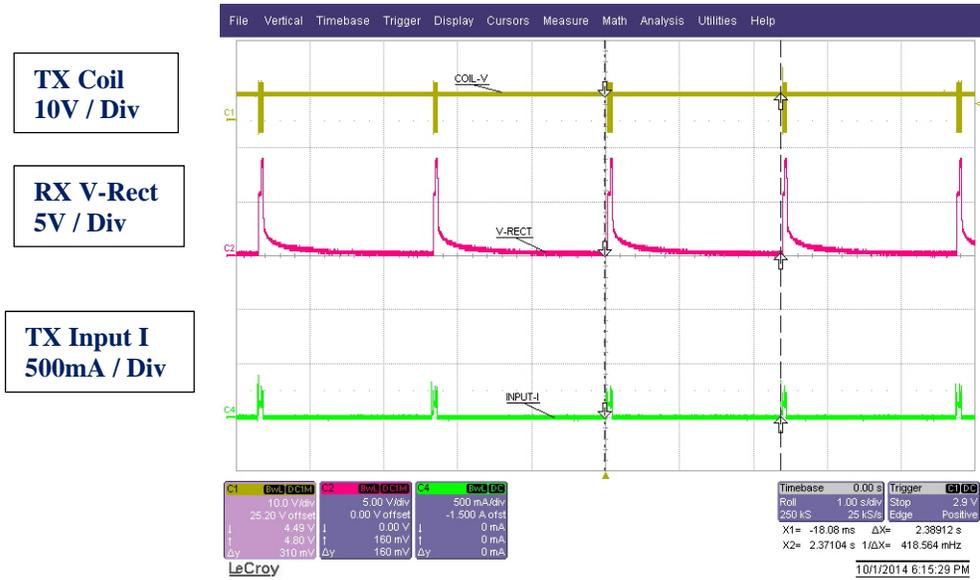


Figure 7 Charge Complete, End Power Transfer 01

- Figure 8 shows the efficiency across the power range with the bq51003EVM-764. This is the total system efficiency including the transmitter, coils and receiver.

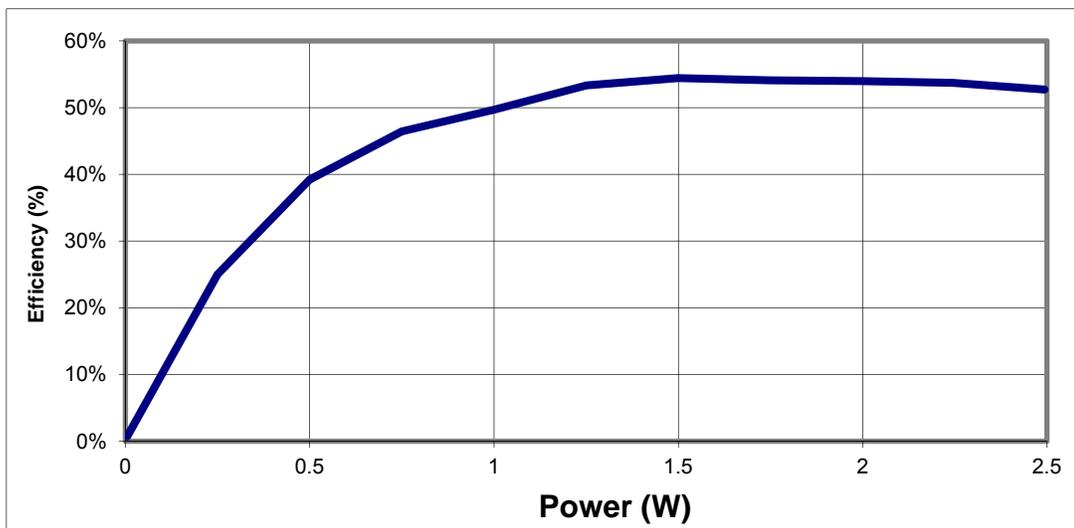


Figure 8 TIDA-00334 Efficiency with bq51003

Thermal Measurements

- The following figure shows a thermal image of the TIDA-00334 operating with the bq51003EVM-764 RX at 500mA output load.

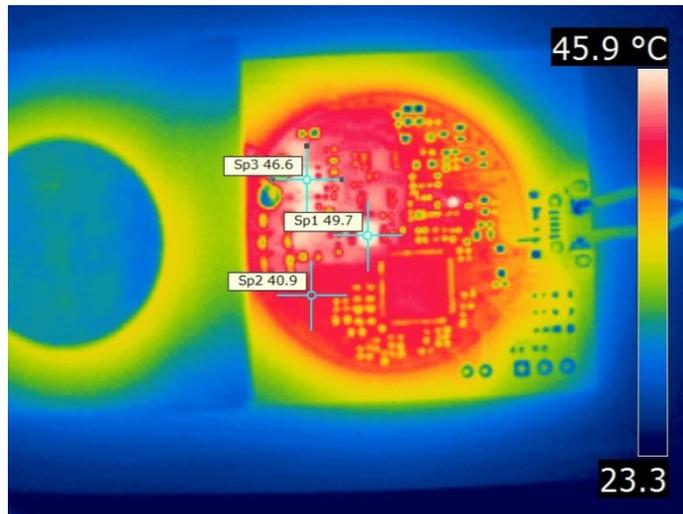


Figure 9 TIDA-00334, RX output current 500mA

References

- Data Sheet bq500212A Wireless Power Controller for WPC (SLUSB6C)

Document History

Version	Date	Author	Notes
2.0	January 2015	Bill Johns	Correct BOM Value, R24, R33, R70, R71, R72, R73 and R99 Changed R23 to 42.2k LED mode 1. Change R24 and R99 to open, FOD optional Change bq500212A pins 21, 25, 26, 27, 29 and 30 to open. Avoid conflict with datasheet.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.