

# PMP8639RevA2 Test Results


---

1	Startup .....	2
2	Shutdown .....	3
3	Efficiency .....	4
4	Load Regulation .....	5
5	Ripple Voltage .....	6
6	Control Loop Frequency Response.....	7
6.1	Type 2 compensation FINAL = 71.2kOhm .....	7
7	Load Transients .....	8
8	Miscellaneous Waveforms .....	9
9	Thermal Image.....	13
10	Loop Appendix.....	15
10.1	Type 3 Compensation.....	15
10.2	Type 2 Compensation Z25Hz P25kHz .....	17
10.3	Type 2 Compensation Z250Hz P25kHz .....	19
10.4	Type 2 Compensation Z75Hz P25kHz bw 1kHz .....	21
11	Inductor Appendix.....	23

Topology: Inverting Cuk, 36Vin/-36Vout  
Device: LM5022

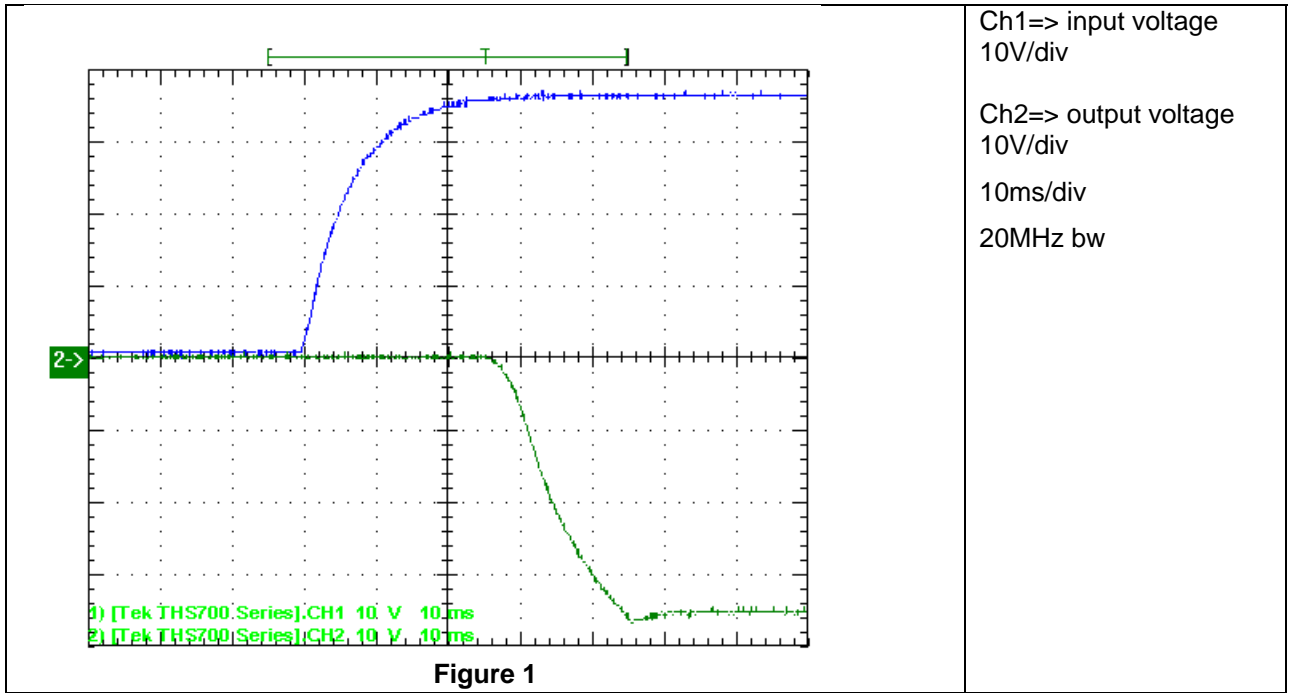
## 1 Startup

The startup waveform is shown in the Figure 1. The input voltage was set at 36V, with 1A load at the output. Power supply was switched on.


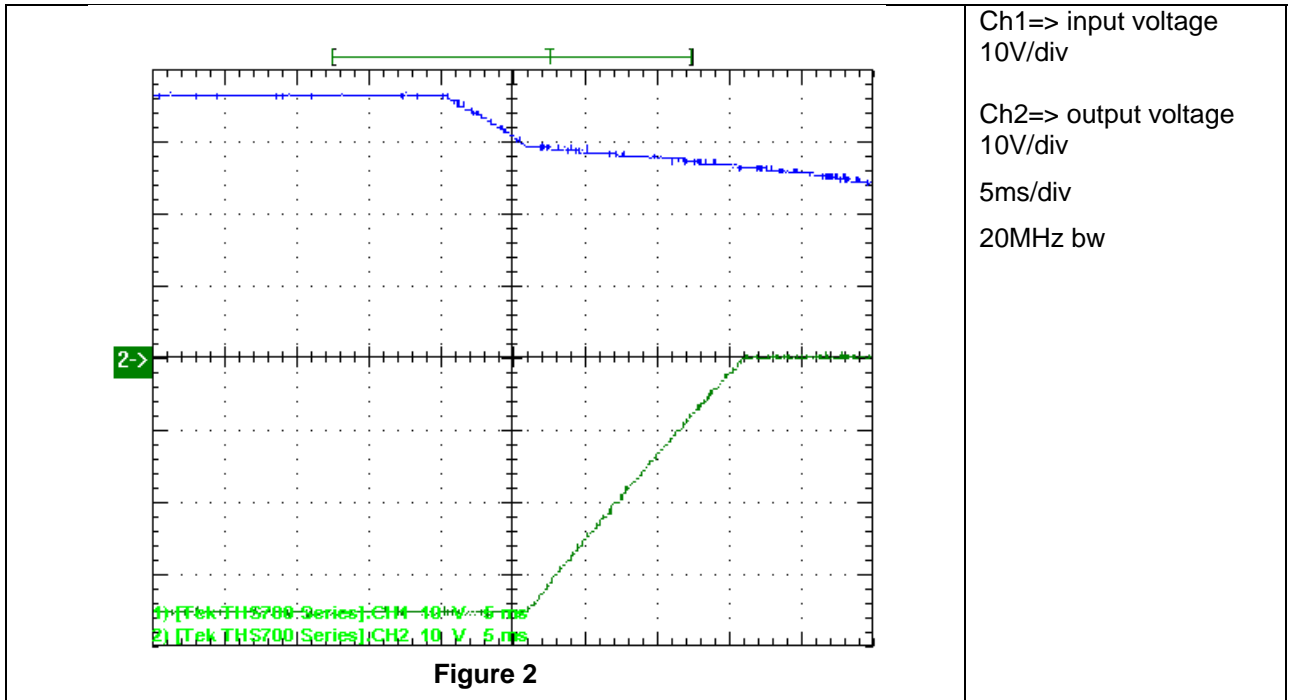
## 2 Shutdown

The shutdown waveform is shown in the Figure 2. The input voltage was set at 36V, with 1A load on the output. The power supply was switched off (short).



## 3 Efficiency

The efficiency is shown in the Figure 3 below. The input voltage was set to 36V.

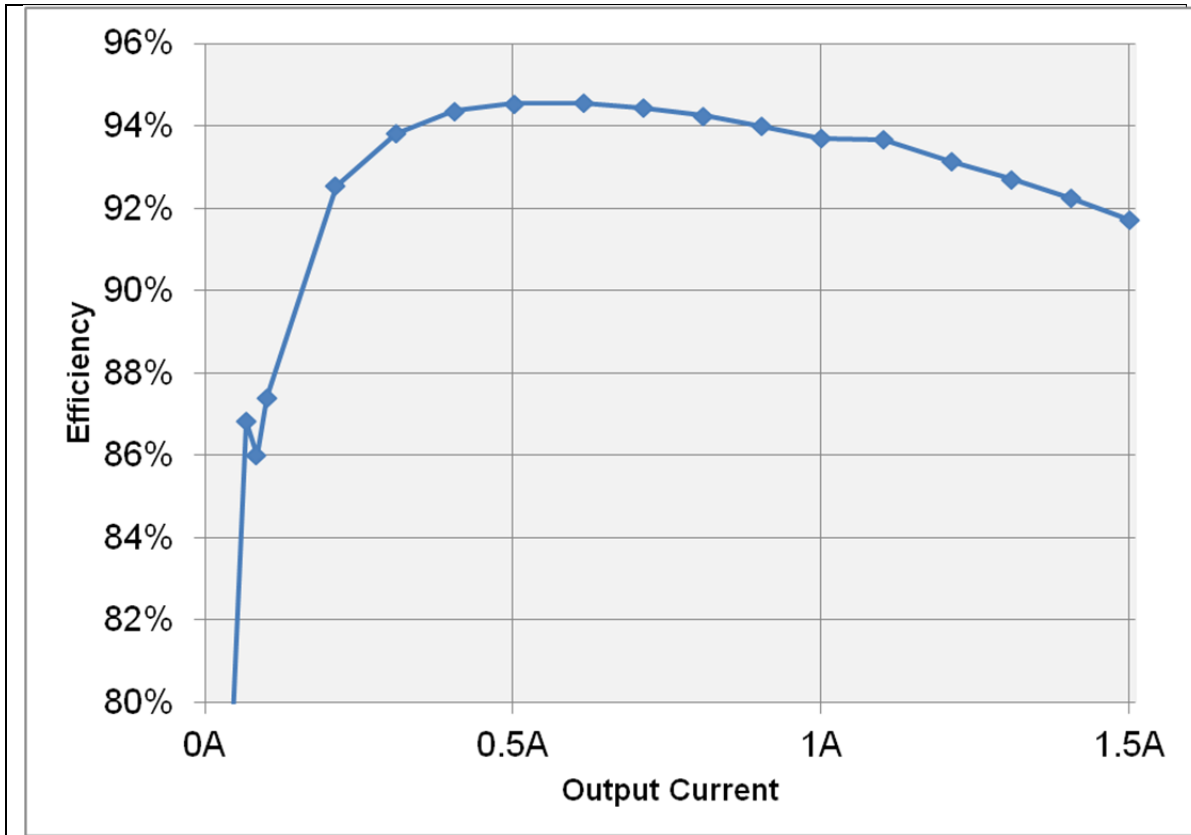


Figure 3

## 4 Load Regulation

The load regulation of the output is shown in the Figure 4 below. The input voltage was set to 36V.


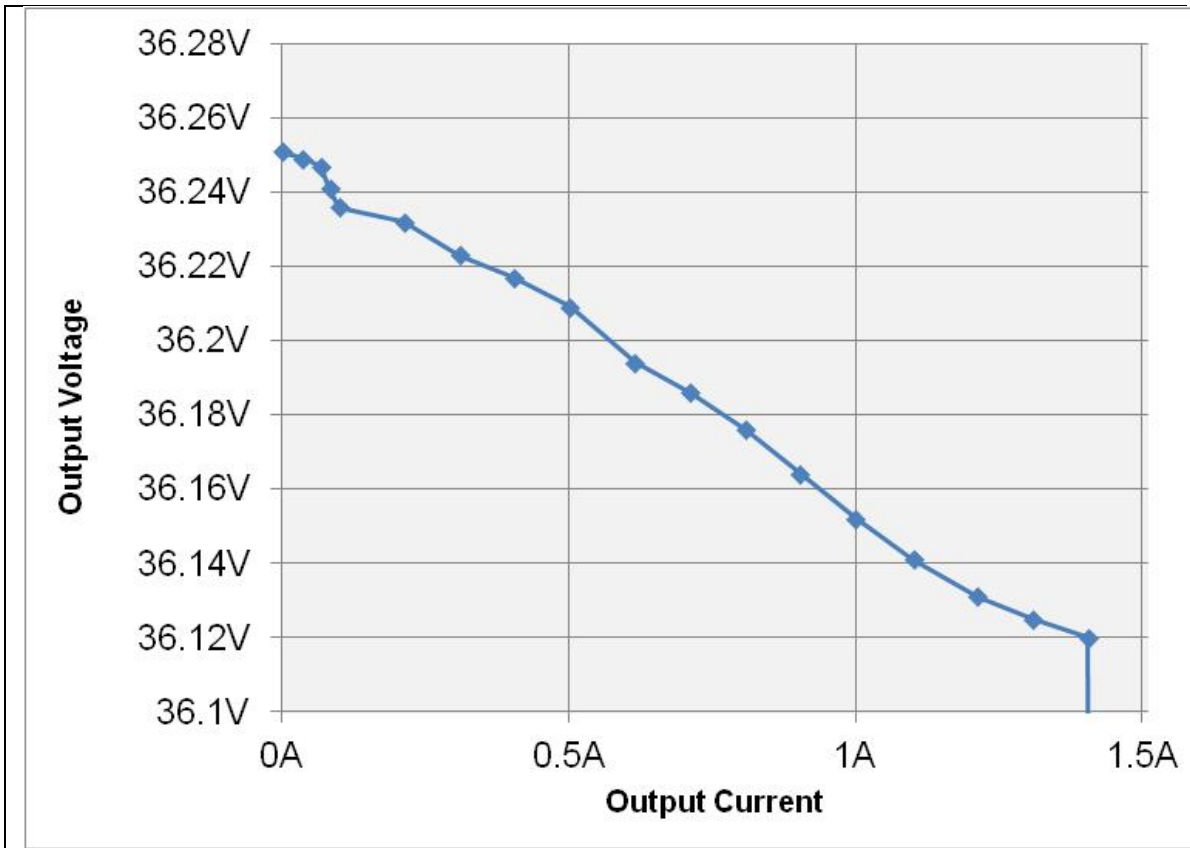



Figure 4
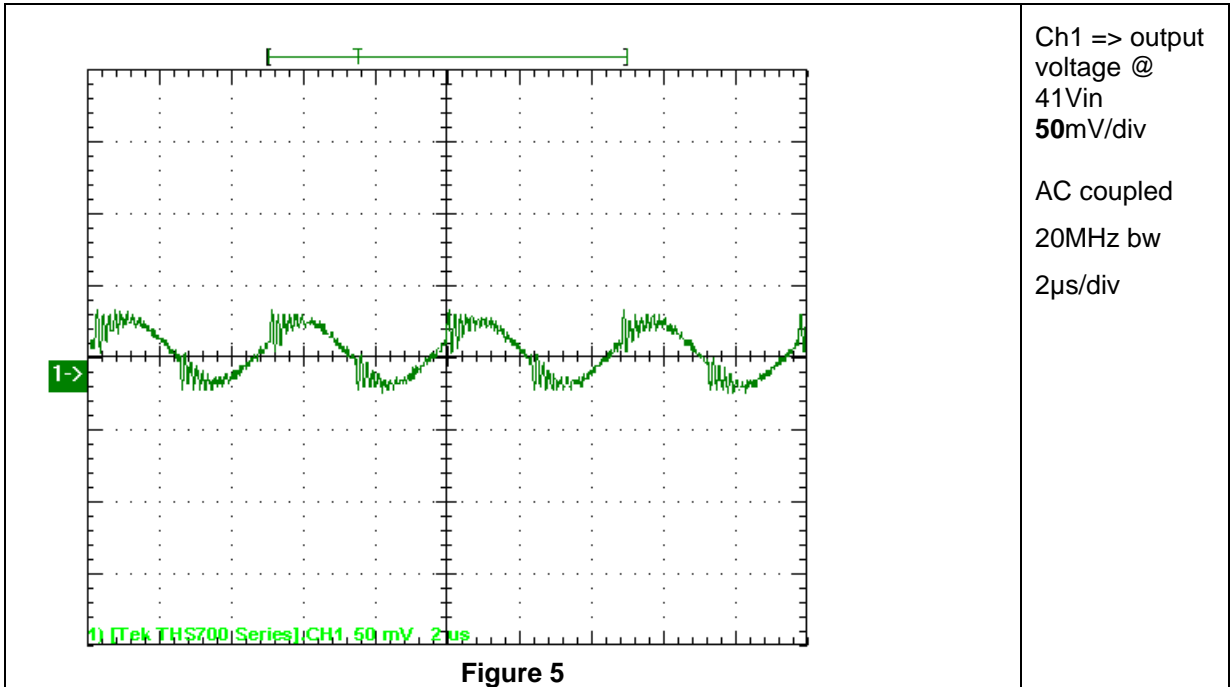
## 5 Ripple Voltage

The output ripple voltage is shown in Figure 5. The image was taken with 1A load and 36V input.



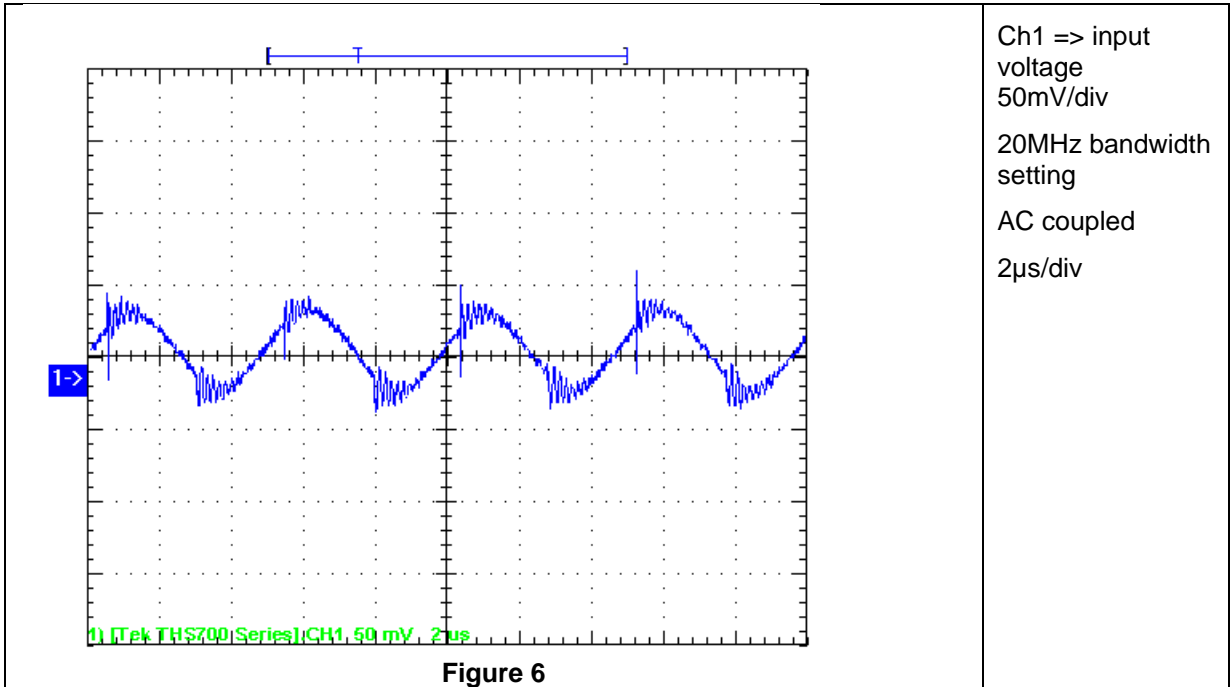The input ripple voltage is shown in Figure 6. The image was taken with 1A load 36V at the input.



## 6 Control Loop Frequency Response

Figure 7 and Figure 17 show the loop response with 1A load and 36V input with different compensation types

### 6.1 Type 2 compensation FINAL = 71.2kOhm

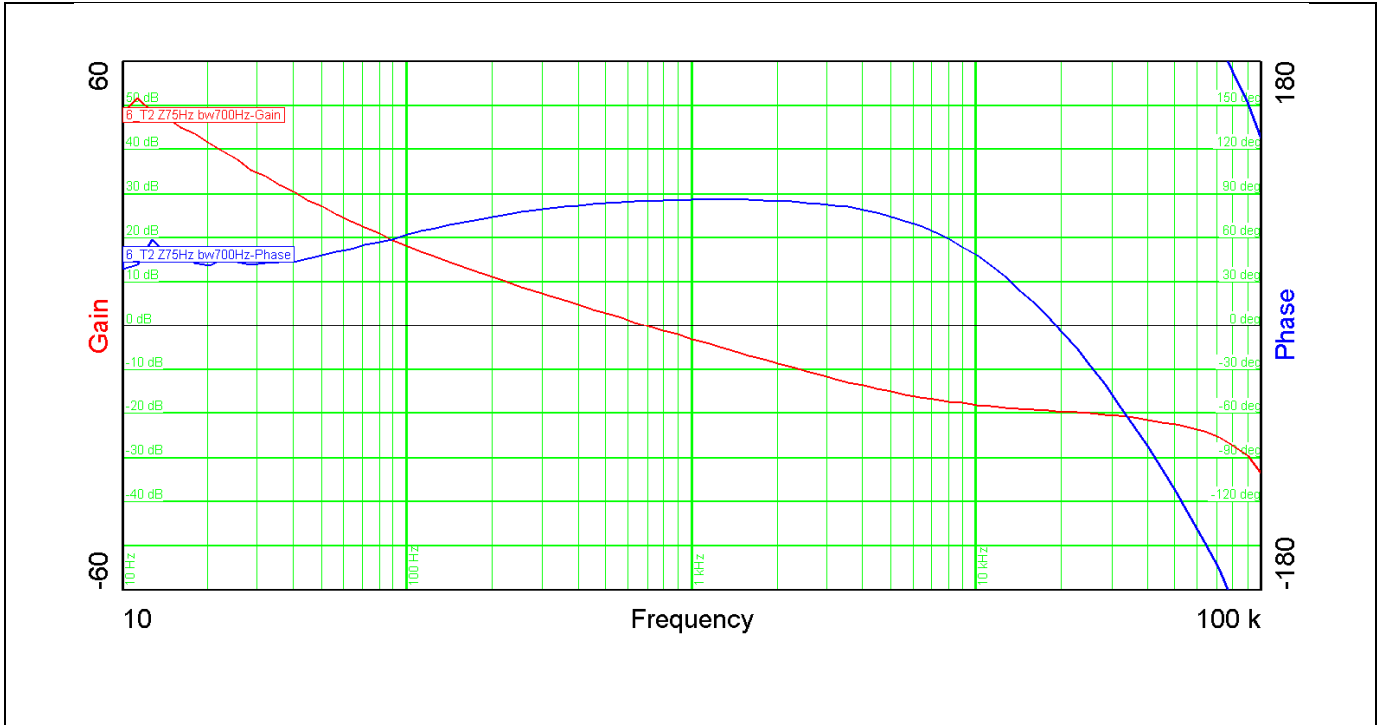


Figure 7

Table 1 summarizes the results from Figure 7


<b>Input Voltage</b>	36V
<b>Bandwidth (Hz)</b>	698
<b>Phasemargin</b>	85°
<b>slope (20dB/decade)</b>	-0.996
<b>gain margin (dB)</b>	-19.5
<b>slope (20dB/decade)</b>	-0.234
<b>freq (kHz)</b>	19

Table 1


Here: R14 71.5k, C17 33nF, C18 100pF
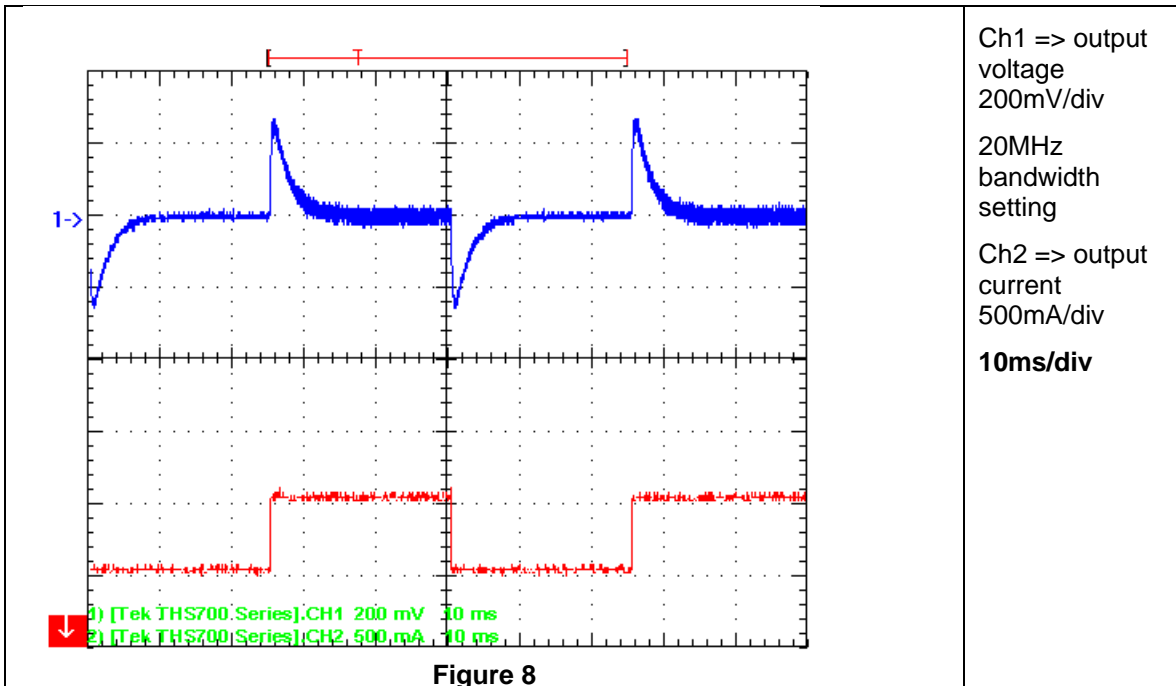
## 7 Load Transients

The Figure 8 shows the response to load transients. The load is switching from 0.5A to 1A, 50% nominal load step. The input voltage was set to 36V:



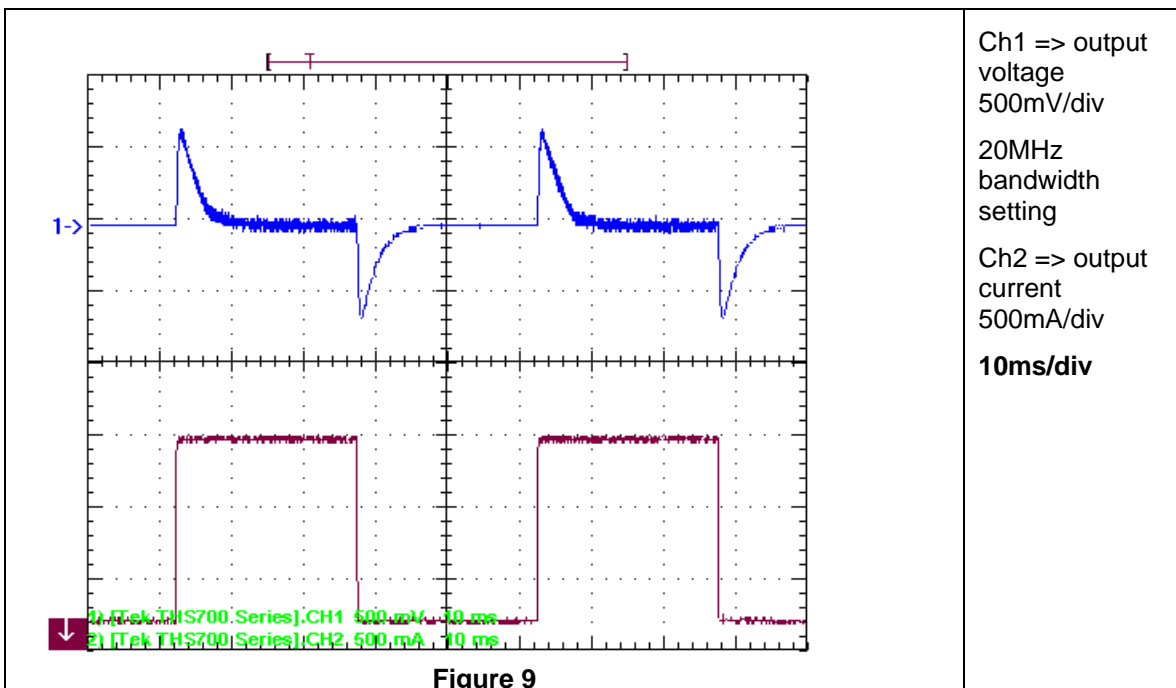The Figure 9 shows the response to load transients. The load is switching from 0.14A to 1.4A. The input voltage was set to 36V.





## 8 Miscellaneous Waveforms

The **drain-source** voltage on Q2 results in the waveform shown in Figure 10. Input voltage was set to 36V and output current to 1A.

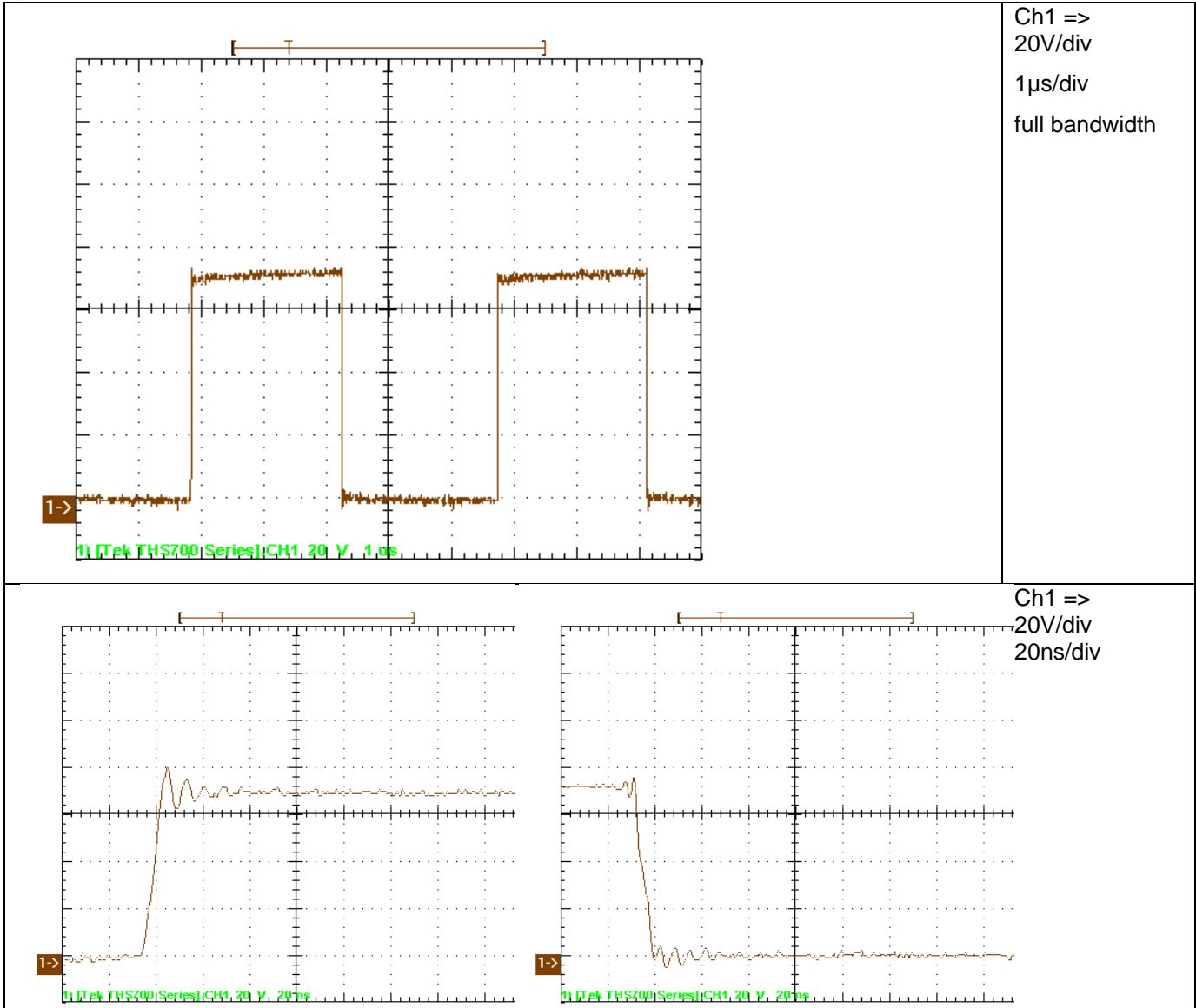


Figure 10

# PMP8639RevA2 Test Results

The **gate-source** voltage on Q1 results in the waveform shown in Figure 11. Input voltage was set to 36V and output current to 1A.

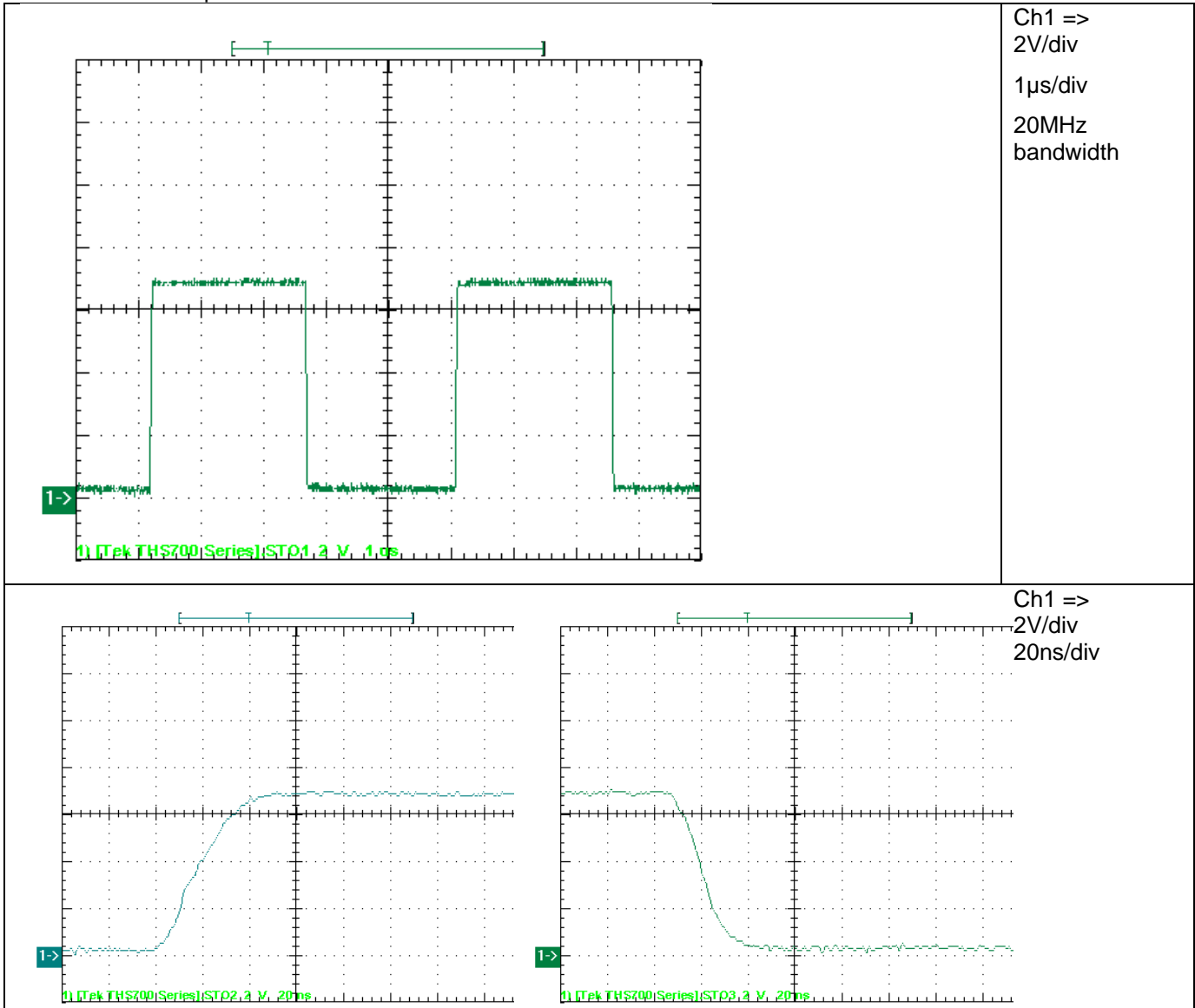


Figure 11

The voltage at D3 results in the waveform shown in Figure 12. Input voltage was set to 36V and output current to 1A.


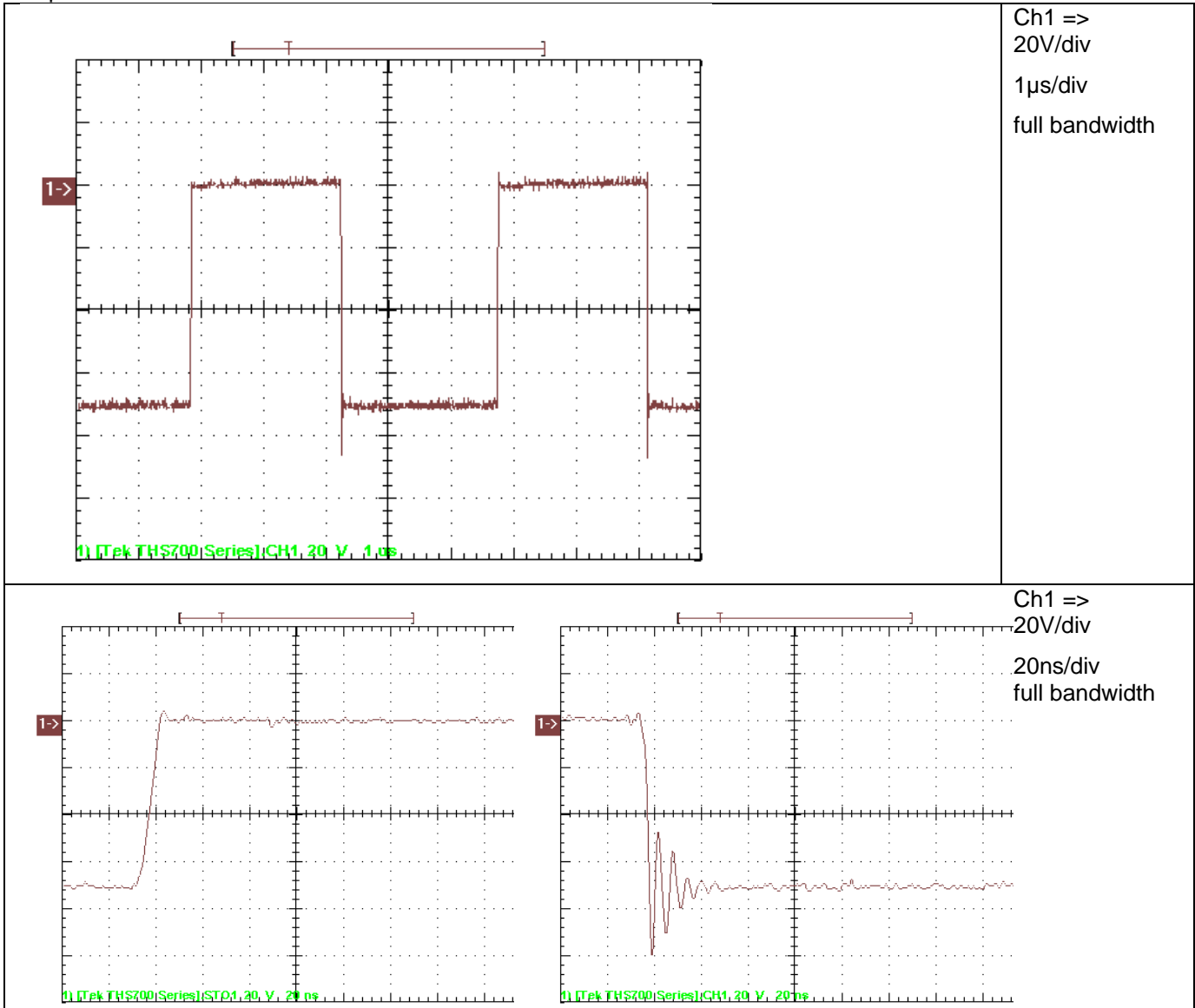


Figure 12

Figure 13 shows the waveform between the two switchnodes (C10, C11, C12, C13, C24, C25)

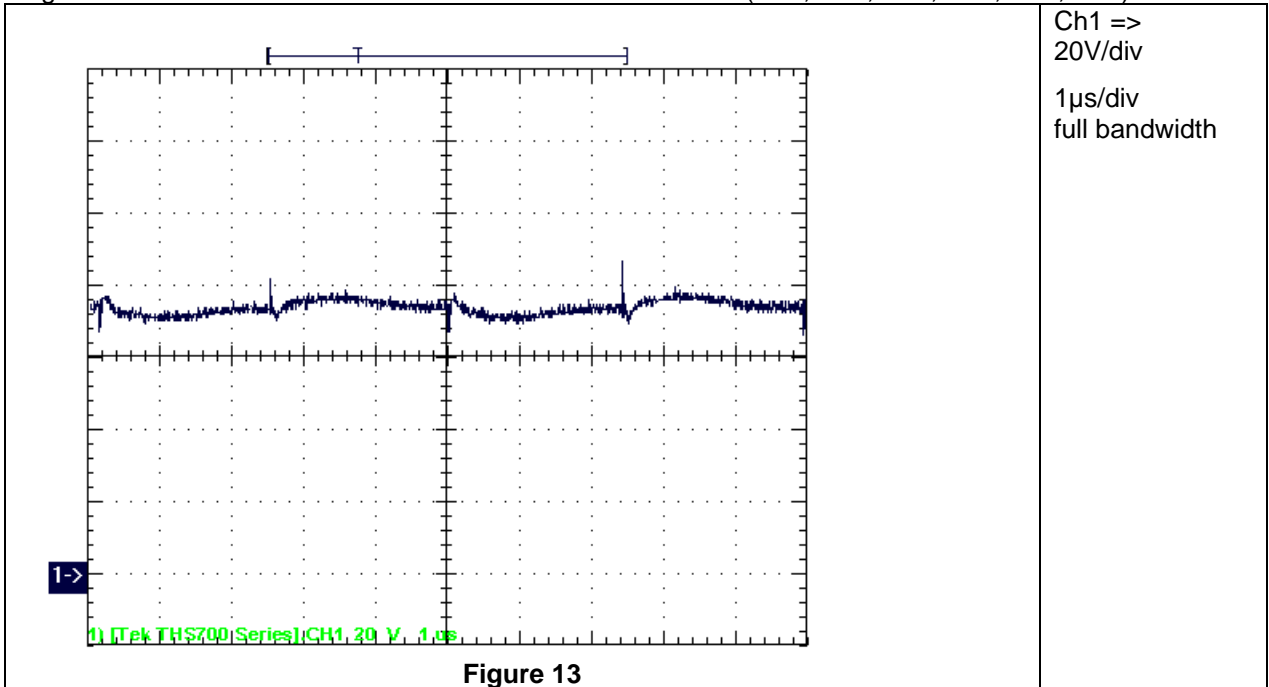

## 9 Thermal Image

Figure 14 shows the IR-Image input voltage was set to 36V with 0.5A output current.

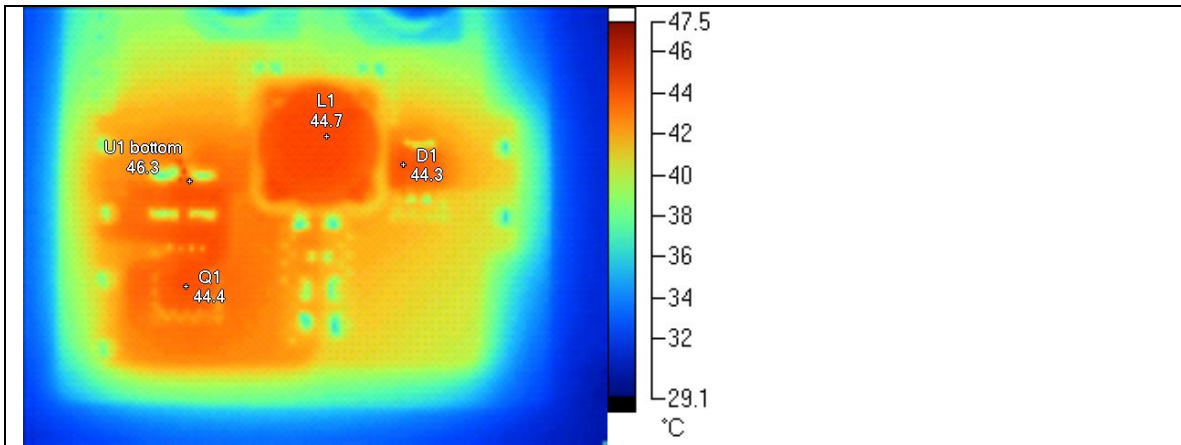


Figure 14

Name	Temperature
U1 bottom	46.3°C
D1	44.3°C
Q1	44.4°C
L1	44.7°C

Table 2

Figure 15 shows the IR-Image input voltage was set to 36V with 1A output current.

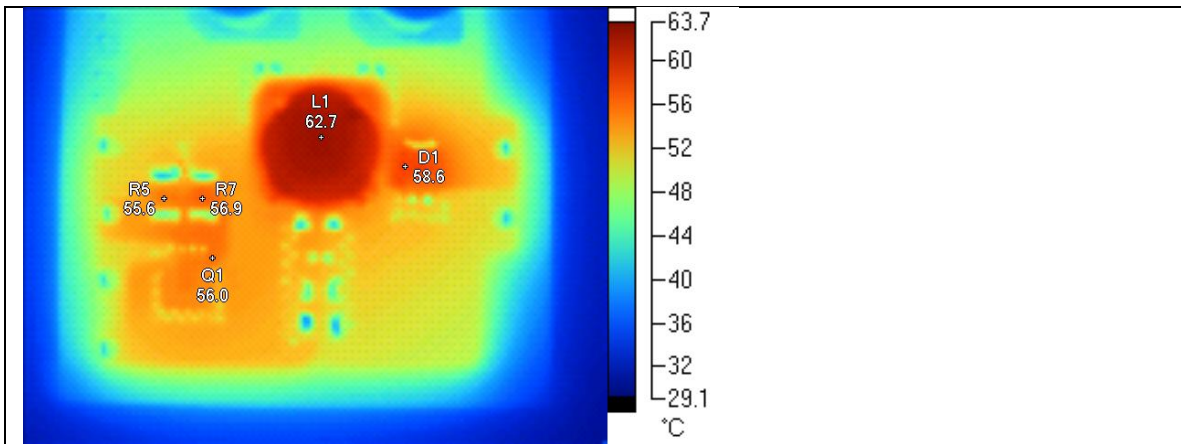



Figure 15

Name	Temperature
L1	62.7°C
D1	58.6°C
Q1	56.0°C
R7	56.9°C
R5	55.6°C

Table 3

# PMP8639RevA2 Test Results

Figure 16 shows the IR-Image input voltage was set to 36V with 1.4A output current.

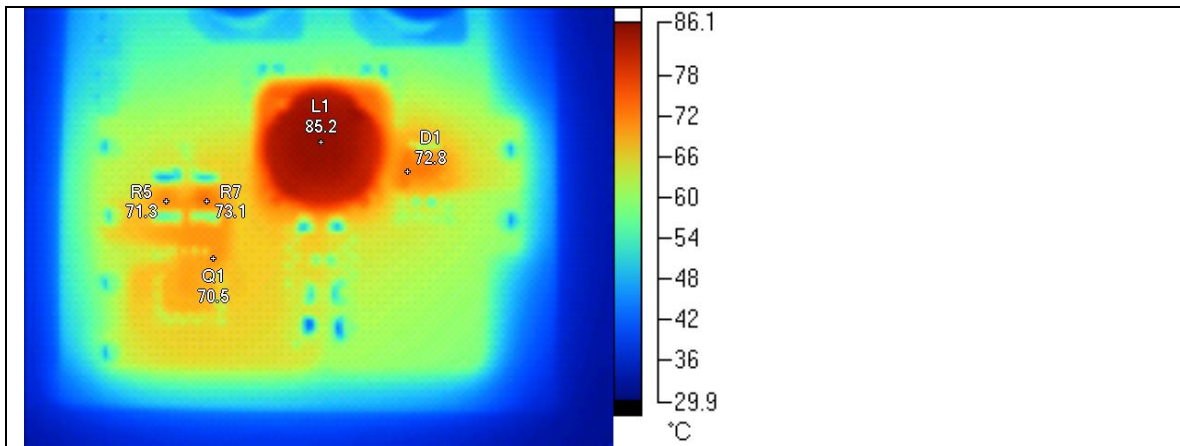

**Figure 16**

Name	Temperature
L1	85.2°C
D1	72.8°C
Q1	70.5°C
R7	73.1°C
R5	71.3°C

**Table 4**

For 1.5A continuous load there is rework on the dual inductor needed; semiconductors and controller still OK

10 Loop Appendix

10.1 Type 3 Compensation

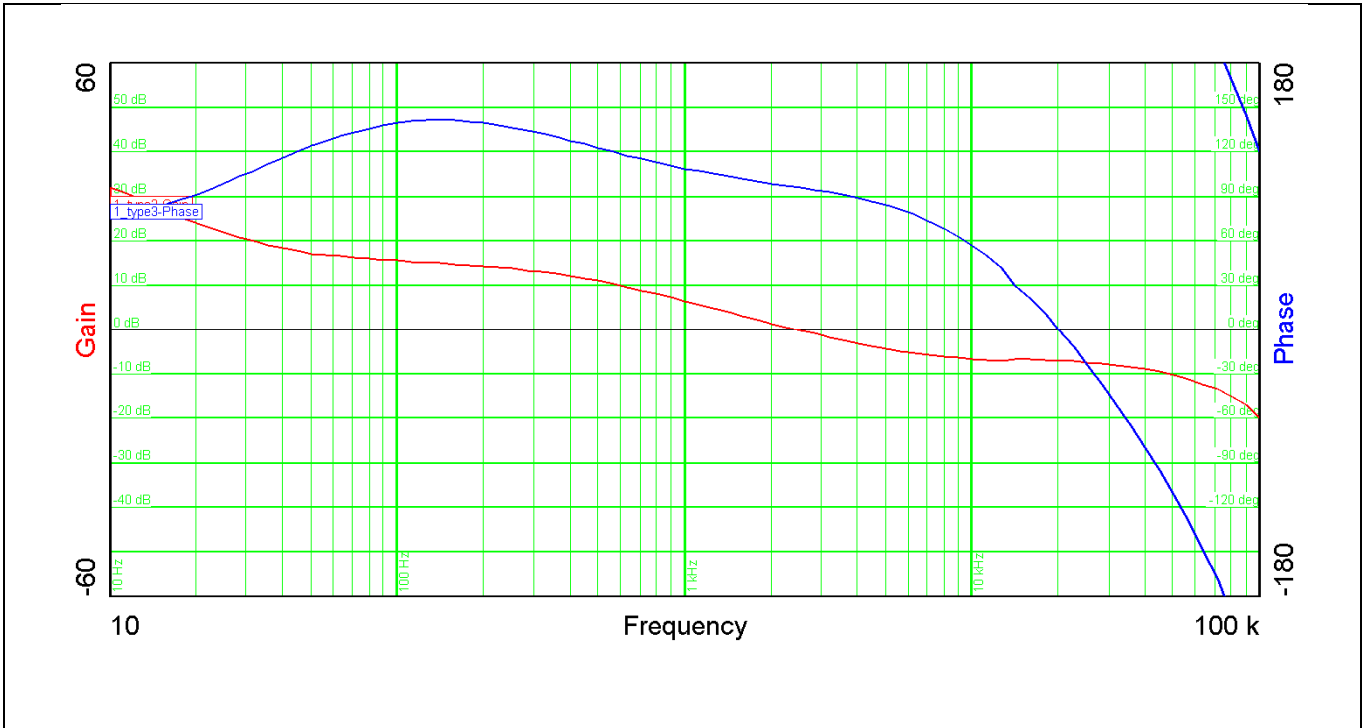


Figure 17

Table 5 summarizes the results from Figure 17,

<b>Input Voltage</b>	36V
<b>Bandwidth (kHz)</b>	2.45
<b>Phasemargin</b>	96°
<b>slope (20dB/decade)</b>	-0.81
<b>gain margin (dB)</b>	-7.1
<b>slope (20dB/decade)</b>	-0.125
<b>Freq (kHz)</b>	20

Table 5

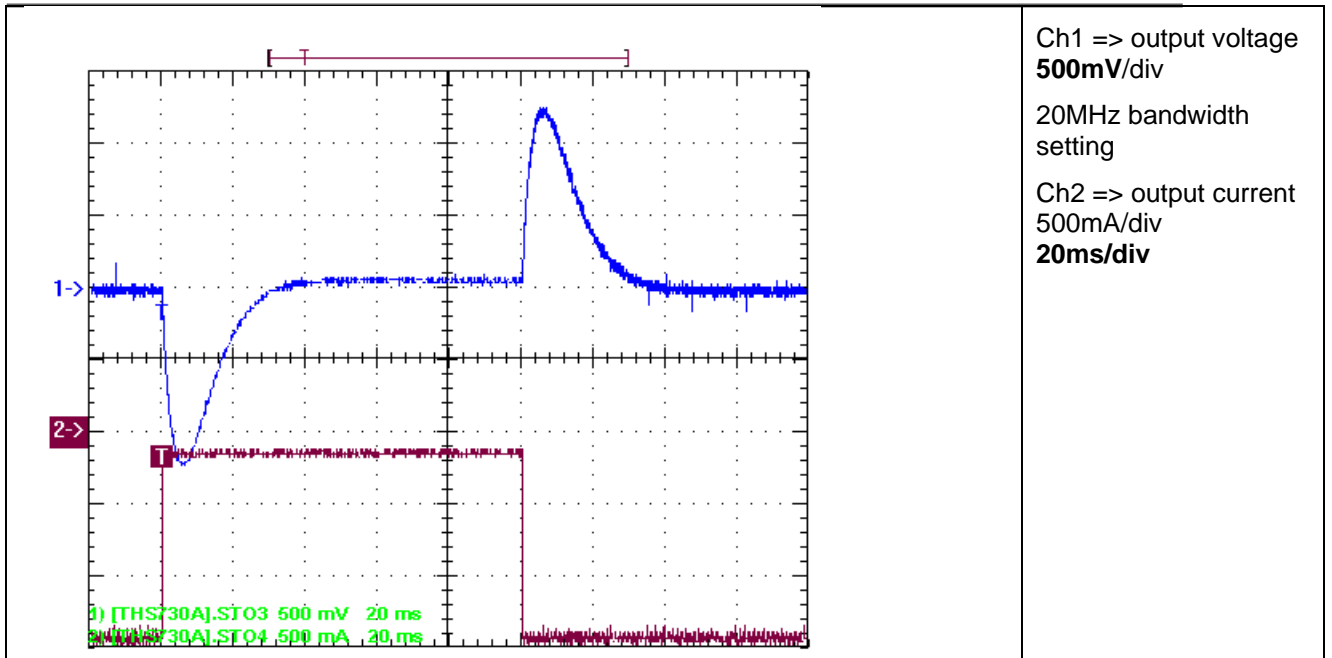


Figure 18

R14 20k, C17 330nF, C18 330pF,  
R2 10k, C1 68nF

### Type 3 compensation:

On a first glance highest bandwidth w/ 2.45kHz, but a very low, flat DC gain – results in transient response **du 1.25V** by di 90% (140mA to 1.4A)



10.2 Type 2 Compensation Z25Hz P25kHz

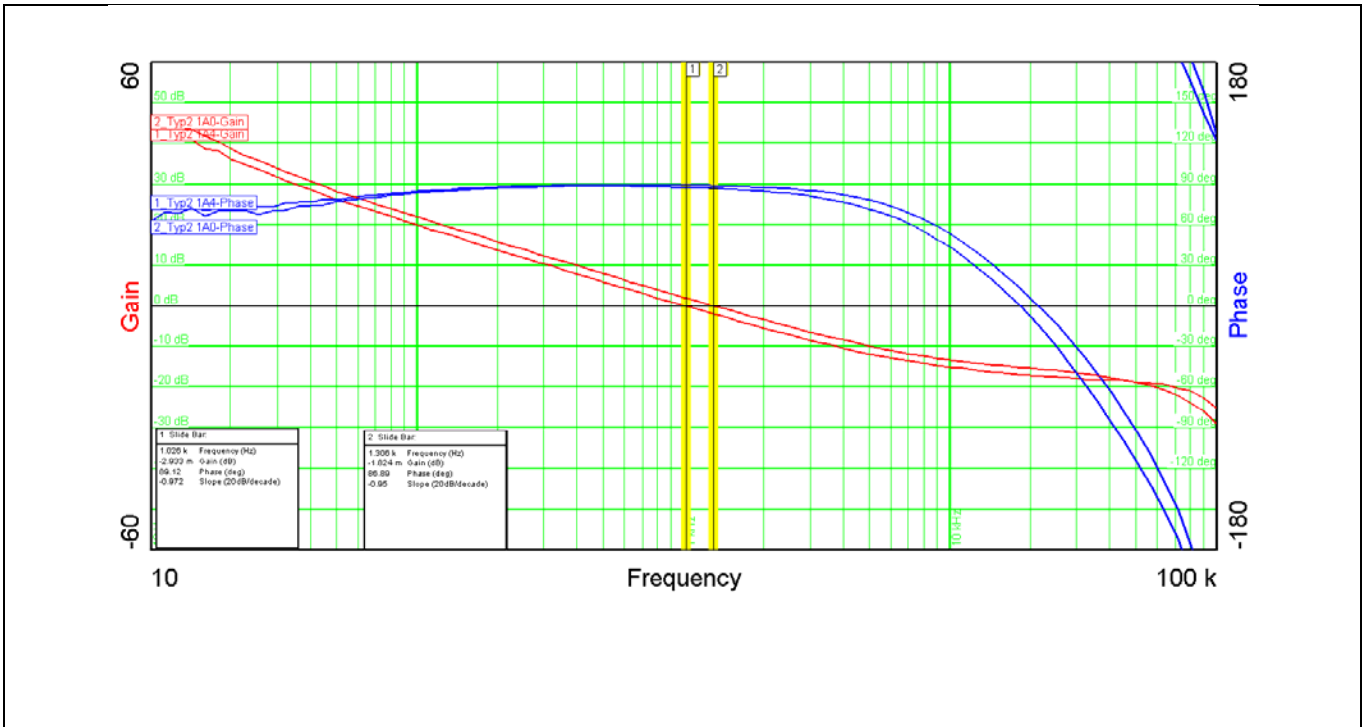


Figure 19

Table 6 summarizes the results from Figure 19,

<b>Output Current</b>	1A	1.4A
<b>Bandwidth (kHz)</b>	1.3	1
<b>Phasemargin</b>	87°	89
<b>slope (20dB/decade)</b>	-0.95	-0.97
<b>gain margin (dB)</b>	-15.2	-17.3
<b>slope (20dB/decade)</b>	-0.28	0.187
<b>Freq (kHz)</b>	18.3	21.5

Table 6

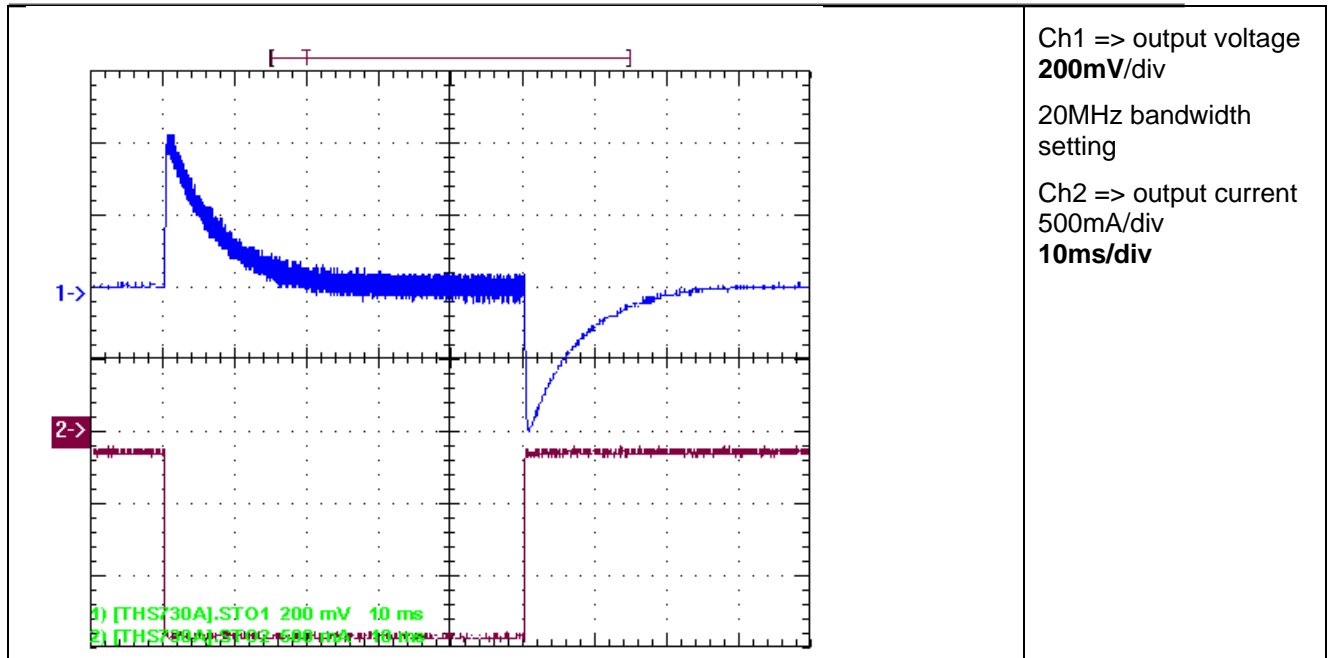


Figure 20

R14 133k, C17 56nF, C18 56pF

#### Type 2 compensation:

Less than half the bandwidth of type 3, but improved DC gain – results in transient response **du 400mV** by di 90% (140mA to 1.4A).

Means only one third derivation than the type 3 compensation !

BUT: due to the high gain at the error amplifier R14 133kOhm = 28.5db (!) signal to noise ratio decreases, results in **gate jitter** and modulating subharmonics to Vout.

Next step: increasing the ZERO and reducing the gain.

10.3 Type 2 Compensation Z250Hz P25kHz

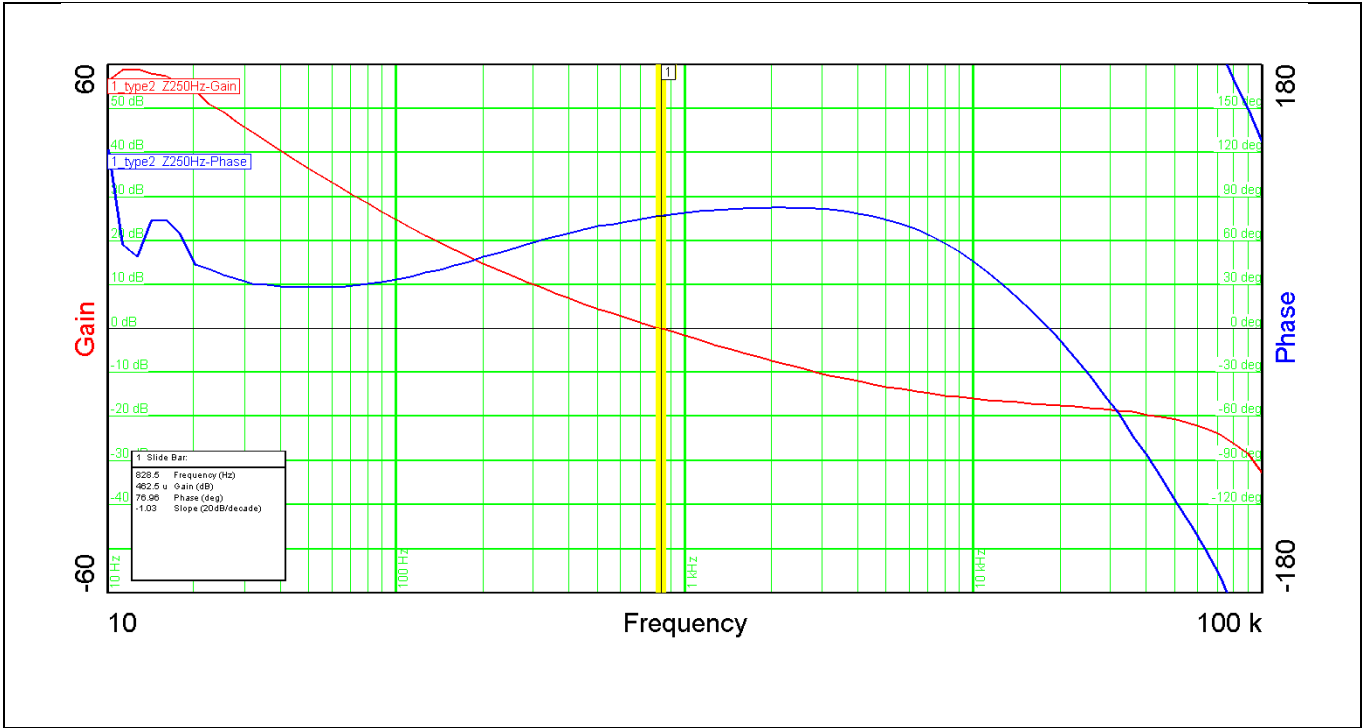


Figure 21

Table 7 summarizes the results from Figure 21

<b>Bandwidth (Hz)</b>	828
<b>Phasemargin</b>	77°
<b>slope (20dB/decade)</b>	-1
<b>gain margin (dB)</b>	-17.3
<b>slope (20dB/decade)</b>	-0.25
<b>Freq (kHz)</b>	18.4

Table 7

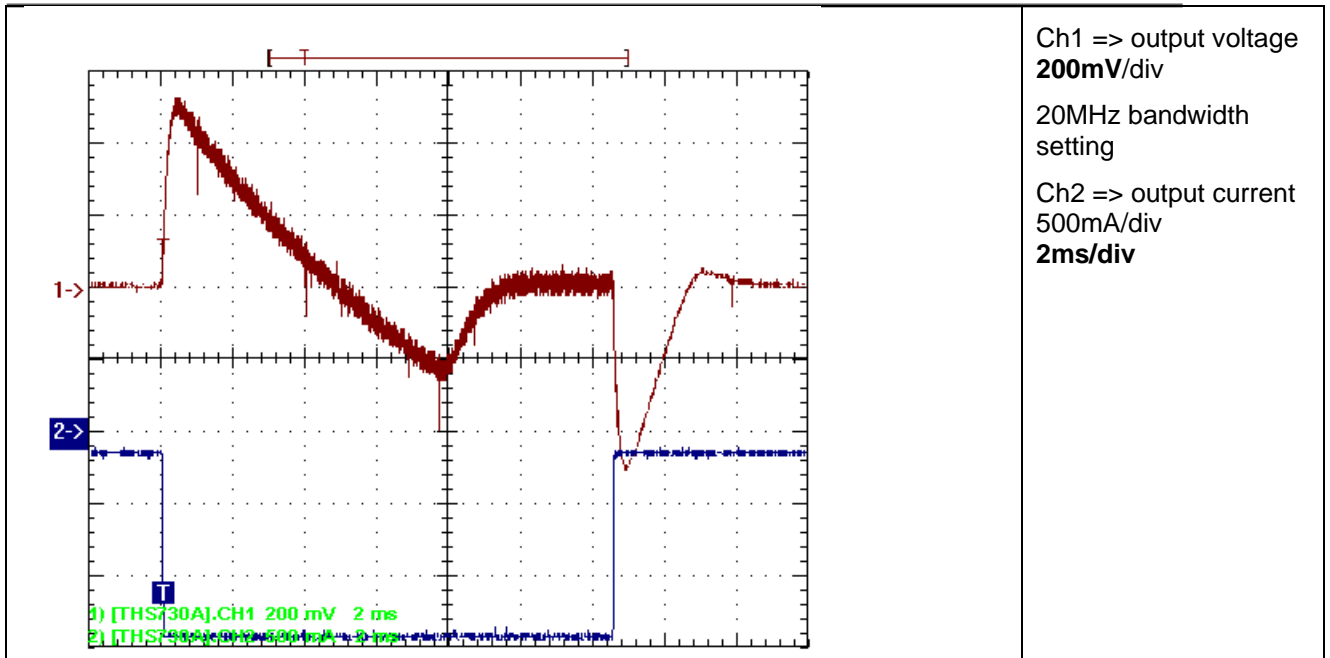


Figure 22

R14 80.6k, C17 10nF, C18 100pF

Tried to improve the DC gain further by increasing the ZERO from 25Hz to 250Hz;  
Though bandwidth is well below 1kHz AOL of the error amplifier is hurt, too much gain.  
The amplifier is clipping, see transient response, curve 1, above !  
Furthermore the phase drops to 30 degs around 50Hz.

Next step: reducing the ZERO from 250Hz to 75Hz, adjusting the gain.

10.4 Type 2 Compensation Z75Hz P25kHz bw 1kHz

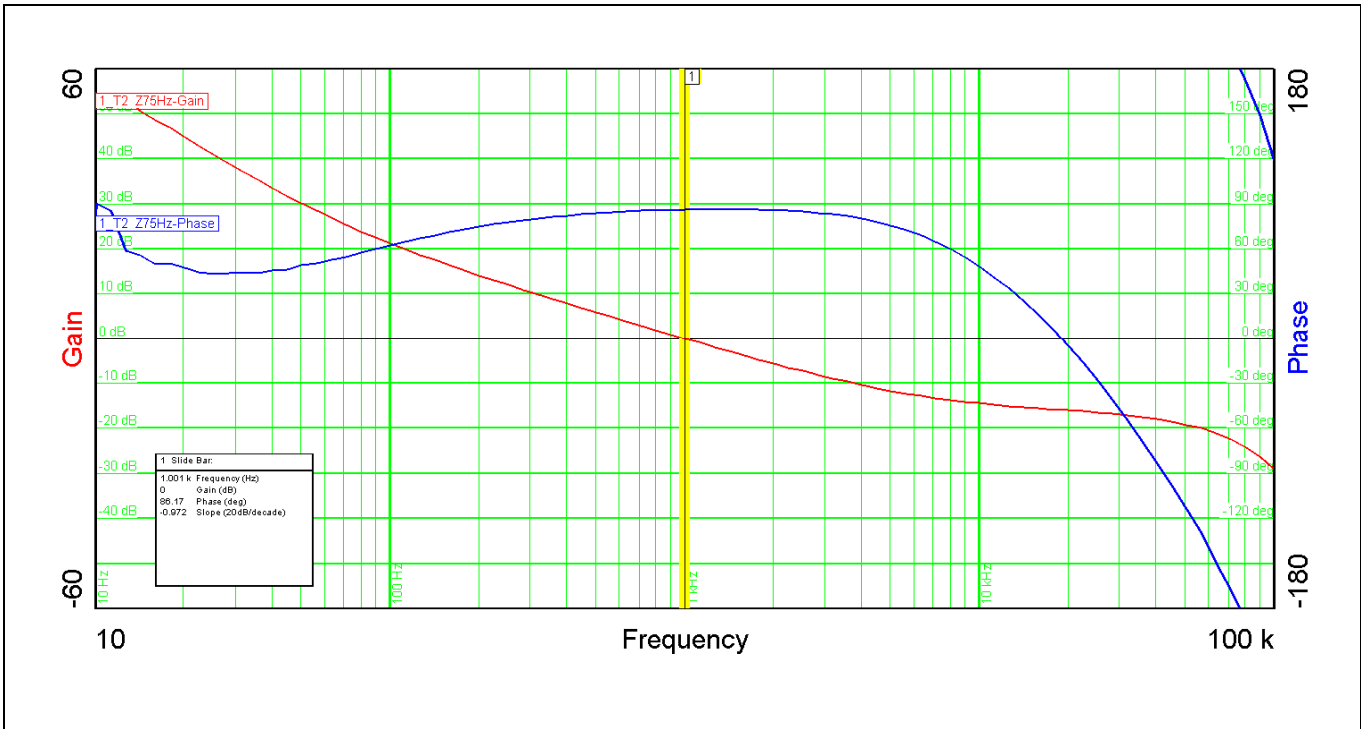


Figure 23

Table 8 summarizes the results from Figure 23

<b>Bandwidth (kHz)</b>	1
<b>Phasemargin</b>	86°
<b>slope (20dB/decade)</b>	-0.97
<b>gain margin (dB)</b>	-15.9
<b>slope (20dB/decade)</b>	-0.174
<b>Freq (kHz)</b>	19

Table 8

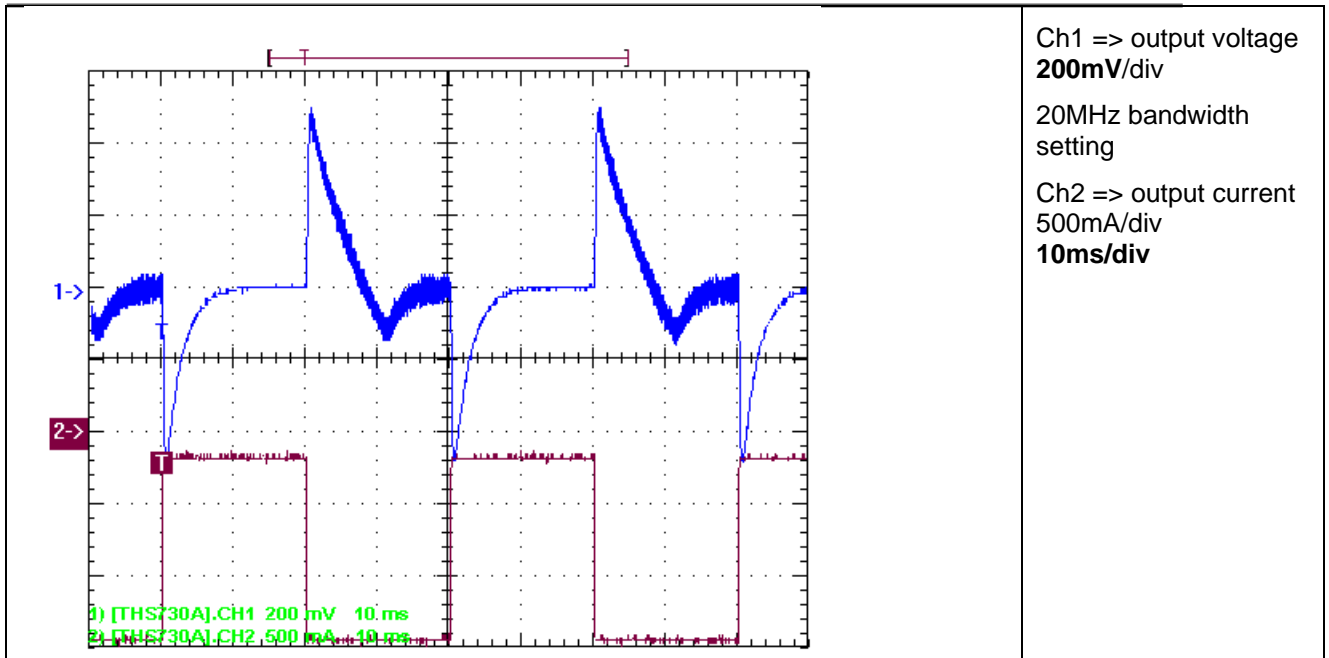


Figure 24

R14 100k, C17 33nF, C18 100pF

Reduced the Zero from 250Hz to 75Hz, set bandwidth to 1kHz – amplifier still clipping !  
 Reduced the gain a bit, this resulted in the final solution, this best trade off on page 7/8.  
 Gain was adjusted to prevent amplifier from clipping. The final solution works then w/ reasonable S/N, so no gate jitter. A derivation of 600mV for 90% transient could be achieved, less than half of the type 3 solution. This means 1.7% of the output voltage, the output capacitors could be reduced further to stay still w/in the limits of 3%.

Working properly on the compensation shows that a Cuk is achieving reasonable transient response, final solution page 7/8: **R14 71.5k, C17 33nF, C18 100pF**

## 11 Inductor Appendix

The circuit of the Cuk-Converter was built up on a PCB from an older Layout (PMP8619 Rev A) for having more board space to use bigger core shapes. Overall system efficiency was tested by using three different coupled inductors (windings ratio 1:1), whose specifications are listed below:

- Coilcraft L = 220  $\mu$ H, Rdc = 230 mOhm, **smallest geometry (red trace)**
- Hand wired, Würth PQ 2016 Core, bifilar wired, 33 windings, d = 0.4 mm, L = 229  $\mu$ H, Rdc = 208 mOhm, **medium geometry (blue trace)**
- Hand wired Würth, PQ 2620 Core, bifilar wired, 19 windings, d = 0.8 mm, L = 150  $\mu$ H, Rdc = 40 mOhm, **largest geometry (yellow trace)**

Result of the efficiency measurement with different load currents between 0.1 A and 1.5 A is that the DC resistance of the inductor has the major impact on the CUK's system efficiency, which is displayed in the graphic below.

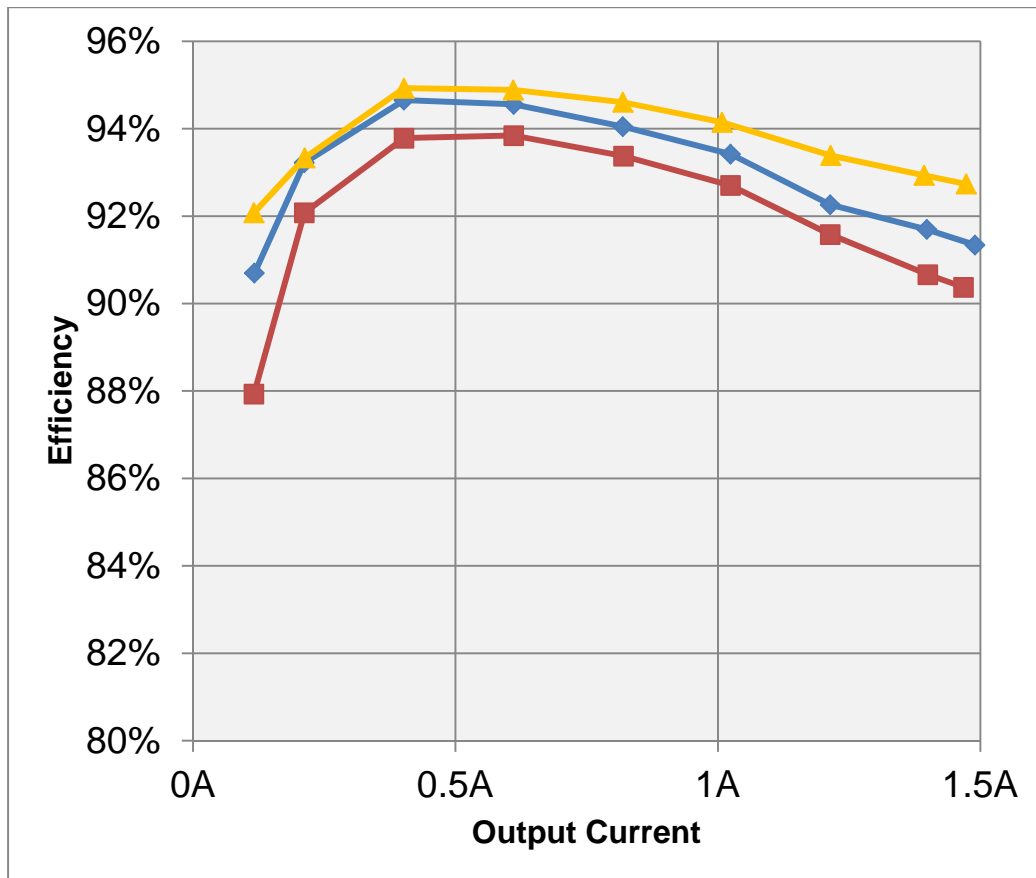


Figure 25: Diagram of the measurement data displayed on page 2  
 = efficiency increases with lower DC resistance of the inductors

**Coilcraft (220 $\mu$ H, R=230mOhm)**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>out</sub> (A)	P <sub>IN</sub> (W)	P <sub>OUT</sub> (W)	Eff	P <sub>Loss</sub> (W)
36,17	0,134	36,74	0,116	4,84678	4,26184	0,879314	0,58494
36,16	0,234	36,75	0,212	8,46144	7,791	0,920765	0,67044
36,13	0,436	36,75	0,402	15,75268	14,7735	0,93784	0,97918
36,09	0,663	36,75	0,611	23,92767	22,45425	<b>0,938422pk</b>	1,47342
36,05	0,895	36,74	0,82	32,26475	30,1268	0,933737	2,13795
36,01	1,127	36,74	1,024	40,58327	37,62176	0,927026	2,96151
35,97	1,354	36,74	1,214	48,70338	44,60236	0,915796	4,10102
35,94	1,579	36,75	1,4	56,74926	51,45	0,90662	5,29926
35,93	1,661	36,74	1,468	59,67973	53,93432	<b>0,903729</b>	5,74541

**handwired PQ 2016, (210 $\mu$ H, R=200mOhm, d=0,4mm, 33 windings)**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>out</sub> (A)	P <sub>IN</sub> (W)	P <sub>OUT</sub> (W)	Eff	P <sub>Loss</sub> (W)
36,16	0,131	36,72	0,117	4,73696	4,29624	0,906961	0,44072
36,15	0,231	36,72	0,212	8,35065	7,78464	0,93222	0,56601
36,11	0,432	36,73	0,402	15,59952	14,76546	<b>0,946533pk</b>	0,83406
36,07	0,658	36,73	0,611	23,73406	22,44203	0,945562	1,29203
36,02	0,888	36,73	0,819	31,98576	30,08187	0,940477	1,90389
35,98	1,119	36,73	1,024	40,26162	37,61152	0,934178	2,6501
35,96	1,344	36,73	1,214	48,33024	44,59022	0,922615	3,74002
35,92	1,559	36,73	1,398	55,99928	51,34854	0,91695	4,65074
35,9	1,669	36,73	1,49	59,9171	54,7277	<b>0,91339</b>	5,1894

**handwired PQ 2620(150 $\mu$ H, R=40mOhm, d=0,8mm, 19 windings)**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>out</sub> (A)	P <sub>IN</sub> (W)	P <sub>OUT</sub> (W)	Eff	P <sub>Loss</sub> (W)
36,17	0,128	36,75	0,116	4,62976	4,263	0,920782	0,36676
36,15	0,232	36,75	0,213	8,3868	7,82775	0,933342	0,55905
36,11	0,431	36,75	0,402	15,56341	14,7735	<b>0,949246pk</b>	0,78991
36,07	0,655	36,75	0,61	23,62585	22,4175	0,948855	1,20835
36,03	0,883	36,75	0,819	31,81449	30,09825	0,946055	1,71624
35,99	1,093	36,74	1,008	39,33707	37,03392	0,941451	2,30315
35,95	1,33	36,75	1,215	47,8135	44,65125	0,933863	3,16225
35,91	1,534	36,75	1,393	55,08594	51,19275	0,929325	3,89319
35,9	1,626	36,75	1,473	58,3734	54,13275	<b>0,927353</b>	4,24065



The system output voltage ripple is dependent on the load current. It increases with big and decreases with small loads. Furthermore is the ripple bigger with a coil of smaller inductance. With a 1.5A load current the peak-to-peak ripple is approximately 250 mV. Considering that the output voltage is -36 V, this is less than 1% deviation. Pictures of the input and output voltage ripple are shown in the following figures:

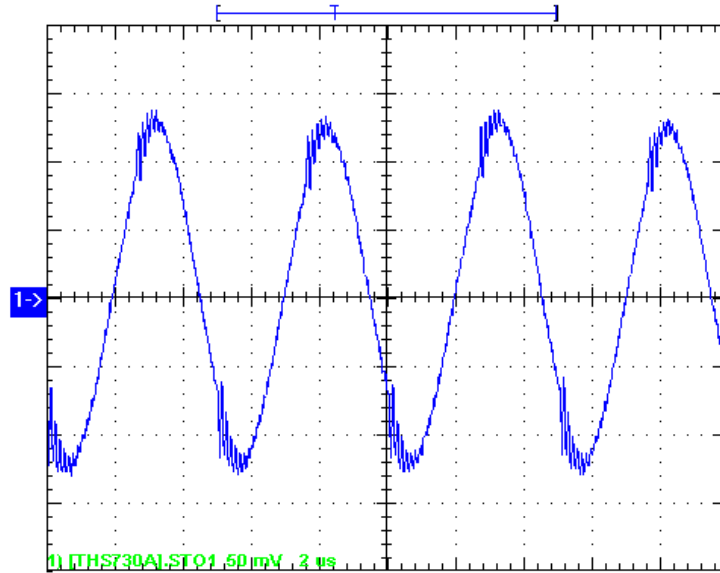


Figure 25: Output Voltage Ripple at 1.5A load current.

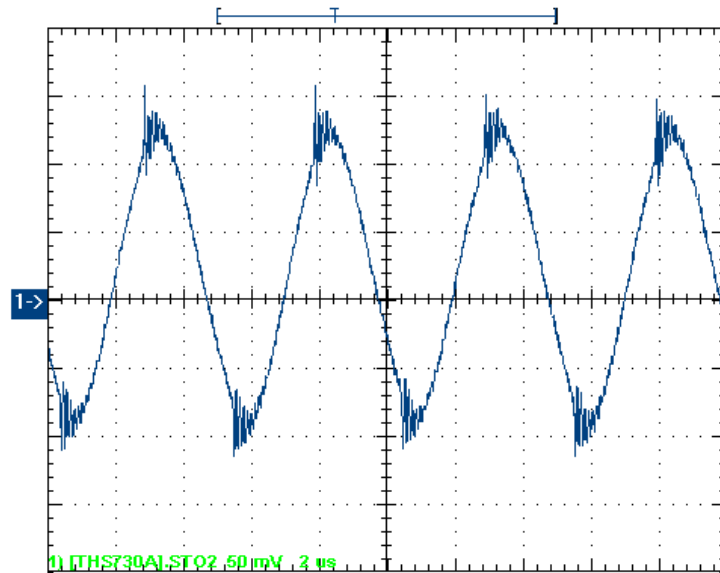


Figure 27: Input Voltage Ripple at 1.5A load current.

The idea of using a transformer with equal DC resistance, but with bigger leakage inductance to reduce the current ripple over the coil and AC capacitor path, did not deliver the desired result of higher system efficiency. The efficiency was even lower than with a good coupled bifilar wired inductor of similar inductance and DC resistance.

***In conclusion for this CUK converter the inductor's DC resistance is responsible for the main part of the power dissipation of the transformer.***

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

TI's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

TI's standard terms of sale for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2016, Texas Instruments Incorporated