

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Originator: H. Meier
--	---	--------------------------------



LF-LF Demonstration System Calculations

With Ferrite Base Station Antenna

(Edit Date 02/16/12, LF-LF_Ferrite-Ferrite_Calc_1d.doc)

<p>PRINTED COPIES OF THIS SPECIFICATION ARE NOT CONTROLLED DOCUMENTS. VERIFY THEIR CORRECT REVISION BEFORE USING.</p>
--

Revision:	01	
LF-LF Demo System Calculation	Page 1 of 24	24-01-02-009

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

Table of Contents	Page
1 Purpose	4
2 Scope	4
3 References	4
4 Responsibilities	4
4.1 Base Station Calculations	5
4.1.1 Base Station Parameters	5
4.1.2 Determination of Receive Quality Factor	5
4.1.3 Determination of Antenna Current	9
4.1.4 Field Strength Calculation	10
4.2 Transponder Parameter	14
4.2.1 Transponder Receive Antenna	14
4.2.1.1 Receive Antenna Parameter	14
4.2.1.2 Antenna Open Circuit Voltage Based on Antenna Parameters	15
4.2.1.3 Empirical Factor for Voltage Calculation (Fv)	15
4.2.1.4 Empirical Factor for Inductance Calculation (FI)	16
4.2.1.5 Calculation of Windings	16
4.2.1.6 Inductance Control Calculation	16
4.2.1.7 Open Circuit Voltage Based on Coil Parameters	16
4.2.1.8 Open Circuit Voltage Based on Coil Sensitivity Specification	16
4.2.1.9 Coupling between Base Station and Receive Transponder Antenna	17
4.2.1.10 RF Input Peak-to-Peak Voltage	18
4.2.1.11 Conclusions	18
4.2.1.12 Calculation of Charge Voltage for Batteryless Functionality	19
4.2.1.13 Conclusions	21
4.2.2 Transponder Transmit Antenna	22
4.2.2.1 Parameter of Transponder Transmit Antenna	22
4.2.2.2 Calculation of Windings	22
4.2.2.3 Effective Antenna Radius	23
4.2.2.4 Peak Antenna Current	23
4.2.2.5 Response Coupling Factor	23
4.2.2.6 Receiver Input Voltage	24
4.2.2.7 Conclusions	24
5 Revision History	24

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

Summary of Figures

Page

Figure 1: Determination of Receive Quality Factor	6
Figure 2: Determination of Rod Permeability	11
Figure 3: Empirical Factors Fv (or Fvant) and Fl as function of lc/lr.....	12
Figure 4: Calculated Base Station Field Strength over distance.....	13
Figure 5: Coupling Factor vs. Distance	17
Figure 6: Calculation Model for Charge Voltage	19
Figure 7: Final Limited Charge Voltage Over Distance	20
Figure 8: Limited Charge Voltage After 50ms Over Distance	21

Summary of Tables

Page

Table 1: Parameters of Base Station RI-ACC-ADR2 with 10 cm Ferrite Coil	5
Table 2: Typical Parameter of 4.7mH NEOSID 3D Transponder Antenna	14
Table 3: Parameters for VCL Calculations	20
Table 4: Typical Parameter of Transponder Transmit Antenna	22

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

1 Purpose

This document describes the calculations for the **LF-LF Demonstration System**, consisting of:

- **RI-ACC-ADR2** Reader (Base Station) including the TMS3705A [1] and the UCC27424 driver [2]
- **10cm ferrite coil antenna** of the 12cm Transponder (50017-A-00)
- LF-LF Dual Antenna Demonstration Board with **TMS37F128** [3]
- **NEOSID 3 x 4.7mH** Transponder receive antenna
- **NEOSID 3 x 2.47mH** Transponder transmit antenna

2 Scope

This information contains TI Internal Data classified information and is intended for the development team and its management on a strict need-to-know base only. Prior to distribution of classified information as contained in this specification to other parts of the organization or under NDA to external persons or companies, approval of the Engineering Manager is required.

3 References

[1] TMS3705A Transponder Base Station IC Rev. 1.1(01/03)

[2] MOSFET Driver Data Sheet UCC27424D

[3] CRAID – TMS37F128 Reference Guide, 11-07-21-003

4 Responsibilities

The Engineering Manager or his designee is responsible to maintain this document.

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.1 Base Station Calculations

4.1.1 Base Station Parameters

The Base Station (RI-ACC-ADR2) using the ASIC TMS3705A [1], is typically equipped with a small 440μH air coil antenna, must be changed to either a bigger 2.5mH air coil or ferrite antenna, to achieve a one meter communication distance. In the calculation example a 10cm ferrite coil antenna (50017-A-00) is used, with the following typical parameters (see Table 1):

PARAMETER	ABBREVIATION	VALUE	UNIT
Length of Antenna Rod	l _{rant}	0.1	m
Radius of Antenna Rod	r _{rant}	0.0039	m
Length of Coil	l _{cant}	0.015	m
Inductance	L _{tx}	2.54	mH
Turns	N _{tx}	163	
Nominal Receive Resonance Frequency	f ₀	127.25	kHz
Antenna Quality Factor	Q _{ant}	194	
Receiver input Resistance	R _{in}	47	kOhm
Supply Voltage (due to serial diode)	U _{sup}	12 (11.3)	V
Full Bridge Drain Source Receive Resistance [2]	R _{dson}	2 x 2.6= 5.2	Ohm
Full Bridge Drain Source Transmit Resistance [2]	R _{dsonTX}	18+ 2.6= 20.6	Ohm
Filter resistors	R _s	2 x 4.7= 9.4	Ohm

Table 1: Parameters of Base Station RI-ACC-ADR2 with 10 cm Ferrite Coil

4.1.2 Determination of Receive Quality Factor

The minimum required bandwidth to receive the two FSK-frequencies is,

$$f_L - f_H = 133.3 - 121.2 = 12.1 \text{ kHz}$$

And the nominal receive resonance frequency is,

$$f_0 = \frac{(f_L + f_H)}{2} = 127.25 \text{ kHz}$$

The receive Quality factor should, therefore, be,

$$Q_{RX} = \frac{f_0}{fbw} = \frac{127.25k}{12.1k} = 10.5$$

The desired Receive Resistance is, therefore,

$$R_{RX} = \frac{2 \cdot \pi \cdot f_0 \cdot L_{tx}}{Q_{RX}} = \frac{2 \cdot \pi \cdot 127250 \cdot 0.00254}{10.5} = 193\Omega$$

The Receive Resistance, R_{RX} , is the sum of internal and external resistances such as:

- Driver Stage On-resistance ($R_{dson} = R_{onN1} + R_{onN2}$)
- Filter Resistors ($R_s = R_{s1} + R_{s2}$)
- Antenna Resistance (R_{ant})
- Antenna Damping Resistor (R_{dmp})
- Receiver Input Resistance (R_{in})

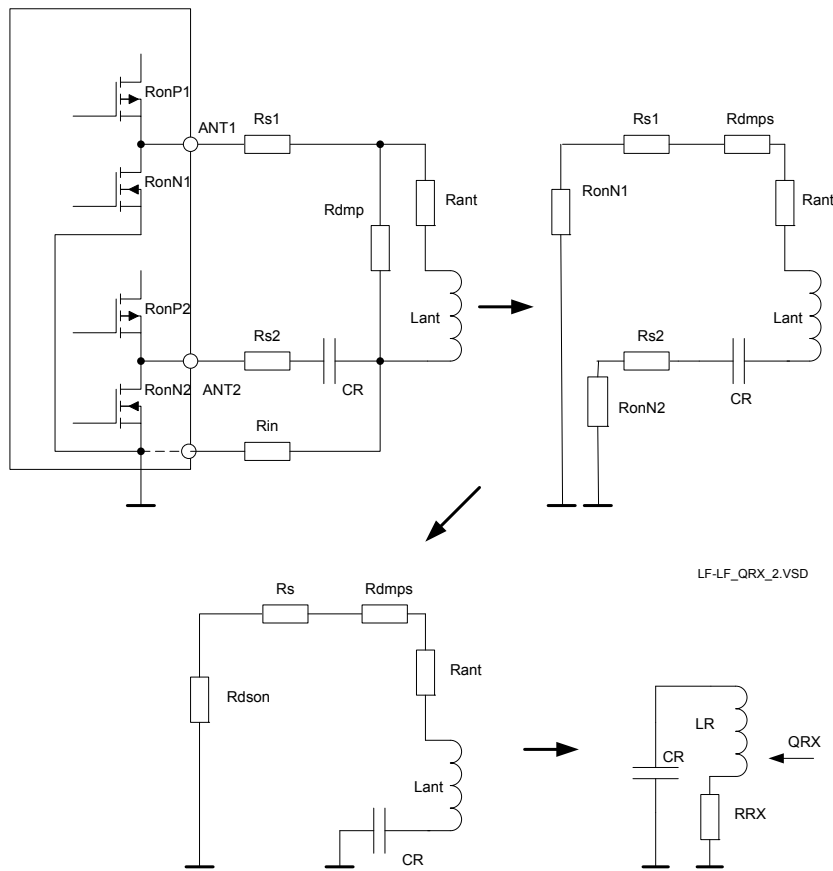


Figure 1: Determination of Receive Quality Factor

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

The antenna resistance (R_{ant}) is calculated for given antenna quality factor (Q_{ant}) and antenna inductance (L_{ant}):

$$R_{ant} = \frac{2 \cdot \pi \cdot f_0 \cdot L_{ant}}{Q_{ant}} = \frac{2030.8}{194} = 10.5\Omega$$

The required total series damping resistor is, therefore,

$$R_{dmps} = R_{RX} - R_{dson} - R_s - R_{ant} = 193 - 5.2 - 9.4 - 10.5 = 167.9\Omega$$

The maximum equivalent total parallel resistance to the antenna (R_p) is,

$$R_p = \frac{(2 \cdot \pi \cdot f_0 \cdot L_{ant})^2}{R_{dmps}} = 24.5k\Omega$$

And the resulting damping resistor is,

$$R_{dmp} = \frac{1}{\left(\frac{1}{R_p} - \frac{1}{R_{in}}\right)} = \frac{1}{\left(\frac{1}{24.5k} - \frac{1}{47k}\right)} = 51.4k\Omega$$

The next lower value is selected:

$$R_{dmp} = 47k\Omega \quad (\text{The physical resistor in parallel with the coil})$$

We now need to solve the above equations in reverse to obtain the actual receive quality factor, Q_{RX} .

The actual parallel resistance is, therefore,

$$R_p = \frac{1}{\left(\frac{1}{R_{dmp}} + \frac{1}{R_{in}}\right)} = \frac{1}{\left(\frac{1}{47k} + \frac{1}{47k}\right)} = 23.5k\Omega$$

$$R_{dmps} = \frac{(2 \cdot \pi \cdot f_0 \cdot L_{ant})^2}{R_p} = 175.5\Omega$$

The total receive resistance (R_{RX}) is, therefore,

$$R_{RX} = R_{dson} + R_s + R_{dmps} + R_{ant} = 5.2 + 9.4 + 175.5 + 10.5 = 200.6\Omega$$

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

And the actual receive quality factor is,

$$QRX = \frac{2 \cdot \pi \cdot f_0 \cdot L_{ant}}{RRX} = 10.1$$

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.1.3 Determination of Antenna Current

Due to the characteristics of UCC driver, the transmit quality factor (QTX) is slightly lower than the receive quality factor (QRX). The full-bridge drain-source resistance (RdsonTX) includes the P-channel and N-channel Rdson and the influence of the bipolar transistors, parallel to the MOSFET drivers; therefore, the transmit resistance is,

$$RTX = RdsonTX + Rs + Rdmps + Rant = 216\Omega$$

The maximum theoretical antenna peak current is the quotient of supply voltage and RTX,

$$Itx[p] = \frac{Vsup}{RTX} \cdot \frac{4}{\pi} = 70.8mA$$

Remark: The serial diode in the supply path must in this case be short circuit or compensated by higher input voltage.

The maximum theoretical peak-to-peak antenna voltage, Utxmax[Vpp], at resonance is,

$$Utxmax[Vpp] = Itx[p] \cdot 2 \cdot \sqrt{(Rant^2 + (2 \cdot \pi \cdot f0 \cdot Lant)^2)} = 287.4V$$

As the TMS3705A driver has a duty cycle of 80 / 20%, a factor of 0.8 must be taken into account for calculation of the peak-to-peak antenna voltage (Utx) and RMS antenna current (Itx),

$$Utx[Vpp] = Utxmax \cdot 0.8 = 229.9V$$

Because the transmit frequency is 134.45 kHz, the amplitude is typically damped by approximately 3dB due to the resonant circuit bandwidth. Including the serial diode, the real maximum antenna voltage of the demonstration system will be less than 200Vpp (~160V).

Important Note: Nevertheless, the resonance capacitor must still have a rated voltage of at least 250V!

The maximum theoretical RMS antenna current, required for the field strength calculation is,

$$Itx = \frac{Itx[p]}{\sqrt{2}} \cdot 0.8 = 40mA$$

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.1.4 Field Strength Calculation

The transmit antenna rod permeability (μ_{rodant}) can be determined using the chart shown in Figure 2, after calculation of the length-of-rod (l_{rant}) to rod diameter ($2 \times r_{rant}$) ratio:

$$l_{rant} / (2 \times r_{rant}) = \frac{0.1}{2 \cdot 0.0039} = 12.82$$

If the rod permeability is above $\mu = 2000$, then the following formula can be used:

$$\mu_{rodant} = 10^{(\log(l_{rant} / 2 \cdot r_{rant}) \cdot 1.371926 + 0.441693)} = 91.5$$

In Figure 2 below, the vertical axis is the effective rod permeability, μ_{rodant} (μ_{rod} in the graph). The family of curves represents different material permeabilities, μ .

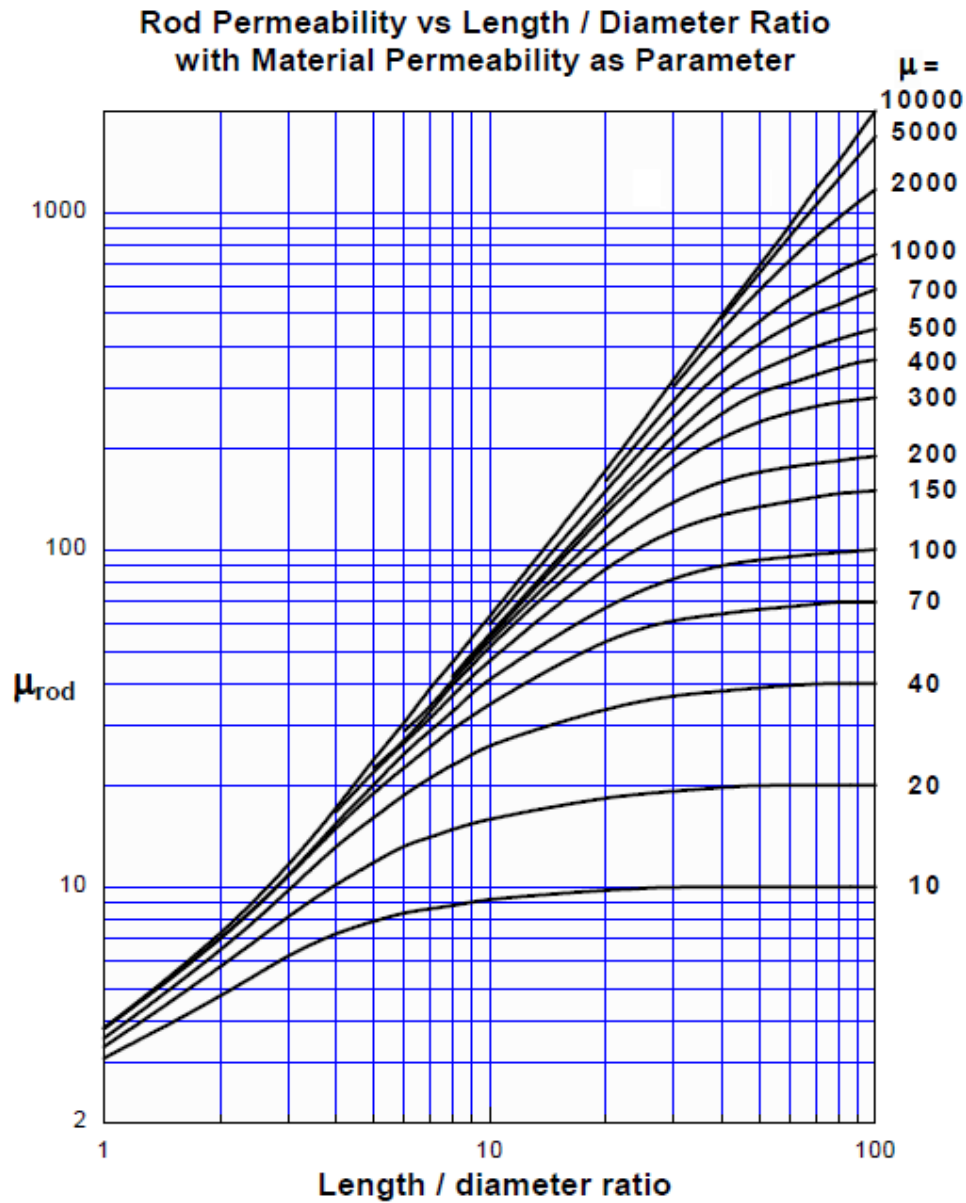


Figure 2: Determination of Rod Permeability

The empirical factor (F_{vant}) can be determined using Figure 3 after calculation of the length-of-coil (l_{cant}) to length-of-rod (l_{rant}) ratio:

$$\frac{l_{cant}}{l_{rant}} = 0.15$$

$$F_{vant} = 0.994$$

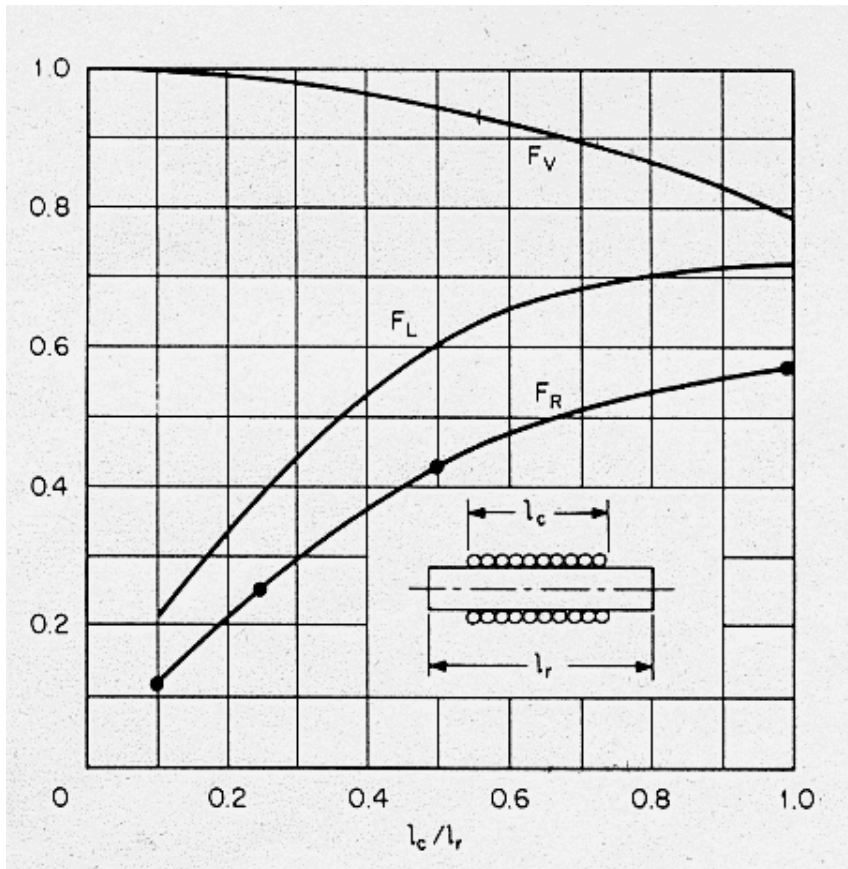


Figure 3: Empirical Factors F_v (or F_{vant}) and F_l as function of l_c/l_r

The effective antenna radius (r_{tx}) depends on the radius of the antenna rod (r_{rant}), the rod permeability (μ_{rodant}) and an empirical factor (F_{vant}):

$$r_{tx} = r_{rant} \cdot \sqrt{\mu_{rodant} \cdot F_{vant}} = 0.0372m$$

The field strength, H, generated by the Base Station at distance, d, in case of a certain antenna current, Itx, is then calculated to be,

$$H[d] = \frac{N_{tx} \cdot r_{tx}^2 \cdot I_{tx}}{2 \cdot (d^2 + r_{tx}^2)^{1.5}}, [A/m]$$

Where Ntx = 163 is the number of turns of the antenna coil from Table 1.

$$H[dB\mu V / m] = 20 \cdot \log(H[A / m] \cdot 10^6) + 51.5$$

And 51.5 is the conversion factor from amps to volts in an air medium ($Z_{air} = 377\Omega$)

In Figure 4 the typical calculated field strength over distance, H[d], is shown.

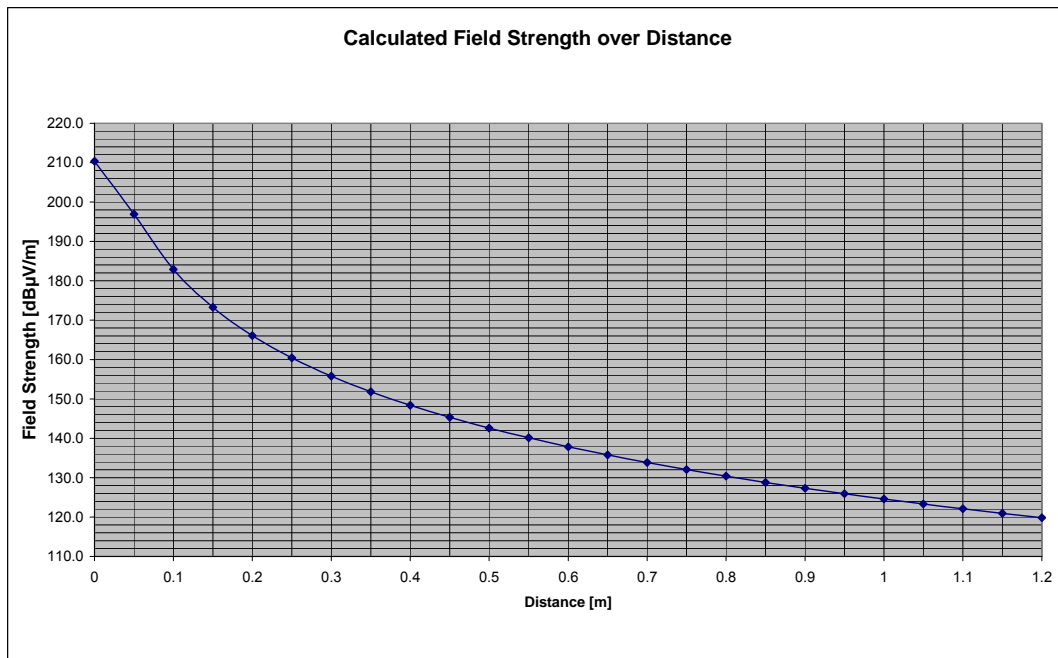


Figure 4: Calculated Base Station Field Strength over distance

4.2 Transponder Parameter

4.2.1 Transponder Receive Antenna

The Transponder receive antenna of the demonstration system is a three-dimensional block shape antenna from NEOSID. Because the inductance of all three coils is equal, the Z-axis typically has higher sensitivity; therefore, the X-axis is calculated here as an example.

4.2.1.1 Receive Antenna Parameter

The X-axis has the following typical parameters, which are known from the antenna data sheet, measured at device, or calculated out of known parameters (see Table 2):

X-AXIS PARAMETER	ABBREVIATION	VALUE	UNIT
Inductance	L _{trp}	4.7	mH
Typical Transp. Quality Factor	Q _{trp}	20	
Coil Sensitivity Specification	S	0.12	V/A/m
Magnetic Field Constant	μ_0	$1.25664 \cdot 10^{-6}$	Vs/Am
Material Permeability (assumed)	μ	2000	
Length of Rod (measured)	l _r	0.0154	m
Width of Rod (measured)	a _r	0.0145	m
Thickness of Rod (measured)	b _r	0.0031	m
Effective Radius of Rod (calculated)	r _r	0.003783	m
Length to Diameter Ratio (calculated)	l _r /2r _r	2.0356	
Rod Permeability (calculated)	μ_{rod}	7.3	
Length of coil to length of rod (calculated)	l _c /l _r	0.45	
Empirical Factor (F _v =f(l _c /l _r))	F _v	0.95	
Empirical Factor (F _l =f(l _c /l _r))	F _l	0.56	
Area of Loop (calculated)	A _{trp}	$4.495 \cdot 10^{-5}$	m ²
Turns (calculated)	N _{trp}	377	

Table 2: Typical Parameter of 4.7mH NEOSID 3D Transponder Antenna

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

As the formulas are for a cylindrical coil, an effective coil radius (rr) and effective coil area (Atrp) are calculated from the rectangular dimensions,

$$rr = \sqrt{\frac{ar \cdot br}{\pi}} = \sqrt{\frac{0.0145 \cdot 0.0031}{\pi}} = 0.003783m$$

$$Atrp = rr^2 \cdot \pi = 4.495 \cdot 10^{-5} m^2$$

4.2.1.2 Antenna Open Circuit Voltage Based on Antenna Parameters

If the antenna is exposed to a certain field strength (B), the sole, unloaded antenna will show an open circuit voltage (Utrp), which depends on,

- Magnetic field constant (μ_0)
- Rod permeability (μ_{rod}),
- Effective coil area (Atrp)
- Number of windings (Ntrp)
- Empirical factor (Fv)

$$Utrp = 2 \cdot \pi \cdot f_0 \cdot \mu_0 \cdot \mu_{rod} \cdot Fv \cdot Ntrp \cdot Atrp \cdot B$$

For rod permeability (μ_{rod}), the length-of-rod (lr) to rod diameter (2rr) ratio is required (see Figure 2):

$$lr / 2rr = \frac{0.0154}{2 \cdot 0.00378} = 2.0356$$

$$\mu_{rod} = 10^{(\log(\frac{lr}{2rr}) \cdot 1.371926 + 0.441693)} = 7.3$$

4.2.1.3 Empirical Factor for Voltage Calculation (Fv)

The empirical factor (Fv) depends on the ratio of length-of-coil (lc) to length-of-rod (lr) and can be determined using Figure 3,

$$\frac{lc}{lr} = 0.45$$

$$Fv = 0.95$$

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.2.1.4 Empirical Factor for Inductance Calculation (Fl)

The empirical factor (Fl) depends on the ratio of length-of-coil (lc) to length-of-rod (lr) and can be determined using Figure 3.

$$\frac{lc}{lr} = 0.45$$

$$Fl = 0.56$$

4.2.1.5 Calculation of Windings

Because the number of windings (Ntrp) is not given for the NEOSID antenna, it must be determined from known and measured parameters,

$$Ntrp = \sqrt{\frac{Ltrp \cdot lc}{\mu_0 \cdot \mu_{rod} \cdot Atrp \cdot Fl}} = 377$$

4.2.1.6 Inductance Control Calculation

To check if the calculated number of windings is valid, the following formula for inductance can be used,

$$Ltrp = \frac{\mu_0 \cdot \mu_{rod} \cdot Fl \cdot Atrp \cdot Ntrp^2}{lc} = 4.7089mH$$

4.2.1.7 Open Circuit Voltage Based on Coil Parameters

At a distance of 1.1m the calculation showed a field strength of B = 0.00339A/m. The calculation of open circuit voltage results in Utrp = 40.2mV.

4.2.1.8 Open Circuit Voltage Based on Coil Sensitivity Specification

In order to check the calculation result based on antenna parameters, the sensitivity (S = 0.12 V/A/m) specification of the NEOSID antenna can be used as follows,

$$Utrp = S \cdot B = 40.6mV$$

4.2.1.9 Coupling between Base Station and Receive Transponder Antenna

The coupling factor (K) over distance (d) between the Base Station and the receive Transponder antenna is calculated by the following formula:

$$K = \frac{\mu_0 \cdot (\mu_{rod} \cdot F_v \cdot A_{trp} \cdot N_{trp}) \cdot (r_{tx}^2 \cdot N_{tx})}{2 \cdot (d^2 + r_{tx}^2)^{1.5} \cdot \sqrt{L_{tx} \cdot L_{trp}}}$$

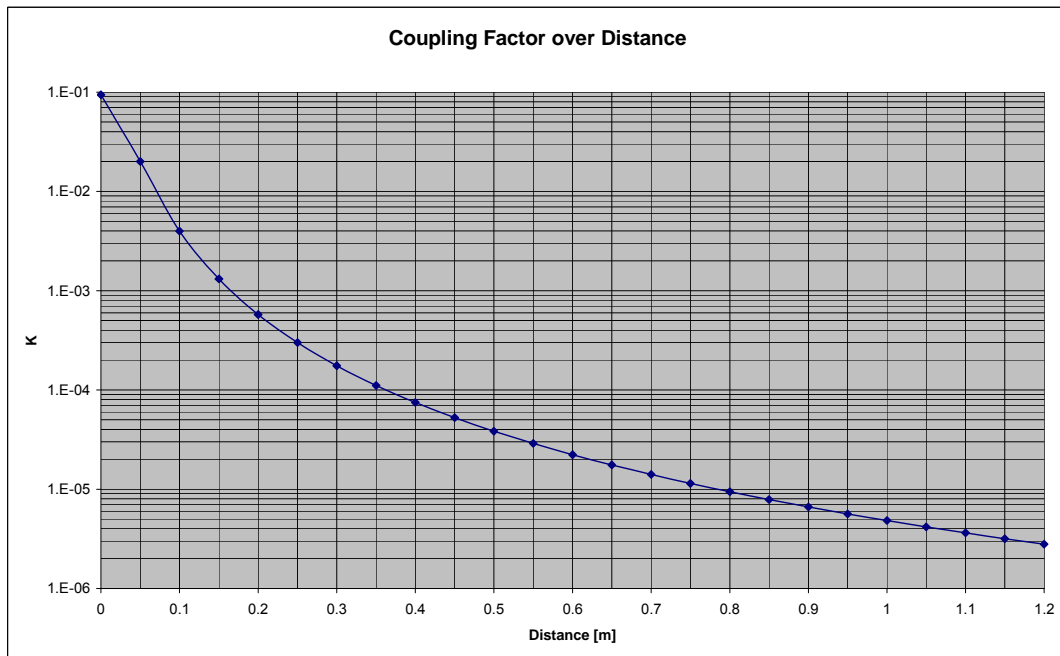


Figure 5: Coupling Factor vs. Distance

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.2.1.10 RF Input Peak-to-Peak Voltage

The effective equivalent voltage source (U_{eff}) of the system arrangement is calculated by,

$$U_{eff} = 2 \cdot \pi \cdot f_0 \cdot Q_{trp} \cdot I \cdot K \cdot \sqrt{L_{trp} \cdot L_{ant}}$$

The effective equivalent voltage source in a distance of $d = 1.1\text{m}$ is $U_{eff} = 8\text{mV}$

The equivalent source resistance (R_{eq}) is calculated by,

$$R_{eq} = 2 \cdot \pi \cdot f_0 \cdot L_{trp} \cdot Q_{trp} = 75.16\text{k}\Omega$$

Together with the input resistance for small input voltages of the IC ($R_i = 1.2\text{M}\Omega$), the RF input peak-to-peak voltage (V_{RFpp}) at the identification device input can be calculated as,

$$V_{RFpp} = \frac{2 \cdot \sqrt{2} \cdot U_{eff} \cdot R_i}{(R_{eq} + R_i)} = 21.4\text{mV}_{pp}$$

4.2.1.11 Conclusions

At a distance of $d = 1.1\text{m}$ the calculation results in $V_{RFpp} = 21.4\text{mV}_{pp}$. Because the sensitivity of the Write Distance Expander (WDE) is a factor of 10 higher, the Wake Sensitivity should be reduced to avoid undesirable wakeup due to noise.

4.2.1.12 Calculation of Charge Voltage for Batteryless Functionality

In Figure 6, the equivalent circuit for determining the charge voltage (VCL) is given.

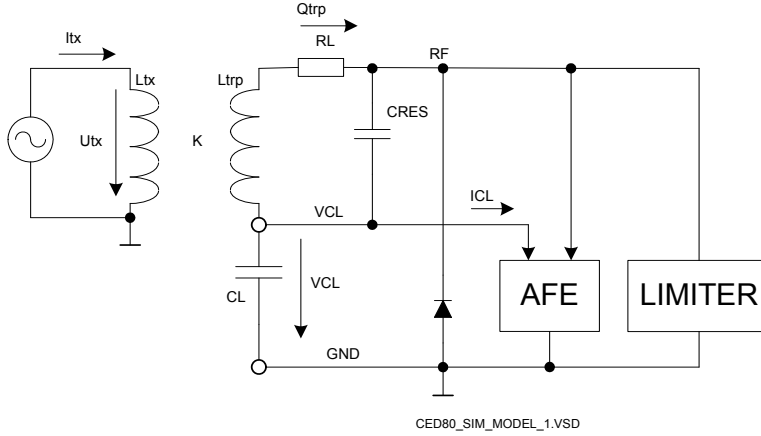


Figure 6: Calculation Model for Charge Voltage

The final charge voltage (VCL) can be calculated with the formula,

$$VCL = \left(I_{tx} \cdot K \cdot \sqrt{L_{tx} \cdot L_{trp}} - I_{CL} \cdot \sqrt{2} \cdot L_{trp} \right) \cdot 2 \cdot \pi \cdot f_{RES} \cdot Q_{trp} \cdot \sqrt{2} + \frac{I_{CL}}{I_{tx} \cdot K \cdot \sqrt{2}} \cdot \sqrt{\frac{L_{trp}}{L_{tx}}} - 0.5$$

,or with the equivalent parameter determined before:

$$VCL = U_{eff} \cdot \sqrt{2} - 2 \cdot R_{eq} \cdot I_{CL} \cdot \left(1 - \frac{1}{U_{eff} \cdot 2 \cdot \sqrt{2}} \right) - 0.5$$

Whereby it is assumed that,

$$f_{RES} = f_{TX} = 127.25 \text{ kHz}$$

Because the real transmit frequency is 134.45 kHz, VCL will be lower.

ICL is the average DC standby current of the IC during charging and Qtrp is the total Transponder quality factor, represented by RL in the calculation model,

$$Q_{trp} = \frac{2 \cdot \pi \cdot f_{RES} \cdot L_{trp}}{RL}$$

For the charts, the parameters shown in Table 3 are assumed.

PARAMETER	ABBREVIATION	VALUE	UNIT
Transponder Quality Factor	Qtrp	20	
Standby Current during Charge	ICL	4.3	μA
Charge Capacitor	CL	220	nF

Table 3: Parameters for VCL Calculations

In Figure 7 the final, limited charge voltage over distance is shown.

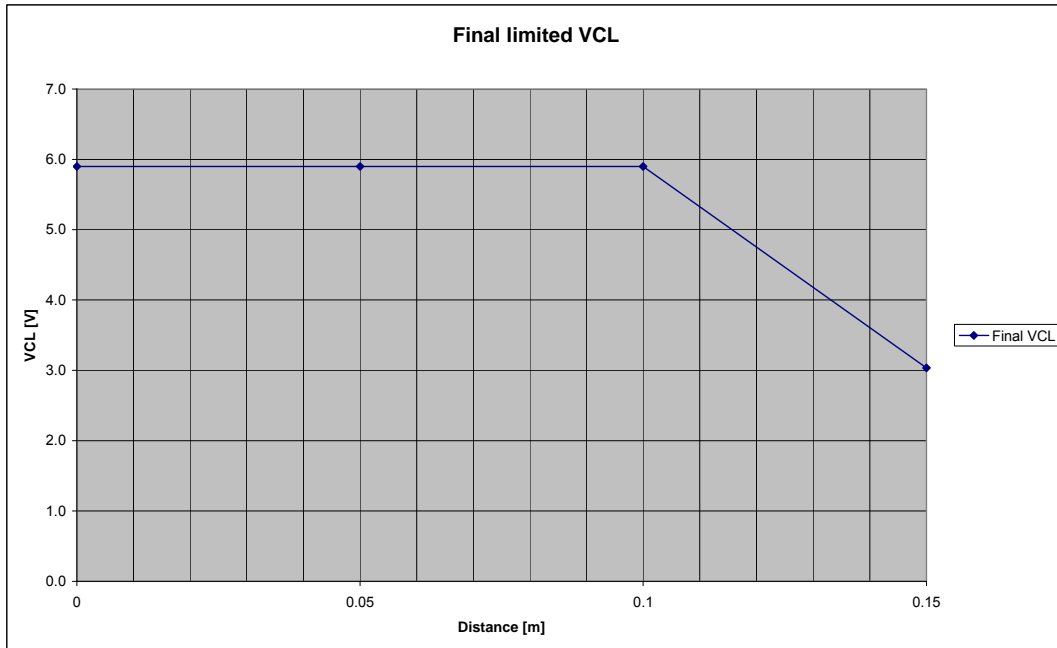


Figure 7: Final Limited Charge Voltage Over Distance

The charge voltage without limitation after 50ms can be calculated by,

$$VCL_{50} = VCL \cdot \left(1 - e^{\frac{-0.05}{4 \cdot \pi \cdot f_{RES} \cdot Q_{trp} \cdot L_{trp} \cdot CL}} \right)$$

In Figure 8, the limited charge voltage over distance for a 50ms charge burst is shown.

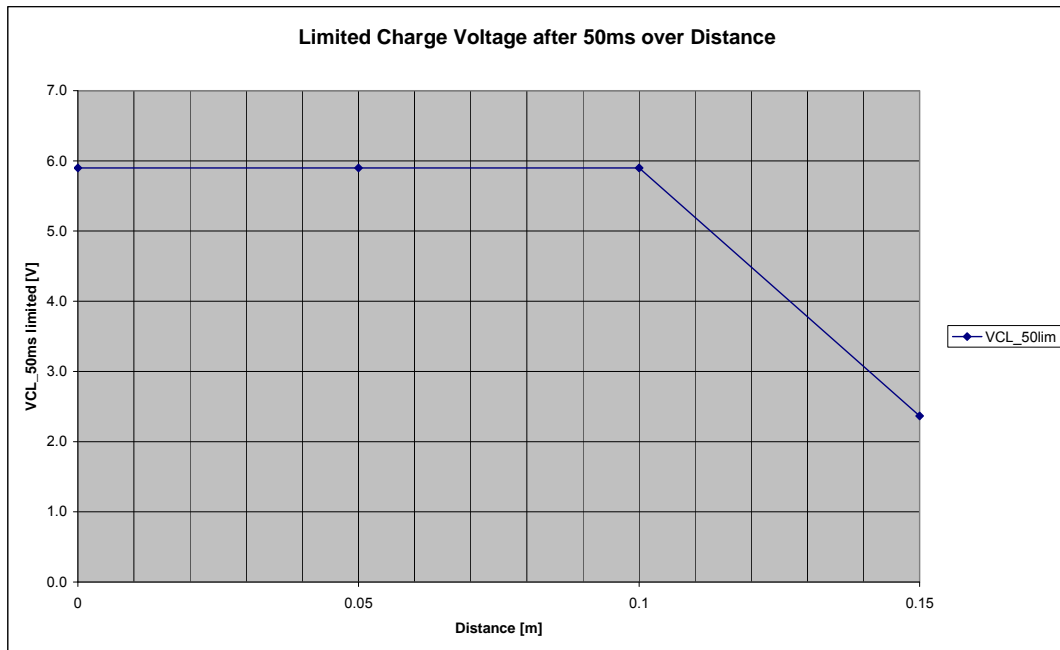


Figure 8: Limited Charge Voltage After 50ms Over Distance

4.2.1.13 Conclusions

The maximum passive (dead battery) communication distance will be about 13cm from the center, or 8 cm from the top, of the transmit antenna.

Important Note: Z- axis of transponder antenna must be in line with axis of transmit antenna. X- and Y- channel are not able to transmit in passive mode!

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.2.2 Transponder Transmit Antenna

The Transponder transmit antenna of the demonstration system is a three-dimensional block shape antenna from NEOSID. Because the inductance of all three coils is equal, the Z-axis typically has higher sensitivity; therefore, the X-axis is calculated here as an example.

4.2.2.1 Parameter of Transponder Transmit Antenna

The X-axis of Transponder Transmit Antenna has the following typical parameters, which are known from the antenna data sheet, from Table 2, or calculated out of known parameters (see Table 4):

X-AXIS PARAMETER	ABBREVIATION	VALUE	UNIT
Inductance	LtrpTX	2.47	mH
Typical Transp. Quality Factor	QtrpTX	30	
Coil Sensitivity Specification	Stx	0.062	V/A/m
Magnetic Field Constant	μ_0	$1.25664 \cdot 10^{-6}$	Vs/Am
Material Permeability (assumed)	μ	2000	
Length of Rod (Table 2)	lr	0.0154	m
Width of Rod (Table 2)	ar	0.0145	m
Thickness of Rod (Table 2)	br	0.0031	m
Effective Radius of Rod (Table 2)	rr	0.003783	m
Length to Diameter Ratio (Table 2)	lr/2rr	2.0356	
Rod Permeability (Table 2)	μ_{rod}	7.3	
Length of coil to length of rod (Table 2)	lc/lr	0.45	
Empirical Factor (Fv=f(lc/lr) (Table 2)	Fv	0.95	
Empirical Factor (Fl=f(lc/lr) (Table 2)	Fl	0.56	
Area of Loop (Table 2)	Atrp	$4.495 \cdot 10^{-5}$	m ²
Turns (calculated)	NtrpTX	273	

Table 4: Typical Parameter of Transponder Transmit Antenna

4.2.2.2 Calculation of Windings

Because the number of windings (Ntrp) is not given for the 2.47mH NEOSID antenna, it must be determined from the calculated windings of 4.7mH antenna:

$$N_{trpTX} = N_{trp} \cdot \sqrt{\frac{L_{trpTX}}{L_{trp}}} = 273$$

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.2.2.3 Effective Antenna Radius

The effective antenna radius of transponder transmit antenna (rr_{tx}) depends on the radius of the antenna rod (rr), the rod permeability (μ_{rod}) and an empirical factor (F_v):

$$rr_{tx} = rr \cdot \sqrt{\mu_{rod} \cdot F_v} = 0.00998m$$

4.2.2.4 Peak Antenna Current

The Transponder transmit antenna is driven in a full-bridge mode, supplied by a battery ($V_{bat} = 3V$). The peak-to-peak current depends on the transmit antenna quality factor (Q_{trpTX}). For the medium frequency ($f_0 = (f_L + f_H)/2$):

$$R_{trpTX} = \frac{2 \cdot \pi \cdot f_0 \cdot L_{trpTX}}{Q_{trpTX}} = \frac{1974}{30} = 65.8\Omega$$

$$I_{trpTX} = \frac{V_{bat}}{R_{trpTX}} \cdot \frac{4}{\pi} = 58mA_p$$

$$U_{trpTX} = I_{trpTX} \cdot 2 \cdot \sqrt{R_{trpTX}^2 + (2 \cdot \pi \cdot f_L \cdot L_{trpTX})^2} = 0.116 \cdot 1975 = 229V_{pp}$$

4.2.2.5 Response Coupling Factor

The response coupling factor (K_{rx}) over distance (d) between the Base Station and the Transponder antenna is calculated as follows,

$$K_{rx} = \frac{\mu_0 \cdot (r_{tx}^2 \cdot \pi \cdot N_{tx}) \cdot (rr_{tx}^2 \cdot N_{trpTX})}{2 \cdot (d^2 + rr_{tx}^2)^{1.5} \cdot \sqrt{L_{tx} \cdot L_{trpTX}}}$$

For a distance of $d = 1.1m$ the response coupling factor is $K_{rx} = 3.63785e-6$.

TI INFORMATION SELECTIVE DISCLOSURE	TEXAS INSTRUMENTS MCU RF SPECIFICATION	Revision: 01
--	---	-----------------

4.2.2.6 Receiver Input Voltage

The Base Station antenna voltage (URX) at a given coupling factor (Krx), induced by a certain Transponder peak-to-peak antenna voltage (UtrpTX) can be calculated as follows,

$$URX = \frac{Krx \cdot \sqrt{LtrpTX \cdot Ltx} \cdot UtrpTX \cdot 2 \cdot \pi \cdot fres}{2 \cdot \sqrt{2} \cdot 2 \cdot \pi \cdot fres \cdot LtrpTX \cdot \sqrt{\frac{1}{QtrpTX^2} + 1}} \approx \frac{UtrpTX \cdot Krx}{2 \cdot \sqrt{2}} \cdot \sqrt{\frac{Ltx}{LtrpTX}}$$

For a distance of d= 1.1m the Base Station antenna voltage is Urx= 298.5µV.

The receiver input voltage is higher due to the quality factor of the receiver resonant circuit, but the amplitude of the receive frequencies (fL= 133.3 kHz, fH= 121.2 kHz) will be damped by approximately 3dB (a factor of 0.7) due to the resonant circuit bandwidth.

$$UIN[Vpp] = URX \cdot QRX \cdot 2 \cdot \sqrt{2} \cdot 0.7 = 6mVpp$$

4.2.2.7 Conclusions

For a distance of 1.1m the receiver input voltage is 6mVpp—sufficient amplitude for the TMS3705A's typical sensitivity of 1.5mVpp. The TMS3705A is the analog front end located in the Base Station.

5 Revision History

Rev.	SCN	Description of Change	Date submitted	By
00		New Issue	02/16/2012	H. Meier