



Hands On with TI's Free SPICE tool "TINA-TI"

(Beginner to Advanced in 30 minutes)

May 2018

Created by Keith Keller
TI Analog Field Applications
Milwaukee Wisconsin

Hands on with TI's Free SPICE Tool "TINA-TI"



- Installing The Software
 - Finding and Placing Components
 - Example Circuits in TINA-TI
 - "Trust but Verify" method for op amps.
 - Average Model, Transient Model and Green-Lis
 - TI ONLINE Precision Labs Training
 - Get Models at WWW.TI.COM/SPICERACK
 - Using a component already in TINA
 - How to Import a .TSM File
 - How to Import a .LIB File
 - Results Window Overview
 - Enable Instant Diagram Drawing
 - Electric Rules Check
 - Offset Voltage Measurement
 - Transient Analysis Input / Output Voltage Swing
 - Bandwidth testing
 - Slew Rate
 - Noise Analysis
 - Voltage Generator as a Square Wave
 - Voltage Generator as a Triangle Wave (Example Circuit)
 - Voltage Generator as a Piecewise Linear Source
 - Phase Delay Calculation
 - Stability Calculation
 - Adding and Removing Variable Sweep Feature
 - Change Axis in Results Window
 - SEPIC Converter Example LM5022 (Transient Model)
 - Flyback Converter Example
 - Adjusting Analysis Parameters when necessary
 - Will Not Converge / Need More Resolution
 - Capacitor on Operation Amplifier Input Causes Convergence Error
 - Need More Memory
 - Output Waveform is Truncated
- TI E2E Online Support:
https://e2e.ti.com/support/development_tools/webench_design_center

Installing Tina-TI

- Search Tina from www.ti.com
- Choose “tina ti download” link
- Choose Link: TINA-TI SPICE-Based Analog Simulation Program | TI.com
- Download in your Preferred Language

www.ti.com

Everything

Tina

tina ti download

tina ti

tina

tina

1

www.ti.com/sitesearch/docs/universalsearch.tsp?searchTerm=tina ti download#linkId=1&src=top

Everything

Products

Technical documents

Support

Cross reference

2

TINA-TI SPICE-Based Analog Simulation Program | TI.com

http://www.ti.com/tool/tina-ti

... SPICE-Based Analog Simulation Program. (ACTIVE) TINA-TI ... Frequently Asked Questions about TINA-TI version 9 TINA-TI provides all the conventional DC, transient and frequency domain analysis of SPICE and much more. ...

www.ti.com/tool/tina-ti?keyMatch=tina ti download&tisearch=Search-EN-Everything

Everything

Search

Products

Applications & designs

Tools & software

Support & training

Order Now

About TI

TI Home > Semiconductors > Amplifiers > SPICE-Based Analog Simulation Program

Worldwide (In E

SPICE-Based Analog Simulation Program

(ACTIVE) TINA-TI

Description & Features

Technical Documents

Support & Training


Order Now

Part Number	Buy from Texas Instruments or Third Party	Alert Me	Status	Current Version	Version Date	OS
TINA-TI_ENGLISH: Analog SPICE-Based Simulation Program	Free Download	Alert Me	ACTIVE	v9.3.150.328 SF-TI	07 Feb 2017	Windows XP, 7, 8
TINA-TI_RUSSIAN: SPICE-Based Analog Simulation Program	Free Download	Alert Me	ACTIVE	v9.3.150.328 SF-TI	07 Feb 2017	Windows XP, 7, 8
TINA-TI_TRA_CHINESE: SPICE-Based Analog Simulation Program	Free Download	Alert Me	ACTIVE	v9.3.150.328 SF-TI	07 Feb 2017	Windows XP, 7, 8
TINA-TI_SIMP_CHINESE: SPICE-Based Analog Simulation Program	Free Download	Alert Me	ACTIVE	v9.3.150.328 SF-TI	07 Feb 2017	Windows XP, 7, 8
TINA-TI_JAPANESE: SPICE-Based Analog Simulation Program	Free Download	Alert Me	ACTIVE	v9.3.150.328 SF-TI	07 Feb 2017	Windows XP, 7, 8


TI's Standard Terms and Conditions for Evaluation Modules apply.

Components Already in TINA

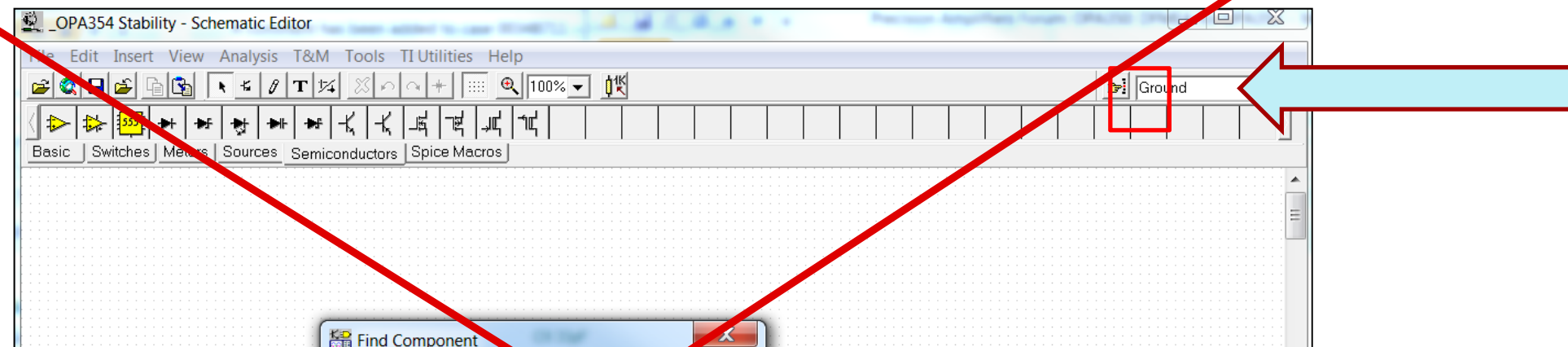
- Click on the Hand Symbol, Far Right, and Search OPA354



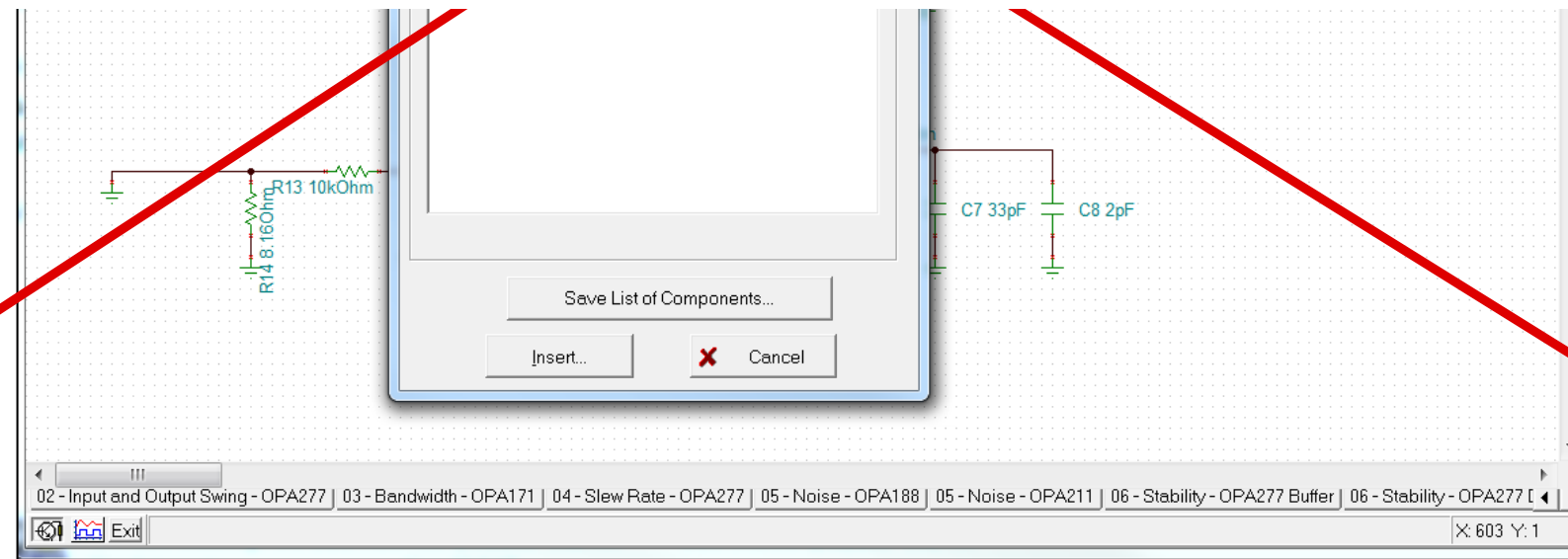USE THE NEWEST MODELS FROM TI.COM
START WITH **.TSC** FILE IF POSSIBLE



Getting Started

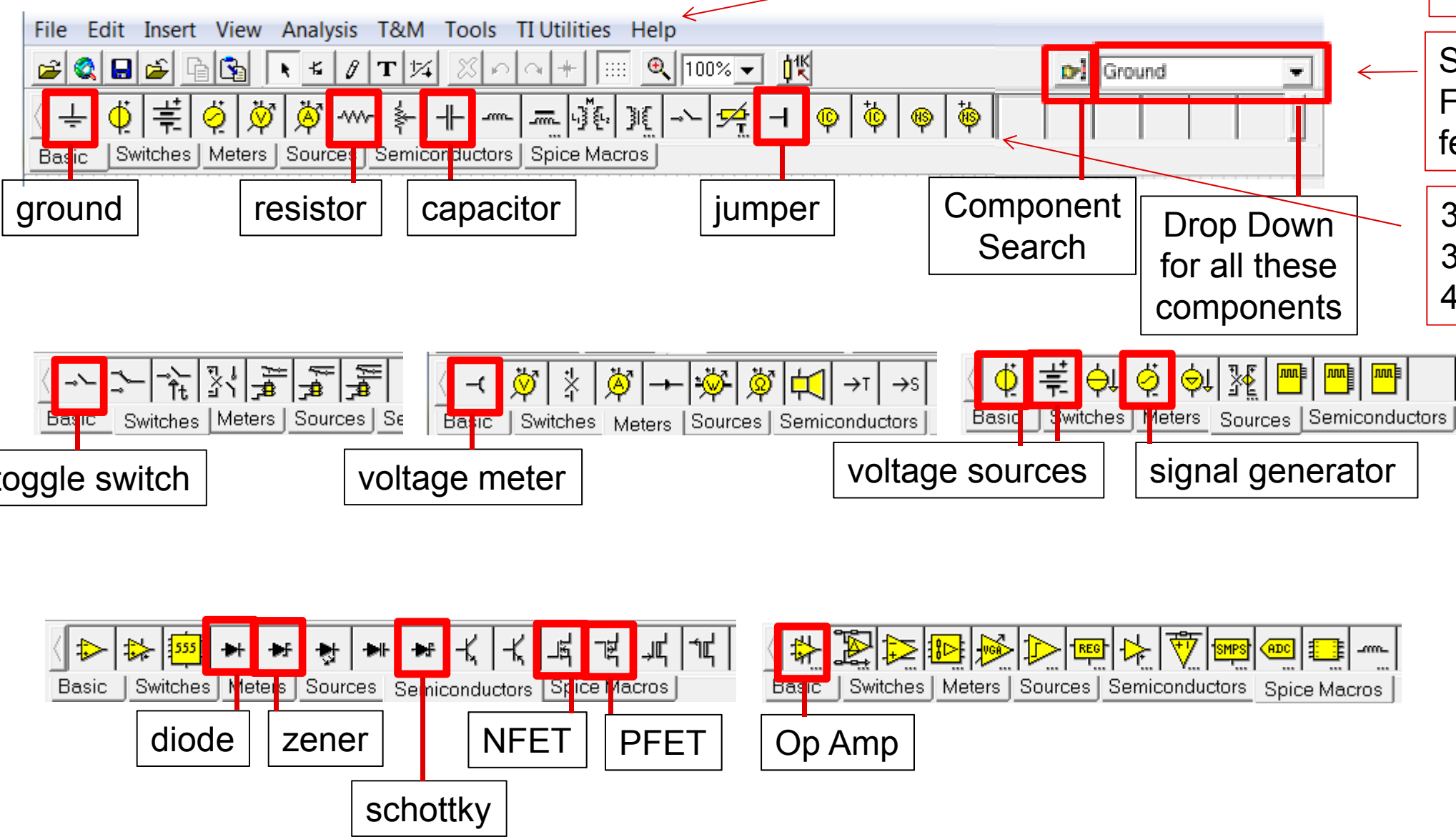

Example: Placing components & Wiring Tool

- Go to Spice Macros and Choose Operational Amplifier



- Scroll Down to OPA330

- Choose a Resistor from the Basic Tab



- Choose Signal Generator from Sources Tab



- Add a Jumper for VCC and VSS to connect to other parts of the circuit





- Practice using Wiring tool with

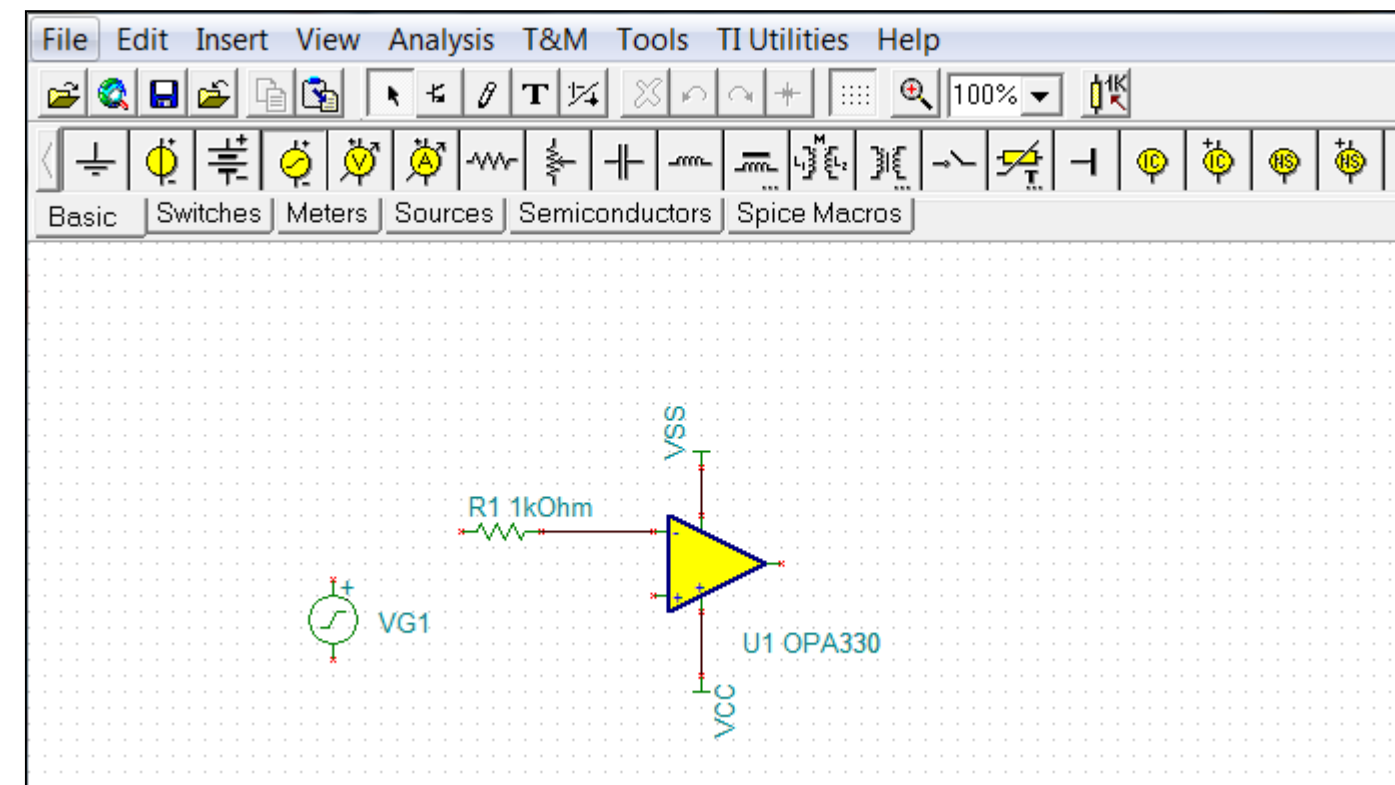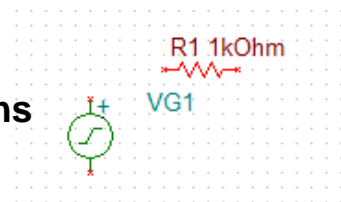1. Space Bar
2. Hover over Red X
3. Might need to hold down on right mouse button to draw

TIP: Wiring Tool

- Hover over Red X on component for Wiring Tool
- Use Space Bar to Start Wiring Tool
- Choose Pencil from Second Row Icons
- Insert → Wiring from Menu
- Hold down on Right Mouse Button to keep Wiring Tool Up (if necessary)



TRUST BUT VERIFY

- On TI's E2E Forums
- https://e2e.ti.com/blogs_/b/analogwire/archive/2017/07/27/trust-but-verify-spice-model-accuracy-part-1-common-mode-rejection-ratio-cmrr

“Trust, but verify” SPICE model accuracy, part 1: common-mode rejection ratio

Facebook 123 Twitter LinkedIn Email + More 18

[SPICE simulation](#) is an immensely valuable tool that allows engineers to have high confidence in their analog designs before ever stepping foot in a lab. While many of us live and die by our simulation results, have you ever stopped to question if your favorite [operational amplifier's](#) (op amp) SPICE model matches the specs promised by its data sheet?

Our competitors' models can often be inaccurate or oversimplified, as shown in the closed-loop output impedance (Z_{out}) comparison in Figure 1. In this case, it's easy to see the difference between what's promised and what's measured. This difference can have a big impact on your designs, potentially causing some unwanted surprises when you fire up your circuit in the lab for the first time.

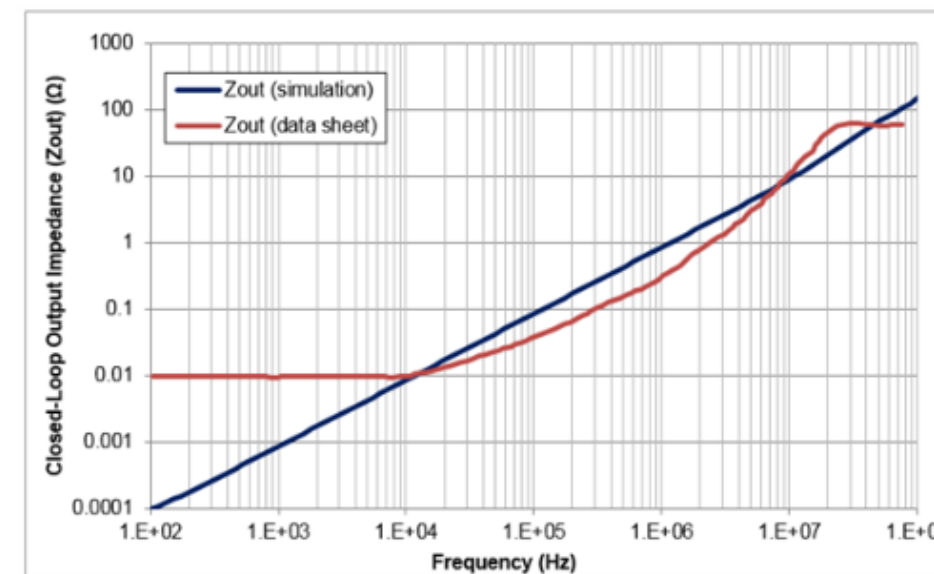



Figure 1: Competitor SPICE model Z_{out} comparison

TI is proud to have some of the most accurate SPICE models in the industry. That being said, it's still a good practice to “trust, but verify” that the models used in your circuit are up to the task. In this [blog series](#), I will show you the recommended test circuits for many of the most critical op amp parameters, starting with common-mode rejection ratio (CMRR).

An op amp's CMRR is formally defined as the ratio of its common-mode gain to its differential-mode gain. In practical terms, the CMRR spec tells you how much additional offset voltage is generated at the op amp's input when the input common-mode voltage changes. A high CMRR is desirable, meaning that you'll see less additional offset voltage. CMRR also changes over frequency, so TI data sheets provide a curve representing typical CMRR over frequency, as shown in Figure 2. For a deeper discussion of CMRR and its impact on circuit performance, watch our [TI Precision Labs – Op Amps video on CMRR](#).


Op Amp Model: Open Loop Gain

Test Circuit for Aol

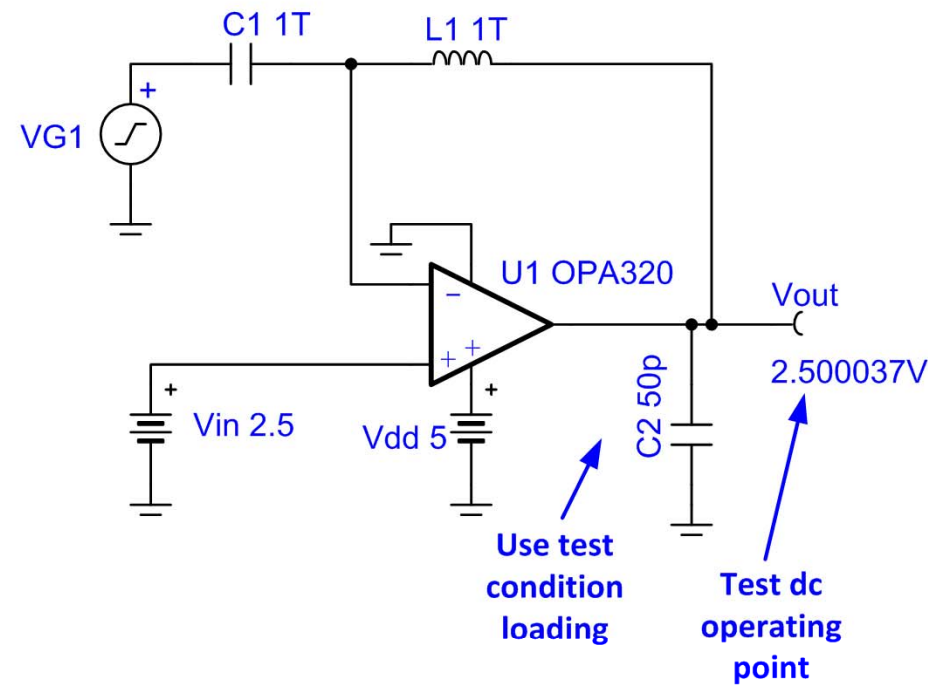


1. Test dc operating point to assure that circuit is correctly wired
 2. Run ac simulation for A_{OL} curve
- $A_{OL} = V_{out}$


Simulated results

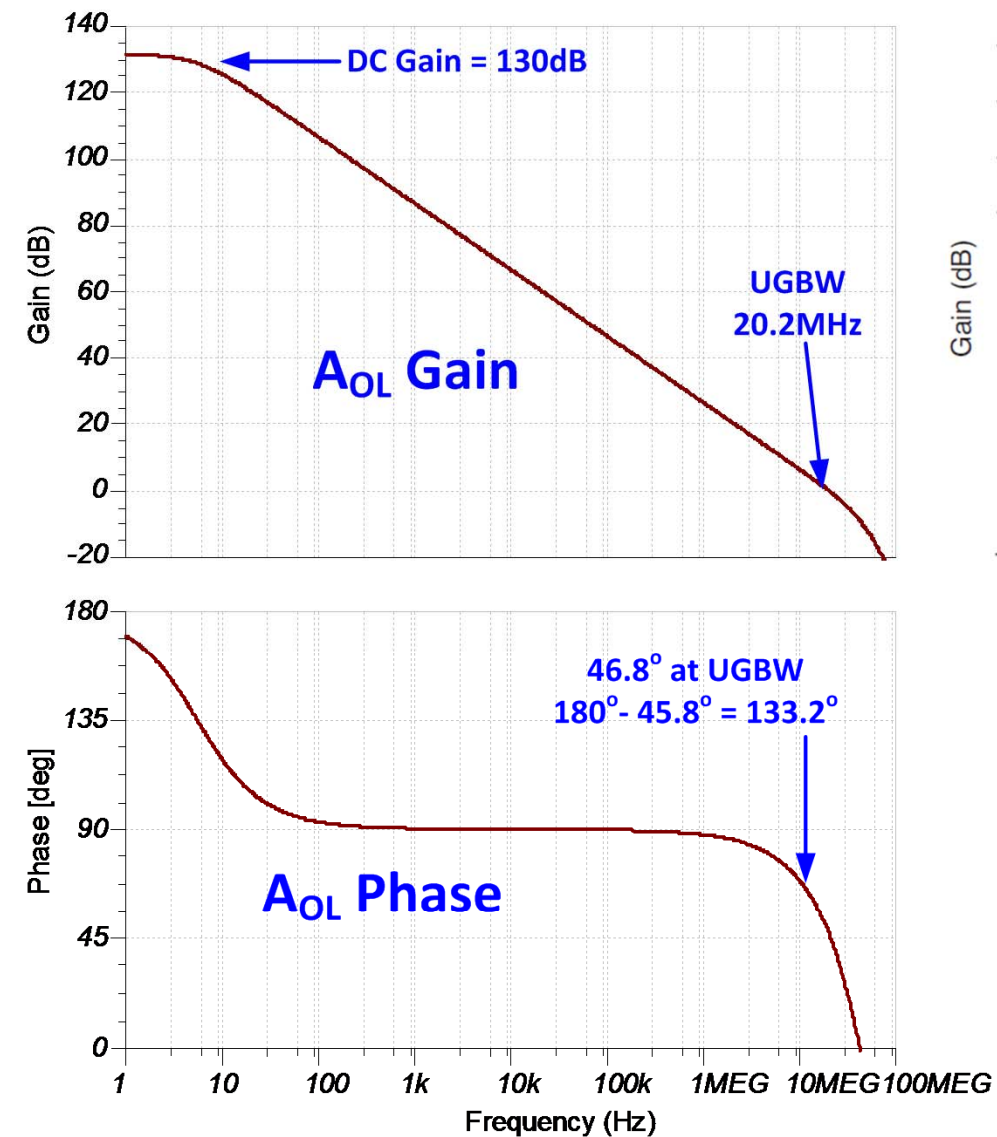

Data Sheet Specification

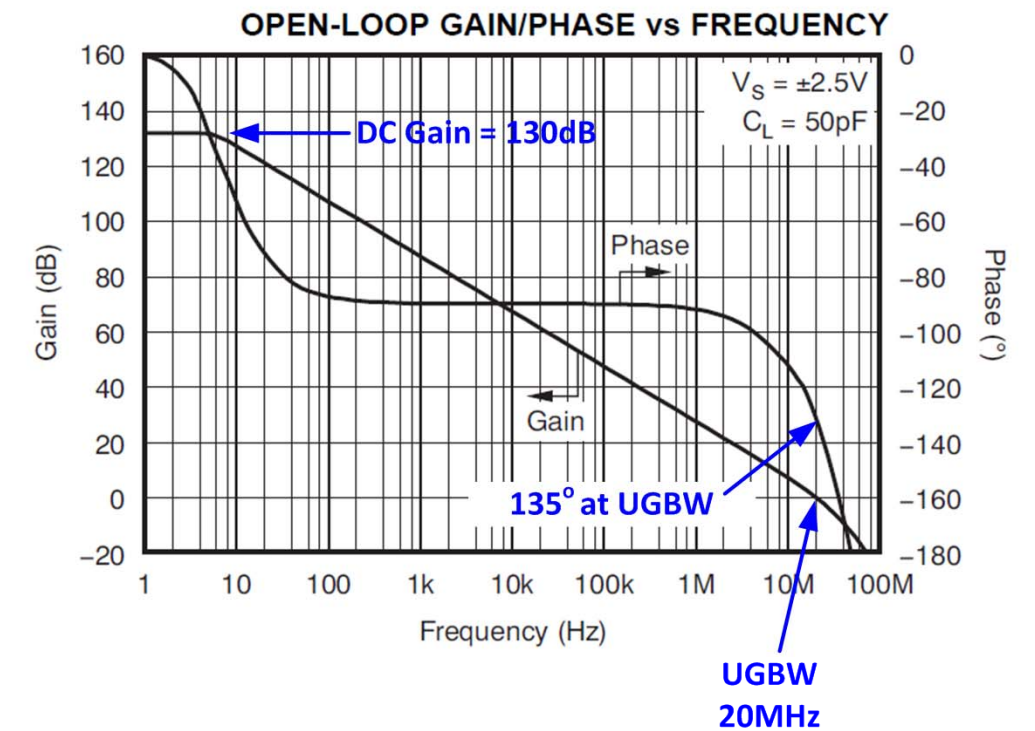


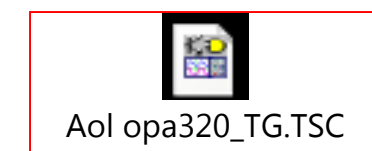Compare key points on simulation results to data sheet curve.



Op Amp Model: Open Loop Output Impedance


Test Circuit for Aol

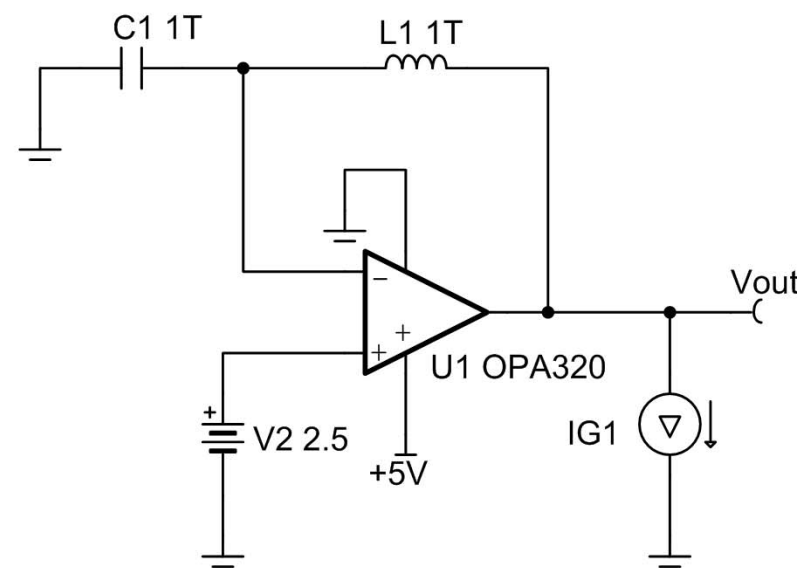


1. Test dc operating point to assure that circuit is correctly wired
2. Run ac simulation for Z_o curve.

$$Z_o(\text{dB}) = V_{\text{out}}(\text{dB})$$
$$Z_o(\text{ohms}) = V_{\text{out}}(\text{Logarithmic})$$

Simulated results

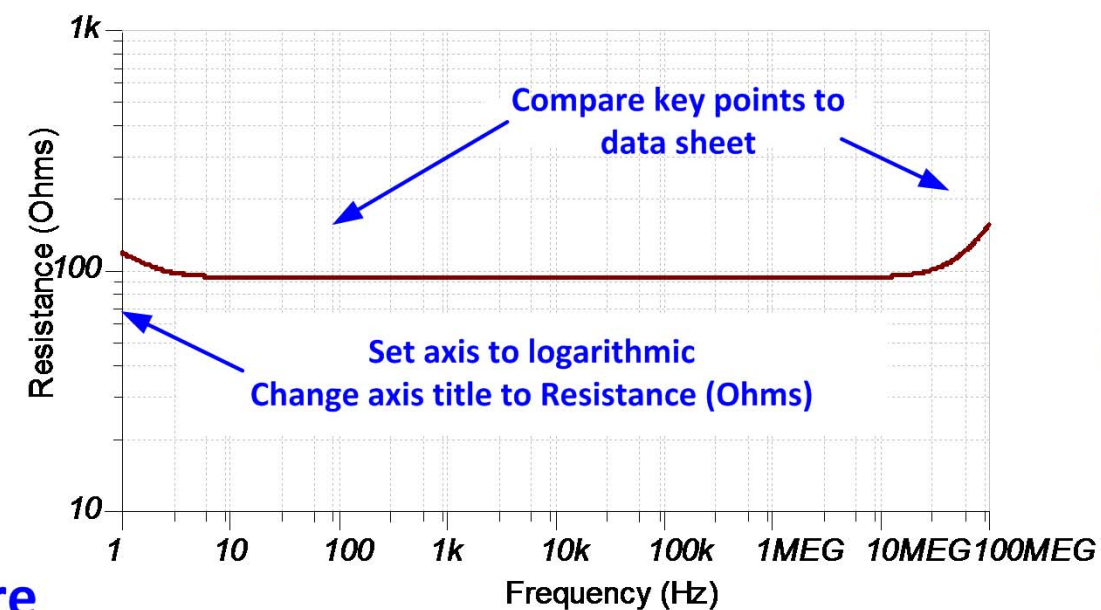


Data Sheet Specification

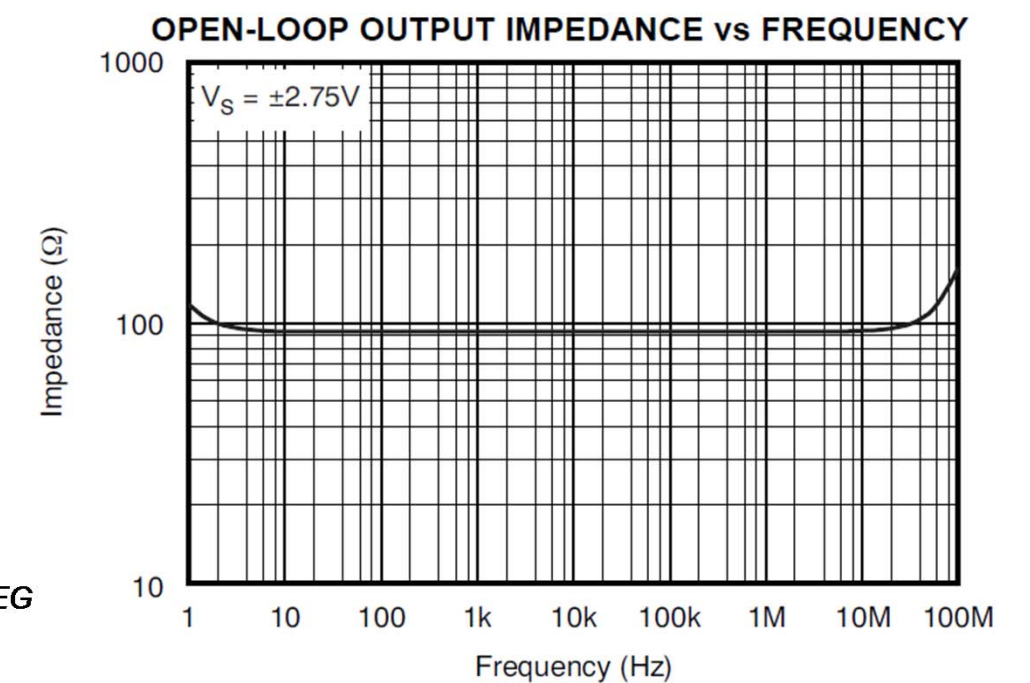

Zo opa320_TG.TSC

Op Amp Model: Closed loop output impedance


Test Circuit for Zout

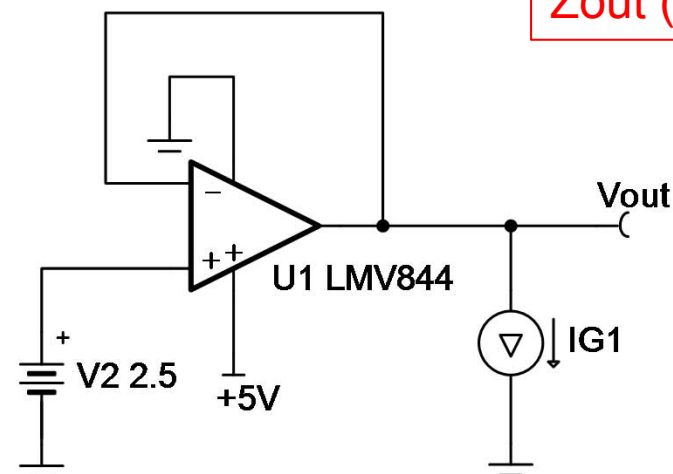

Should Be:
Zout (ohms)

1. Test dc operating point to assure that circuit is correctly wired
2. Run ac simulation for Z_{out} curve.
 $Z_{out} = V_{out}$.
3. Change the vertical axis to logarithmic scale

Simulated results

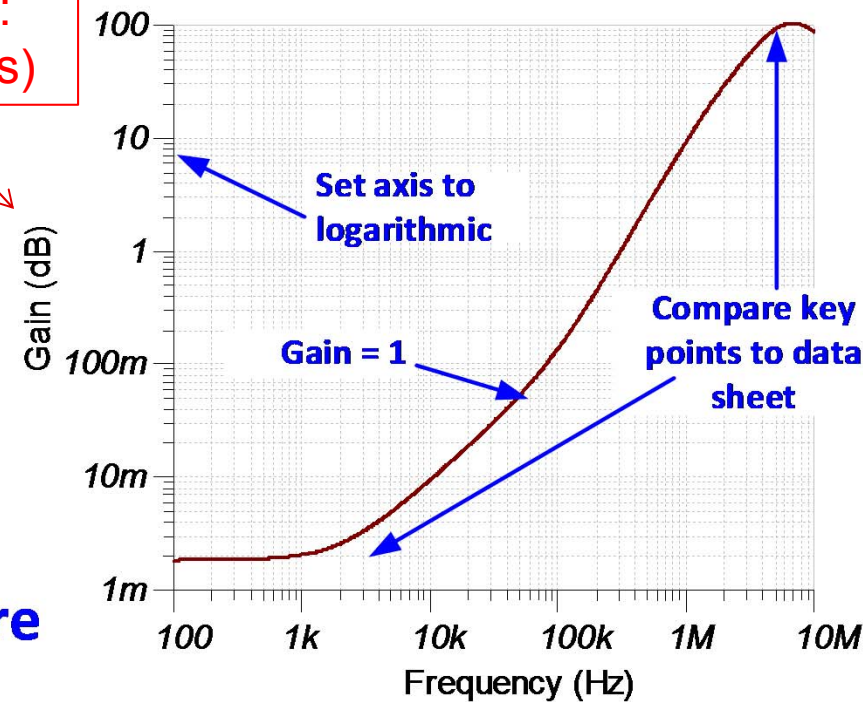

$Z_{out}(dB) = V_{out}(dB)$
 $Z_{out}(ohms) = V_{out}(\text{Logarithmic})$

Data Sheet Specification

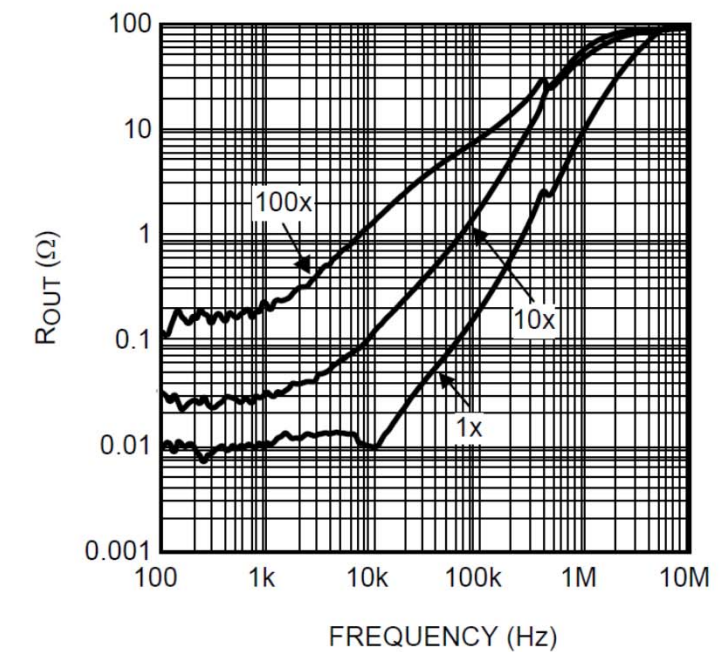


Figure 33. Closed-Loop Output Impedance vs Frequency



LMV844 Zout_TG.TSC

Offset Voltage Measurement




- Example Circuits:

- “01 - Vos and Ib - OPA188.TSC”
- “01 - Vos and Ib - OPA211.TSC”

- Analysis → DC Analysis → Calculate nodal voltages

01 - Vos and Ib - OPA188.TSC

01 - Vos and Ib - OPA211.TSC

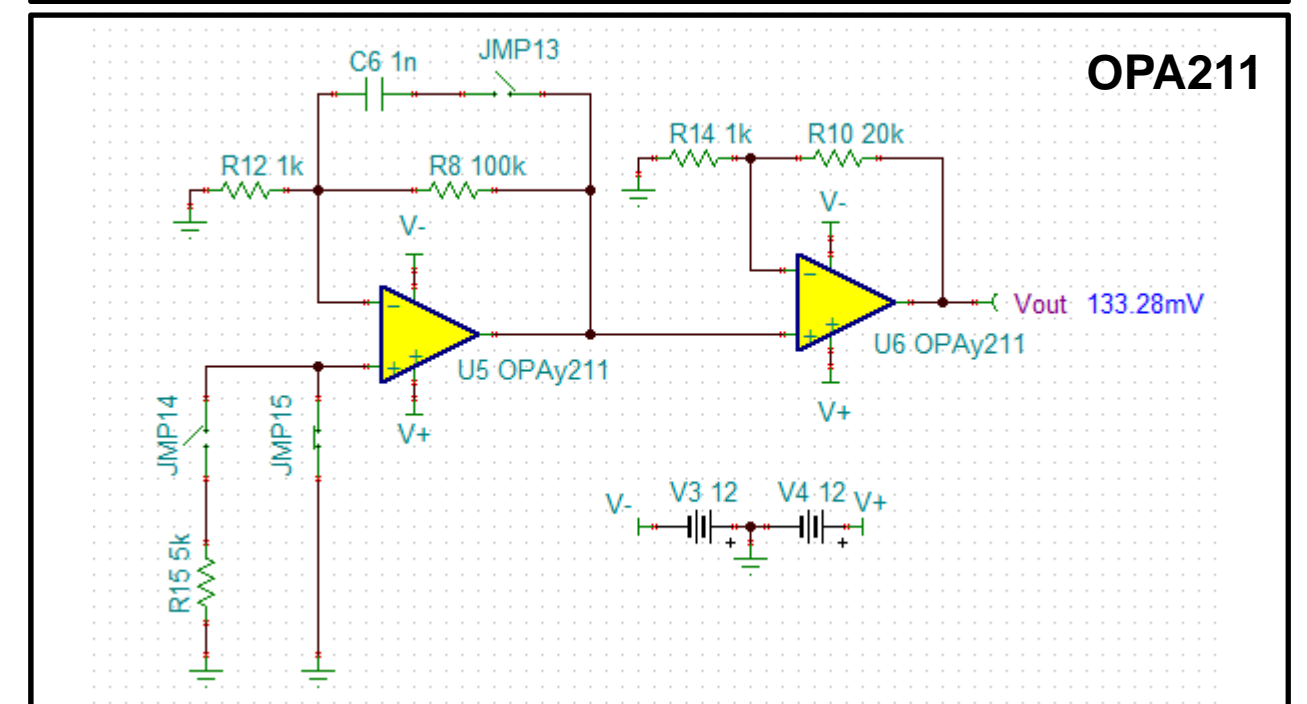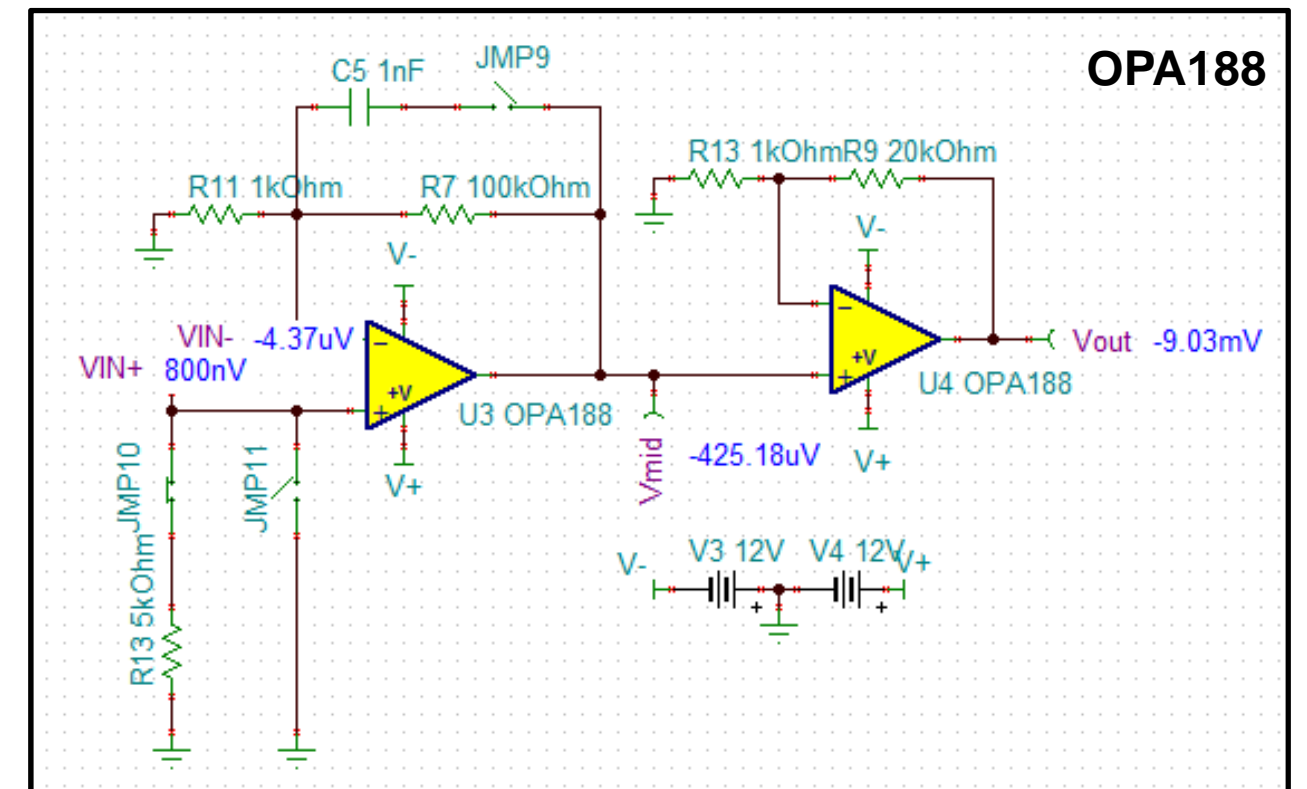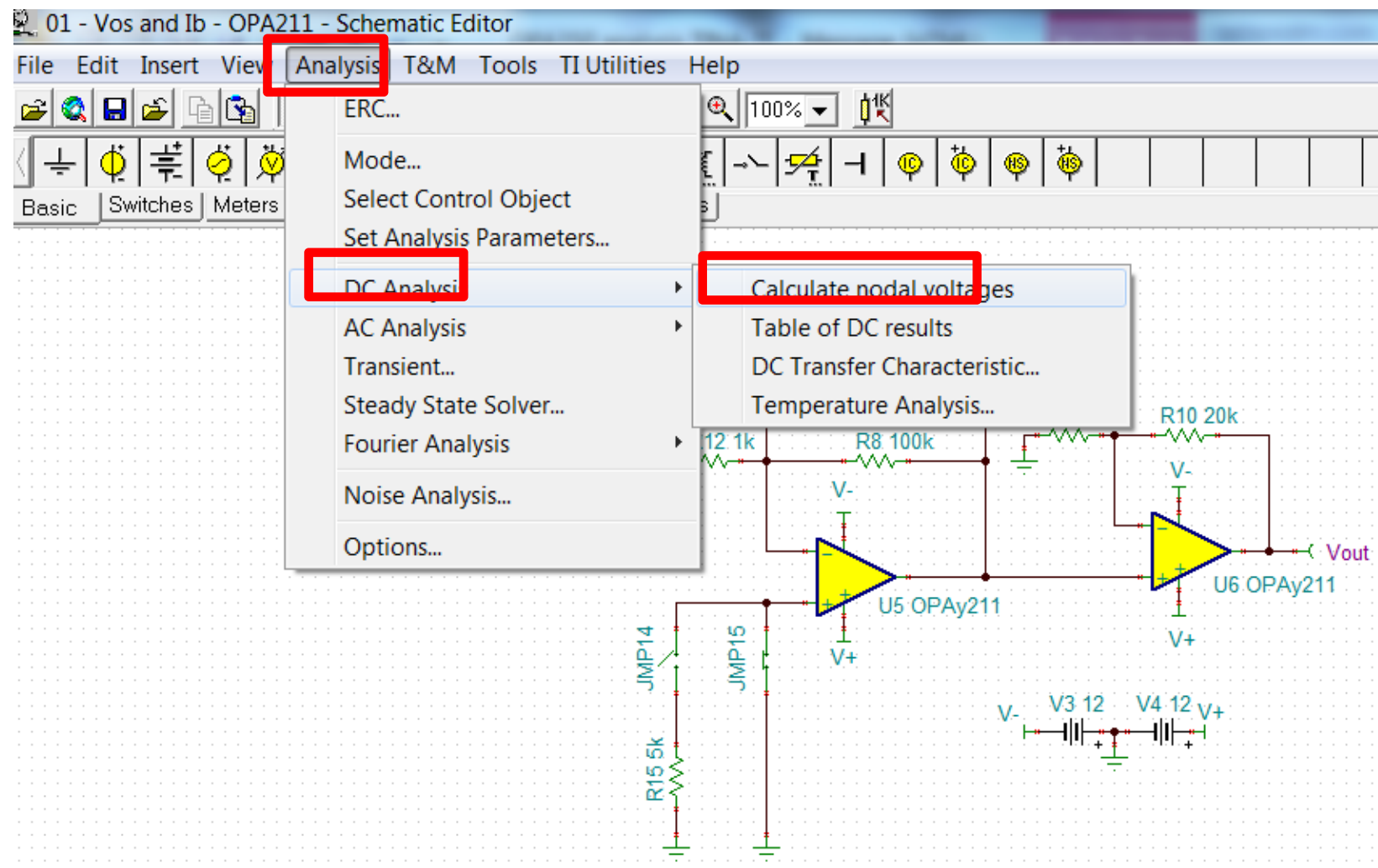

Transient Analysis Input / Output Voltage Swing

- Example Circuits:

1. “02 - Input and Output Swing - OPA140.TSC”
2. “02 - Input and Output Swing - OPA277.TSC”

- Analysis → Transient → OK




- View → Separate Curves



02 - Input and Output Swing - OPA140.TSC




02 - Input and Output Swing - OPA277.TSC

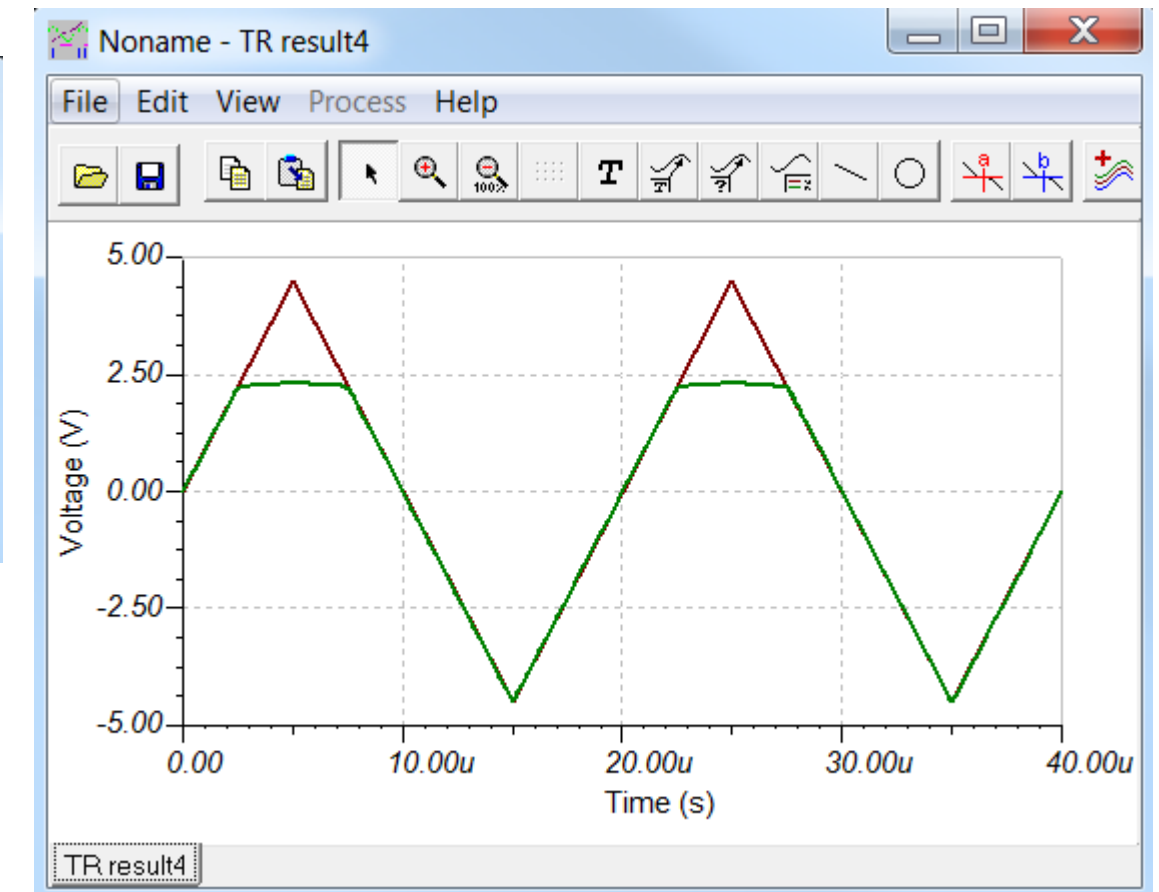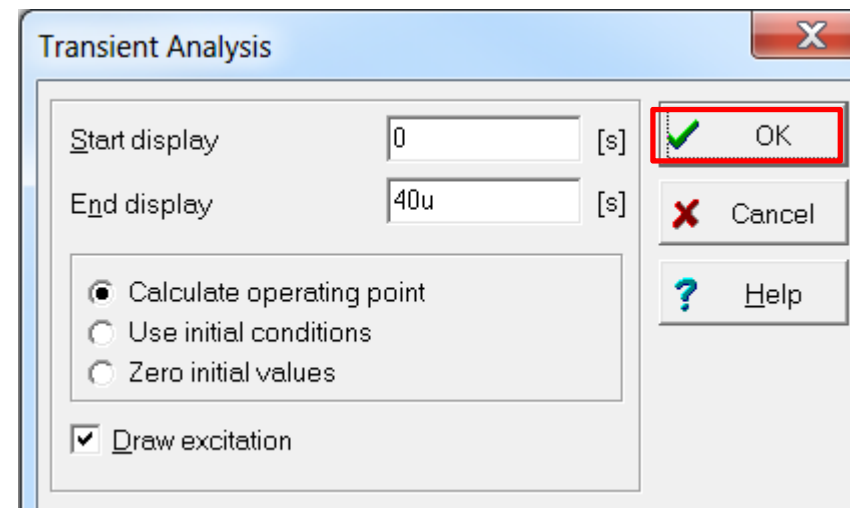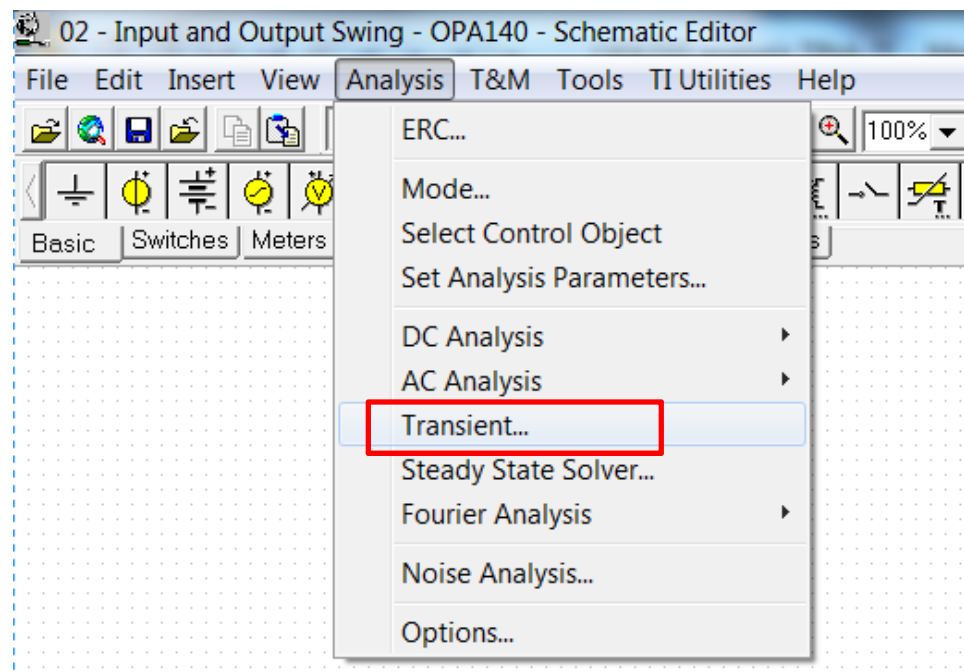


Results Window

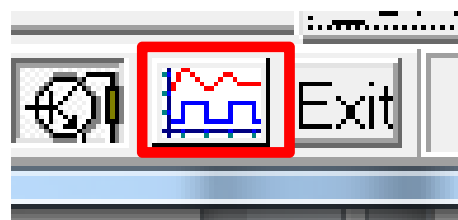- Cursor Window Stays on Top
- Bottom Left Corner has Red & Blue Button to get Results Window Back




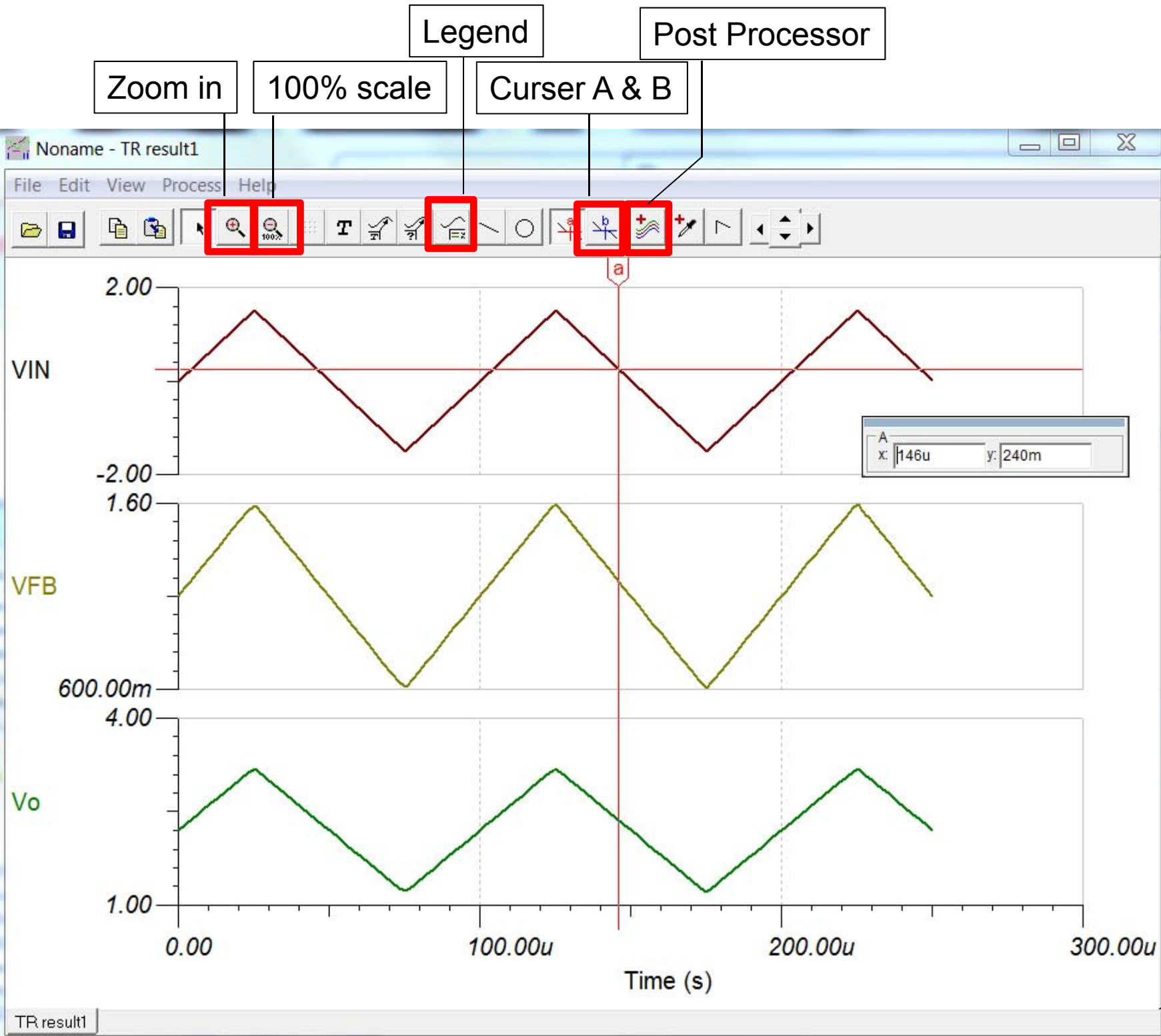- Right Click Mouse for Automatic Gain and Phase Calculation



Enable Instant Diagram Drawing

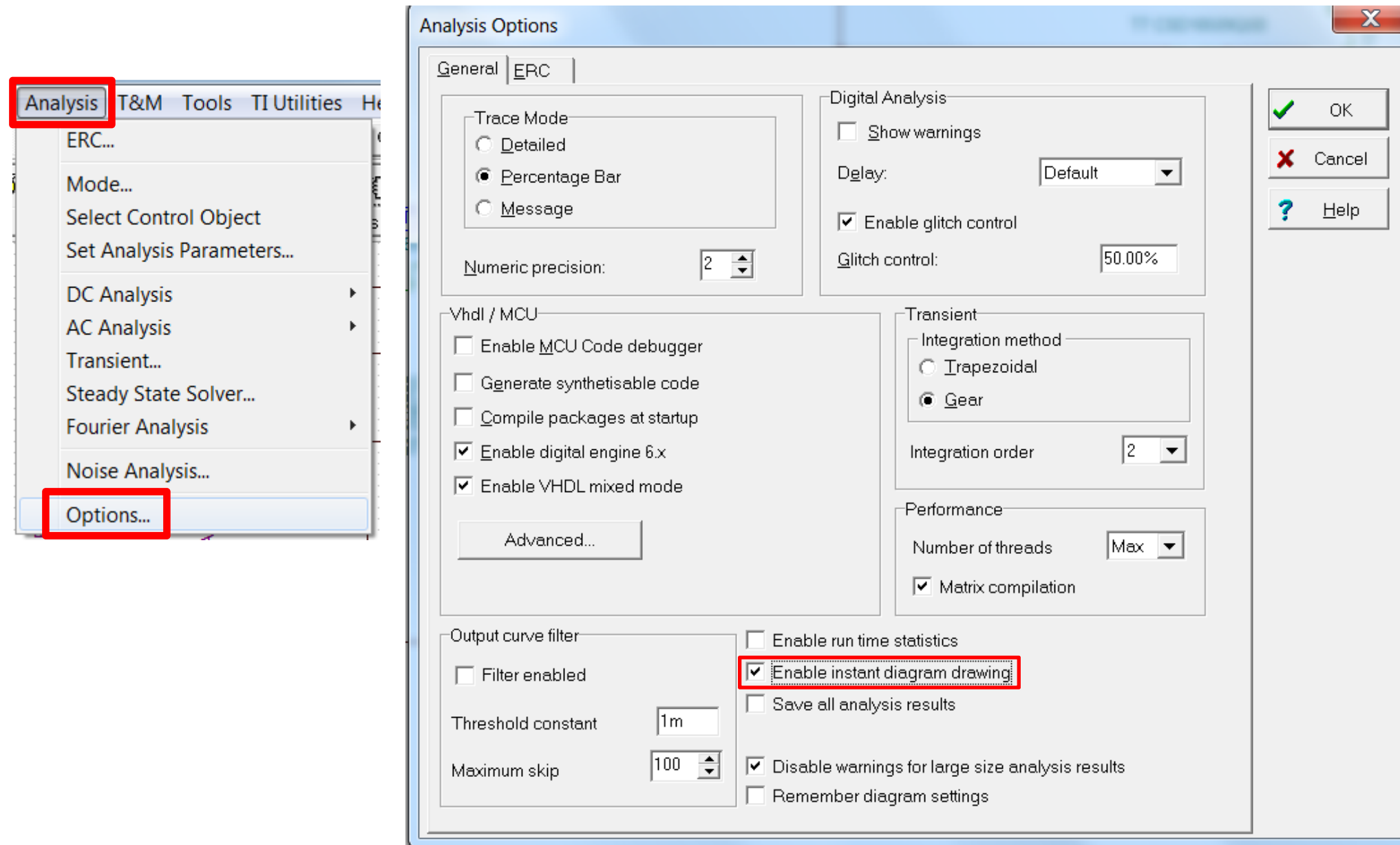
- This has the results window refresh continuously during a simulation
- Analysis → Options → check box “Enable instant diagram drawing”




Separating

TIP: add “:1” to any meter name to show all output Waveforms separately.

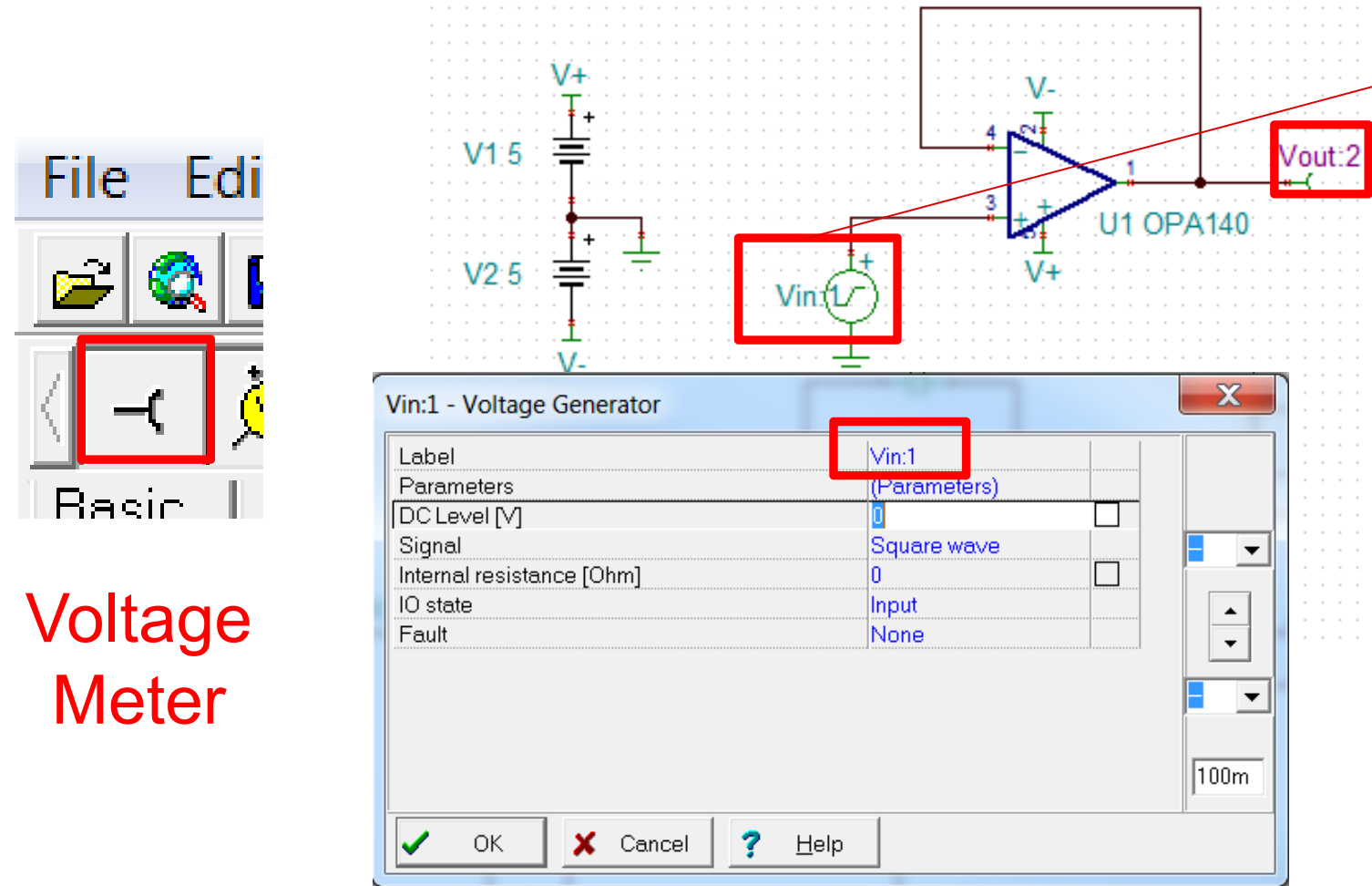Example Double Click “Vin” to **Vin:1** to open voltage generator menu and change Label to “Vin:1”.



Voltage
Meter

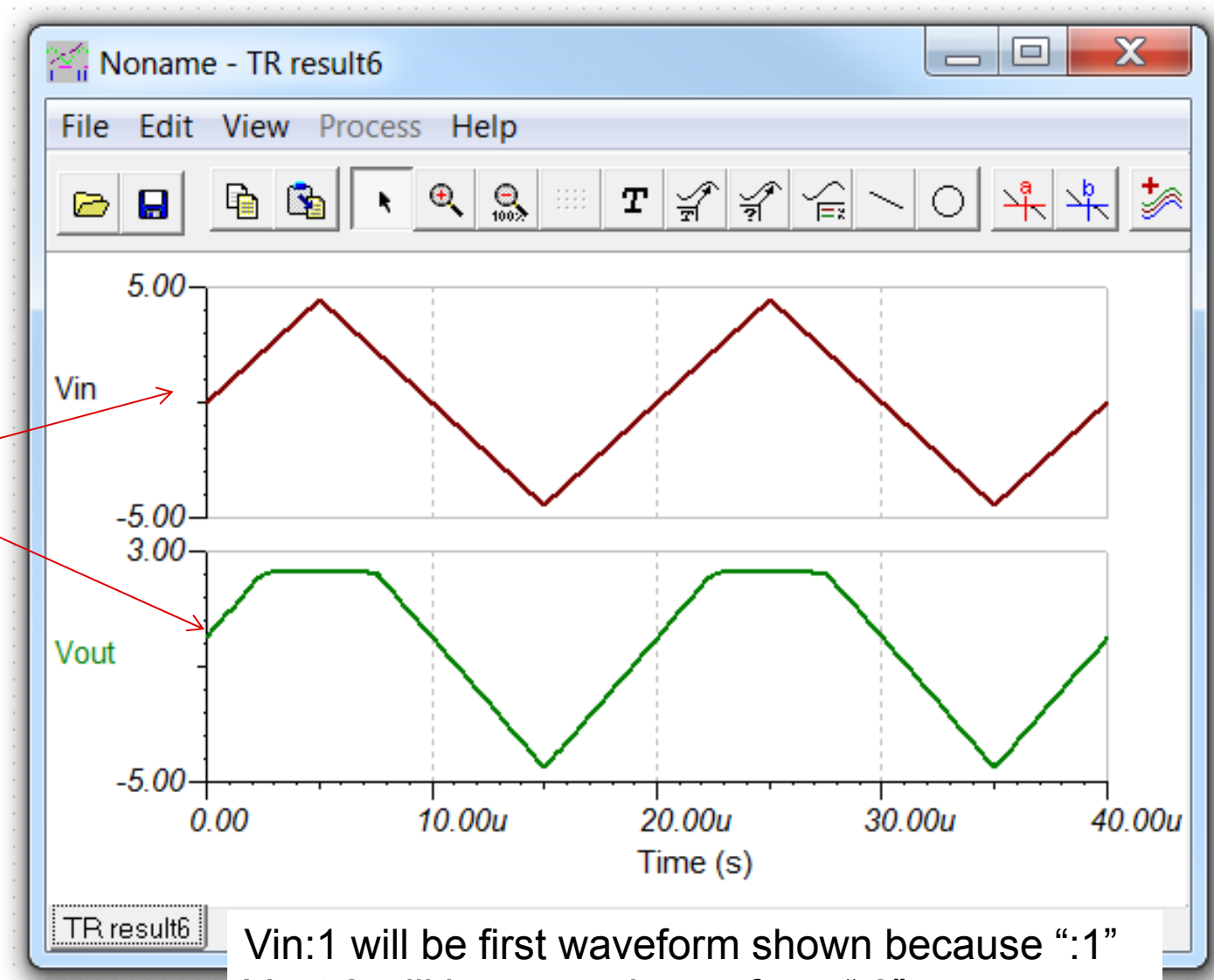




Vin:1 will be first waveform shown because “:1”
Vout:2 will be second waveform “:2”

Bandwidth Testing

- Example Circuit:
 - “03 - Bandwidth - OPA171.TSC”
- Analysis → AC Analysis → AC Transfer Characteristic → OK
- Use “a” “b” cursers for analysis.
- -3dB point is 23dB Gain & 160kHz Bandwidth






03 - Bandwidth - OPA171.TSC

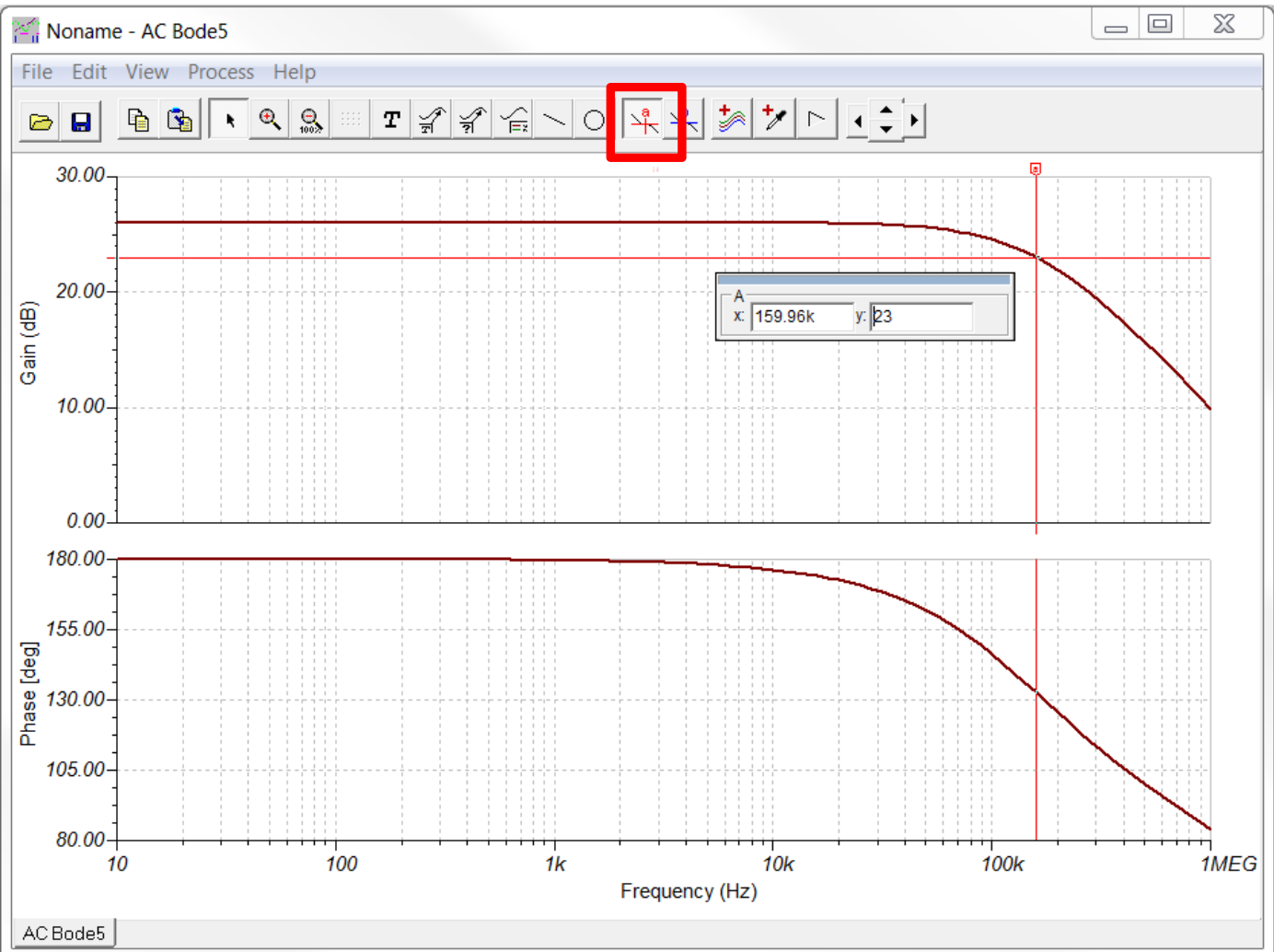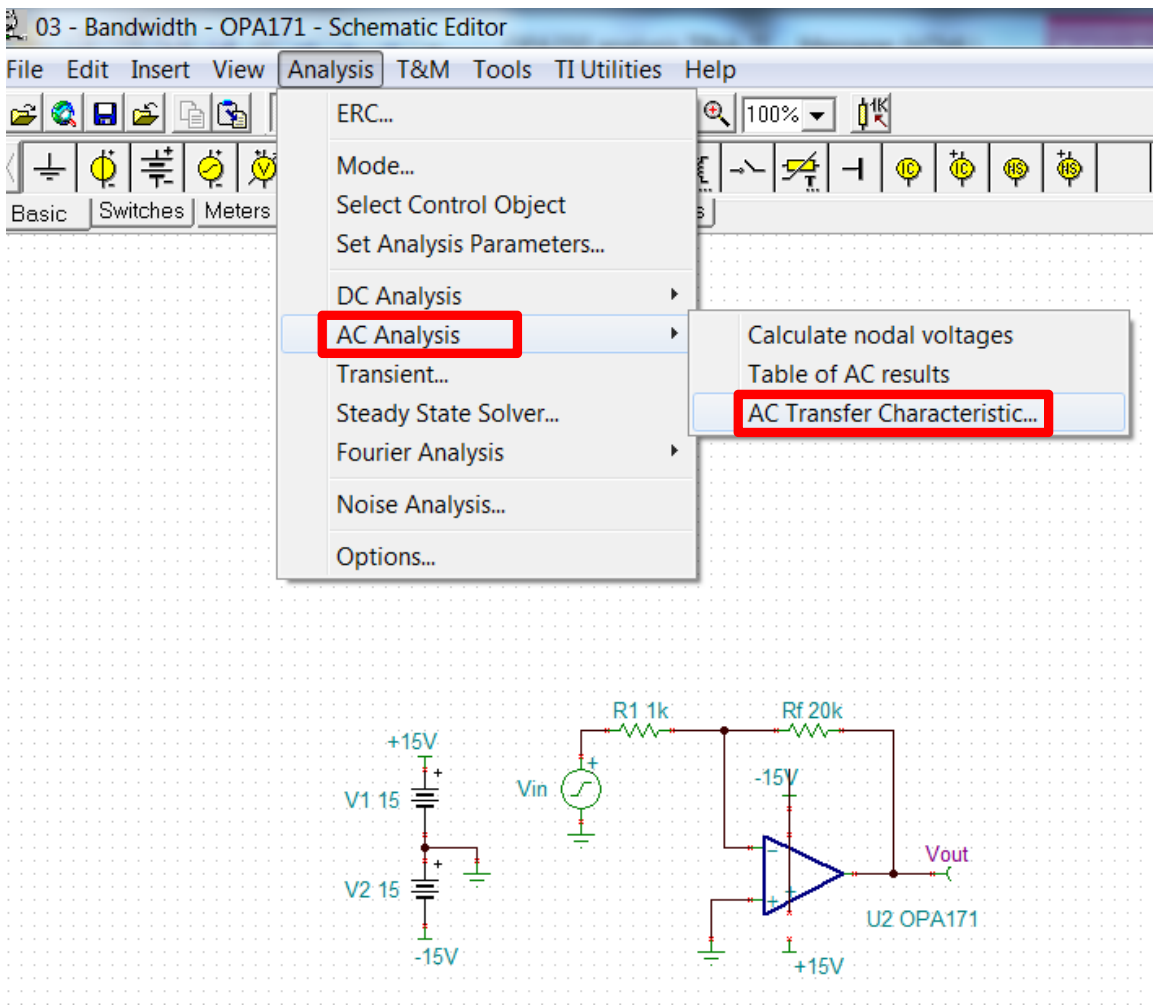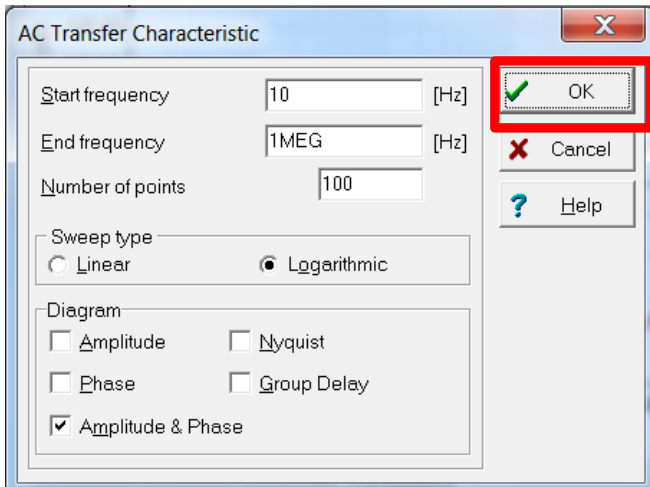

Slew Rate

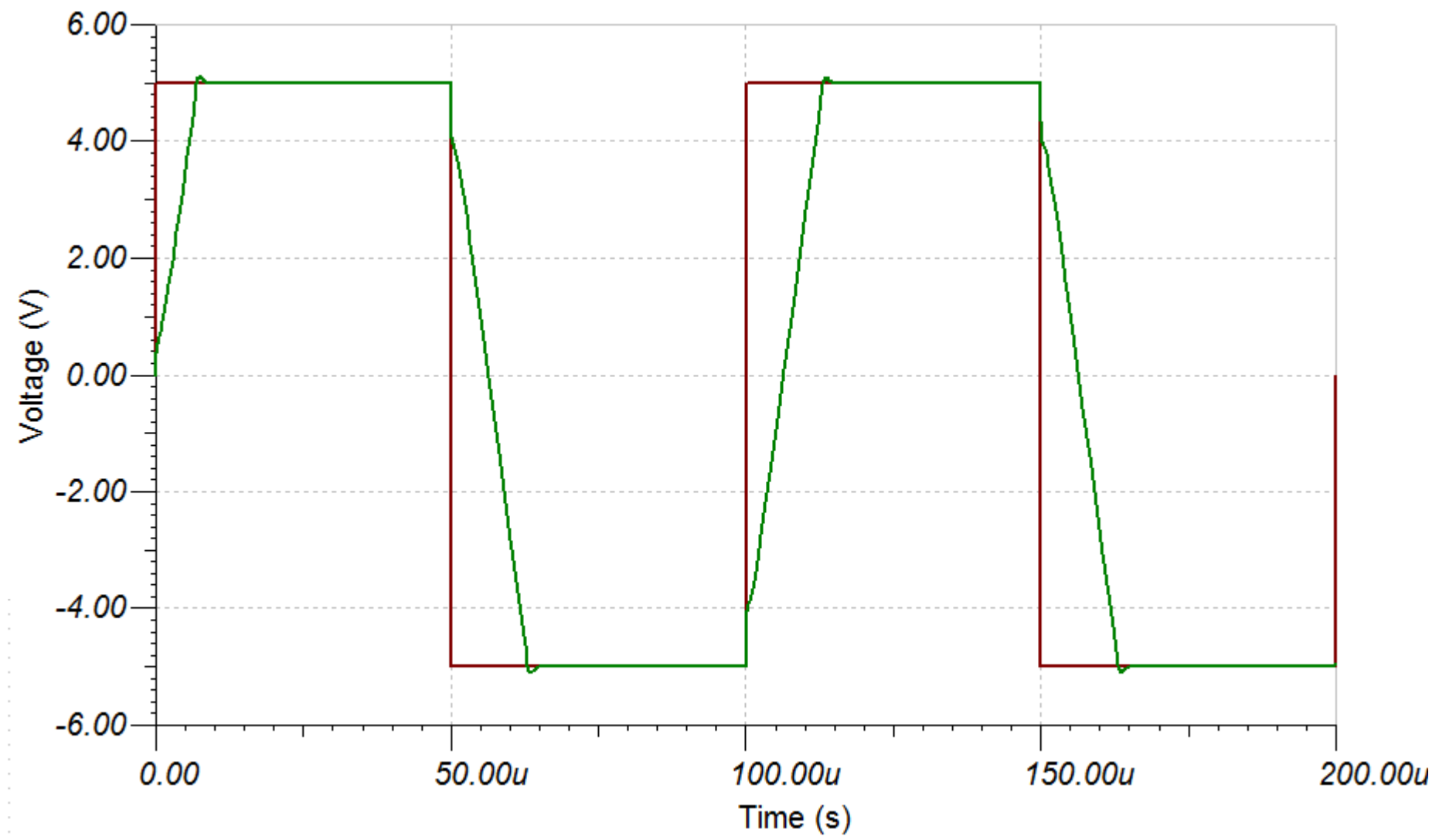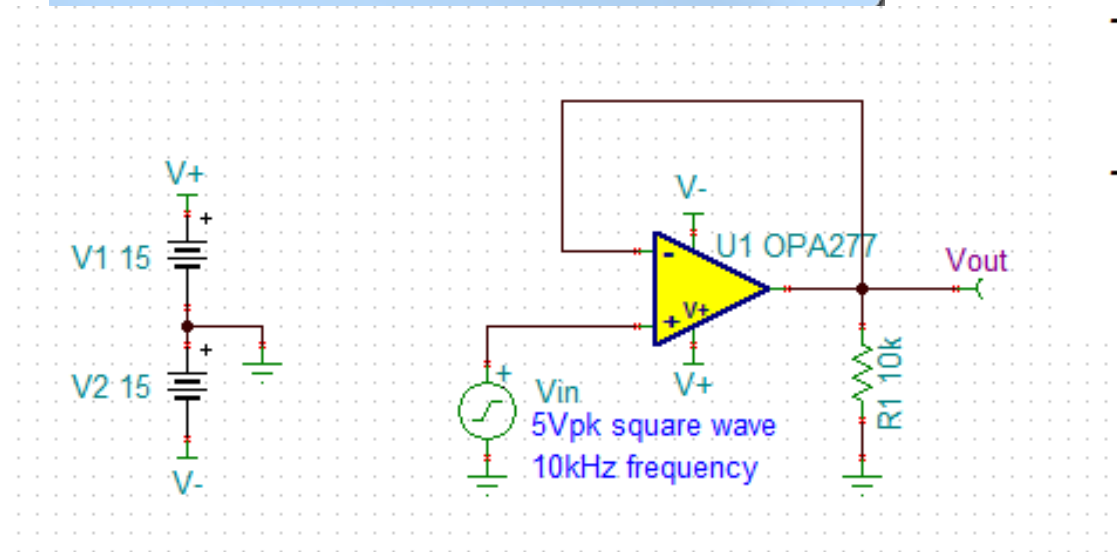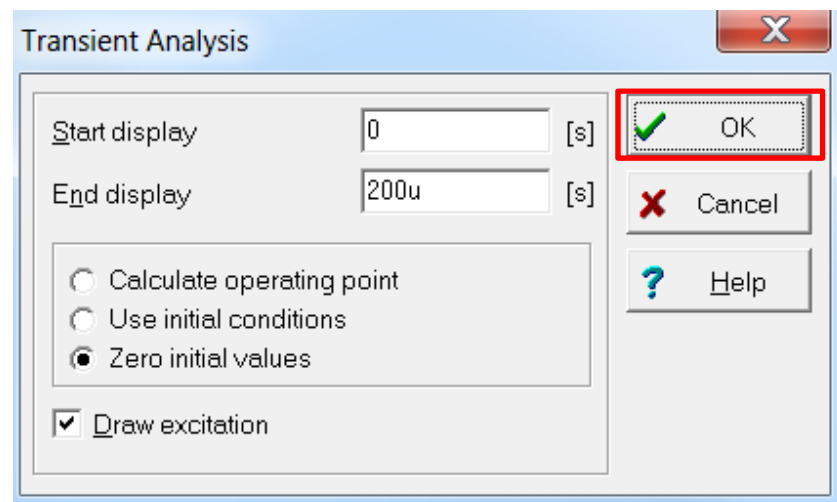- Example Circuit:
 - “04 - Slew Rate - OPA277.TSC”
- Analysis → Transient → OK




04 - Slew Rate - OPA277.TSC

Voltage Generator Configuration

- Example:
Set Voltage Generator for 0V to 3.3V 10kHz Square Wave

- Choose Voltage Generator Symbol

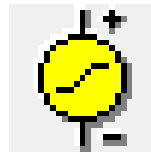

- Double Click to Set Parameters



- Set DC Level [V] → 1.65V

- Go to Signal → Unit Step → Press  Button


- Set Amplitude [V] (A) → 1.65

- Set Frequency [Hz](f) → 10k


- Set Rise / fall time [s] (tau) 10n

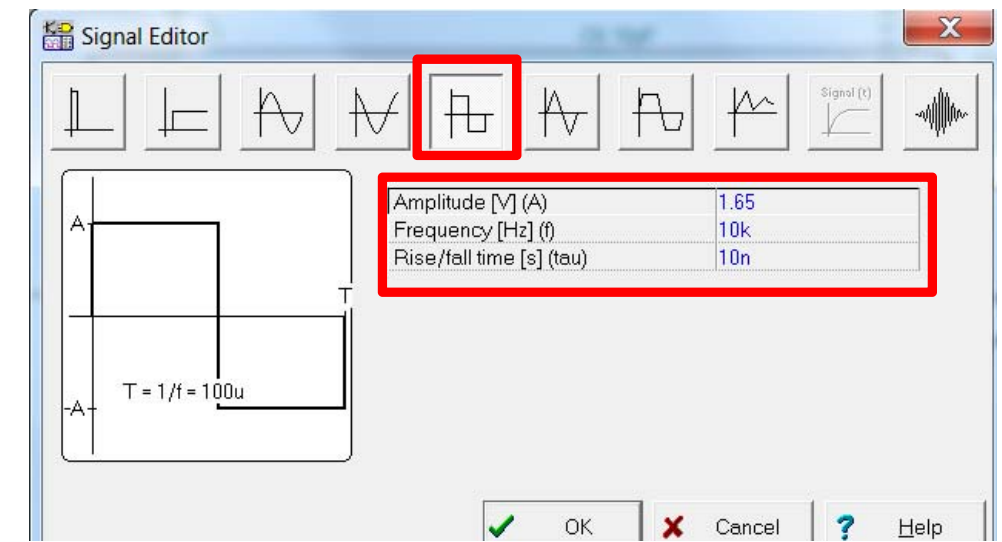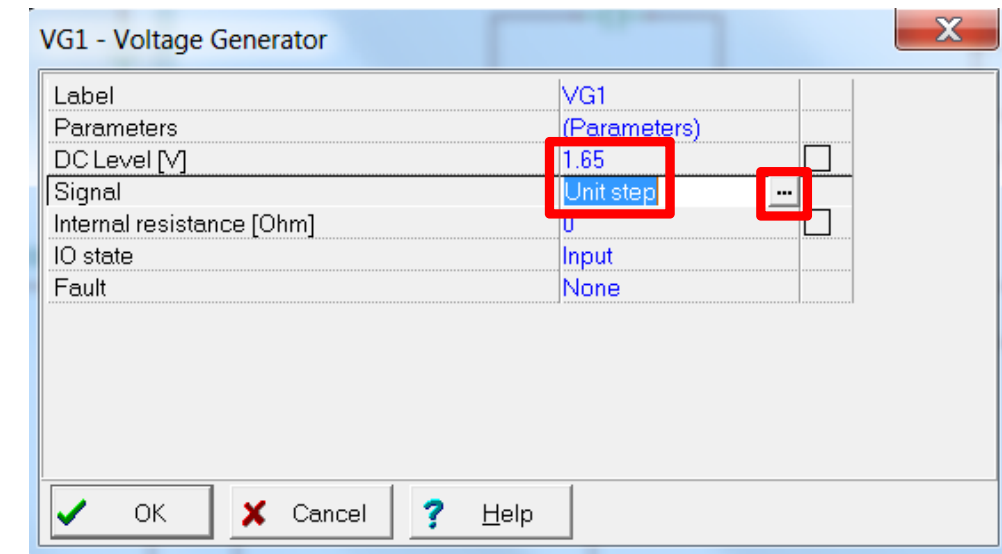


Waveform Results →


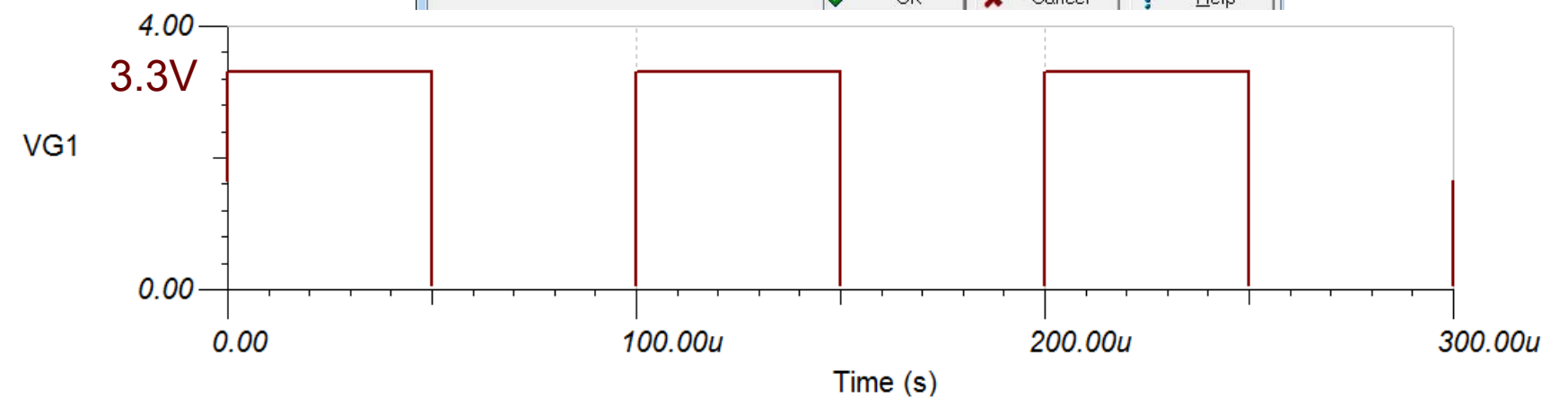


Voltage Generator as a Triangle Wave – OPA354

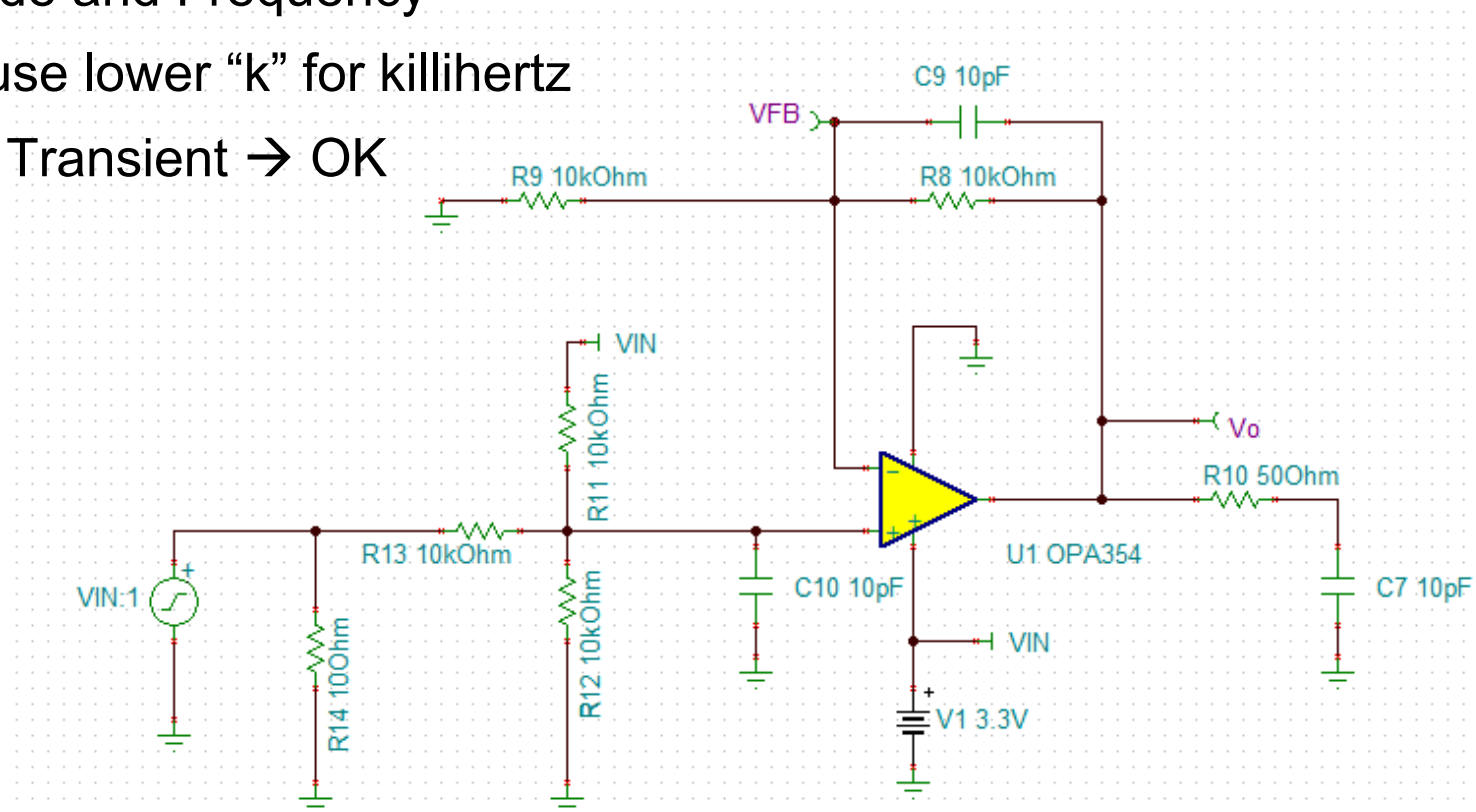
- Example Circuit:
 - “_OPA354 Circuit.TSC”
- Double Click on “VIN:1” Voltage Generator Symbol
- Set a “DC Level [V]”
- Choose the  3 dots next to Signal
- Choose Triangle Waveform at Top
- Set Amplitude and Frequency
- Be sure to use lower “k” for killihertz
- Analysis → Transient → OK






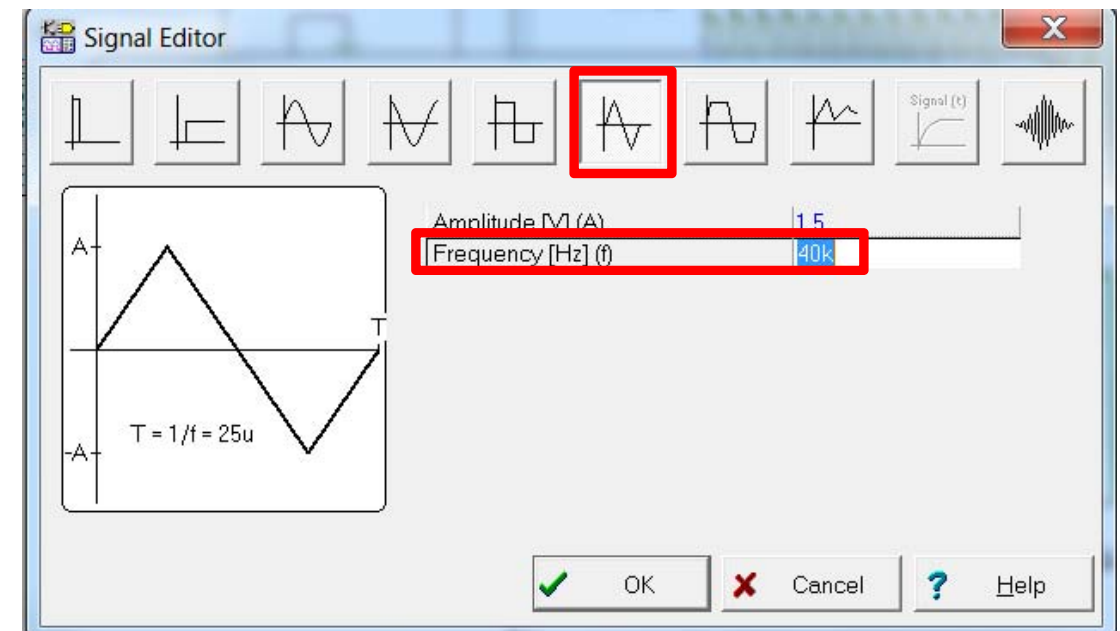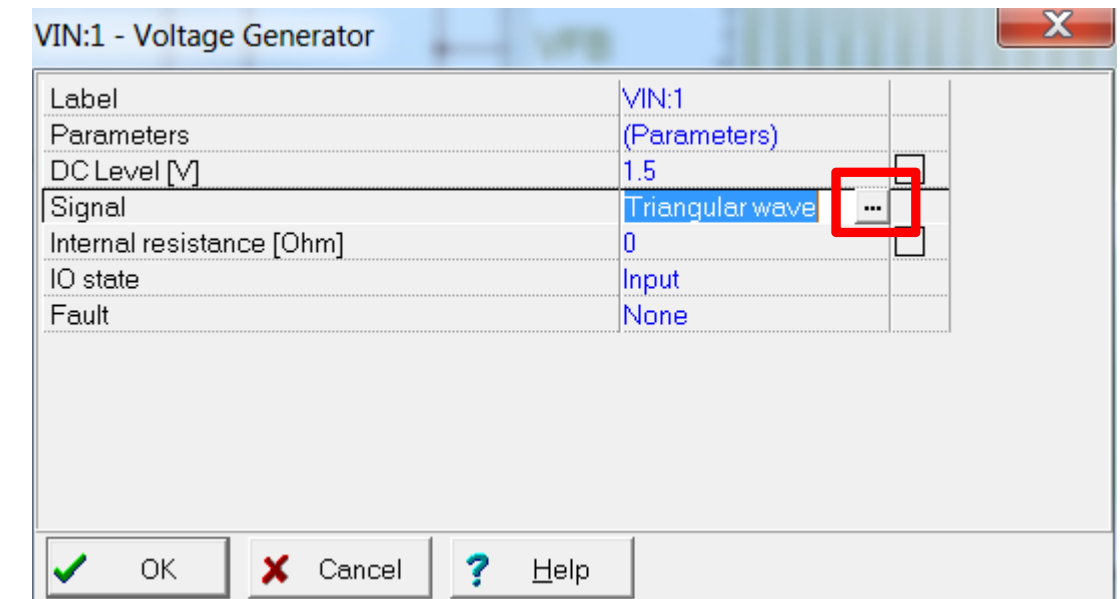This Creates a Triangle Wave from 0 to 3.3V



Generating a Piecewise Linear Voltage Source

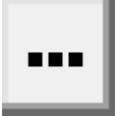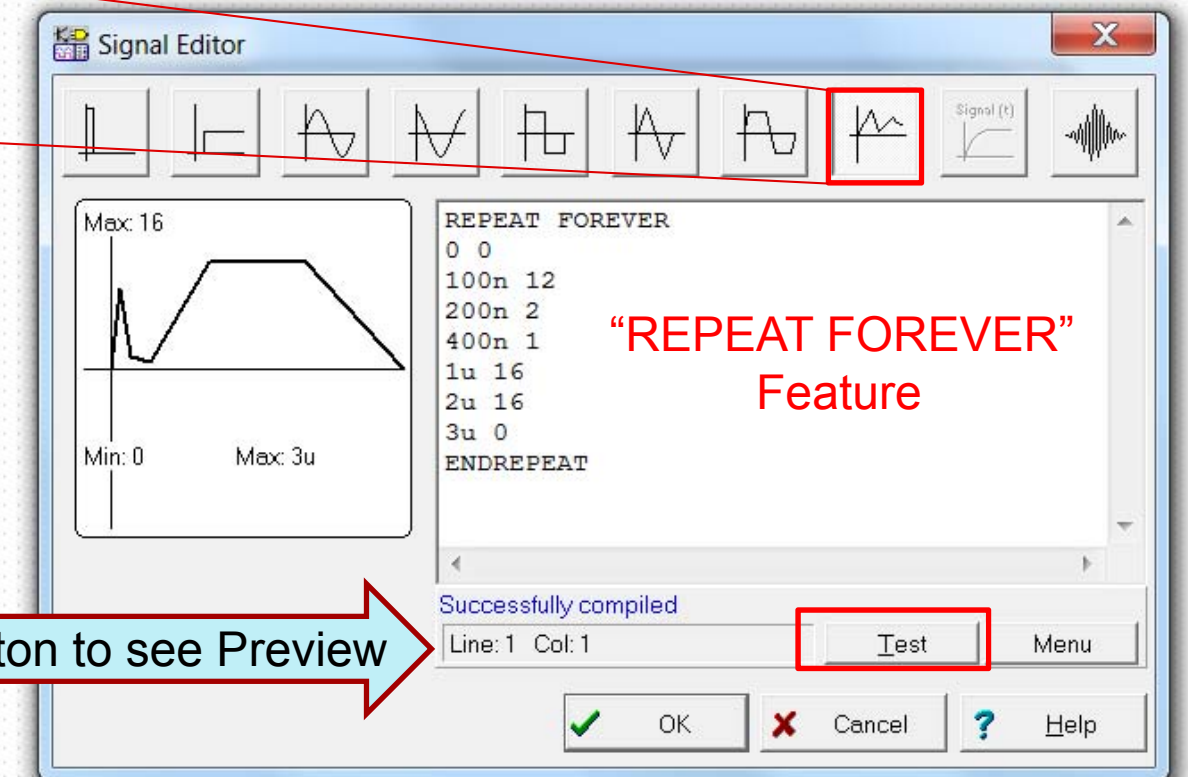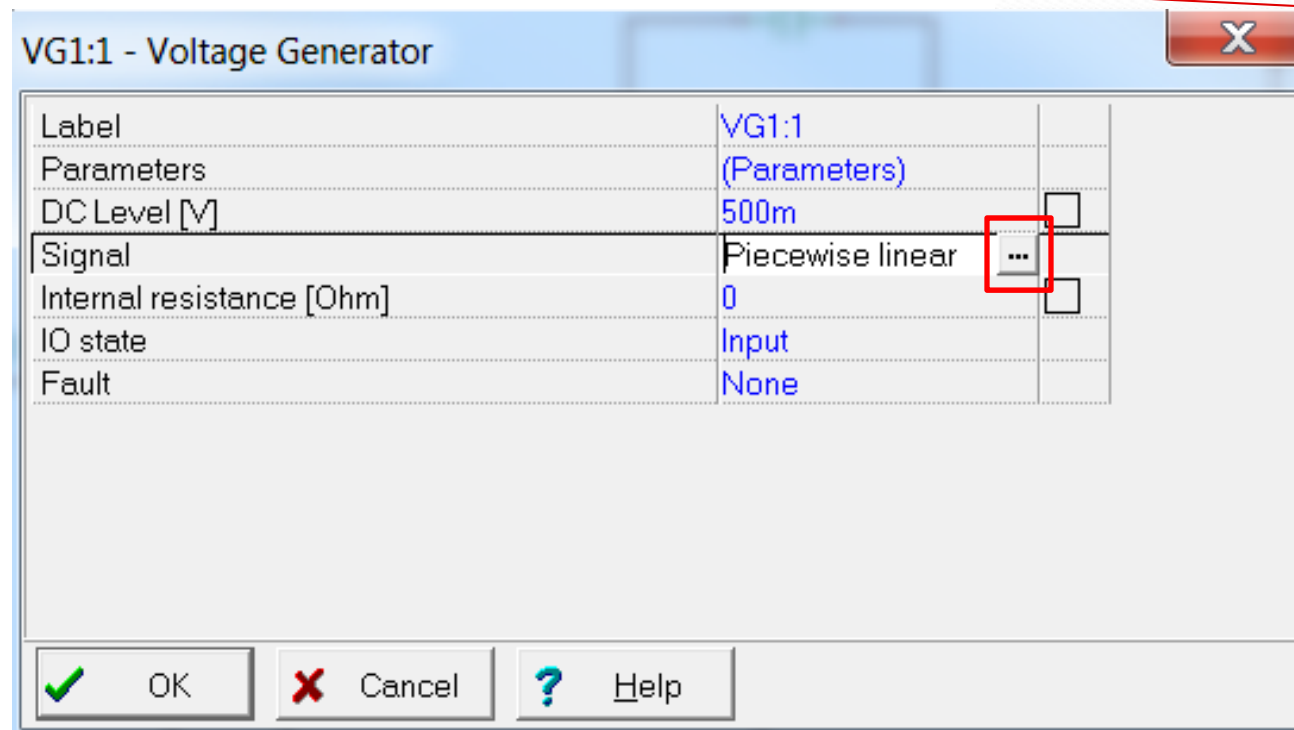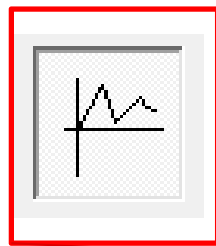- Double Click on “Vin” Voltage Generator Symbol
- Choose the  3 dots next to Signal
- Choose Piecewise Linear at Top
- Add in REPEAT FOREVER feature




Phase Delay Calculation

- Example Circuit:
 - “_OPA354 Circuit Phase Shift.TSC”
- Analysis → AC Transfer Characteristic → OK
- Delete VFB Curve
- User Cursor to check phase delay at 40kHz, result is 1.22 degrees lag



_OPA354 Circuit Phase Shift.TSC


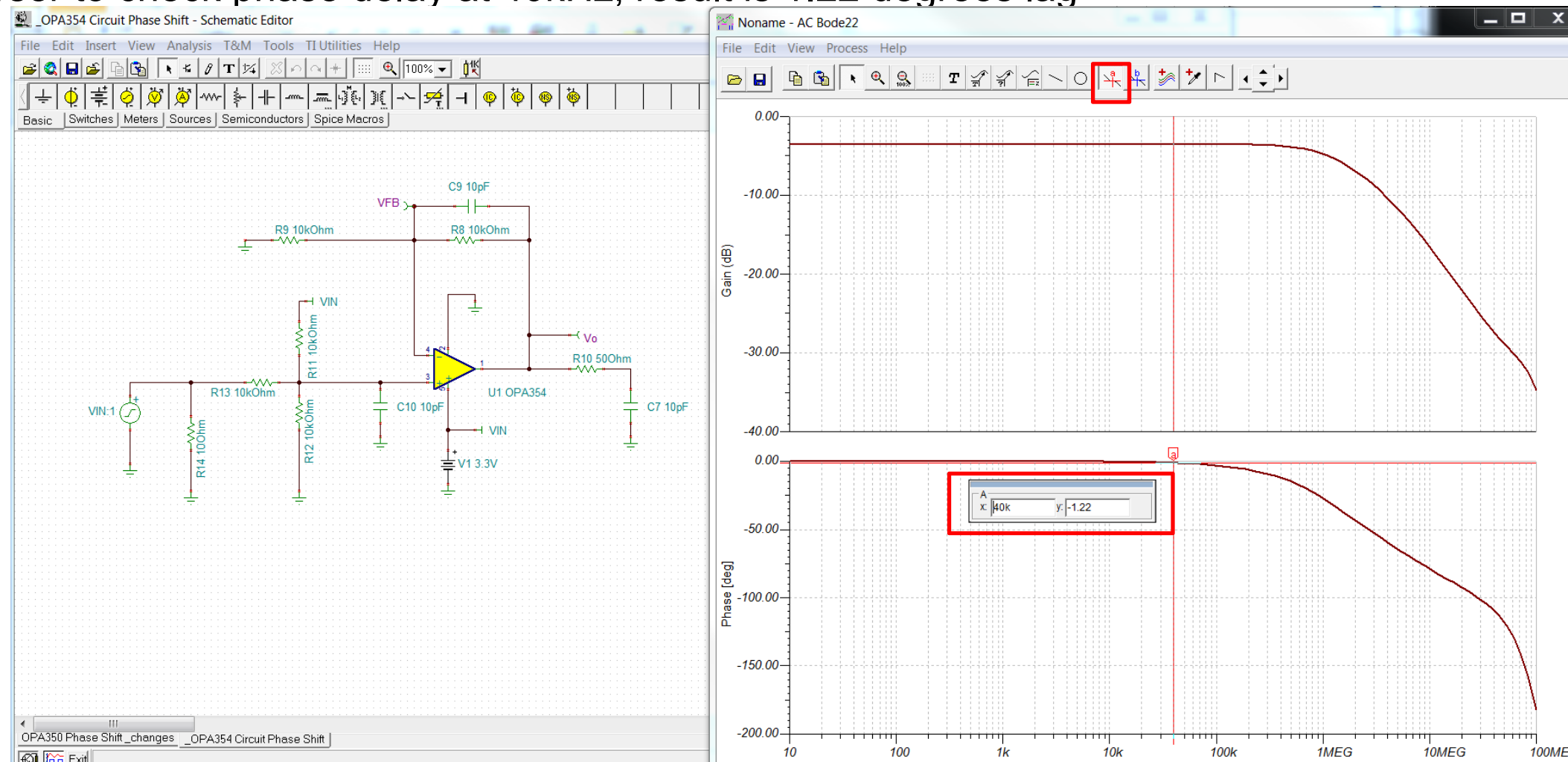


Stability Calculation – OPA354 (1 of 2)

- Example Circuit:
 - “_OPA354 Stability.TSC”
- Add in 1TF capacitor and 1TH Inductor into Feedback Loop
- Add Voltage Generator VG1
- Analysis → AC Analysis → AC Transfer Characteristic → OK



_OPA354 Stability Measurement.TSC

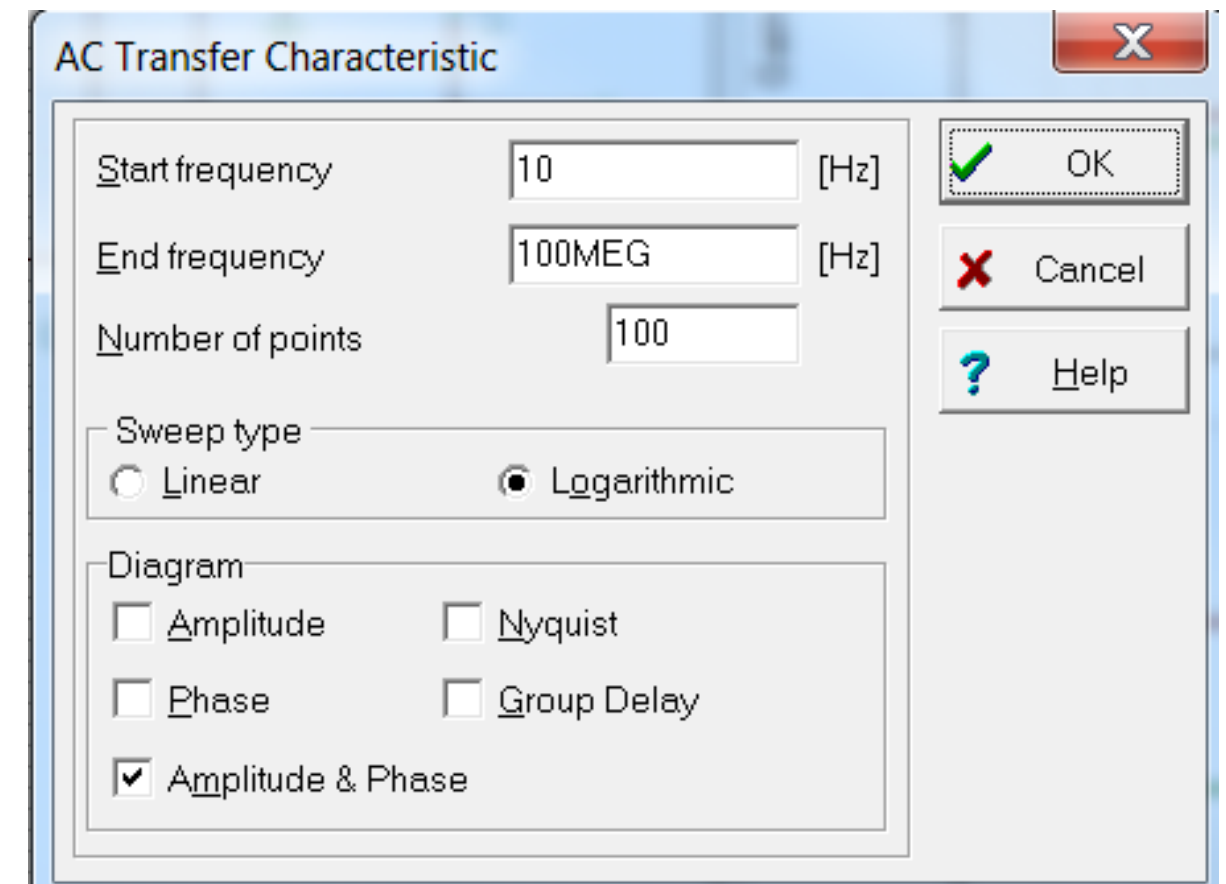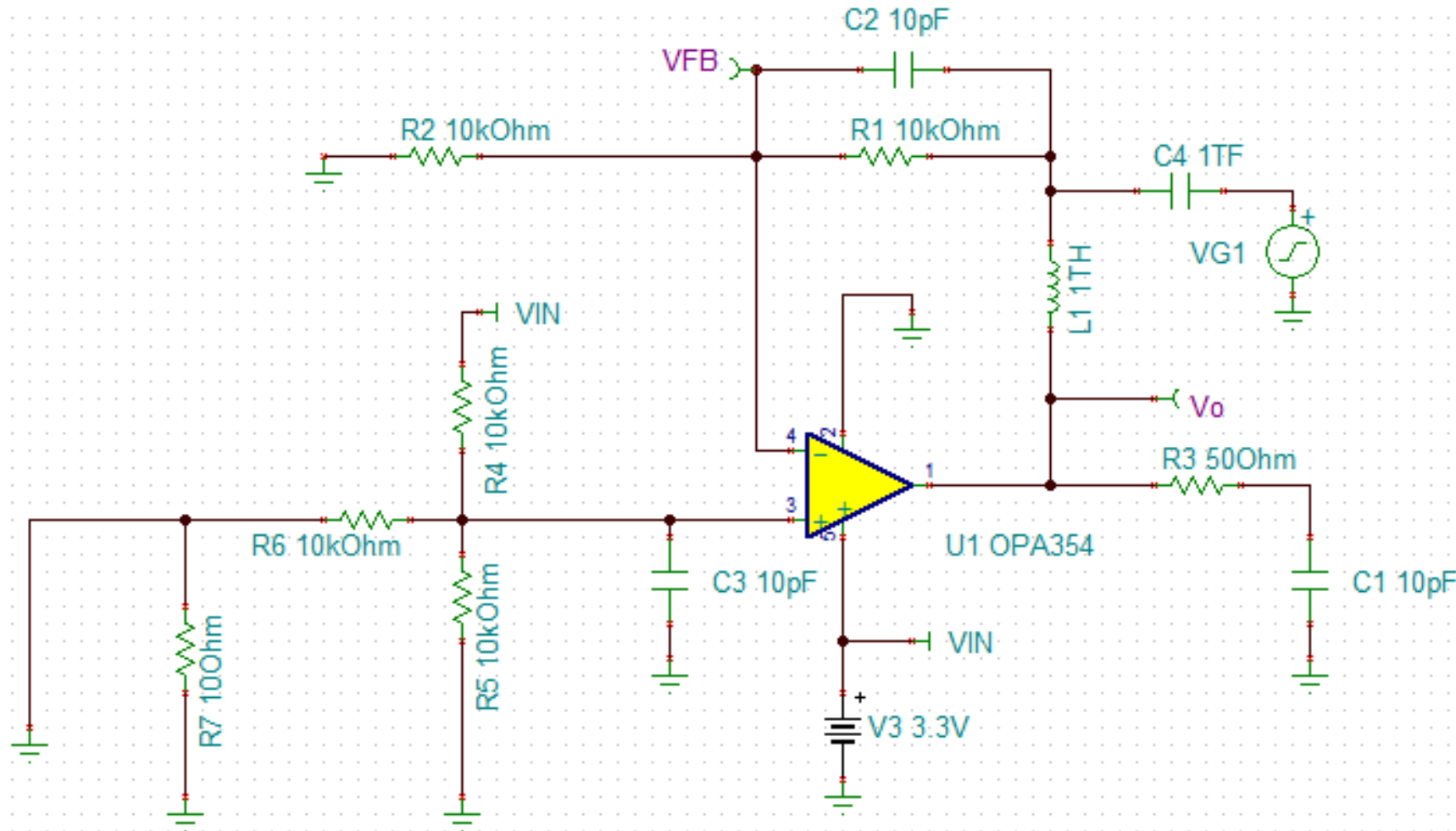


Stability Calculation – OPA354 (2 of 2)

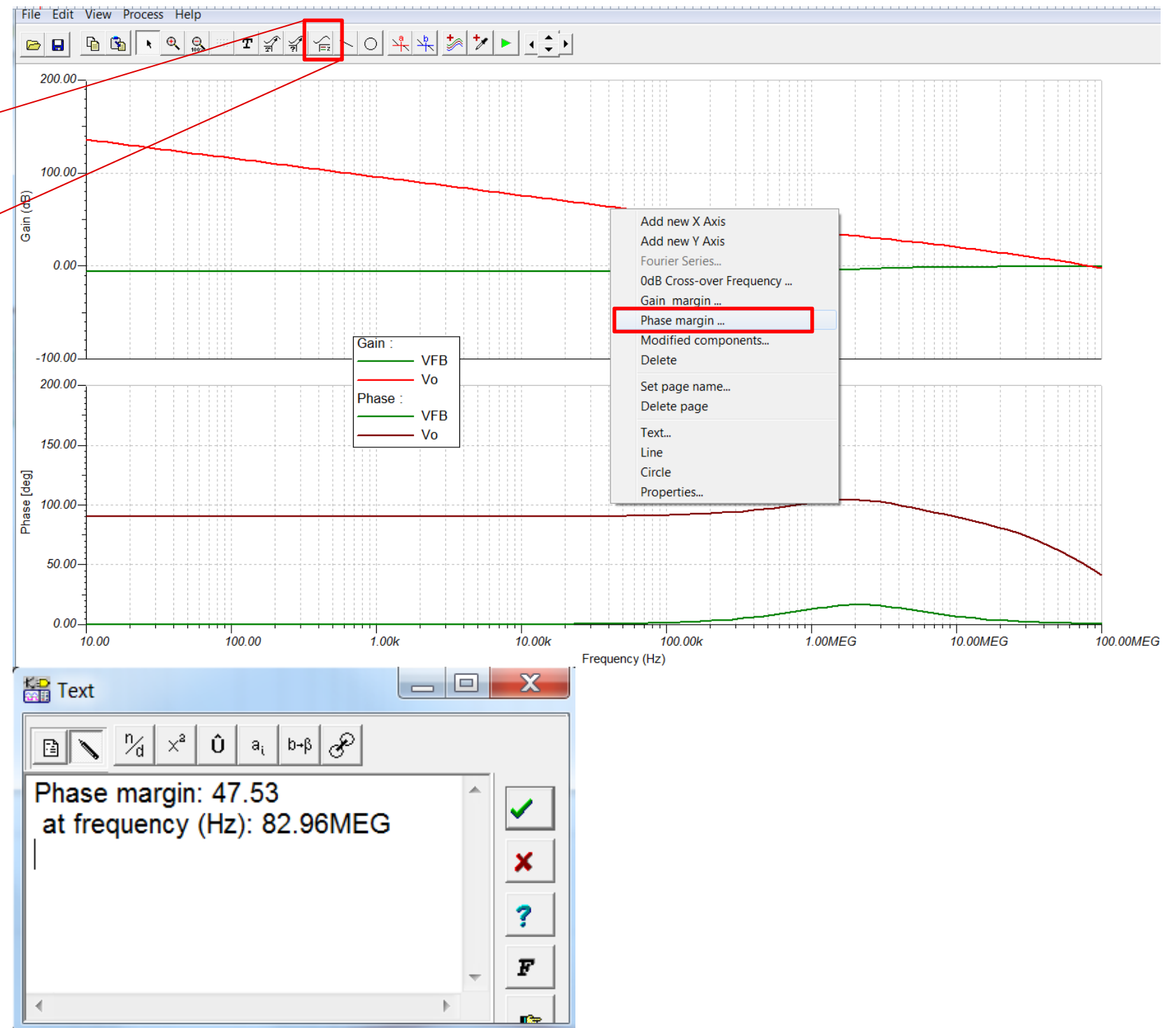- Example Circuit:
 - “_OPA354 Stability.TSC”
- Add
 - Use Legend Feature and Delete: VFB and Vo curves.
 - Choose Legend Feature
 - Delete **Phase** Curves for: Aol, OneOverBeta, VFB
 - Choose Vo Curve from top of Legend “**Gain**”
 - Separate Curves
 - Collect Curves (now see Vo Phase from 40 – 110)
 - Right Click and Choose “Phase margin...”
 - Box will display showing Calculated Phase Margin




**Right Mouse Button
“Phase margin” Feature**


Add new X Axis
Add new Y Axis
Fourier Series...
0dB Cross-over Frequency ...
Gain margin ...
Phase margin ...
Modified components...
Delete
Set page name...
Delete page
Text...
Line
Circle
Properties...



Post Processor Function (1 of 2)

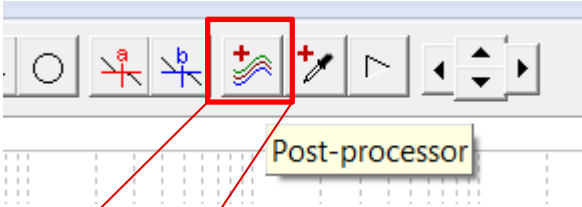

Choose Post Processor Feature

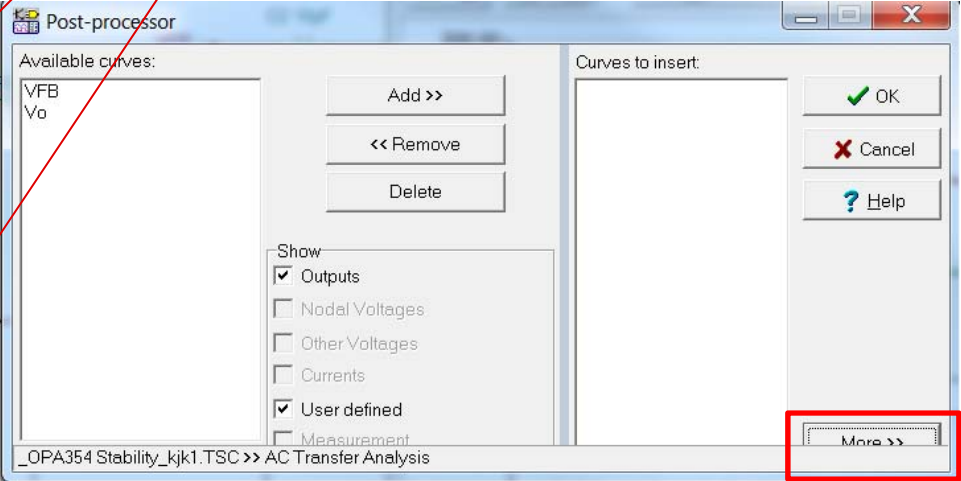

Post-processor

Available curves:

VFB
Vo

Add >>
<< Remove
Delete


Show

☒ Outputs
☐ Nodal Voltages
☐ Other Voltages
☐ Currents
☒ User defined
☐ Measurement

Curves to insert:

OK
Cancel
Help

More >>







Post Processor Button
In Results Window

MORE
Button

Choose "More >>"

Post Processor Function (2 of 2)

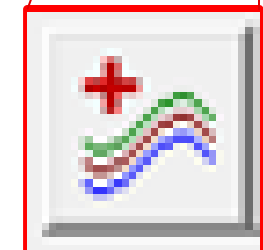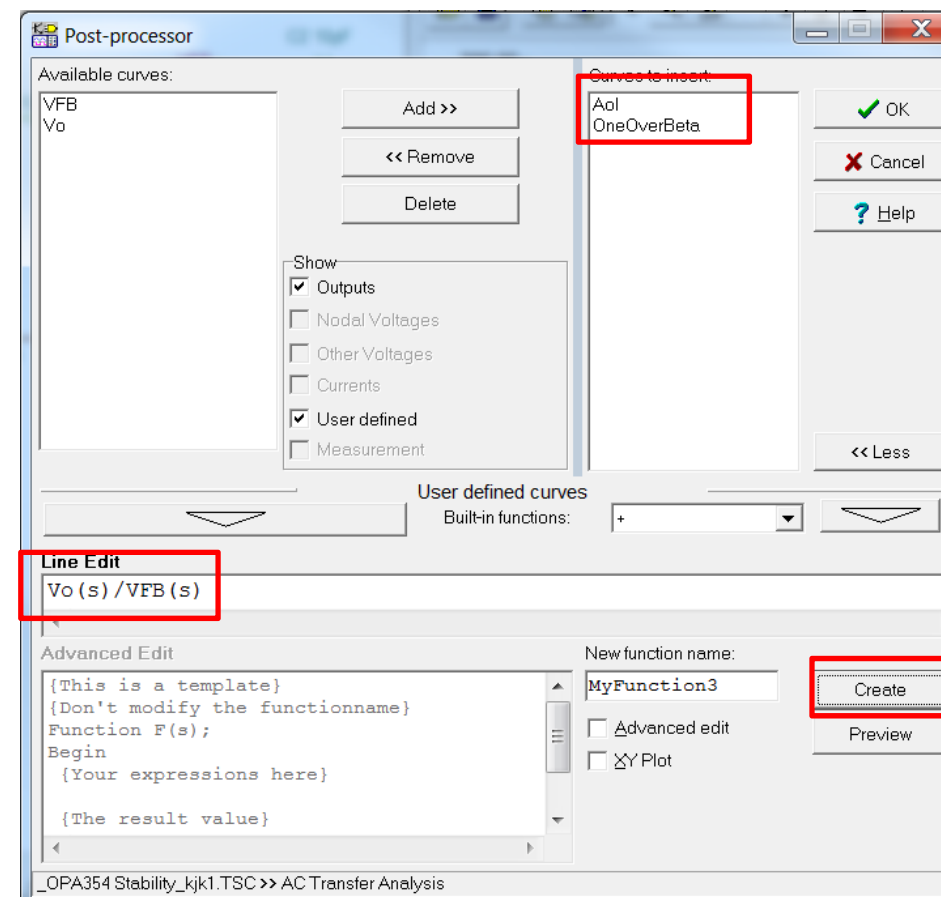
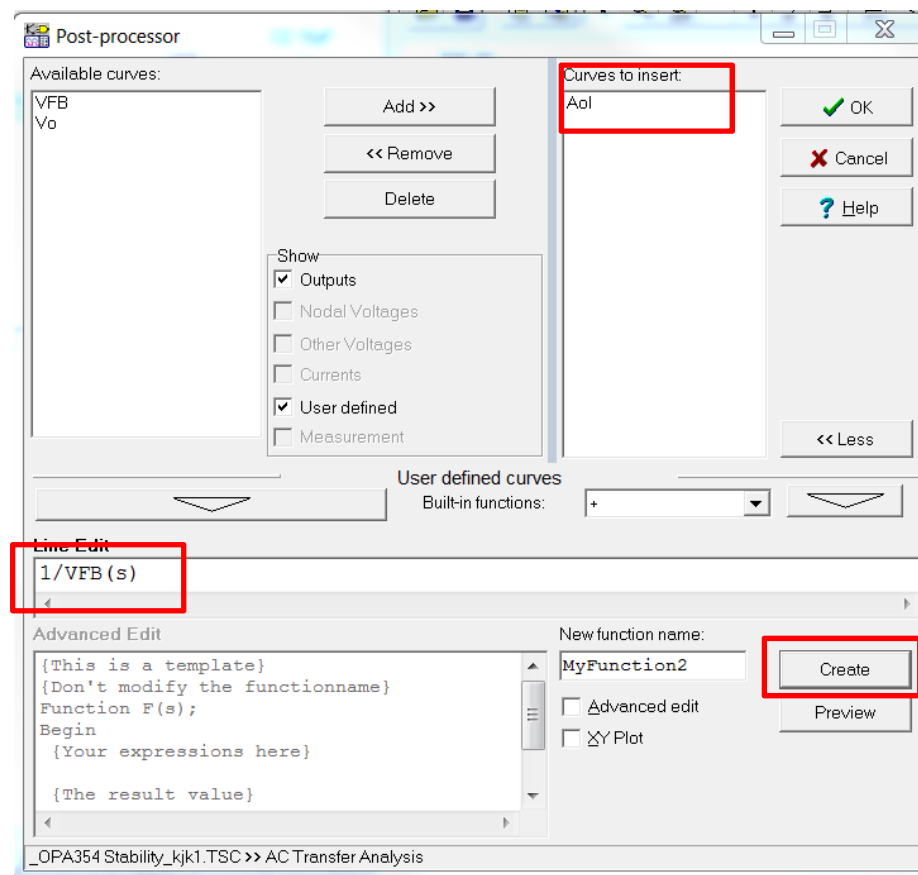
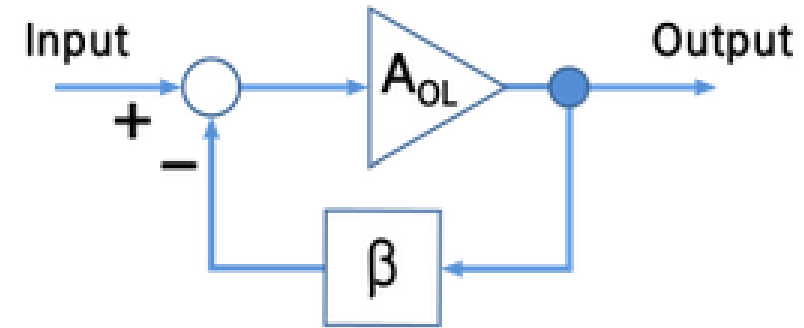
- Example Circuit:
 - “_OPA354 Stability.TSC”
- Add Calculations
 - Open Loop Gain $A_{OL} = 1/VFB(s)$
 - Closed Loop Gain Curve $1/\beta = V_o(s)/VFB(s)$ (Tina does not allow a “1” to start, so name “OneOverBeta”)
 - V_o is loop gain = $A_{OL} \times \beta$
- STEPS: Line Edit “ $1/VFB(s)$ ”, New function Name “ A_{OL} ” → Create
Line Edit “ $V_o(s)/VFB(s)$ ”, New function Name “OneOverBeta” → Create






Post Processor Button
In Results Window

Noise Analysis

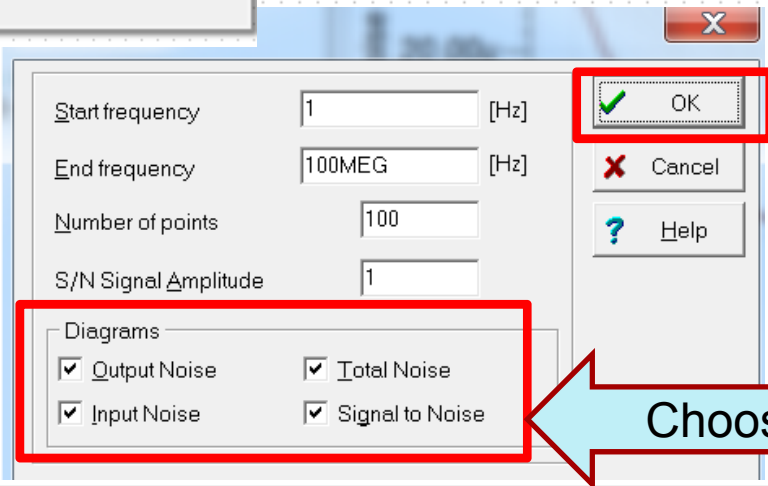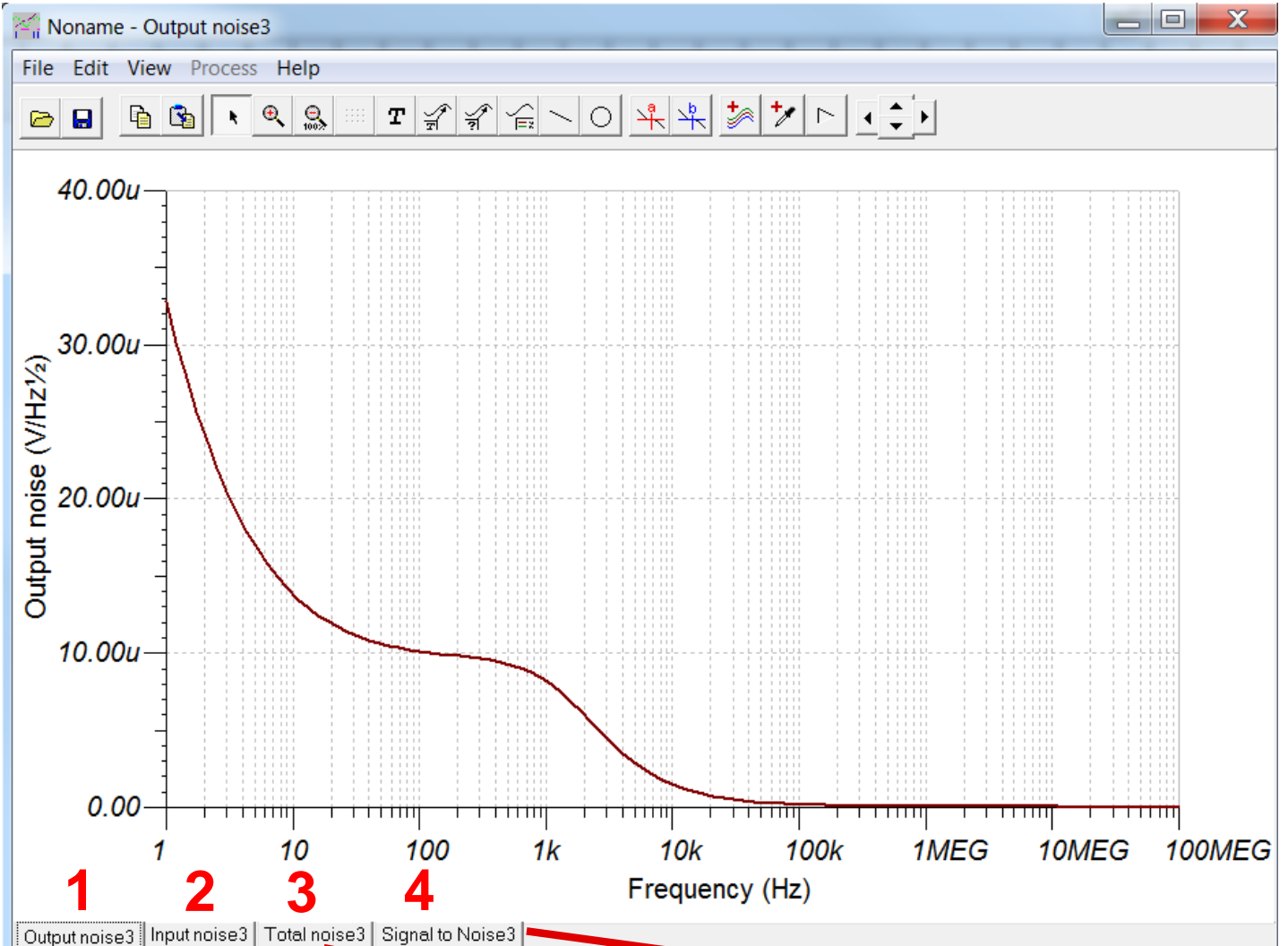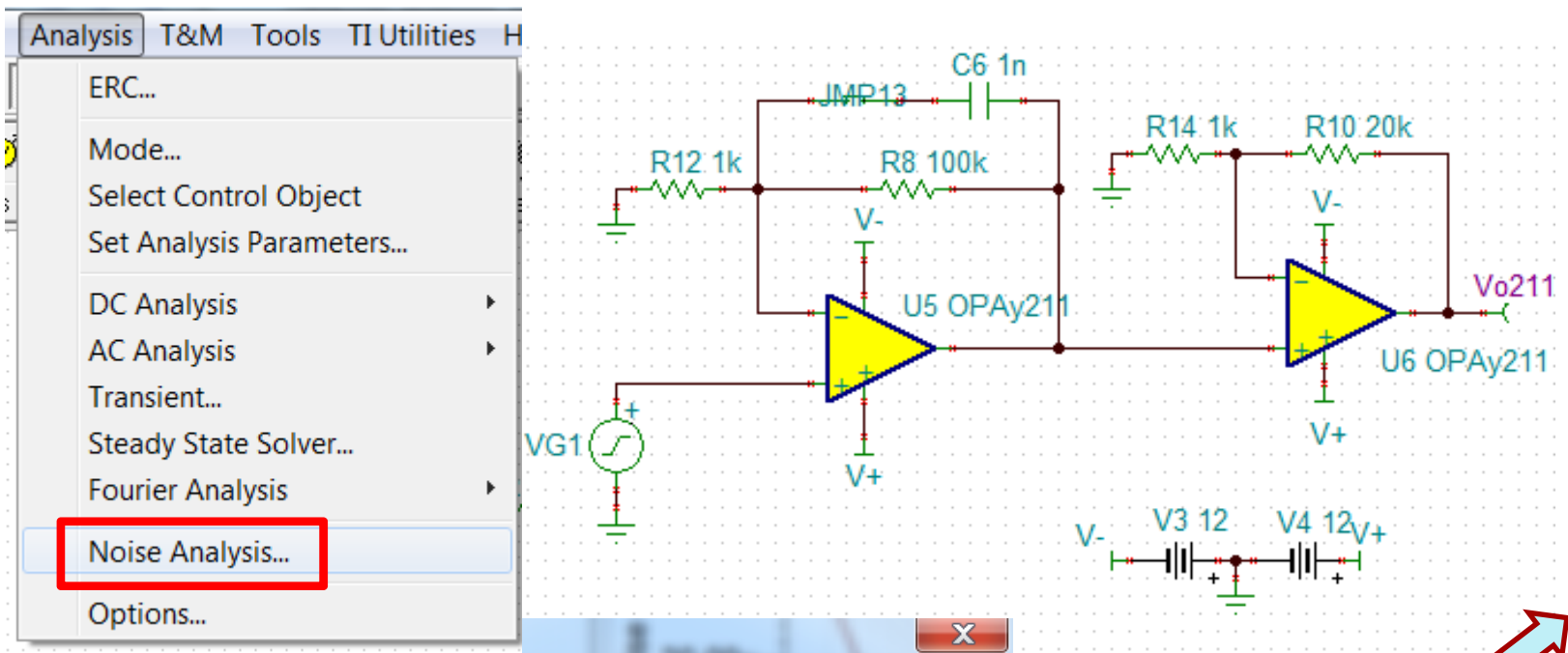- Example Circuit:
 - “05 - Noise - OPA211.TSC”
- Analysis → Noise Analysis → OK
- **4 Results** Are Calculated



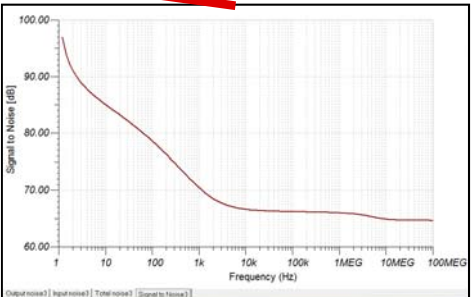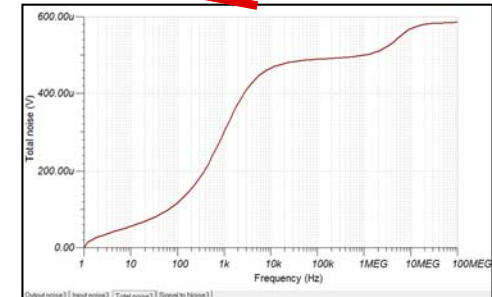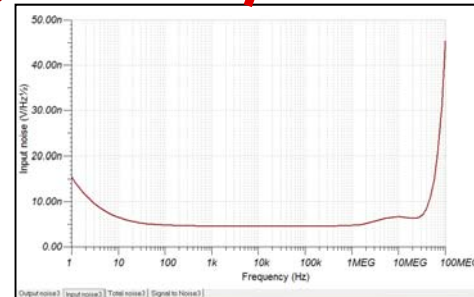


Choose all 4 check boxes





Adding & Removing Variable Sweep Feature



To Add Component Parameter Sweep

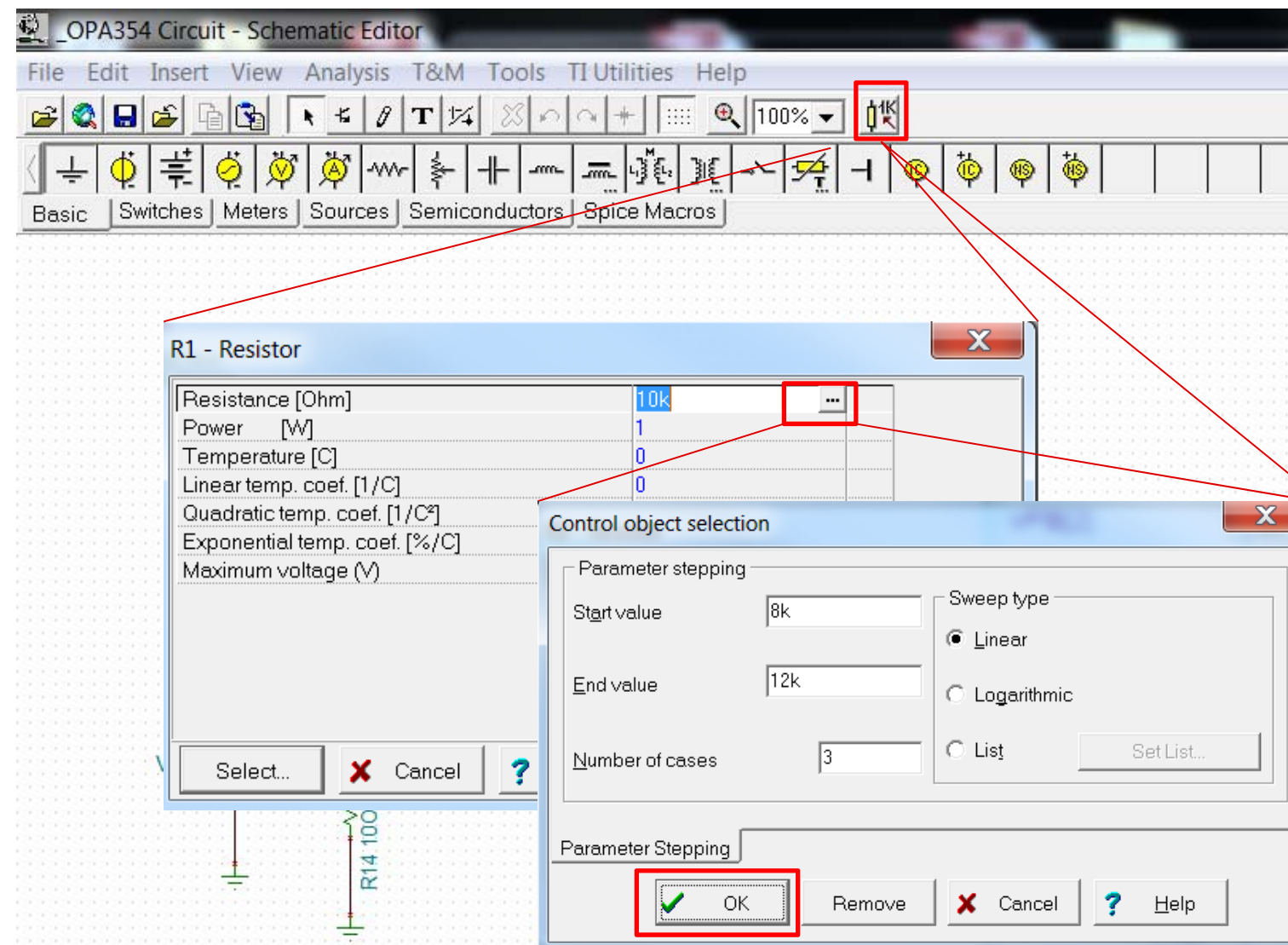1. Example Circuit: “_OPA354 Circuit.TSC”
2. Click on  button next to zoom.
3. Click on  and choose Start/End/Number of Cases



To Remove Component Parameter Sweep

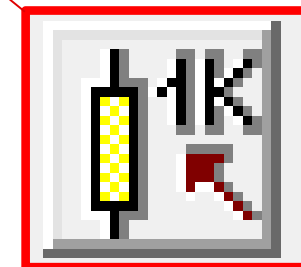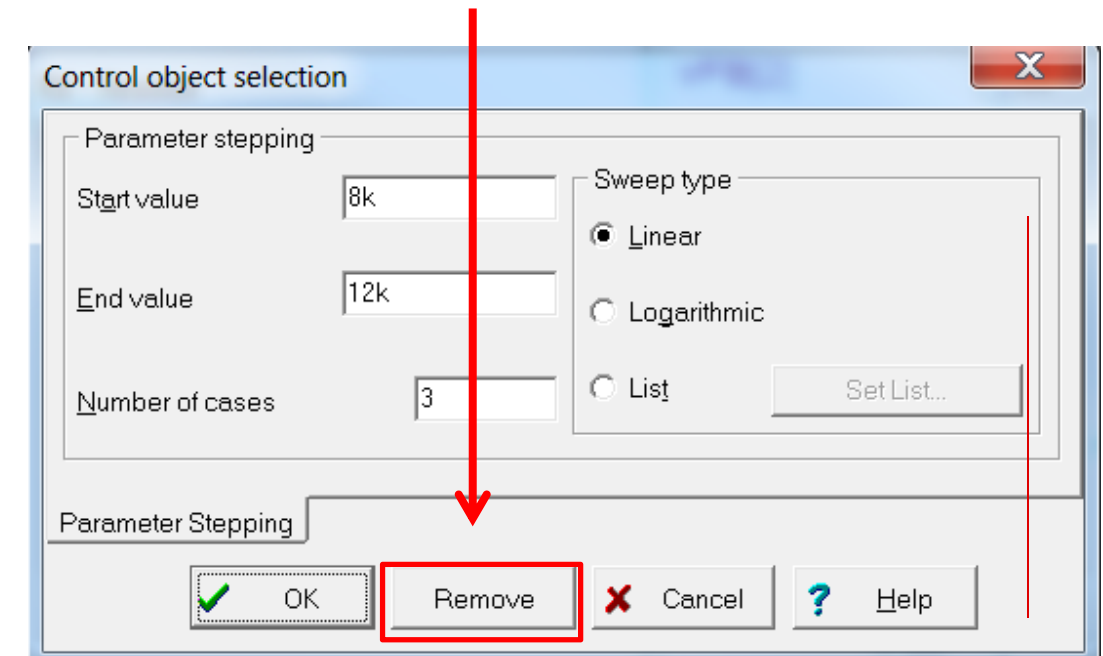
1. Follow the same steps to get to “Control object selection”  → 
2. Press “Remove”



Variable Sweep Button

Double Click on Axis to Change Settings

- Double Click on Axis Values to Change

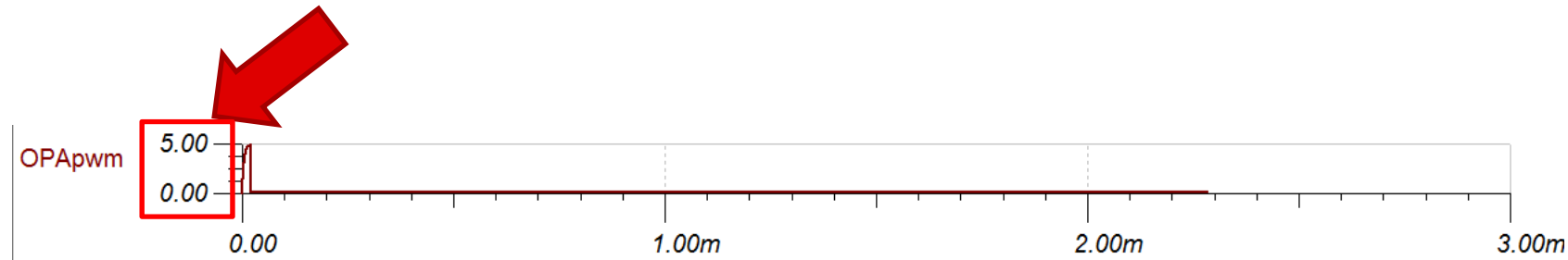


The 'Set Axis' dialog box is shown. It has three sections: Label, Numbers, and Scale. The Label section shows 'Text: OPApwm' and 'Font: Arial Size: 12 Style: Normal'. The Numbers section shows 'Format: Engineering: 1k', 'Divide by factor: 1', 'Precision: 2', and 'Font: Arial Size: 12 Style: Italic'. The Scale section shows 'Linear' as the scale type, 'Lower limit: 0', 'Upper limit: 5', and 'Ticks: 2'. There are checkboxes for 'Force size settings when resize window' (unchecked) and 'Round axis scale' (checked). A red arrow points to the 'Upper limit' field.

Op Amp to Drive SAR Converter

- Analysis → Transient → OK
- View → S




SAR drive with OPA320.TSC

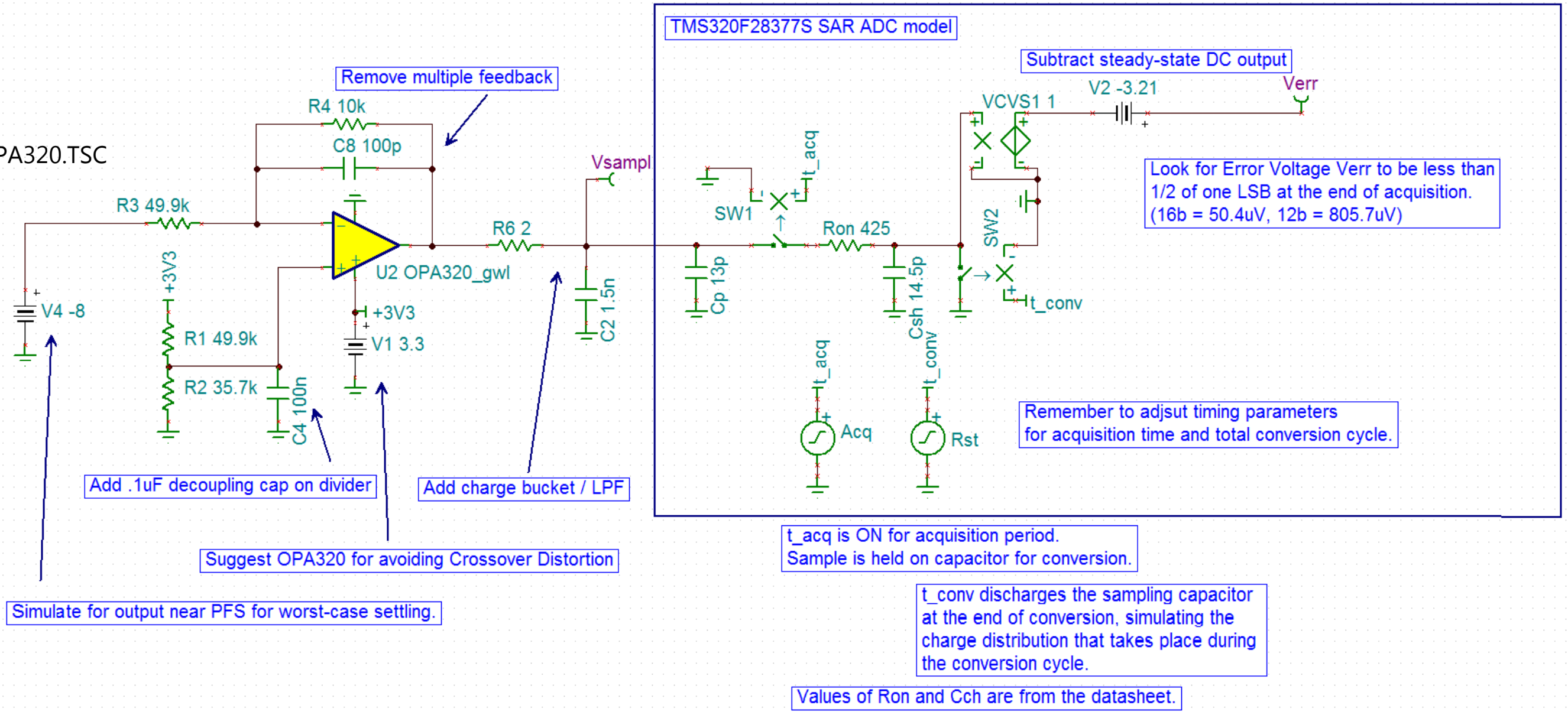

Flyback Converter using UCC28C44 – Transient Model

- Example Circuit: _UCC28C44 Flyback.TSC
- Standard Flyback Converter with Optocoupler Feedback.
- Includes UCC PWM controller, Transformer, Vref TL431 and Opto-coupler

 _UCC28C44 Flyback.TSC

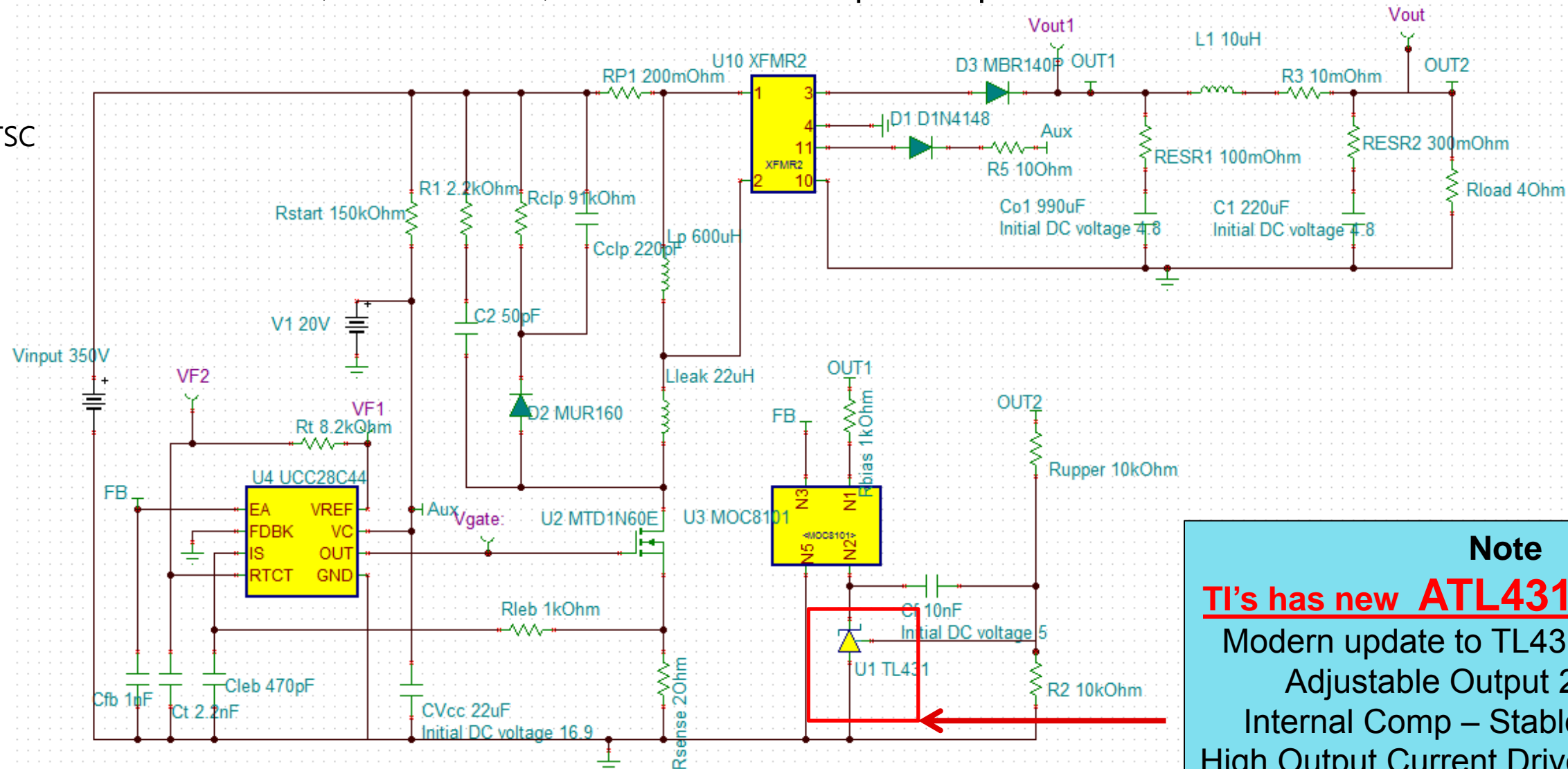


Note

TI's has new **ATL431** and **ATL432**

Modern update to TL431, TLV431, etc.
Adjustable Output 2.5 – 36Vin
Internal Comp – Stable with no Cap
High Output Current Drive 35uA – 100mA
Min Cathode Current for Reg = 35uA

Lots of Example Circuits

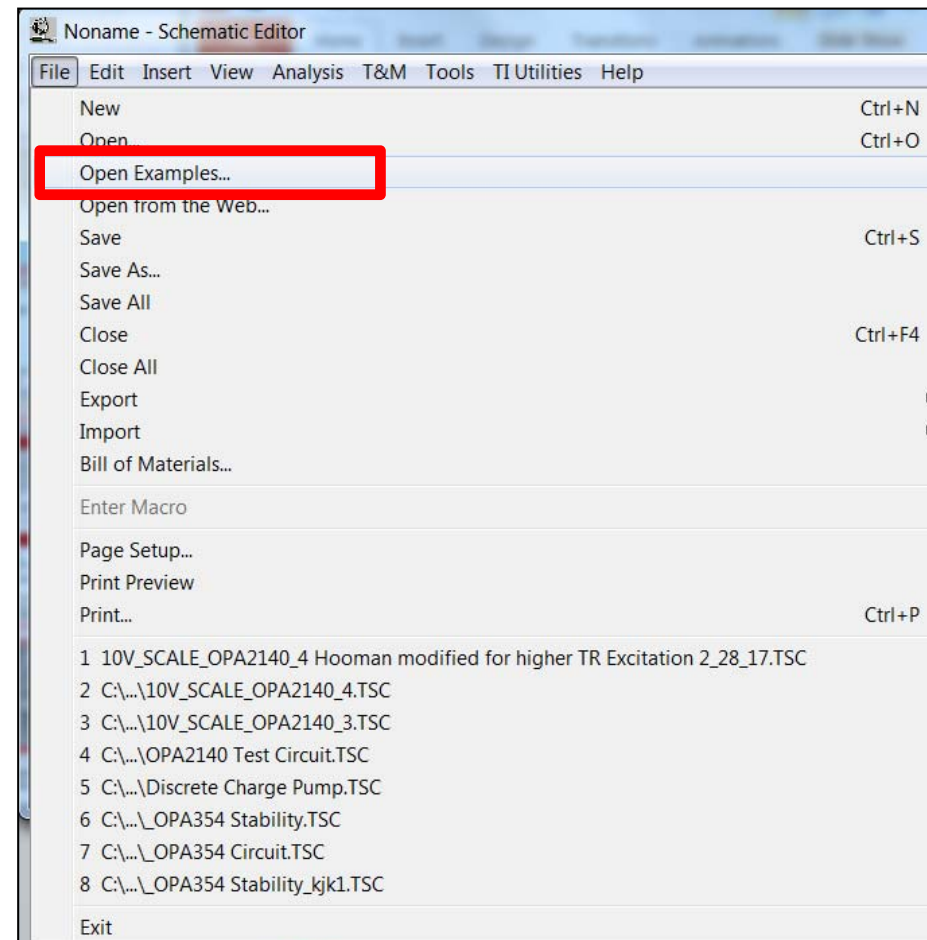- In TINA-TI Examples Folder C:\Program Files (x86)\DesignSoft\Tina 9 - TI\EXAMPLES
- TI's online E2E Forum Community
- The circuits and models provided in this training



- Cap Load Comp
- Comparator
- Control Loop
- Current Loop
- Current Measurement
- DAC
- Difference Amps
- Filters_FilterPro
- Filters_Others
- Misc
- Noise Sources
- NSC Test Circuits
- Oscillators
- Power Amps
- Precision
- RTD Simulator
- Sensor_Condition
- Signal_Process
- Single Supply
- Smmps
- SPICE
- TI Test Circuits
- Transimpedance
- Voltage_to_Current
- WAV file examples
- WIDEBAND

TI Precision Labs Training Online

- TINA-TI Video Training Series: <https://training.ti.com/tina-ti-video-training-series>
- Webench Power Designer Training Series: <https://training.ti.com/webench%C2%AE-power-designer-training-series>
- Webench Filter Designer Video: <https://training.ti.com/webench%C2%AE-filter-designer-video>




1. TINA-TI Training Series			
Multiple Video courses showing how to use TINA-TI to solve Engineering problems with			
#	🔒	Title	Duration
1.1		Introduction to TINA-TI(TM) Simulator	07:30
1.2		Using the TINA-TI(TM) simulator – ERC and Analysis types	07:03
1.3		Configuring Sources in TINA-TI(TM) simulator	06:31
1.4		TINA-TI(TM) Waveform Viewer, Part 1	07:12
1.5		TINA-TI(TM) Waveform Viewer, Part 2	05:32
1.6		Sweeping parameters in TINA-TI(TM) simulator	04:15
1.7		Noise, Fourier analysis and Signal Chain content in TINA-TI(TM) simulator	06:04
1.8		Power product simulation in TINA-TI(TM) simulator	08:23
1.9		Importing SPICE models into TINA-TI(TM) simulator	05:21
1.10		Tips and Tricks for TINA-TI(TM) simulator	12:54
1.11		How to use the Controlled Source Wizard in the TINA-TI(TM) simulator	06:51
1.12		Using WEBENCH® simulation export to create files for TINA-TI(TM) simulator	06:43

1. WEBENCH® Power Designer Training Series			
#	🔒	Title	Duration
1.1		Learn WEBENCH® Power Series Overview	03:19
1.2		Starting WEBENCH® Power Designer	01:43
1.3		WEBENCH® Visualizer - Filtering	04:09
1.4		WEBENCH® Visualizer - Charting	02:17
1.5		WEBENCH® Optimizer Dial	05:14
1.6		WEBENCH® Power Designer	03:12
1.7		Viewing Your Schematic with WEBENCH® Power Designer	02:23
1.8		Viewing the BOM with WEBENCH® Power Designer	03:35
1.9		Using WEBENCH® Power Designer to View Operating Values and Charts	04:10
1.10		Optimize Circuit Design with WEBENCH® Power Designer	02:28
1.11		Electrical Simulation in WEBENCH® Power Designer	04:22
1.12		Thermal Simulation with WebTHERM™ Simulation	03:38
1.13		Creating Documentation with WEBENCH® Power Designer	01:57
1.14		Exporting from WEBENCH® Power Designer	01:30
1.15		Sharing Designs with WEBENCH® Power Designer	01:29

WEBENCH® Filter Designer Video		
This video series takes you through Filter Designer and all its features inclu		
Table of contents		
1. Videos		
1. Videos		
#	Title	Duration
1.1	Select, Design, Analyze	04:29
1.2	Lowpass Filter Selection	04:52
1.3	Filter Designer Visualizer	04:20
1.4	Filter Designer Design Summary	04:17
1.5	Highpass Filter Selection	05:16
1.6	Bandpass Filter Selection	05:26
1.7	Bandstop or Notch Filter Selection	05:43
1.8	Simulation Tool	05:59
1.9	Selecting Filter Order	04:18
1.10	Group Delay Step Response Specifications	05:42

How to Import a .TSM file ?

- Insert → Macro → find .TSM file → Open

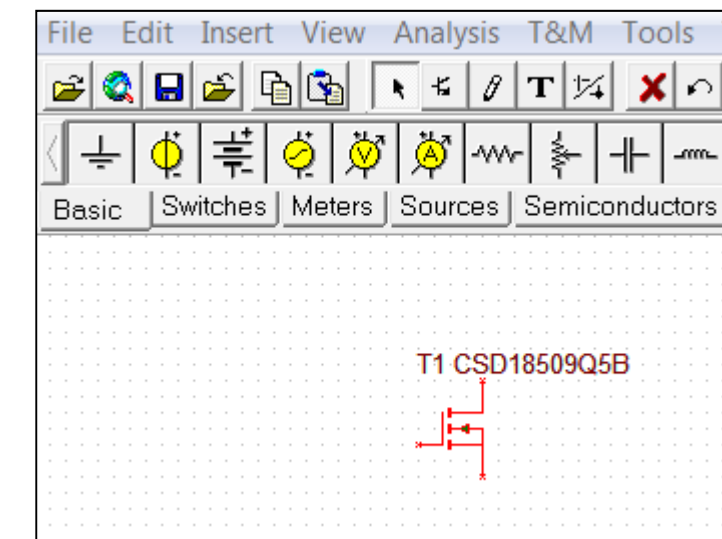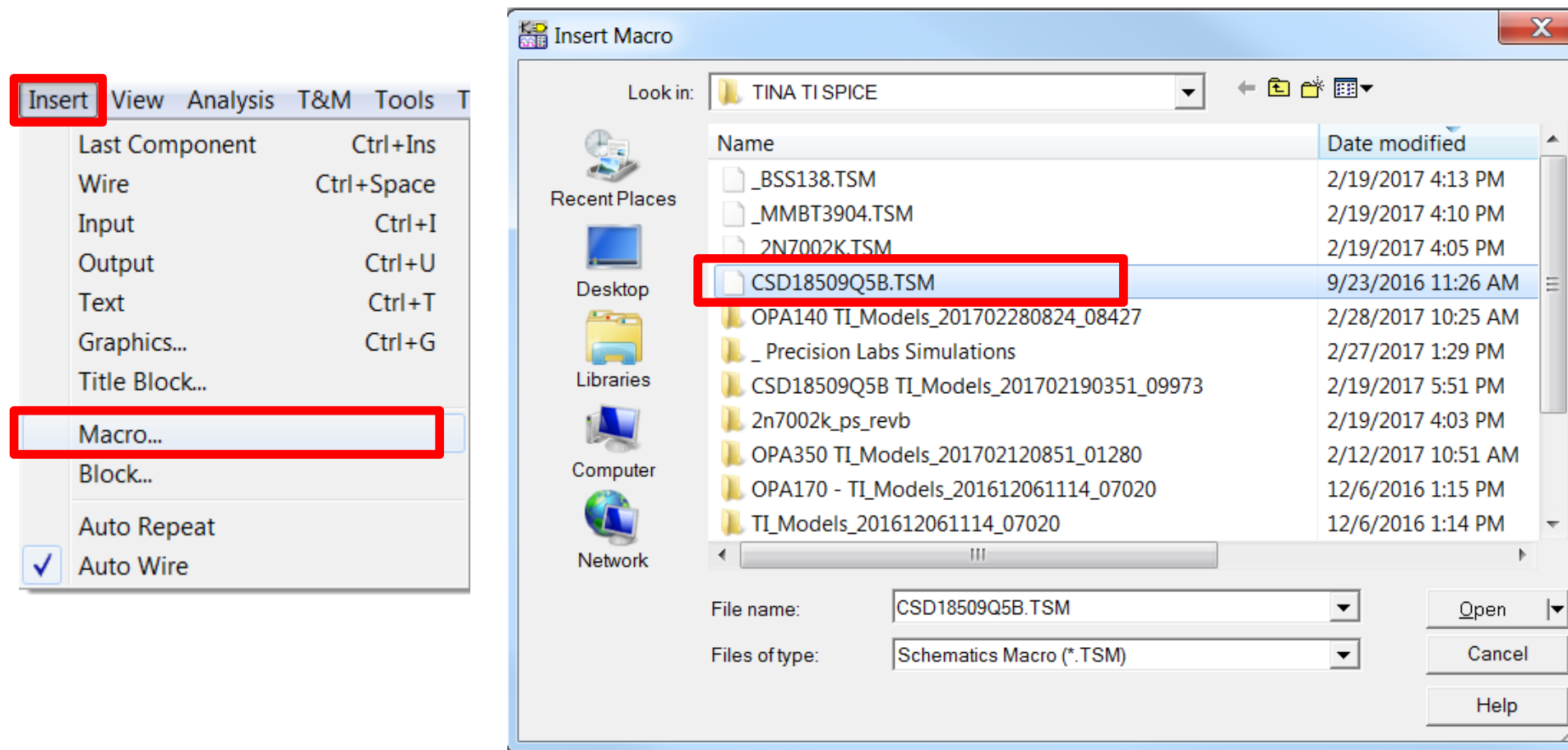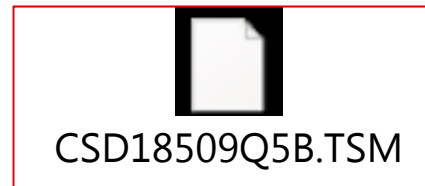

Where can you find SPICE Models?

www.ti.com/spicerack

TEXAS INSTRUMENTS

WEBENCH® SpiceRack Device Model Search

WEBENCH Design Center

Show models released from 07/27/1998 to 02/24/2017

Search

Help

Download Selected (0)


☐ Show only selected

13208 Results found

<input type="checkbox"/>	TI Part	Part Description	Model Description	Family Tree	Release Date
<input type="checkbox"/>	74AC16244	16-Bit Buffers And Line Drivers With 3-State Outputs	Revision 74AC16244 IBIS Model (Rev. A)	Logic-->Buffer/Driver/Transceiver-->Non-Inverting Buffer/Driver	2003-Sep-10
<input type="checkbox"/>	74SSTUB32864A	25-Bit Configurable Registered Buffer with SSTL_18 Inputs and Outputs	Hspice_SSTUB32864A_Encrypted.zip	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Mar-26
<input type="checkbox"/>	74SSTUB32864A	25-Bit Configurable Registered Buffer with SSTL_18 Inputs and Outputs	Revision SSTUB32864A IBIS ZKE1 Model (Rev. A)	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Jul-2
<input type="checkbox"/>	74SSTUB32865	28-Bit to 56-Bit Registered Buffer with Address-Parity Test	74SSTUB32865 IBIS Model	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Dec-3
<input type="checkbox"/>	74SSTUB32865A	28-Bit to 56-Bit Registered Buffer with Address-Parity Test	74SSTUB32865A IBIS Model	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Dec-3
<input type="checkbox"/>	74SSTUB32866A	25-Bit Configurable Registered Buffer w/Address-Parity Test	Revision SSTUB32866A IBIS ZKE1 Model (Rev. A)	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Jul-2
<input type="checkbox"/>	74SSTUB32866A	25-Bit Configurable Registered Buffer w/Address-Parity Test	Hspice_SSTUB32866A_Encrypted.zip	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Mar-26
<input type="checkbox"/>	74SSTUB32868A	28-Bit to 56-Bit Registered Buffer with Address-Parity Test	74SSTUB32868A IBIS Model	Clock and Timing-->Memory Interface Clocks and Registers-->DDR2 Register	2007-Aug-23
<input type="checkbox"/>	ACF2101	Low Noise, Dual Switched Integrator	ACF2101 PSpice Model	Amplifiers-->Operational Amplifiers (Op Amps)-->Precision Op Amps	2000-Oct-25
<input type="checkbox"/>	ADC07D1520	7-Bit, Dual 1.5-GSPS or Single 3.0-GSPS Analog-to-Digital Converter (ADC)	ADC07D1520 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Aug-27
<input type="checkbox"/>	ADC081000	High Performance, Low Power 8-Bit, 1 GSPS A/D Converter	ADC081000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC081500	8-Bit, 1.5-GSPS Analog-to-Digital Converter (ADC)	ADC081500 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC083000	8-Bit, 3.0-GSPS Analog-to-Digital Converter (ADC)	ADC083000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC08D1000	8-Bit, Dual 1.0-GSPS or Single 2.0-GSPS Analog-to-Digital Converter (ADC)	ADC08D1000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC08D1500	8-Bit, Dual 1.5-GSPS or Single 3.0-GSPS Analog-to-Digital Converter (ADC)	ADC08D1500 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC08D1520	8-Bit, Dual 1.5-GSPS or Single 3.0-GSPS Analog-to-Digital Converter (ADC)	ADC08D1520 IBIS MODEL	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2015-Sep-15
<input type="checkbox"/>	ADC08D502	Dual-Channel, 8-Bit, 500-MSPS Analog-to-Digital Converter (ADC)	ADC08D502 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Oct-9
<input type="checkbox"/>	ADC10D020	Dual-Channel, 10-Bit, 20-MSPS Analog-to-Digital Converter (ADC)	ADC10D020 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC10D040	Dual-Channel, 10-Bit, 40-MSPS Analog-to-Digital Converter (ADC)	ADC10D040 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC10D1000	10-Bit, Dual 1.0-GSPS or Single 2.0-GSPS Analog-to-Digital Converter (ADC)	ADC10D1000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC12D1000	12-Bit, Dual 1.0-GSPS or Single 2.0-GSPS Analog-to-Digital Converter (ADC)	ADC12D1000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14
<input type="checkbox"/>	ADC12D1000RF	12-Bit, Dual 1.0-GSPS or Single 2.0-GSPS, RF Sampling Analog-to-Digital Converter (ADC)	ADC12D1000 IBIS Model	Data Converters-->Analog-to-Digital Converters (ADCs)-->High Speed ADCs (>10MSPS)	2012-Jan-14

How to Import a .LIB file ?

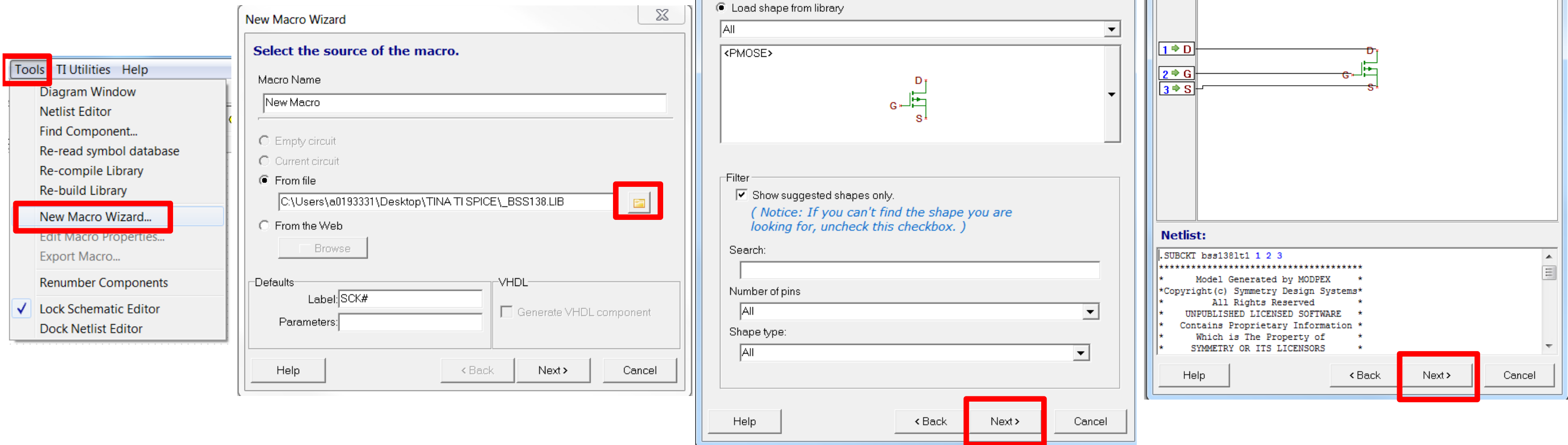- Tools → New Macro Wizard
- Press the Yellow Button and Choose your .LIB file.
- Chose Next, then Nexts again.
- Save off new .TSM file




The image shows a sequence of four screenshots from the TINA-TI software, illustrating the steps to import a .LIB file:

- Tools Menu:** The 'Tools' menu is open, and 'New Macro Wizard...' is highlighted with a red box.
- Select the source of the macro:** The 'New Macro Wizard' dialog is shown. Under 'Select the source of the macro', 'From file' is selected. The file path 'C:\Users\ao193331\Desktop\TINA TI SPICE_BSS138.LIB' is entered, and a yellow button icon is highlighted with a red box.
- Select the shape you want to assign:** The 'New Macro Wizard' dialog is shown. Under 'Select the shape you want to assign', 'Load shape from library' is selected. A diode symbol is shown in the list, and the 'Next >' button is highlighted with a red box.
- Netlist:** The 'New Macro Wizard' dialog is shown with the 'Netlist' tab selected. The netlist content is displayed, and the 'Next >' button is highlighted with a red box.

Will Not Converge / Need More Resolution

CONVERGENCE ISSUES

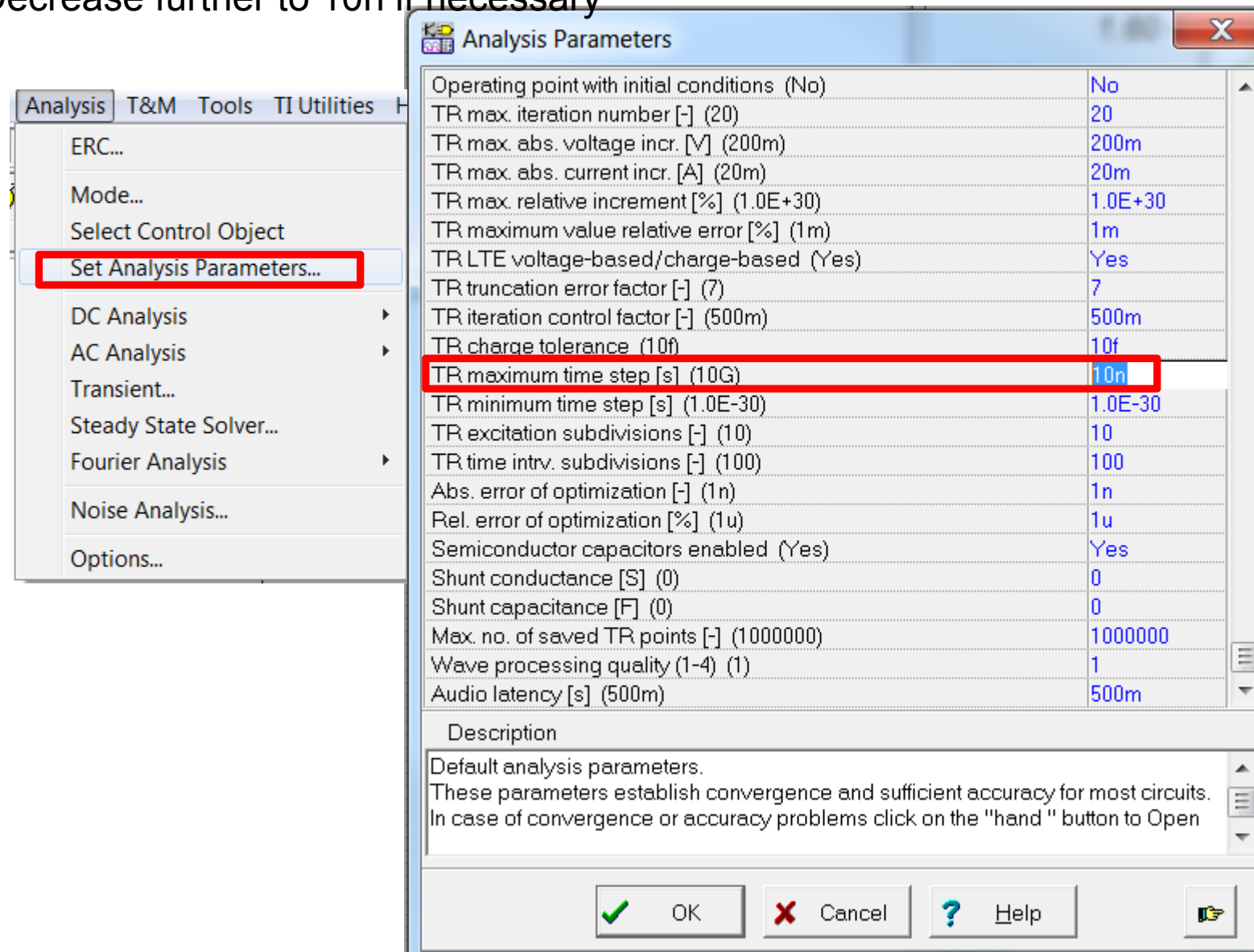- Go to Analysis → Ste Analysis Parameters → “TR maximum time step [s]”
 - Decrease from default 10G to 1u (to start)
 - Decrease further to 10n if necessary





Try 1u to start
Then go to 10n or more

Capacitor on Operation Amplifier Input Causes Convergence Error

CONVERGENCE ISSUES

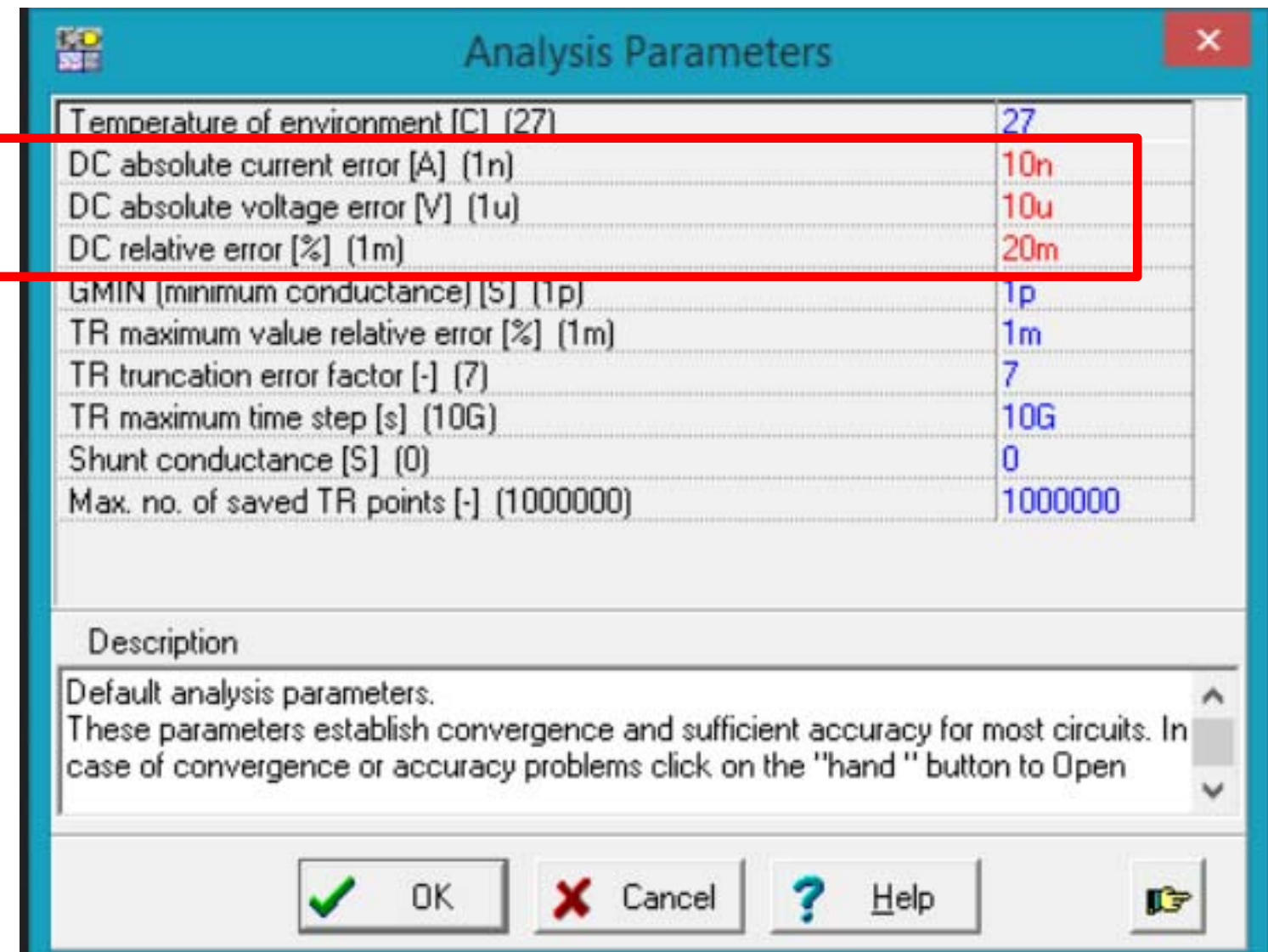
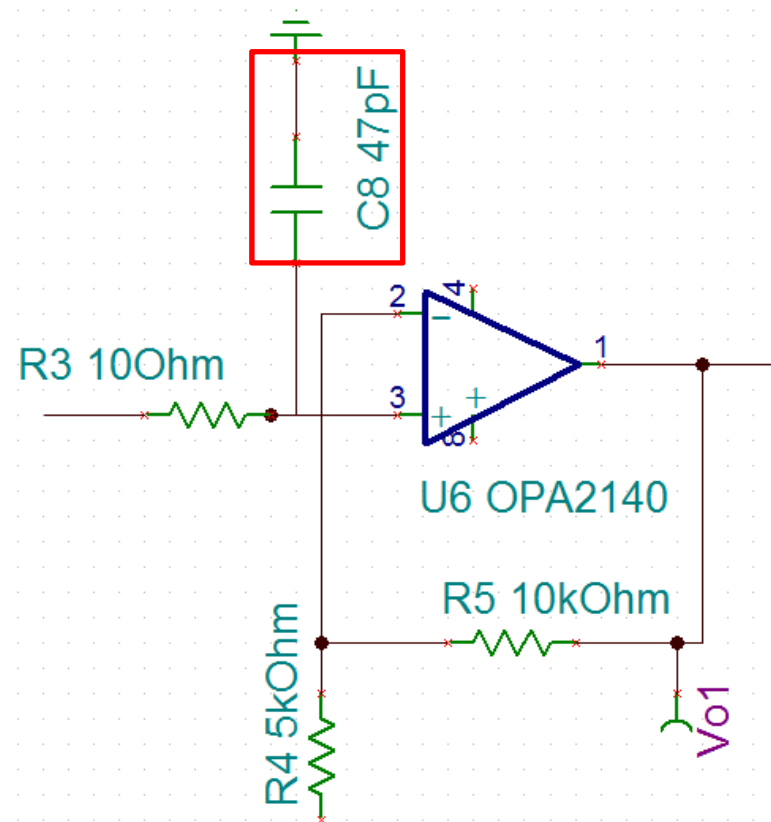
- Problem: Capacitor added to input of Operation Amplifier causes a Convergence Error.
- The problem is that due to the small capacitance value inserted, the program subdivides times steps in order to reach the required accuracy and the time step goes too low, which may cause numerical instability.
- Set Analysis Parameters
 - DC absolute current error [A] (1n) → set to 10n
 - DC absolute voltage error [V] (1u) → set to 10u
 - DC relative error [%] (1m) → set to 20m



Need More Memory?

CONVERGENCE ISSUES

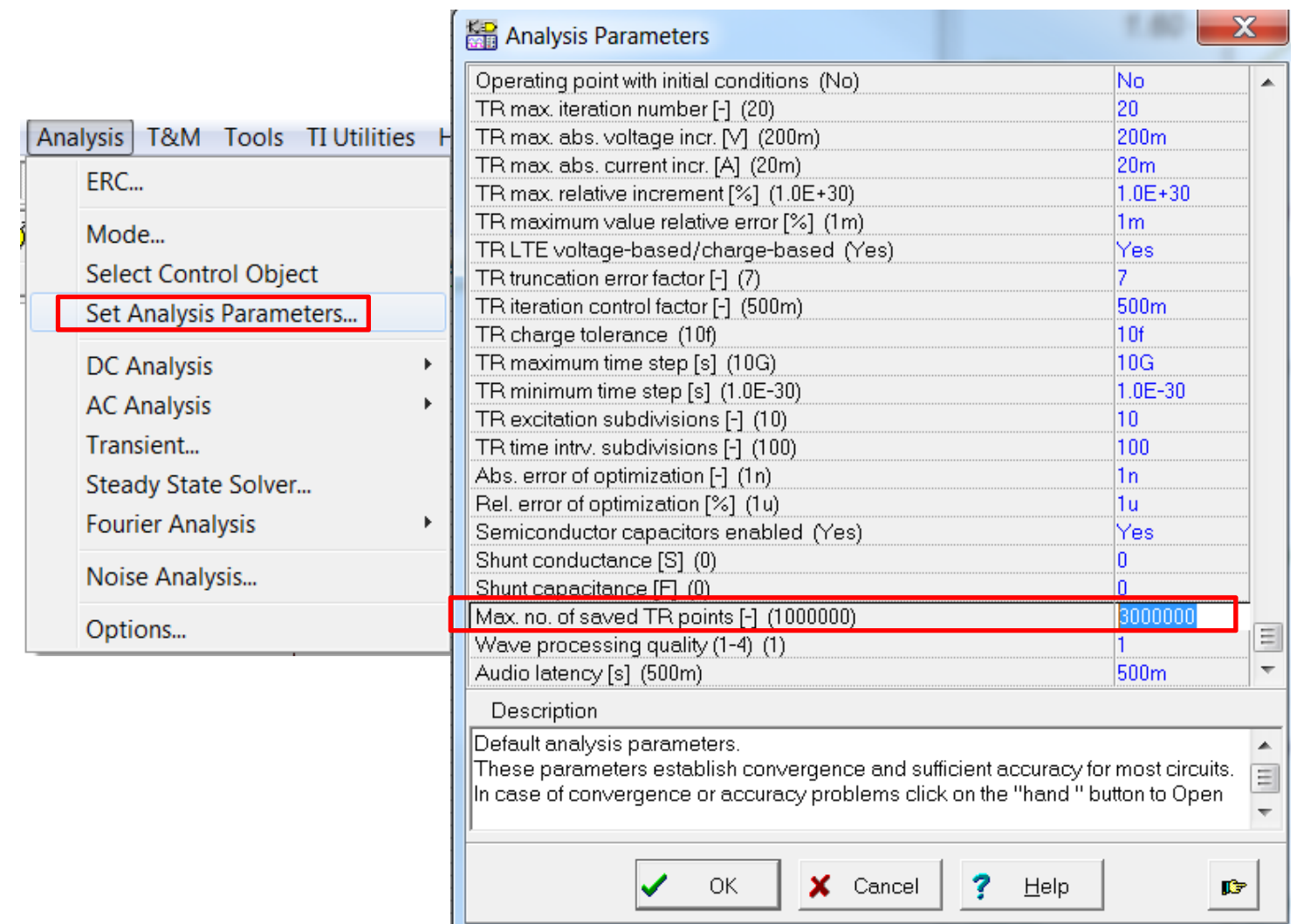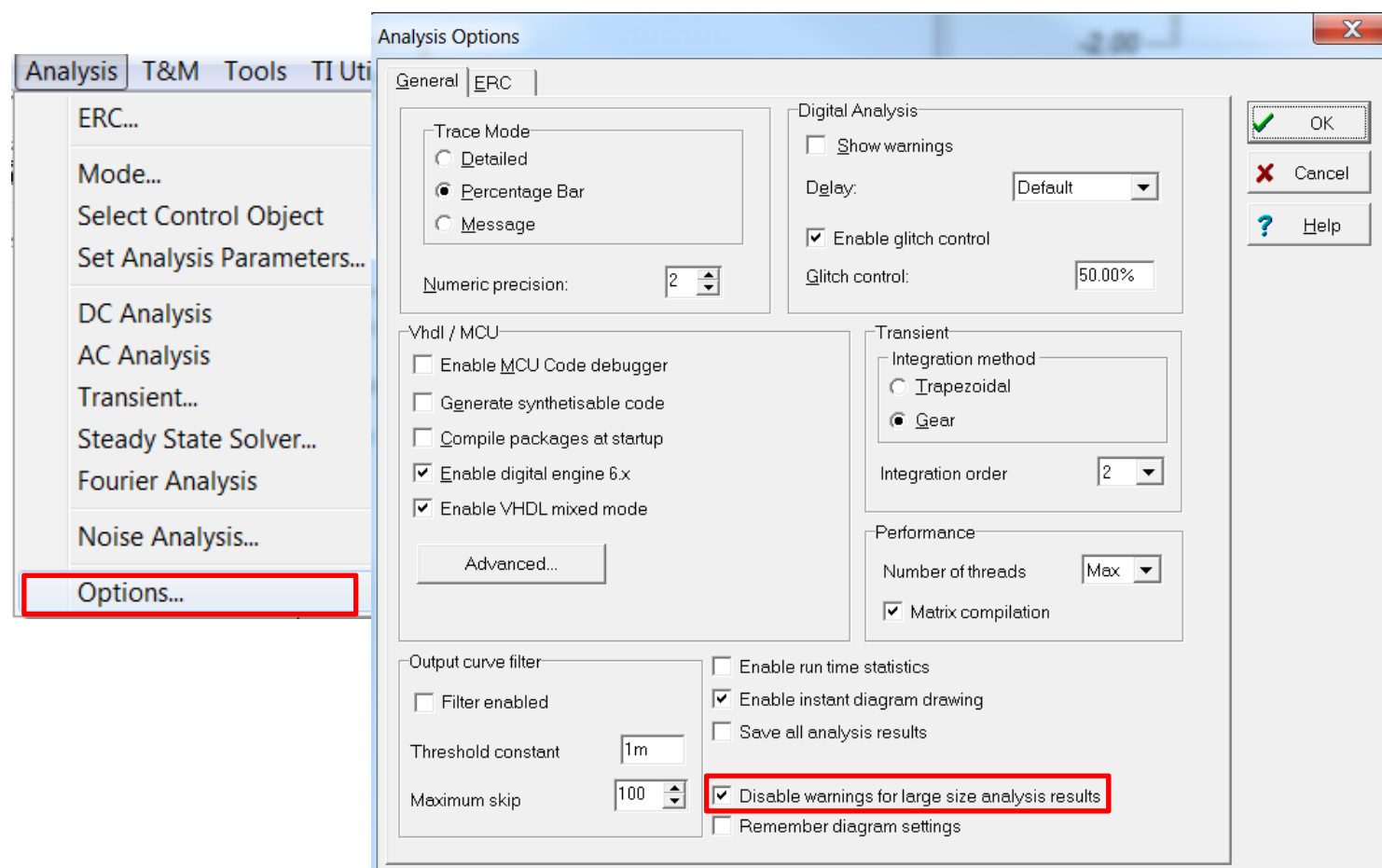- Analysis → Options ... → Check “Disable Warnings for Large Size...”
- Analysis → Set Analysis Parameters → Max no. of saved TR points
 - Increase to 3000000





Output Waveform is Truncated – Search our E2E Forums

CONVERGENCE
ISSUES

<http://e2e.ti.com>

- Square wave output of Signal Generator is truncated
- Solution is to change “**TR excitation subdivisions**” from default of 10 to 1000.
- Analysis → Set Analysis Parameters... → Scroll down to Bottom to find Parameter
- See all the details on this particular issue our E2E Forums:
http://e2e.ti.com/support/development_tools/webench_design_center/f/234/t/371450
- TI's E2E forums are the place to ask questions of TI applications engineers

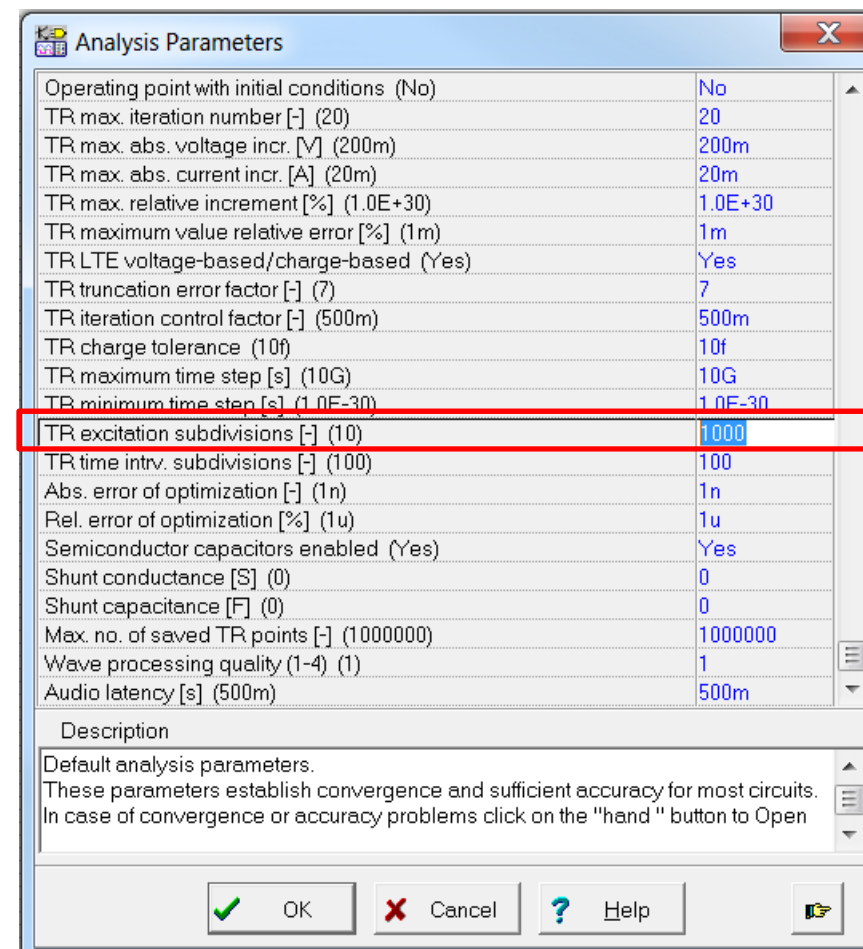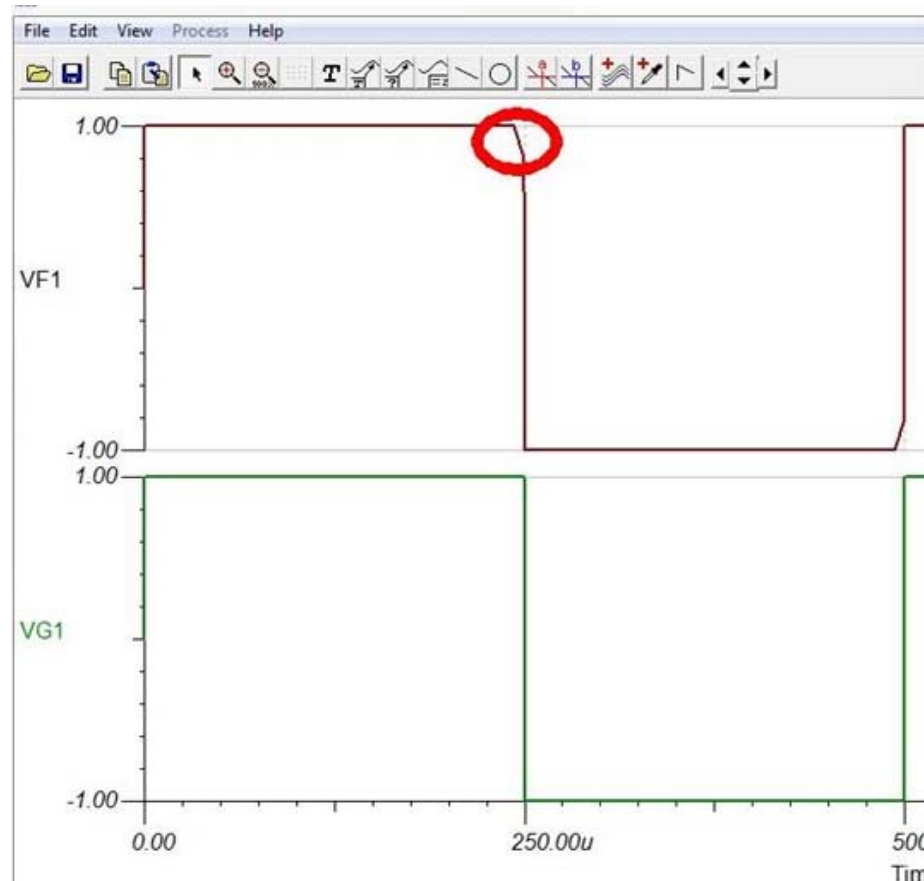

39



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com