

# AN ERROR ANALYSIS OF THE ISO102 IN A SMALL SIGNAL MEASURING APPLICATION

High accuracy measurements of low-level signals in the presence of high isolation mode voltages can be difficult due to the errors of the isolation amplifiers themselves.

This error analysis shows that when a low drift operational amplifier is used to preamplify the low-level source signal, a low cost, simple and accurate solution is possible.

In the circuit shown in Figure 1, a 50mV shunt is used to measure the current in a 500VDC motor. The OPA27 amplifies the 50mV by 200X to 10V full scale. The output of the OPA27 is fed to the input of the ISO102, which is a unity-gain isolation amplifier. The 5k $\Omega$  and 1k $\Omega$  potentiometers connected to the ISO102 are used to adjust the gain and offset errors to zero as described in the ISO102 data sheet.

## SOME OBSERVATIONS

The total errors of the op amp and the iso amp combined are approximately 0.6% of full-scale range. If the op amp had not been used to preamplify the signal, the errors would have been 74.4% of FSR. Clearly, the small cost of adding the op amp buys a large performance improvement.

After gain and offset nulling, the dominant errors of the iso amp are gain nonlinearity and power supply rejection. Thus, well regulated supplies will reduce the errors even further.

The rms noise of the ISO102 with a 120Hz bandwidth is only 0.18mVrms, which is only 0.0018% of the 10V full-scale output. Therefore, even though the  $16\mu V/\sqrt{Hz}$  noise spectral density specification may appear large compared to other isolation amplifiers, it does not turn out to be a significant error term. It is worth noting that even if the bandwidth is increased to 10kHz, the noise of the iso amp would only contribute 0.016% FSR error.

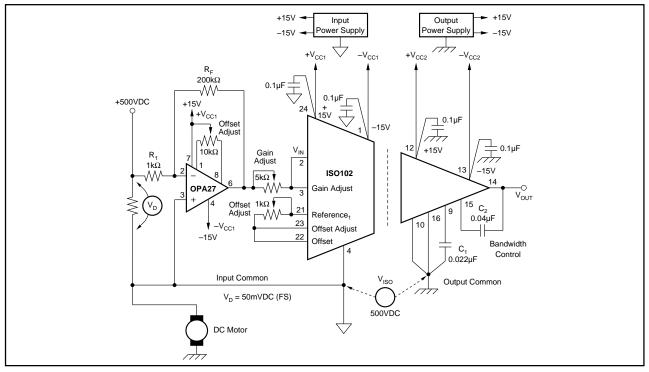


FIGURE 1. 50mV Shunt Measures Current in A 500VDC Motor.

The information provided herein is believed to be reliable; however, BURR-BROWN assumes no responsibility for inaccuracies or omissions. BURR-BROWN assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. BURR-BROWN does not authorize or warrant any BURR-BROWN product for use in life support devices and/or systems.

©1994 Burr-Brown Corporation

#### THE ERRORS OF THE OP AMP AT 25°C (Referred to Input, RTI)

$$V_{E (OPA)} = V_{D} \left[ 1 - \frac{1}{1 + \frac{1}{\beta A_{VOL}}} \right] + V_{OS} \left[ 1 + \frac{R_{1}}{R_{F}} \right] + I_{B}R_{1} + PSR + Noise$$

V<sub>E (OPA)</sub> = Total Op Amp Error (RTI)

V<sub>D</sub> = Differential Voltage (Full Scale) Across Shunt

$$1 - \frac{1}{1 + \frac{1}{\beta A_{VOL}}} = \text{Gain Error Due to Finite Open Loop Gain}$$

 $\beta$  = Feedback Factor

 $V_{os} =$  Open Loop Gain at Signal Frequency  $V_{os} =$  Input Offset Voltage  $I_{B} =$  Input Bias Current

PSR = Power Supply Rejection (µV/V) [Assuming a 20% change with ±15V supplies. Total error is twice that due to one supply.]

Noise =  $5nV/\sqrt{Hz}$  (for  $1k\Omega$  source resistance and 1kHz bandwidth)

ERROR <sub>(OPA)</sub> (RTI) GAIN ERROR				OFFSET		PSR		NOISE		
V <sub>e (opa)</sub>	=50	$mV \left[ 1 - \frac{1}{1 + \frac{1}{10^6 / 20}} \right]$	$\left[-\frac{1}{0}\right] + \left[0\right]$	$0.025 \text{mV}\left(1+\frac{1}{200}\right)+40 \times 10^{-9} \times 10^{-9}$	<sup>3</sup> ] +	[20µV/V x 3V x 2]	+	[5nV√120 (nVrms)]		
	=	0.01mV	+	[0.0251mV + 0.04mV]	+	0.12mV	+	55nVrms		
Error as % of FSR	=	0.02%	+	[0.05% + 0.08%]	+	0.24%	+	0.00011%		
After Nulling	= =	0.01mV 0.13mV	+	[0mV + 0mV]	+	0.12mV	+	55nVrms		
Error as % of FSR <sup>(1)</sup>	= =	0.02% 0.26% of 50mV	+	[0% + 0%]	+	0.24%	+	0.00011%		

NOTE: (1) FSR = Full-Scale Range. 50mV at input to op amp, or 10V at input (and output) of ISO amp.

#### THE ERRORS OF THE ISO AMP AT 25°C (RTI)

$$V_{E(ISO)} = \frac{1}{200} \left[ \frac{V_{ISO}}{IMR} + V_{OS} + GE + Nonlinearity + PSR + Noise \right]$$

V<sub>E (ISO)</sub> = Total ISO Amp Error IMR = Isolation Mode Rejection

.....

V<sub>os</sub> = Input Offset Voltage

 $V_{ISO} = V_{IMV}$  = Isolation Voltage = Isolation Mode Voltage

GE = Gain Error (% of FSR)

Nonlinearity = Peak-to-peak deviation of output voltage from best-fit straight line. It is expressed as ratio based on full-scale range.

PSR = Change in  $V_{os}/10V$  x Supply Change

Noise = Spectral noise density x \bandwidth. It is recommended that bandwidth be limited to twice maximum signal bandwidth for optimum dynamic range.

ERROR <sub>(ISO)</sub> (RTI)	IMR		V <sub>os</sub>	GAIN ERROR		NONLINEARITY		PSR		NOISE
V <sub>E (ISO)</sub>	$= \frac{1}{200} \qquad \boxed{\frac{500 \text{VDC}}{140 \text{dB}}}$	+ 7	′0mV +	20V X $\frac{0.25}{100}$	+	$\frac{0.75}{100}$ x 20V	+	3.7mV x 3V x 2	+	16μV√120 (rms)
Error as % of FSR <sup>(1)</sup> After Nulling	$=\frac{1}{200}$ [ 0.05mV	+ 7	'0mV +	50mV	+	15mV	+	22.2mV	+	0.175mVrms
	$=\frac{1}{200}$ 0.0005%	+ 0	).7% +	0.5%	+	0.15%	+	0.22%	+	0.00175%
V <sub>E (ISO)</sub>	$=\frac{1}{200}$ [ 0.05mV	+ (	0mV +	0mV	+	15mV	+	22.2mV	+	0.175mVrms
	$=\frac{1}{200}$ 37.2mV									-
	= <b>C</b> 0.19mV									_
Error as % of FSR	$= \frac{1}{200}  L  0.0005\%$ = 0.37% of 50mV	+	0% +	0%	+	0.15%	+	0.22%	+	0.00175%
Total Error	= V <sub>E (OPA)</sub> = 0.13mV = 0.32mV = 0.64% of 50mV		/ <sub>E (ISO)</sub> 19mV							

### **IMPORTANT NOTICE**

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.

Copyright © 2000, Texas Instruments Incorporated