

TPS6108x: A boost converter with extreme versatility

By Jeff Falin

Senior Applications Engineer

Introduction

The TPS61080 and TPS61081 are highly integrated boost converters that have adjustable outputs of up to 27 V with input voltages as low as 2.5 V. The difference between the two versions is the current-limit rating of the integrated power switches (typically 0.5 A and 1.3 A, respectively). The TPS6108x boost converters have a traditional current-mode-control scheme and a constant pulse-width-modulation (PWM) frequency for low-noise operation. The switching frequency can be configured to either 600 kHz for light-load efficiency or 1.2 MHz for smaller, external components. With integrated feedback compensation, internal power switches, and fast PWM switching, the 3×3 -mm QFN package enables an extremely small boost converter for a wide variety of applications. An example is a 12- or 24-V industrial power rail from a 3.3- or 5-V bus. Additional features include high efficiency, an adjustable reference voltage, and redundant protection circuits—all of which make the TPS6108x ideal for boosting the 3.6-V Li-ion battery voltage used in most portable applications. The converters also support the higher voltages needed for powering thin-film-transistor (TFT) LCDs, OLED displays, WLED backlights, or camera flashlights.

Powering displays

Figure 1 shows the converter in a typical boost configuration that provides a regulated output voltage. When up to 20 V and 100 mA are required to drive each column of a passive-matrix OLED (PMOLED), the 1.3-A switch rating makes the TPS61081 the best choice. When less than 10 V and only tens of milliamps per column for the active-matrix OLED (AMOLED) are provided, the 0.5-A switch rating of the TPS61080 may be more appropriate. In either case,

Figure 1. Typical application for a 12-V boosted output


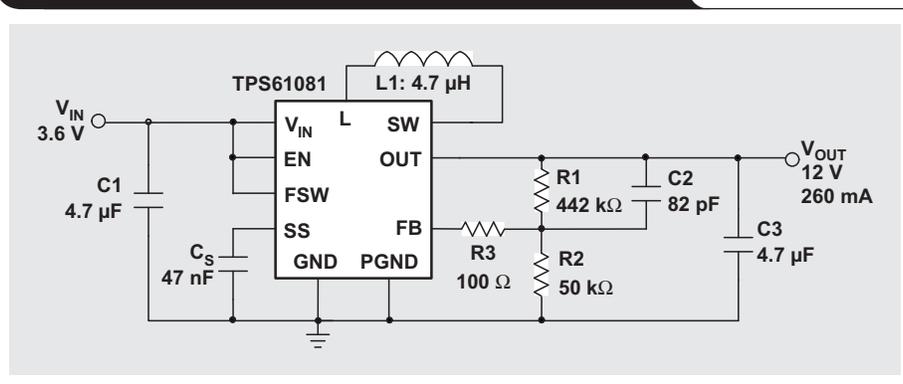


Figure 2. Efficiency with $V_{IN} = 3.6$ V

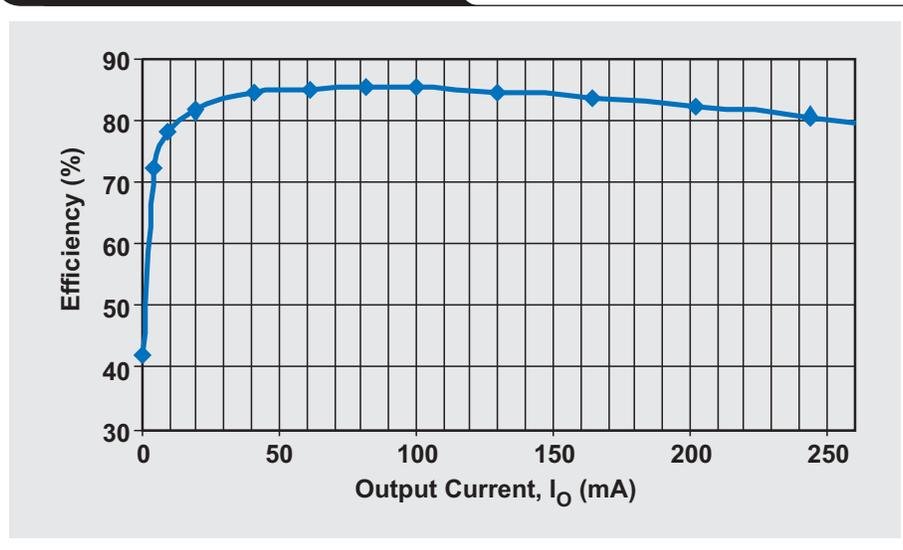

the low- $R_{DS(on)}$ internal switches and the choice of switching frequency provide optimal supply efficiency. Figure 2 shows efficiency data for a 12-V output when a Li-ion battery with a typical 3.6-V source voltage is used.

To support the gates of the TFT drivers for active-matrix LCDs or OLED displays, the high-voltage rail must be capable of fast transients. The TPS61080 has current-mode control and optimized internal compensation; and it can operate at 1.2 MHz with a 4.7- μ H inductor, making it ideal

for fast-transient response. Figure 3 shows the transient response of the TPS61080, which was configured as shown in Figure 1 except for an additional 4.7- μ F output capacitor.

WLED-display backlight driver

As shown in Figure 4, most boost converters can be used to power WLEDs if the voltage-feedback network is replaced with the WLED strings and a series current-sense resistor, R3. The TPS6108x can be used to drive several series WLEDs in parallel for backlighting larger displays.

The voltage across the current-sense resistor is fed back to provide regulation. Traditional boost converters use 1.2-V feedback voltages; therefore, the power loss due to R3 is $P_{\text{LOST}} = I_{\text{WLED}}^2 \times R3 = 1.2 \text{ V} \times I_{\text{WLED}}$. The TPS6108x converters have an SS pin that is used to provide variable soft startup for boosted voltage-regulation applications. The SS pin can also be used to lower the FB-pin reference voltage and to reduce sense-resistor power loss in a WLED current-regulation application. Simply connecting a resistor, R1, from the SS pin to GND will lower the FB-pin reference voltage. The reference voltage equates to the resistance of R1 times the SS-pin bias current ($I_{\text{SS}} = 5 \mu\text{A}$ typical), resulting in the WLED current calculation:


$$I_{\text{WLED}} = \frac{I_{\text{SS}} \times R1}{R3}$$

A second resistor, R2, in series with the FET and Q1 and in parallel with R1 provides analog dimming by lowering the regulated FB-pin voltage across the sense resistor.

Protection


Two of the most common boost-converter design challenges are how to handle the conduction path from input to output and how to prevent overvoltage. The conduction path creates three problems: leakage voltage under shutdown,

Figure 3. Transient response of TPS61080

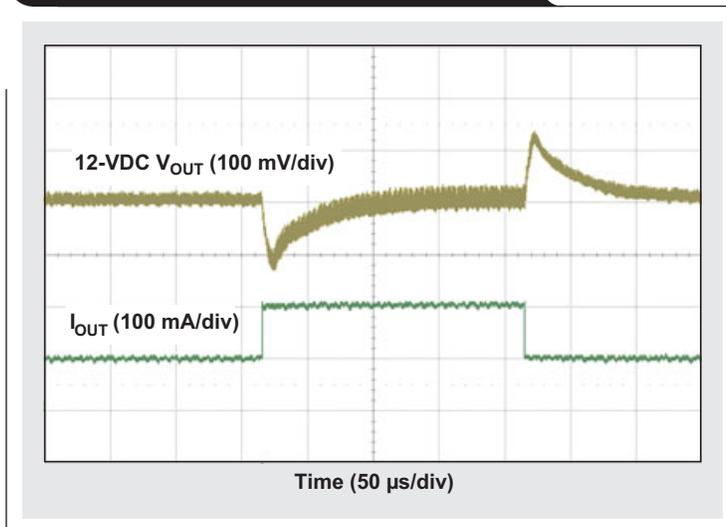

inrush current during startup, and excessive short-circuit current. To address these issues, the TPS6108x has an integrated isolation switch that opens during shut-down mode to prevent a possible current path. This isolation switch and the soft-start circuitry also control inrush current during startup to prevent the input supply from drooping and possibly causing system instability. The TPS6108x keeps the isolation FET off until the EN pin is pulled high and V_{IN} rises above the undervoltage-lockout threshold. The Vgs of the isolation FET is clamped so that its high on-resistance limits the inrush current related to charging the output capacitor to V_{IN} . When the output capacitor reaches V_{IN} , the IC fully turns on the low $R_{\text{DS(on)}}$ isolation FET and activates soft start as programmed by the soft-start capacitor on the SS pin. In the event that V_{OUT} stays below V_{IN} for more than 2 ms, indicating a short-circuit condition, the isolation

Figure 4. TPS61081 WLED backlight driver circuit

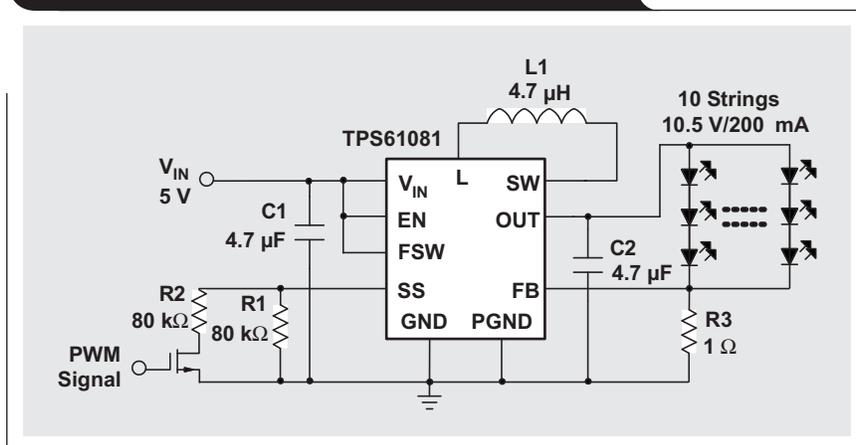

FET turns off and the IC will not restart until the EN pin toggles or V_{IN} goes through power-on reset (POR).

The TPS6108x also has pulse-by-pulse overcurrent limiting, which turns off the power switch once the inductor current reaches a preset value (0.7 A for the TPS61080 and 1.6 A for the TPS61081). The power switch turns back on at the beginning of the next switch cycle. When the inductor current stays above the short-circuit current limit for more than 13 μ s or the V_{OUT} -pin voltage goes 1.4 V below V_{IN} , the IC assumes that there is a short-circuit condition and turns off the isolation FET. After 57 ms, the IC attempts to restart. If a momentary short is cleared, the output returns to its regulation voltage and switches normally. For a permanent short, the isolation FET turns off again and waits for POR or EN-pin toggling. Although the isolation switch has a low $R_{DS(on)}$ for minimum power loss, shorting the V_{IN} and L pins can bypass the switch and further enhance the efficiency.

When the TPS61081 is configured for regulated current output as shown in Figure 4, the output voltage could run away if the output impedance becomes too high (i.e., if a WLED burns out or the load is disconnected). To prevent the power switch from exceeding its maximum voltage rating, the overvoltage-protection (OVP) circuit turns off the power switch when the output voltage exceeds the OVP threshold. When the output voltage falls below the OVP threshold, the converter resumes normal PWM operation.

Conclusion

This extremely versatile, integrated-FET boost converter is ideal for industrial, medical, telecom, and consumer applications that require boosted voltages. Features such as variable-reference voltage and multiple-protection circuitry make the TPS6108x also well-suited for powering LCDs and OLED displays.

Reference

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. "High Voltage DC/DC Boost Converter with 0.5-A/1.3-A Integrated Switch," TPS61080/1 Datasheet	slvs644

Related Web sites

power.ti.com

www.ti.com/sc/device/TPS61080

www.ti.com/sc/device/TPS61081

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone

European Free Call	00800-ASK-TEXAS (00800 275 83927)
--------------------	--------------------------------------

International	+49 (0) 8161 80 2121
---------------	----------------------

Russian Support	+7 (4) 95 98 10 701
-----------------	---------------------

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Fax

International	+81-3-3344-5317	Domestic	0120-81-0036
---------------	-----------------	----------	--------------

Internet/Email	support.ti.com/sc/pic/japan.htm		
----------------	--	--	--

International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone

International	+886-2-23786800
---------------	-----------------

Domestic	Toll-Free Number
----------	------------------

Australia	1-800-999-084	Malaysia	1-800-80-3973
-----------	---------------	----------	---------------

China	800-820-8682	New Zealand	0800-446-934
-------	--------------	-------------	--------------

Hong Kong	800-96-5941	Philippines	1-800-765-7404
-----------	-------------	-------------	----------------

India	+91-80-41381665 (Toll)	Singapore	800-886-1028
-------	------------------------	-----------	--------------

Indonesia	001-803-8861-1006	Taiwan	0800-006800
-----------	-------------------	--------	-------------

Korea	080-551-2804	Thailand	001-800-886-0010
-------	--------------	----------	------------------

Fax	+886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		
			ti-china@ti.com

C062907

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2007 Texas Instruments Incorporated