


Driver simulation setup example

SN65DSI8X
LVDS driver



It is critical that 100 ohm onchip termination is created when running simulation. The IBIS model does NOT contain this termination resistance. Please use 115 ohm for min/weak corner and 85 ohm for max/strong corner.
For LVDS driver with 200 ohm onchip setting, please change the resistor value to 200ohm(typ corner), 230ohm(min corner) and 170 ohm(max corner)

Receiver simulation setup example

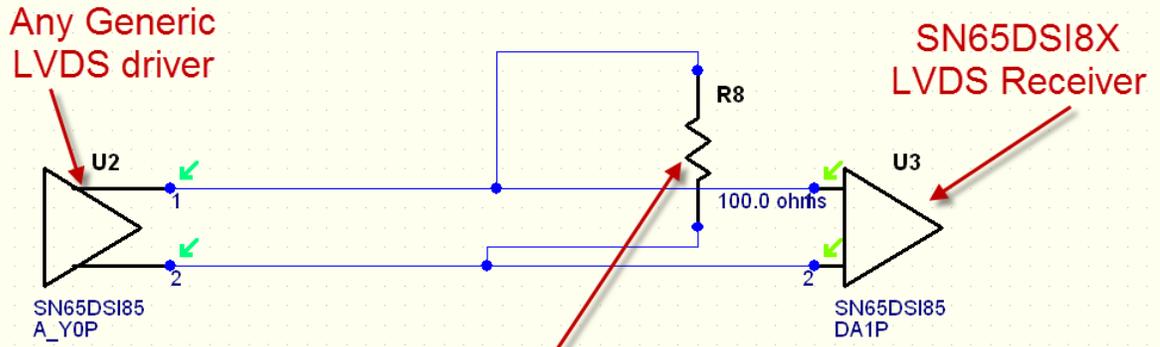

It is critical that 100 ohm onchip termination is created when running simulation. The IBIS receiver model does NOT contain this termination resistance. Please use 115 ohm for min/weak corner and 85 ohm for max/strong corner.