




**TI Technology Days 2010**

# **How to drive your AD-Converter?**

**Katharina Berberich**

**Carsten Schlegel**

# Analog to Digital Conversion

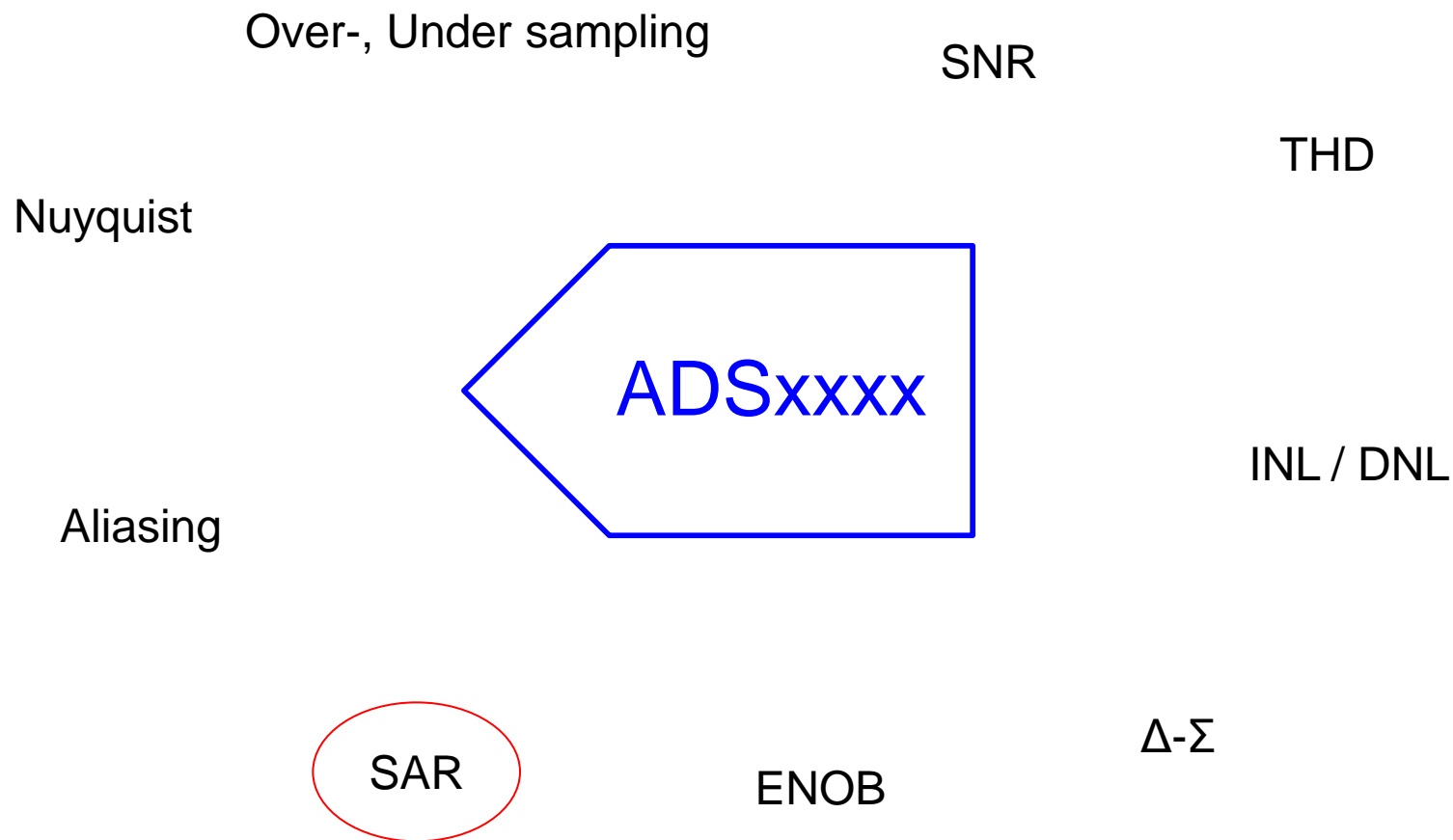


# The Size of the Least Significant Bit (LSB)

RESOLUTION N	$2^N$	VOLTAGE of LSB (10V FS)	ppm FS	% FS	dB FS
2-bit	4	2.5 V	250,000	25	-12
4-bit	16	625 mV	62,500	6.25	-24
6-bit	64	156 mV	15,625	1.56	-36
8-bit	256	39.1 mV	3,906	0.39	-48
10-bit	1,024	9.77 mV (10 mV)	977	0.098	-60
12-bit	4,096	2.44 mV	244	0.024	-72
14-bit	16,384	610 $\mu$ V	61	0.0061	-84
16-bit	65,536	153 $\mu$ V	15	0.0015	-96
18-bit	262,144	38 $\mu$ V	4	0.0004	-108
20-bit	1,048,576	9.54 $\mu$ V (10 $\mu$ V)	1	0.0001	-120
22-bit	4,194,304	2.38 $\mu$ V	0.24	0.000024	-132
24-bit	16,777,216	596 nV*	0.06	0.000006	-144

**\*600nV is the Johnson Noise in a 10kHz BW of a 2.2k $\Omega$  Resistor @ 25 C**


**Remember: 10-bits and 10V FS yields an LSB of 10mV, 1000ppm, or 0.1%.  
All other values may be calculated by powers of 2.**

# Analog to Digital Conversion

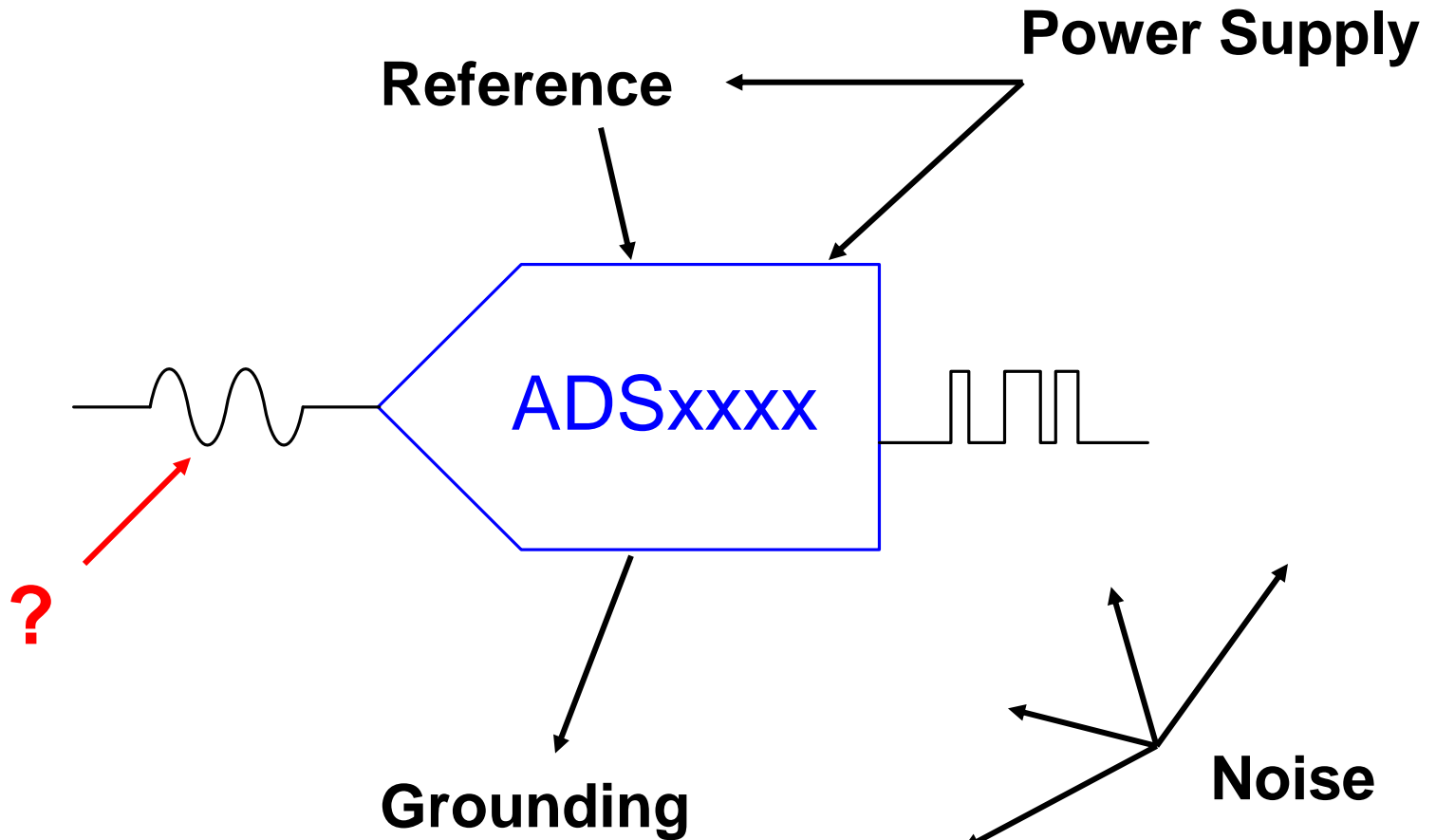

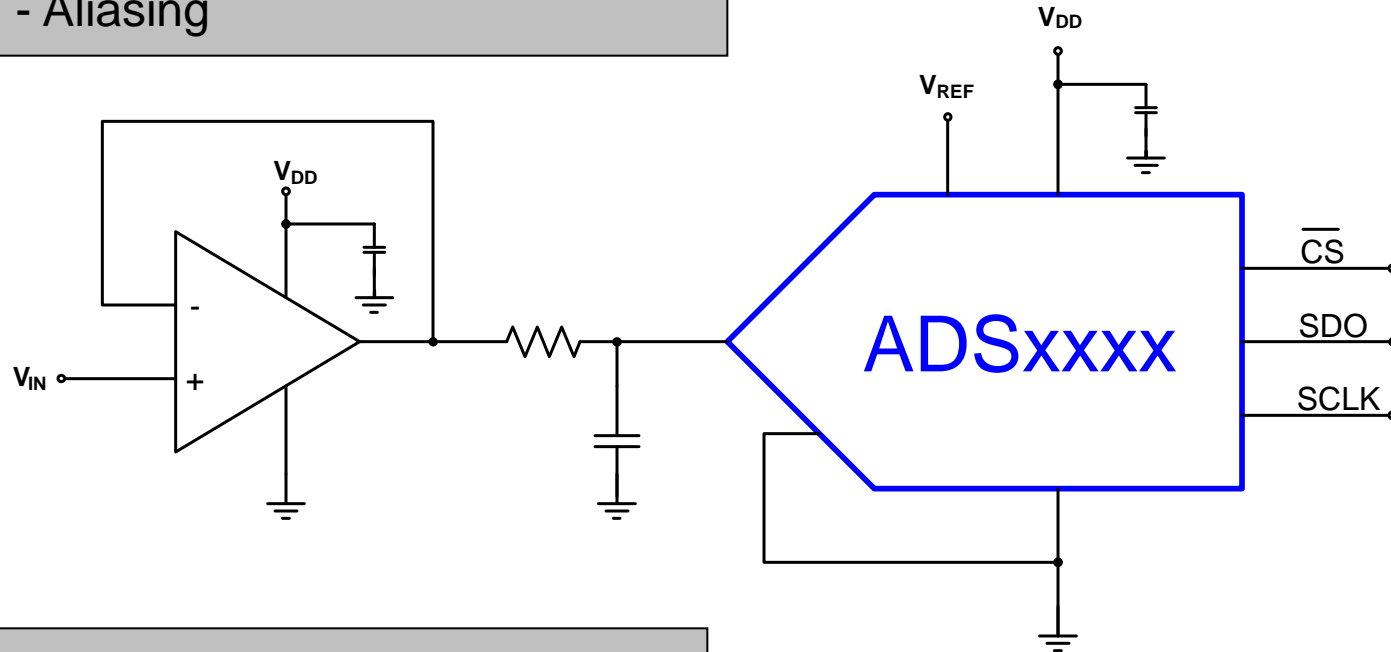
# Typical ADC Input Drive Circuit

- Signal conditioning
- Adaptation to ADC input range
- MUX, Range extension
- Anti - Aliasing




- Buffer for Impedance Matching
- Dynamic Load (Switched Capacitor)
- Acquisition Time

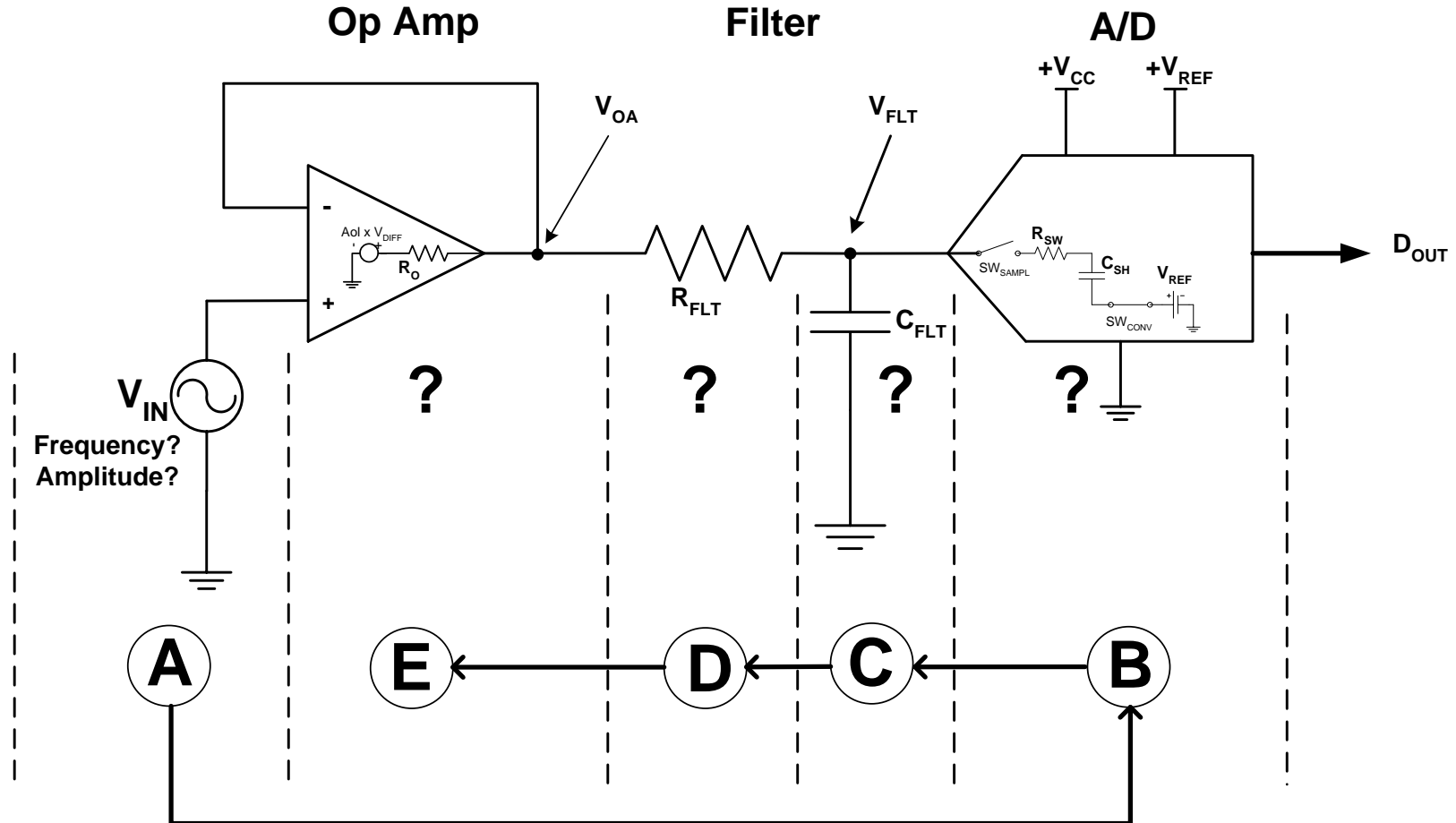
# CDAC SAR ADC Input Buffer and Filter Selection


 
# Simplified Model of SAR-ADC Input Stage




# SAR ADC Input Voltage during Sampling

 




# More detailed SAR Input Stage

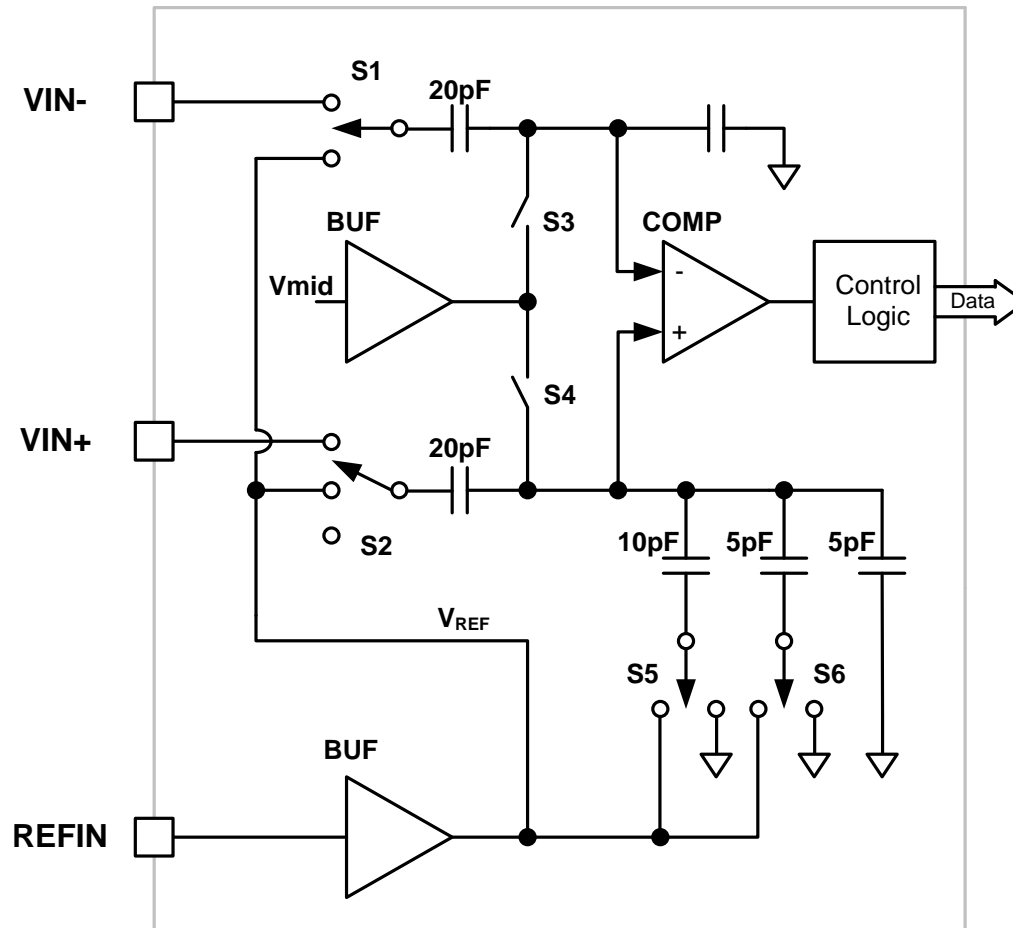


3 bits of ADS8361
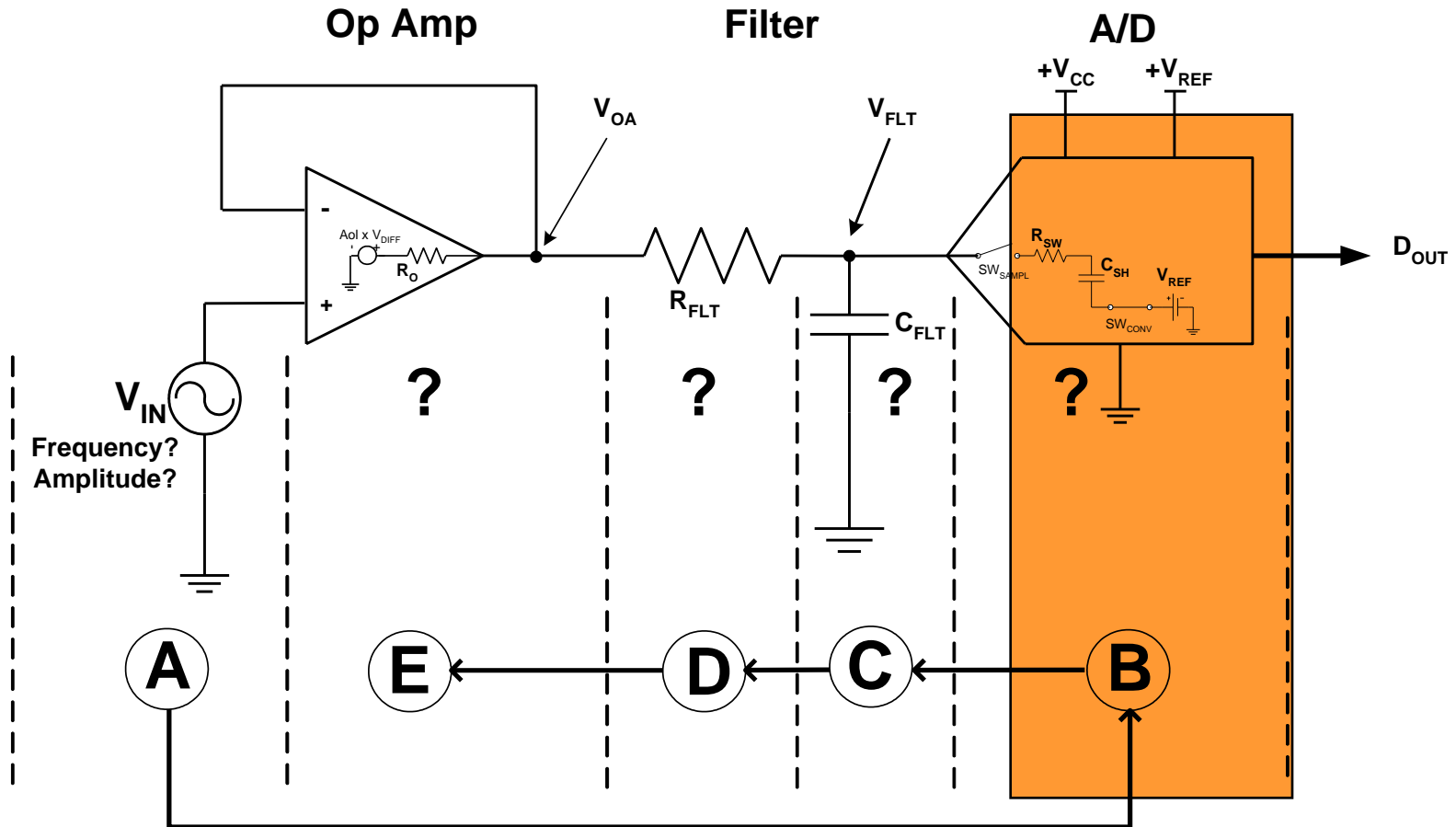
# CDAC SAR ADC Input Buffer and Filter Selection



# Voltage Across the Sampling Capacitor

 

# Voltage Across Sampling Capacitor

$$V_{CSH}(t) = V_{CSH}(t_0) + (V_{IN} - V_{CSH}(t_0)) \times (1 - e^{-\frac{t}{\tau}})$$

$V_{CSH}(t)$  is voltage in time across the sampling capacitor,  $C_{SH}$

$V_{CSH}(t_0)$  is voltage across the  $C_{SH}$ , at beginning of acquisition time

$V_{IN}$  is the input voltage to the ADC

$\tau$  is acquisition time constant and equal to  $R_{S1} \times C_{SH}$

$t$  is a time variable in seconds

# Settling Time as Function of $\tau$

$$V_{IN} - V_{CSH}(t_{AQ}) \leq \frac{1}{2} LSB$$

$V_{CSH}(t_{AQ})$  is voltage across the  $C_{SH}$ , at the end of the sampling period

$t_{AQ}$  is acquisition time, the time from the beginning of the sampling period ( $t_0$ ) to the end of the sampling period

$$\frac{1}{2} LSB = \frac{FSR}{2^{N+1}}$$

(LSB = Least Significant Bit, FSR is the full-scale range of the N-Bit converter)

$$t_{AQ} \geq k_1 \times \tau$$


$$k_1 = \ln\left(\frac{V_{IN} - V_{SH0}}{FSR} \cdot 2^{N+1}\right)$$

# Time-Constant-Multiplier for SAR ADC

ADC Resolution	k1 time-constant-multiplier 1/2 LSB accuracy, $1/2^{N+1}$
8	6.2
10	7.6
12	<u>9.0</u>
14	10.4
16	<u>11.8</u>
18	13.2
20	14.6


\*note – using worst case values:  $V_{IN}$  = full-scale voltage or  $2^N$ ,  $V_{SH0} = 0V$

# Data Acquisition Time

 



$$t_{AQ} \geq k_1 \times \tau$$

# Charge Injection

 


  
# External and Internal Acquisition Capacitors



# Charge Distribution between $C_F$ and $C_{SH}$

$$Q_{IN} = C_F \times V_{IN}$$

$$Q_{SH} = C_{SH} \times V_{SH0}$$

After the closure of S1, the charge on  $C_F$  and  $C_{SH}$  distributes.

$$C_{TOT} = C_F + C_{SH}$$

$$Q_{TOT} = Q_{IN} + Q_{SH}$$

$$V_{TOT} = \frac{C_F}{C_F + C_{SH}} \cdot V_{IN} + \frac{C_{SH}}{C_F + C_{SH}} \cdot V_{SH0}$$

$$V_{TOT} = \frac{a}{a+1} \cdot V_{IN} + \frac{1}{a+1} \cdot V_{SH0} \quad a = \frac{C_F}{C_{SH}}$$

# New Time Constant Multiplier

$$k_2 = \ln \left[ \frac{\left(1 - \frac{a}{a+1}\right) \cdot V_{IN} - \frac{1}{a+1} \cdot V_{SH0}}{FSR} \cdot 2^{N+1} \right]$$

“ $k$ ” is not only function of the initial charge  $V_{SH0}$ , but it is also a function of the value of the applied external capacitor  $C_F$ . In the case of the lower frequency input signal ( $\sim f_s/10$ ) the calculation of the initial charge  $V_{SH0}$  of the  $C_{SH}$  is  $\frac{1}{2}$  FSR. On the other hand, for the multiplexed signal at the input to the converter, we need to use 0V for  $V_{SH0}$ .

$$k_2 = \ln \left( \frac{1}{a+1} \cdot 2^{N+1} \right)$$

# New Time-Constant-Multiplier for SAR ADC

ADC Resolution	$C_F$ [pF]	$a$ $C_F/C_{SH}$	$k_2$ time-constant-multiplier 1 LSB accuracy, $1/2^N$	$R_F$ [ $\Omega$ ]
16	200	8	9.6	1,576
16	400	16	9.0	894
16	1000	40	8.1	411
16	4000	160	6.7	126

\*note – using worst case values:  $V_{IN}$  = full-scale voltage or  $2^N$ ,  $V_{SH0} = 0V$

Assumed:  $t_{AQ}=3.4\mu s$  and  $C_{SH}=25pF$

# Charge Bucket I

- Charge Transfer Equation:  $Q = CV$
- Charge required to charge  $C_{SH}$  to  $V_{REF}$ 
  - $Q_{SH} = C_{SH} V_{REF}$
  - $Q_{SH} = 25\text{pF} \cdot 4.096\text{V} = 102\text{pC}$
- IDEAL  $C_{FLT}$ 
  - “Charge Bucket” to fill  $C_{SH}$  with only a  $31.25\mu\text{V}$  ( $1/2\text{LSB}$ ) droop on  $C_{FLT}$
  - $Q_{FLT} = Q_{SH}$
  - $Q_{FLT} = C_{FLT} (31.35\mu\text{V})$
  - $102\text{pC} = C_{FLT} (31.25\mu\text{V}) \rightarrow C_{FLT} = 3.3\mu\text{F}$
- IDEAL  $C_{FLT} = 3.3\mu\text{F}$ 
  - Not a good, small, cheap high frequency capacitor
  - Not practical for Op Amp to drive directly (stability, transient current)
  - Isolation resistor likely not large enough to help isolate Cload and still meet necessary filter time constant




# Charge Bucket II




- **Partition the “Charge Bucket”**
  - 95% from  $C_{FLT}$
  - 5% from Op Amp
- **$C_{FLT}$  value required to provide  $Q_{SH}$  with <5% droop on  $C_{FLT}$** 
  - $Q_{FLT} = Q_{SH}$
  - $Q_{FLT} = C_{FLT} (0.05V_{REF})$
  - $102\text{pC} = C_{FLT} (0.05 \cdot 4.096\text{V}) \rightarrow C_{FLT} = 500\text{pF}$
- **During  $t_{ACQ}$  the Op Amp must replace 5%  $V_{REF}$  on  $C_{FLT}$** 
  - Ensure  $C_{FLT}$  is at least  $10 \times C_{SH}$ 
    - This implies dominant load for Op Amp Buffer is  $C_{FLT}$
    - $500\text{pF} = 20 \times 25\text{pF} \rightarrow C_{FLT} > 20 \times C_{SH}$
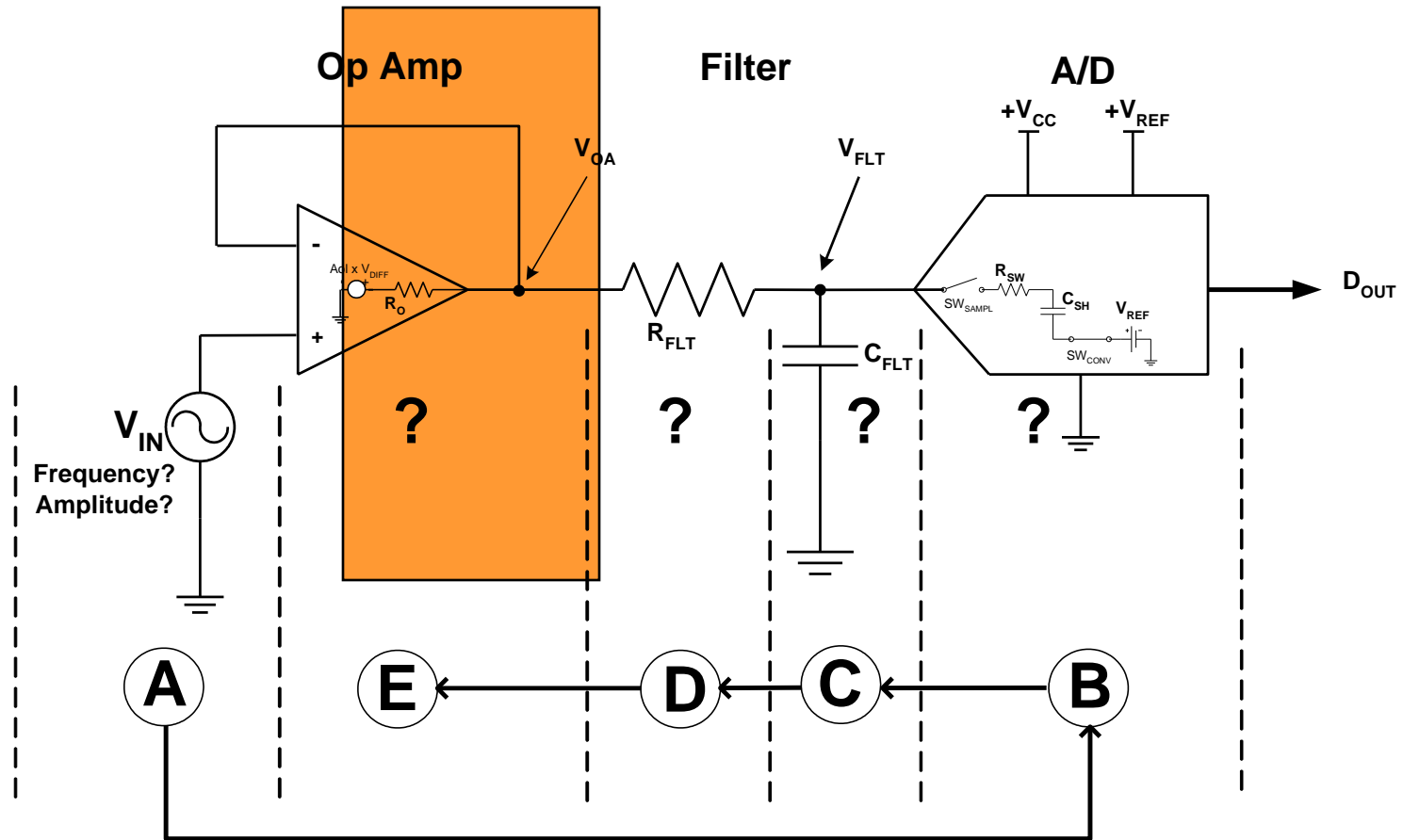
# CDAC SAR ADC Input Buffer and Filter Selection




# Buffer Output Impedance

 




# OPA364 Open-Loop Output Impedance

 

$R_O$  Open-Loop output resistance

$f_{ZO}$  Frequency of Zero in the Open-Loop output impedance

# OPA364 Open-Loop Output Impedance

 

Values from Tina model


$$R_o = 107.3\Omega$$

$$f_{zo} = 6.32kHz$$


$$f_{zo} = \frac{1}{2\pi \cdot R_o \cdot C_o}$$

$$C_o = 0.235\mu F$$


# OPA364 Open-Loop Voltage Gain

 

# Op Amp with external RC-Filter

 

# Op Amp with External RC Filter

 

# Added Pole and Zero

**BiPOLAR  
OpAmp**

$$f_{PX} = \frac{1}{2\pi \cdot (R_O + R_F) \cdot C_F}$$

$$f_{ZX} = \frac{1}{2\pi \cdot R_F \cdot C_F}$$

**2-Stage CMOS RRO  
OpAmp**

$$f_{PX} = \frac{1}{2\pi \cdot (R_O + R_F) \cdot \left[ \frac{C_O \cdot C_F}{C_O + C_F} \right]}$$

$$f_{ZX} = \frac{1}{2\pi \cdot R_F \cdot C_F}$$

# Gain of Added Pole and Zero

Gain of added pole

$$G_{PX} = -20 \cdot \log \left[ \frac{f_{PX}}{f_U} \right]$$

Gain of added zero


$$G_{ZX} = G_{PX} - 40 \cdot \log \left[ \frac{f_{ZX}}{f_{PX}} \right]$$

Modify close-loop  
unity gain frequency

$$G_C = 0dB = G_{ZX} - 20 \cdot \log \left[ \frac{f_C}{f_{ZX}} \right]$$

$$f_C = f_{ZX} \cdot 10^{G_{ZX}/20}$$

# Test Circuit

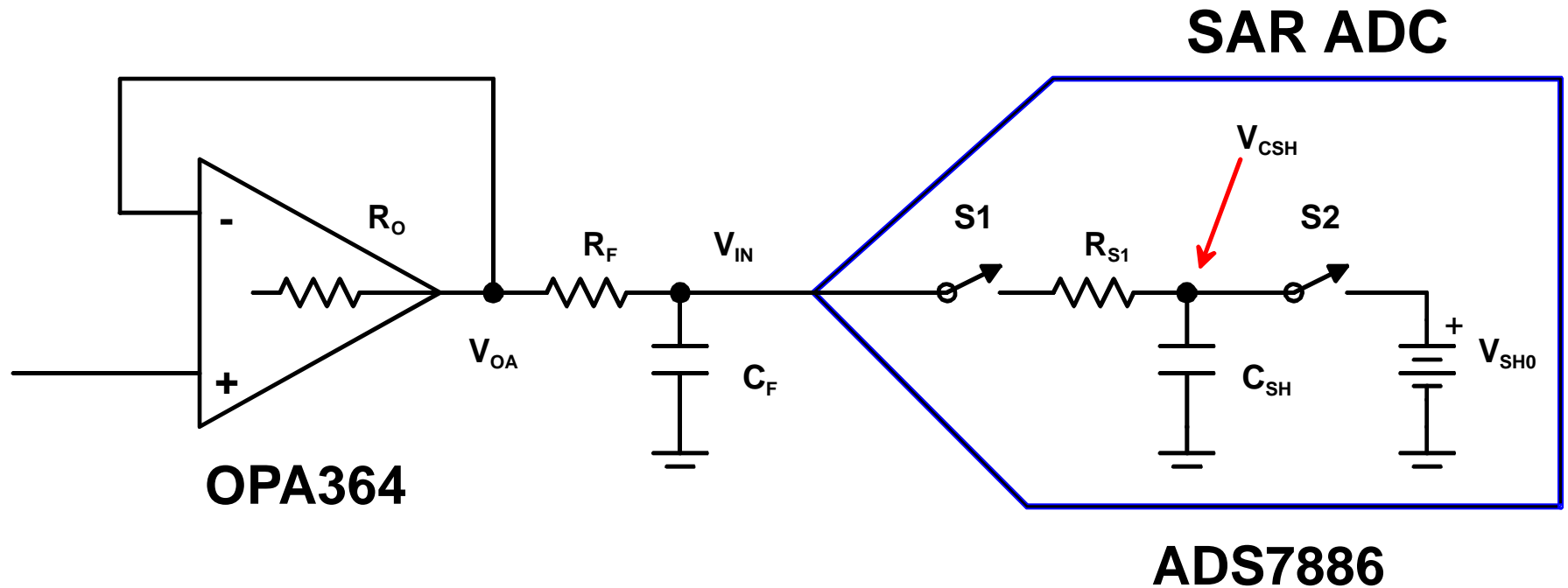



# Design Criteria (w/o Phase Margin)

1) Critically stable:

$$f_{ZX} = f_c (-40dB / decade)$$


2) Marginally stable:

$$G(f_{ZX}) = 3dB \quad or \quad f_{ZX} = \frac{f_c}{1.41}$$

3) Good design:

$$G(f_{ZX}) = 6dB \quad or \quad f_{ZX} = \frac{f_c}{2}$$

# A Good Design Guideline

 

$$f_C \leq \frac{1}{2} f_U$$

$$f_{ZX} \leq \frac{1}{2} f_C$$

or

$$f_{ZX} \leq \frac{1}{4} f_U$$


$$G_{ZX} \geq +6dB$$

- Phase Shift -

$$f_{PX} > \frac{1}{10} f_{ZX}$$

$$R_F \geq \frac{R_O}{9}$$
 
# OPA364 with $R_F=15\Omega$ and $C_F=1,500pF$



- Open-Loop voltage gain
- Modify Open-Loop voltage gain
- 0 dB
- Phase Shift

$$f_{PX} = 873kHz$$

$$G_{PX} = 15.3dB$$

$$f_{ZX} = 7.07MHz$$

$$G_{ZX} = -5.2dB$$

$$f_C = 2.49MHz$$

$$\theta(f_C) = -141.3^\circ$$


## Phase Margin

$$\psi(f_C) = 180^\circ - \theta(f_C)$$


$$\psi(f_C) = 38.7^\circ$$
 
# Small Signal Step Response

$R_F=15\Omega$  and  $C_F=1,500\text{pF}$   
50mV/div 250ns/div




OPA364 Output

 

ADC Input
 
# OPA364 with $R_F=66.5\Omega$ and $C_F=1,500pF$



- Open-Loop voltage gain
- Modify Open-Loop voltage gain
- 0 dB
- Phase Shift

$$\begin{aligned}f_{PX} &= 616 \text{ kHz} \\G_{PX} &= 18.9 \text{ dB} \\f_{ZX} &= 1.59 \text{ MHz} \\G_{ZX} &= 7.12 \text{ dB} \\f_C &= 3.04 \text{ MHz} \\\theta(f_C) &= -106.3^\circ\end{aligned}$$


## Phase Margin

$$\psi(f_C) = 180^\circ - \theta(f_C)$$


$$\psi(f_C) = 73.7^\circ$$
 
# Small-Signal Step Response

$R_F = 66.5\Omega$  and  $C_F = 1,500\text{pF}$   
50mV/div 250ns/div





OPA364 Output

 

ADC Input

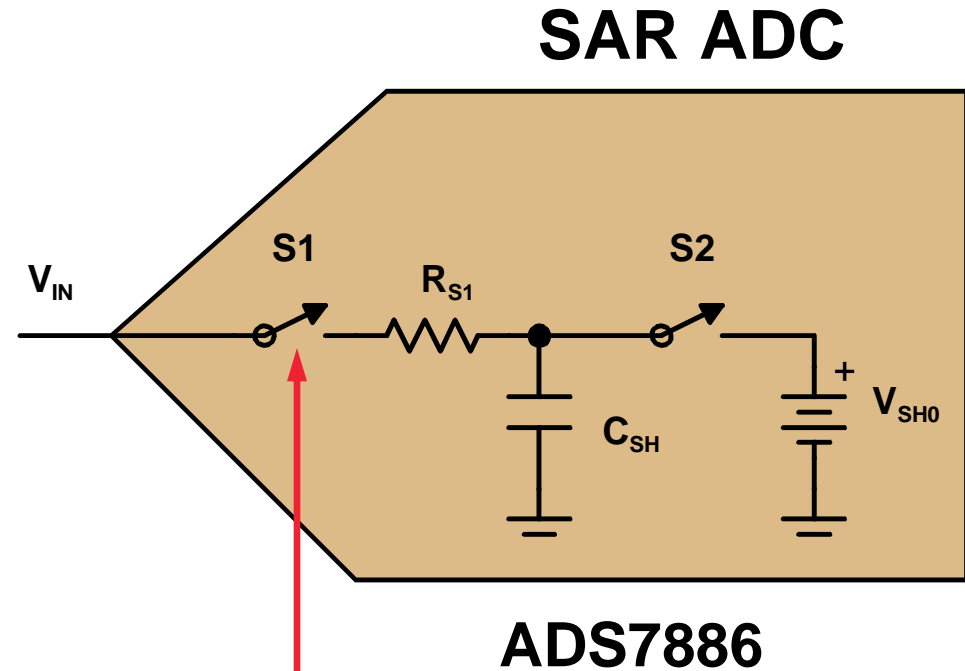 
# Histogram Results for Different $t_{AQ}$



$t_{AQ} = var$

ON/OFF

# Histogram Results for Different $t_{AQ}$

 

ADS7886  
Resolution 12 Bit  
FSR 4.096 V  
65535 Samples per  $t_{AQ}$

— 150 Ohm 1,500 pF  
— 66.5 Ohm 1,500 pF

$\sigma_{MAX} = 0.55 \text{ LSB}$   
 $V_{n_{MAX}} = 548 \mu V_{RMS}$

$\sigma_{MAX} = 0.16 \text{ LSB}$   
 $V_{n_{MAX}} = 164 \mu V_{RMS}$



# Minimum Acquisition Time and OpAmp's GBW

1) Find Unity Gain Bandwidth

$$f_U = GBW$$

2) Calculate frequency of added zero

$$f_{ZX} = \frac{1}{4} f_U$$

3) Determine minimum time-constant

$$\tau = \frac{1}{2\pi \cdot f_{ZX}}$$

4) Calculate time-constant multiplier

$$k = \ln\left(\frac{1}{a+1} \cdot 2^{N+1}\right) \quad a = \frac{C_F}{C_{SH}}$$

5) Find minimum acquisition time

$$t_{AQ} \geq k \cdot \tau$$

# Minimum Acquisition Time for Some OpAmp's

		GBW (MHz)	f <sub>z</sub> (MHz)	τ (ns)	12 Bit t <sub>AQ</sub> (ns)	16 Bit t <sub>AQ</sub> (ns)
INA155	Medium Speed, Precision INA	0.55	0.14	1,157	5,672	8,881
INA128	High Precision, 120dB CMRR	1.3	0.33	490	2,400	3,757
INA331	High Bandwidth, Single Supply	5.0	1.25	127	624	977
OPA340	CMOS, 0.0007% THD+N	5.5	1.38	116	567	888
OPA363	1.8V, High CMRR, SHDN	7.0	1.75	91	446	698
OPA2613	Dual VFB, Low Noise	12.5	3.13	51	250	391
OPA627	Ultra-Low THD+N, Wide BW	16.0	4.00	40	195	305
OPA381	Precision High-Speed Amp	18.0	4.50	35	173	271
OPA727	CMOS, e-trim™, Low Noise	20.0	5.00	32	156	244
OPA228	Precision, Low Noise, G ≥ 5	33.0	8.25	19	95	148
OPA350	Precision ADC Driver	38.0	9.50	17	82	129
OPAy365	High-Speed, Zero-Crossover	50.0	12.50	13	62	98
OPA2889	Dual, Low Power, VFB	75.0	18.75	8	42	65
OPA211	36V, Bipolar Precision	80.0	20.00	8	39	61
THS4281	Very Low Power RRIO	80.0	20.00	8	39	61
OPA358	CMOS, 3V Operation, SC70	80.0	20.00	8	39	61

# After selecting ADC and Op Amp

1) Determine  $C_F$

$$20 \cdot C_{SH} \leq C_F \leq 60 \cdot C_{SH}$$

2) Calculate “a”

$$a = \frac{C_F}{C_{SH}}$$

3) Calculate time-constant multiplier

$$k = \ln\left(\frac{1}{a+1} \cdot 2^{N+1}\right)$$

4) Calculate frequency of added zero

$$f_{ZX} = \frac{t_{AQ}}{k}$$

5) Verify frequency of added zero

$$f_{ZX} \leq \frac{1}{4} f_U$$

# After selecting ADC and OpAmp

1) Calculate  $R_F$

$$R_F = \frac{1}{2\pi \cdot C_F \cdot f_{ZX}}$$

2) Verify value  $R_F$

$$R_F \geq \frac{R_O}{9}$$

3) Calculate frequency of added pole

$$f_{PX} = \frac{1}{2\pi \cdot (R_F + R_O) \cdot C_F}$$

4) Keep added pole and zero  
less then decade a part

$$f_{PX} \geq \frac{1}{10} f_{ZX}$$

5) Verify gain of added zero

$$+6dB \leq G_{ZX} = -20 \cdot \log \left[ \frac{f_{PX}}{f_U} \right] - 40 \cdot \log \left[ \frac{f_{ZX}}{f_{PX}} \right]$$

