



TI Technology Days 2010

AC/DC Solutions for High Efficiency

Juergen Schneider

System Engineer Power Solutions

Agenda

- **General thoughts, standards and solutions**
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary

Efficiency increase – directives and legislation

- Enforcement Levels
 - Incentive Programs



- Voluntary



EC Code of Conduct (EU)

- Mandatory



Australian Government
Department of Climate Change



[EC EuP Eco-Directive \(EU\) 2005/32/EC](#)

EuP – EPS $\leq 250\text{W}$ (External Power Supplies)

COMMISSION REGULATION (EC) No 278/2009 of 6 April 2009

No-load power consumption

$\leq 300\text{mW}$ for $P_{\text{OUT}} \leq 51\text{W}$

$\leq 500\text{mW}$ for $P_{\text{OUT}} > 51\text{W}$

**Average active efficiency
at 25 / 50 / 75 / 100% of rated P_{OUT}
for $1\text{W} < P_{\text{OUT}} \leq 51\text{W}$**


2011 EPS (Low Voltage Excluded)

$$0.063 \times \ln(P_{\text{OUT}}) + 0.622$$

2011 Low Voltage EPS

($V_{\text{OUT}} < 6\text{V}$ & $I_{\text{OUT}} \geq 550\text{mA}$)
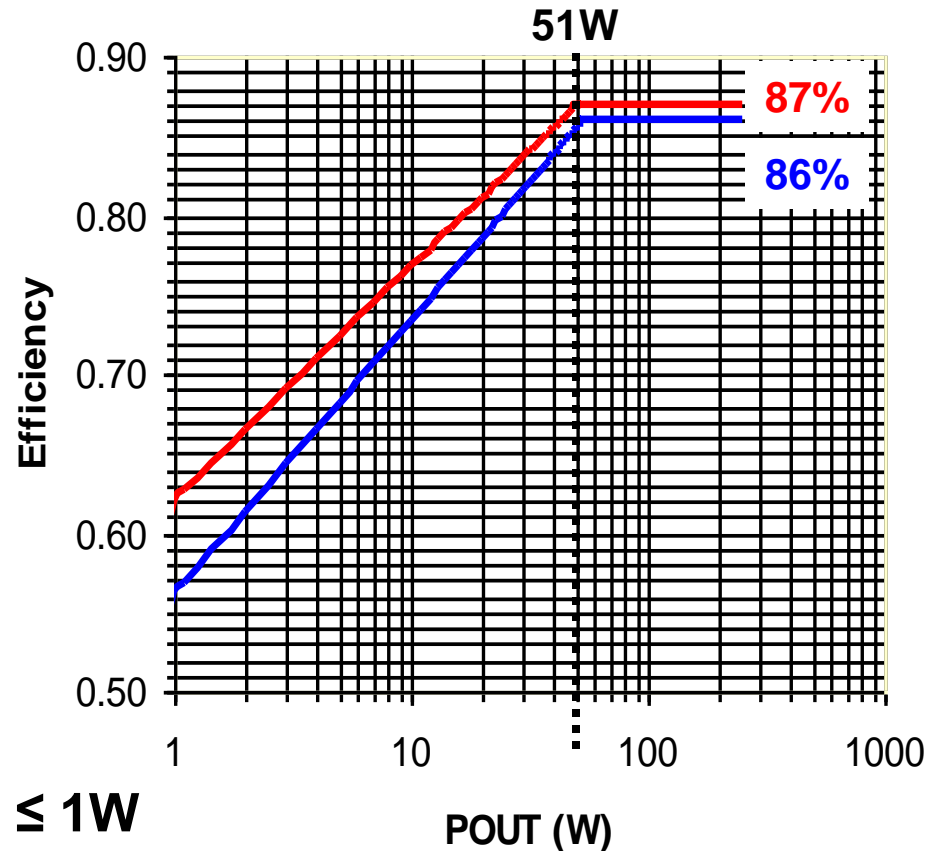
$$0.075 \times \ln(P_{\text{OUT}}) + 0.561$$



**Additional requirements for $P_{\text{OUT}} \leq 1\text{W}$
(Not shown here)**

EuP - Standby and off mode power consumption

COMMISSION REGULATION (EC) No 1275/2008 of 17 December 2008

- Equipment shall, ... provide:
 - off mode and/or
 - standby mode, and/or
 - another condition which does not exceed ... power consumption requirements for off mode and/or standby mode when the equipment is connected to the mains power source.

Power Consumption	Form January 2010 on , Power Consumption (W)	January 2013, Power Consumption (W)
OFF Mode	1	0.5
Standby Mode providing only reactivation function w/ or w/o indication of enabled reactivation function	1	0.5
Standby Mode providing only <i>information or status display</i> w/ or w/o a reactivation function	2	1
Power Management for automatic transition into OFF Mode or Standby Mode	-	YES


Ways to achieve required efficiency

- Select proper power stage topology
- Optimize components in power stage
- Utilize power saving modes & features
 - Low start-up and operation quiescent currents
 - Quasi-resonant and resonant techniques
 - ZVS (Zero Voltage Switching)
 - Phase management
 - Burst mode
 - Synchronous rectification

Agenda

- General thoughts, standards and solutions
- **Quasi-resonant green mode flyback (UCC28600)**
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary

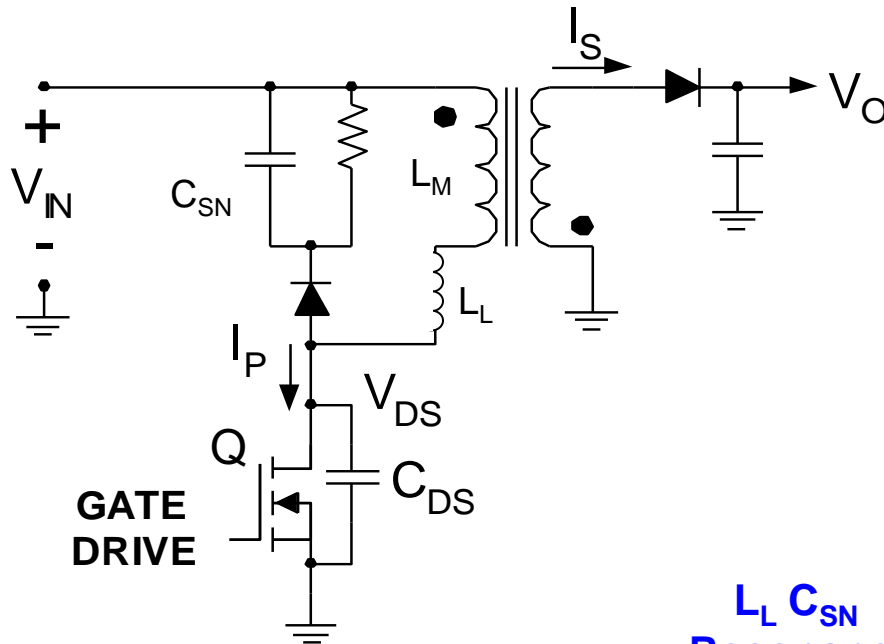
UCC28600 – Valley switching makes the difference




Energy in C_{DS} is lost each time Q is switched ON

$\frac{1}{2} C_{DS} V_{DS}^2$

**$L_L C_{SN}$
Resonance**

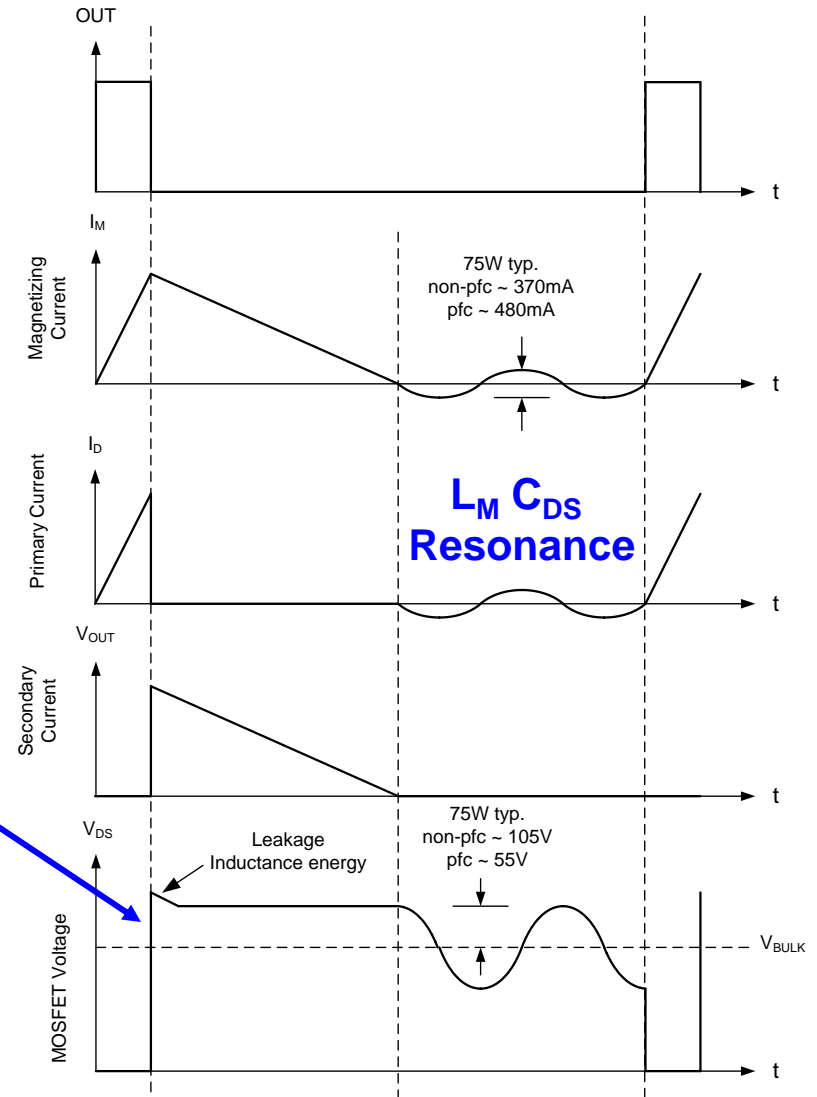


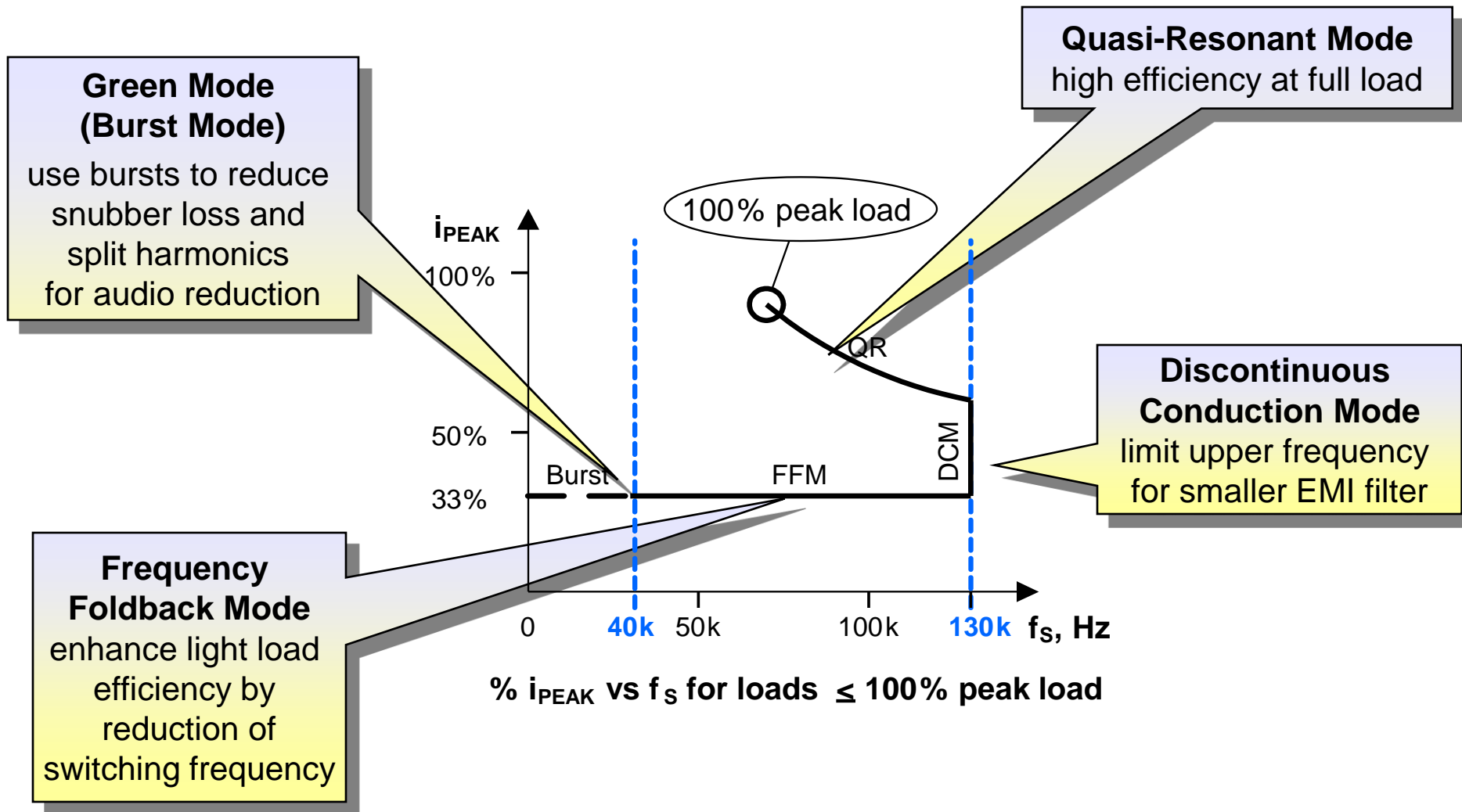UCC28600 – Multiple operation modes make the difference




QR and FFB valley switching

36W, QR mode

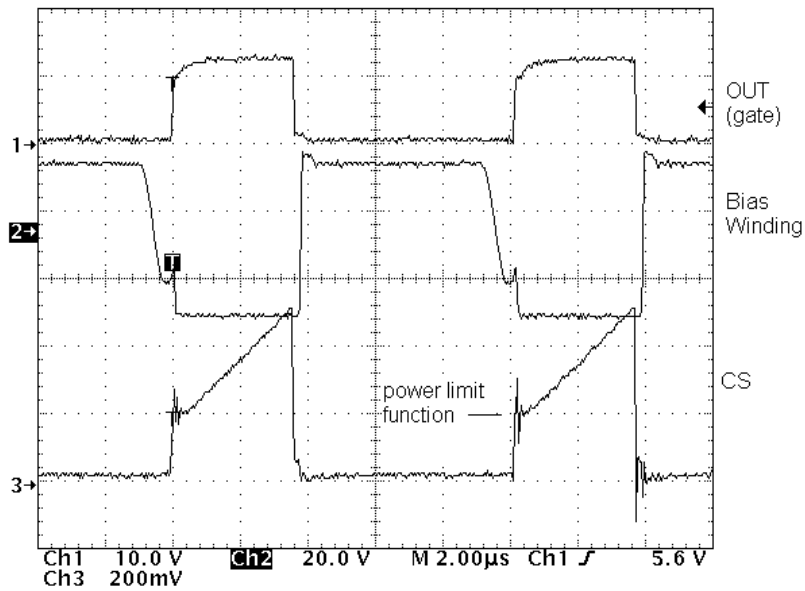


13.8W, FFB mode

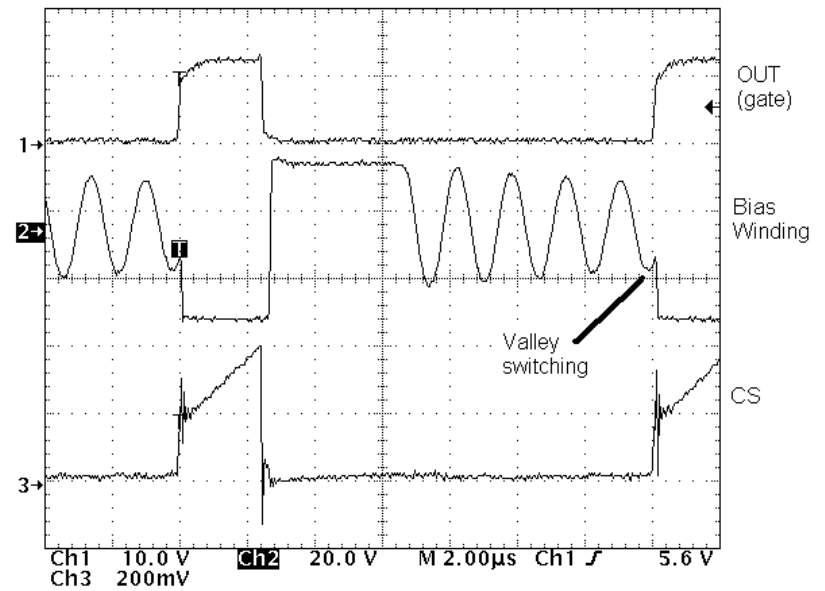

UCC28600 - 8-pin QR green mode PWM controller



Multi - function pins give full features in 8-pins instead of 14 !

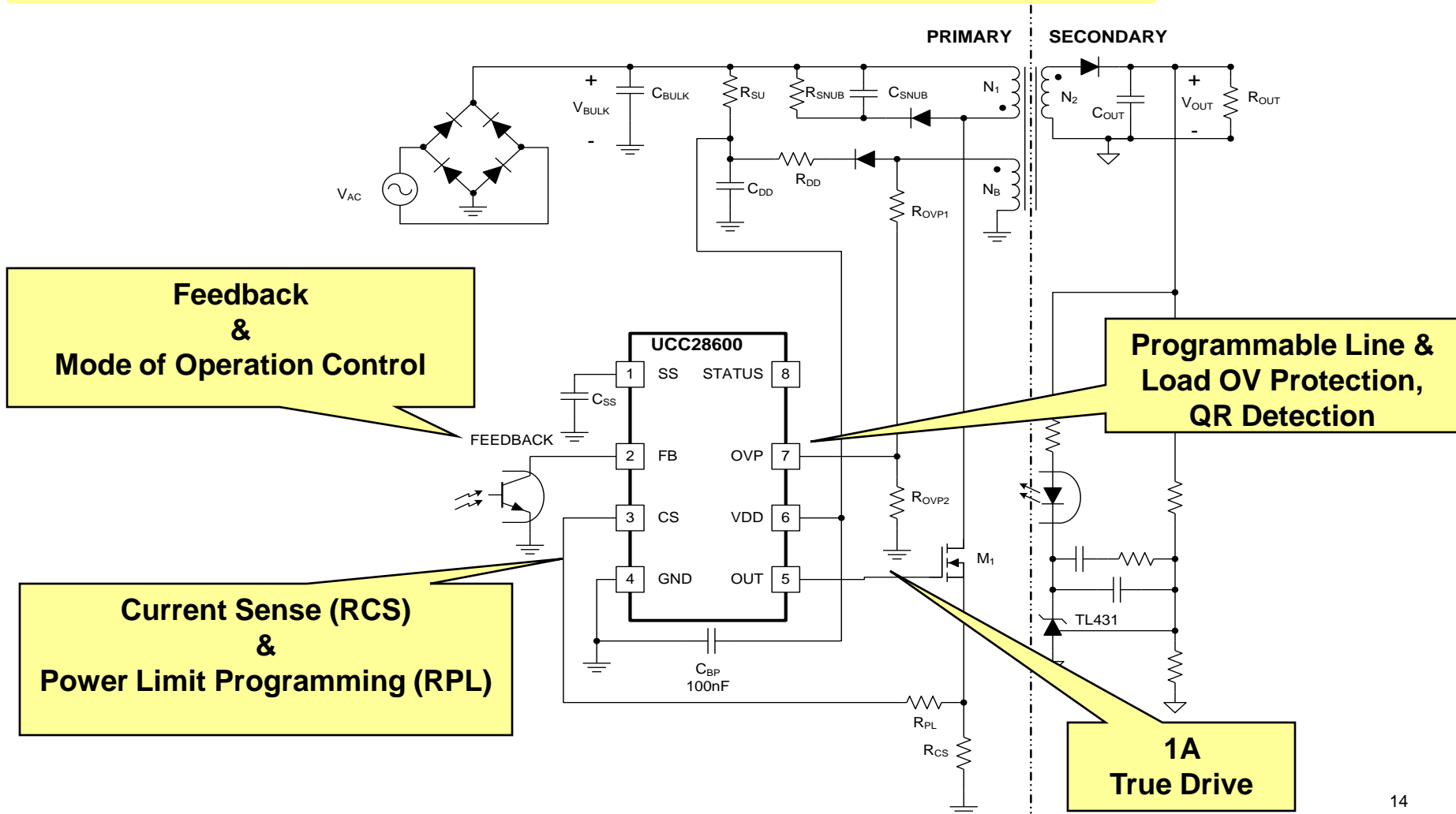


UCC28600 – Design support


- Application Notes
 - Bootstrap circuit for green mode applications ([slua373](#))
 - Design considerations for the UCC28600 ([slua399b](#))
 - Flyback transformer design for the UCC28600 ([slua418](#))
- Seminar topics
 - Seminar 1700 - topic 2: Green-mode power by the milli-Watt ([topic2mm](#))
 - [2010/2011 Seminar](#) – topic 1: Under the Hood of Flyback SMPS Designs
- EVMs
 - 65W universal input
 - 120W universal input with PFC
- Design tools
 - UCC28600 design calculator ([slvc104f](#))
- Reference Designs
 - More than 100 tested designs from 0.5W to 80W

UCC28600 – 18V / 65W universal input design EVM


**R2, R3, R4 – Start-up resistors (2M Ω in total)
~ 52 mW dissipation @ 230V !
~ 2 s start-up delay time @ 115V !**

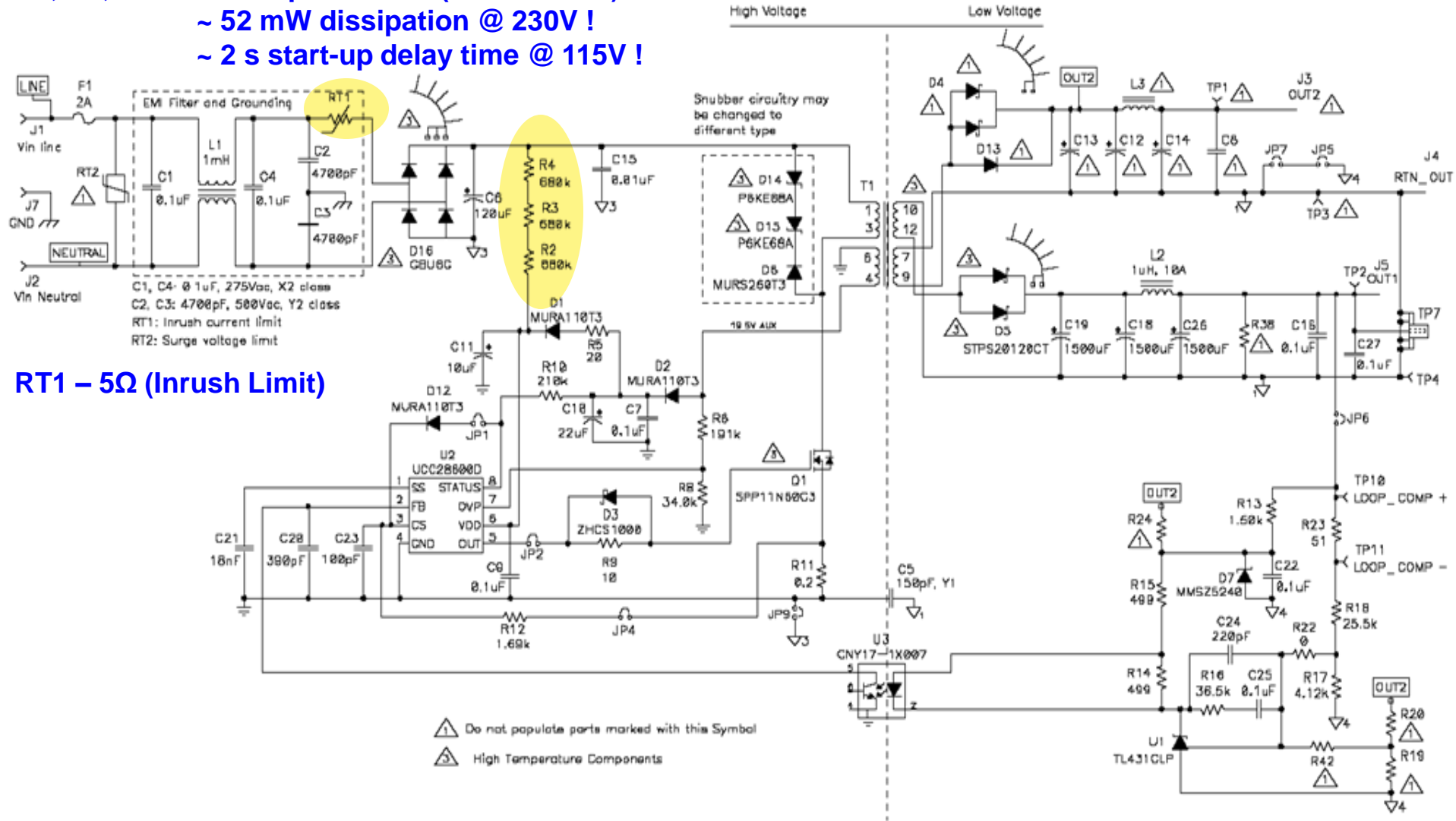

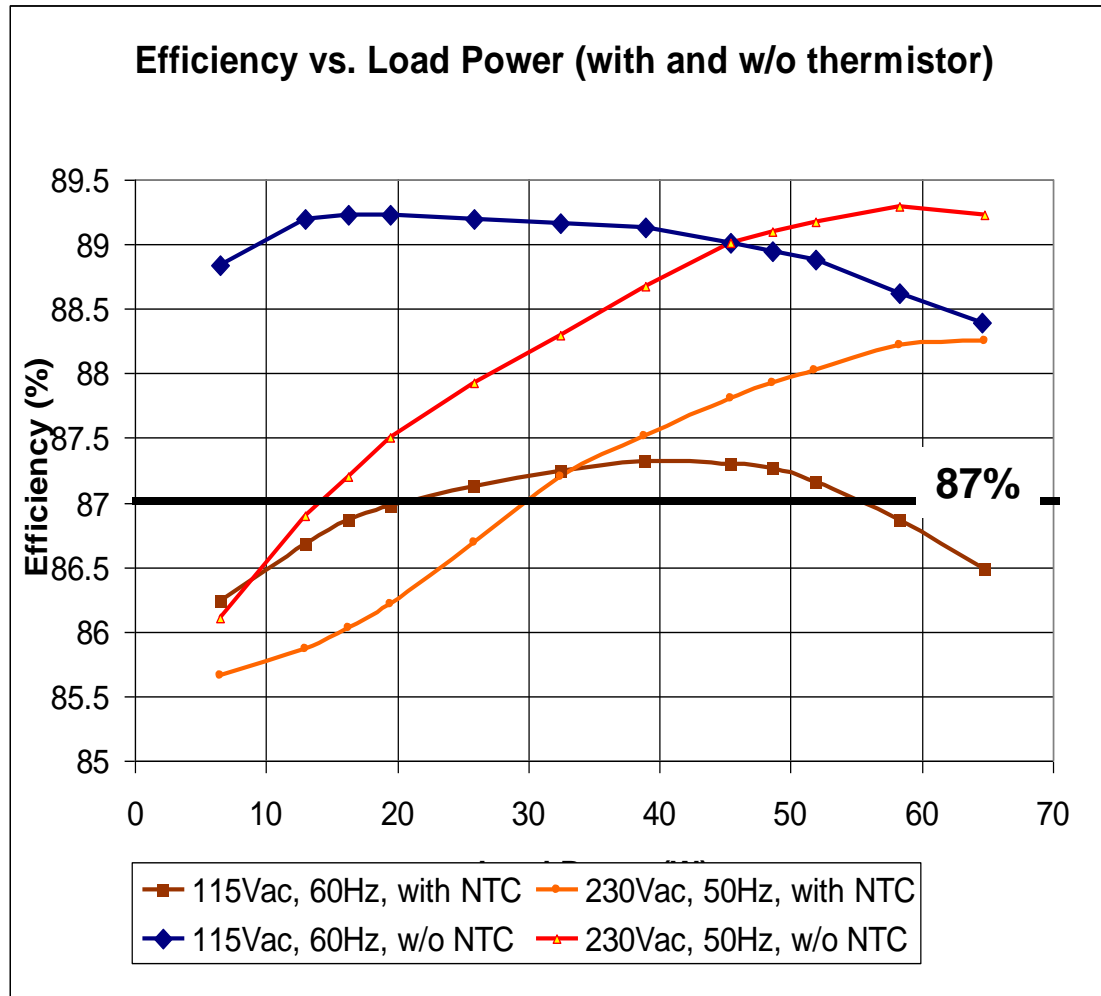UCC28600 – 18V / 65W universal input design EVM




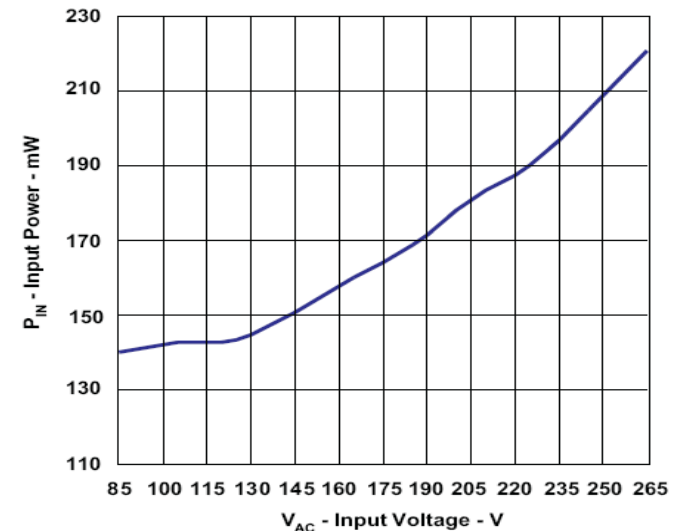**INPUT POWER
vs
INPUT VOLTAGE AT NO LOAD**



Improved start-up

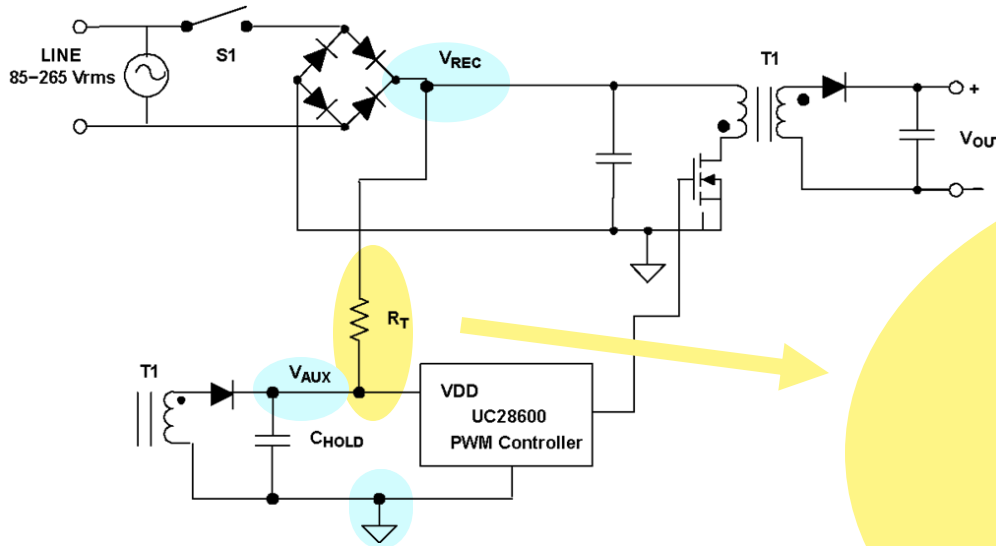
- Reduce continuous dissipation in start-up resistor
 - Reduce no-load power loss caused by start-up resistor
- Reduce start-up delay time
- App Note : Bootstrap Circuit for Green Mode Applications (slua373)



Standard start-up circuit
82 kΩ selected for R_T to reduce
start-up delay to 200 – 600 ms

BUT 1.2 W continuous power dissipation (@230V) !

Improved start-up circuit

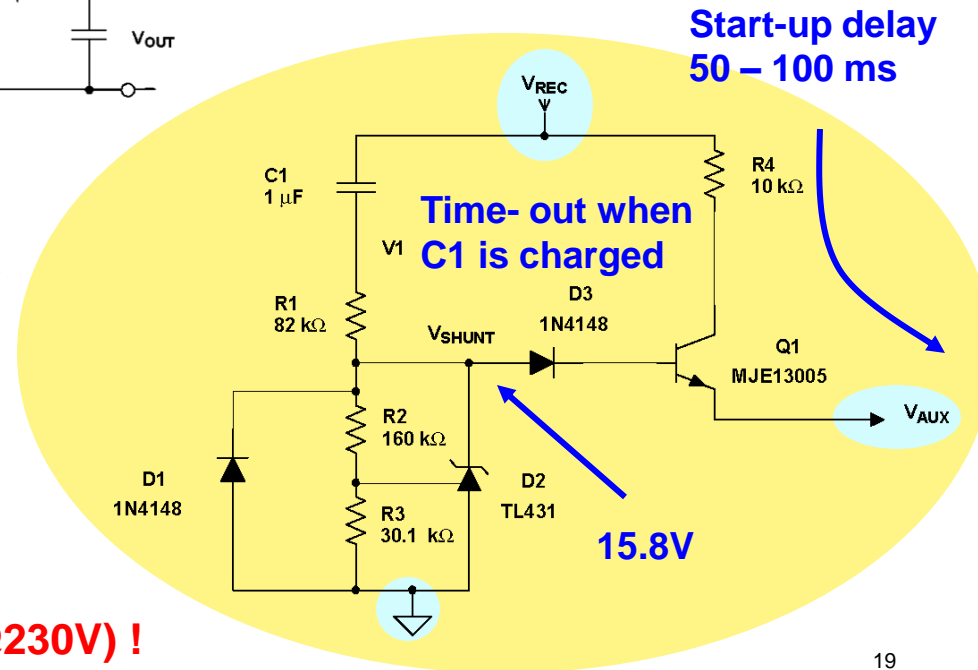


Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- **Cascoded green mode flyback (UCC28610)**
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary


UCC28610 - Cascoded 12 - 65W Green Mode PWM Controller

- Cascoded MOSFET drive for
 - **Integrated current control (no R_{SENSE} required)**
 - **Fast start-up**
 - **Improved MOSFET drive**
 - **Ruggedized design**
- Full Green mode support
 - Frequency and amplitude modulation (FM, AM) and burst mode depending on load
 - Quasi valley switching
 - Ultra-low no-load consumption
- Full set of protection features
 - Advanced OC protection for input & output
 - Timed overload (retry or latch-off)
 - Opto-less output OV protection
 - Fastest latched fault recovery

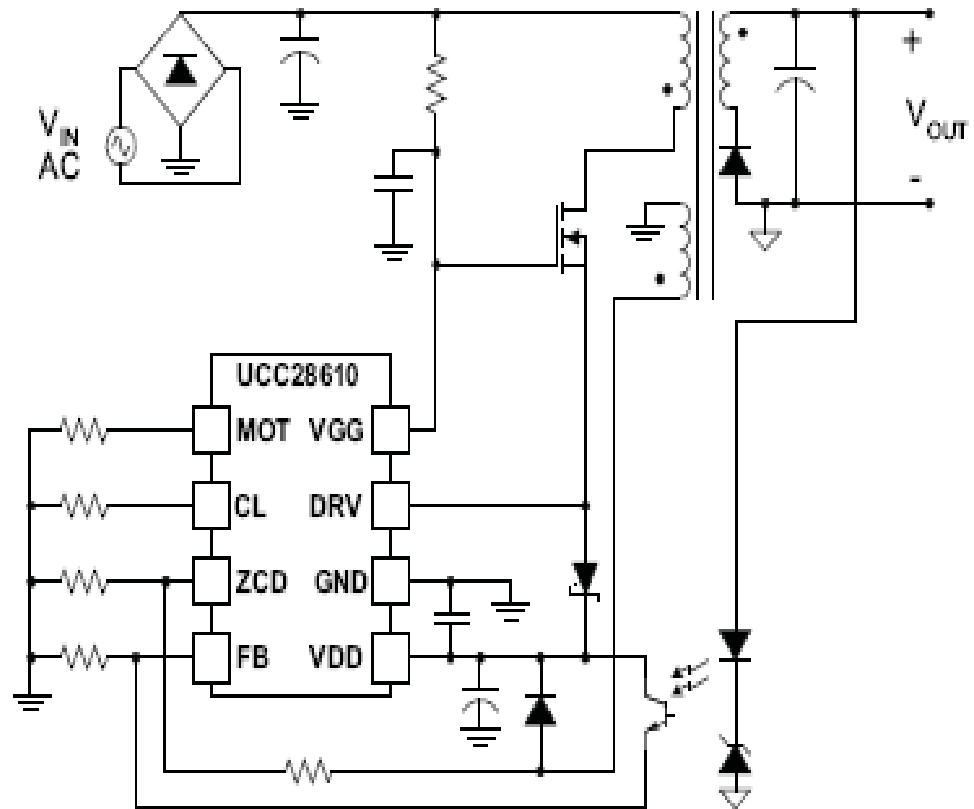


UCC28610 – Design support

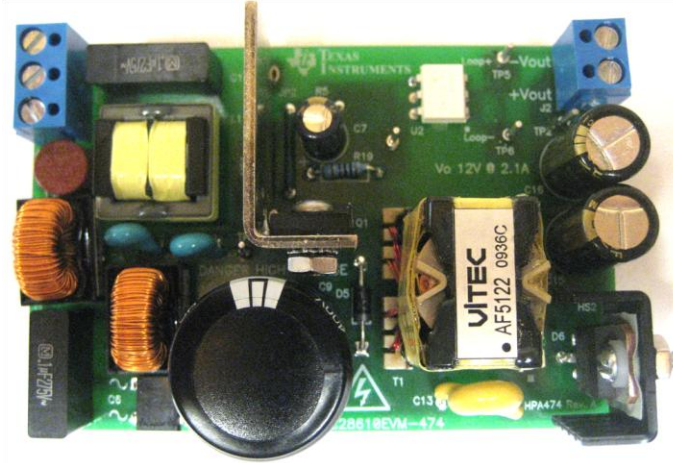- Design tools
 - UCC28610 Design Calculator ([sluc113](#))
- EVMs
 - 25-W Universal Off-Line Flyback Converter EVM ([sluu383a](#))




- Reference designs (15)
- [2010/2011 TI Power Supply Design Seminar](#)
 - topic 1: Under the Hood of Flyback SMPS Designs

UCC28610 – 12V / 25W Universal Off-Line Flyback EVM

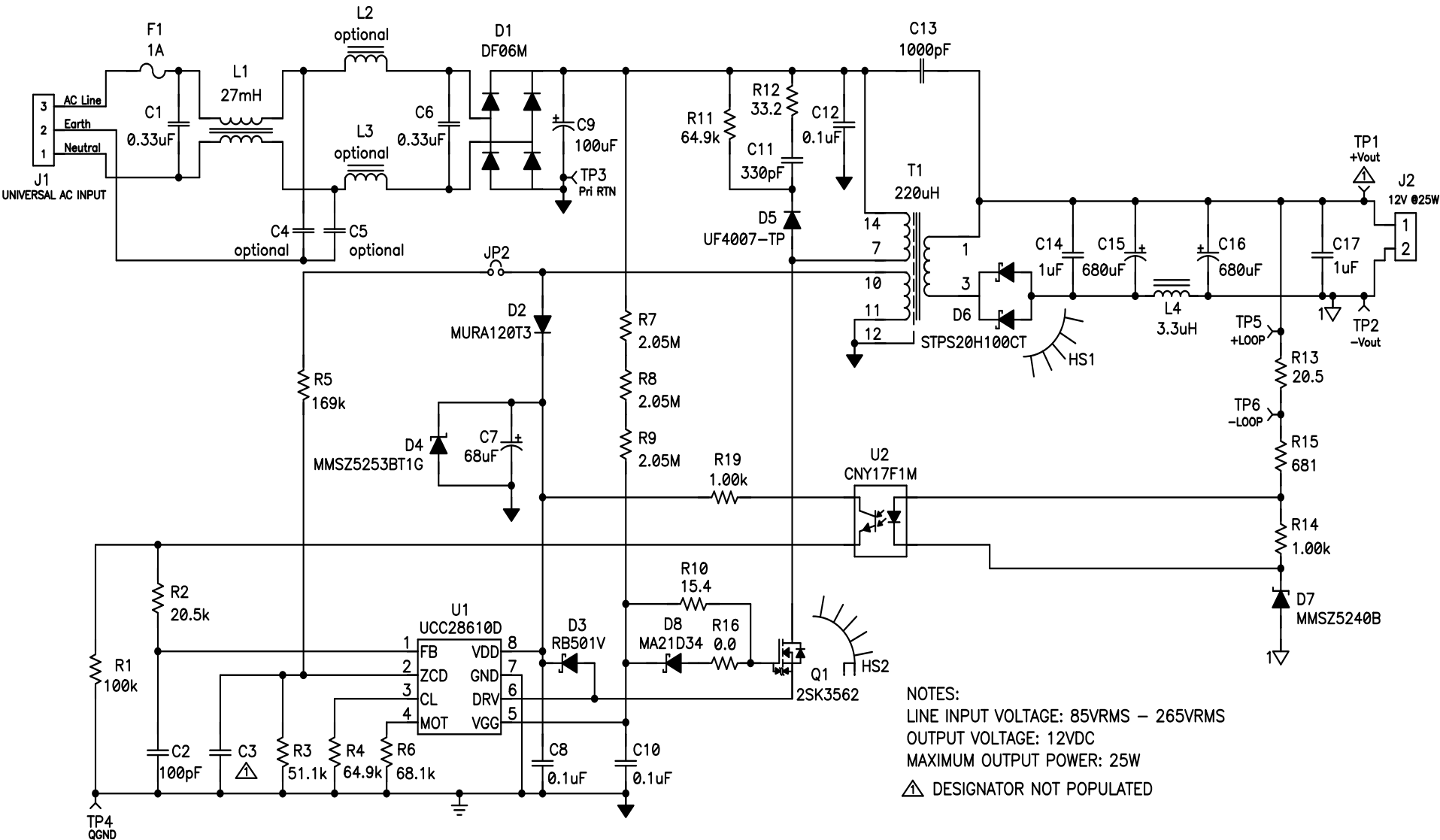

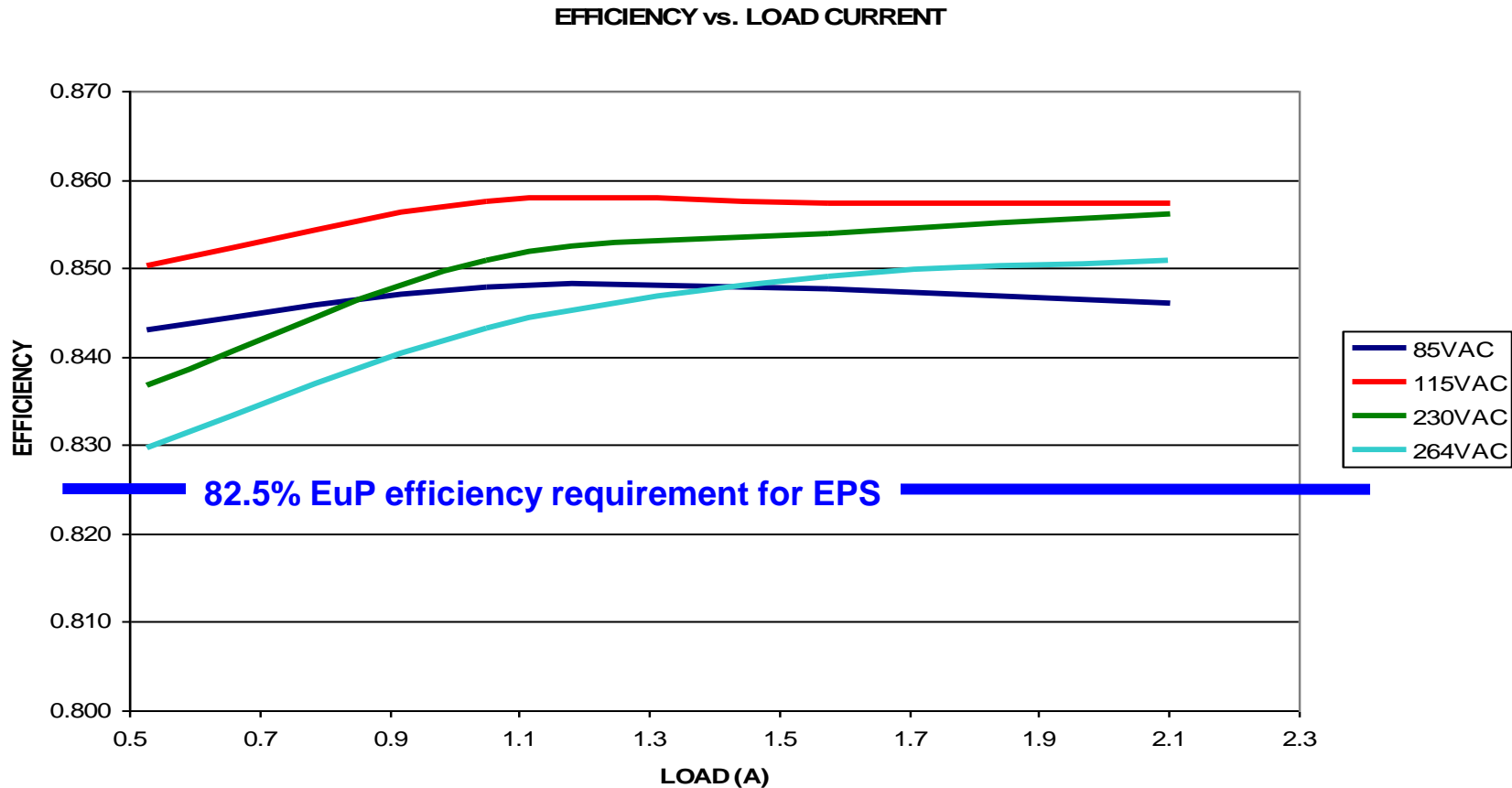UCC28610 – 12V / 25W Universal Off-Line Flyback EVM




- Design fulfills also no-load power consumption requirement: 115mW @ 230V achieved, 300mW allowed by standard
- Start-up delay reduced to roughly 150ms !!!


Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- **Active clamp (UCC289x family)**
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary


(Forward) Transformer Reset Techniques

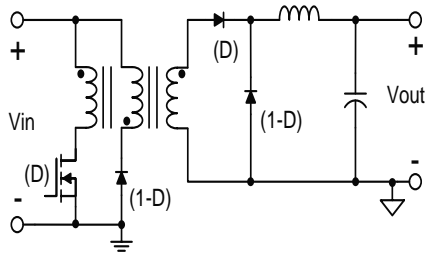


Reset Winding

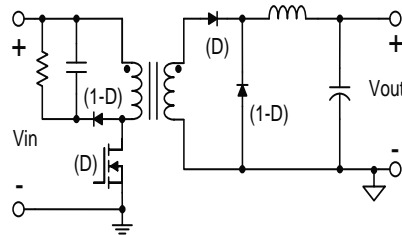

RCD Clamp

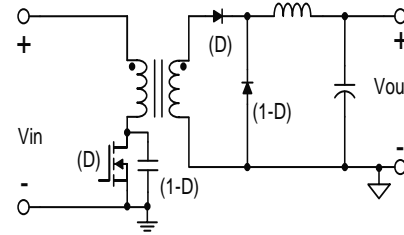

Resonant Reset

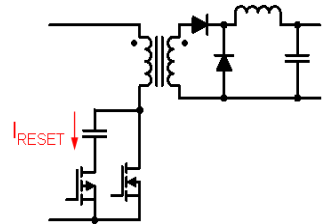


Active Clamp & Reset


	Reset Winding	RCD Clamp	Resonant Reset	Active Clamp and Reset
Soft Switching (ZVS)	No	No	No	✓
Recycles Inductive Energy	✓	No	✓	✓
Recycles Capacitive Energy	No	No	No	✓
> 50 % Dutycycle	No	✓	✓	✓
Complexity	High	Low	Lowest	Highest
Efficiency		Lowest		Highest

UCC2891 / 92 / 93 / 94 / 97A – Active Clamp Controller

	UCC2891	UCC2892	UCC2893	UCC2894	UCC2897A
Additional 2nd level current limit					✓
P-channel Aux FET drive	✓	✓			✓
Bi-directional synchronization					✓
Line overvoltage lockout & hysteresis		✓		✓	
Internal 110V Start-up circuit	✓		✓		✓
Targeted for Off-line AC/DC				✓	

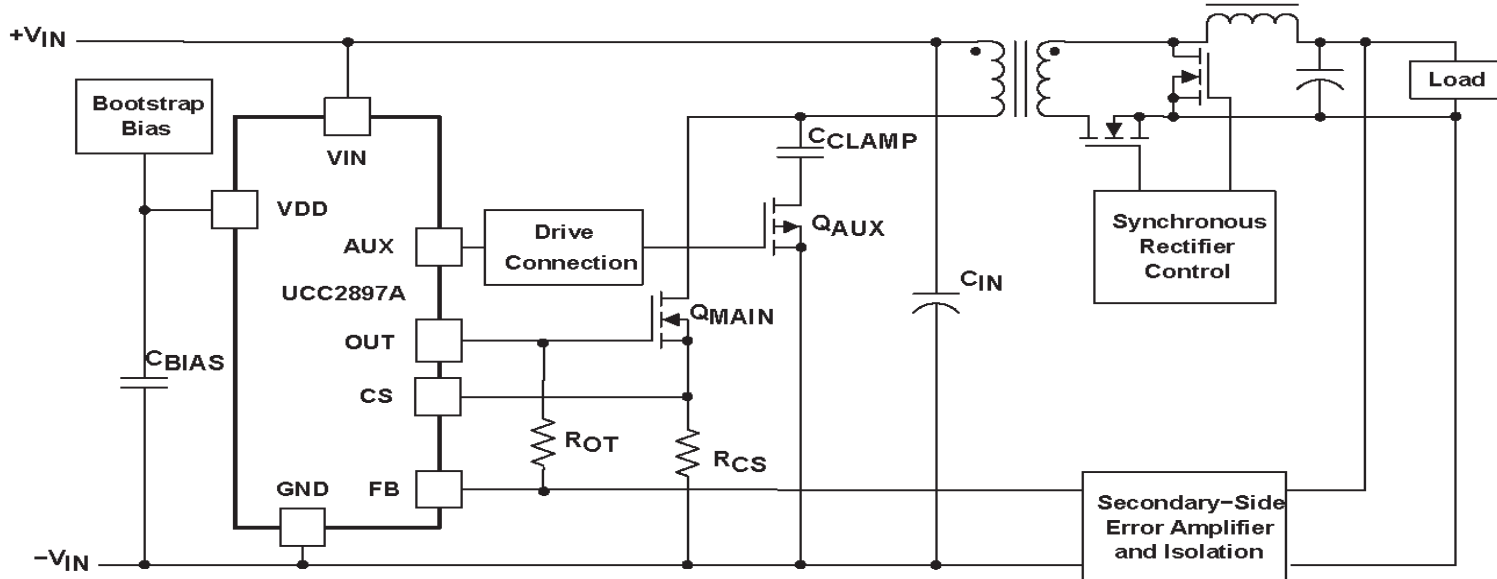

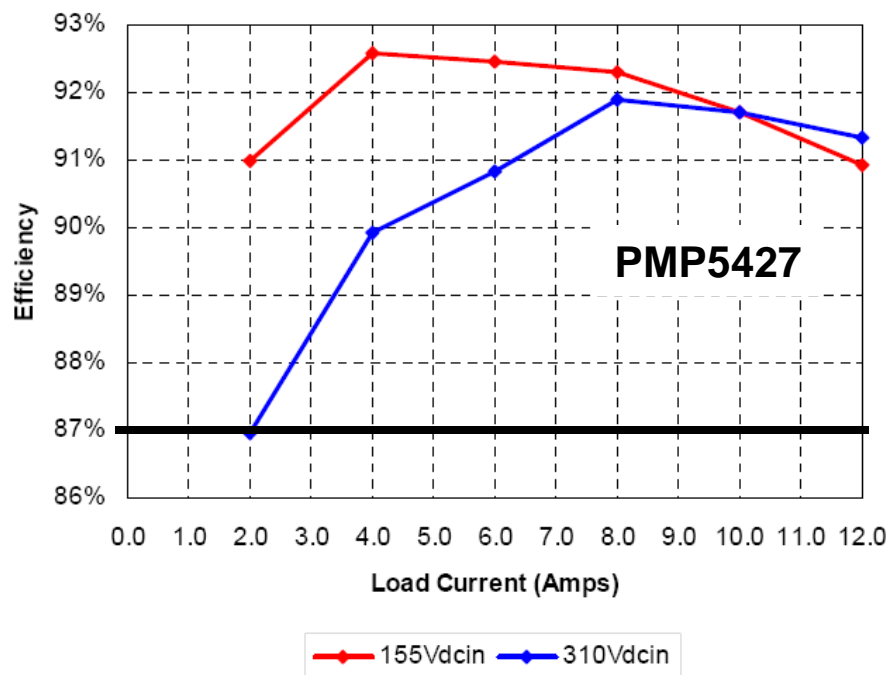UCC2894 – Active clamp forward universal AC input 12V/150W output reference design (PMP5427)



Efficiency was measured by
applying a DC input to the AC lines.

← Design fulfills easily the EuP
requirements for EPS,

BUT most likely an additional PFC stage
will be needed (for >75W) as front-end,
lowering the total efficiency!

PFC provides a regulated output voltage,
allowing to optimize the active clamp
forward converter for that specific
voltage as operating point.

Good PFC efficiency will be in the range
of 92 – 97%, resulting in 85 – 88%
average total efficiency at 25 / 50 / 75 /
100% of rated load.



UCC2891 / 92 / 93 / 94 / 97A – Design support

- Application Notes
 - Understanding and Designing an Active Clamp Current Mode Controlled Converter ([slua535](#))
 - Designing for high efficiency with the active clamp UCC2891 PWM controller ([slua303](#))
 - Active clamp transformer reset: high side or low side? ([slua322](#))
 - U-138 Zero Voltage Switching Resonant Power Conversion ([slua159](#))
- Seminar topics
 - Seminar 1000 - topic 3: active clamp and reset technique enhances forward converter performance ([slup108](#))
 - Seminar 1100 - topic 3: - Consideration for Active Clamp and Reset ([slup112](#))
 - [2010/2011 Seminar](#) – topic 2: Incorporating Active-Clamp Technology to Maximize Efficiency in Flyback and Forward Designs
- EVMs
 - UCC2891EVM, UCC2897EVM (both telecom input)
- Reference Designs
 - More than 150 tested designs for industrial, automotive, telecom and AC/DC off-line applications


Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- **Interleaved PFCs (UCC2806x / 28070)**
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary

CCM - vs. TM - PFC

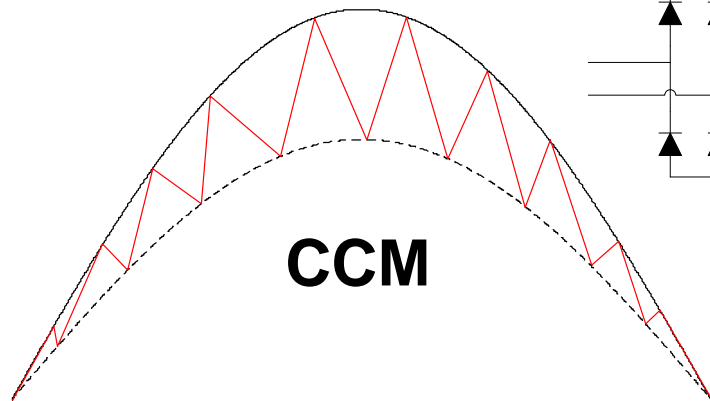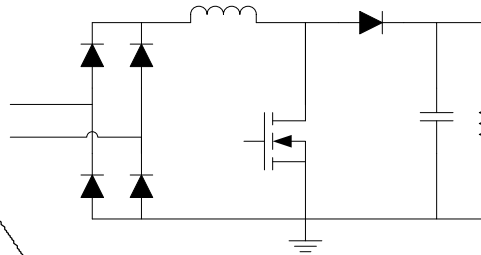


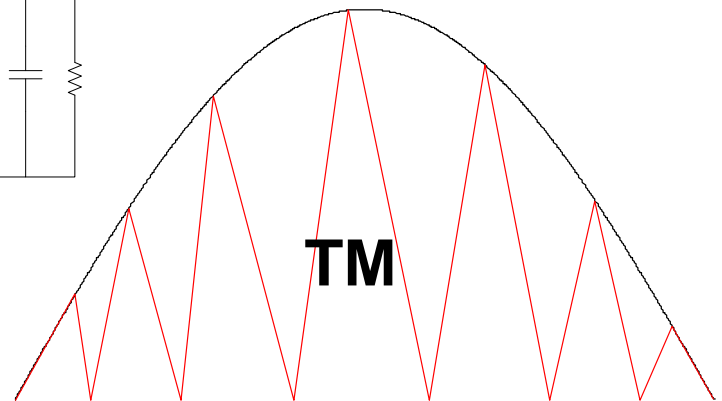- Smaller ripple current
- Smaller EMI filter
- Constant switching frequency
- Better for higher power
- Switching loss may be higher due to diode reverse recovery current
- High components cost to maintain high efficiency




- No reverse recovery loss - ZCS
- Lower cost solution
- Soft switching possible
- Variable switching frequency
“Natural spread spectrum”
- Better for lower power
- Large HF current ripple, larger conduction loss (AC resistance!)
- Larger EMI filter

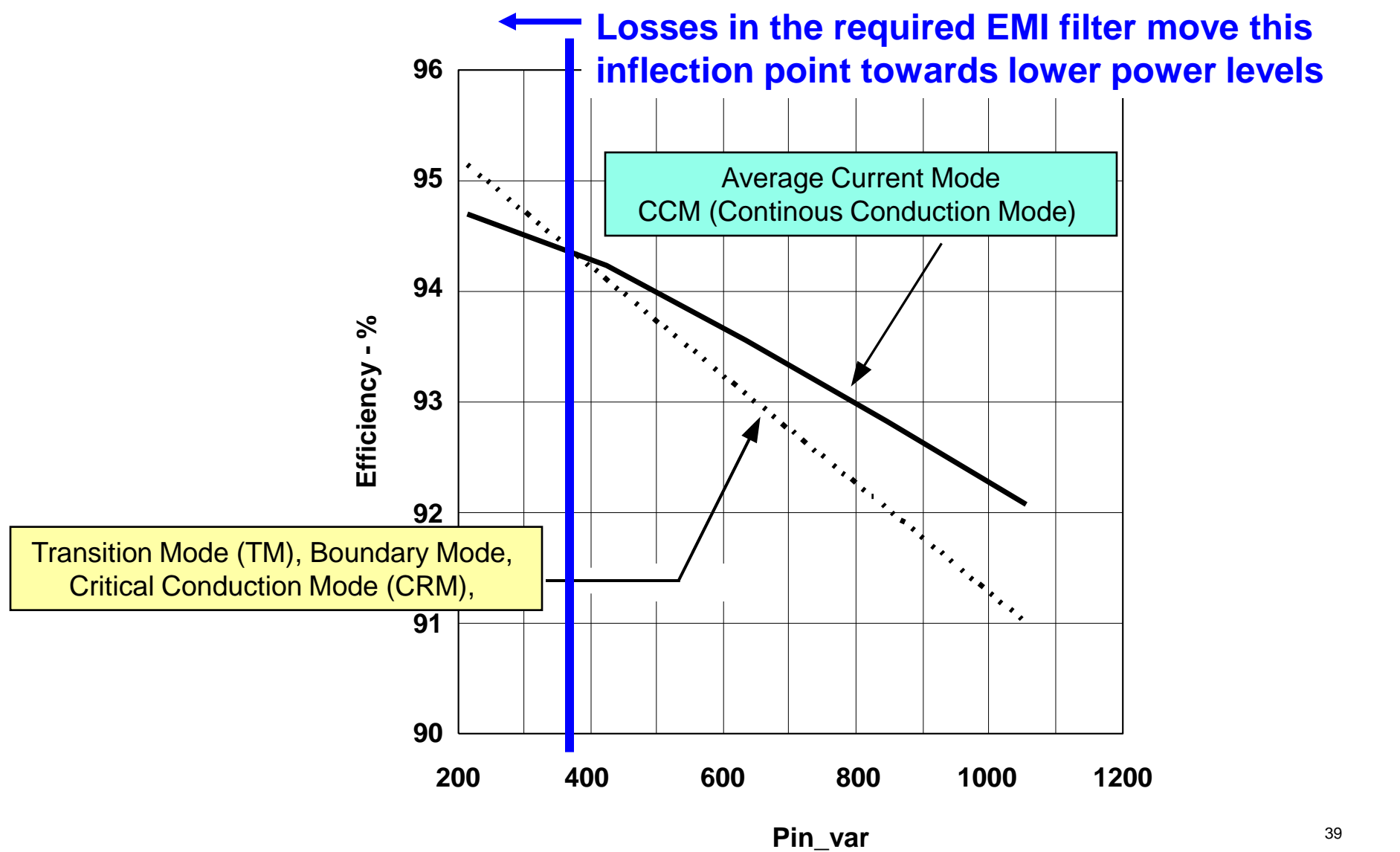
Inflection Point TM vs. CCM w/o input EMI filter (single phase)



Interleaved PFC

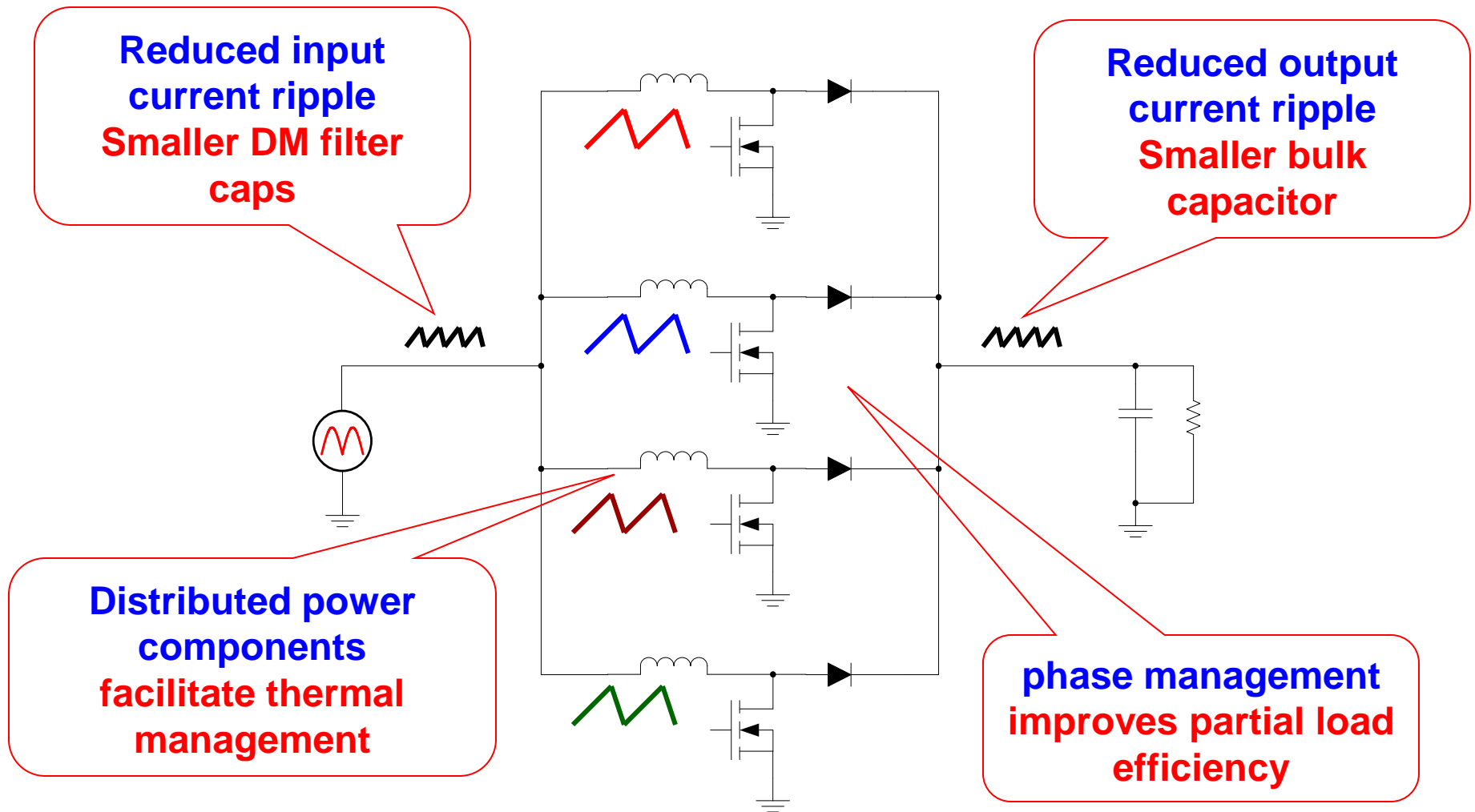

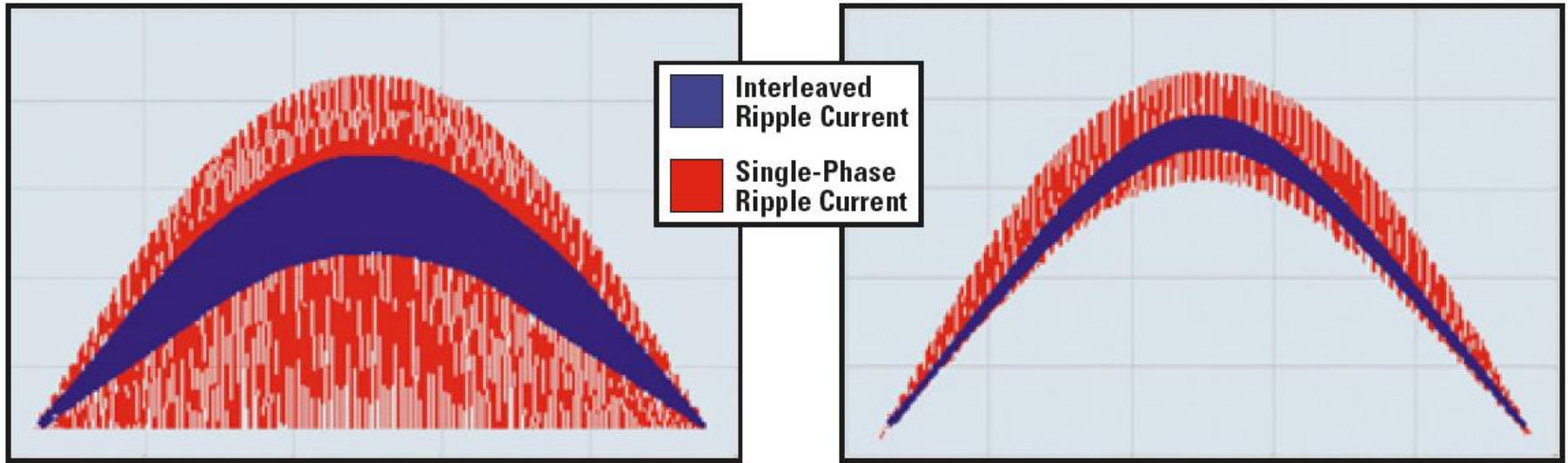Interleaved PFC – Significant input ripple current reduction



UCC28060 Transition Mode PFC with Natural Interleaving™ technique.

UCC28070 Continuous Conduction Mode PFC.

EMI-Filter needs to take care of Ripple Current



- EMI-Filtering can be drastically reduced due to drastically reduced ripple current
- Ripple of Interleaved TM is similar to Single Phase CCM

TI solves the interleaving problems for TM boost PFC

UCC28060 Industry's First Natural Interleaving™ Transition Mode PFC


UCC28061 **UCC28060**

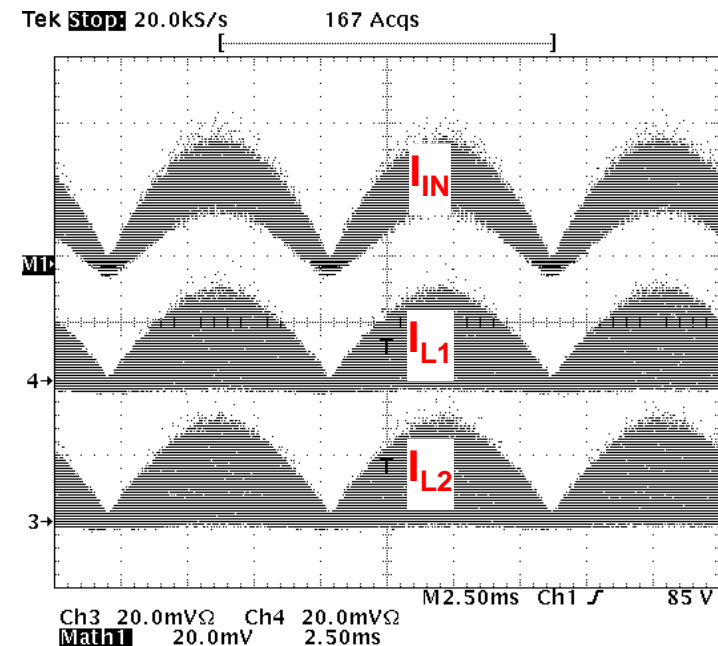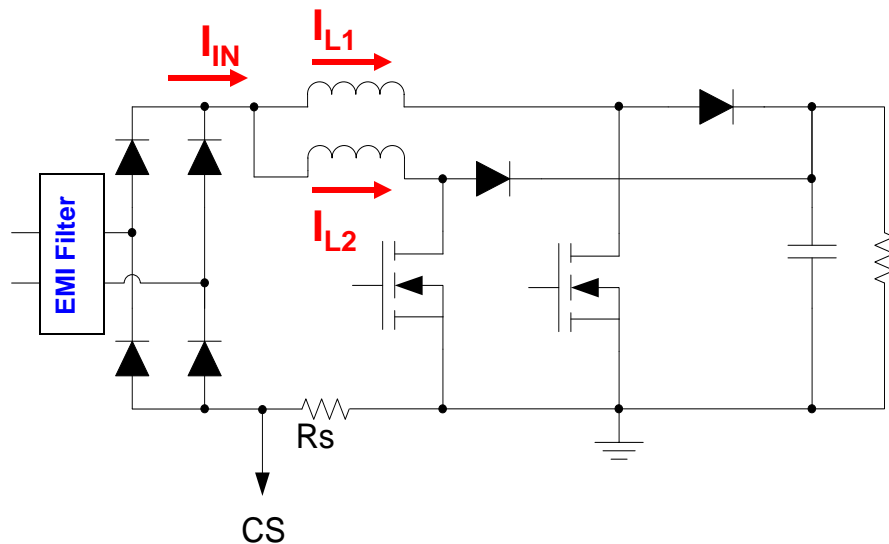- w/ improved audible noise performance
- w/ auto soft re-start after OV-Faults
- w/o Burstmode @ light load




UCC 28060 / 61 uses Natural Interleaving

Master- Slave Method

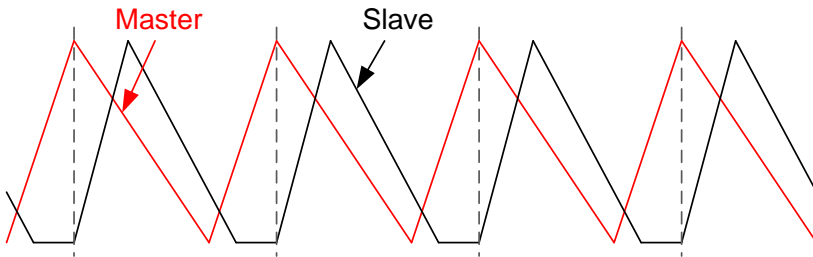

- Lower Inductance in the slave phase to prevent entering CCM
- Phase shift not optimal
- Current sharing not optimal


Natural Interleaving

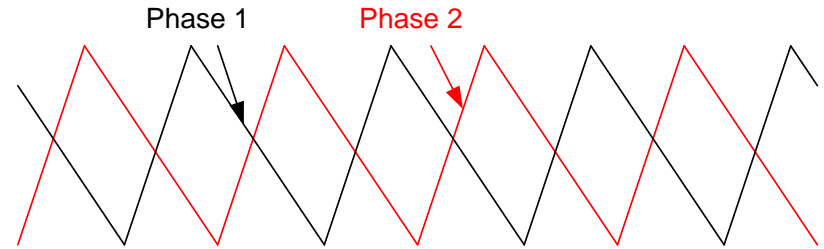



- Both channels operate in TM
- Phase shift of the phases is 180
- No Master / no Slave

**Better current sharing
and lower ripple current**

UCC28060 / 28061 Typical circuit

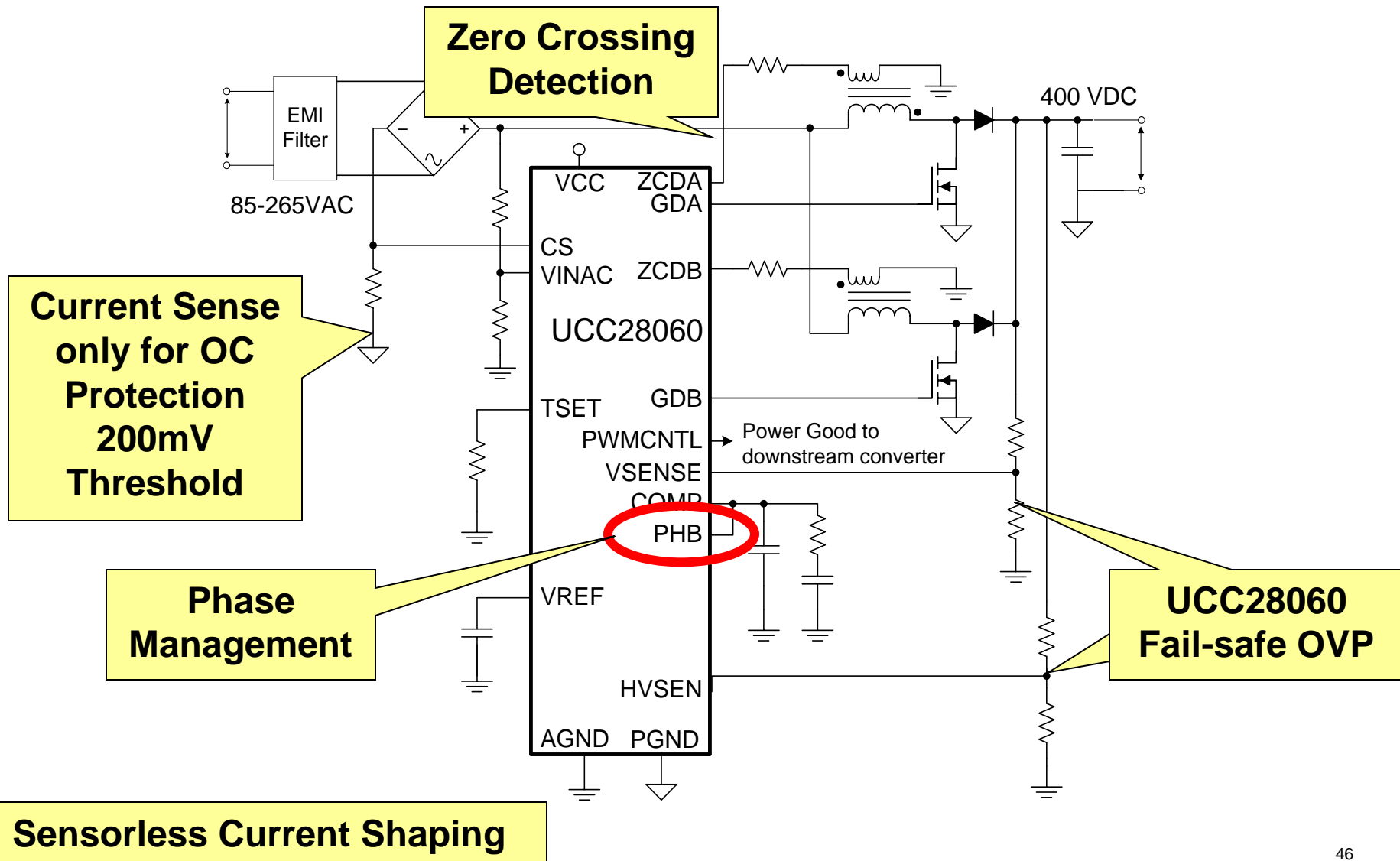

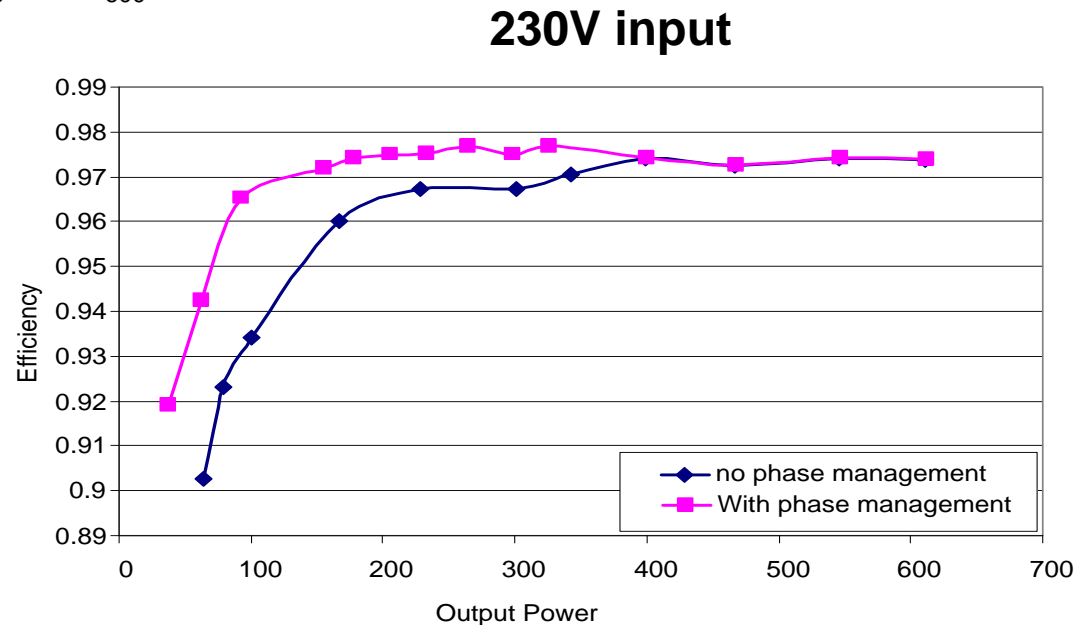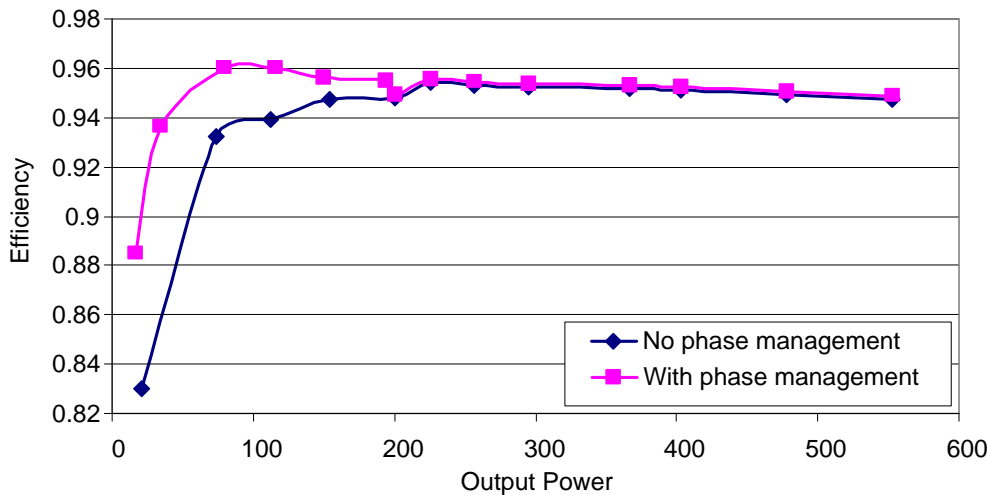
UCC28060 - Phase management improves light load efficiency



- Single-phase operation at light load conditions improves system efficiency
- Phase management improves system efficiency at different line and load conditions

UCC28060 / 61 - Design support

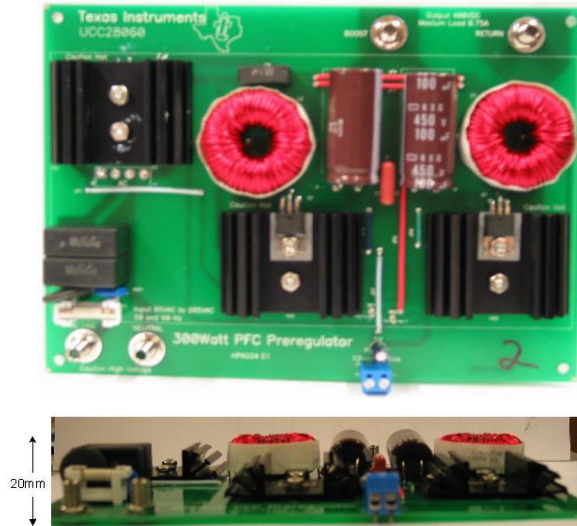- 300W EVM ([sluu280b](#) , [sluu316](#))
20mm height



- 600W Design User Guide ([sluu299a](#))
- AppNotes:
 - A 300-W, Universal Input, Isolated PFC Power Supply for LCD TV Applications ([sluu341b](#))



- Excel Design Tool ([sluc072b](#))

UCC28060 Controller Setup Tool		
Note this tool was designed to work with the UCC28060 data sheet design example		
Please enter design parameters into the shaded cells;		
Calculated results will be in RED		
Design Parameters:	Variable Names	
Minimum RMS Input Voltage	V _{IN_MIN}	85
Maximum RMS Input Voltage	V _{IN_MAX}	265
Minimum Line Frequency	f _{LINE}	47
Maximum Line Frequency		63
Maximum Output Power	P _{OUT}	300
Full Load Efficiency (Needs to be less than 0.99)	η	0.92
Minimum Switching Frequency	f _{MIN}	4.50E+04
Output Voltage	V _{OUT}	390


- Additional AppNotes and MathCAD
Files in productfolder of UCC38050 / 51
 - UCC38050 100W Critical Conduction (PFC) Reference Design ([sluu138a](#))
 - MathCAD Calculation Tool for UCC38050 Transition Mode PFC Controller ([UCC38050-CALC](#))

PFC - TI solves the interleaving problems for CCM Boost PFC

UCC28070 Industry's First Interleaved CCM Boost PFC

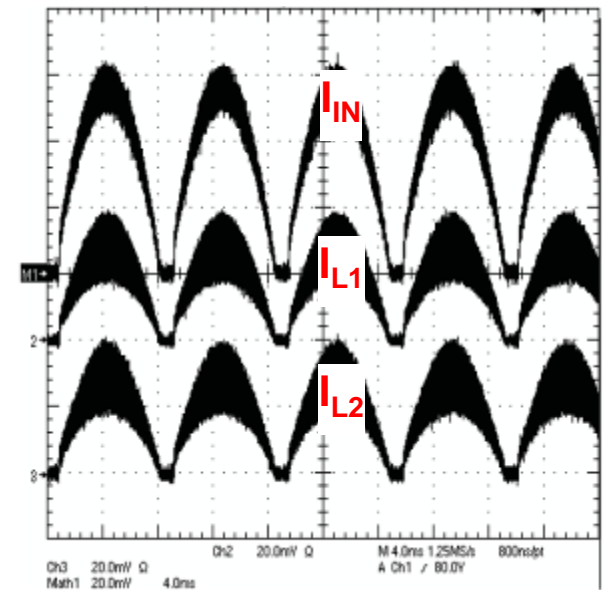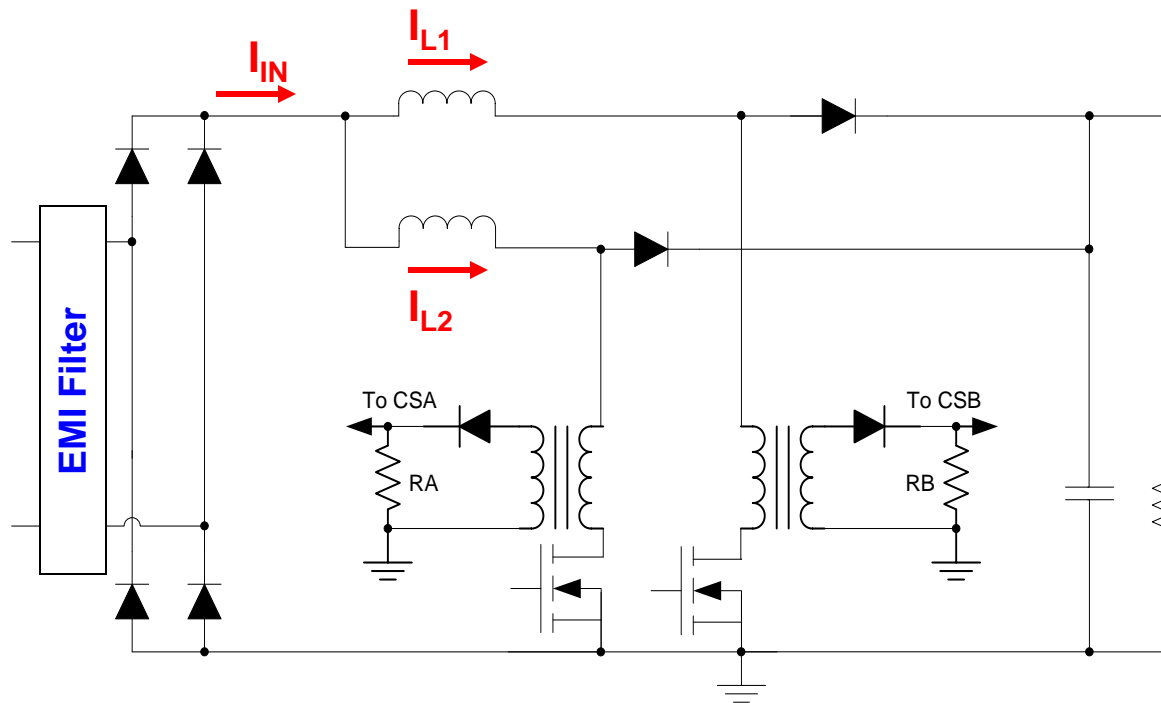

UCC28070 - Average CM interleaved PFC

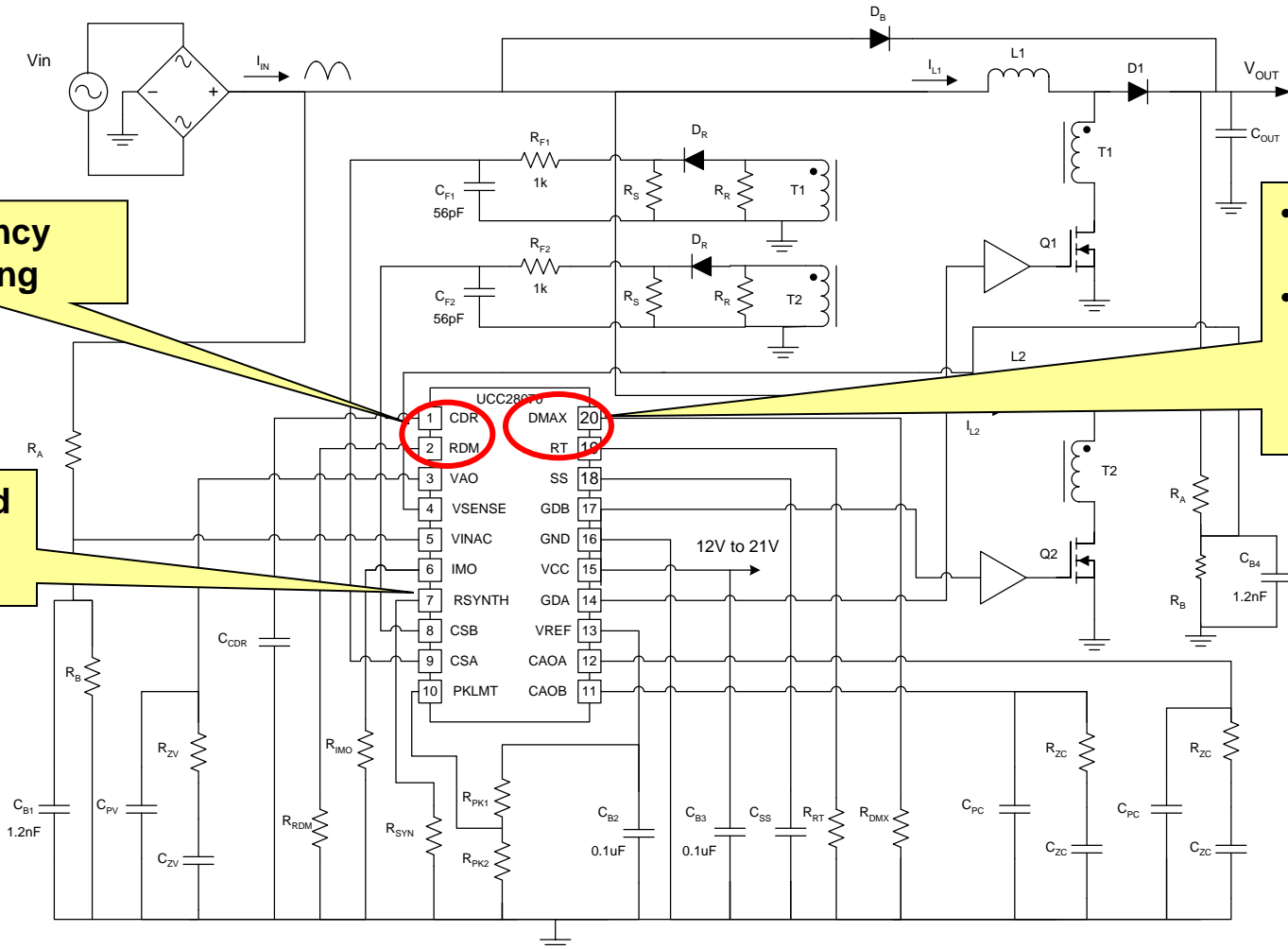

Frequency
Dithering

Synthesized
Diode
Current

- Max
Dutycycle
- Switching
Frequency
(30 ... 300kHz
per Phase)



UCC28070 - Current syntheses reduces component count

➤ Traditional Current Sensing in PFC Boost

- ✓ Requires a CT network in series with Q1
- ✓ Requires a CT network in series with D3



➤ UCC28070 Synthesizes Diode Current

- ✓ Setup with Single Resistor to Gnd (R_{SYN})
- ✓ **Removes CT network in series with D3**
- ✓ **6 components are eliminated in interleaved configuration**
 - ❖ **Results in a cheaper BOM cost**

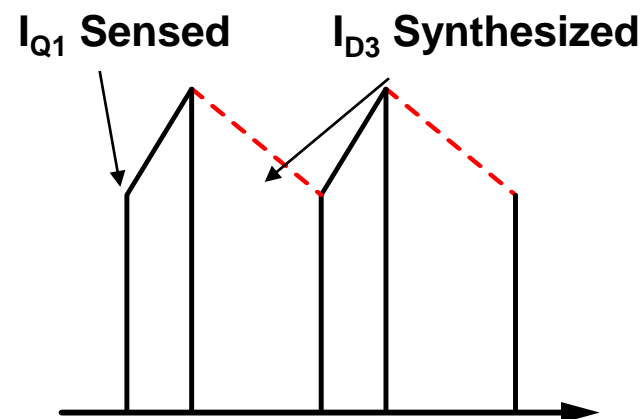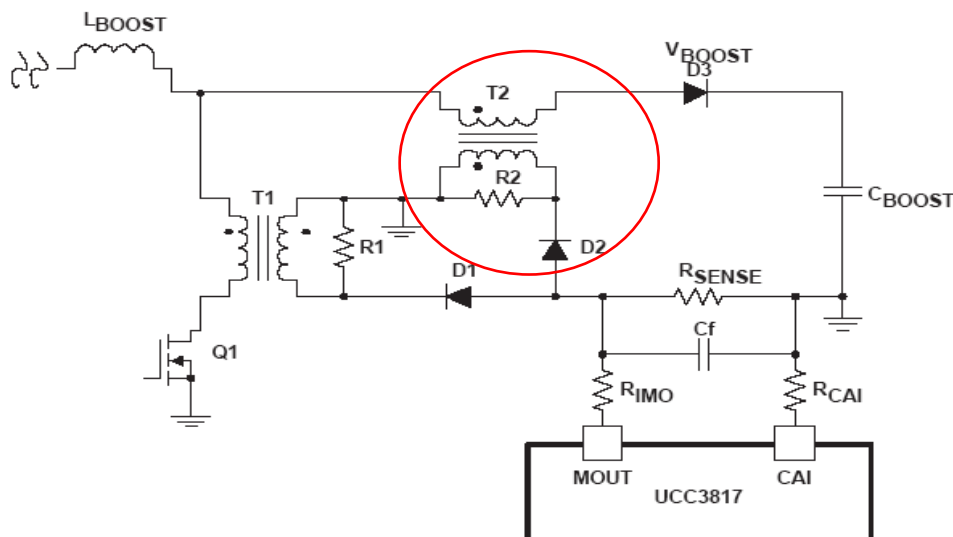

UCC28070 - Support & design tools

- Detailed Application Note
 - (Design Review) ([slua479a](#))
 - UCC28070 Bridgeless PFC ([slua517](#))
- 300 W Evaluation Module ([sluu312b](#))
 - ✓ Same Power as UCC28060
- ✓ UCC28070 Video Cast SLUC083
- Excel Design Tool ([sluc114](#))
 - ✓ Theoretical Small Signal Analysis
- ✓ PSpice Models
 - ✓ UCC28070 PSpice Average Model
 - ✓ UCC28070 PSpice Transient Model

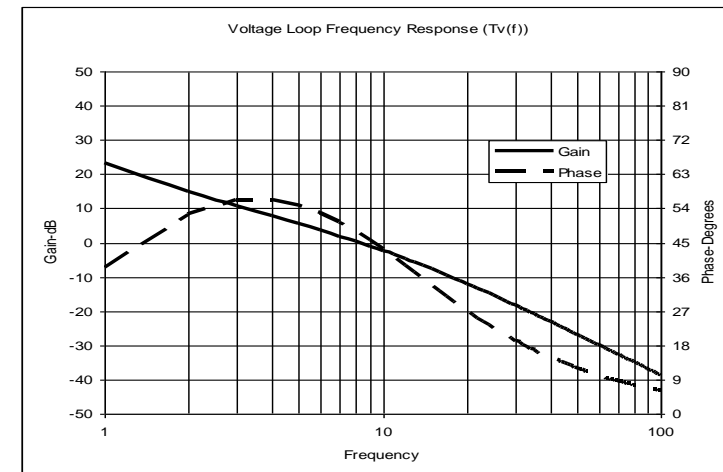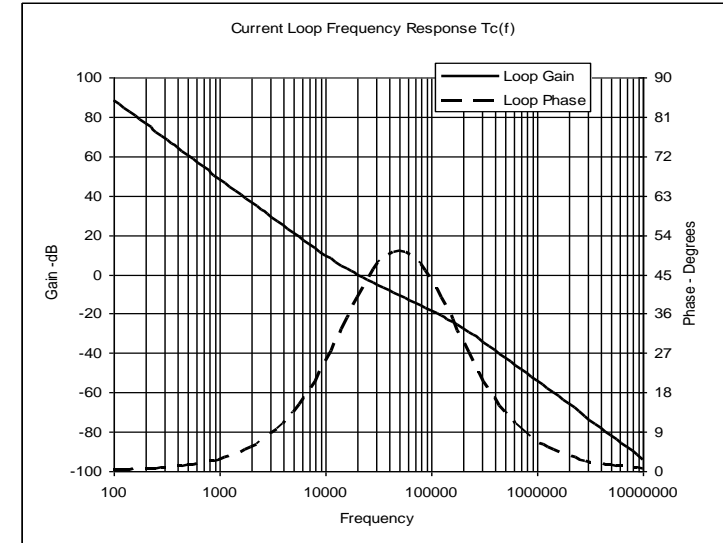

UCC28070 – 1.2kW Reference Design w/ implemented Phase Management



Enormous reduction in size of boost inductors
by use of 2-phase interleaved approach




PR779 / 780

Phase Management w/ Interleaved PFCs (UCC28070 – 1.2KW Example Shown)

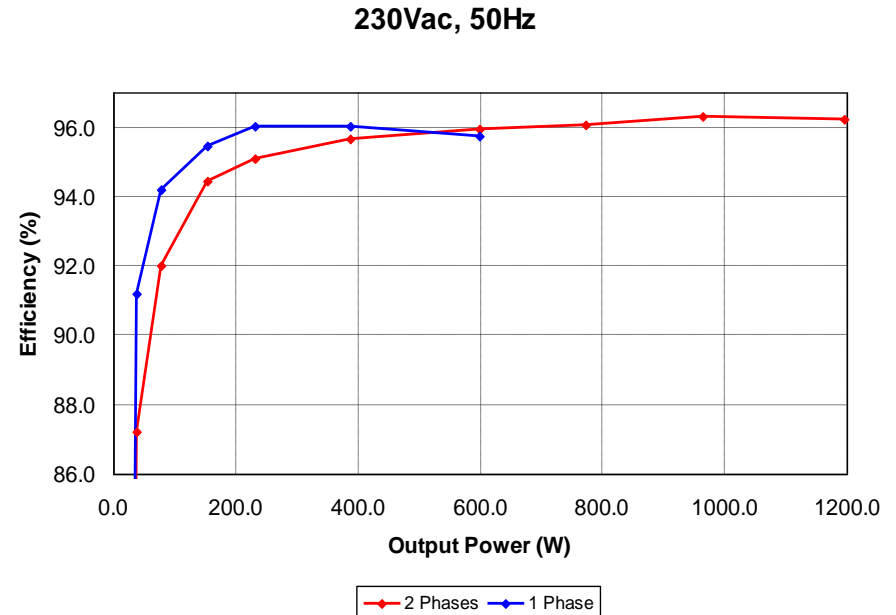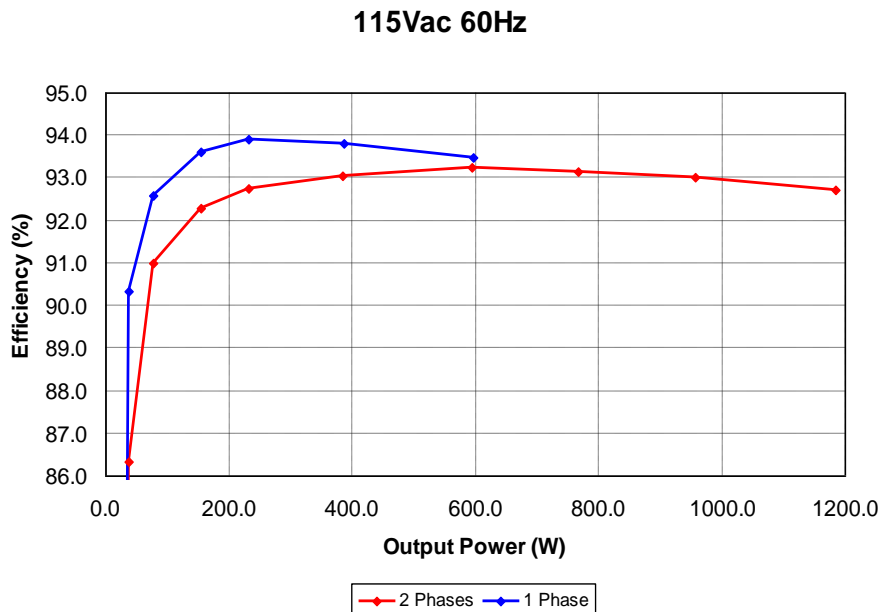Phase Management Ensures
Highest Efficiency under all Load Conditions





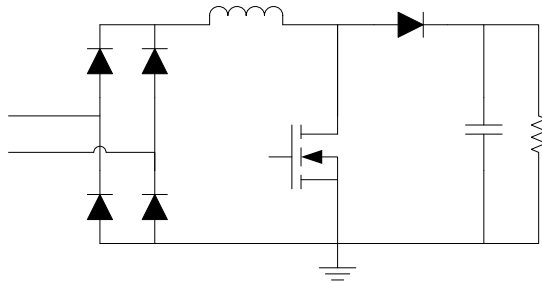Increase PFC efficiency further? Implementation of bridgeless PFC




Classical PFC with bridge rectifier

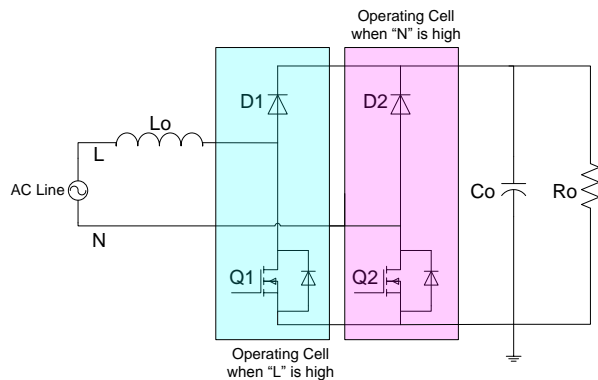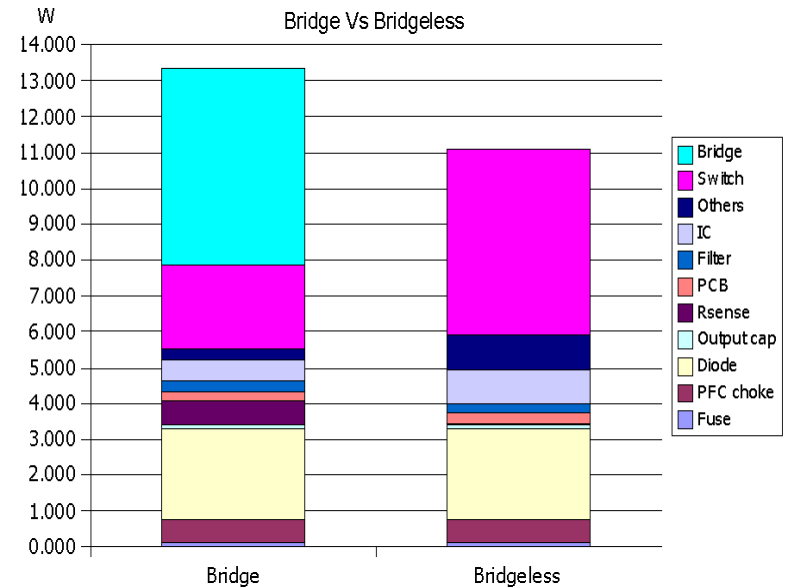Goal of bridgeless PFC:
Increase efficiency by eliminating
some of the losses of the bridge rectifier



Classical bridgeless PFC implementation

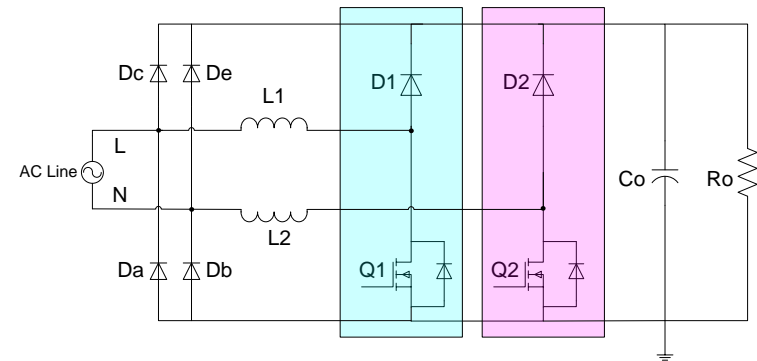


Semi-bridgeless PFC implementation

Increase PFC efficiency further? Implementation of bridgeless PFC

- UCC28070 Implement Bridgeless Power Factor Correction (PFC) Pre-Regulator Design – [SLUA517](#)

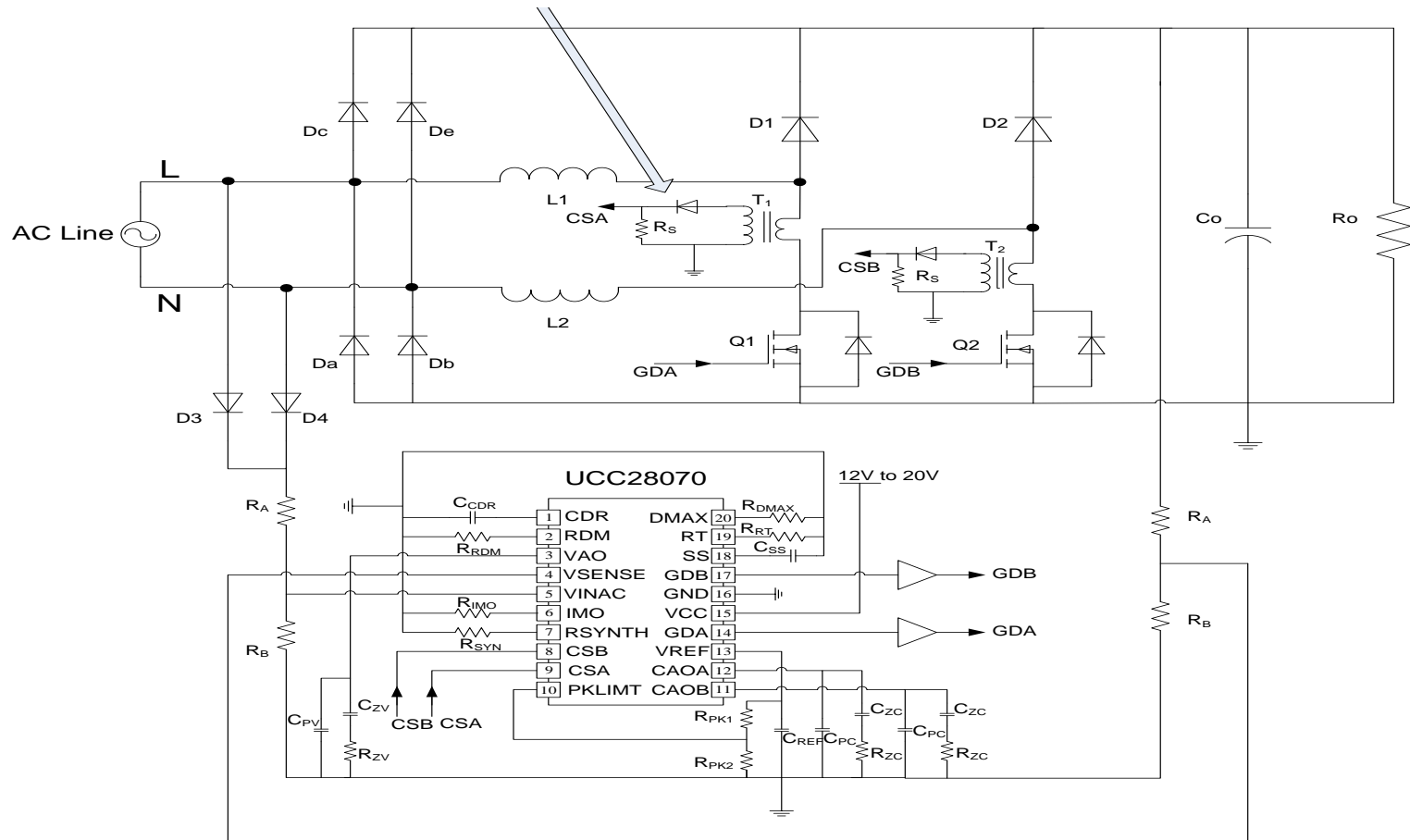Current synthesizing of UCC28070 simplifies implementation



Increase PFC efficiency further? Implementation of bridgeless PFC

- UCC28070 Implement Bridgeless Power Factor Correction (PFC) Pre-Regulator Design – [SLUA517](#)

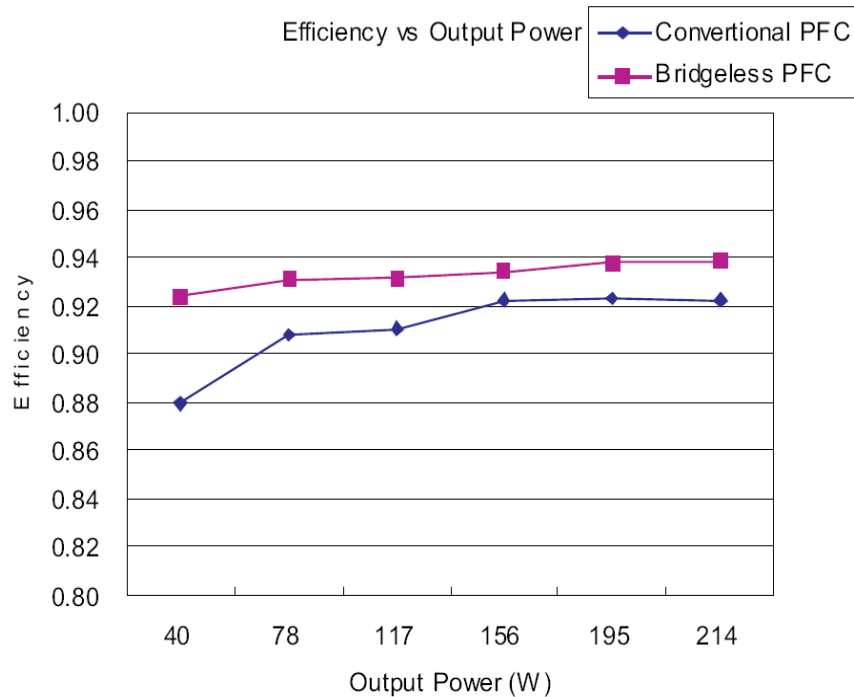


Figure 9. Efficiency at $V_{IN}=110 V_{AC}$


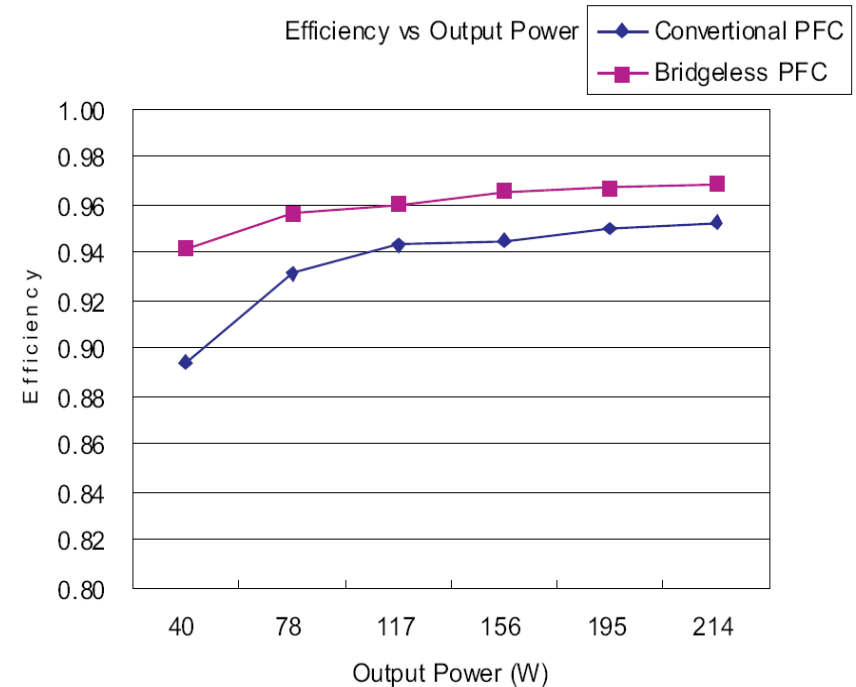


Figure 10. Efficiency at $V_{IN} = 220 V_{AC}$

Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- **LLC resonant half bridge (UCC25600)**
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary


LLC Resonant half bridge – the details

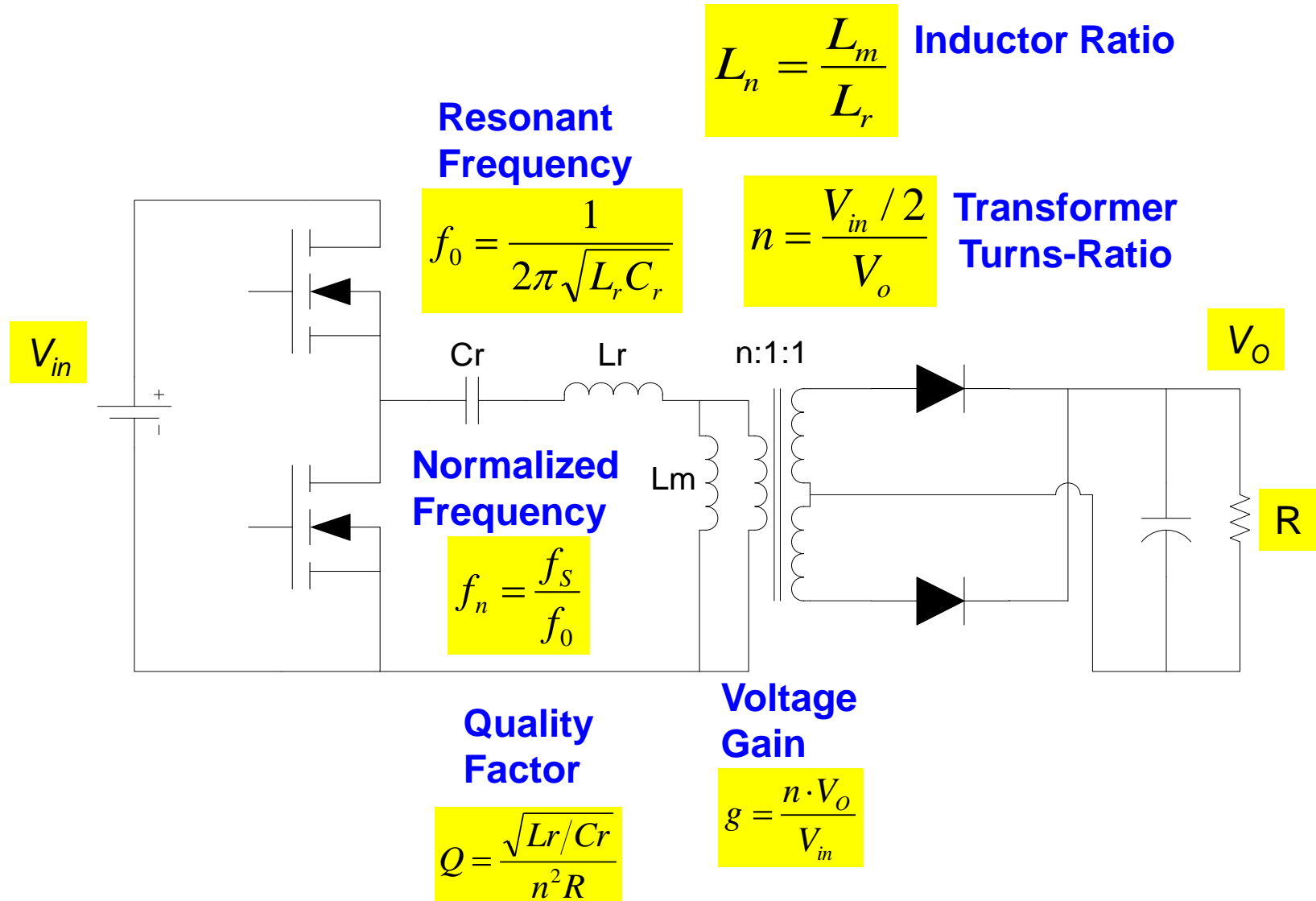

LLC Resonant half bridge

UCC25600

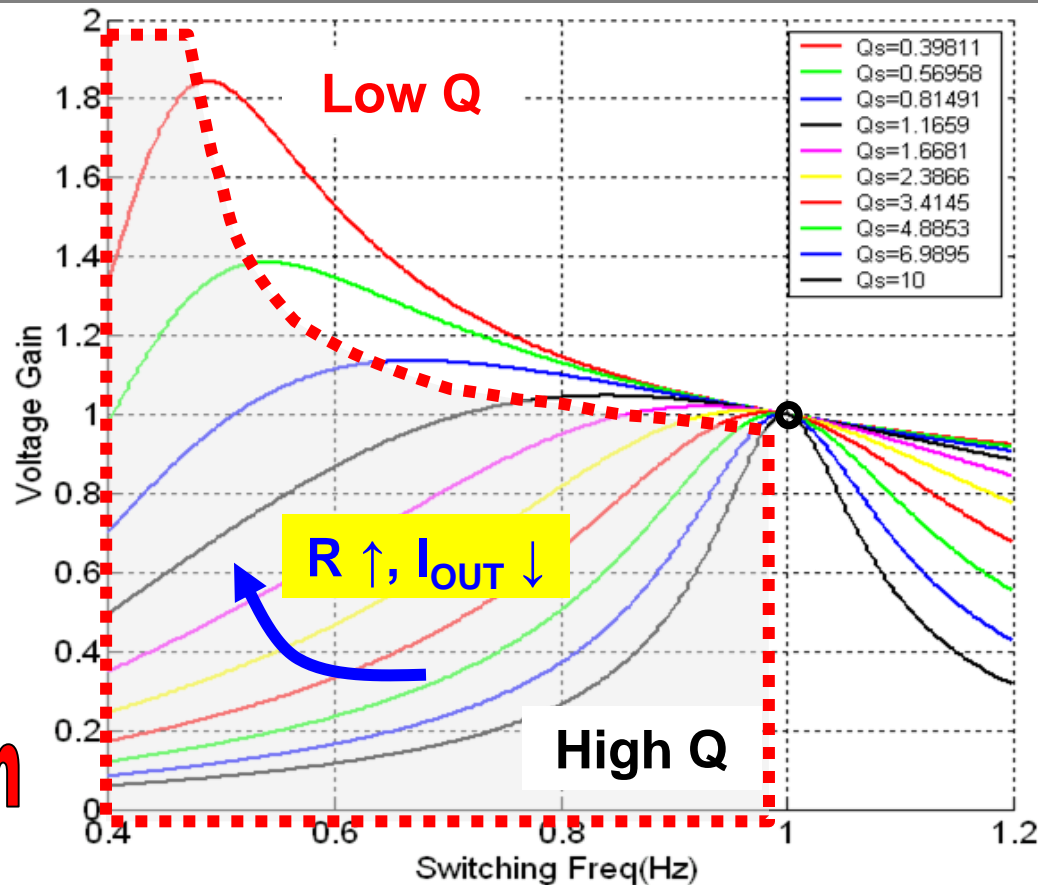8-Pin Optimized High Performance LLC HB Resonant Mode Controller




ZVS region

$$Q = \frac{\sqrt{L_r / C_r}}{n^2 R}$$

ZCS region

UCC25600 Application Circuit

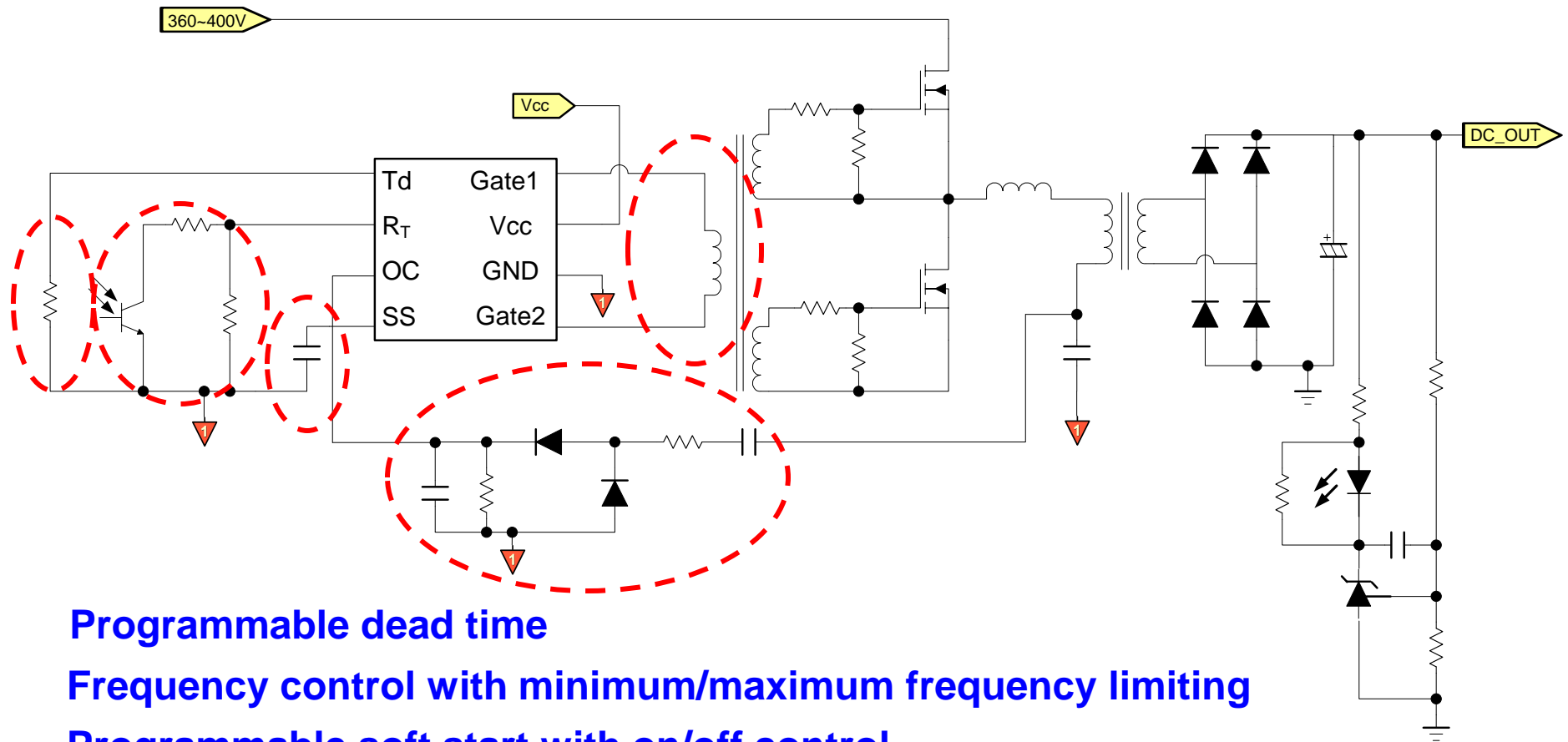

Programmable dead time

Frequency control with minimum/maximum frequency limiting

Programmable soft start with on/off control

Two level over current protection, auto-recovery and latch up

Matching output with 50ns tolerance


UCC25600 - Support & design tools

➤ App Note

- A 300-W, Universal Input, Isolated PFC Power Supply for LCD TV Applications ([sluu341b](#))
- U-138 Zero Voltage Switching Resonant Power Conversion ([slua159](#))

➤ Evaluation Module

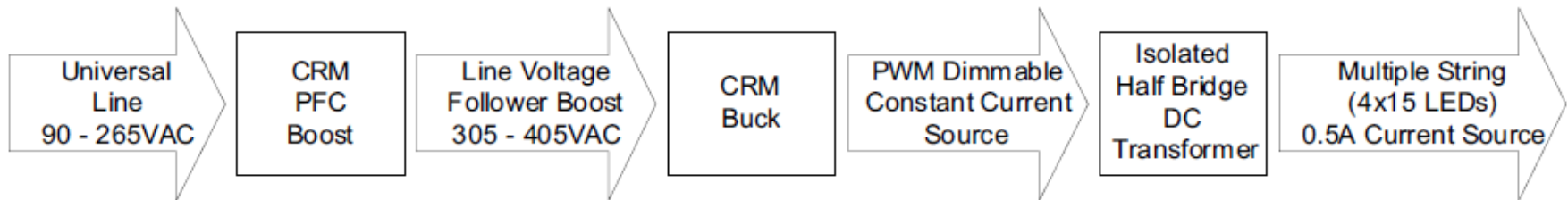- LLC Resonant Half Bridge Converter 300 W Evaluation Module ([sluu361](#))
- UCC28810EVM-003 110W Multiple String LED Driver with Universal Line Input and PF ([sluu380a](#))




➤ Excel Design Tool ([sluc146](#))



➤ Seminar Topics

- Seminar 700 Topic 6: Resonant Mode Converter Topologies -Additional Topics ([slup092](#))
- Seminar 600 Topic 1: Resonant Mode Converter Topologies ([slup085](#))
- [2010/2011 Seminar](#) – topic 3: Designing an LLC Resonant Half-Bridge Power Converter

UCC25600 – 300W EVM Performance VIN: 390VDC, VOUT:12V

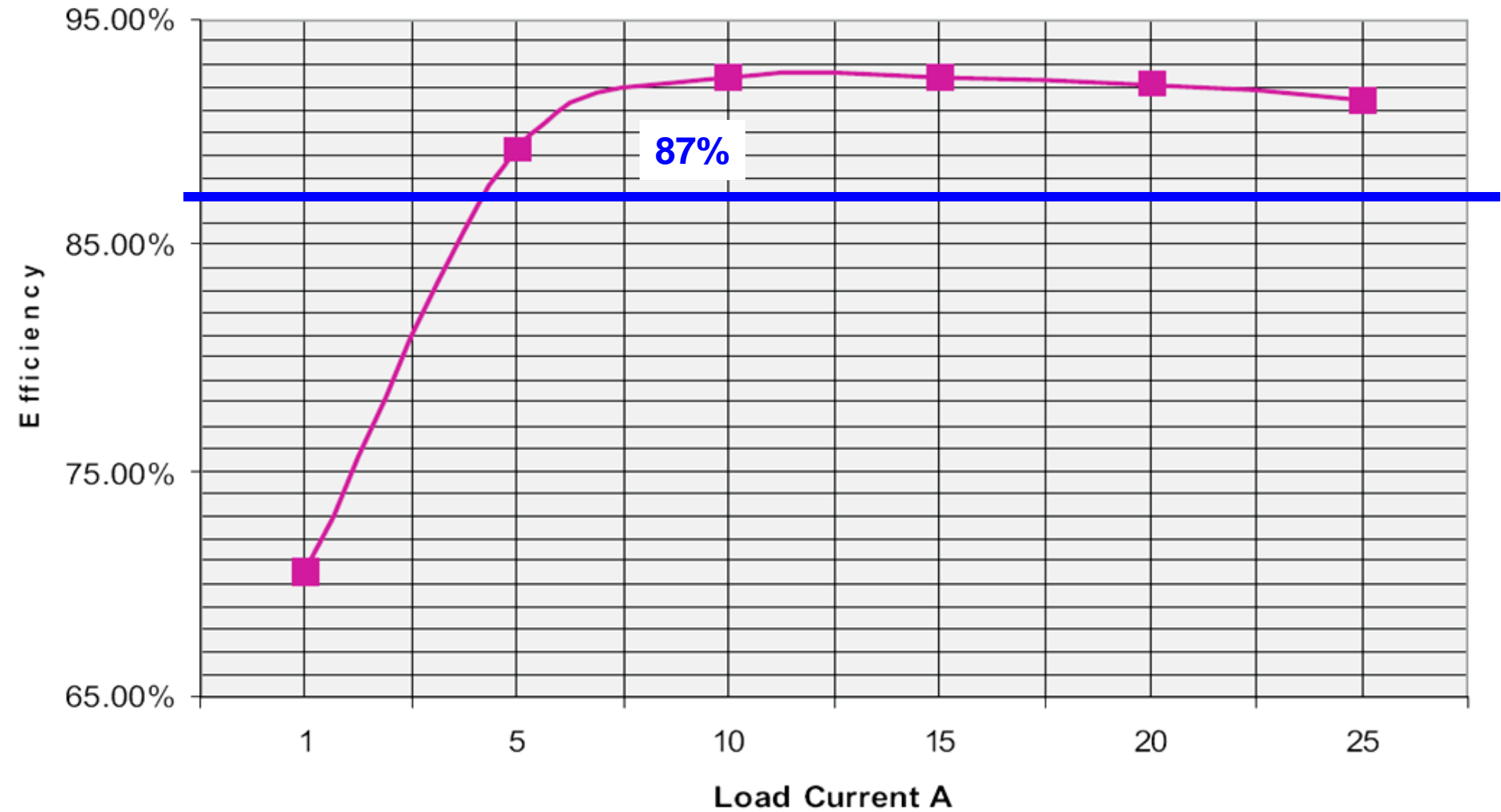

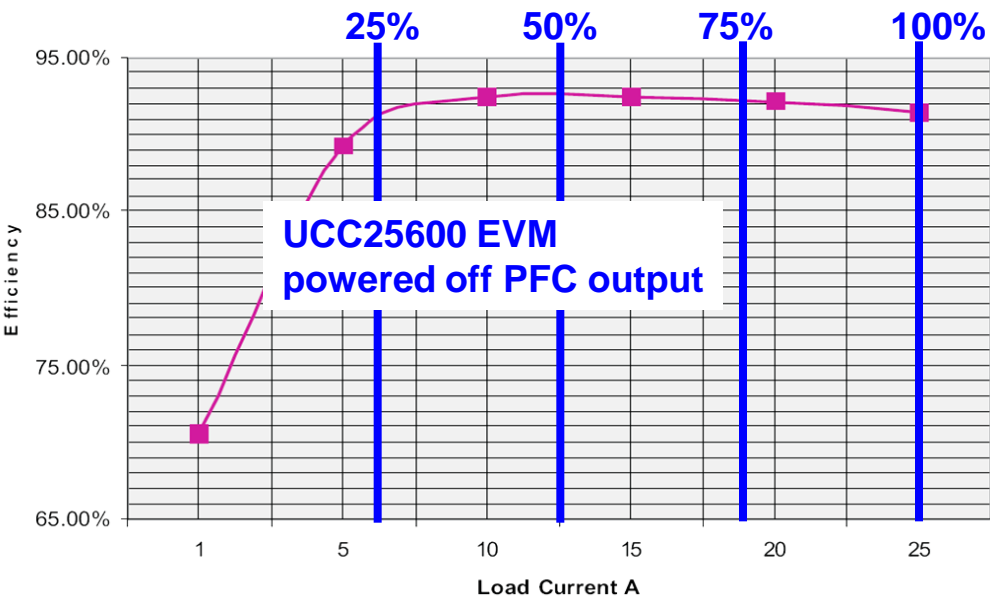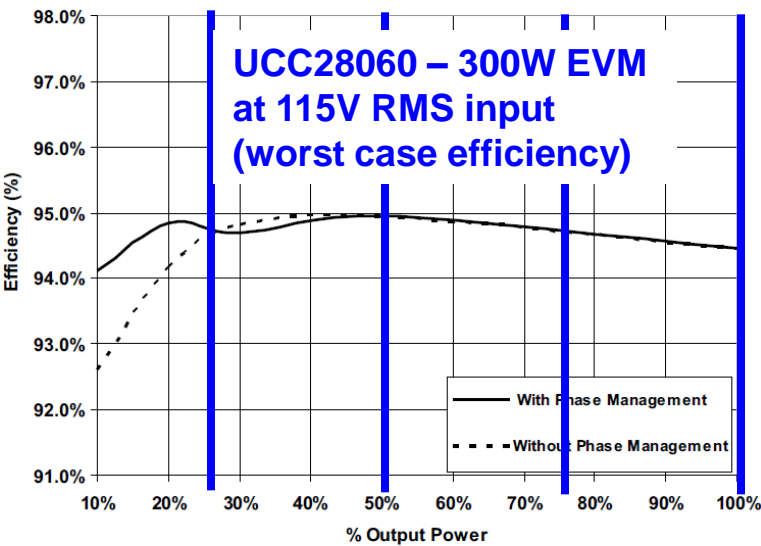UCC25600 – 300W EVM: total efficiency together w/ UCC28060 EVM




% of rated POUT	η of PFC (%)	η of LLC HB (%)	Total Efficiency (%)
25	94.7	91.0	86.2
50	94.9	92.7	88.0
75	94.7	92.2	87.3
100	94.4	91.5	86.4
Average			87.0

UCC25600 + UCC28060 fulfill 87% efficiency requirements for EPS as requested by EuP directive

Agenda


- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- **Green synchronous rectifier controller (UCC24610)**
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support
- Summary

Schottky Diode vs. Synchronous Rectifier

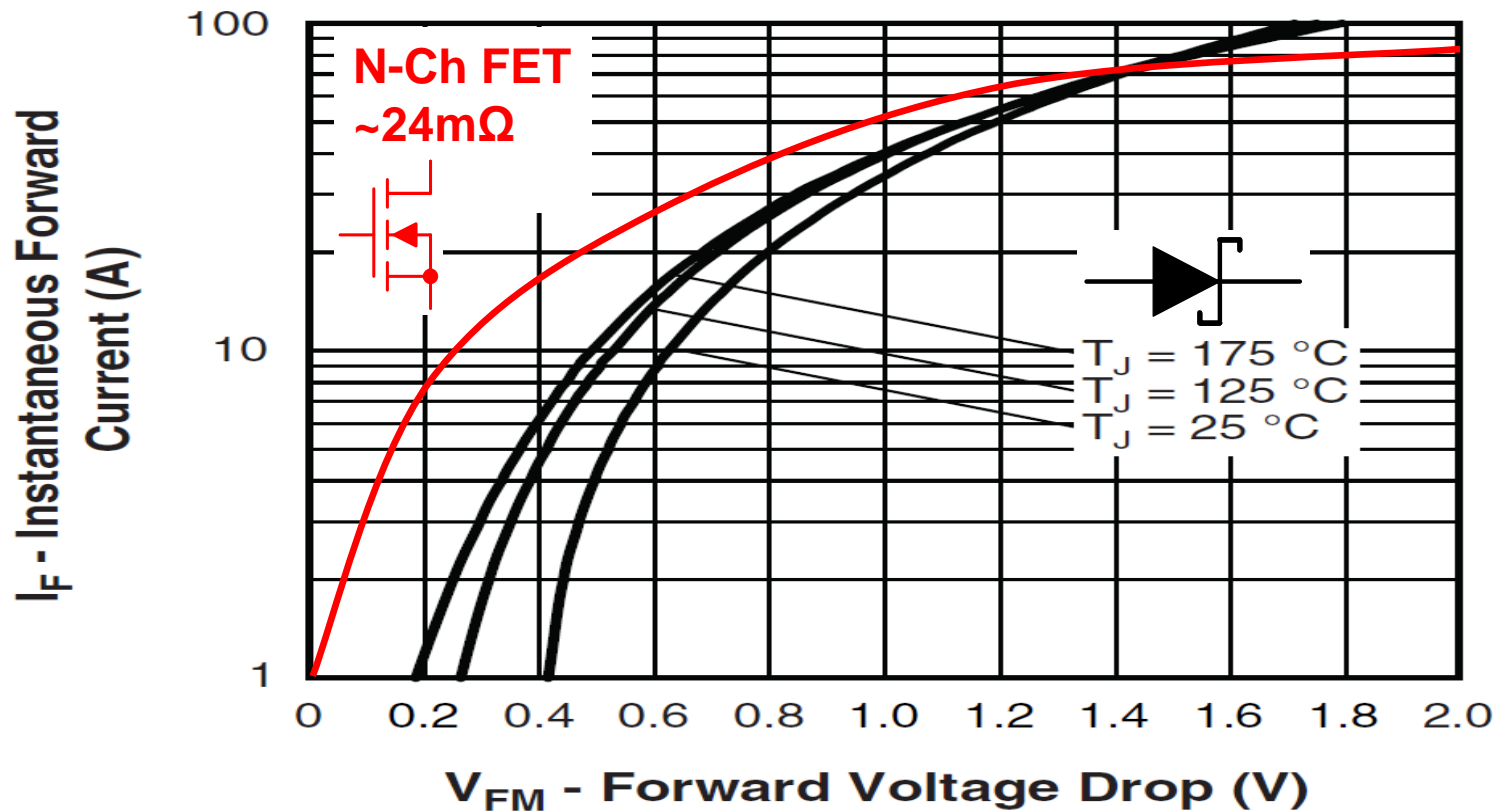


- Synchronous rectification reduces the conduction loss significantly
- Higher efficiency can be expected for low-voltage applications
- BUT: Dominance of switching and gate drive losses under no or low load condition

SR Control in Different Applications (I)

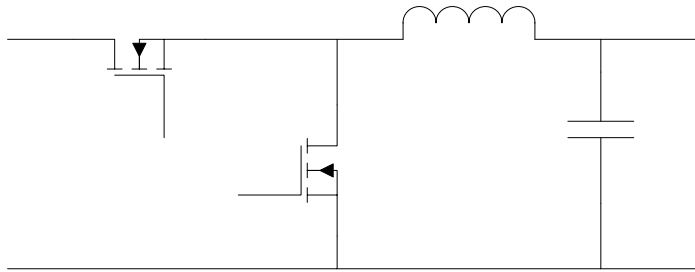

Synchronous Buck

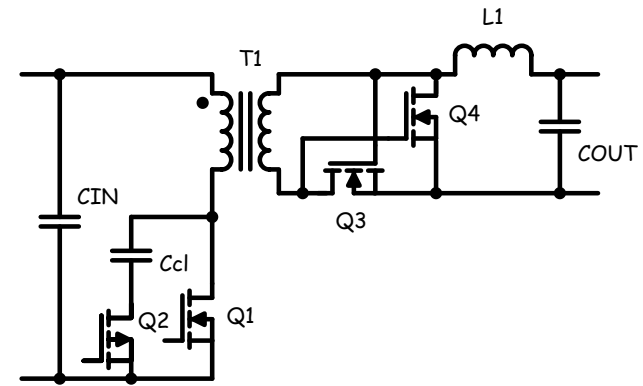- Complementary conduction
- Adaptive turn-on to reduce body-diode loss




Active Clamp Forward Converter

- Self-driven based on transformer voltage


- Most power-conversion topologies can easily implement synchronous rectifier control without dedicated SR-controller IC
- Because of complicated operation modes, timing, and efficiency requirements, Flyback and LLC applications need dedicated SR-controller

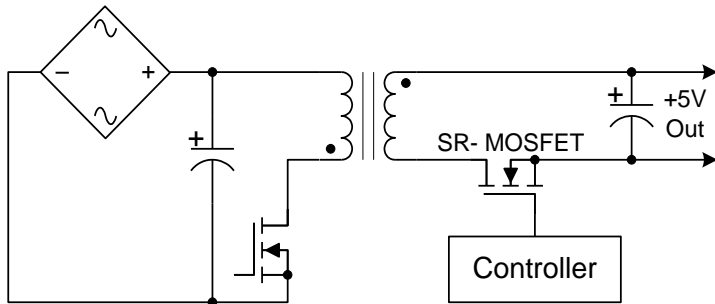SR Control in Different Applications (II)



Flyback Converter

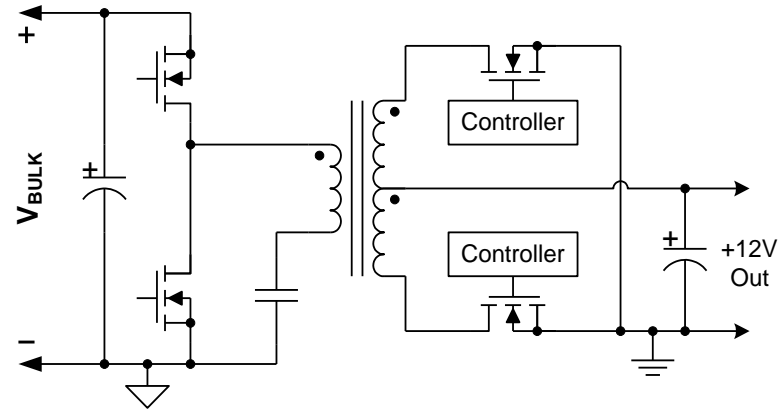- Ground-referenced MOSFET source
- CCM operation may need synchronization signal from primary



LLC Resonant Converter


- Synchronization may be based on primary-side gate-drive signals

- SR may be required to operate in DCM or CCM, depending on topology and load and line conditions
- Intelligent control is necessary to prevent reverse current or cross-conduction in SR-MOSFET

Major Challenges for SR Control


- **Noise associated with turning on and off SR**
 - False trigger might happen due to parasitic ringing
 - Wrong action makes the ringing worse and the false triggering never ends
- **CCM operation**
 - Difficult to detect proper point in time to turn SR OFF
- **Special waveforms**
 - LLC converter has special current waveform that needs special treatment
- **Light-load efficiency**
 - At very light load, the conduction loss is very small, gate-driver loss might be significant

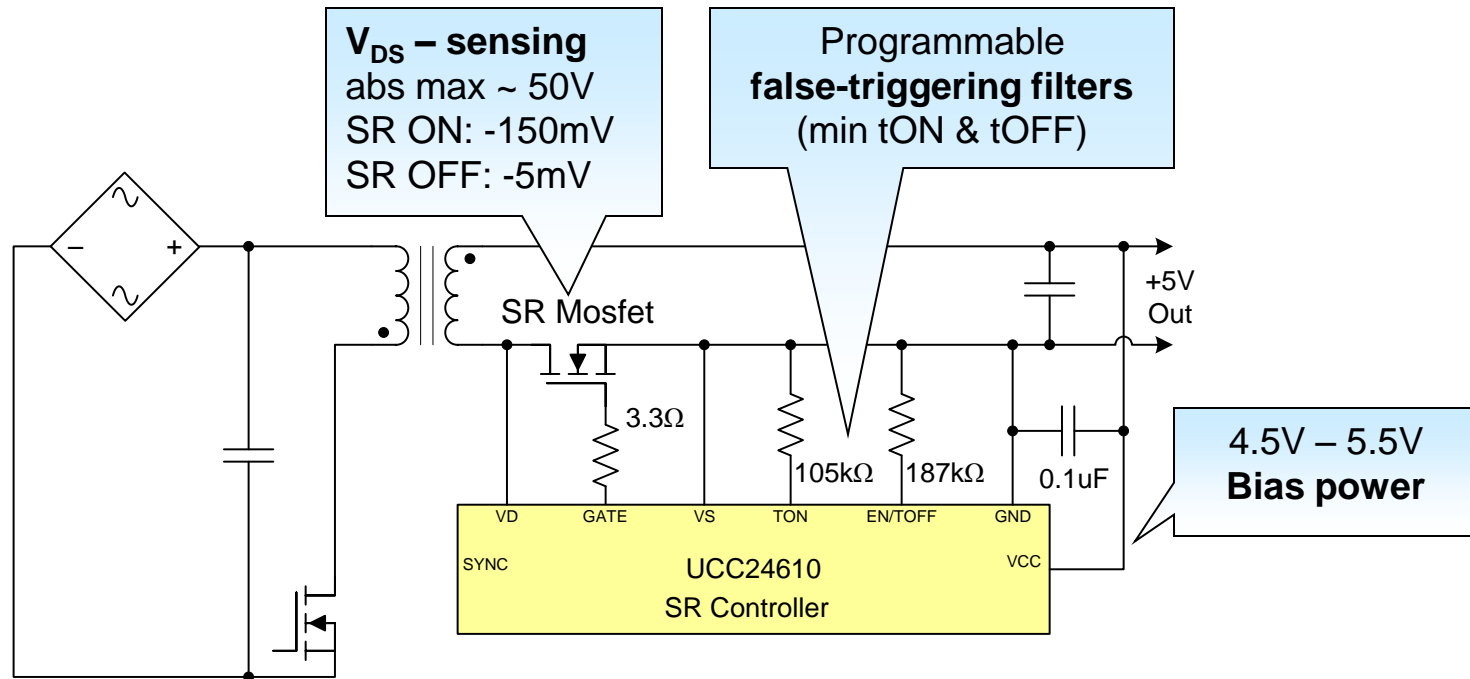UCC24610 - TI Synchronous Rectifier Solution





- Self – synchronizing
- Up to 600kHz operation
- Automatic Light-Load Mode
- 1.6Ω sink, 2.0Ω source gate - drive
- Micro-power Sleep current for 90+ efficiency
- Synchronous wake-up from Sleep and Light-Load modes
- Protection features on programming inputs
- 8-pin SOIC and QFN packages

UCC24610 - CCM Implementation with SYNC

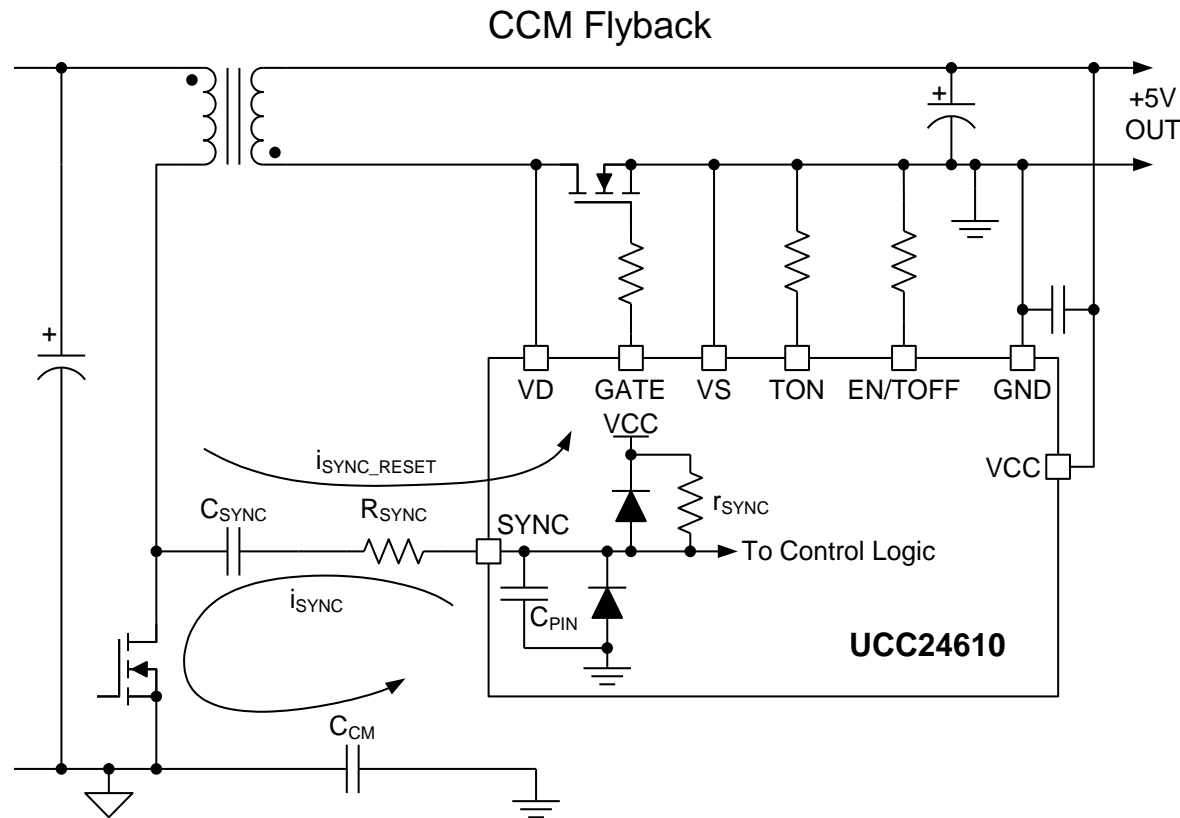

The SYNC function allows the SR to turn off before its current becomes negative, which improves system efficiency and avoids cross-conduction stress

UCC24610 – (12V) LLC Implementation

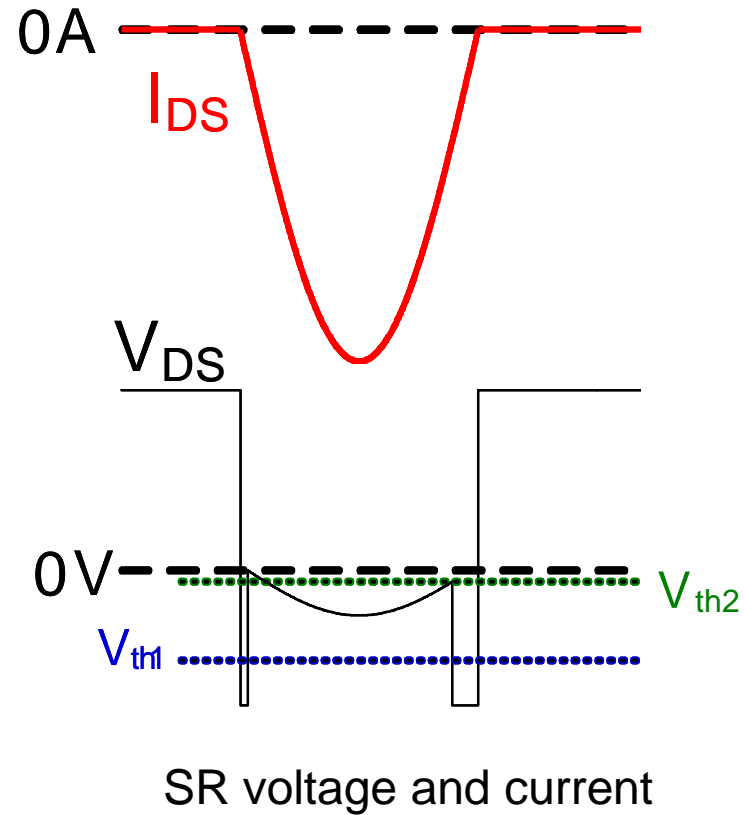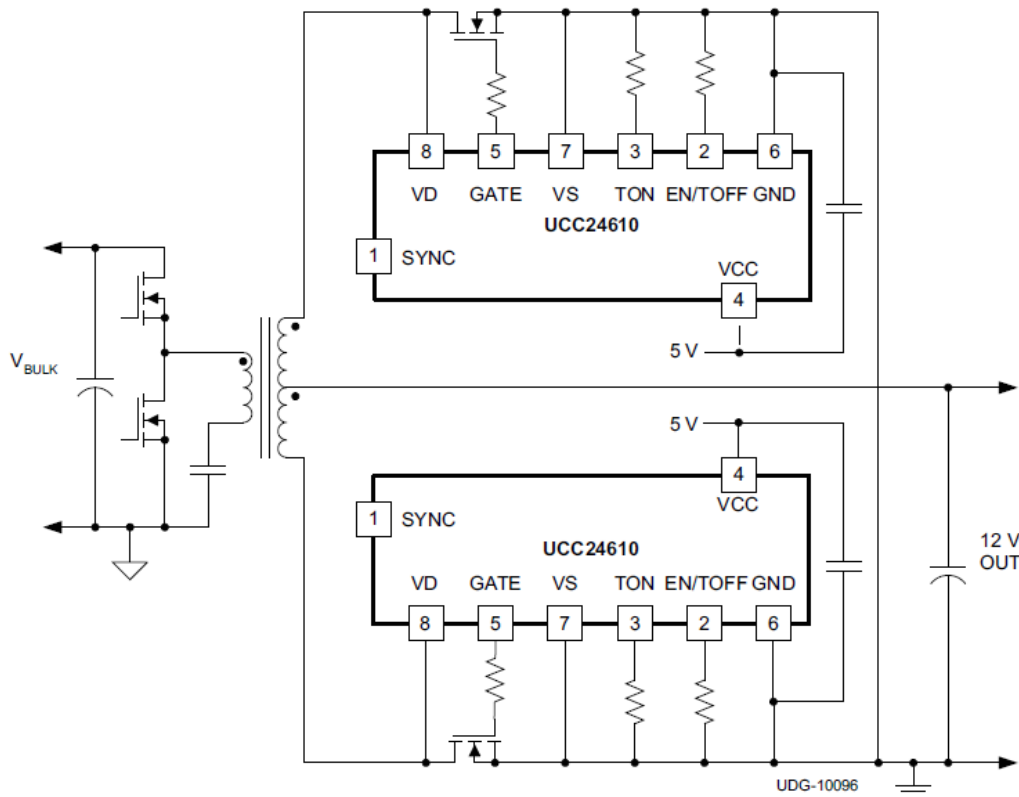


- 5V VCC needs to be generated by LDO or low power buck off the 12V output voltage
- Programmable min tON forces SR to stay ON until current rises above the turn-off threshold.

UCC24610 – 10W Quasi-Resonant Flyback


Efficiency Comparison: ~3 ... 5% Improvement

115 VAC Input

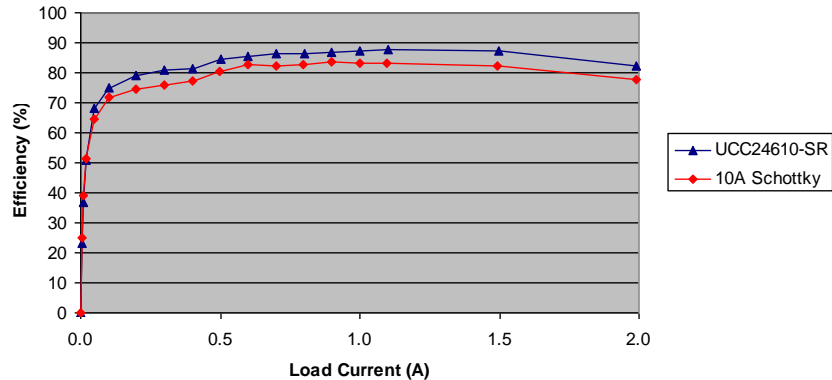10W Flyback Efficiency Comparison, Vin = 115Vac




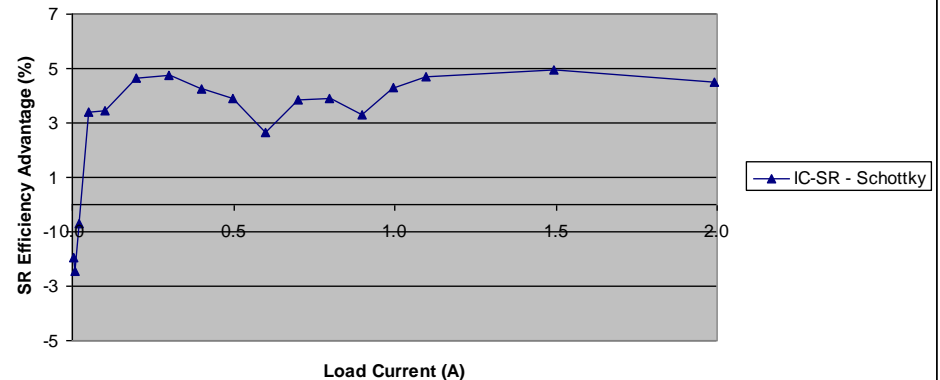10W Flyback Efficiency Difference SR - Schottky, Vin = 115Vac




230 VAC Input

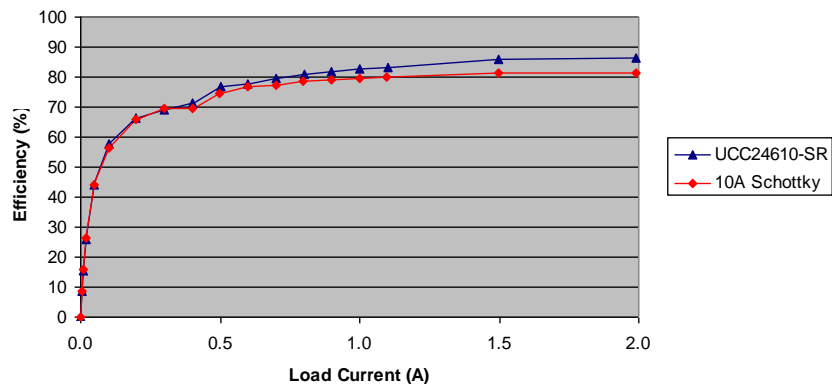10W Flyback Efficiency Comparison, Vin = 230Vac



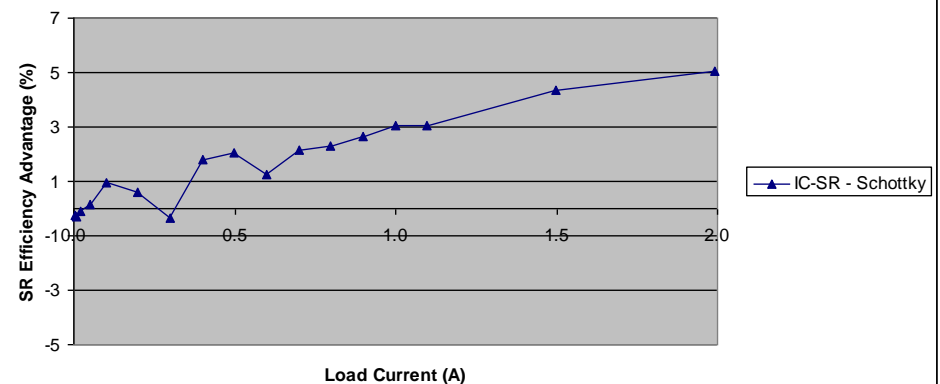
10W Flyback Efficiency Difference SR - Schottky, Vin = 230Vac




Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- **Advanced green mode phase shifted full bridge (UCC28950)**
- Other sources for support
- Summary

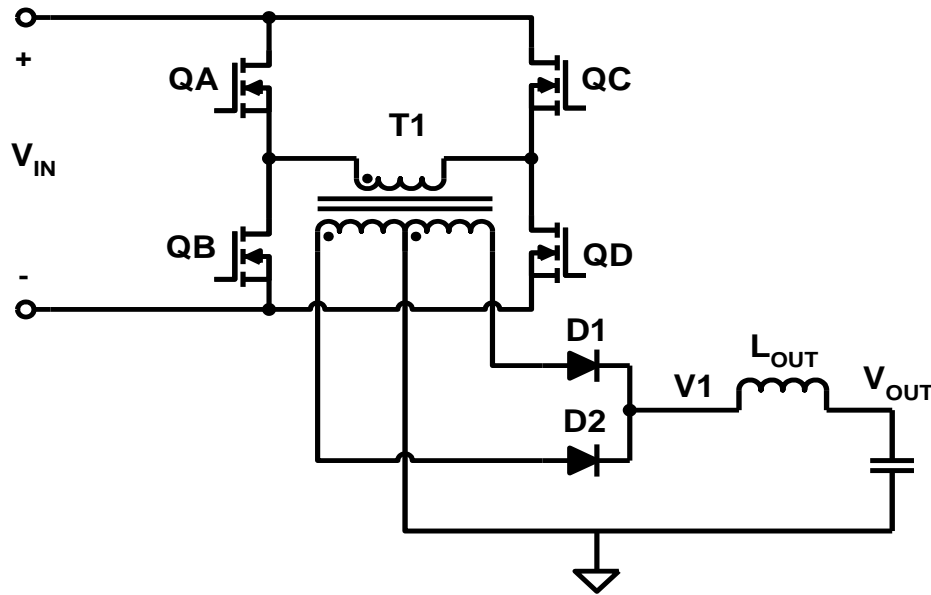
Full bridge topology for high power converters



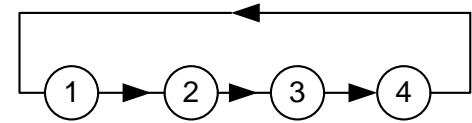
- Control signals for QA ... QD make the difference
 - Conventional full bridge:**
 - duty cycle controlled
 - Phase shifted full bridge:**
 - controlled by phase shift θ b/w QA (QB) and QC (QD)
 - each leg is operating w/ 50% dutycycle
 - QA (QC) and QB (QD) are 180° out of phase




Conventional full bridge

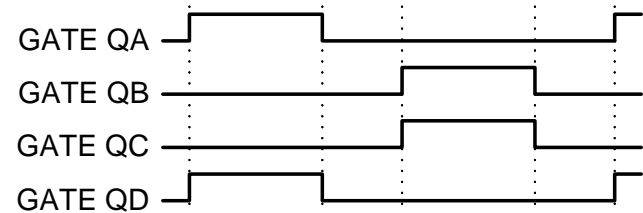



Phase shifted full bridge

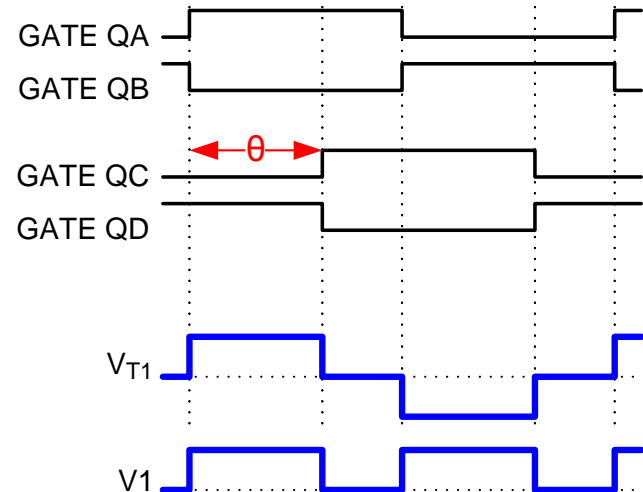

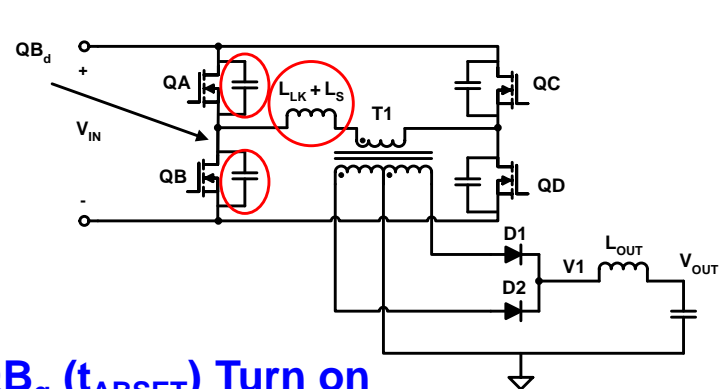
Phase shifted full bridge enables ZVS of switches on primary side



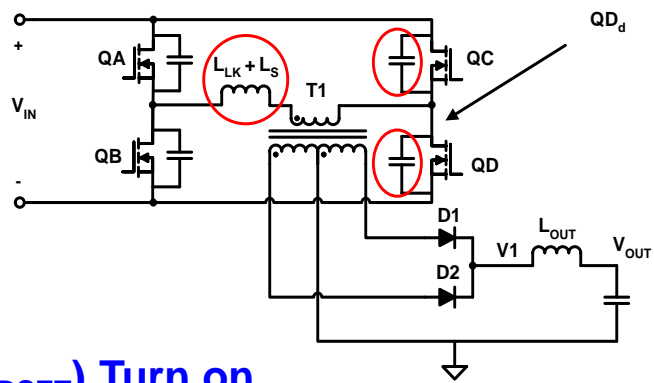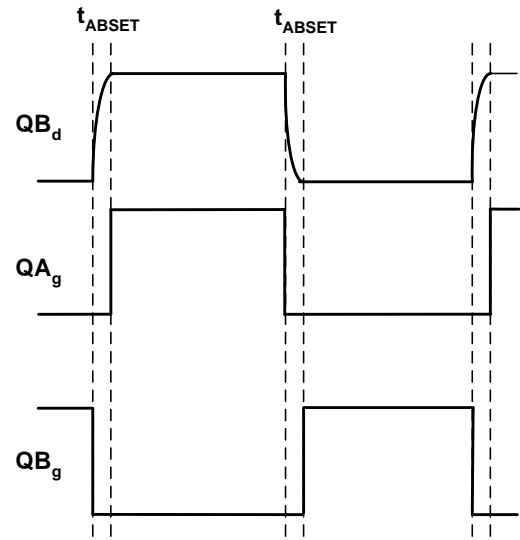- Add Delay QA_g and QB_g (t_{ABSET}) Turn on
- L_{LK} + L_S Tanking with Capacitance at Switch Node (QB_d)
- Allows for ZVS at switch node QB_d



- Add Delay QC_g and QD_g (t_{CDSET}) Turn on
- L_{LK} + L_S Tanking with Capacitance at Switch Node (QD_d)
- Allows for ZVS at switch node QD_d

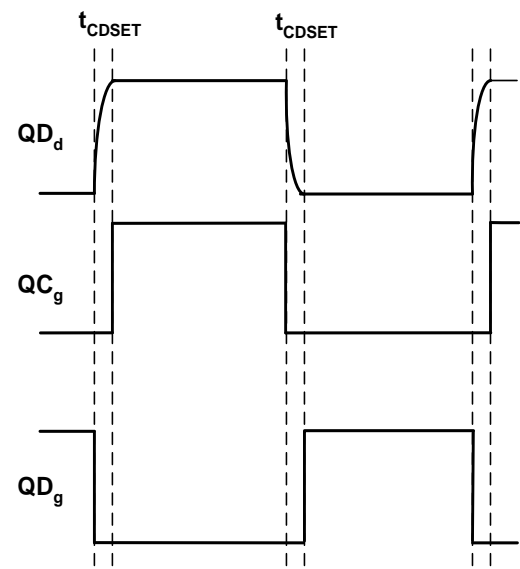


UCC28950 – Successor of the industry standard UCC2895

• More Advanced


- Control outputs for primary FETs **and for synchronous rectifiers (SR)**
- Selectable VM, avg. or peak CM
 - Programmable slope compensation
- Phase shifted SYNC_IN/OUT for easy interleaving
- Optimized SR drive by adaptive delay and SR drive overlap
- Possible location on secondary side improves accuracy and dynamic behavior
- Improved:
 - ZVS by increased adaptive delay range (10:1) for primary FETs
 - VREF accuracy (1.5%)
 - Current Limit (3%)

• More green


- Optimized for 90+ Efficiency (Platinum)
- Light load efficiency management by
 - Burst Mode
 - DCM mode, programmable SR On/Off

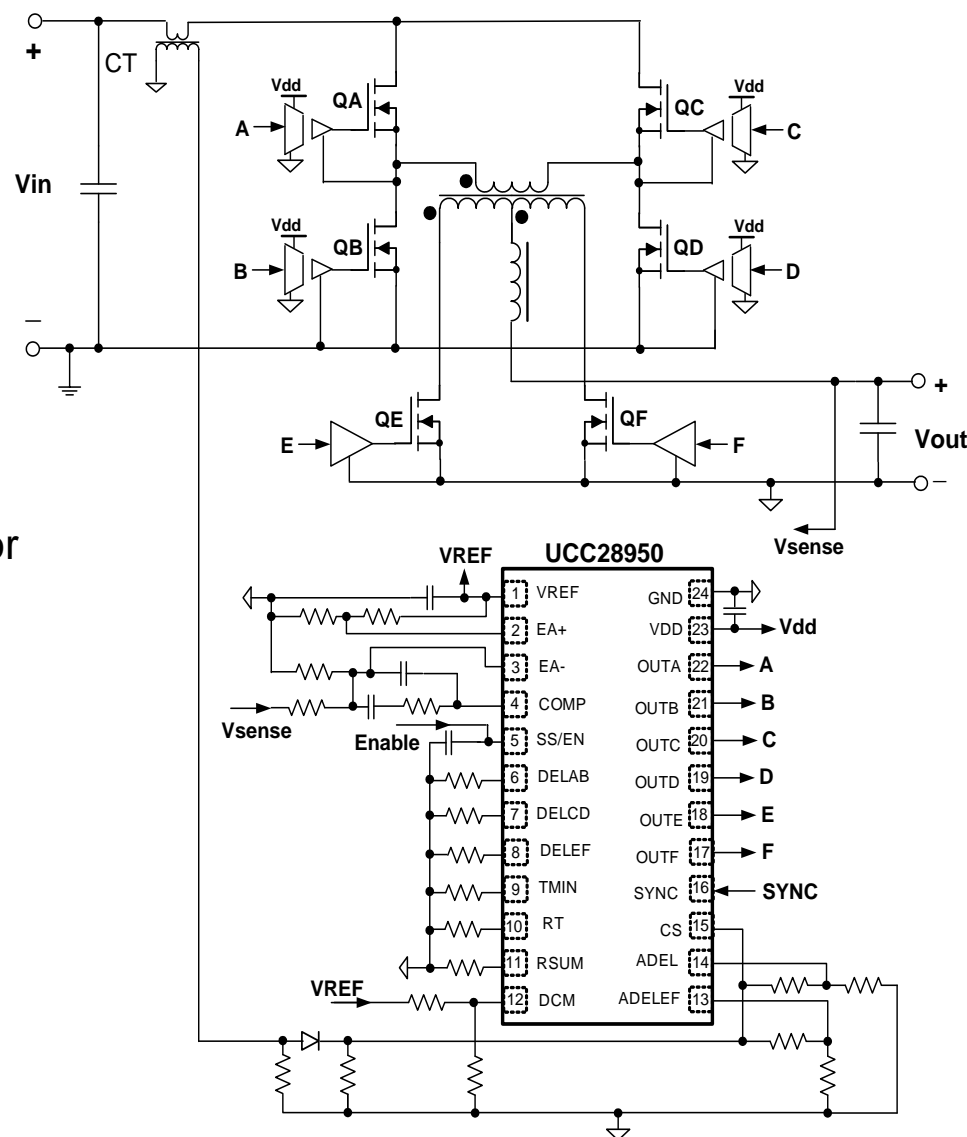

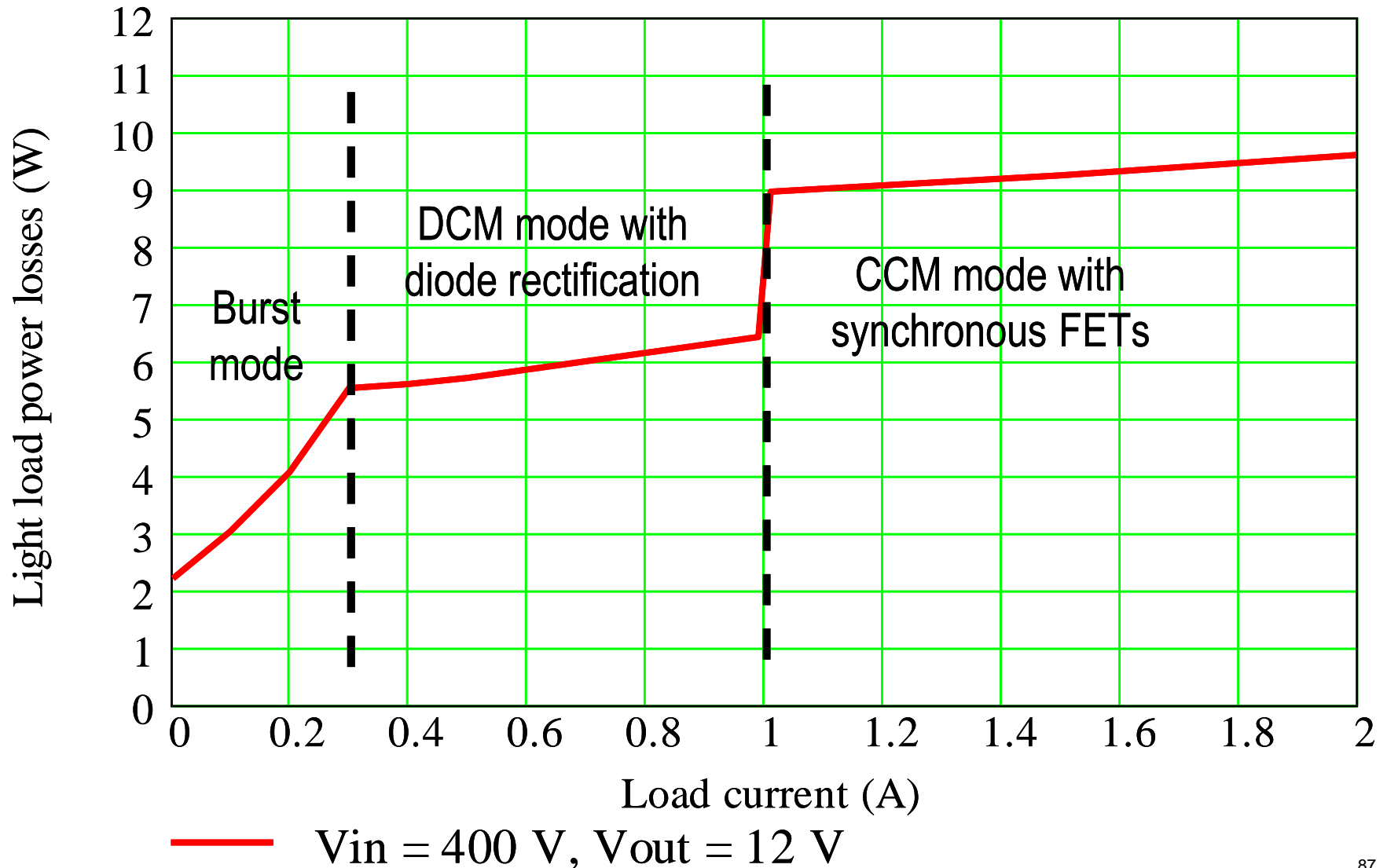UCC28950 - Power Losses Reduction at Light Load





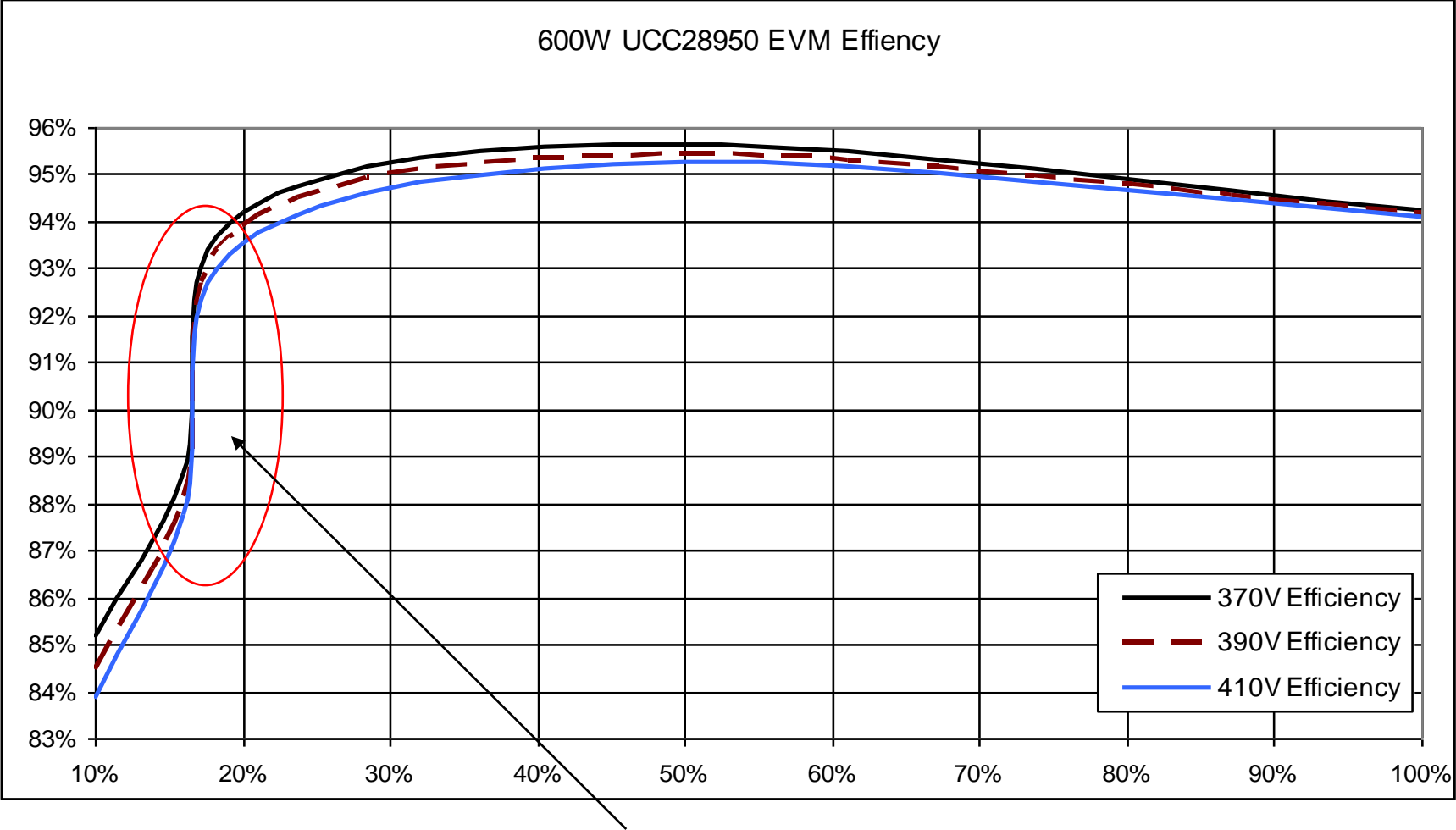UCC28950EVM - 370 ... 410VDC IN / 12V / 600W OUT



Note step in efficiency is due to FETs Turned Off

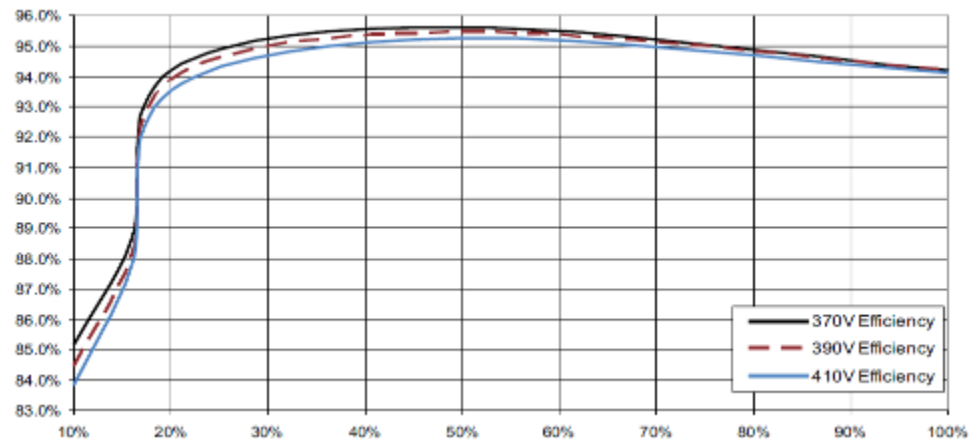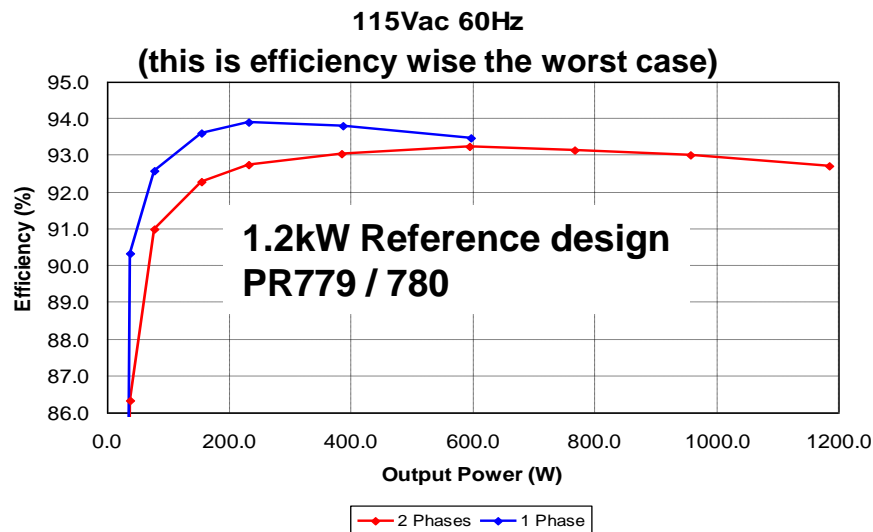UCC28950 – 600W EVM: total efficiency w/ UCC28070 EVM



Energy Star® requirements for server power supplies

Power Supply Type	Rated Output Power	10% Load	20% Load	50% Load	100% Load
Single-Output (AC-DC & DC-DC)	> 500 – 1000 W	75.00%	85.00%	89.00%	85.00%

UCC28070 + UCC28950

PFC (UCC28070)	scaling down to 600W	92.8%	93.8%	93.5%	92.7%
Phase shifted full bridge (UCC28950)	600W	84.5%	94.0%	95.4%	94.1%
Total efficiency	600W	78.4%	88.2%	89.2%	87.2%

UCC28950 + UCC28070 fulfill stringent Energy Star® efficiency requirements for server power supplies

UCC28950 – Design support

- EVM
 - 370 ... 410VDC input / 12V / 600W output
 - User Guide ([SLUU421A](#))
- Application Note
 - Should release to web shortly
- MathCAD Design Tool
 - Should post to the web shortly
- Related App Notes
 - U-136A Phase shifted, zero voltage transition design considerations ([slua107](#))
 - U-138 Zero voltage switching resonant power conversion ([slua159](#))
 - DN-63 The current-doubler rectifier: An alternative rectification technique ([slua121](#))
 - Current doubler rectifier offers ripple current cancellation ([slua323](#))
 - Synchronous rectifiers of a current doubler ([slua287](#))
- Related Seminar Topics
 - Seminar 700 Topic 6: Resonant mode converter topologies -Additional topics ([slup092](#))
 - Seminar 600 Topic 1: Resonant mode converter topologies ([slup085](#))
 - SEM800 – Fixed-frequency, resonant switched PWM with phase shifted control ([slup096](#))
 - SEM900 - Designing a phase shifted Zero Voltage Transition power converter ([slup101](#))
 - SEM900 – Design review: 500 Watt, 40W/in³ phase shifted ZVT power converter ([slup102](#))

Agenda

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- **Other sources for support**
- Summary

Other sources for support

- TI E2E™ Community - <http://e2e.ti.com>
 - Support, videos, blogs, groups
 - Specific support for PFC and PWM controllers under:
[Support / Power Management / Isolated Controllers, Motor Controllers](#)
- On demand online training under:
 - [Training & Events](#) / [Analog, Online Training](#)
- TI Power Supply Design Seminar ([2010 / 2011 series](#))
- All former UNITRODE and TI Power Design Seminars on ti.com under:
 - [Training & Events](#) / [Analog, Archived Seminars](#)



Summary

- General thoughts, standards and solutions
- Quasi-resonant green mode flyback (UCC28600)
- Cascoded green mode flyback (UCC28610)
- Active clamp (UCC289x family)
- Interleaved PFCs (UCC2806x / 28070)
- LLC resonant half bridge (UCC25600)
- Green synchronous rectifier controller (UCC24610)
- Advanced green mode phase shifted full bridge (UCC28950)
- Other sources for support

The shown solutions will help you to fulfill the stringent efficiency requirements now and in the future.

Thank You