



Power Beginner's Hands-on Workshop

David Strasser

Applications
Texas Instruments
d-strasser@ti.com

Heath Gallimore

Software Designer
Texas Instruments
heath@ti.com

Rich DelRossi

Marketing
Texas Instruments
delrossi@ti.com





Power Basics


David Strasser





Agenda

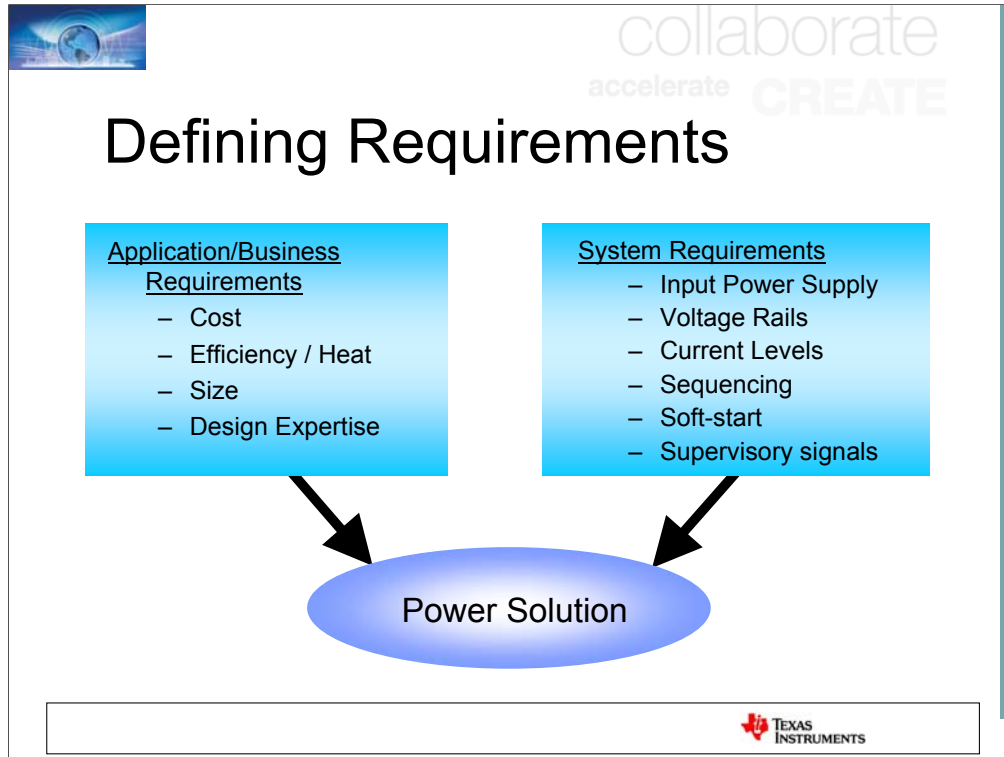- Linear Regulator Basics
- Switching Power Supply Basics
- Component Selection Careabouts
 - Input Caps
 - Output Caps
 - Inductor
 - FETs
 - Phase & Gain Plots



System level/application specific requirements drive the overall dc/dc power supply design

Cost vs. Size vs. Efficiency in a portable vs. PC system application

Cost includes not only component cost but also time involved in designing the supply

Size of the complete solution (i.e., board space allocated to the power supply) is typically a major concern in portable systems

Efficiency

Portable app might have low power mode thus requiring high efficiency over a wide load range to prolong battery life

System application may have higher currents in a closed loop and therefore need higher efficiency and/or additional heat sinking to accommodate power dissipation

Noise sensitive application?

Are there some ICs that would be sensitive to noise?

Digital rails, e.g. "core" and I/O rails, use switcher or linear reg because they are not sensitive to noise

Analog rails, e.g. for powering audio ICs, need low noise linear regulators

May require special layout and/or shielding

Hysteretic vs. constant frequency controller?

Which FPGA?

Different families have different rails and power requirements

Other components with power needs

DDR memory needs power a power supply and a termination voltage

Any boosted voltages necessary



Basic Theory of Linear Regulators



Linear Regulators

- **Features**

- Simple low-cost design
- Easy to Design with
- No switching noise
- High PSRR
- Excellent transient response

- **Limitations**

- Use only to generate a lower voltage
- *Potential* Poor Efficiency: V_{OUT} / V_{IN}
- Power dissipation may be a concern

- **Variations**

- Low Drop Out
- Adjustable Output
- Fixed Output


Best Used When

- V_{IN} to V_{OUT} is small
- Low output noise is important
- Space and cost are important


These reasons are why they are used whenever possible.



Basic Application Circuit

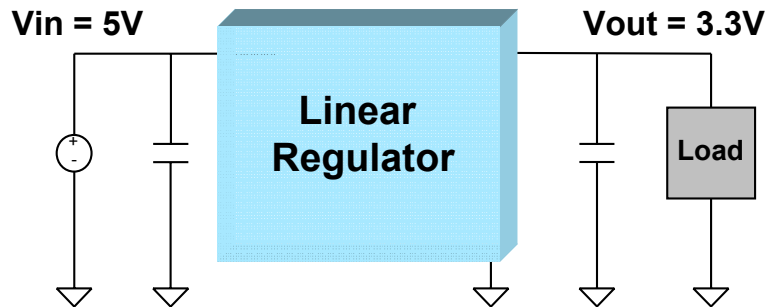

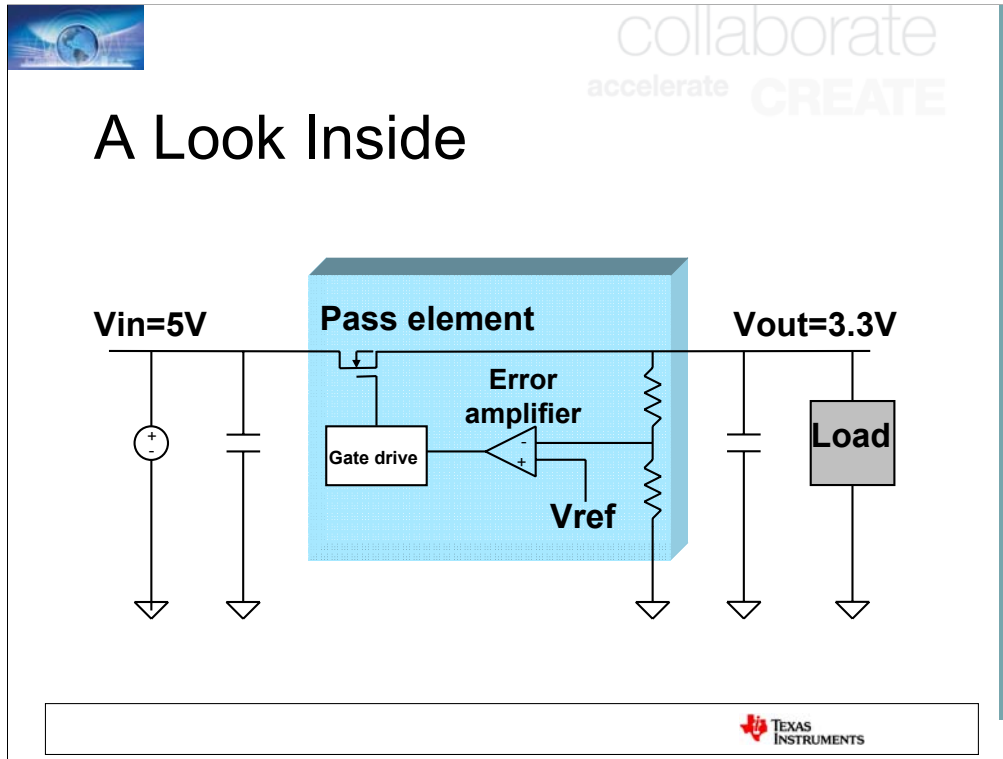This is a typical application. Note that there are only two external capacitors and no inductors. Very easy and simple design.



The pass element reduces the input voltage and regulates it to the output voltage. The pass element operates in the linear region and dissipates power unlike the FETs in a switching power supply that are either on or off. The feedback network and the gate drive circuit close the feedback path to modulate the pass element to provide the regulated output.

Regulator dropout classification:


Standard dropout: $>1V$

Low dropout: $< 1V$


Pass element:

STD regulator darlington or NPN

LDO: PMOS, NMOS or sometimes a PNP

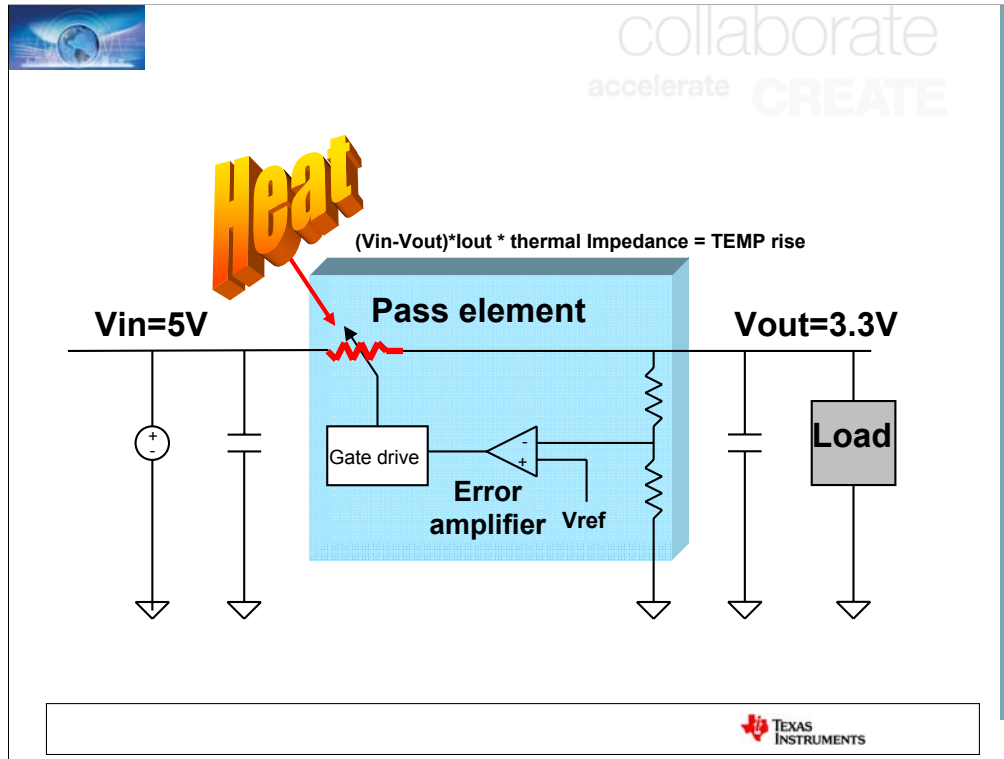

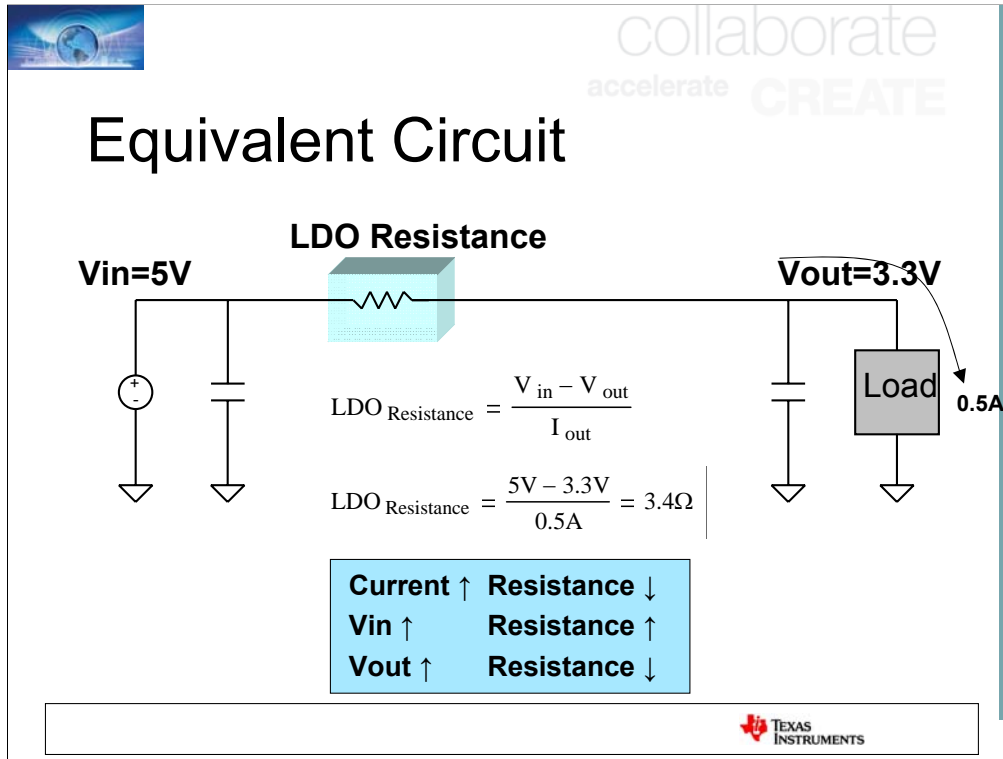Since the pass element is operated in the linear region, it acts as a voltage variable resistor. The feedback network drives the gate of the pass element to make it the correct resistor value to compensate for changes in V_{in} , V_{out} , or I_{out} .



Under steady state conditions, an LDO can be replaced by a discrete resistor. However, no system operates at a single operating point (V_{in} & I_o = constant) so the equivalent resistance must change.



Voltage Dropout

- A linear regulator is in dropout when its output voltage falls out of regulation because the regulator can not adjust its resistance any lower
- Dropout voltage is defined as the differential voltage across the regulator when it enters dropout.


Why Do We Care?

$$(V_{in}-V_{out}) \cdot I_{out} \cdot \text{thermal Impedance} = \text{TEMP rise}$$

↑
we'd like to minimize



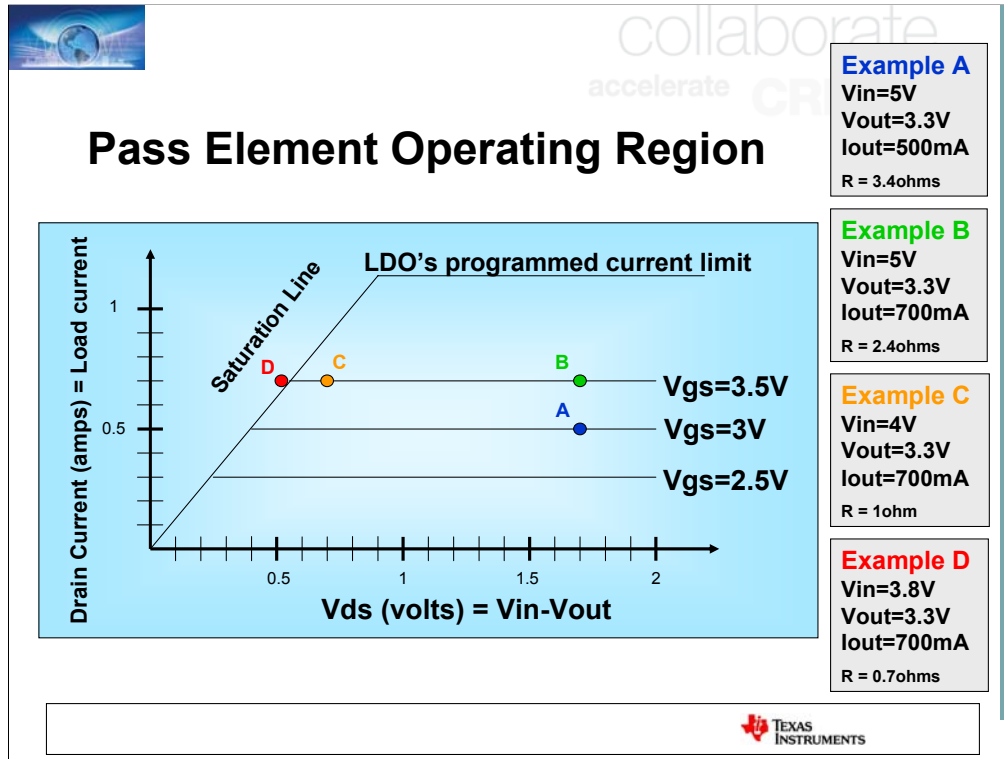The LDO pass element has a minimum resistance when fully enhanced, and when the circuit requires the LDO resistance to be lower than this value, the LDO goes into dropout. In the system, this happens when the output voltage drops out of regulation. The term “dropout voltage” is used to define the differential voltage across the LDO when the LDO goes into dropout.



The graph illustrates the V-I characteristics of a FET pass element. Each point represents the operating point of the FET under the specified conditions. The FET must operate on these curves. The FET's resistance is defined by the line from the origin to the operating point. The FET can NOT operate at point D. Example D puts the LDO into dropout. The actual operating point of example D is on the saturation line.

A. $1.7V / 0.5A = 3.4ohms$ B. $1.7V / 0.7A = 2.4ohms$ C. $0.7V / 0.7A = 1ohm$

Range of operation:

Limited by the saturation region of the pass element or the device's programmed current limit.




collaborate
accelerate
CREATE

Design Application

Design requirement

- Low cost
- $V_{in} = 3.15V$ to $3.45V$
- $V_{out} = 3.0V$
- $I_{out} = 170mA$

Proposed Solution is TPS79330

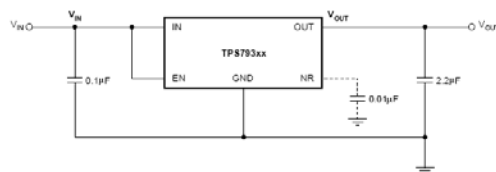

FEATURES

- 200-mA RF Low-Dropout Regulator With Enable
- Available in 1.8-V, 2.5-V, 2.8-V, 2.85-V, 3-V, 3.3-V, 4.75-V, and Adjustable (1.22-V to 5.5-V)
- High PSRR (70 dB at 10 kHz)
- Ultralow-Noise ($32 \mu V_{RMS}$, TPS79328)
- Fast Start-Up Time (50 μs)
- Stable With a 2.2- μF Ceramic Capacitor
- Excellent Load/Line Transient Response
- Very Low Dropout Voltage (112 mV at Full Load, TPS79330)
- 5- and 6-Pin SOT23 (DBV) and NanoStar Wafer Chip Scale (YEQ, YZQ) Packages



Will this LDO meet the customer's requirements. Note that the front page of the datasheet provides typical values only.



Will it Work?

- Parametric Data
 - Ensured
 - One operating point



TPS79301			MIN	TYP	MAX	UNIT
Dropout voltage ⁽²⁾ ($V_{IN} = V_{OUT(nom)} - 0.1V$)	TPS79328	$I_{OUT} = 200\text{ mA}$		120	200	mV
	TPS793285	$I_{OUT} = 200\text{ mA}$		120	200	
	TPS79330	$I_{OUT} = 200\text{ mA}$		112	200	
	TPS79333	$I_{OUT} = 200\text{ mA}$		102	180	
	TPS793475	$I_{OUT} = 200\text{ mA}$		77	125	

200mV is more than the required dropout voltage of 150mV, but this number is specified at 200mA. We only need 170mA.



Will it Work?

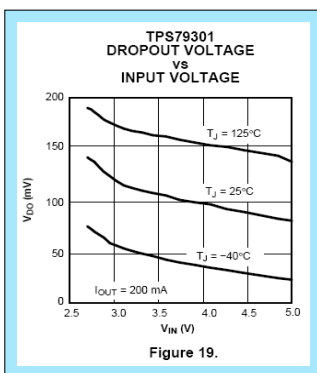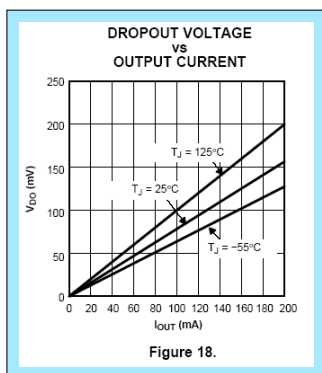- Datasheet Graphs
 - Typical data
 - Not ensured over all conditions
 - Many operating points





Will it Work?

- Parametric table does not assure performance @ 170mA
- Typical graphs do not assure performance over temperature



The answer to whether or not this LDO works for the customer can be found by calculating the LDOs minimum resistance.

collaborate
accelerate CREATE

Calculating Minimum Rdson


TPS79301

			MIN	TYP	MAX	UNIT
Dropout voltage ⁽²⁾ (V _{IN} = V _{OUT(nom)} - 0.1V)	TPS79328	I _{OUT} = 200 mA		120	200	mV
	TPS793285	I _{OUT} = 200 mA		120	200	
	TPS79330	I _{OUT} = 200 mA		112	200	
	TPS79333	I _{OUT} = 200 mA		102	180	
	TPS793475	I _{OUT} = 200 mA		77	125	


$$R_{dson_min} = \frac{\text{Dropout_voltage}}{\text{Test_current}} = \frac{200\text{mV}}{200\text{mA}} = 1\Omega$$

Guaranteed_dropout_voltage = I_{load} × R_{dson} = 170mA × 1Ω = 170mV

- Vin = 3.15V to 3.45V
- Vout = 3.0V
- Iout = 170mA



Does NOT Work



Guaranteed minimum resistance can be calculated from the parametric table. Be sure to use the maximum dropout voltage. 1st calculate the resistance at the test current. Then use this number to calculate the guaranteed dropout voltage at the customer's specific operating current. Note that the LDO has 170mV of dropout, which is higher than the 150mV requirement. This LDO does not work for the customer application, even though the front page of the datasheet implied that it would.



Effects of Dropout

(or: what happens if I operate at the dropout voltage?)

- **Reduced PSRR** (power supply rejection ratio)
 - LDO pass element operates in the saturation region
 - Error amp is saturated
 - Circuit can not respond to changes in input voltage
- **Reduced Output Noise Rejection**




Operating in dropout reduces the PSRR of the LDO since the error amp is saturated and can't respond to voltage changes on the input. Most LDO PSRR data is taken with $V_{in} = V_{out} + 1V$.

When the LDO is in dropout the attenuation at V_{out} can be modeled as a single pole response due to the R_{DSon} of the pass element and the output capacitance.




Thermal Considerations

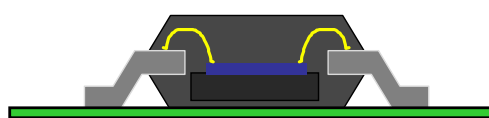
- Must consider package thermal characteristics
 - Different packages have different capabilities to handle heat dissipation



Junction Temperature

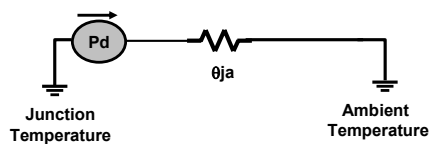

Package Power Dissipation

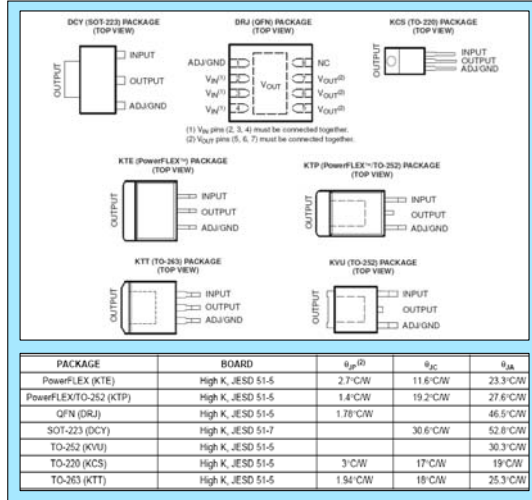

Max Power Dissipation

- T_j : Max Junction Temp
- T_a : Max Ambient Temp

$$P_d = (T_j - T_a) / \theta_{JA}$$

Lowest θ_{JA} can dissipate the most heat.

Trade-offs between package size and thermal properties



collaborate
accelerate
CREATE

Linear Regulators : What We Learned

- LDO regulates output by changing it's equivalent resistance
- Minimum resistance sets dropout voltage
- LDO datasheets can't specify all operating conditions.
- User can interpolate the dropout specs to any specific operating condition
- Operating in dropout affects PSRR and Noise performance
- Proper design involves thermal calculations and proper package selection





Switching Regulators

- **Features**

- Boost, Buck or Inverting Types
- Wide range of V_{IN} and I_{OUT}
- Very Efficient
- Good Transient Response
- Limited Power Dissipation

- **Limitations**

- Larger solution size
- More expensive to implement
- Noise

- **Variations**

- Buck
- Boost
- Buck-Boost
- SEPIC
- Flyback

Best Used When


- Need best efficiency for battery life
- Higher currents are needed
- V_{IN} and V_{OUT} are wide

These reasons are why they are used whenever possible.



collaborate
accelerate
CREATE

Topologies – Buck Regulator

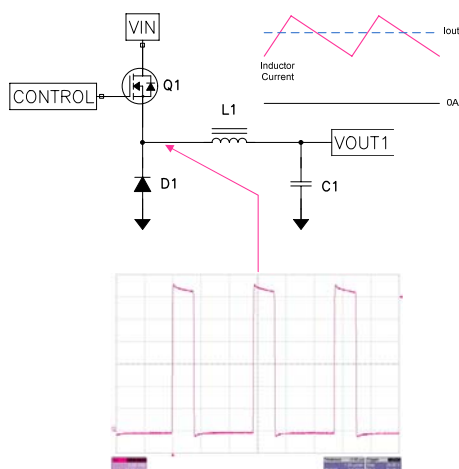

Used When?

- Non-isolated
- $V_{in} > V_o$

Variations


- Module/Switch/Discrete
- Continuous/Discontinuous Current
- N/P Channel FET
- Synchronous/not
- Multiphase





collaborate
accelerate CREATE

Topologies – Sync vs Non-sync Buck

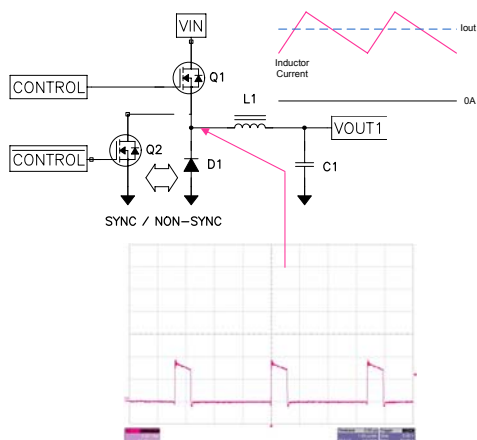

Used When?

- Sync for Highest Efficiency
- Non-sync for lowest cost

Sync ICs

- TPS40190 (Single)
- TPS51020 (Dual)
- TPS54310 (SWIFT)

Non-Sync ICs

- TPS40200 (Ext. P-FET)
- TPS5430 (SWIFT)





collaborate
accelerate **CREATE**

Design Considerations






Inductor Considerations

- Benefits of low L values
 - Lower DCR
 - Higher I_{sat}
 - Higher di/dt
 - Transient response improves
 - Less output capacitance required for given transient performance
- Benefits of high L values
 - Lower ripple current
 - Lower AC losses (skin effect, hysteresis)
 - Lower RMS current in MOSFETs
 - Lower RMS capacitor current (mainly output)
 - Continuous inductor current over broader load range
 - Less C required for equivalent output ripple



collaborate
accelerate **CREATE**

Inductor Types

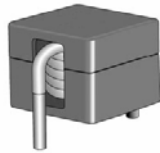



Power MOSFET Selection

- Compare different MOSFETs in each position
- In general higher F and higher input voltage require lower Q_g to cut switching losses in switch MOSFET
- For rectifier MOSFET, low $R_{DS(on)}$ is most important, but don't ignore gate power



No known method for calculating a “best” Q_g & $R_{DS(on)}$ in a given situation.

Limited by the data the MOSFET manufacturers provide- inconsistent format, etc.

Mention spreadsheet that allows examination of predicted system losses with changing MOSFET parameters.


For SW MOSFET, lower Q_g does give faster switching time, but this contributes to more parasitic turn-on of the rectifier MOSFET. There is a happy medium somewhere.



Buck Regulator – P Ch vs. N Ch FET


- **P Channel**

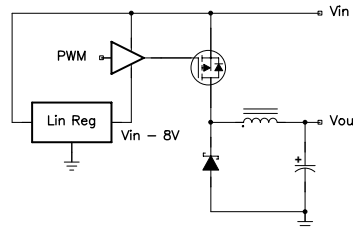- Lower Cost Controller
- Higher V_{in} operation
- Fewer pins required



- **N Channel**

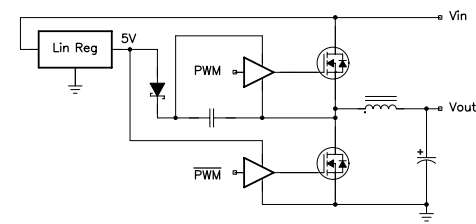- Greater Selection
- Lower cost than P-Ch (same $R_{ds(on)}$)
- Higher Efficiency
- Typically implemented as synchronous buck



P-CH - Fewer pins required (SW node deleted)



Power Capacitors Selection

- Power Dissipation
 - ESR
- Ripple Performance
 - ESR
- Transient Performance
 - ESL
 - Capacitance
 - ESR
- Cost
- Size
- Reliability



Relative Capacitor Characteristics

	ESR	Cost	Current Rating	Reliability
Std Al Electrolytic	high	low	low	low
OSCON	low	medium	high	High
Solid Polymer (SP)	low	very high	medium	high
POSCAP	low	high	medium	high
Tantalum	medium	medium	medium	medium
Ceramic	very low	very high	high	high



Choosing Capacitor Size


- Input Filter
 - Sized for AC current handling
- Output Filter
 - Transient events on load
 - Output voltage ripple



Output Capacitor Selection Criteria

- Transient performance
 - Bulk capacitance
 - ESR
 - ESL
- Output Ripple
 - ESR
 - Bulk value
 - ESL has minor effect

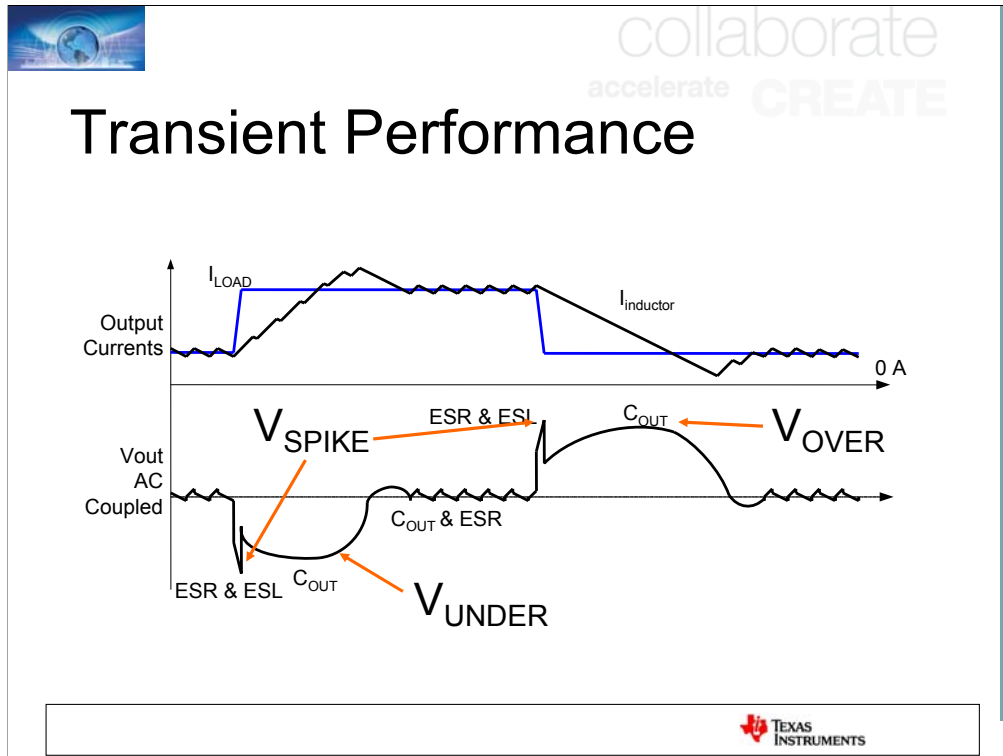Just a listing of what parameters are important in selecting the output cap




An idealized picture showing contributions of output capacitor characteristics and where they occur in a load transient event.

Note the di/dt of the load causing the ESL spiking.

Note fixed inductor current slopes causing the bulk of the transient event disturbance.

Recovery from load step increase depends on energy stored in output capacitor and voltage loop response time

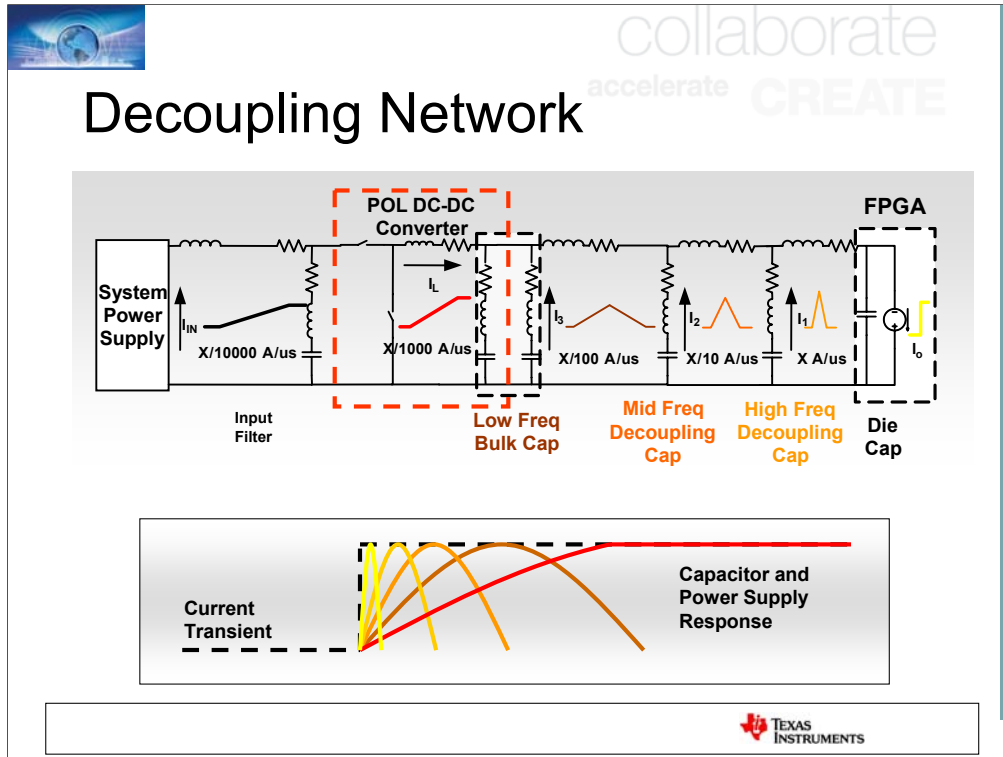Recovery from load step decrease depends on energy stored in output inductor, output capacitor size, and voltage loop response time.



All POL dc/dc converters have finite response time, whether the converter has a traditional feedback loop with a bandwidth set by the loop's crossover frequency or a hysteretic converter with fixed on or off time. Therefore, additional capacitance is almost always required on a power rail to assist the converter in handling the transient step. As shown in the figure, a decoupling network is used to handle the different frequency components of the transient so that the POL dc/dc converter, and ultimately its input power supply, only see the small low frequency component of the load step.



Small pf to 1 uF range capacitors handle the high frequency component of the load step. Capacitors from 1 uF to 22 uF handle the mid-frequency component of the load step. Low ESR bulk capacitors from 47 uF to 1000 uF handle the low frequency portion of the transient. A common method for optimizing the decoupling network (i.e., minimizing the amount of capacitance) is the target impedance method, as explained more fully in SLUA110. This method requires that worst case load transient step of the device being powered (e.g., from 200 mA to 2.2 A in 0.5 us or 4A/us for 10us) be known as well as some idea of the transient response capabilities of the POL converter. If the POL converter is not close to the load and the board layout requires that the power rail use small traces and/or vias to get to the load, then approximations of the board resistance and inductance may be necessary for the model as illustrated in the figure.

For most FPGA and DSP applications, the worst case load transient is rarely known and it is simpler to use rules of thumb to design the decoupling network. For example, it is not uncommon to allocate a certain amount or percentage of each type of capacitor (high-, mid-, and low-frequency) per the number of power pins used in total or per section of the digital IC. While effective, this method tends to overdesign the decoupling network, resulting in underutilization of the dc/dc converter's transient response capabilities as well as recommending more capacitors than absolutely necessary be placed around the IC, taking up board space.

In this example, the 1.5V supply for the Virtex-II device supplies VCCO for banks 1 and 6, and VCCINT. There are 44 VCCINT pins on this device. Banks 1 and 6 were previously calculated to use two pins each. Adding the 44 VCCINT pins and the four VCCO pins for Banks 1 and 6 equals 48 pins. Therefore, there should be 48 capacitors total on the 1.5V supply.



Compensation Networks

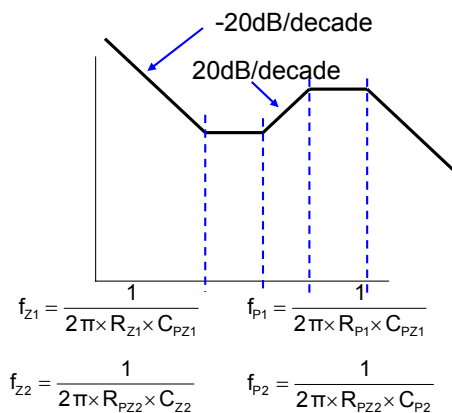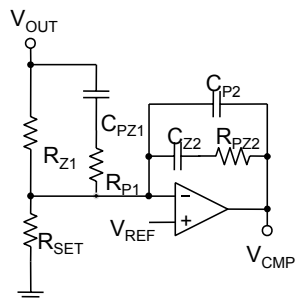


Type 3

- Three poles one at origin, one set by R_{PZ2} & C_{P2} and one by R_{P1} & C_{PZ1}
- Two zeros one set by C_{Z2} & R_{PZ2} and one by R_{Z1} & C_{PZ1}



Power Supply Stability Considerations

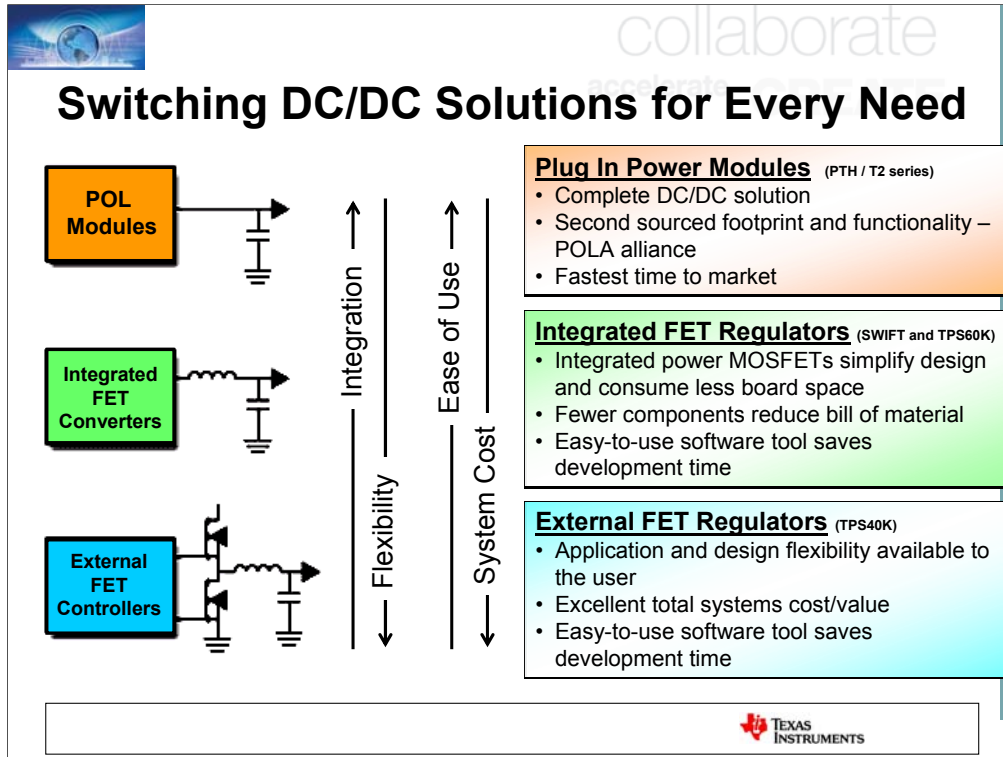- Phase/gain margin critical for stability of closed-loop feedback systems.
- Computer simulation helpful but inadequate
 - Device models unavailability or inaccurate
 - Parasitic/stray elements play a role
 - Mechanical decisions affect models
 - “Proof” is in final measurements



Plug In Power Modules - PTH series

Modules – these are a complete DC/DC solution. Minimal design effort is needed, and customer can get into production fastest. Typically, these are the most expensive of the single output converters. [Complete DC/DC solution](#)

[Second sourced footprint and functionality – POLA alliance](#)

[Fastest time to market](#)

Integrated FETs (SWIFT)

Integrated power MOSFETs simplify design and consume less board space

Fewer components reduce bill of material

[Easy-to-use software tool saves development time](#)

2) SWIFT and TPS6xxx DC/DC Converters –The emphasis of these products has been to integrate as much of the power solution as possible into a single IC – including the power FETs. As few as 6 external components are all that is needed to develop a solution – newer designs enable up to 14A of output current from a 3.3V supply. These parts are 'simple discrete' solutions for the customer

External FETs (DC/DC Controllers)

[Application and design flexibility available to the user](#)

[Excellent total systems cost/value](#)

[Easy-to-use software tool saves development time](#)

3) In many applications, using a standalone controller, TPS40k, TPS5xxx without the on board FETs offers customers the most flexibility – and the ability to provide higher output currents. The customer has higher levels of design flexibility, and the ability to optimize performance and cost. The trade-off is that typically, this solution will require more design work and board space. So, if system cost includes not only component cost but board space and design time, then IFET converters for low to medium current applications are lower cost than controllers with external FETs.

The modules and the IFET products are available in various current steps: PTH from 2A to 30A, SWIFT from 1.5A to 14A.



Switching Regulators : What We Learned

- **Switching regulators offer flexibility whether you want to increase, decrease, or invert your board voltages**
- **Choosing the correct components is important to meet your design goals**
- **Simulation tools are a good way to make initial design decisions, but the ultimate test is in putting real products on circuit boards**



Questions?



SwitcherPro™

Heath Gallimore





SwitcherPro™

- SwitcherPro is a complete on-line design tool for non-isolated switching DC/DC converter designs
- Access SwitcherPro from the ti.com website
 - Keyword search for “SwitcherPro”
 - Select “Power Management” (upper left)
 - “Tools and Software”
 - SwitcherPro is one of the listed items
- Log in using my.TI.com user account



SwitcherPro Startup Screen

The **Power Design Wizard** can be used to start a design, or it can be closed and the design can be created using the Create Design file folder at the left. The **Design Wizard** and the **Create Design** button both access the same design utilities. We will use the **Design Wizard** to create our custom design.

Select: **Create a new custom design**

Start by entering specifications


Advanced Inputs button



Switcher Pro™ Example

- DC Design Parameters
 - $V_{in} = 12.0V \pm 10\%$
 - $V_{out} = 2.5V \pm 2\%$
 - $I_{out} = 2.0A$ max. $0.2A$ min
 - Optimize for size
 - SMD, shielded inductor, ceramic output caps
- AC Design Parameters
 - V_{out} ripple voltage: $10mV$ p-p
 - V_{in} ripple voltage: $100 mV$ p-p

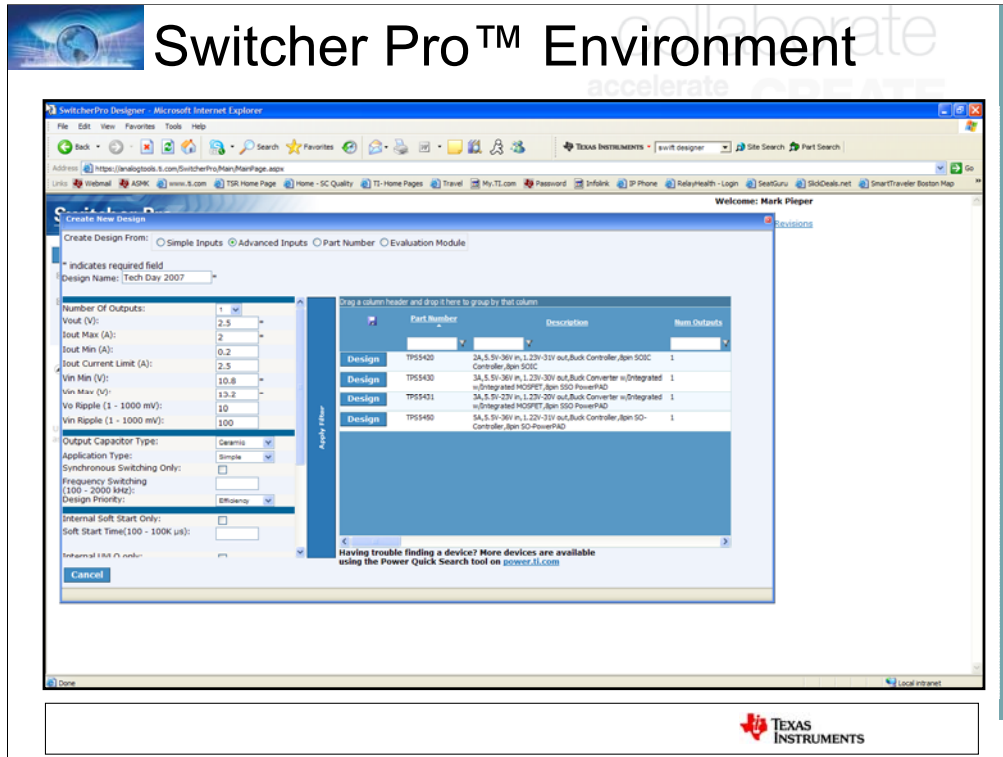These are the design parameters for our example. This data is entered into the **Advanced Inputs** tab in the **Create New Design** window. After entering this data and Enter on the keyboard, the selection of parts narrows to those that are capable of fulfilling the requirements.




Enter the design requirements into the list at left.

Select **Apply Filter**

Applicable components are displayed.

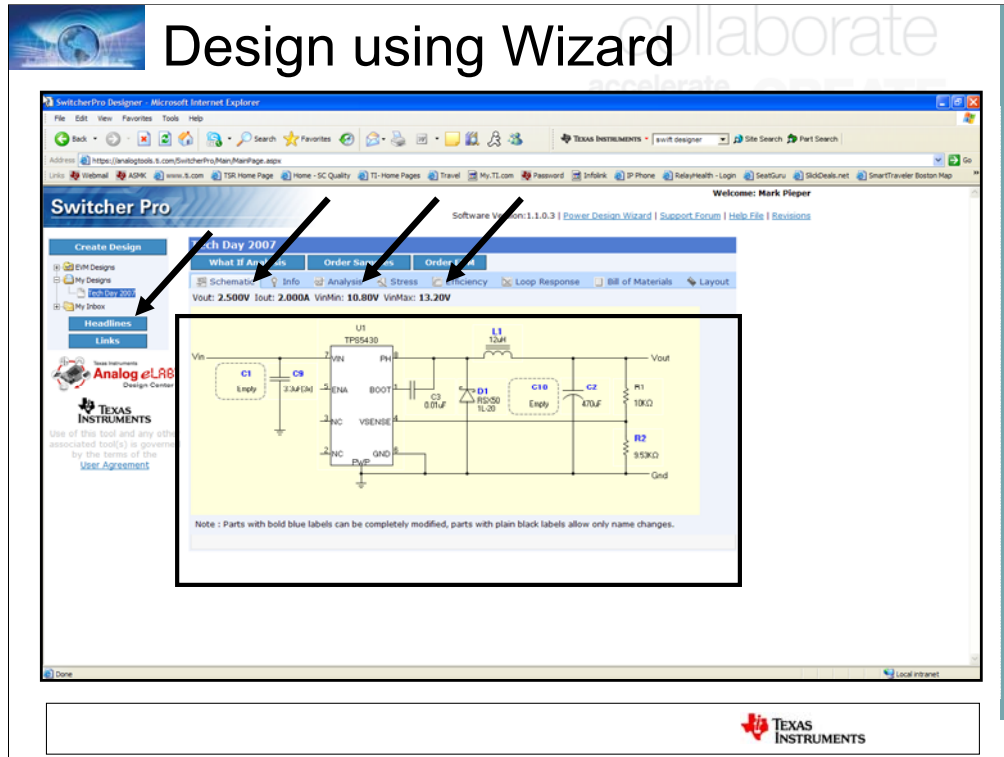Since we are interested in a TPS5430 SWIFT design, select **Design** next to the **TPS5430**.



The design is displayed <click> and shows up as an entry under the **My Designs** folder <click>.

The main window has three buttons:

What if Analysis: <click> Allows examining the impact of various component changes to the performance of the design (more on this later).

Order Samples: <click> Is a link to the product page where samples can be ordered.

Order EVM: <click> Is a link to the Tools and Software section of the product page where evaluation modules can be ordered.

Schematic components with blue Ref Des can be selected and changed to a different component. Also note that when the mouse hovers over a component, information about that component is displayed. Balloons that have components that are labeled “empty” are optional components that you may choose to add. Examples are bulk input capacitors, additional output capacitors, and sometimes snubber networks.

Select D1 and evaluate alternatives. Change D1 to a MBR340T3

Changing a Component

SwitcherPro Designer - Microsoft Internet Explorer

Address: https://analogtools.ti.com/SwitcherPro/ManPage.aspx

Instructions: This form allows you to view and modify a Diode. The currently selected diode is displayed on the left side. The table on the right contains all the available diodes to choose from. Change diodes by clicking the "Select" button on the row of the desired diode. To narrow down the list of parts use the filter text boxes at the top of each column to filter parts by that column. To use a filter enter text into the text box and select the desired filter type from the filter icon. To clear a filter select "No Filter" from the filter icon. Tip: to use the between filter enter two values in the text box separated by a space. If multiple pages of parts are available, then you can use the paging control at the bottom of the table to change pages.

Current Diode

Name: D1

Part Number: RSK501L-20

Manufacturer: Rohm Electronics

Quantity: 1

Locked: ☐

Breakdown Voltage: 20V

Forward Voltage: 380mV

Forward Current: 5A

Leakage Current: 500A

Package Name: SMD6

Package Area: 13mm²

Close Apply

Available Diodes

Drop a column header and drag it here to group by that column


Part Number	Manufacturer Name	Type	Filter Icon	Volts	Forward Current	Reverse Current
Select	MBR120L-071	On-Sem	Schottky	1	0.350	0.400
Select	83408	Diodex, Inc.	Schottky	1	0.310	0.400
Select	8320	Diodex, Inc.	Schottky	1	0.290	0.500
Select	8310A	Diodex, Inc.	Schottky	1	0.300	0.510
Select	MBRS340T3	Motorola	Schottky	1	0.244	0.525
Select	MBR1M120C	On-Sem	Schottky	1	0.400	0.530
Select	C29H5-40	Central Sem	Schottky	1	0.300	0.550
Select	88610-40C	Diodex, Inc.	Schottky	2	0.290	0.550
Select	58L945	Diodex, Inc.	Schottky	1	0.300	0.550
Select	501034W	Diodex, Inc.	Schottky	1	0.190	0.600
Select	58L945	Diodex, Inc.	Schottky	1	0.210	0.600
Select	84T54	Diodex, Inc.	Schottky	1	0.220	0.630
Select	8350C	Diodex, Inc.	Schottky	1	0.340	0.700
Select	8160	Diodex, Inc.	Schottky	1	0.600	0.700
Select	MURS120T3	On-Sem	Ultra Fast	1	0.570	0.810

Page 1 of 1




Changing D1 to MBR340T3:


Select the button next to the **MBRS340** <click>




Design using Wizard

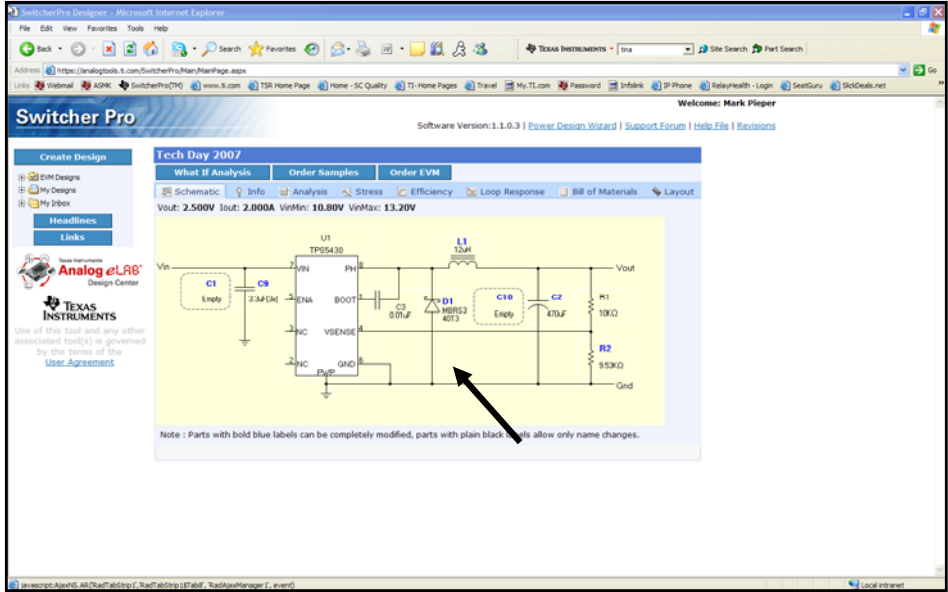

Note : Parts with bold blue labels can be completely modified, parts with plain black labels allow only name changes.



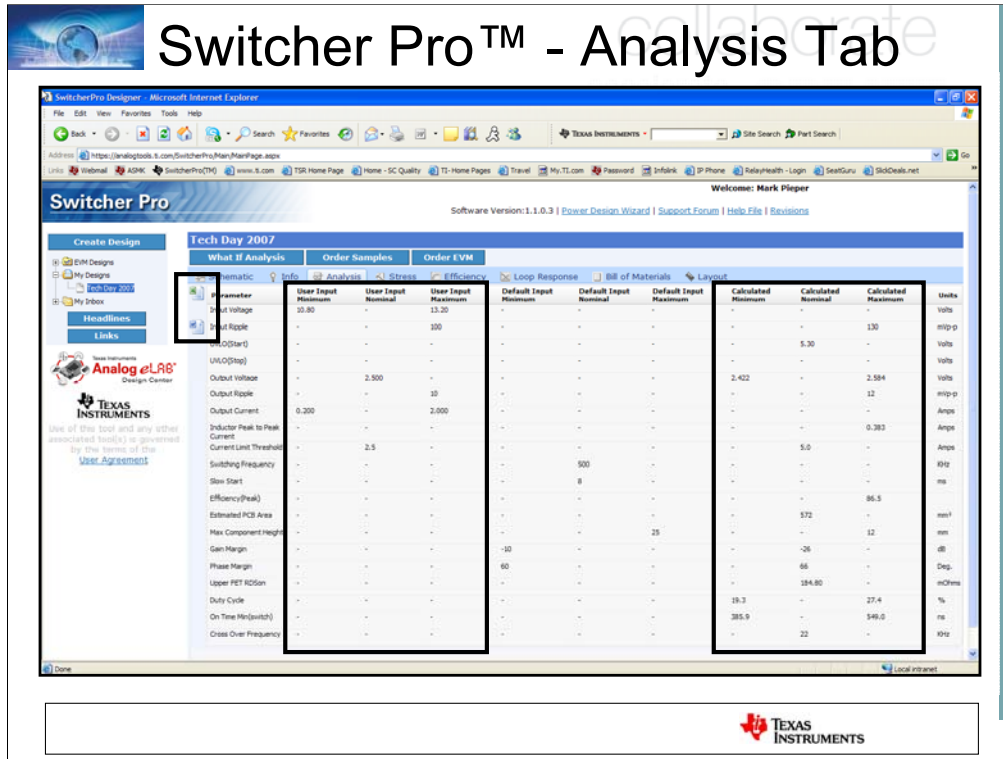D1 is changed to a MBR340T3 on the schematic page



The Switcher Pro Analysis tab provides a comparison between the specified design requirements (**User Inputs**) <click> and the anticipated performance (**Calculated**) <click>.

The Analysis table can be exported to either Excel or Word documents by selecting the appropriate icon in the upper left <click>.

Switcher Pro™ - Stress Tab

Switcher Pro Designer - Microsoft Internet Explorer

Address: <https://analogtools.ti.com/SwitcherPro/MainPage.aspx>

Welcome: Mark Pieper

Software Version: 1.1.0.3 | [Power Design Wizard](#) | [Support Forum](#) | [Help File](#) | [Revisions](#)

Switcher Pro

What If Analysis | Order Samples | Order EVM

Schematic | Info | Analysis | Stress | Efficiency | Loop Response | Bill of Materials | Layout

Device	Rated Voltage	Calculated Voltage	Rated Current (RMS)	Calculated Current (RMS)	Power	Calculated Max Temp
C1 (High-Prec. Input Cap)	50V	13.2V	1.85A	0.85A	24W	-
C2 (Bulk Output Cap)	6.3V	2.5V	3.96A	0.11A	20W	-
L1 (Output Inductor)	-	-	2.9A	2A	100mW	-
D1 (Switch Diode)	40V	13.2V	3A	1.8A	24W	37°C
U1 (Controller)	30V	13.2V	3A	1.05A	33W	-

Max Junction Temperature is calculated using Ambient Temperature 25°C along with the resistance (junction to ambient) specified by the manufacturer, with their standards for board layout. It is recommended that the user review the specifications given by the FET manufacturer for their board layout standards. Using a low cost PCB with minimal copper will have a great impact on heat dissipation and could lead to much higher junction temperatures. Calculated voltage does not take into account spike voltages caused by various parasitic inductances and capacitances that are factors of board layout.


TEXAS INSTRUMENTS

The Switcher Pro Stress tab provides stress analysis for the critical components in the design.

It compares component rated voltage and current to the calculated value in the design.


It calculates the power dissipation for each component, and if a thermal impedance is associated with that component it calculates the max temperature for that component.

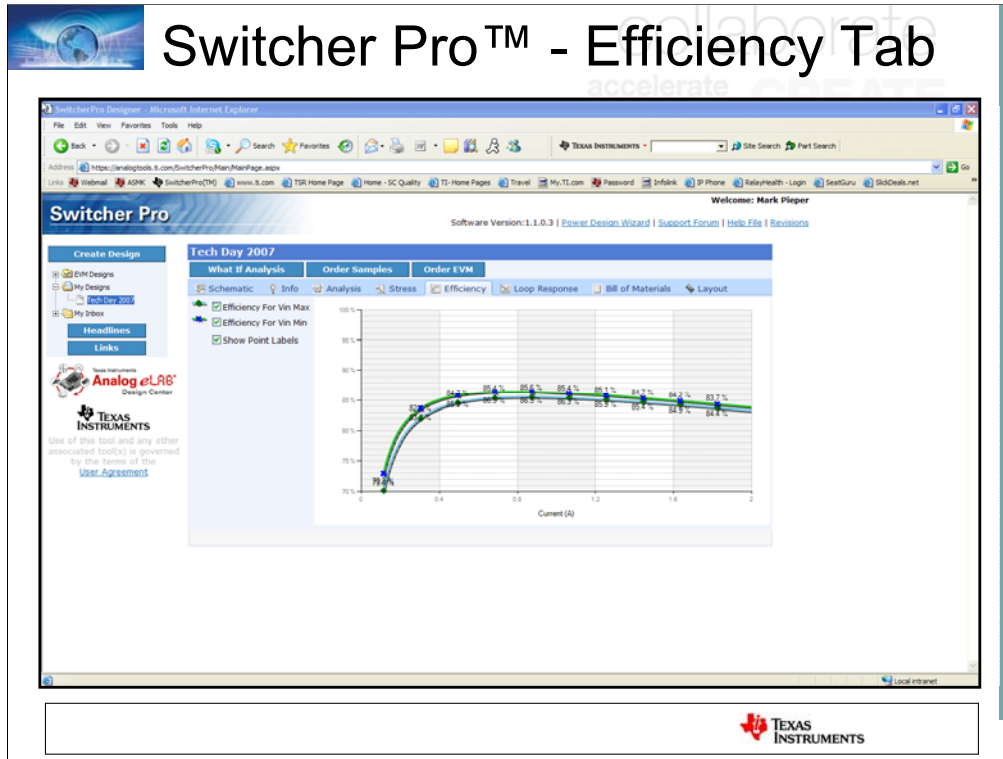The Stress table can be exported to either Excel or Word documents by selecting the appropriate icon in the upper left.




The Switcher Pro Efficiency tab displays the calculated efficiency curves for the design for both Vin min and Vin max.

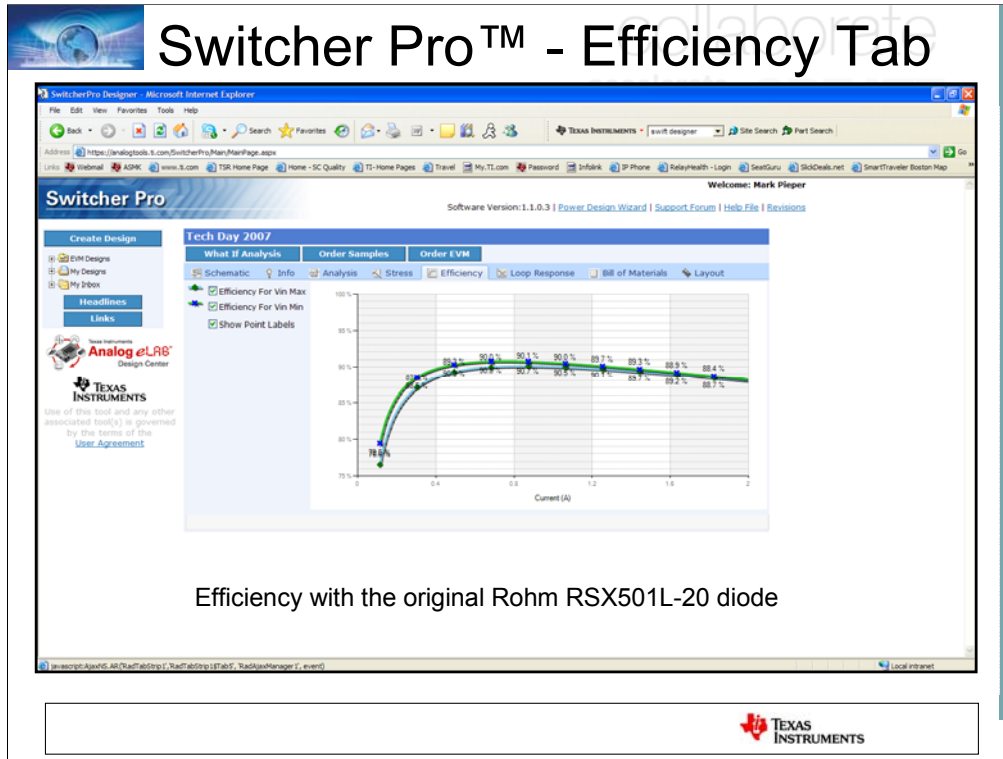The buttons allow customizing the graph to show or hide data.




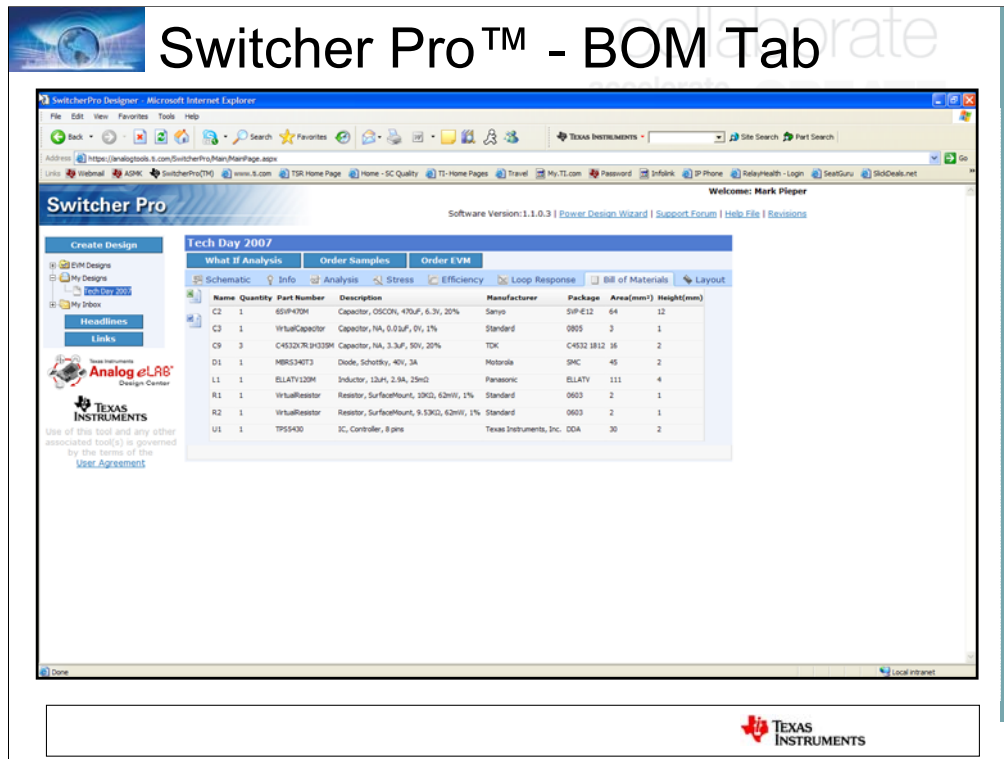This is the efficiency curve for the original design before the diode was changed. Note that SwitcherPro had selected a more efficient component.




The Switcher Pro Bill of Materials tab displays the purchasing data for the components in the design. Notice that these are all real (not ideal) components. The various parasitic parameters (capacitor ESR, FET $R_{ds(on)}$, Inductor resistance) are all included in the model used for the design analysis.

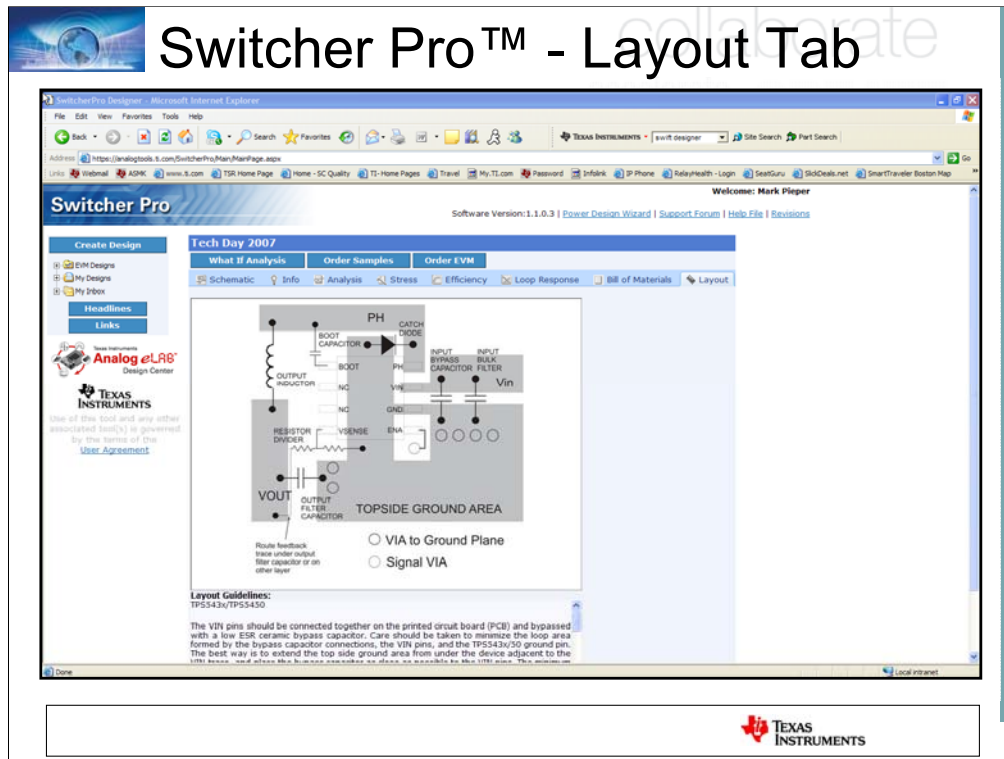The BOM table can be exported to either Excel or Word documents by selecting the appropriate icon in the upper left.




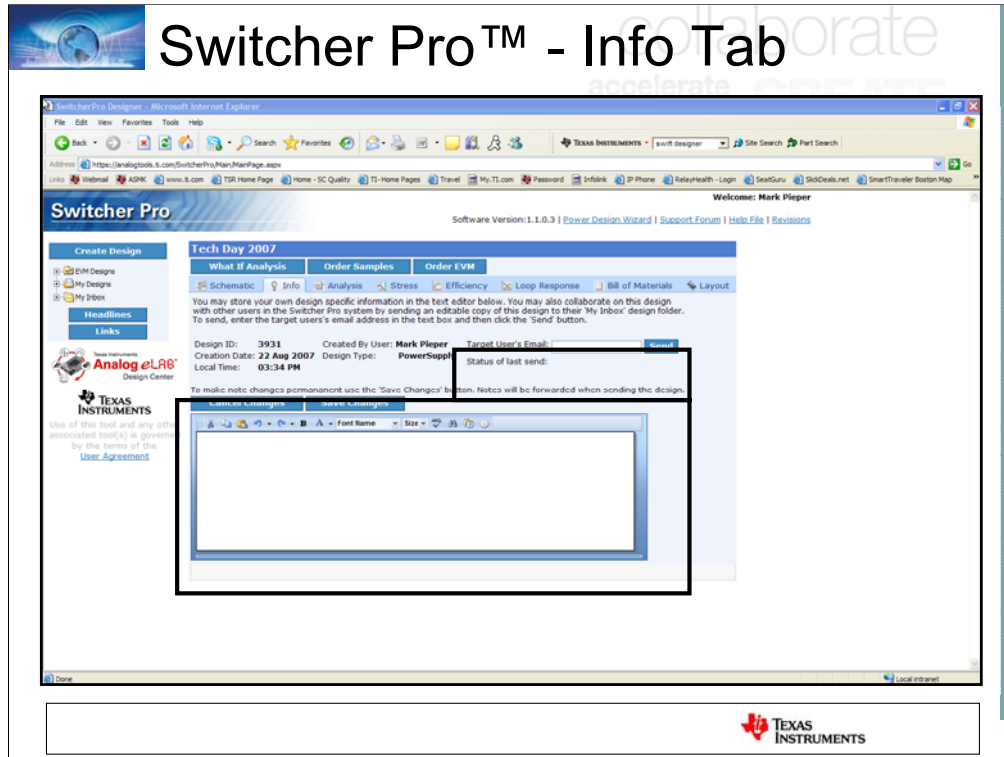The Layout tab presents an example PCB layout for the specific controller selected. Additionally, layout guidelines are included that explain the specific issues that need to be considered during the PCB design.



The Switcher Pro Info tab is a place to store notes, design analysis, or any other information related to the design that is needed <click>.

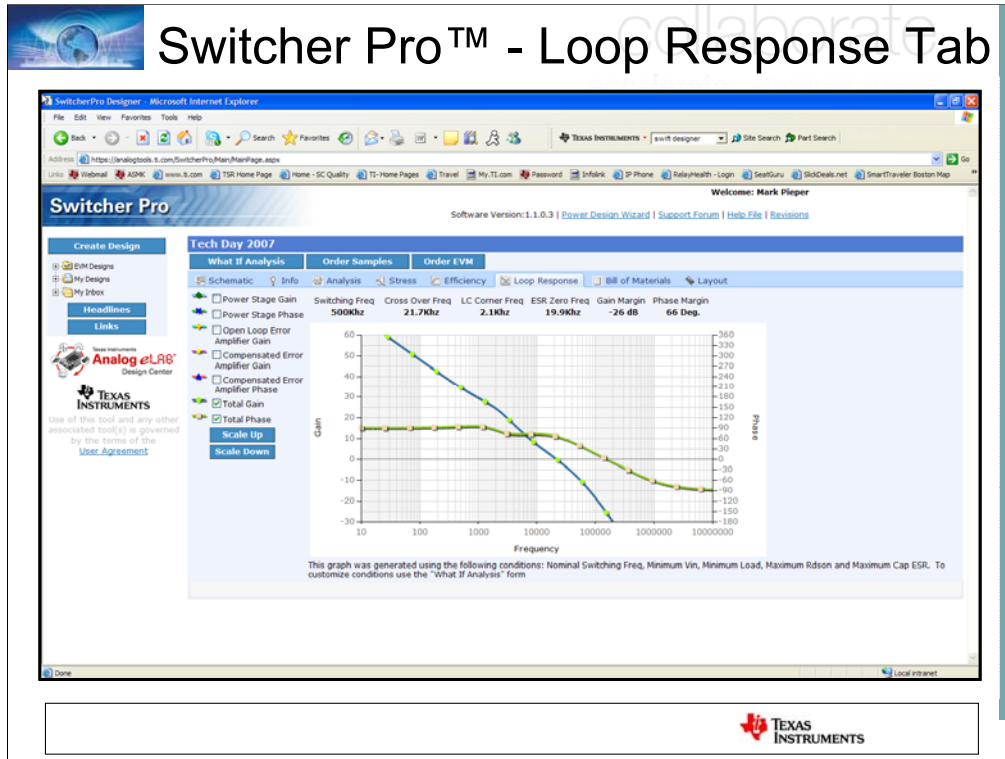This tab also enables you to send the design to a co-worker for collaboration and/or review <click>.



The Loop Response tab enables the designer to examine the bode plot of the Power Stage, compensation <click> (feedback including the error amplifier), and the total closed loop bode plot <click>.


The bode plot is a means of assessing the relative stability of the power supply design.

Phase Margin is the phase above 360° when the gain = 0dB. The phase margin should be above 45 degrees, and 60 degrees is a good goal.

Gain margin is the gain below 0dB when the phase crosses over 360 degrees. Gain margin of 10dB or greater is a good design goal.



What If Analysis Tool

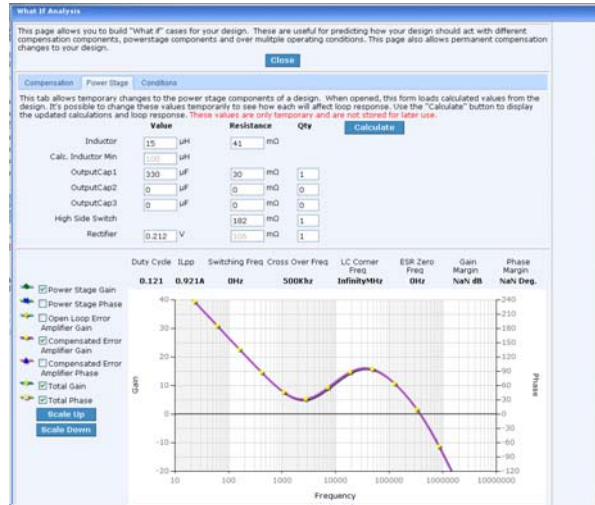



Working with the tool

- 3 Examples to try on your own



Questions?



Batteries for Portable Systems

Rich DelRossi





Agenda

- The Portable System
- Common Battery Technologies
- Li-Ion Technology
- Battery Management Overview
 - Fuel Gauging
 - Safety
 - Authentication
 - Charge Management

The Portable System

The diagram illustrates a portable system architecture. On the left, a **Battery Pack** contains a **Li-Ion/Poly** battery and three management blocks: **Fuel Gauge**, **Security**, and **Safety**. A **USB** symbol and a USB cable icon are shown above the main power distribution blocks. The power flow starts from the battery pack, passing through a **CFE** (Central Fuel Element) and a **Charger** block. The **Charger** block is connected to a **PC** and an **HDQ** (High-Density Quad) interface. The power then splits into several parallel paths, each containing a conversion block: **Buck/Boost**, **Boost Converter**, **RF LDO**, **Boost Converter**, **Charge Pump**, and **LCD Bias**. These blocks are connected to various system components: **Hard Drive**, **Memory**, **RF Module**, **LED Backlight**, **Audio Supply**, and **SFF LCD Display**. A **Supervisor** block is connected to the **Charger** and the **PMU** (Power Management Unit). The **PMU** is connected to the **DSP** (Digital Signal Processor), which is also connected to the **Supervisor**. The **DSP** is shown with a small icon of a person, suggesting it is the central processing unit for the system.



Portable Development Focus






- What makes power management products for portable end equipment different?


Needs

- Low quiescent current
- Higher Efficiency
- Small Solution Size / Packaging
- Lower Cost
- More Voltage Levels

collaborate
accelerate CREATE

Common Power Sources

	→ Alkaline AAA,AA,C,D →	1.5V (max) to .9V (min)
	→ Alkaline 9V →	9V (max) to 5V (min)
	→ Secondary Li-Ion/Poly →	4.2V (max) to 2.9V (min)
	→ Secondary NiMH/NiCD →	1.5V (max) to 1.0V (min)
	→ LiMgDO2 (CR2032) →	3.0V (max) to 2.0V (min)



There are several different battery chemistries that one can choose from in designing their power source. They range from Alkaline, to Li-Ion, Ni based chemistries. The voltage output on these batteries ranges from a minimum of 1.5V to a maximum of 9V. These batteries drop from fully charged to discharged through the battery life.

You could also have a regulated bus which provides you with a voltage of 5V or 12V and that stays constant.



Chemistry Comparison

	Ni-Cd	Ni-MH	Li-Ion	Li-Polymer	Alkaline
Operating Voltage	1V - 1.4V	1V - 1.4V	2.5V - 4.2V	2.5V - 4.2V	0.9V-1.5V
Cell Cap. (Ah)	0.3 -10	0.1 -12.5	0.13 -5.6	0.15 -4.4	D-12; C-6 AA-2; AAA-1
Cost	\$	\$\$	\$\$\$	\$\$\$\$	\$
Advantage	Low Cost & Medium Self Discharge Rate; Rechargeable	Low Cost & Lower Self Discharge Rate; Rechargeable	Good Energy Density; Doesn't suffer from memory loss; Rechargeable	Good Energy Density and flexible form factor; Doesn't suffer from memory loss; Rechargeable	Low Cost & Virtually no self discharge rate
End Equipment	Portable hand tools. Remote controlled toys -anything requiring a fast discharge	Digital cameras and other common electronic devices	Consumer electronics: cellular phones, digital cameras, and notebook computers	Consumer electronics: cellular phones, digital cameras, and notebook computers	low-drain electronics like smoke detectors



1)The first thing to look at is operating voltage. Know the range of voltage that your unit can handle and where your cutoff voltages should be.

Cutoff voltages are extremely important

A small variation in cutoff voltage will affect cycle life

2)Note the advantages of each chemistry. This can help you understand the designers' goals.


3)What is different about Alkaline batteries? They are non-rechargeable. Whatever you do – don't try to sell TI chargers to an engineer that is using Alkaline batteries.



collaborate
accelerate
CREATE

Li-Ion Battery Growth

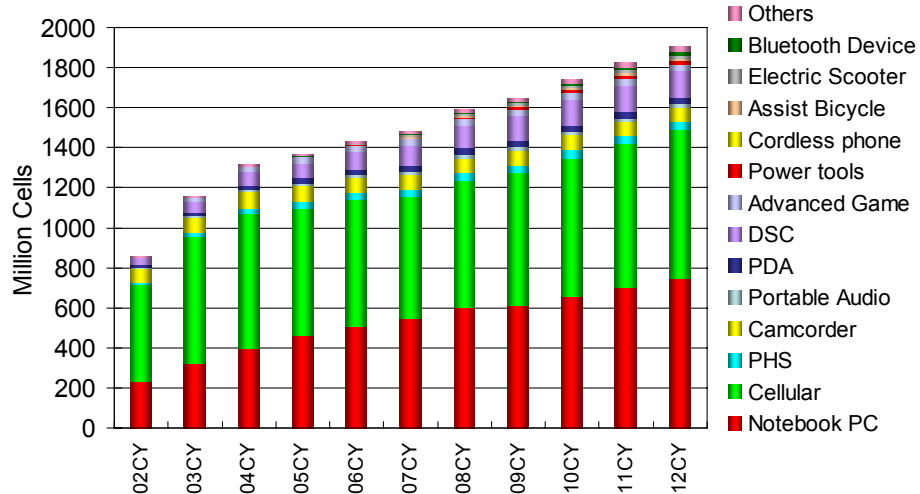WW LIB/LIP Cell Demand For Portable Devices (HEV not included)






Driving forces of Li-Ion Development

- **Cost reduction (Co elimination/reduction)**
- **Higher energy (capacity/voltage increase)**
- **Higher discharge rate capability**
- **Increased safety**



Cost reduction need

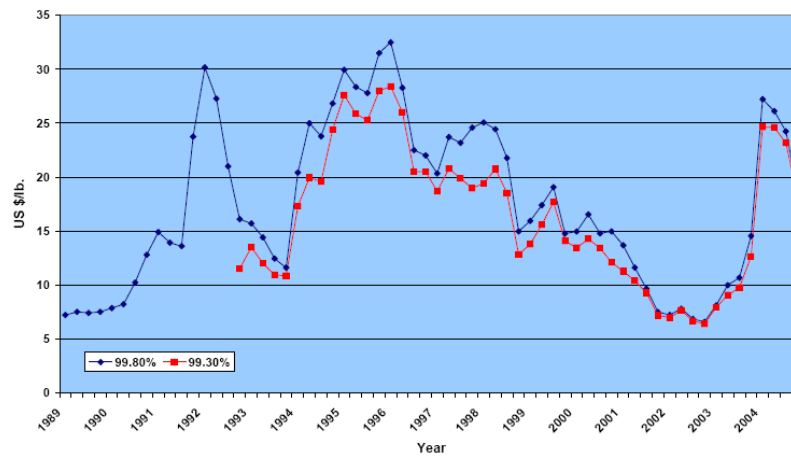Cobalt Price 1989-2004 (Quarterly Averages)



Cobalt News, April 2005, http://www.thecdi.com/cdi/images/news_pdf/Cobalt_News_April_2005.pdf






Need for higher energy

Flat batteries



Mobile devices:
2001=100

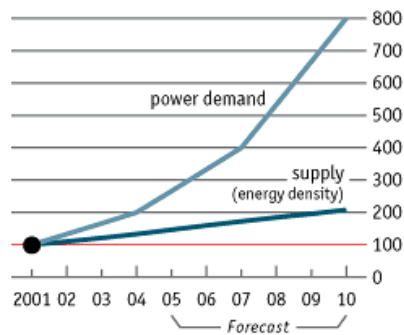

Source: Boston Consulting Group



Higher discharge rates problem

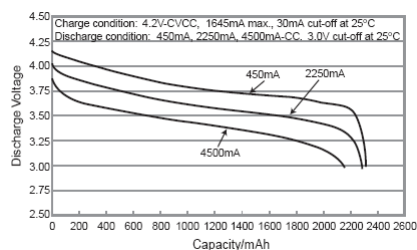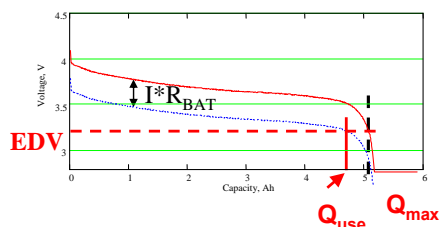

*Panasonic CGR18650D datasheet

- High internal resistance of traditional Li-ion battery causes large $I \cdot R$ drop at discharge rates above 2C rate
- Minimal system voltage is reached too early, reducing useable capacity
- Some markets that Li-ion makers try to penetrate require full discharge in 5-20 min (15C-3C rate)




Need for improved safety



- **Lithium-ion battery is known to undergo thermal run-away on overcharge or overheating**
- **Large battery support is needed for moving into new markets such as power tools and hybrid vehicles**
- **Explosion of mobile battery is a dangerous accident, but explosion of a larger hybrid car battery is likely to be a disaster**

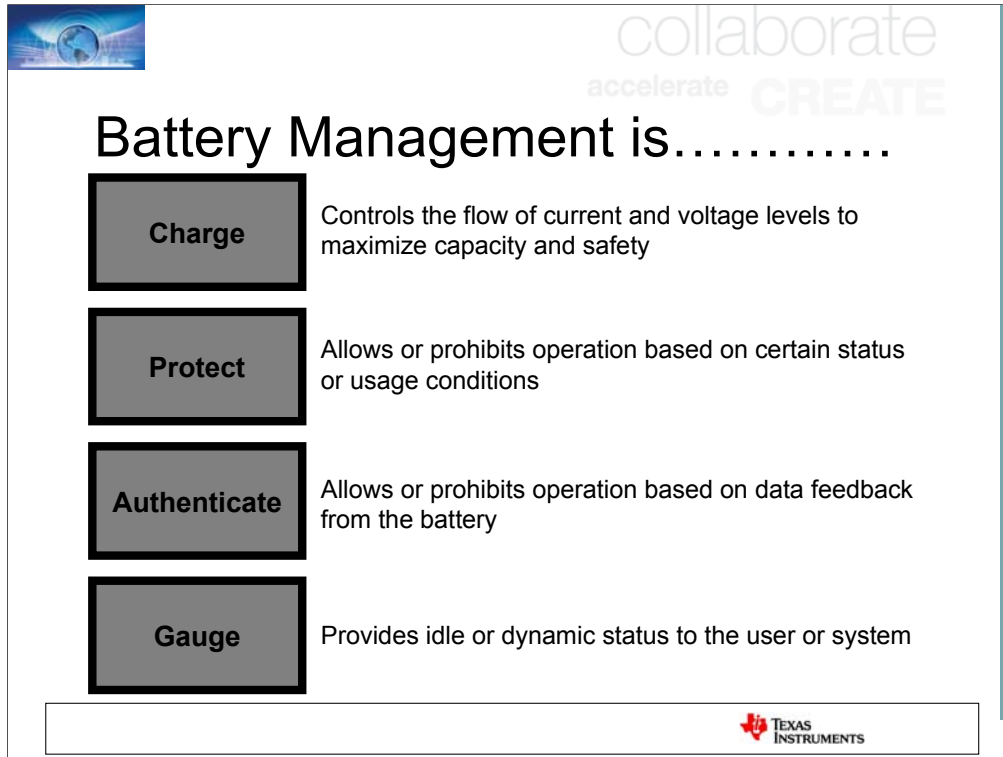Screen shot from Valence Technology video of large battery overcharge



Systems require battery management to:

- Extend run times
- Maximize safety
- Maximize battery life

Components of Battery Management:

Battery Fuel Gauging: Continuous battery monitoring & communication

Charge Management: Battery charge control

Battery Protection: Primary battery protection from abuse conditions

Battery Authentication: Identifies peripherals

Note on Protection:

A second set of design challenges results from the basic properties of rechargeable lithium cells. First, there are certain safety issues when designing with the most common lithium batteries: Lilon and LiPolymer. A Lilon pack contains multiple levels of protection, including mechanical and electrical protection-circuit modules, which prevent charging above 4.3 V, discharging below 2.3 V, and short circuits.



collaborate

Customer Demands for Battery Management



- ◆ Number of mobile users increasing
- ◆ Functionality increasing
- ◆ More power applications
- ◆ Power demand increasing 2x faster than battery improvements
- ◆ Efficiency increasing
- ◆ Cost
- ◆ Portable consumers demand more out of their battery





Fuel Gauging

- Predicts battery capacity **under all system active and inactive conditions**
- Battery capacity **can be reported in terms of accurate percentage, time to empty/full, milliamp-hours or watt-hours, talk time, idle time, # of pictures, etc.**
- Other data **can be obtained for battery health and safety diagnostics.**
 - # of charge/discharge cycles
 - Maximum operating temperature
 - Current I, V & T conditions
 - Fully charged, empty conditions
 - Near empty warnings
 - Over- / under-charge conditions



73%
Run Time 6:23

Fuel Gauging – Ease of Use

Standard Gauging (Today):

- Measures current, voltage, and temperature, and integrate current over time (*coulomb counting*).
- Models the battery cells reaction to discharge rate, temperature, age.
- Models self-discharge and non-measurable currents.
- **Re-learns** the full charge capacity over time
- Calculates and accumulates prediction error (could increase significantly over six months).
- Remaining Capacity = full charge capacity - $\sum i \Delta t$ - self discharge - module current - residual capacity - error.

Impedance Track™

Directly measures effect of discharge rate, temp, age and other factors on cell impedance

Calculates effect on remaining capacity and full charge capacity

No models/learning needed



Design capacity

Full charge capacity

Available capacity




Residual capacity





collaborate
accelerate
CREATE

Li-Ion Current Load Discharge Profile

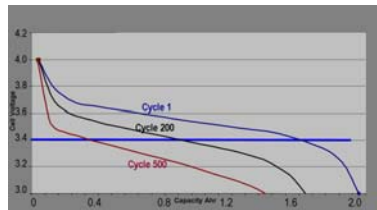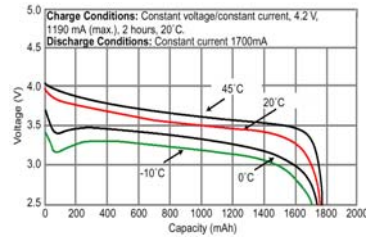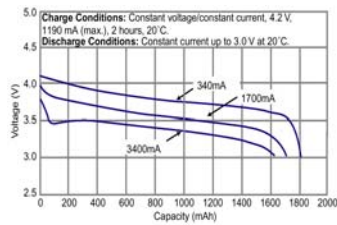

Usable Capacity and Shutdown Voltage vary with Discharge Rate, temperature, and cycle count



Li-ion battery rate capability can be tailored in wide range by using thicker or thinner layers of active materials. Thinner layers mean higher rate capability but less energy density. Typical 18650 cylindrical cells used in notebooks are designed for maximal C rate discharge. However, there are cells rated for 10C discharge used in portable power-tools, and even cells capable to 60C rate discharge used for power backup/regenerative braking in hybrid gas-electric vehicles.

Rate capability is severely degraded at low temperatures below 0°C because of low conductivity of organic electrolytes. Some electrolytes are better than other, therefore referring to manufacturers data on low-temperature discharge is important.




Fuel Gauging Benefits

- Accurate report of remaining run time
- Better Power Management
- Orderly shutdown
 - Automatically save data to flash with reserve energy when battery dies
- Longer Run Time
 - Power management
 - Accuracy: less guard band needed for shutdown
 - Variable shutdown voltage with temperature, discharge rate, and age based on impedance



collaborate
create

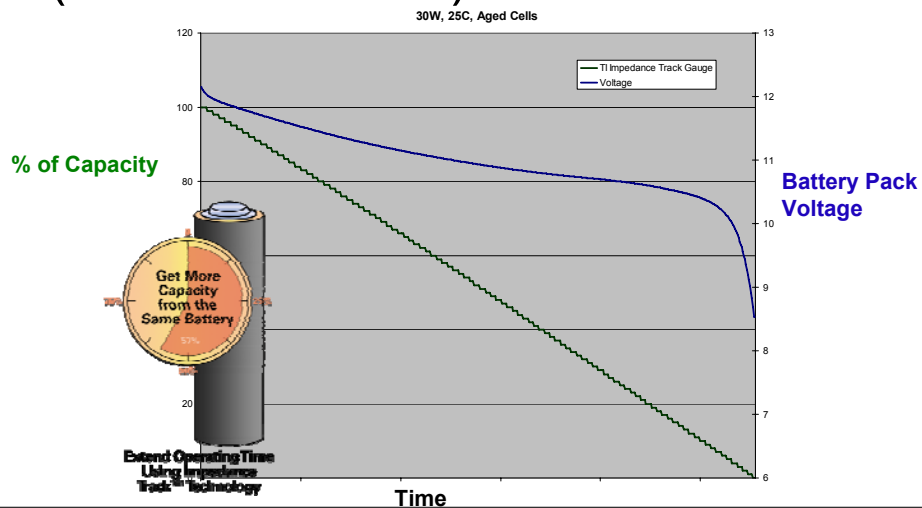Results! Reported Capacity (3 cells in series)





Why the need for Battery Authentication?

Front page news on EETimes 09/20/2004:

"Fake batteries blow up in the Industry's face"

Also:

- HELSINKI (Reuters Oct 2003) - Nokia pointed the finger at counterfeit batteries after another of its phones exploded and burned its user, the third such case in two months, and said original batteries sold with its phones were safe..... Following the latest Dutch incident, which left a 15-year-old boy in the town of Hengelo with leg burns, the country's consumer watchdog said it would probe the case.
- June 2004: 50,000 Verizon phones recalled with fake LG batteries – 18 reports of injuries or property damage due to exploding batteries.
- October 2004: Kyocera recalls 1,000,000 cell phones due to fraudulent batteries in its KE/KX 400 series of phones



Why the need for Battery Authentication?

- Safety
 - System compatibility (charger, battery, system)
- Brand Protection
 - People say “The *Nokia Phone* caught fire...”, not “The *aftermarket battery* caught fire...”
- Protect Business Model
 - Maintain and control after market battery sales
- IP Protection
 - Protect IP embedded in battery management system







Protection

- ALL Li-Ion battery packs MUST have protection circuits
- Over & Under Voltage, Over Current and some have Over Temp
- Primary IC Controls CHG and DCHG FET
- Common solutions include 1-4 cell in series
 - Series = Add Voltage
 - Parallel = Add Capacity
- Additional system side protection is also available




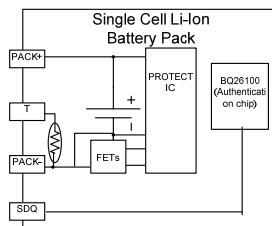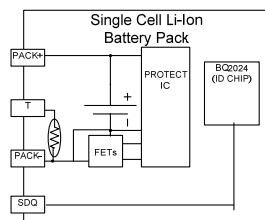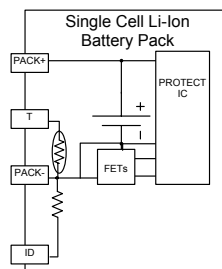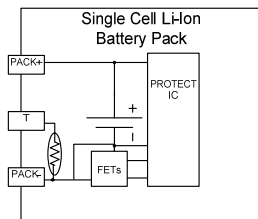Protection + Authentication in 1S Battery Packs





System Side Protection

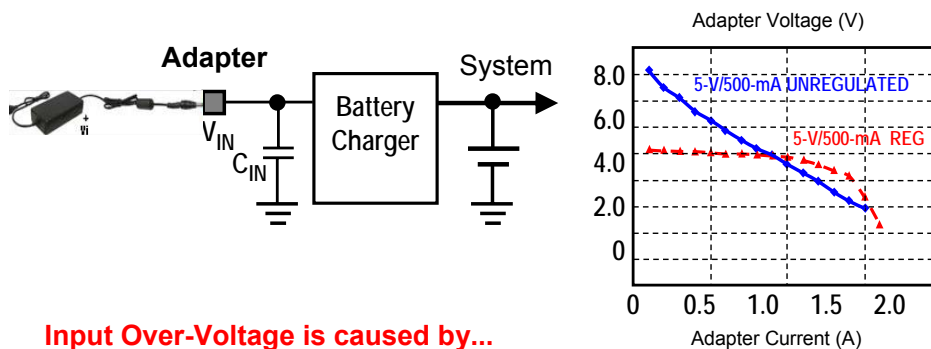

Input Over-Voltage is caused by...


- ◆ Wrong adapter or after-market adapter
- ◆ Transformer-rectifier adapters (un-regulated)
- ◆ Hot-plug event



New USB Standard driven by China




AC 100-240 V 50/60 Hz
DC 5 V, 0.31 A

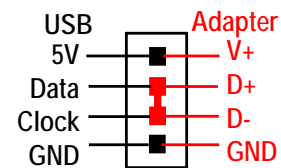

- ◆ **USB type A connector for cell phone charger**
- ◆ **Purpose is to share adapter and cable among different cell phones to save cost and save environment**
- ◆ **New standard to drive “after-market” accessory makers to develop phone adapters that may or may not need safety standards**
 - This drives the need for redundant safety features



CFE Improves Safety

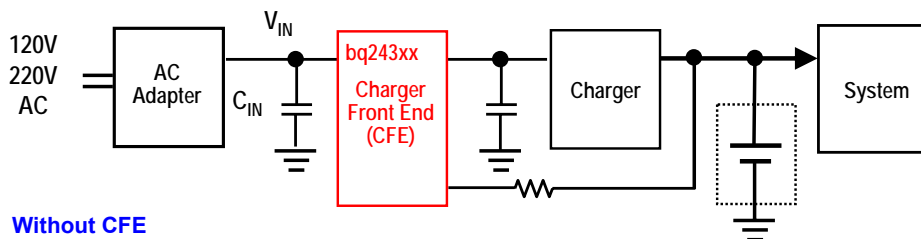

Without CFE

If charger fails for any reason...

- System will be in over-voltage condition and fail
- Battery will be over-charged

CFE Provide System Level Protections

- Input transient over-voltage up to 30V
- Steady state over-voltage
- Up to 1.5A Over-current protection
- Optional adapter reverse polarity
- Battery over-voltage





Charge Management

Linear Charger

Features

- ✓ Simple low-cost design
- ✓ Uses few external components
- ✓ No switching noise
- ✓ Fast transient response
- ✓ Low quiescent current

Limitations

- ✓ *Potential* Poor Efficiency: V_{OUT}/V_{IN}
- ✓ Power dissipation may be a concern

Best Used When

- ✓ V_{IN} to V_{OUT} is small
- ✓ Low output noise is important
- ✓ Space and cost are important
- ✓ Low output current

1S Segment

Switchmode Charger

Features

- ✓ Wide range of V_{IN} and I_{OUT}
- ✓ Very Efficient
- ✓ Limited Power Dissipation

Limitations


- ✓ Larger solution size
- ✓ More expensive to implement
- ✓ Noise

Best Used When


- ✓ Need best efficiency for battery life
- ✓ Higher currents are needed
- ✓ V_{IN} and V_{OUT} are wide

2,3,4S Segment



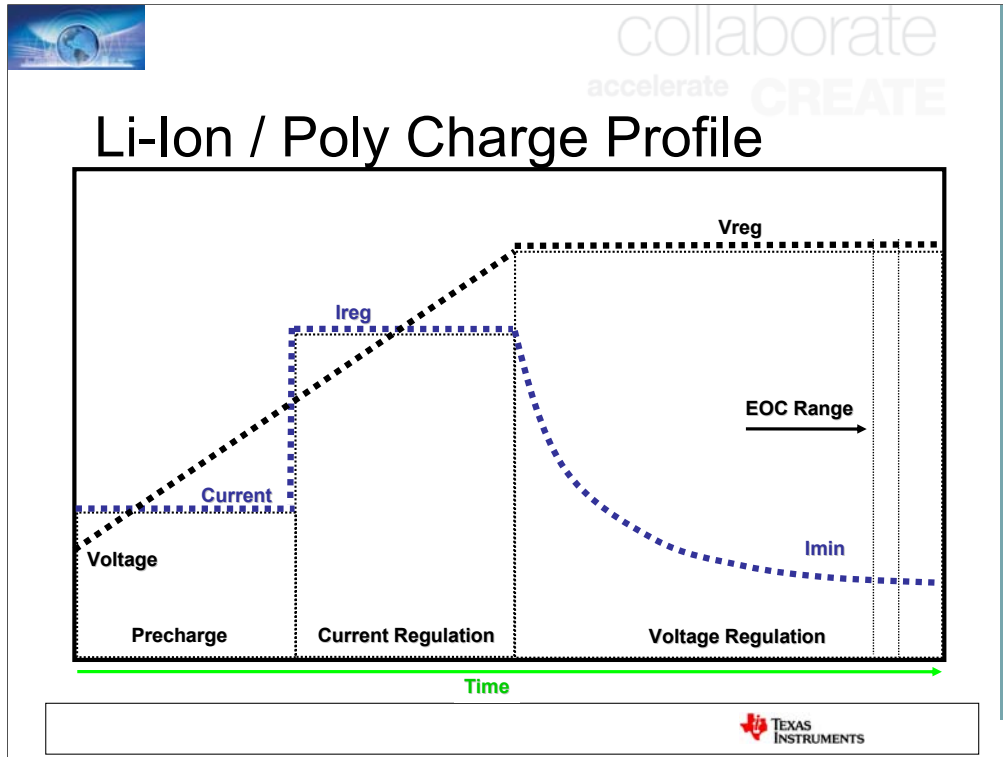

This is a lithium-ion charge profile → It is a constant current/constant voltage configuration. During the linear voltage increase in the pre-charge phase the current stays the same. Once it hits the current Regulation phase the current jumps up to I_{reg} or the maximum current output. Once the voltage hits 4.15-4.2 Volts its at its' V_{reg} - max voltage in the safe zone for lithium ion batteries. It will stay charging at the V_{reg} while the current slopes down. Once the current is detected at a minimum the charger will stop discharging.

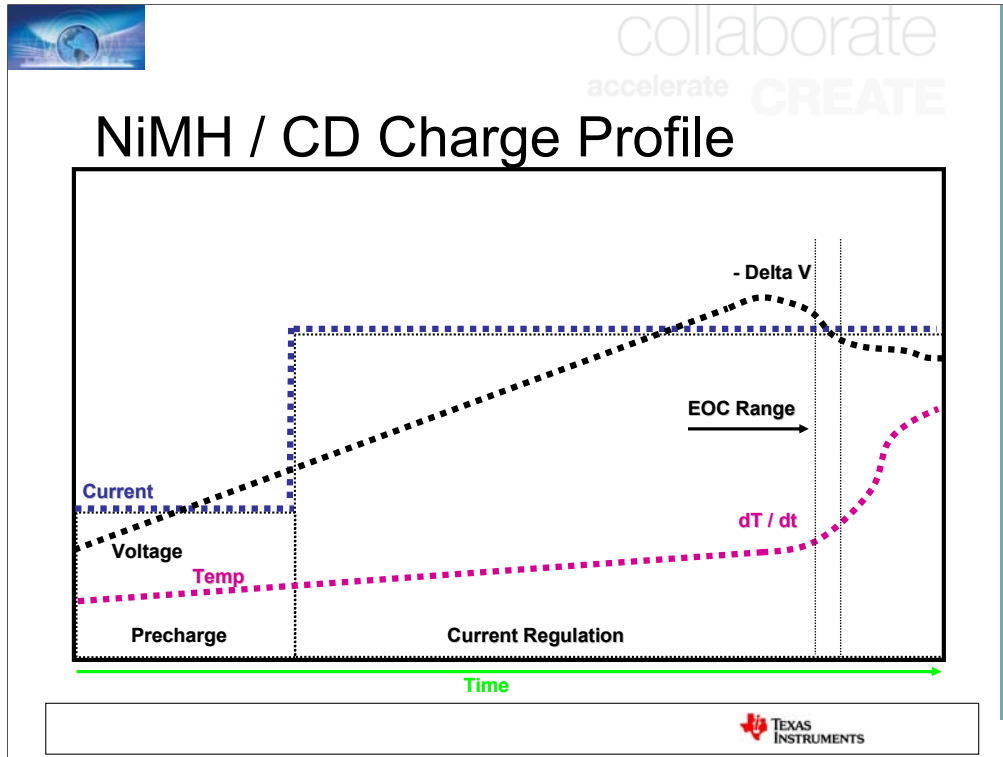

The NiMH Charge Profile is a little different. This profile is known as a constant current profile. In the pre-charge phase the current is stable and then it hits a certain voltage and jumps to the max where the current stays constant. The voltage will continue to increase until it reaches a threshold where it begins to fall off. This is known as $-\Delta V$ and is one indicator that the battery is charged. The other indicator is that the DT/dt gets higher and higher as the voltage keeps increasing and the current stays the same – the IC gets Hotter. When the dT/dt reaches a certain point the charger will enter the end of charge range and stop charging the battery.



Do I need?

- Thermal Regulation
 - The ability to lower charge current when high temp conditions exist
- Powerpath Management
 - The ability to run the system at full power while charging the battery
 - System has priority power
- Over Voltage Protection
 - An extra level of voltage transient protection on the input
- Single or Dual Input
 - USB and Supply



collaborate
accelerate CREATE

Single Cell Charger trend

- Linear dominate the 1S segment but some customers are moving to Switchmode for better charge times plus less heat



Dec 2007


- ◆ Highly efficient charging from USB or AC/DC
- ◆ Reduces charge time vs. linear charger approach
- ◆ Ultra-small solution for USB On-the-Go (3-MHz, WCSP, integrated reverse-boost function)
- ◆ Compatible with new battery chemistries (adjustable regulation voltage)





collaborate
CREATE

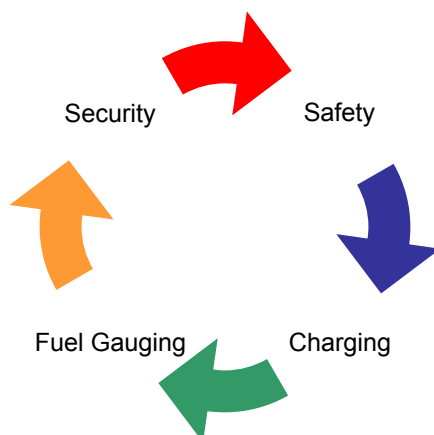Battery Management is a System level approach





Final Question:

What battery management products do you think are in these products?

Example #1



Example #2



Example #3





Conclusion

- The Li-Ion battery is evolving into different “Versions” generating new voltage levels and power characteristics
- The solutions that manage Li-Ion need to work together to provide the maximum performance and safety
- TI is the leader in power & battery management and continues to deliver innovative products that meet the changing environment



Questions?



Thank You!