



# **Power Supply Layout Considerations**

**Seminar Paper at:**

**<http://focus.ti.com/lit/ml/slup230/slup230.pdf>**





## Agenda

- ➔ DC Parasitics (Resistance)
- ◆ AC Parasitics
- ◆ Grounds and Grounding
- ◆ Thermal Considerations
- ◆ Design Examples




## You Mean Copper is Not a Perfect Conductor?

- ◆ Since it is not, it impacts
  - Regulation
  - Efficiency
  - Temperature rise



## Sample Resistance Calculation

 

Material	$\mu\Omega\text{-cm}$	$\mu\Omega\text{-in}$
Copper	1.70	0.67
Gold	2.2	0.87
Lead	22.0	8.66
Silver	1.5	0.59
Tin -Lead	15	5.91
Palladium	11	4.3

$$R = \frac{\rho l}{A}$$

$\rho = \text{resistivity}$




The numbers given for Plated Copper are worst-case values.

Typically, they will lie somewhere between pure copper and these values.


 
## Count Squares to Estimate Trace Resistance

- ◆ Copper resistivity is  $0.67 \mu\Omega$  in. at  $25^\circ\text{C}$  and doubles for  $254^\circ\text{C}$  rise



$$R = \frac{\rho(\ell)}{t(\ell)}$$

$$R = \frac{\rho}{t}$$


Copper Weight (Oz.)	Thickness (mm/mils)	mΩ per Square (25°C)	mΩ per Square (100°C)
1/2	0.02/0.7	1.0	1.3
1	0.04/1.4	0.5	0.65
2	0.07/2.8	0.2	0.26




 
## Vias Have Resistance Too

◆ Typical rule of thumb is 1 A to 3 A per via



$$R = \frac{\rho l}{A}$$

$$R = \frac{\rho l}{\pi(r_o^2 - r_i^2)}$$

$$R = \frac{2.36 \times 10^{-6} \times 0.06}{\pi(0.01^2 - 0.009^2)} = 2.4 \text{ m}\Omega$$





## Agenda


- ◆ DC parasitics (resistance)
- AC parasitics
  - When is a capacitor not a capacitor ?
- ◆ Grounds and grounding
- ◆ Thermal considerations
- ◆ Design examples



## Capacitors Are Inductive...
 
### Above Their Self-Resonant Frequency

- ◆ Measured ESL correlates well with rule of thumb inductance of 15 nH/inch








## Bypass Capacitor Layout

- ◆ Minimize lead inductance
  - Minimize bypass loop area
  - Short lengths on high di/dt paths
  - Use ground planes where possible
  - Bring current path across capacitor terminals

- ◆ Parallel different capacitor types for reduced impedance across a frequency band

- ◆ Parallel different ceramic capacitors values and sizes to reduce impedance in the 2-20 MHz frequency range (0.1  $\mu\text{F}$  & 0.01  $\mu\text{F}$ )

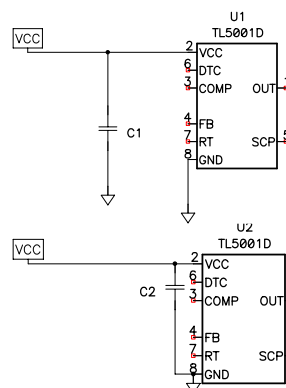
- ◆ Draw your schematic so the layout person knows the critical routes




 
## Sample Capacitance Calculation

Consider two 10 mil traces crossing with 10 mil PWB thickness



$$C = \frac{\epsilon_R \times \epsilon_O \times A}{t}$$

$$C = 5 \left( \frac{10^{-9}}{36\pi} \right) \left( \frac{0.00025^2}{0.00025} \right)$$

$$C = 0.01 \text{ pF}$$

Note: 10 mils = 0.00025 m


Not much capacitance but consider the area of all those components connected to the summing node




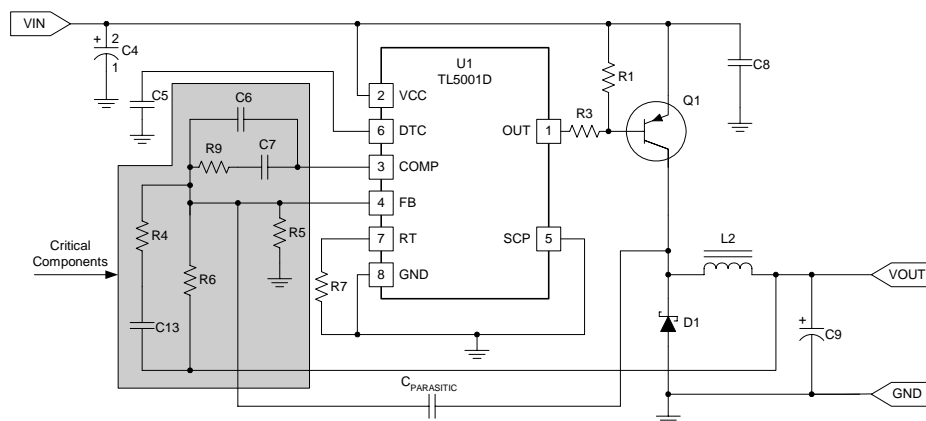
## Chaos Created by Noise Injection


Ten  $0.05 \times 0.02 \text{ in}^2$  pads in summing junction can increase parasitic capacitance to 2 pF




 
## And Inductors Turn Into Capacitors


- ◆ Inductive at low frequency
- ◆ High frequency, distributed capacitance and  $\mu_r$  reduction




 
## Self Inductance of PWB Traces

- ◆ Due to the natural logarithmic relationship, large changes in conductor width have minimal impact on inductance



$$L = 2\ell \left( \ln \left( \frac{\ell}{t + w} \right) + \frac{1}{2} \right) nH (cm)$$

$$L = 5\ell \left( \ln \left( \frac{\ell}{t + w} \right) + \frac{1}{2} \right) nH (in)$$


w (mm/in)	T(mm/in)	Inductance (nH/cm or nH/in)
0.25/0.01	0.07/0.0028	10/24
2.5/0.1	0.07/0.0028	6/14
12.5/0.5	0.07/0.0028	2/6




 
## PWB Traces Over Ground Planes

- ◆ Substantial inductance reduction
- ◆ Inductance inversely proportional to width




Metric			English		
h (cm)	w (cm)	Inductance (nH/cm)	h (in)	w (in)	Inductance (nH/in)
0.25	2.5	0.2	0.01	0.1	0.5
1.5	2.5	1.2	0.06	0.1	3.0




 
## Magnetic Coupling

- ◆ Consider alternate orientation of second inductor to minimize coupling





## Watch Out for Parasitic Components

### ◆ Wiring inductance

- Especially low impedance circuits-filters, power switching, timing
- Use ground planes and wide conductors to minimize

### ◆ Board capacitance

- High impedance or noise sensitive circuits
- Watch out for coupling between planes and to component pads

### ◆ Magnetic coupling

- Inductor to inductor, especially toroids, consider alternate mounting directions
- Loop to loop, minimize loop areas, use ground planes






## Agenda

- ◆ DC parasitics (resistance)
- ◆ AC parasitics
- Grounds and grounding
  - Construction from the ground up
- ◆ Thermal considerations
- ◆ Design examples




## Single Point Grounds

### Series

 

- ◆ Simple wiring
- ◆ Common impedance causes different potentials
- ◆ High impedance at high frequency ( $>10$  kHz)

### Parallel

 


- ◆ Complicated wiring
- ◆ Low differential potentials at low frequencies
- ◆ High impedance at high frequency ( $>10$  kHz)





## Multipoint Grounding

 


- ◆ Ground plane provides low impedance between circuits to minimize potential differences
- ◆ Also, reduces inductance of circuit traces
- ◆ Goal is to contain high frequency currents in individual circuits and keep out of ground plane


 
## Ground Planes

Don't route ground plane under common mode inductors






## Agenda

- ◆ DC parasitics (resistance)
- ◆ AC parasitics
- ◆ Grounds and grounding
- ➔ Thermal considerations
  - Getting the heat out
- ◆ Design examples



 
## Temperature Rise

- ◆ **R<sub>JC</sub>**: Junction to case thermal resistance, usually specified
- ◆ **R<sub>CS</sub>**: Interface resistance, specified for heat sink insulators, negligible for solder connections
- ◆ **R<sub>SA</sub>**: Sink to ambient resistance, specified for heatsinks, otherwise ill-defined


 
### Electrical Equivalent


$$T = P_{\text{DISS}} \times (R_{\text{JC}} + R_{\text{CS}} + R_{\text{SA}}) + T_{\text{A}}$$





## Power Supplies Components

### Many Are PWB Mounted and Cooled

 


- ◆ Power is conducted through device base into circuit board
- ◆ It spreads laterally through copper conductors
- ◆ Final path is convection cooling from board surface to ambient


 
## Typical Thermal Requirements

- ◆ Ambient temperature: 70°C,  $T_A$
- ◆ Maximum semiconductor: 125°C, Max  $T_J$
- ◆ Maximum board temperature: 120°C
- ◆ Typical semiconductor loss: 2 W
- ◆ PowerPAD™ SO-8 thermal resistance: 2.3°C/W
- ◆ Calculated PWB temperature under semiconductor is  
 $125^\circ\text{C} - (2\text{ W} \times 2.3^\circ\text{C/W}) = 120^\circ\text{C}$







## Convection Cooling (English Units)

- ◆ To a first approximation, temperature rise is proportional to power dissipation and inversely proportional to surface area ( $S_a$ )
- ◆ The proportionality constant,  $h$ , is called heat transfer coefficient and is about  $0.006 \text{ W/in}^2/\text{°C}$  for air

$$\Delta T = \frac{P}{(S_a \times h)} = \frac{P}{(S_a \times 0.006)} \quad \Delta T = \frac{166 \times P}{S_a} \quad R_{SA} = \frac{166}{S_a}$$

- ◆ Or 1 W over a square inch yields about  $166\text{°C}$  rise
- ◆ More precise equation accounting for the nonlinearity of  $h$

$$\Delta T = P^{0.8} S_a^{-0.7} (100^\circ \text{C})$$





## Convection Cooling (Metric Units)

- ◆ To a first approximation, temperature rise is proportional to power dissipation and inversely proportional to surface area
- ◆ The proportionality constant,  $h$ , is called heat transfer coefficient and is about  $0.001 \text{ W/cm}^2/\text{°C}$  for air

$$\Delta T = \frac{P}{(Sa \times h)} = \frac{P}{(Sa \times 0.001)} \quad \Delta T = \frac{1000 \times P}{Sa} \quad R_{sa} = \frac{1000}{Sa}$$

- ◆ Or 1 W over a square cm yields about  $1000\text{°C}$  rise
- ◆ More precise equation accounting for the nonlinearity of  $h$

$$\Delta T = P^{0.8} Sa^{-0.7} (650\text{°C})$$





## Convection Cooling Area Calculations (English)

- ◆ Applying the simple formula and solving for 50°C rise

$$\Delta T = \frac{166 \times P}{Sa}$$

$$Sa = \frac{166 \times P}{\Delta T}$$

$$Sa = \frac{166 \times 2}{50}$$

$$Sa = 7$$

- ◆ The package is much smaller than this dimension and something must be done to provide a larger cooling surface



## Convection Cooling Area Calculations (Metric)

- ◆ Applying the simple formula and solving for 50°C rise

$$\Delta T = \frac{1000 \times P}{Sa}$$

$$Sa = \frac{1000 \times P}{\Delta T}$$

$$Sa = \frac{1000 \times 2}{50}$$

$$Sa = 40$$

- ◆ The package is much smaller than this dimension and something must be done to provide a larger cooling surface




## Thermal Conductivity of Other Materials

Material	W/(cm °C)	W/(in °C)
Air	0.0002	0.0007
Alumina	0.2	0.9
Aluminum	1.8	4.4
Beryllia	1.6	4
Copper (OFC)	3.6	9
Epoxy (PC board)	0.0003	0.007
Ferrite	0.04	0.10
Steel	0.15	0.60
Tin-lead	0.4	1.00



## Lateral Heat Flow

 


Metric	English
<b>2-oz, 0.07-mm thick copper</b>	<b>2-oz, 2.8-mils thick copper</b>
$R = \frac{l}{(\sigma \times l \times t)}$ $R = \frac{1}{(0.4 \times 0.07)}$ $R = 40^\circ C/W$	$R = \frac{l}{(\sigma \times l \times t)} = \frac{1}{(\sigma \times t)}$ $R = \frac{1}{(9 \times 0.0028)}$ $R = 40^\circ C/W$
<b>1.5-mm FR4</b>	<b>0.06-inch FR4</b>
$R = \frac{1}{(0.00028 \times 1.5)}$ $R = 2400^\circ C/W$	$R = \frac{1}{(0.007 \times 0.06)}$ $R = 2400^\circ C/W$




 
## Thermal Resistance

Through board is much less than board-ambient



$$R = \frac{t}{(\sigma \times A)}$$

$$R = \frac{1.5}{(0.0003 \times 25.4 \times 25.4)} \quad \text{Metric}$$

$$R = \frac{0.06}{(0.007 \times 1)} \quad \text{English}$$

$$= 8^{\circ}\text{C/W}$$



Calculations based on one square inch of board area.




  
## Thermal Resistance

A single via has about 100°C/W thermal resistance and they can be paralleled



$$R = \frac{l}{(\sigma \times A)}$$

$$R = \frac{l}{\sigma \times \pi \times (r_o^2 - r_i^2)}$$

$$R = 100^\circ \text{C} / \text{W}$$







## Dissipation on Double-Sided Board

2 W of point source dissipation on double-sided board calculates to  $\sim 30^{\circ}\text{C}$  rise under the source

**Metric**

 

**English**

 



## Vertical Cools Better Than Horizontal

Surface Orientation	K' (cm. °C, and W)	K' (in. °C, and W)
Vertical	650	100
Horizontal plane, top surface	675	104
Horizontal, bottom surface	1375	204

$$\Delta T = Pd^{0.8} \times \frac{K'}{A^{0.7}}$$






## PWB Cooling Strategy

- ◆ Use many large, thick copper planes to distribute heat across PWB surface
- ◆ Maximize the thermal paths with poured copper wherever practical
- ◆ Use both sides of the board to cool
- ◆ Reasonably low thermal resistance is possible through the PWB material but substantial improvements can be made with thermal vias
- ◆ Avoid breaks in planes as they substantially degrade lateral heat flow
- ◆ Buried planes can also improve the lateral heat flow
- ◆ Cooling strategy often opposed to noise reduction




## Even a Whisper of Air can Reduce Temperatures

**Metric**

 

**English**

 

System airflow yields 20% to 60% drops in temperature rise






## Agenda

- ◆ DC parasitics (resistance)
- ◆ AC parasitics
- ◆ Grounds and grounding
- ◆ Thermal considerations
- Design examples
  - Let's get real!




## Proper Sensing of Output Voltage

Sensing at Output Connector

 

Poor Sense Location

 


◆ How many  $m\Omega$  between L2 and J3?






## Output Capacitor Connection

Low Series Inductance

 

High Series Inductance

 


◆ How much inductance in series with C39? (length ~ 1 in.)




 
## Connect Power Components Properly

- ◆ Very high  $di/dt$  in current path
- ◆ Any inductance in path results in ringing on switched node
- ◆ Minimize loop area
  - Draw schematic to reflect this
  - Consider two sided mounting, FET's one side, cap other
  - Make sure components are placed and routed accordingly
- ◆ Proper design can eliminate need for snubber








## Input Capacitor Placement
 
### Good input capacitor placement and layout




- ◆ Input caps located close to top FET Q5 with large plane
- ◆ Input caps GND side drops into GND plane through multiple vias
- ◆ Bottom FET Q6 GND drops into GND plane through multiple vias
- ◆ Solid uninterrupted GND plane


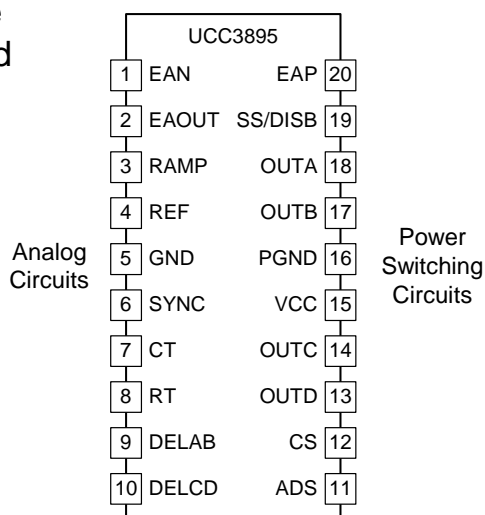
## Partitioning Circuits


- ◆ Many control ICs recognize noisy/quiet circuit areas and pin out accordingly
- ◆ Some even provide a separate pin for power and analog ground
- ◆ Good practice plans layout around pin out, uses a ground plane, and keeps high current out of it.






## Separate Power Path

Separate power path from control signals

 




## Layout of Controller Small Signals

 

- ◆ Very short etch runs
- ◆ Error Amp connections (pins - 7,8) are noise sensitive and should be routed carefully
- ◆ Use GND plane on layer 2
- ◆ Drop returns into GND plane without long etches
- ◆ Feedback to output voltage routed away from switching power signals




## High Current Layout Example

 

- ◆ Maximize copper
- ◆ Duplicate on several layers
- ◆ Thermal vias near heat sources
- ◆ Eliminate bottlenecks
- ◆ Use low  $\theta_{JC}$  components




## Good EMI Filter Layout

 

- ◆ Common mode inductor T2 input pins do not cross output pins
- ◆ No GND plane under EMI filter
- ◆ Wide, short etch used to minimize losses
- ◆ Wide spacing between etches meets HV requirements and minimizes coupling capacitance



## Thermal Image

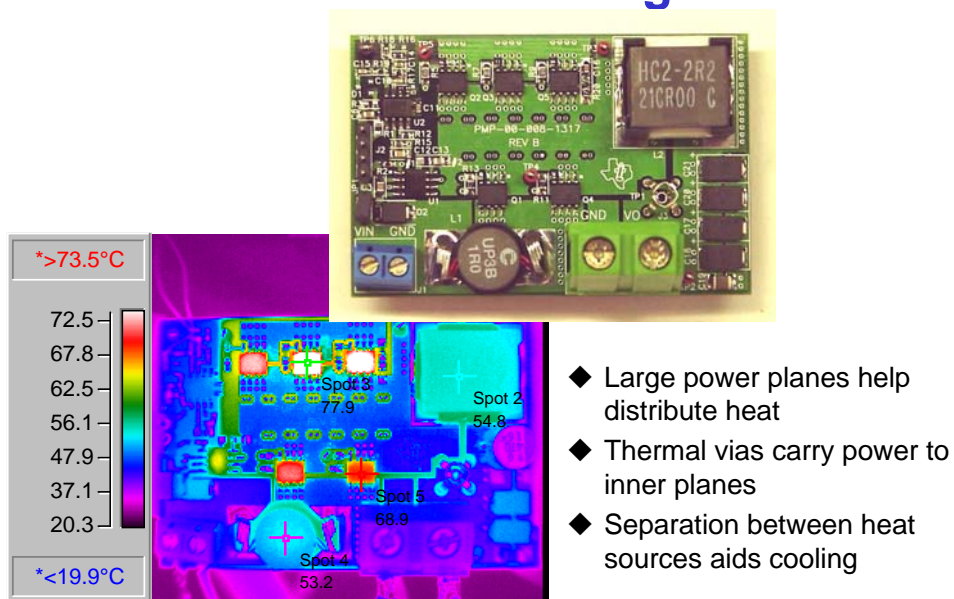

- ◆ Large power planes help distribute heat
- ◆ Thermal vias carry power to inner planes
- ◆ Separation between heat sources aids cooling





## **A Good Layout**

### **Makes For A Successful Design**

- ◆ Power supply layout is as important as any other design consideration
- ◆ The power supply engineer must be involved in parts placement and routing
- ◆ But it is not 'black magic', it is an understanding of AC and DC parasitics, grounding, and cooling that makes a successful design

### **Seminar Paper at:**

**<http://focus.ti.com/lit/ml/slup230/slup230.pdf>**

