

# Hardware Applications

---

---

---

---

---

---

## 3.1 I/O Port Usage

The each I/O of Port0, Port1, and Port2 has interrupt capability for the leading edge and trailing edge of an input signal. This has the following advantages:

- More than one interrupt input is available
- Eight resp. 24 external events can wake-up from Low Power Modes 3 or 4
- No glue logic is necessary for most applications: all inputs can be observed without the need of gates connecting them to a single interrupt input.
- Wake-up is possible out of any input state (high or low)
- Due to the edge-triggered characteristic of the interrupts, no external switch-off logic is necessary for long-lasting input signals, therefore no multiple interrupt is possible therefore.

### 3.1.1 General Usage

Six peripheral registers controlling the activities of the I/O–Port0 are shown in Table 3–1.

*Table 3–1. I/O–Port0 Registers*

Register	Usage	State After Reset
Input register	Signals at I/O terminals	Signals at I/O terminals
Output register	Content of output buffer	Unchanged
Direction register	0: Input 1: Output	Reset to input direction
Interrupt flags	0: No interrupt pending 1: Interrupt pending	Set to 0
Interrupt edges	0: Low to high causes Interrupt 1: High to low causes Interrupt	Unchanged
Interrupt enable	0: Disabled 1: Enabled	Set to 0

The interrupt vectors, flags and peripheral addresses of I/O–port 0 are shown in Table 3–2.

*Table 3–2. I/O–Port0 Hardware Addresses*

Name	Mnemonic	Address	Contents	Vector
Input Register	P0IN	010h	P0IN.7 ... P0IN.0	—
Output Register	P0OUT	011h	P0OUT.7 ... P0OUT.0	
Direction Register	P0DIR	012h	P0DIR.7 ... P0DIR.0	—
Interrupt Flags	P0IFG	013h	P0IFG.7 ... P0IFG.2	0FFE0h
	IFG1.3	002h	P0IFG.1	0FFF8h
	IFG1.2	002h	P0IFG.0	0FFFAh
Interrupt Edges	P0IES	014h	P0IES.7 ... P0IES.0	
Interrupt Enable	P0IE	015h	P0IE.7 ... P0IE.2	
	IE1.3	000h	P0IE.1	
	IE1.2	000h	P0IE.0	

The other I/O–Ports are organized the same way except the following items:

- Port1 and Port2 contain eight equal I/Os, the special hardware for bits 0 and 1 is not implemented. Additionally, the ports have two function select registers, P1SEL and P2SEL .
- Port3 and Port4 do not have interrupt capability and registers P3IFG, P4IFG, P3IES, P4IES, P3IE and P4IE do not exist. Additionally, the ports have two function select registers P3SEL and P4SEL. These registers determine if the normal I/O–Port function is selected (PxSEL.y = 0) or if the terminal is used for a second function (PxSEL.y = 1) (see Table 3–3).

The MSP430C33x uses the two function select registers P3SEL and P4SEL for the following purposes:

- P3SEL.y = 1: The Timer\_A I/O functions are selected (see Table 3–3)
- P4SEL.y = 1: The USART functions are selected (see the MSP430x33x Data Sheet, SLAS163)

Table 3–3. *Timer\_A I/O–Port Selection*

<b>P3SEL.y = 0</b>	<b>P3SEL.y = 1 Compare Mode</b>	<b>P3SEL.y = 1 Capture Mode</b>
Port I/O P3.0	Port I/O P3.0	Port I/O P3.0
Port I/O P3.1	Port I/O P3.1	Port I/O P3.1
Port I/O P3.2	Timer Clock input TACLK	Timer Clock input TACLK
Port I/O P3.3	Output TA0	Capture input CCI0A
Port I/O P3.4	Output TA1	Capture input CCI1A
Port I/O P3.5	Output TA2	Capture input CCI2A
Port I/O P3.6	Output TA3	Capture input CCI3A
Port I/O P3.7	Output TA4	Capture input CCI4A

*Example 3–1. Using Timer\_A in the MSP430C33x System*

An MSP430C33x system uses the Timer\_A. The Capture/Compare Blocks are used as follows:

- An external clock frequency is used: input at terminal TACLK (P3.2)
- Capture/Compare Block 0: outputs a rectangular signal at terminal TA0 (P3.3)
- Capture/Compare Block 1: outputs a PWM signal at terminal TA1 (P3.4)
- Capture/Compare Block 2: captures the input signal at terminal TA2 (P3.5)

To initialize Port3 for the previous functions the following code line needs to be inserted into the software (for hardware definitions see Section 6.3, *Timer\_A*):

```
MOV.B #TA2+TA1+TA0+TACLK,&P3SEL ; Initialize Timer I/Os
```

*Example 3–2. MSP430C33x System uses the USART Hardware for SCI (UART)*

A MSP430C33x system uses the USART hardware for SCI (UART). To initialize terminal P4.7 as URXD and terminal P4.6 as UTXD the following code is used:

```
MOV.B #URXD+UTXD,&P4SEL ; Initialize SCI I/Os
```

---

*Example 3–3. The I/O–ports P0.0 to P0.3 are used for input only.*

The I/O–ports P0.0 to P0.3 are used for input only. Terminals P0.4 to P0.7 are outputs and initially set low. The conditions are:

```
P0.0    Every change is counted
P0.1    Any high-to-low change is counted
P0.2    Any low-to-high change is counted
P0.3    Every change is counted
;
; RAM definitions
;
        .BSS      P0_0CNT,2          ; Counter for P0.0
        .BSS      P0_1CNT,2          ; Counter for P0.1
        .BSS      P0_2CNT,2          ; Counter for P0.2
        .BSS      P0_3CNT,2          ; Counter for P0.3
;
; Initialization for Port0
;
        MOV.B     #000h,&P0OUT       ; Output register low
        MOV.B     #0F0h,&P0DIR       ; P0.4 to P0.7 outputs
        MOV.B     #00Bh,&P0IES       ; P0.0 to P0.3 Hi-Lo, P0.2 Lo-Hi
        MOV.B     #00Ch,&P0IE       ; P0.2 to P0.3 interrupt enable
        BIS.B     #00Ch,&IE1        ; P0.0 to P0.1 interrupt enable
;
; Interrupt handler for P0.0. Every change is counted
;
P0_0HAN  INC      P0_0CNT            ; Flag is reset automatically
        XOR.B     #1,&P0IES         ; Change edge select
        RETI
;
; Interrupt handler for P0.1. Any Hi-Lo change is counted
;
P0_1HAN  INC      P0_1CNT            ; Flag is reset automatically
        RETI
;
; Interrupt handler for P0.2 and P0.3
```

```

; The flags of all read transitions are reset. Transitions
; occurring during the interrupt routine cause interrupt after
; the RETI
;
P0_23HAN PUSH      R5                ; Save R5
        MOV.B     &P0FLG,R5         ; Copy interrupt flags
        BIC.B     R5,&P0FLG         ; Reset read flags
        BIT      #4,R5              ; P0.2 flag to carry
        ADC      P0_2CNT            ; Add carry to counter
        BIT      #8,R5              ; P0.3 flag to carry
        JNC      L$304
        INC      P0_3CNT            ; P0.3 changed
        XOR.B     #8,P0IES          ; Change edge select
L$304   POP      R5                  ; Restore R5
        RETI
;
        .SECT    "INT_VECT",0FFF8h
        .WORD    P0_1HAN            ; P0.1 INTERRUPT VECTOR;
        .WORD    P0_0HAN            ; P0.0 INTERRUPT VECTOR;
;
        .SECT    "INT_VECT1",0FFE0h
        .WORD    P0_23HAN          ; P0.2/7 INTERRUPT VECTOR

```

### 3.1.2 Zero Crossing Detection

With the external components shown in Figure 3–1 it is possible to build a zero crossing input for the MSP430. The components shown are designed for an external voltage ac = 230 V. With a circuit capacitance (wiring, diodes) of C1 = 30 pF as shown in Figure 3–1, the following delays occur (all values for ac = 230 V, f = 50 Hz, V<sub>CC</sub> = +5 V, timing is in μs):

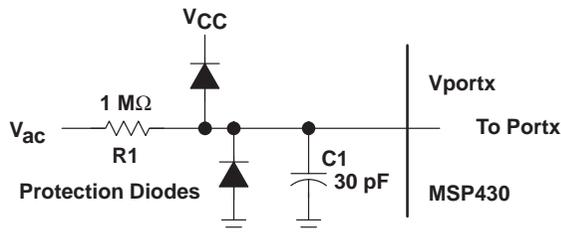


Figure 3–1. MSP430 Input for Zero-Crossing

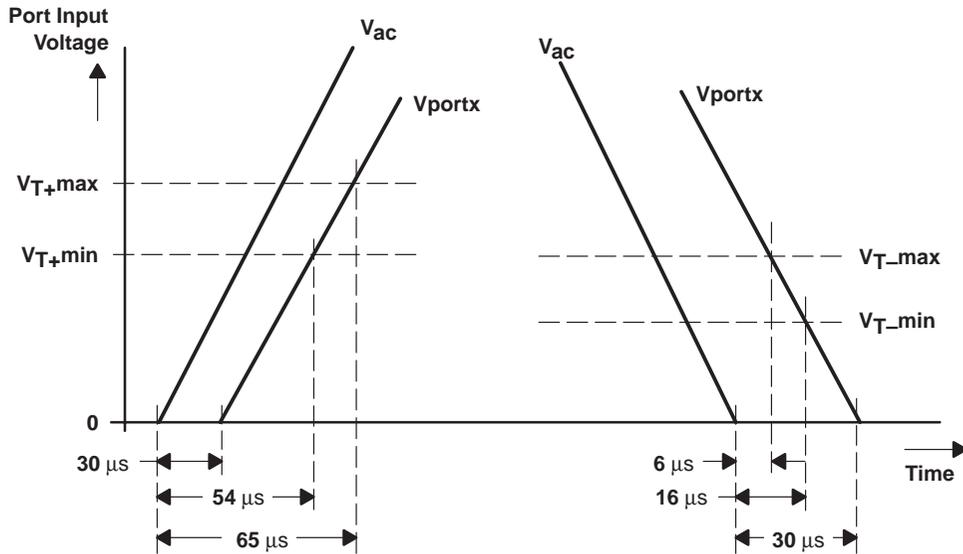


Figure 3–2. Timing for the Zero Crossing

Delay caused by RC (1 M $\Omega$  x 30 pF): 30  $\mu s$  or 0.54° (same value for leading and trailing edges).

Delay caused by input thresholds:

Leading edge: 24  $\mu s$  to 35  $\mu s$ . ( $V_{T+} = 2.3$  V to 3.4 V)

Trailing edge: 14  $\mu s$  to 24  $\mu s$ . ( $V_{T-} = 1.4$  V to 2.3 V)

The resulting delays are:

Leading edge: 54  $\mu s$  to 65  $\mu s$ .

Trailing edge: 6  $\mu s$  to 16  $\mu s$ .

These small deviations do not play a role for 50 Hz or 60 Hz phase control applications with TRIACs. If other input conditions than 230 V and 50 Hz are used then the resulting delays can be calculated with the following formulas:

$$t_D = \frac{V_T}{S_V}; S_V = \frac{d(U \times \sin\omega t)}{dt} = U \times \omega \times \cos\omega t$$

Where:

$t_D$	Delay time caused by the input threshold voltage	[s]
$V_T$	Input threshold voltage	[V]
$S_V$	Slope of the input voltage	[V/s]
$\omega$	Angular frequency $2\pi f$	[1/s]
$U$	Peak value of the input voltage $U_{ac}$	[V]

---

For  $t = 0$  (zero crossing time) the previous equation becomes:

$$t_D = \frac{V_T}{U \times \omega \times 1} = \frac{V_T}{U \times \omega}$$

### 3.1.3 Output Buffering

The outputs of the MSP430 (P0.x, P1.x, P2.x, P3.x, P4.x, Ox) have nominal internal resistances depending on the supply voltage,  $V_{CC}$ :

$$V_{CC} = 3 \text{ V: Max. } 333 \Omega \quad (\Delta V = 0.4 \text{ V max. @ } 1.2 \text{ mA})$$

$$V_{CC} = 5 \text{ V: Max. } 266 \Omega \quad (\Delta V = 0.4 \text{ V max. @ } 1.5 \text{ mA})$$

These internal resistances are non-linear and are valid only for small output currents (see the previous text). If larger currents are drawn, saturation effects will limit the output current.

These outputs are intended for driving digital inputs and gates and normally have too high an impedance level for other applications, such as the driving of relays, lines, etc. If output currents greater than the previously mentioned ones are needed then output buffering is necessary. Figure 3–3 shows some of the possibilities. The resistors shown in Figure 3–3 for the limitation of the MSP430 output current are minimum values. The application is designed for  $V_{CC} = 5 \text{ V}$ . The values shown in brackets are for  $V_{CC} = 3 \text{ V}$ .

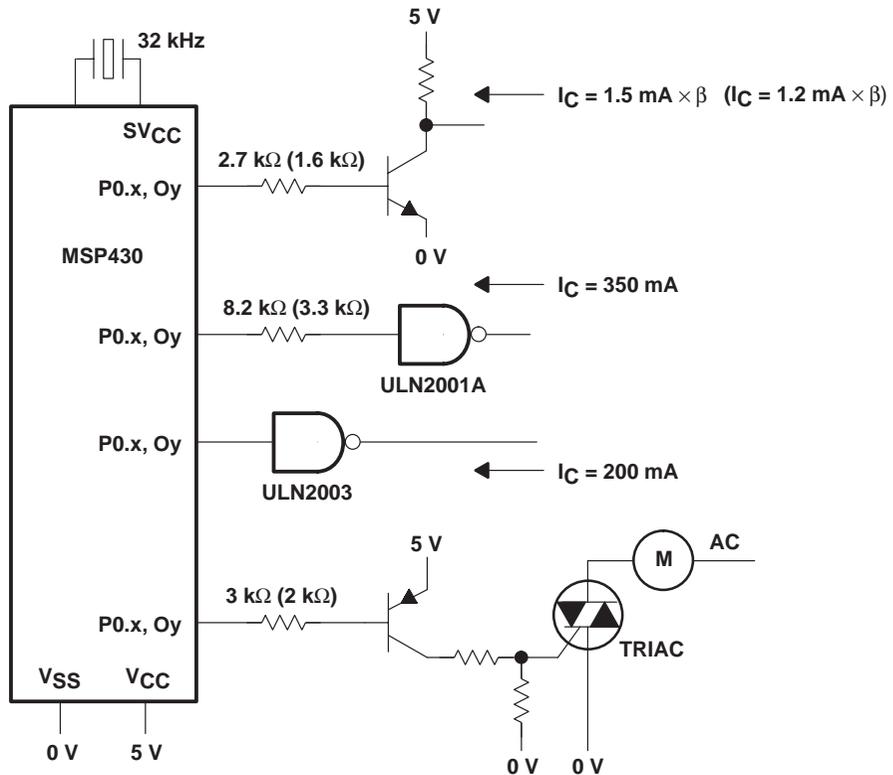


Figure 3–3. Output Buffering

### 3.1.4 Universal Timer/Port I/Os

If the Universal Timer/Port is not used for analog-to-digital conversion or is only partially used for this purpose, then the unused terminals are available as outputs that can be switched to high impedance. The Universal Timer/Port can be used in three different modes (see Figure 3–4):

- Two 8-bit timers, two inputs, one I/O, and 5 output terminals
- One 16-bit timer, two inputs, one I/O, and 5 output terminals
- An analog-to-digital converter with two to six output terminals

Ports TP0.0 to TP0.5 are completely independent of the analog-to-digital converter. Any of the ports can be used for the sensors and reference resistors.

After a power-up, the data register is set to zero and all TP0.x ports are switched to high impedance.

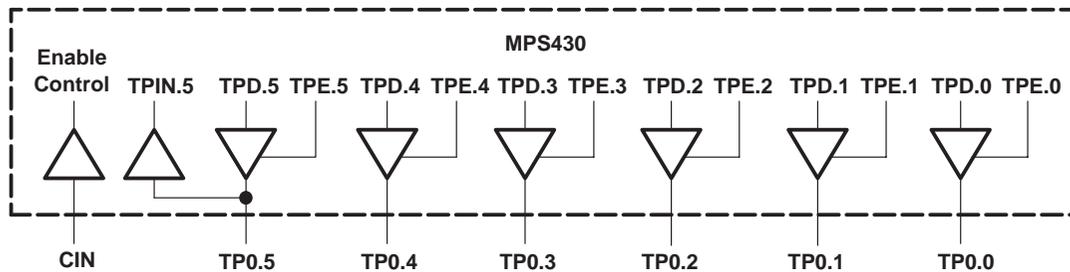


Figure 3–4. The I/O Section of the Universal Timer/Port Module

### 3.1.4.1 I/Os Used with the Analog-to-Digital Converter

The analog-to-digital conversion uses terminal CIN and at least two of the TP0.x terminals (one for the reference and one for the sensor to be measured); therefore up to 4 outputs are available. Bit instructions BIS.B, BIC.B, and XOR.B can only be used for the modification of the outputs. This is due to the location of the control bits in the data register TPD and data enable register TPE. The programming of the port is the same as described in the following section.

#### Note:

For precise ADC results, changes of the TP-ports during the measurement should be avoided. The board layout and the physical distance of the switched port determine the influence on the CIN terminal. Spikes coming from the switching of ports can change the result of a measurement. This is especially true if they occur near the crossing of the threshold voltage.

### 3.1.4.2 I/Os Used Without the ADC

This mode allows 5 outputs that can be switched to high impedance (TP0.0 to TP0.4) and one I/O terminal (TP0.5). Additionally, two 8-bit timers or one 16-bit timer are available. If one of the timers is used, only bit instructions BIT.B, BIS.B, BIC.B, or XOR.B can be used to operate the port. The four timer control bits are located in the data register TPD and data enable register TPE. If the MOV.B instruction is used, all the bits are affected.

---

### Example 3–4. All Six Ports are Used as Outputs

All six ports are used as outputs. The possibilities of the port are shown in the following:

```
;
; Definitions for the Counter Port
;
TPD      .EQU    04Eh          ; Data Register
TPE      .EQU    04Fh          ; Data Enable Register. 1:
                                output enabled
TP0      .EQU    001h          ; TP0.0 bit address
TP1      .EQU    002h          ; TP0.1 bit address
TP2      .EQU    004h          ; TP0.2 bit address
TP3      .EQU    008h          ; TP0.3 bit address
TP4      .EQU    010h          ; TP0.4 bit address
TP5      .EQU    020h          ; TP0.5 bit address
;
; Reset all ports and switch all to output direction
;
        BIC.B    #TP0+TP1+TP2+TP3+TP4+TP5,&TPD      ; Data to low
        BIS.B    #TP0+TP1+TP2+TP3+TP4+TP5,&TPE      ; Enable outputs
;
; Toggle TP0.0 and TP0.4, set TP0.5 and TP0.2 afterwards
;
        XOR.B    #TP0+TP4,&TPD                      ; Toggle TP0.0 and TP0.4
        BIS.B    #TP5+TP2,&TPD                      ; Set TP0.5 and TP0.2
;
; Switch TP0.1 and TP0.3 to HI-Z state
;
        BIC.B    #TP1+TP3,&TPE                      ; HI-Z state for TP0.1
                                                and TP0.3
```

### 3.1.5 I/O Used for Fast Serial Transfers

The combination of hardware and software, shown in the following, allows a fast serial transfer with the MSP430 family. The data line needs to be Px.0. Any other port can be used for the clock line. Any data length is possible. The LSB is transferred first. This can be easily changed by using RLC instead of RRC.

```

;
POOUT .EQU 011h ; Port0 Output register
PODIR .EQU 012h ; Port0 Direction register
P00 .EQU 01h ; Bit address of P0.0: Data
P01 .EQU 02h ; Bit address of P0.1: Clock
;
MOV DATA,R5 ; 1st 16bit data to R5
CALL #SERIAL_FAST_INIT ; 1st transfer, initialization
MOV DATA1,R5 ; 2nd 16bit data to R5
CALL #SERIAL_FAST ; 2nd transfer, LSB to MSB
.... ; aso.
;
; Initialization of the fast serial transfer: uses SERIAL_FAST too
;
SERIAL_FAST_INIT ; Initialization part
    BIC.B #P00+P01,&P0OUT ; Reset P0.0 and P0.1
    BIS.B #P00+P01,&PODIR ; P0.0 and P0.1 to output dir.
;
; Part for 2nd and all following transfers
;
SERIAL_FAST ; Initialization is made
    RRC R5 ; LSB to carry 1 cycle
    ADDC.B #P01,&P0OUT ; Data out, set clock 4 cycles
    BIC.B #P00+P01,&P0OUT ; Reset data and clock 5 cycles
;
    RRC R5 ; LSB+1 to carry 1 cycle
    ADDC.B #P01,&P0OUT ; Data out, set clock 4 cycle
    BIC.B #P00+P01,&P0OUT ; Reset data and clock 5 cycles
;
    ..... ; Output all bits the same way
;
    RRC R5 ; MSB to carry 1 cycle
    ADDC.B #P01,&P0OUT ; Data out, set clock 4 cycles
    BIC.B #P00+P01,&P0OUT ; Reset data and clock 5 cycles
RET
;

```

---

Each bit needs 10 cycles for the transfer, this results in a maximum baud rate for the transfer:

$$\text{Baud rate}_{\text{max}} = \frac{\text{MCLK}}{10}$$

This means if MCLK = 1.024 MHz then the maximum baud rate is 102.4 kbaud.

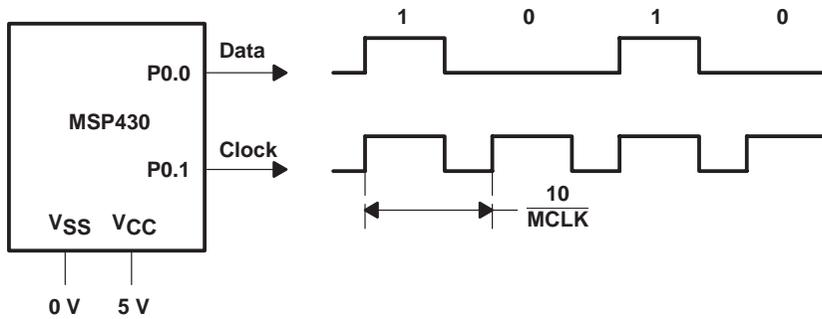


Figure 3–5. Connections for Fast Serial Transfer

## 3.2 Storage of Calibration Constants

Metering devices, such as electricity meters, gas meters etc., normally need to store calibration constants (offsets, slopes, limits, addresses, correction factors) for use during the measurements. Depending on the voltage supply (battery or ac), these calibration constants can be stored in the on-chip RAM or in an external EEPROM. Both methods are explained in the following sections.

### 3.2.1 External EPROM for Calibration Constants

The storage of calibration constants, energy values, meter numbers, and device versions in external EEPROMs may be necessary if the metering device is ac powered. This is because of the possibility of power failures.

The EEPROM is connected to the MSP430 by dedicated inputs and outputs. Three (or two) control lines are necessary for proper function:

- Data line SDA: an I/O port is needed for this bidirectional line. Data can be read from and written to the EEPROM on this line.
- Clock line SCL: any output line is sufficient for the clock line. This clock line can be used for other peripheral devices as long as no data is present on the data line during use.
- Supply line: if the current consumption of the idle EEPROM is too high, then switching of the EEPROM  $V_{CC}$  is needed. Three possible solutions are shown:
  - The EEPROM is connected to  $SV_{CC}$ . This is a very simple way to have the EEPROM powered off when not in use.
  - The EEPROM is switched on and off by an external PNP transistor driven by an output port.
  - The EEPROM is connected to 5 V permanently, when its power consumption is not a consideration.

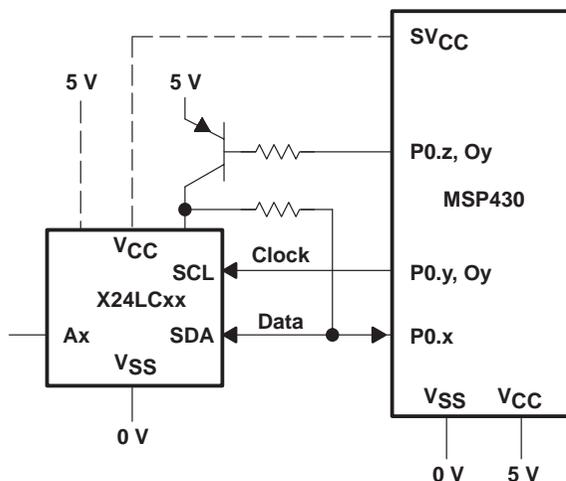


Figure 3–6. External EPROM Connections

An additional way to connect an EEPROM to the MSP430 is shown in Section 3.4, *I<sup>2</sup>C Bus Connection*, describing the I<sup>2</sup>C Bus.

**Note:**

The following example does not contain the necessary delay times between the setting and the resetting of the clock and the data bits. These delay times can be seen in the specifications of the EEPROM device. With a processor frequency of 1 MHz, each one of the control instructions needs 5  $\mu$ s.

*Example 3–5. External EEPROM Connections*

The EEPROM, with the dedicated I/O lines, is controlled with normal I/O instructions. The SCL line is driven by O17, the SDA line is driven by P0.6. The line is driven high by a resistor and low by the output buffer.

```

P0OUT    .EQU    011h           ; Port0 Output register
P0DIR    .EQU    012h           ; Port0 Direction register
SCL      .EQU    0F0h           ; O17 controls SCL, 039h LCD Address
SDA      .EQU    040h           ; P0.6 CONTROLS SDA
LCDM     .EQU    030h           ; LCD control byte
;
; INITIALIZE I2C BUS PORTS:
; INPUT DIRECTION:   BUS LINE GETS HIGH
; OUTPUT BUFFER LOW: PREPARATION FOR LOW SIGNALS
;

```

```

        BIC.B    #SDA,&P0DIR                ; SDA TO INPUT DIRECTION
        BIS.B    #SCL,&LCDM+9              ; SET CLOCK HI
        BIC.B    #SDA,&P0OUT              ; SDA LOW IF OUTPUT
        ...
;
; START CONDITION: SCL AND SDA ARE HIGH, SDA IS SET LOW,
; AFTERWARDS SCL GOES LO
;
        BIS.B    #SDA,&P0DIR                ; SET SDA LO (SDA GETS OUTPUT)
        BIC.B    #SCL,&LCDM+9              ; SET CLOCK LO
;
; DATA TRANSFER: OUTPUT OF A "1"
;
        BIC.B    #SDA,&P0DIR                ; SET SDA HI
        BIS.B    #SCL,&LCDM+9              ; SET CLOCK HI
        BIC.B    #SCL,&LCDM+9              ; SET CLOCK LO
;
; DATA TRANSFER: OUTPUT OF A "0"
;
        BIS.B    #SDA,&P0DIR                ; SET SDA LO
        BIS.B    #SCL,&LCDM+9              ; SET CLOCK HI
        BIC.B    #SCL,&LCDM+9              ; SET CLOCK LO
;
; STOP CONDITION: SDA IS LOW, SCL IS HI,    SDA IS SET HI
;
        BIC.B    #SDA,&P0DIR                ; SET SDA HI
        BIS.B    #SCL,&LCDM+9              ; Set SCL HI
;

```

The examples, shown in the previous text, for the different conditions can be implemented into a subroutine, which outputs the contents of a register. This shortens the necessary ROM code significantly. Instead of line Ox for the SCL line another I/O port P0.x can be used. See Section 3.4, *I<sup>2</sup>C Bus Connection*, for more details of such a subroutine.

### 3.2.2 Internal RAM for Calibration Constants

The internal RAM can be used for storage of the calibration constants, if a permanently connected battery is used for the power supply. The use of low power mode 3 or 4 is necessary for these kinds of applications and can get battery life times reaching 8 to 12 years.

### 3.3 M-Bus Connection

The MSP430 connection to the M-Bus (metering bus) is shown in Figure 3–7. Three supply modes are possible when used with the TSS721:

- Remote supply: The MSP430 is fully powered from the TSS721
- Remote supply/battery support: The MSP430 power is supplied normally from the TSS721. If this power source fails, a battery is used for backup power to the MSP430
- Battery Supply: The MSP430 is always supplied from a battery.

All these operating modes are described in detail in the *TSS721 M-Bus Transceiver Applications Book*.

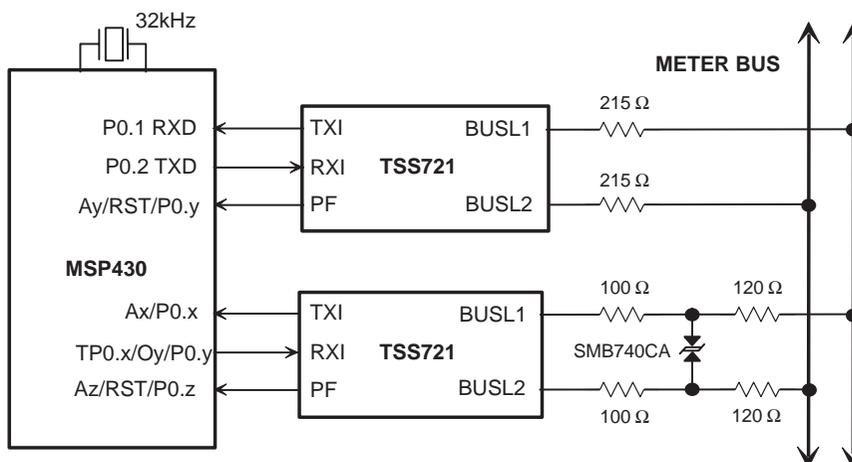


Figure 3–7. TSS721 Connections to the MSP430

Two different TSS721 connections are shown in Figure 3–7:

- If the 8-bit interval timer with its UART is used then the upper connection is necessary. TXI or TX are connected to RXD (P0.1) and RXI or RX is connected to TXD (P0.2).
- If a strictly software UART or an individual protocol is used, then any input and output combination can be used

The second connection uses a proven hardware for environments with strong EMV conditions. The 40-V suppressor diode gives the best results with this configuration.

For more details, see Section 3.8, *Power Supplies for MSP430 Systems*.

### 3.4 I<sup>2</sup>C Bus Connection

If more than one device is to be connected to the I<sup>2</sup>C-Bus, then two I/O ports are needed for the control of the I<sup>2</sup>C peripherals. This is needed to switch SDA and SCL to a high-impedance state.

Figure 3–8 shows the connection of three I<sup>2</sup>C peripherals to the MSP430:

- An EEPROM with 128x8-bit data
- An EEPROM with 2048x8-bit data
- An 8-bit DAC/ADC

The bus lines are driven high by the R<sub>p</sub> resistors (P0.x is switched to input direction) and low by the output ports itself (P0.x is switched to output direction).

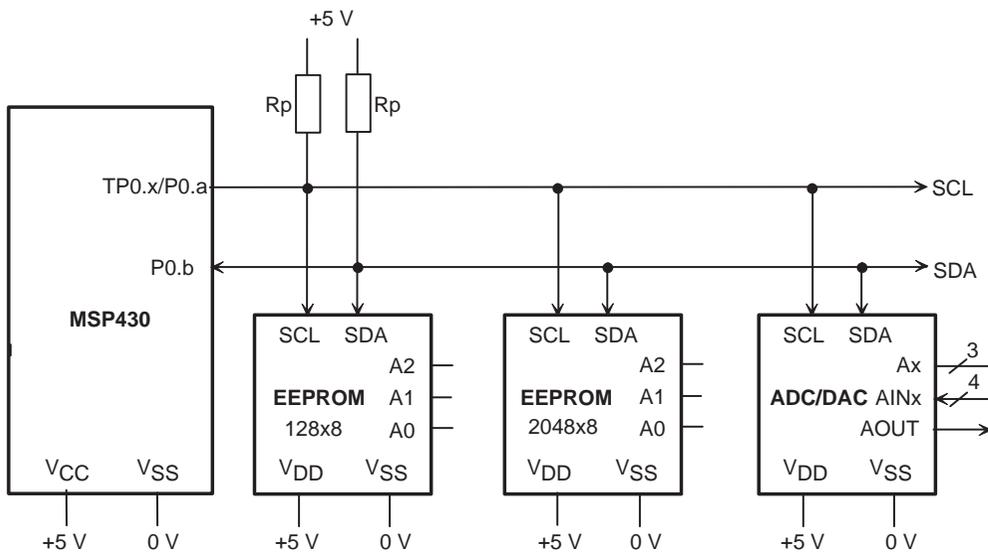


Figure 3–8. I<sup>2</sup>C Bus Connections

The following software example shows a complete I<sup>2</sup>C handler. It is designed for an EEPROM 24C65 with the following values:

- MCLK Frequency: 3.8 MHz
- Address Length: 13 bits
- Device Code: selectable by Code definition

```

; I2C-Handler: Transmission of 8-bit data via the I2C-bus
; Author: Christian Hernitscheck TID
;
; Definitions for I2C Bus
    
```

```

;
SCL      .EQU      040h          ; P0.6 controls SCL line (pull-up)
SDA      .EQU      080h          ; P0.7 controls SDA line (pull-up)
SCLIN    .EQU      010h          ; P0 input register P0IN
SDAIN    .EQU      010h          ; P0 input register P0IN
SCLDAT   .EQU      011h          ; P0OUT register address
SDADAT   .EQU      011h          ; P0 output direction register P0DIR
SCLEN    .EQU      012h          ; P0DIR register address
SDAEN    .EQU      012h          ; P0 direction register
Code     .equ       0A0h          ; Device Code 10 (24C65)
;
Address  .EQU      0200h          ; address pointer for EEPROM
I2CData  .EQU      0202h          ; used for I2C protocol
;
; Register definitions
;
Data     .EQU      R5
Count    .EQU      R6
Mask     .EQU      R7
;
; Initialization in main program
;
        BIC.B      #SCL+SDA,&SDAEN      ; SCL and SDA to input direction
        BIC.B      #SCL+SDA,&SDADAT     ; SCL and SDA output buffer lo
        ...                ; Continue
;
; Subroutines of the I2C-Handler
;
; Write 8-bit data <data> into EEPROM address <address>:
;
; Call   MOV      <address>,Address      ; EEPROM data address
;        MOV.B    <data>,I2CData        ; 8-bit data
;        CALL    #I2C_Write             ; Call subroutine
;        JC      Error                  ; Acknowledge error
;        JN      Error                  ; Arbitration error
;        ...                ; Continue program

```

```

;
; Read 8-bit data from EEPROM address <address>:
;
;     MOV     <address>,Address      ; EEPROM data address
;     CALL   #I2C_Read              ; Call subroutine
;     JNC    Error                  ; Acknowledge error
;     JN     Error                  ; Arbitration error
;     ...                               ; Data in I2CData (byte)
;
; Status Bits on return:
;
; C: Acknowledge Bit
; N: 1: Arbitration Error          0: no error
;
; Used Registers: R5 = Data (pushed onto Stack)
;                               R6 = Count (pushed onto Stack)
;                               R7 = Mask (pushed onto Stack)
;
; Used RAM:
;                               Address      0200h
;                               I2CData     0202h
;                               I2CData+1   0203h
;                               I2CData+2   0204h
;                               I2CData+3   0205h
;                               I2CData+4   0206h
;
;
I2C_Write    MOV.B   I2CData,I2CData+3 ; Data to be written to EEPROM
             CALL   #ControlByte      ; Control byte
             MOV.B  Address+1,I2CData+1 ; Hi byte of EEPROM address
             AND.B  #01Fh,I2CData+1   ; Delete A2, A1 and A0 bits
             MOV.B  Address,I2CData+2  ; Lo byte of EEPROM address
             JMP    I2C                ; To common part
;
I2C_Read    CALL   #ControlByte      ; I2CData = Control byte
             MOV.B  Address+1,I2CData+1 ; Hi byte of EEPROM address
             AND.B  #01Fh,I2CData+1   ; Delete A2, A1 and A0 bits

```

```

        MOV.B    Address,I2CData+2        ; Lo byte of EEPROM address
        MOV.B    I2CData,I2CData+4      ; Control byte 2
        BIS.B    #01h,I2CData+4        , To common part
;
; Common I2C-Handler
;
I2C    PUSH     Count                    ; Save registers
        PUSH     Data
        PUSH     Mask
        CLR      Count
        BIS.B    #SDA,&SDAEN            ; Start Condition: set SDA Lo
        MOV.B    I2CData,Data           ; Send slave address and RW bit
        CALL    #I2C_Send
        JC      I2C_Stop
;
;                               Write or Read?
        BIT.B    #01h,I2CData+4        ; _
        JC      I2C_SubRead             ; R/W bit is 1: read
;
;                               _
; Write data (R/W = 0)
;
I2C_Data INC     Count
        CMP      #4,Count
        JEQ     I2C_Stop
        CALL    #I2C_Send
        JNC     I2C_Data
;
;                               ; Stop Condition:
I2C_Stop BIS.B    #SCL,&SCLLEN          ; SCL = 'L'
        BIS.B    #SDA,&SDAEN          ; SDA = 'L'
        NOP     ; Delay 7 cycles
        NOP
        NOP
        NOP
        NOP
        NOP
        NOP
        BIC.B    #SCL,&SCLLEN          ; SCL = 'H'

```

```

        CALL    #NOP9                ; Delay 9 cycles
        BIC.B   #SDA,&SDAEN          ; SDA = 'H'
        CLRN                    ; Reset error flags
;
I2C_End POP    Mask                ; Restore registers
        POP    Data
        POP    Count
        RET                    ; Carry info valid
;
; Read data (R/W = 1)
;
I2C_SubRead INC    Count
        CMP    #3,Count
        JEQ   I2C_SubRead1
        CALL  #I2C_Send
        JC   I2C_Stop
        JMP  I2C_SubRead
I2C_SubRead1 BIS.B  #SCL,&SCLEN      ; SCL='L'
        CALL  #NOP9
        BIC.B #SCL,&SCLEN          ; SCL='H'
        NOP
        NOP
        NOP
        NOP
        NOP                    ; Start condition:
        BIS.B #SDA,&SDAEN          ; SCL='H', SDA='H' => 'L'
        MOV.B I2CData+4,Data
        CALL  #I2C_Send            ; Send Control Byte
        JC   I2C_Stop
        BIS.B #SCL,&SCLEN          ; SCL = 'L'
        BIC.B #SDA,SDAEN          ; SDA = Input
        CLR  I2CData
        MOV  #8,Count              ; Read 8 bits
;
I2C_Read1        BIC.B  #SCL,&SCLEN ; SCL = 'H'
                BIT.B   #SDA,&SDAIN ; Read data to carry

```

```

        RLC.B    I2CData                ; Store received Bit
        NOP
        NOP
        BIS.B    #SCL,&SCLLEN           ; SCL = 'L'
        NOP
        NOP
        NOP
        NOP
        NOP
        NOP
        DEC     Count
        JNZ     I2C_Read1
;
        CALL    #I2C_Ackn               ; Test acknowledge bit to C
        JMP     I2C_Stop
;
; Send byte
;
I2C_Send MOV.B    #80h,Mask            ; Bit mask: MSB first
;
I2C_Send1     BIT.B    Mask,I2CData(Count) ; Info bit -> Carry
        JC     I2C_Send2
        BIS.B    #SCL,&SCLLEN           ; Info is 0: SCL = 'L'
        BIS.B    #SDA,&SDAEN           ; SDA = 'L'
        CALL    #NOP9
        BIC.B    #SCL,&SCLLEN           ; SCL = 'H'
        JMP     I2C_Send3
I2C_Send2     BIS.B    #SCL,&SCLLEN     ; Info is 1: SCL = 'L'
        BIC.B    #SDA,&SDAEN           ; SDA = 'H'
        CALL    #NOP9
        BIC.B    #SCL,&SCLLEN           ; SCL = 'H'
        BIT.B    #SDA,SDAIN           ; Arbitration
        JNC     Error_Arbit
;
I2C_Send3     CLRC
        RRC.B    Mask                ; Next address bit

```

```

        NOP
        NOP
        NOP
        JNC      I2C_Send1          ; No Carry: continue
;
I2C_Ackn NOP
        NOP
        BIS.B   #SCL,&SCLEN        ; SCL = 'L' Acknowledge Bit
        BIC.B   #SDA,&SDAEN       ; SDA = 'H'
        CALL    #NOP8
        BIC.B   #SCL,&SCLEN        ; SCL = 'H'
        BIT.B   #SDA,&SDAIN       ; Read data to carry
        RET     ; (acknowledge bit)
;
; I2C-Bus Error
Error_Arbit ADD #2,SP            ; Remove return address
        SETN   ; Set arbitration error
        JMP    I2C_End
;
; Build control byte
;
ControlByte CLR I2CData
        MOV.B  Address+1,I2CData  ; Hi byte of EEPROM address
        RRC   I2CData            ; Shift MSBs to bits 3..1
        RRC   I2CData
        RRC   I2CData
        RRC   I2CData
        AND.B  #0Eh,I2CData       ; A2, A1 and A0
        ADD.B  #Code,I2CData      ; Add device code (24C65)
        RET
;
; Delay subroutine. Slows down I2C Bus speed to spec
;
NOP9    NOP                      ; 9 cycles delay
NOP8    RET                       ; 8 cycles delay
```

## 3.5 Hardware Optimization

The MSP430 permits the use of unused analog inputs (A7 to A0) and segment lines (S29 to S2) for inputs and outputs, respectively. The following two sections explain in detail how to program and use these inputs and outputs.

### 3.5.1 Use of Unused Analog Inputs

Unused analog-to-digital converter (ADC) inputs can be used as digital inputs or, with some restrictions, as digital outputs.

#### 3.5.1.1 Analog Inputs Used for Digital Inputs

Any ADC input A7 to A0 can be used as a digital input. It only needs to be programmed (for example, during the initialization) for this function. Three things are important if this feature is used:

- Any activity at these digital inputs has to be stopped during ongoing sensitive ADC measurements. This activity will cause noise, which invalidates the ADC results. Activity in this case means:
  - No change of the AEN register (switching between digital and analog mode)
  - No input change at the digital ADC inputs (this rarely allows changing signals at these inputs).
- All bits that are switched to ADC inputs will read zero when read. Therefore, it is not necessary to clear them with software after reading.
- Not all analog inputs are implemented in a given device

#### Example 3–6. A0 – A4 are used as ADC Inputs and A5 – A7 as Digital Inputs

```
AIN      .EQU    0110h          ; Address DIGITAL INPUT REGISTER
AEN      .EQU    0112h          ; Address DIGITAL INPUT ENABLE REG.
A7EN     .EQU    080h           ; Bits in Dig. Input Enable Reg.:
A6EN     .EQU    040h           ; 0: ADC      1: Digital Input
A5EN     .EQU    020h           ;
; INITIALIZATION: A7 TO A5 ARE SWITCHED TO DIGITAL INPUTS
; A4 TO A0 ARE USED AS ANALOG INPUTS
;
      MOV      #A7EN+A6EN+A5EN,&AEN      ; A7 TO A5 DIGITAL MODE
      ...
;
```

```
; NORMAL PROGRAM EXECUTION:
; CHECK IF A7 OR A5 ARE HIGH. IF YES: JUMP TO LABEL L$100
;
    BIT      #A7EN+A5EN,&AIN          ; A7 .OR. A5 HI?
    JNZ     L$100                    ; YES
    . . .                            ; NO, CONTINUE
;
; CHECK IF ALL DIG. INPUTS A7 TO A5 ARE LOW. IF YES: Go to L$200
;
    TST     &AIN                     ; A7 TO A5 LO?
    JZ      L$200                    ; YES, (ANALOG INPUTS READ ZERO)
```

### 3.5.1.2 Analog Inputs Used as Digital Outputs

If outputs are needed then the unused ADC inputs with the current source connection can be used with the following restrictions:

- Only one ADC input can be high at a given time (1 out of n principle)
- Only the ADC inputs A0 to A3 are usable (only they are connected to the current source)
- The outputs can go high only while the ADC is not using the current source.
- The output current is directly related to the supply voltage,  $V_{CC}$ .
- The output voltage is only about 50% of the supply voltage,  $V_{CC}$ . Logic levels have to be carefully monitored. A transistor stage might be necessary (if not there already, e.g. for a relay).
- The output current is the current of the current source. Again, logic levels have to be carefully monitored. The pull-down resistor has to be big enough to allow the maximum output level.

The example in Figure 3–9 shows the ADC using inputs A0 and A1 as digital outputs driving two stages; a transistor stage (energy pulse, e.g. with an electricity meter) and a 3.3-V gate (3.3 V ensures that the input levels are sufficient).

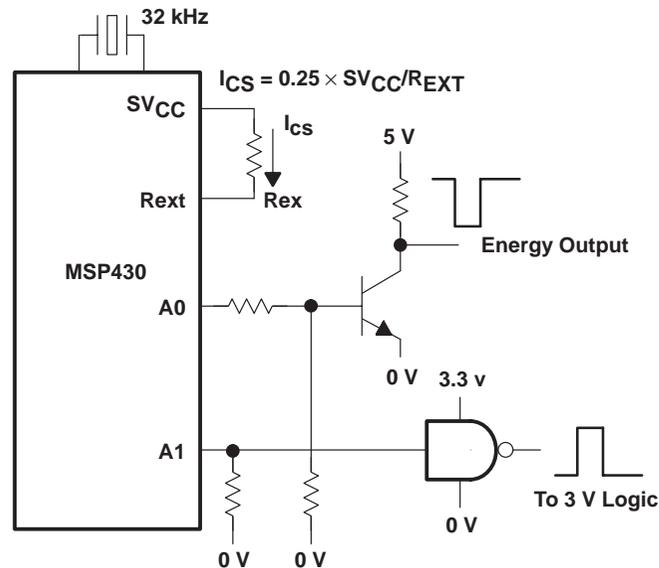


Figure 3–9. Unused ADC Inputs Used as Outputs

### Example 3–7. Controlling Two Inputs as Outputs

To control the two outputs shown in Figure 3–9, the following software program is necessary:

```

ACTL      .EQU      0114h                ; ADC CONTROL REGISTER ACTL
VREF      .EQU      02h                  ; 0: Ext. Reference    1: SVCC ON
A0        .EQU      0000h                ; AD INPUT SELECT A0
A1        .EQU      0004h                ;                                     A1
CSA0      .EQU      0000h                ; CURRENT SOURCE TO A0
CSA1      .EQU      0040h                ;                                     A1
CSOFF     .EQU      0100h                ; CURRENT SOURCE OFF BIT
;
; SET A0 HI FOR 3ms: SELECT A0 FOR CURRENT SOURCE AND INPUT
MOV        #VREF+A0+CSA0,&ACTL          ; PD = 0, SVCC = on
CALL       #WAIT3MS                      ; WAIT 3ms
BIS        #CSOFF,&ACTL                  ; CURRENT SOURCE OFF;
;
; SET A1 HI FOR 3ms: SELECT A1 FOR CURRENT SOURCE AND INPUT
MOV        #VREF+A1+CSA1,&ACTL          ; PD = 0, SVCC = on
CALL       #WAIT3MS                      ; WAIT 3ms

```

BIS

#CSOFF, &amp;ACTL

; CURRENT SOURCE OFF

### 3.5.2 Use of Unused Segment Lines for Digital Outputs

The LCD driver of the MSP430 provides additional digital outputs, if the segment lines are not used. Up to 28 digital outputs are possible by the hardware design, but not all of them will be implemented on a given chip. The addressing scheme for the digital outputs O2 to O29 is as illustrated in Table 3–4.

Table 3–4 shows the dependence of the segment/output lines on the 3-bit value LCDP. When LCDP = 7, all the lines are switched to LCD Mode (segment lines). Only groups of four segment lines can be switched to digital output mode. LCDP is set to zero by the PUC (O6 to O29 are in use).

**Note:**

Table 3–4 shows the digit environment for a 4-MUX LCD display. The outputs O0 and O1 are not available: S0 and S1 are always implemented as LCD outputs. (digit 1).

The digital outputs Ox have to be addressed with all four bits. This means that 0h and 0Fh are to be used for the control of one output.

Only byte addressing is allowed for the addressing of the LCD controller bytes. Except for S0 and S1, the PUC switches the LCD outputs to the digital output mode (LCDP = 0).

Table 3–4. LCD and Output Configuration

Address	7	6	5	4	3	2	1	0	Digit Nr.	LCDP
03Fh		O29			O28				Digit 15	6 to 0
03Eh		O27			O26				Digit 14	6 to 0
03Dh		O25			O24				Digit 13	5 to 0
03Ch		O23			O22				Digit 12	5 to 0
03Bh		O21			O20				Digit 11	4 to 0 S20/S21
03Ah		O19			O18				Digit 10	4 to 0
039h		O17			O16				Digit 9	3 to 0
038h		O15			O14				Digit 8	3 to 0
037h		O13			O12				Digit 7	2 to 0
036h		O11			O10				Digit 6	2 to 0 S10/S11
035h		O09			O08				Digit 5	1 to 0
034h		O07			O06				Digit 4	1 to 0
033h		O05			O04				Digit 3	0
032h		O03			O02				Digit 2	0
031h	h	g	f	e	d	c	b	a	Digit 1	S0/S1

**Example 3–8. S0 to S13 Drive a 4-MUX LCD**

S0 to S13 drive a 4-MUX LCD (7 digits). O14 to O17 are set as digital outputs.

```

; LCD Driver definitions:
;
LCDM    .EQU    030h           ; ADDRESS LCD CONTROL BYTE
LCDM0   .EQU    001h           ; 0: LCD off      1: LCD on
LCDM1   .EQU    002h           ; 0: high        1: low Impedance
MUX     .EQU    004h           ; MUX: static, 2MUX, 3MUX, 4MUX
LCDP    .EQU    020h           ; Segment/Output Definition LCDM7/6/5
O14     .EQU    00Fh           ; O14 Control Definition
O15     .EQU    0F0h           ; O15
O16     .EQU    00Fh           ; O16
O17     .EQU    0F0h           ; O17
;
; INITIALIZATION: DISPLAY ON:      LCDM0 = 1
;                                 HI IMPEDANCE      LCDM1 = 0
;                                 4MUX:              LCDM4/3/2 = 7
;                                 O14 TO O17 ARE OUTPUTS:      LCDM7/6/5 = 3
;
MOV.B   #(LCDP*3)+(MUX*7)+LCDM0,&LCDM      ; INIT LCD
...
;
; NORMAL PROGRAM EXECUTION:
; SOME EXAMPLES HOW TO MODIFY THE DIGITAL OUTPUTS O14 TO O17:
;
BIS.B   #O14,&LCDM+8              ; SET O14, O15 UNCHANGED
BIC.B   #O15+O14,&LCDM+8          ; RESET O14 AND O15
MOV.B   #O15+O14,&LCDM+8          ; SET O14 AND O15
MOV.B   #O17,&LCDM+9              ; RESET O16, SET O17
XOR.B   #O17,&LCDM+9              ; TOGGLE O17, O16 STAYS UNCHANGED

```

## 3.6 Digital-to-Analog Converters

The MSP430 does not contain a digital-to-analog converter (DAC) on-chip, but it is relatively simple to implement the DAC function. Five different solutions with distinct hardware and software requirements are shown in the following:

- The R/2R method
- The weighted-resistors method
- Integrated DACs connected to the I<sup>2</sup>C Bus
- Pulse width modulation (PWM) with the universal timer/port module
- Pulse width modulation with Timer A

### 3.6.1 R/2R Method

With a CMOS shift register or digital outputs, a DAC can be built for any bit length. The outputs Q<sub>x</sub> of the shift register switch the 2R-resistors to 0 V or V<sub>CC</sub> according to the digital input. The voltage at the non-inverting input and also at the output voltage V<sub>out</sub> of the operational amplifier is:

$$V_{\text{out}} = \frac{k}{2^n} \times V_{\text{CC}}$$

Where:

- k      Value of the digital input word with n bits length
- n      Number of Q outputs, maximum length of input word
- V<sub>CC</sub>    Supply voltage

Signed output is possible by level shifting or by splitting of the power supply (+V<sub>CC</sub>/2 and -V<sub>CC</sub>/2). With split power supplies the voltage at the output of the operational amplifier is:

$$V_{\text{out}} = \frac{k}{2^n} \times V_{\text{CC}} - \frac{V_{\text{CC}}}{2} = V_{\text{CC}} \left( \frac{k}{2^n} - \frac{1}{2} \right)$$

Advantages of the R/2R Method

- Only two different resistors are necessary (R and 2R)
- Absolute monotony over the complete output range
- Internal impedance independent of the digital value: impedance is always R
- Expandable to any bit length by the adding of shift registers
- With only three digital outputs (O<sub>x</sub>, TP0.x, Portx), an inexpensive solution is possible.

If enough digital outputs are available in an application, then the shift register(s) can be omitted. The outputs QA to QH of Figure 3–10 are substituted by O outputs, ports or TP outputs of the MSP430.

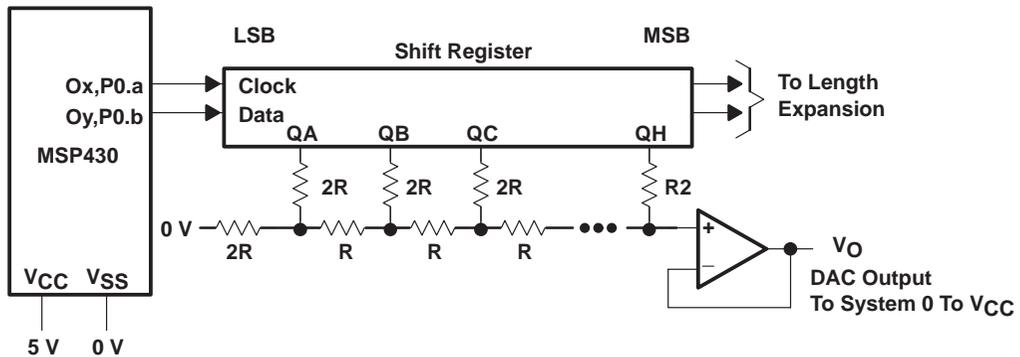


Figure 3–10. R/2R Method for Digital-to-Analog Conversion

### 3.6.2 Weighted Resistors Method

The simplest digital-to-analog conversion method, only  $(n+3)$  resistors and an operational amplifier are required for an  $n$ -bit DAC. This method is used when the DAC performance can be low.

The example shown in Figure 3–11 delivers  $2^{n+1}$  different output voltage steps. They can be seen as signed if the voltage  $V_{CC}/2$  is seen as a zero point. The output voltage  $V_{out}$  of this DAC is:

$$V_{out} = V_{ninv} - \sum I_n \times R = \frac{V_{CC}}{2} \times \left( 1 + \left( a \times 2^{-1} + b \times 2^{-2} + c \times 2^{-3} \dots + x \times 2^{-(n+1)} \right) \right)$$

Where:

- $V_{out}$  Output voltage of the DAC
- $V_{ninv}$  Voltage at the noninverting input of the operational amplifier ( $V_{CC}/2$ )
- $V_{CC}$  Supply voltage of the MSP430 and periphery
- $R$  Normalized resistor used with the DAC
- $a\dots x$  Multiplication factors for the weighted resistors  $R$  to  $2^n \times R$ :
  - +1 if port is switched to  $V_{SS}$
  - 0 if port is switched to input direction (high impedance)
  - 1 if port is switched to  $V_{CC}$

Normally all of the ports are switched to the same potential ( $V_{SS}$  or  $V_{CC}$ ) or are disabled. This allows signed output voltages referenced to  $V_{CC}/2$ .

- Advantage of the Weighted Resistor-Method: Simplicity
- Disadvantage: Monotony not possible due to resistor tolerances

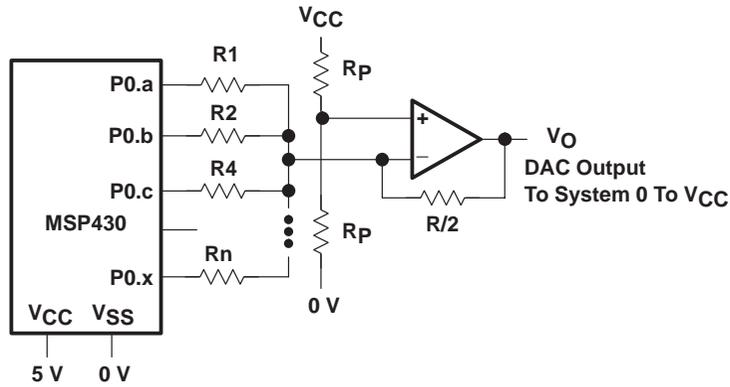


Figure 3–11. Weighted Resistors Method for Digital-to-Analog Conversion

### 3.6.3 Digital-to-Analog Converters Connected Via the I<sup>2</sup>C Bus

Figure 3–12 shows two different DACs that are connected to the MSP430 via the I<sup>2</sup>C Bus:

- A single output 8-bit DAC (with additional 4 ADC inputs); one analog output, AOUT, is provided.
- An octuple 6-bit DAC; eight analog outputs, DAC0 to DAC7, are available for the system

The generic software program to handle these devices is contained in the Section 3.4, *I<sup>2</sup>C Bus Connection*, explaining the I<sup>2</sup>C-Bus.

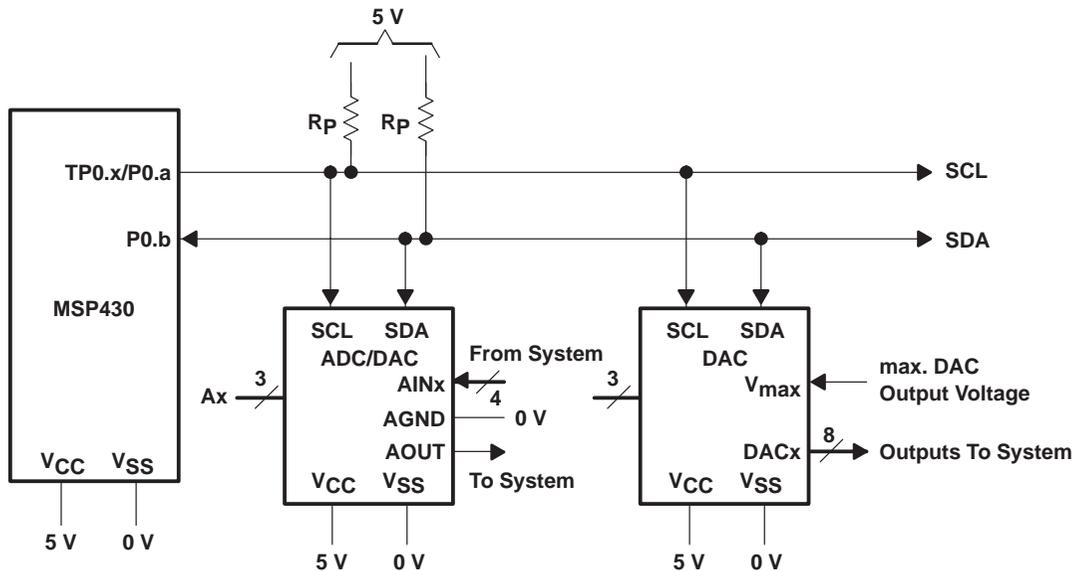


Figure 3–12. *I<sup>2</sup>C-Bus for Digital-to-Analog Converter Connection*

### 3.6.4 PWM DAC With the Universal Timer/Port Module

The two timers contained in the universal timer/port module can be used for one or two independent PWM generators. The ACLK frequency is used for the timing of these PWMs. The basic timer determines the period of the PWM signals. Its interrupt handler sets the programmed outputs and loads the two timer registers TPCNT2 and TPCNT1 with the negated pulse length values (see Table 3–5). The universal timer/port module terminates the pulses. Its interrupt handler resets the outputs when the counters, TPCNTx, overflow from 0FFh to 00h. The length of one step is always 1/ACLK, which is 30.51758  $\mu$ s if a 32.768 kHz crystal is used.

Table 3–5 shows the necessary basic timer frequency, which is dependent on the PWM resolution used.

Table 3–5. *Resolution of the PWM-DAC*

Resolution Bits	Resolution Steps	Basic Timer Frequency
8	256	128
7	128	256
6	64	512
5	32	1024

Table 3–6 shows the values to be written into timer register TPCNT1 or TPCNT2 to get a certain PWM output value (related to  $V_{CC}$ ); it is the desired value subtracted from the resolution value. The PWM switch (a byte in RAM) determines if the output is enabled (1) or disabled (0).

Table 3–6. Register Values for the PWM-DAC

PWM Output (Relative to $V_{CC}$ )	TPCNTx Value 256 Steps	TPCNTx Value 128 Steps	TPCNTx Value 64 Steps	TPCNTx Value 32 Steps	PWM Switch
0	x	x	x	x	0
0.25	C0h	E0h	F0h	F8h	1
0.50	80h	C0h	E0h	F0h	1
0.75	40h	A0h	D0h	E8h	1
1.00	00h	80h	C0h	E0h	1

**Note:**

The interrupt latency time plays an important role for this kind of PWM generation. Real time programming is necessary. Therefore, the first instruction of each interrupt handler must be the EINT instruction.

Example 3–9. PWM DAC With Timer/Port Module

Two PWM outputs with 8-bit resolution are realized. To get the highest speed, TP0.2 and TP0.1 are used as outputs (they have the same bit addresses as the flags RC2FG and RC1FG). The schematic is shown in Figure 3–13. The output ripple is shown in an exaggerated manner. If the PWM information is needed (as for DMC) then the signal at TP0.x is used directly.

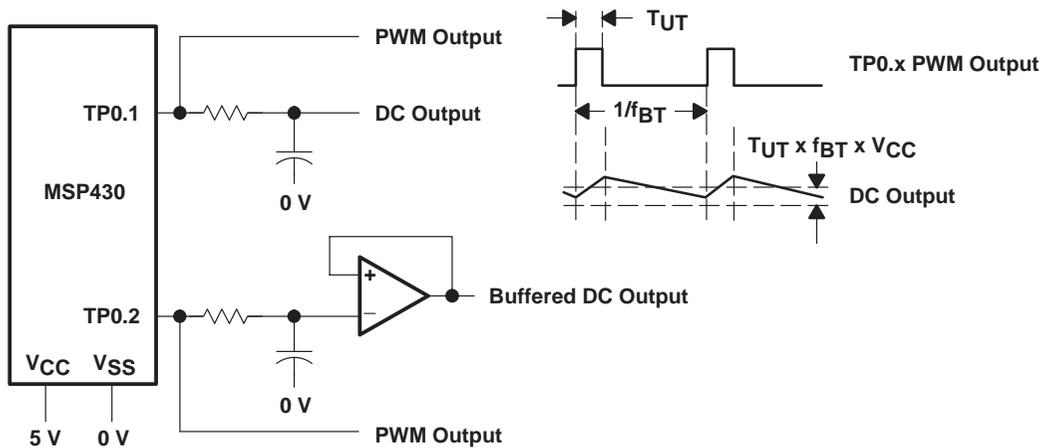


Figure 3–13. PWM for the DAC

Figure 3–14 illustrates the counting of the 8-bit counter during the PWM generation. The interrupt handler of the basic timer sets the 8-bit counter to a negative number of counts ( $-n1$ ) and sets the output to high; the interrupt handler of the universal timer/port resets the output to zero when it overflows.

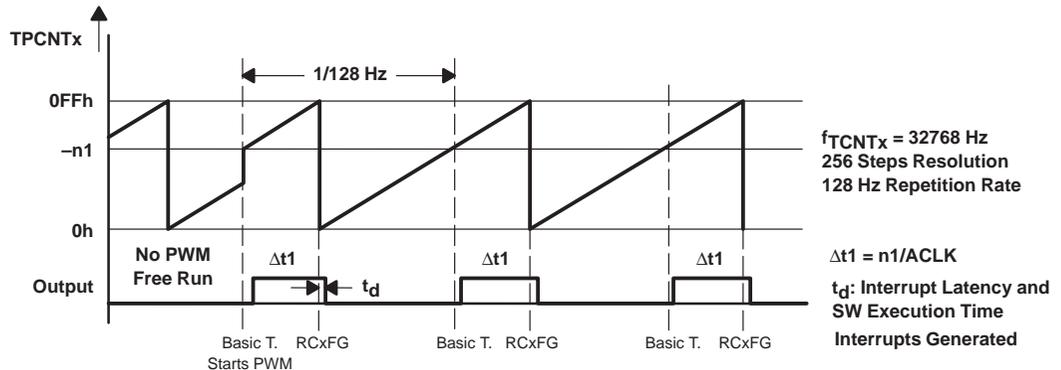


Figure 3–14. PWM Timing by the Universal Timer/Port Module and Basic Timer

```
; MSP430 Software for 8 bit PWM with Universal/Timer Port
```

```
; Definitions of the MSP430 hardware
```

```
;
```

```
Type .equ 310 ; 310: MSP43C31x 0: others
```

```
BTCTL .equ 040h ; Basic Timer: Control Reg.
```

```
BTCNT1 .equ 046h ; Counter
```

```
BTCNT2 .equ 047h ; Counter
```

```
BTIE .equ 080h ; : Intrpt Enable
```

```
SSEL .equ 080h ;
```

```
DIV .equ 020h ; BTCTL: xCLK/256
```

```
IP2 .equ 004h ; BTCTL: Clock Divider2
```

```
IP1 .equ 002h ;
```

```
IP0 .equ 001h ; Clock Divider0
```

```
;
```

```
SCFQCTL .equ 052h ; FLL Control Register
```

```
MOD .equ 080h ; Modulation Bit: 1 = off
```

```
;
```

```
CPUoff .equ 010h ; SR: CPU off bit
```

```
GIE .equ 008h ; SR: General Intrpt enable
```

```
;
```

```

TPCTL    .equ    04Bh           ; Timer Port:      Control Reg.
TPCNT1   .equ    04Ch           ;                  Counter Reg.Lo
TPCNT2   .equ    04Dh           ;                  Counter Reg.Hi
TPD      .equ    04Eh           ;                  Data Reg.
TPE      .equ    04Fh           ;                  Enable Reg.
TP1      .equ    002h           ; Bit address     TP0.1
TP2      .equ    004h           ;                  TP0.2
TP3      .equ    008h           ;                  TP0.3
TP4      .equ    010h           ;                  TP0.4
TP5      .equ    020h           ;                  TP0.5
;
        .if    Type=310         ; MSP430C31x?
TPIE     .equ    004h           ; ADC: Intrpt Enable Bit
        .else
TPIE     .equ    008h           ; MSP430C32x configuration
        .endif
IE2      .equ    001h           ; Intrpt Enable Byte
TPSSEL3  .equ    080h           ;
TPSSEL2  .equ    040h           ;
TPSSEL1  .equ    080h           ; Selects clock input (TPCTL)
TPSSEL0  .equ    040h           ;
ENB      .equ    020h           ; Selects clock gate (TPCTL)
ENA      .equ    010h           ;
EN1      .equ    008h           ; Gate for TPCNTx   (TPCTL)
RC2FG    .equ    004h           ; Carry of HI counter (TPCTL)
RC1FG    .equ    002h           ; Carry of LO counter (TPCTL)
EN1FG    .equ    001h           ; End of Conversion Flag "
B16      .equ    080h           ; Use 16-bit counter (TPD)
; RAM Definitions
;
SW_PWM   .equ    0200h          ; Enable bits for TP0.2 and TP0.1
TIM_PWM1 .equ    0201h          ; Calc. PWM result PWM1
TIM_PWM2 .equ    0202h          ; Calc. PWM result PWM2
;
;=====
;

```

```

.sect      "INIT",0F000h          ; Initialization Section
;
INIT      MOV      #0300h,SP      ; Initialize Stack Pointer
          MOV.B    #IP2+IP1+IP0,&BTCTL ; Basic Timer 128Hz
;
          MOV.B    #TPSSEL0+ENA,&TPCTL ; ACLK, EN1=1, TPCNT1
          CLR.B    &TPCNT1        ; Clear PWM regs
          CLR.B    &TPCNT2
          CLR.B    &TPD           ; Output Data = Low
          MOV.B    #TPSSEL2+TP2+TP1,&TPE ; TPCNT2: ACLK
          BIS.B    #TPIE+BTIE,&IE2  ; INTRPTS on
          CLR.B    SW_PWM         ; No PWM output
          BIC.B    #RC2FG+RC1FG,&TPCTL ; Reset flags
          EINT
          ...                    ; Continue with SW
;
; Start both PWMs: calculation results in R6 and R5
;
          MOV.B    R6,TIM_PWM1    ; (256 - result1)
          MOV.B    R5,TIM_PWM2    ; (256 - result2)
          BIS.B    #TP2+TP1,SW_PWM ; Enable PWM2 and PWM1
          ...                    ; Continue
;
; Disable PWM2: Output zero
;
          BIC.B    #TP2,SW_PWM    ; Disable PWM2
          ...
;
; Interrupt Handler for the Basic Timer Interrupt: 128Hz
;
BT_INT    BIC.B    #RC2FG+RC1FG,&TPCTL ; Clear flags
          MOV.B    TIM_PWM2,&TPCNT2 ; (256 - time2)
          MOV.B    TIM_PWM1,&TPCNT1 ; (256 - time1)
          BIS.B    SW_PWM,&TPD     ; Switch on enabled PWMs
          RETI
;

```

```

; End of Basic Timer Handler
;-----
; Interrupt Handler for the Universal Timer/Port Module
; For max. speed TP0.2 and TP0.1 are used (same bit locations
; as RC2FG and RC1FG). If other locations are used, RLA
; instructions have to be inserted after the flag clearing
;
UT_HNDL PUSH.B    &TPCTL                ; INTRPT from where?
            AND    #RC2FG+RC1FG,0(SP)    ; Isolate flags
            BIC.B  @SP,&TPCTL            ; Clear set flag(s)
            BIC.B  @SP+,&TPD             ; Reset actual I/O(s)
            RETI
;
; End of Universal Timer/Port Module Handler
;-----
;
        .sect    "INT_VECT",0FFE2h
        .WORD    BT_INT                  ; Basic Timer Vector
        .if      Type=310
        .sect    "INT_VEC1",0FFEAh      ; MSP430C31x
        .else
        .sect    "INT_VEC1",0FFE8h      ; Others
        .endif
        .WORD    UT_HNDL                 ; UTP Vector (31x)
        .sect    "INT_VEC2",0FFFEh
        .WORD    INIT                    ; Reset Vector

```

### Example 3–10. PWM Outputs With 7-Bit Resolution

Two PWM outputs with 7-bit resolution are realized. TP0.4 and TP0.3 are used as PWM outputs (this makes shifting necessary). The schematic is shown in Figure 3–15. Due to the inverting filters at the PWM outputs, the outputs of the MSP430 are also inverted to compensate for this. The output ripple is shown

in an exaggerated manner. If the PWM information is needed (as for DMC) then the signal at TP0.x can be used directly.

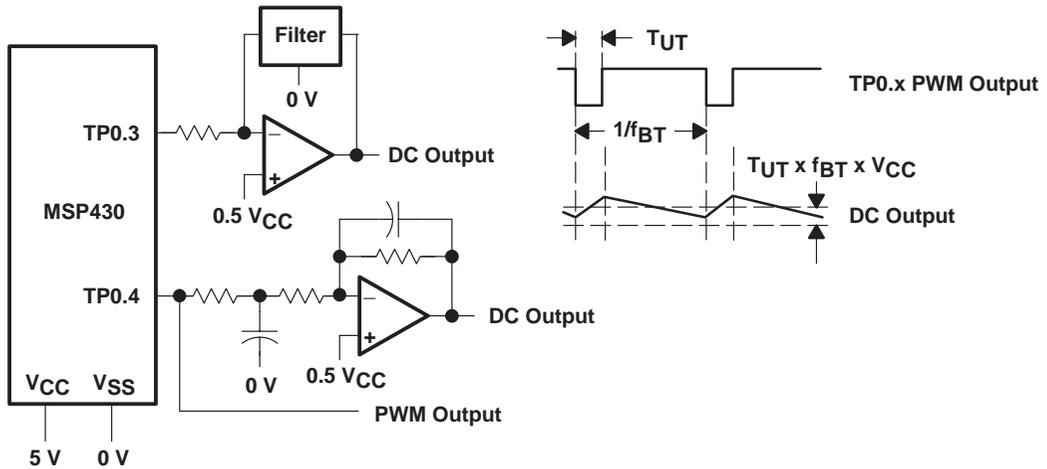


Figure 3–15. PWM for DAC

Figure 3–16 illustrates the operation of the 8-bit counter during the PWM generation. The interrupt handler of the basic timer sets the 8-bit counter to the negative number of counts ( $-n1$ ) and resets the output to low; the interrupt handler of the universal timer/port sets the output to high when it overflows.

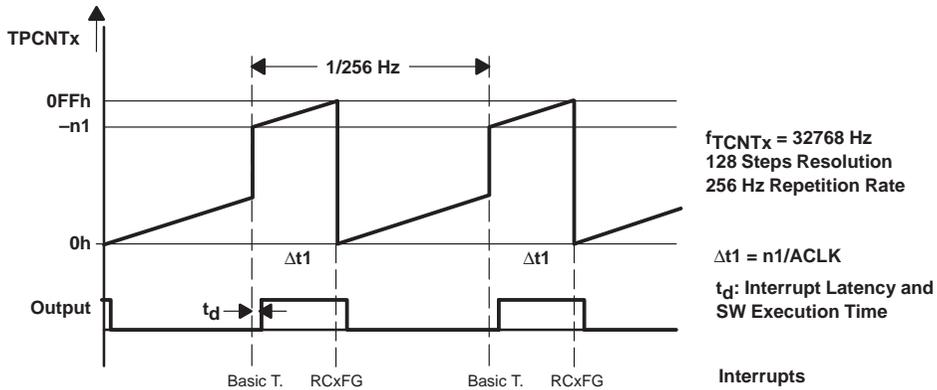


Figure 3–16. PWM Timing by Universal Timer/Port Module and Basic Timer

; MSP430 Software for 7 bit PWM with Universal/Timer Port

; Definitions of the MSP430 hardware like above

;

```
.sect "INIT",0F000h ; Initialization Section
```

;

```
INIT MOV #0300h,SP ; Initialize SP
```

```
MOV.B #IP2+IP1,&BTCTL ; Basic Timer 256Hz
```

;

```
MOV.B #TPSSEL0+ENA,&TPCTL ; ACLK, EN1=1, TPCNT1
```

```
CLR.B &TPCNT1 ; Clear PWM regs
```

```
CLR.B &TPCNT2
```

```
BIS.B #TP4+TP3,&TPD ; Output Data = high
```

```
MOV.B #TPSSEL2+TP2+TP1,&TPE ; TPCNT2: ACLK
```

```
BIS.B #TPIE+BTIE,&IE2 ; INTRPTS on
```

```
CLR.B SW_PWM ; No output
```

```
BIC.B #RC2FG+RC1FG,&TPCTL ; Clear flags
```

```
EINT
```

```
...
```

; Start both PWMs: Calculation results in R6 and R5

;

```
MOV.B R6,TIM_PWM1 ; (128 - result)
```

```
BIS.B #TP3,SW_PWM ; Enable PWM1
```

```
MOV.B R5,TIM_PWM2 ; (128 - result)
```

```
BIS.B #TP4,SW_PWM ; Enable PWM2
```

```

...
; Disable PWMs: Output is zero
;
        BIC.B    #TP4+TP3,SW_PWM          ; No output
;
; Interrupt Handler for the Basic Timer Interrupt: 256Hz
; The enabled PWMs are switched on
;
BT_INT  BIC.B    #RC2FG+RC1FG,&TPCTL      ; Clear flags
        MOV.B    TIM_PWM2,&TPCNT2        ; (128 - time2)
        MOV.B    TIM_PWM1,&TPCNT1        ; (128 - time1)
        BIC.B    SW_PWM,&TPD             ; Switch on enabled PWMs
        RETI
;
; End of Basic Timer Handler
;-----
; Interrupt Handler for the UT/PM. The PWM-channel that
; caused the interrupt is switched off.
;
UT_HNDL PUSH    R6                      ; Save R6
        MOV.B    &TPCTL,R6              ; INTRPT from where?
        AND      #RC2FG+RC1FG,R6        ; Isolate flags
        BIC.B    R6,&TPCTL               ; Clear set flag(s)
        RLA     R6                      ; To TP0.4/TP0.3
        RLA     R6
        BIS.B    R6,&TPD                 ; Set actual I/O(s)
        POP     R6                      ; Restore R6
        RETI
;
; End of Universal Timer/Port Module Handler
;-----
; Vectors like with the example before

```

### 3.6.5 PWM DAC With the Timer\_A

Timer\_A of the MSP430 family is ideally suited for the generation of PWM signals. The output unit of each one of the (up to five) capture/compare registers is able to generate seven different output modes. The PWM generation depends mainly on which mode of the Timer\_A was used.

- Continuous Mode: the timer register runs continuously upwards and rolls over to zero after the value 0FFFFh. The capture/compare register 0 is used like the other capture/compare registers. This mode allows up to five independent timings. The continuous mode is not intended for PWM applications. But, it can be used for relatively slow PWM applications, if other timings are also needed. Interrupt is used for the setting and the resetting of the PWM output. The output unit controls the PWM output and the interrupt handler adds the next time interval to the capture/compare register and modifies the mode of the output unit (set, toggle, or reset).
- Up Mode: The timer register counts up to the content of capture/compare register 0 (here the period register) and restarts at zero when it reaches this value. The capture/compare register 0 contains the period information for all other capture/compare registers.
- Up-Down Mode: The timer register counts up to the content of capture/compare register 0 (here the period register) and counts down to zero when it reaches this value. When zero is reached again, the timer register counts up again. capture/compare register 0 contains the period information for all other capture/compare registers.

All three modes are explained in detail in the Section 6.3, *Timer\_A*. Software program examples are also given. If dc output is needed, the same output filters can be used as shown in the previous section. The only difference is the possible speed of the Timer\_A (input frequency can be up to the MCLK frequency).

#### 3.6.5.1 PWM DAC With Timer\_A Running in Continuous Mode

Up to five completely different PWM generations are possible. If the Timer Register equals one of the four capture/compare latches (programmed to compare mode), the hardware task programmed to the output unit is performed (set, reset, toggle etc.) and an interrupt is requested. Figure 3–17 illustrates the generation of a PWM signal with the capture/compare registers 0. The interrupt handler is responsible for the following tasks:

- The time difference (represented by the clock count  $n_x$ ) to the next interrupt is added to the used capture/compare register by software: once  $\Delta t_0$ , once  $\Delta t_1$



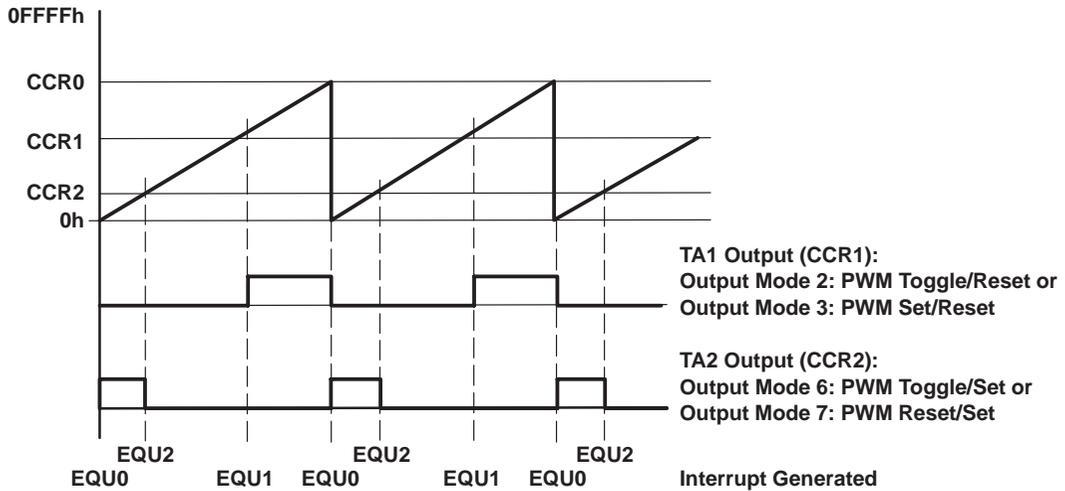


Figure 3–18. PWM Generation With Up Mode

### 3.6.5.3 PWM-DAC With Timer\_A Running in Up-Down Mode

Up to four different PWM generations with an equal period are possible. If the timer register equals one of the four capture/compare latches (programmed to compare mode), the hardware task programmed to the output unit is performed (set, reset, toggle etc.) and an interrupt is requested. During the interrupt handler, the necessary software task is completed. No reloading of the capture/compare register is necessary except if the pulse width changes. The timer register continues to count upward until the value of capture/compare register 0 is reached. Then it counts downward to zero. When it reaches the value of a capture/compare register, the programmed task is made by the output unit and an interrupt is requested again. When zero is reached, the sequence restarts. This way, symmetric PWM generation is possible. The value of the capture/compare register is reached twice for each up-down cycle. Figure 3–19 illustrates the generation of two independent PWM signals with the capture/compare registers 1 and 3.

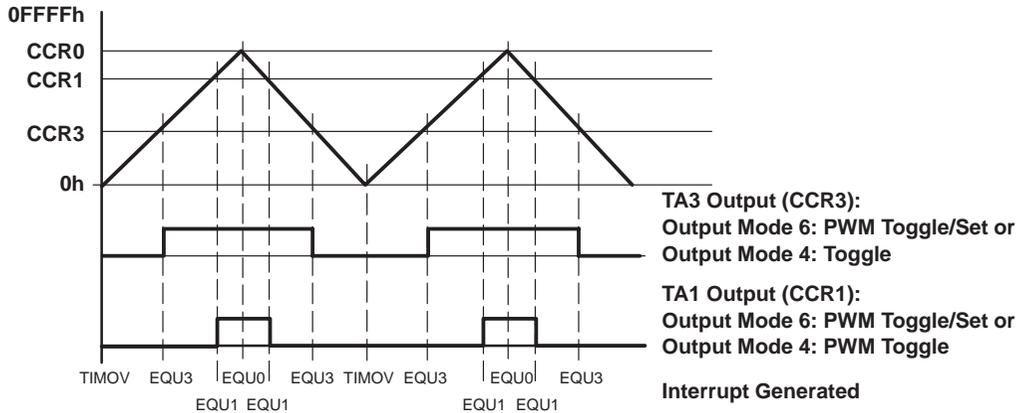


Figure 3–19. PWM Generation with Up-Down Mode

### 3.7 Connection of Large External Memories

For a lot of MSP430 applications, it is necessary to be able to store large amounts of measured data. For this purpose external memories can be used:

- Dynamic RAMs like the TMS44460 (1M × 4 bits)
- Synchronous Dynamic RAMs like the TMS626402 (2M × 4 bits)
- Flash memories like the TMS28F512A (512K × 8-bits)
- EEPROMs

DRAM versions with a self-refresh feature are recommended, otherwise the necessary refresh cycles would waste too much of the processing time.

Figure 3–20 shows the simplest way to control external memory. The unused LCD segment lines are used for addressing and control of the external memory. Four bidirectional I/O lines of port 0 (or another available port) are used for the bidirectional exchange of data. The necessary steps to read from or write to the example TMS44460 DRAM memory are:

- 1) Output row address to address lines A9 to A0
- 2) Set the RAS control line low
- 3) Output column address to address lines A9 to A0
- 4) Set CAS control lines low and reset them back to high
- 5) If a read is desired, set OE low and W control lines high. Then read data from DQ4 to DQ1.
- 6) If a write is desired, set OE high, set W low, and then write the data to DQ4 to DQ1.

The proposal shown in Figure 3–20 needs approximately 200 MCLK cycles for each block of 4-bit nibbles when the O-output lines are used.

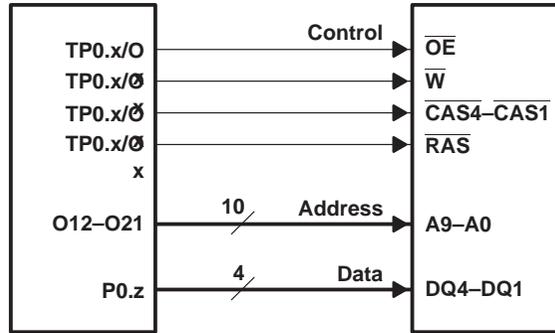


Figure 3–20. External Memory Control With MSP430 Ports

Example 3–11. External Memory Connected to the Outputs

For the circuit shown in Figure 3–20, the 10 address lines of an external memory are connected to the O-outputs, O12 (LSB) to O21 (MSB). The subroutine O\_HNDLR is used for the row and column addressing. The driver software and the subroutine call follows:

```

N      .EQU      10/2          ; 10 O-outputs are controlled (O13 to O4)
O_STRT .EQU      037h         ; Control byte for O12 and O13 (1st byte)
;
      MOV      #03FFh,R5      ; Start with row addressing
      CALL    #O_HNDLR
      ...
      MOV      R9,R5          ; Column address in R9
      CALL    #O_HNDLR      ; Output column address
      ...
      ; Output @CAS signals
;
; Subroutine outputs address info in R5 to O-outputs
; Bit 0 is written to the MSB of the O-outputs. R5 is destroyed
; Execution time: 69 cycles for 8 O-outputs (including CALL)
;                  129 cycles for 16 O-outputs (like above)
;
O_HNDLR CLR      R6          ; Clear counter
O_HN    MOV      R5,R4      ; Copy actual info
    
```

```

AND     #3,R4                ; Isolate next two address bits
MOV.B   TAB(R4),O_STRT(R6)   ; Write address bits
RRA     R5                   ; Prepare next two address bits
RRA     R5
INC     R6                   ; Increment counter
CMP     #N,R6               ; Through?
JNZ     O_HN                 ; No, next two bits
RET

;
; Table contains bit pattern used for the O-outputs
;
TAB     .BYTE    0,0Fh,0F0h,0FFh        ; Patterns 00, 01, 10, 11
    
```

Figure 3–21 gives an example to use when the LCD segment lines are not available. Two 8-bit shift registers are used for addressing and control of the external memory. Four bidirectional I/O lines of port 0 (or another available port) are used for the exchange of data. Instead of outputting the address and control signals in parallel, this solution's signals are output in series. The output enable signals G2 and G1 are used to omit bad signals that are due to the shifting of the information. The example shown in Figure 3–21 needs approximately 500 cycles for each block of 4-bit nibbles.

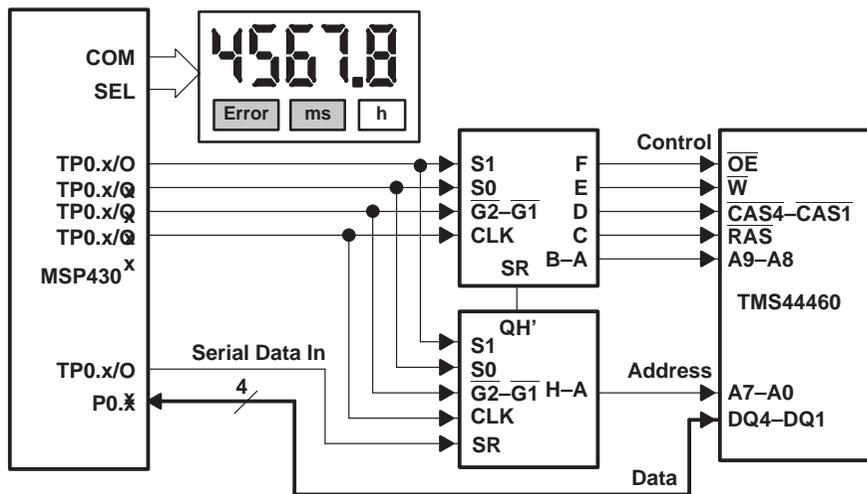


Figure 3–21. External Memory Control With Shift Registers

With nearly the same two hardware solutions, other external memories can be controlled also.

- ❑ Synchronous Dynamic RAM (TMS626402 2M × 4 bits) with 12 address lines and 6 control lines. Row and column addressing is used. It also uses 4 data bits.
- ❑ Flash memory (TMS28F512A 512K × 8-bit) with 16 address lines and 3 control lines. Direct addressing is used. It also uses 8 data bits.

Any combination of unused outputs (port, TP0.x, O<sub>y</sub>) and shift registers can be used. If DRAMs without self-refresh are used, the low address bits should be controlled by a complete port (port 1, 2, 3, or 4) to get minimum overhead for the refresh task.

The different versions of the MSP430C33x allow a much simpler and faster solution because of the five available I/O ports. Figure 3–22 illustrates the connection of an AT29LV010A EEPROM (128K × 8 bit) to the MSP430C33x. The example shown in Figure 3–22 needs approximately 30 to 50 MCLK cycles for each byte read or written. The control lines at the MSP430 are I/Os with no second function. All the peripheral functions are available and can be used freely. The MSP30C31x and 32x can address this type of memory by its TP0.x and O<sub>x</sub> ports.

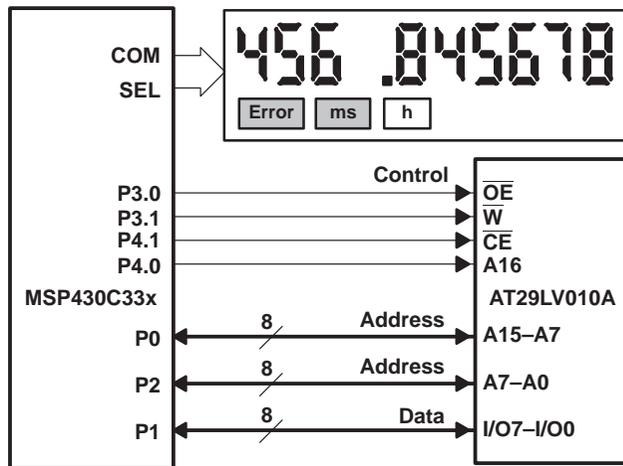


Figure 3–22. EEPROM Control With Direct Addressing by I/O Ports

Figure 3–23 shows the use of an MSP430C33x for the addressing of an external 1-MB RAM. The actual address of the external memory is stored in I/O Ports P0, P2, and P4. The special architecture of the MSP430 allows this method to be used. This method results in the fastest possible access time. The software used for addressing and reading of the next byte is in the following text (this assumes that the address ports are initialized).

			Cycles
;			
INC.B	&P2OUT	; Address next Byte	4
JNC	L\$1	; No carry to A15..A8	2
ADC.B	&P0OUT	; Carry to A15..A8	4
L\$1	MOV.B	&P1IN,R15	3

The reading of a byte needs  $(4 + 2 + 3) = 9$  cycles. An MCLK frequency of 3.8 MHz results in a read time of  $2.37 \mu\text{s}$ . This access time can be compared with the internal access time of an 8-bit microcomputer. The initialization of a 64-KB memory block is shown in the following text (memory block 1).

			Cycles
;			
MOV.B	#0,&P2OUT	; A7..A0 = 00	4
MOV.B	#0,&P0OUT	; A15..A8 = 00	4
MOV.B	#CS1+WE,&P4OUT	; Address memory block1	4

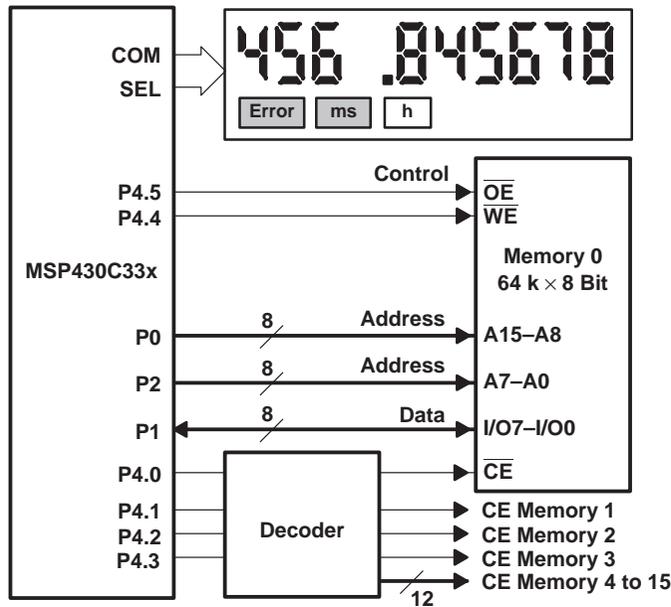


Figure 3–23. Addressing of 1-MB RAM With the MSP430C33x

Figure 3–24 shows how to address an external 1-MB RAM with an MSP430C31x. The actual address of the external memory (stored in the internal RAM) is output with the O-outputs (alternative use of the select lines) and the 6 TP ports. The software for addressing and reading of the next bytes is given in the following text (the address ports are initialized).

			Cycles
;			
	INC.B	A7_0 ; Address next byte	4
	JNC	L\$1 ; No carry to A15..A8	2
	ADC.B	A15_8 ; Carry to A15..A8	4
;			
;	Address A15 to A8 is output to O17 to O10.		
;	This part is necessary for only 0.4% of all accesses		
;			
	MOV.B	A15_8,R14 ; A15..8 -> R14	3
	MOV	R14,R15 ;	1
	AND	#3,R15 ; Next 2 address bits	2
	MOV.B	TAB(R15),&036h ; A9..8 to O11..10	6
	RRA	R14 ; Next 2 address bits	1
	RRA	R14	1
	MOV	R14,R15	1
	AND	#3,R15 ; Address A7..6 aso.	2
	...	; 4 x the same A15..6	36
;			
;	Address bits A7 to A0 output to TP-Port and O27/26		
;			
L\$1	MOV.B	A7_0,&TPD ; A7..A2 to TP-Port	6
	MOV.B	A7_0,R15 ; A1..A0 generated	3
	AND	#3,R15 ; A1..A0 in R15	2
	MOV.B	TAB(R15),&LCDx ; A1..A0 to O27 and O26	6
	MOV.B	&P0IN,R15 ; Read data at Port0	3
	...	; Process data	
;			
TAB	.BYTE	0, 0Fh, 0F0h, 0FFh ; For O-outputs	

The reading of one byte needs 26 cycles (addresses A15 – A8 are unchanged) or 83 cycles when A15 – A8 must be changed. An MCLK frequency of 3.8 MHz results in 6.9  $\mu$ s or 21.8  $\mu$ s for one byte, respectively.

The decoding of the 64-KB memory blocks is made with a normal 4-to-16 line decoder.

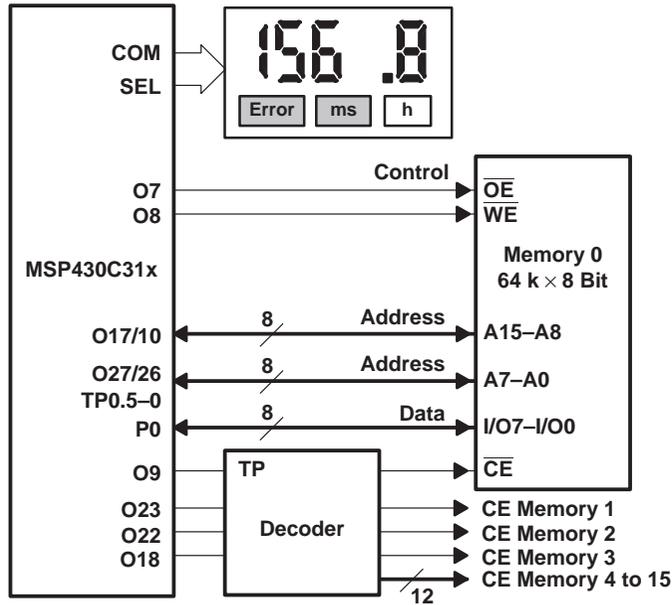


Figure 3–24. Addressing of 1-MB RAM With the MSP430C31x

## 3.8 Power Supplies for MSP430 Systems

There are various ways to generate the supply voltage(s) for the MSP430 systems. Due to the extremely low-power consumption of the MSP430 family, this is possible with batteries, accumulators, the M-Bus, fiber-optic lines, and ac. Every method uses completely different hardware and is explained in depth. Wherever possible, the formulas necessary for the hardware design are given too.

### 3.8.1 Battery-Power Systems

Due to the extremely low current consumption of the MSP430 family it is possible to run an MSP430 system with a 0.5-Ah battery more than 10 years. This makes possible applications that were impossible before. To reach such extended time spans, it is only necessary to observe some simple rules. The most important one is to always switch off the CPU when its not needed (e.g., after the calculations are completed). This reduces the current consumption from an operational low of 400  $\mu$ A down to 1.6  $\mu$ A.

The Figures 3–25 and 3–26 are drawn in a way that makes it easier to see how the battery needs to be connected to get the highest accuracy out of the ADC.

Figure 3–25 illustrates the MSP430C32x with its separated digital and analog supply terminals. This provides a separation of the noise-generating digital parts and the noise-sensitive analog parts.

Figure 3–26 shows how to best separate the two parts for the MSP430 family members with common supply terminals for the analog and digital parts of the chip.

If the battery used has a high internal resistance,  $R_I$ , (like some long-life batteries) then the parallel capacitor  $C_{ch}$  must have a minimum capacity. The supply current for the measurement part (which cannot be delivered by the battery) is delivered via  $C_{ch}$ . The equation includes the small current coming from the battery.

$$C_{chmin} \geq t_{meas} \times \left( \frac{I_{AM}}{\Delta V_{ch}} - \frac{1}{R_I} \right)$$

Between two measurements, the capacitor  $C_{ch}$  needs time,  $t_{ch}$ , to get charged-up to  $V_{CC}$  for the next measurement. During this charge-up time, the MSP430 system runs in low-power mode 3 to have the lowest possible power consumption. The charge-up time,  $t_{ch}$ , to charge  $C_{ch}$  to 99% of  $V_{CC}$  is:

$$t_{chmin} \geq 5 \times C_{chmax} \times R_{imax}$$

Where:

- $I_{AM}$  Medium system current (MSP430 and peripherals) (A)
- $t_{meas}$  Discharge time of  $C_{ch}$  during measurement (s)
- $\Delta V_{ch}$  Tolerable discharge of  $C_{ch}$  during time  $t_{meas}$  (V)
- $R_i$  Internal resistance of the battery ( $\Omega$ )

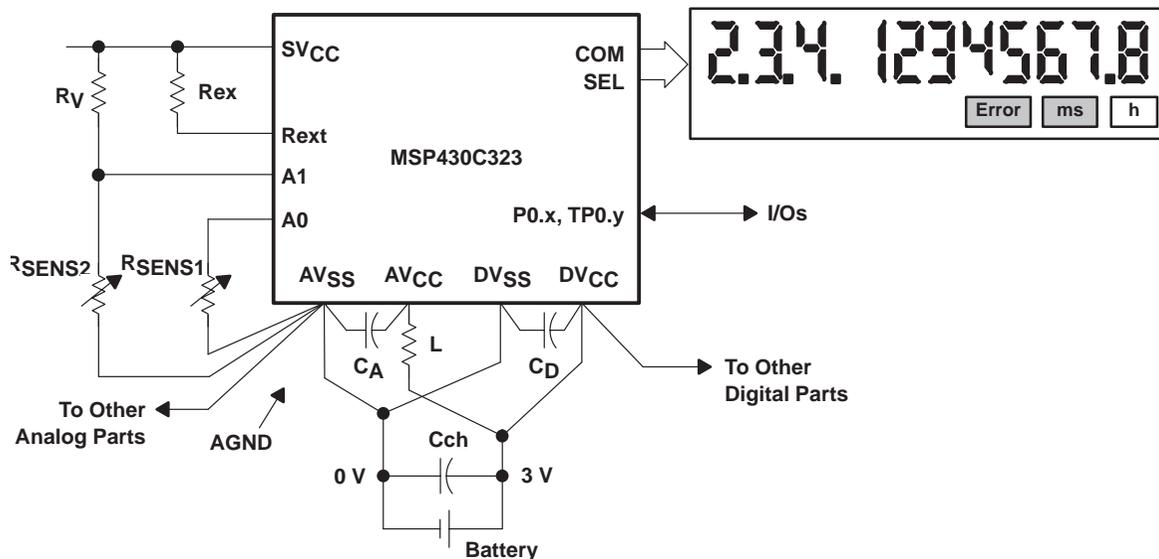


Figure 3–25. Battery-Power MSP430C32x System

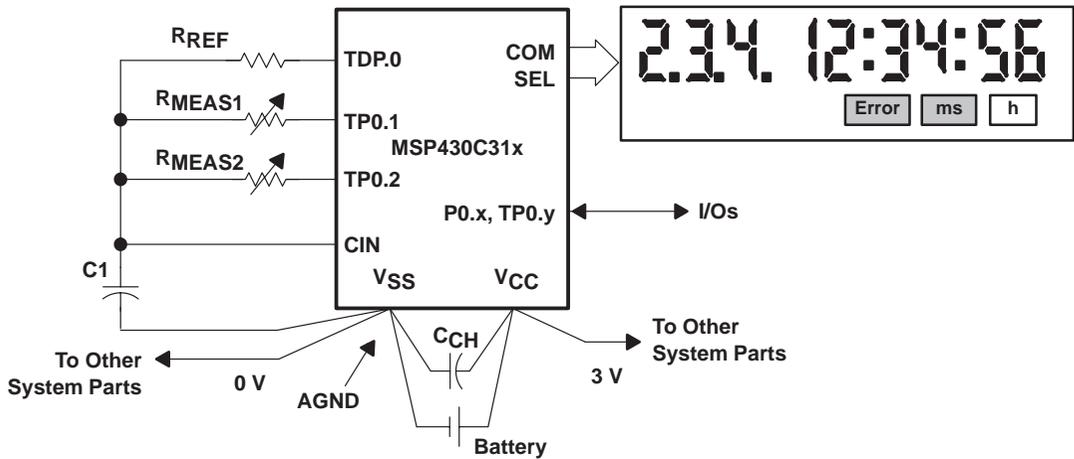


Figure 3–26. Battery-Power MSP430C31x System

**Note:**

The way the battery is connected to the MSP430 (shown in Figures 3–25 and 3–26) is not restricted to battery-driven MSP430 systems. The decoupling of the analog and the digital parts is necessary for all methods of supplied power. The following schematics are drawn in a simpler way to give better readability.

### 3.8.2 Accumulator-Driven Systems

The MSP430 can also be supplied from an accumulator. An advantage of this solution is that the MSP430 can also take over the battery management for the accumulator.

- ❑ **Current Measurement:** Summing up of the charge and discharge currents. If these currents (measured with sign) are multiplied with constants that are unique for the accumulator type used (e.g. NiCd, Pb) then it is possible to have a relatively accurate value for the actual charge. The current is measured with a shunt. The measured voltage drop is shifted into the middle of the ADC range by the current  $I_{cs}$  (generated by the MSP430's internal current source) that flows through  $R_c$ . This method allows signed current measurements.

- ❑ **Temperature Measurement:** All of the internal processes of an accumulator (e.g., maximum charge, self discharge) are strongly dependent on the temperature of the pack. Therefore, the temperature of the pack is measured with a sensor and used afterwards with the calculations. When the MSP430's current source is used, the voltage drop of its current  $I_{cs}$  across the sensor resistance is measured with the ADC input A2.
- ❑ **Voltage Measurement:** The voltage of an accumulator pack is an indication of the states full charge and complete discharge. Therefore, the voltage of the pack is measured with the voltage divider consisting of R1 and R2.
- ❑ **Charge Control:** Dependent on the result of the charge calculations, the MSP430 can decide if the charge transistor needs to be switched on or off. This decision can also be made in PWM (Pulse Width Modulation) mode. Figure 3–27 shows three possible charge modes. If replaceable accumulators are used, the charge control is not needed.
- ❑ **Rest Mode Handling:** During periods of non-use, the low power mode 3 of the MSP430 allows the control of the rest mode. The rest mode has nearly no current consumption. In fact, the supply current has the same magnitude as the self-discharge current of the accumulator. All system peripherals are switched off; the MSP430 wakes-up at regular intervals, which are controlled by its basic timer. It then calculates, every few hours, the amount of self discharge of the accumulator. This calculated value is subtracted from the actual charge level.

Figure 3–27 illustrates an MSP430 system driven by an accumulator. The battery management is done by the MSP430 also. The hardware needed is simple. As shown in the figure, just a few resistors and a temperature sensor. The actual charge of the accumulator is indicated in the LCD with a bar graph ranging from Empty to Full.

All necessary constants and a security copy of the actual charge are contained in an external EEPROM typically with 128 x 8 bits.

**Note:**

The hardware shown in Figure 3–27 can also be used for an intelligent accumulator controller. Only the hardware necessary for this task is shown. The measurement parts for voltage, current, and temperature are exactly the same as shown.

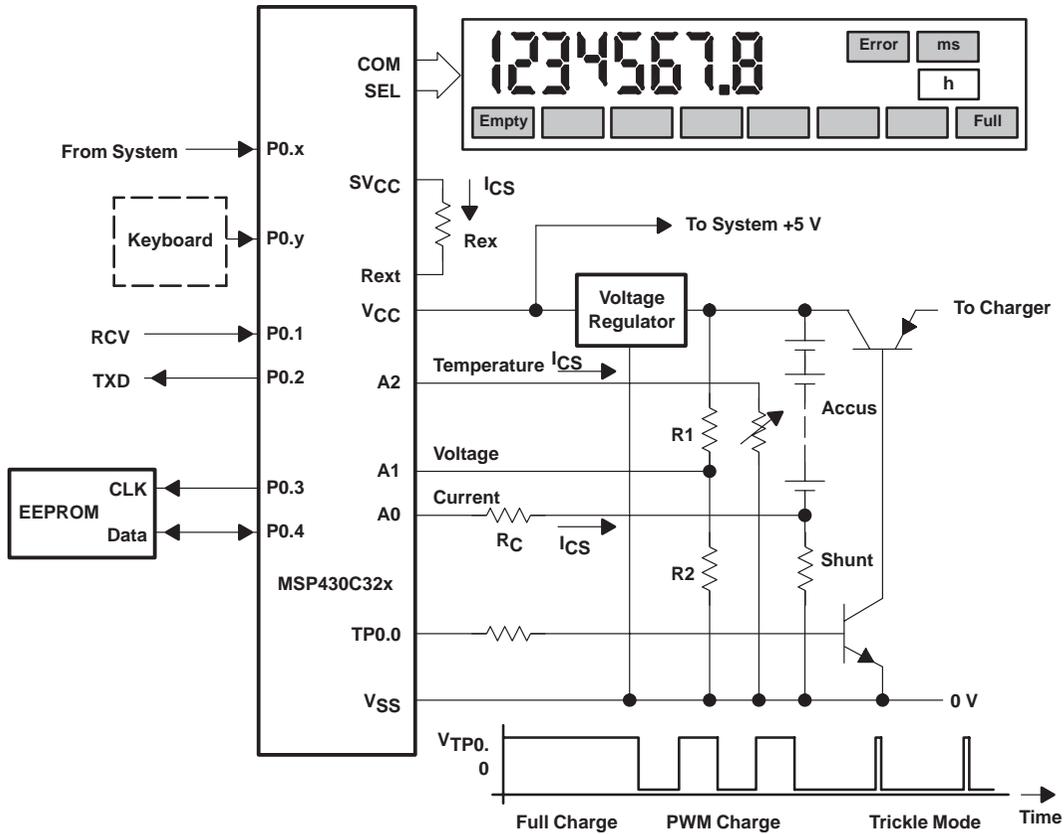


Figure 3–27. Accumulator-Driven MSP430 System With Battery Management

### 3.8.3 AC-Driven Systems

The current consumption of microcomputer systems gets more and more important for ac-driven systems. The lower the power consumption of a microcomputer system, the simpler and cheaper the power supply can be

### 3.8.3.1 Transformer Power Supplies

Transformers have two big advantages:

- Complete isolation from ac. This is an important security attribute for most systems.
- Very good adaptation to the needed supply voltage. This results in a good power efficiency.

Most ac-driven applications are only possible because of the isolation from the ac the transformer provides.

#### Half-Wave Rectification

Half-wave rectification uses only one half-wave of the transformer's secondary voltage,  $V_{SEC}$ , for the powering of an application. Figure 3–28 illustrates the voltages used with the equations.

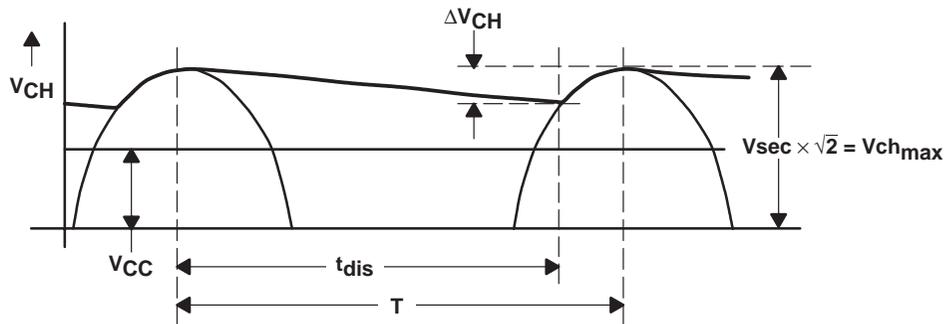


Figure 3–28. Voltages and Timing for the Half-Wave Rectification

- Advantages
  - Simplified hardware
  - Rectification with the voltage drop of only one diode
- Disadvantages
  - Charge capacitor,  $C_{CH}$ , must have doubled capacity compared to full-wave rectification
  - Higher ripple on the dc supply voltage
  - DC flows through the transformer's secondary winding

Figure 3–29 shows the most simple ac driven power supply. The positive half-wave of the transformer's secondary side charges the load capacitor,  $C_{CH}$ .

The capacitor's voltage is stabilized with a Zener diode having a Zener voltage equal to the necessary supply voltage  $V_{CC}$  of the MSP430.

Two conditions must be met before a final calculation is possible:

$$V_{SECmin} \times \sqrt{2} - \Delta V_{ch} > V_Z$$

and:

$$\frac{T}{2 \times C_{chmin}} < R_V < \frac{V_{SECmin} \times \sqrt{2} - \Delta V_{ch} - V_Z}{I_{AMmax}}$$

The charge capacitor,  $C_{CH}$ , must have a minimum capacity:

$$C_{chmin} \geq \frac{T}{2} \times \left( \frac{1}{R_V} + \frac{I_{AM}}{V_{SECmin} \times \sqrt{2} - V_Z} \right)$$

The peak-to-peak ripple voltage  $V_{N(PP)}$ , of the supply voltage,  $V_{CC}$ , is:

$$V_{npp} \approx \frac{\frac{V_{CC}}{I_{AM}} \parallel R_Z}{R_V + \frac{V_{CC}}{I_{AM}} \parallel R_Z}$$

The final necessary secondary voltage,  $V_{SEC}$ , of the ac transformer is ( $\Delta V_{CH} = 0.1 \times V_{CHmax}$ ):

$$V_{SECmin} \geq \frac{1}{\sqrt{2}} \times \left( \frac{0.45 \times T \times I_{AM}}{C_{chmin} - \frac{0.45 \times T}{R_V}} + V_Z \right)$$

Where:

$I_{AM}$	Medium system current (MSP430 and peripherals)	[A]
T	Period of the ac frequency	[s]
$\Delta V_{ch}$	Discharge of Cch during time tdis	[V]
$V_{CC}$	Supply voltage of the MSP430 system	[V]
$V_Z$	Voltage of the Zener diode	[V]
$R_Z$	Differential resistance of the Zener diode	[ $\Delta V/\Delta A$ ]
$R_V$	Resistance of the series resistor	[ $\Omega$ ]
$V_{sec}$	Secondary (effective) voltage of the transformer (full load conditions)	[V]

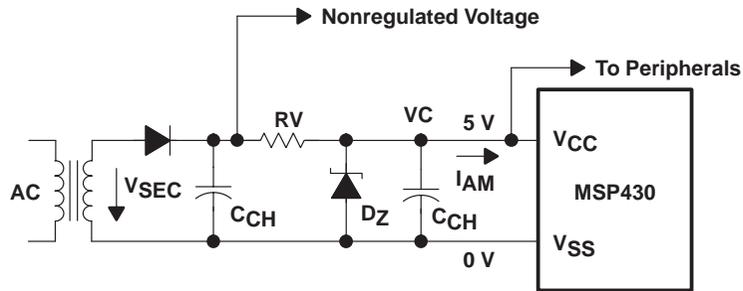


Figure 3–29. Half-Wave Rectification With 1 Voltage and a Zener Diode

Figure 3–30 shows a simplified power supply that uses a voltage regulator like the  $\mu$ A78L05. The charge capacitor,  $C_{ch}$ , must have a minimum capacity:

$$C_{chmin} \geq \frac{I_{AM} \times t_{dis}}{\Delta V_{ch}}$$

The peak-to-peak ripple  $V_N(PP)$  on the output voltage  $V_{reg}$  depends on the used voltage regulator. The regulators ripple rejection value can be seen in its specification. The necessary secondary voltage  $V_{sec}$  of the ac transformer under full load conditions is:

$$V_{SECmin} \geq \frac{1}{\sqrt{2}} \times \left( V_{reg} + V_r + V_d + t_{dis} \times \frac{I_{AM}}{C_{chmin}} \right)$$

The discharge time  $t_{dis}$  used with the previous equations is:

$$t_{dis} = T \times \left[ 1 - \frac{\arcsin \left( 1 - \frac{\Delta V_{ch}}{V_{SEC} \times \sqrt{2}} \right)}{2\pi} \right]$$

Where:

$t_{dis}$	Discharge time of $C_{ch}$	[s]
$V_d$	Voltage drop of one rectifier diode	[V]
$V_r$	Dropout voltage (voltage difference between output and input) of the voltage regulator for function	[V]
$V_{reg}$	Nominal output voltage of the voltage regulator	[V]

For first estimations the value of  $t_{dis}$  is calculated for two different discharge values:

- 10% discharge of  $C_{ch}$  during  $t_{dis}$   $t_{dis} = 0.93T$
- 30% discharge of  $C_{ch}$  during  $t_{dis}$   $t_{dis} = 0.88T$

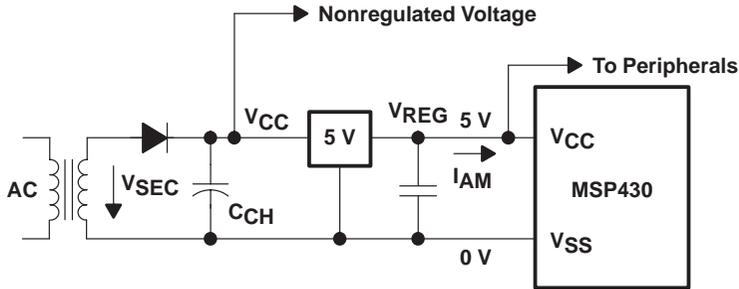


Figure 3–30. Half-Wave Rectification With One Voltage and a Voltage Regulator

Figure 3–31 shows an MSP430 system that uses two supply voltages: +5 V and –5 V. The negative supply voltage is used for analog interfaces. Simple resistor dividers interface the 10-V analog part into the 5 V range of the MSP430. The formulas for the calculation of the charge capacitor,  $C_{ch}$ , and the necessary secondary voltage,  $V_{sec}$ , are the same as shown for the circuitry in Figure 3–30. The same circuitry can be used for a system with +2.5 V and –2.5 V (see Figure 3–37 for more details).

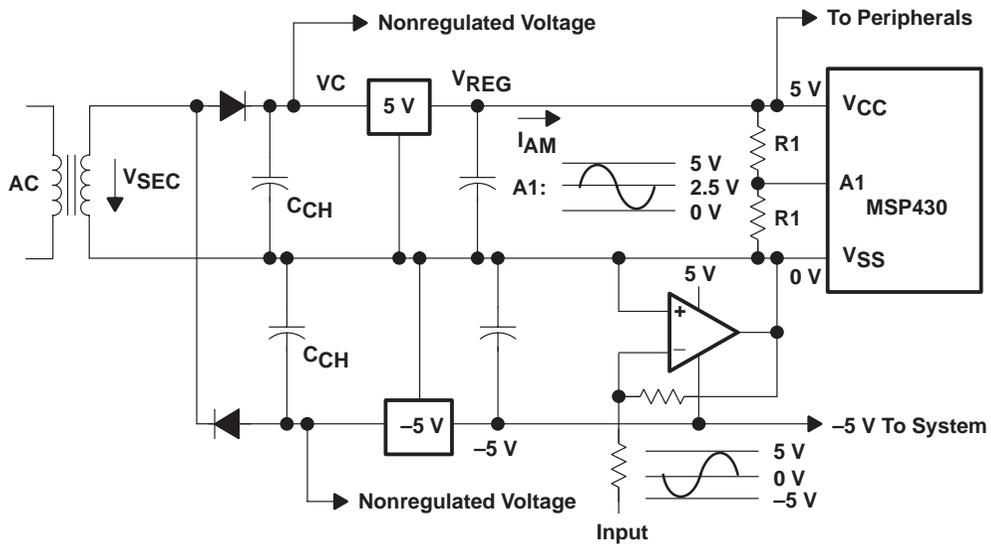


Figure 3–31. Half-Wave Rectification With Two Voltages and Two Voltage Regulators

### Full-Wave Rectification

Full-wave rectification uses both half-waves of the secondary voltage,  $V_{sec}$ , for the powering of the application.

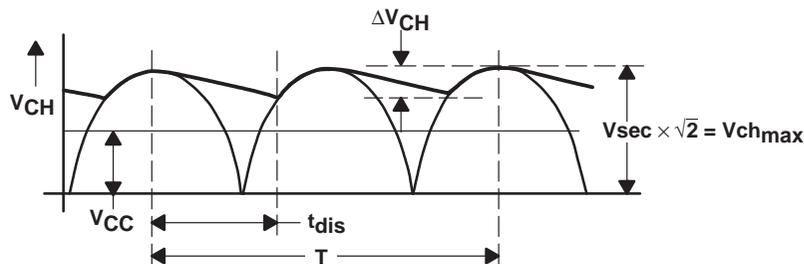


Figure 3–32. Voltages and Timing for Full-Wave Rectification

#### Advantages

- Smaller charge capacitor  $C_{ch}$
- Lower ripple voltage
- No dc current through transformer's secondary winding

#### Disadvantages

- Four diodes or a transformer with center tap is necessary
- Voltage drop of two diodes in series (except with a transformer having a center tap)

Figure 3–33 shows a simple power supply that uses a  $\mu\text{A78L05}$  voltage regulator. The charge capacitor,  $C_{\text{ch}}$ , must have a minimum capacity:

$$C_{\text{chmin}} \geq \frac{I_{\text{AM}} \times t_{\text{dis}}}{\Delta V_{\text{ch}}}$$

The peak-to-peak ripple,  $V_{\text{npp}}$ , on the voltage,  $V_{\text{CC}}$ , depends on the voltage regulator used. The ripple rejection value can be seen in the voltage regulator specification. The necessary secondary voltage,  $V_{\text{sec}}$ , of the ac transformer is for the upper rectifier with four diodes (full load conditions):

$$V_{\text{SECmin}} \geq \frac{1}{\sqrt{2}} \times \left( V_{\text{reg}} + V_{\text{r}} + 2 \times V_{\text{d}} + t_{\text{dis}} \times \frac{I_{\text{AM}}}{C_{\text{chmin}}} \right)$$

For the center tap transformer,  $V_{\text{d}}$ , in the previous equation is multiplied by one ( $1 \times V_{\text{d}}$ ). The discharge time  $t_{\text{dis}}$  used with the previous equations is:

$$t_{\text{dis}} = T \times \left[ 0.5 - \frac{\arcsin \left( 1 - \frac{\Delta V_{\text{ch}}}{V_{\text{SEC}} \times \sqrt{2}} \right)}{2\pi} \right]$$

For first estimations the value of  $t_{\text{dis}}$  is calculated for two different discharge values:

- 10% discharge of  $C_{\text{ch}}$  during  $t_{\text{dis}}$   $t_{\text{dis}} = 0.43T$
- 30% discharge of  $C_{\text{ch}}$  during  $t_{\text{dis}}$   $t_{\text{dis}} = 0.38T$

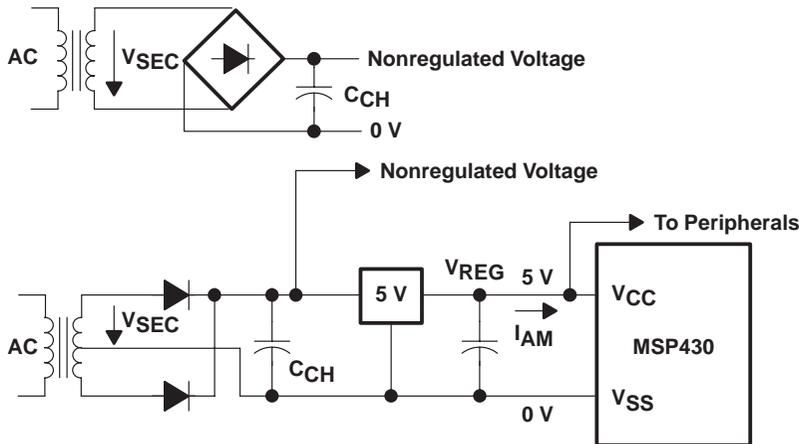


Figure 3–33. Full Wave Rectification for one Voltage with a Voltage Regulator

Figure 3–34 shows an MSP430 system that uses two supply voltages: +2.5 V and –2.5 V. The formulas for the calculation of the charge capacitor,  $C_{ch}$ , and the necessary secondary voltage,  $V_{sec}$ , are the same as given for the circuitry in Figure 3–33. The circuitry of Figure 3–34 can also be used for a system with +5-V and –5-V supply (see Figure 3–31 for more details).

Also shown, is how to connect a TRIAC used for ac motor control. The relatively high gate current needed is taken from the non-regulated positive voltage. This reduces the noise within the regulated MSP430 supply. The current flowing through the motor is measured with the ADC for control purposes. The ADC result for 0 V (measured at A0) is subtracted from the current ADC value and results in a signed, offset-corrected value. If a single supply voltage is used (+5V only), the current source can be used to shift the signed current information into the range of the ADC. See Figure 3–27 for the current measurement circuit.

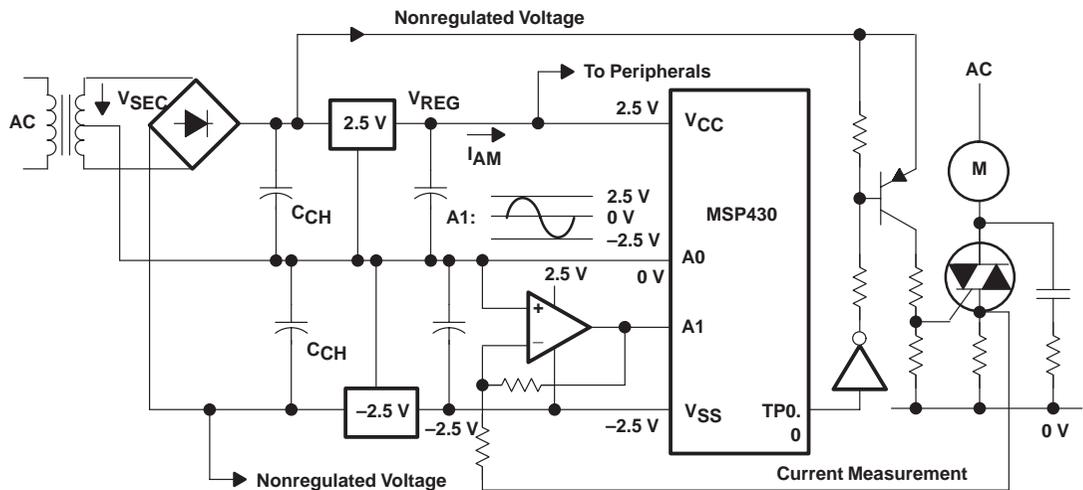



Figure 3–34. Full-Wave Rectification for Two Voltages With Voltage Regulators

### 3.8.3.2 Capacitor Power Supplies

Applications that do not need isolation from the ac supply or that have a defined connection to the ac supply (like electricity meters) can use capacitor power supplies. The transformer is not needed and only the series capacitor,  $C_m$ , must have a high voltage rating due to the voltage spikes possible on ac source.

The ac resistance of the series capacitor,  $C_m$ , is used in a voltage divider. This means relatively low power losses. The active power losses are restricted to the protection resistor,  $R_m$ , connected in series with  $C_m$ . This protection resistor is necessary to limit the current spikes due to voltage spikes and high frequency parts overlaid to the ac voltage. The current  $I_{ac}$  through the circuitry is:
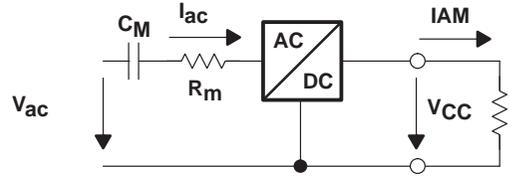
$$I_{ac} = \frac{V_{ac}}{\frac{1}{j\omega \times C_m} + R_m} \approx \frac{V_{ac}}{\sqrt{\frac{1}{\omega^2 \times C_m^2} + R_m^2}}$$



Where:

- $V_{ac}$  ac voltage [V]
- $f_{ac}$  Nominal frequency of the ac [Hz]
- $\omega$  Circle frequency of the ac:  $\omega = 2\pi f$  [1/s]
- $C_m$  Series capacitor [F]
- $R_m$  Series resistor [ $\Omega$ ]

The previous formula for  $I_{ac}$  is valid for all shown capacitor power supplies. The formula assumes low voltages will be generated (< 5% of the ac voltage). For a dc current,  $I_{AM}$ , the necessary ac current  $I_{ac}$  is:

$$I_{ac} \geq I_{AM} \times \frac{\pi}{\sqrt{2}} = I_{AM} \times 2.221$$

The capacitor,  $C_m$ , is:

$$C_{mmin} \geq \frac{1}{2\pi \times f_{acmin}} \times \frac{1}{\sqrt{\left(\frac{V_{acmin} \times \sqrt{2}}{\pi \times I_{AM}}\right)^2 - R_{mmax}^2}}$$

This formula for  $C_m$  is valid for all shown capacitor supplies. The calculated value for  $C_m$  includes the tolerances for the ac voltage and the ac frequency; the minimum values used for  $V_{ac}$  and  $f_{ac}$  ensure this.

The protection resistor,  $R_m$ , for a maximum spike current  $I_{max}$  generated by a voltage spike  $V_{spike}$  is:

$$R_m \geq \frac{V_{spike}}{I_{max}}$$

The charge capacitor,  $C_{ch}$ , must have a minimum capacity:

$$C_{chmin} \geq \frac{I_{AM} \times T}{2 \times \Delta V_{ch}}$$

- ☐ Advantages
  - No transformer necessary
  - Very simple hardware
- ☐ Disadvantages
  - No isolation from ac

### Capacitor Supplies for a Single Voltage

Figure 3–35 shows the simplest capacitor power supply. The Zener diode used for limiting the voltage of the charge capacitor,  $C_{ch}$ , is used for the voltage regulation too. The peak-to-peak ripple voltage,  $V_{npp}$ , on voltage,  $V_{CC}$ , is:

$$V_{npp} \approx I_{AM} \times \frac{T}{C_{ch} \times 2}$$

The voltage of the Zener diode,  $D_z$ , is:

$$V_z \approx V_{CC} + V_d$$

$C_{ch}$  is calculated as shown in Section 3.8.3.2, *Capacitor Power Supplies*.

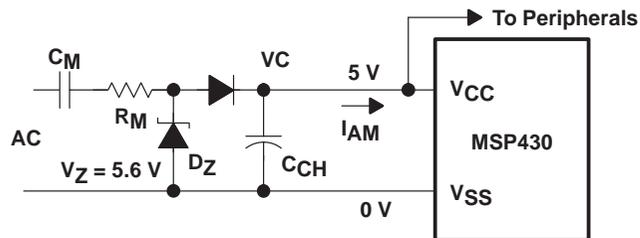


Figure 3–35. Simple Capacitor Power Supply for a Single Voltage

Figure 3–36 shows a hardware proposal for a regulated output voltage,  $V_{CC}$ . The voltage,  $V_z$ , of the Zener diode,  $D_z$ , must be:

$$V_z \geq V_d + V_{reg} + V_r + T \times \frac{I_{AM}}{2 \times C_{chmin}}$$

C<sub>ch</sub> is calculated as shown in Section 3.8.3.2, *Capacitor Power Supplies*.

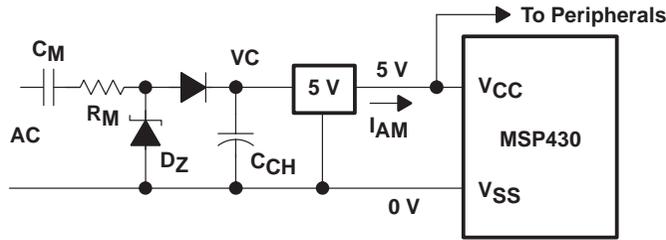


Figure 3–36. Capacitor Power Supply for a Single Voltage

### Capacitor Supplies for Two Voltages

Applications that need two voltages (e.g., +2.5 V and –2.5 V) can also use a capacitor supply.

Figure 3–37 shows a split power supply with two regulated output voltages. Together, they deliver the supply voltage, V<sub>CC</sub>. The split power supply allows the measurement of the voltage of the 0-V line at A0. This value can be subtracted from all other measured analog inputs. This results in offset corrected, signed values. The voltage, V<sub>Z</sub>, of each Zener diode, D<sub>Z</sub>, must be:

$$V_Z \geq V_r + V_{reg} + T \times \frac{I_{AM}}{2 \times C_{chmin}}$$

The two charge capacitors, C<sub>ch</sub>, must have the values:

$$C_{chmin} \geq \frac{I_{AM} \times T}{\Delta V_{ch} \times 2}$$

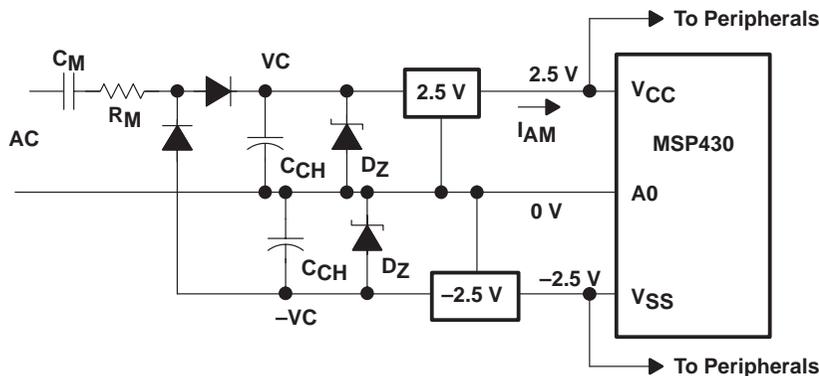


Figure 3–37. Split Capacitor Power Supply for Two Voltages

Figure 3–38 shows a split power supply for +2.5 V and –2.5 V made in a completely different way. It is capable of delivering relatively large output currents due to the buffer transistors. If the high current capability is not needed, the transistors can be omitted and the loads connected to the outputs of the two operational amplifiers directly. The reference for all voltages is a reference diode, LMx85. The highly stable 1.25 V output of this diode is multiplied by two (for +2.5V) or multiplied by –3 and added to the reference value, which delivers –2.5 V. The voltage drop of each one of the two diodes, D, is compensated by the series connection of the two Zener diodes, Dz. The required Zener voltage, Vz, of the two diodes Dz is:

$$V_Z \geq \frac{V_{CC}}{2} + V_{BE} + (V_{CC} - V_{om}) + T \times \frac{I_{AM}}{2 \times C_{chmin}}$$

Where:

$V_{BE}$	Basis-Emitter voltage of a transistor	[V]
$V_{om}$	Maximum peak output voltage swing of the operational amplifier with VC	[V]

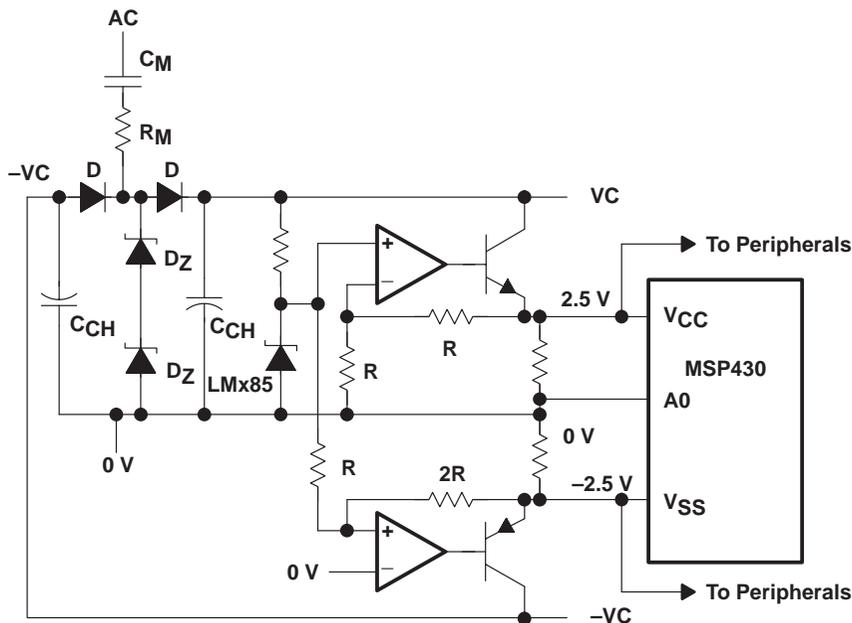


Figure 3–38. Split Capacitor Power Supply for Two Voltages With Discrete Components

### 3.8.4 Supply From Other System DC Voltages

Existing dc voltages of the controlled system, like +12 V or +24 V, can be used for the supply to the MSP430 system. This is possible due to the low current consumption of the MSP430. So there is nearly no power wasted in the voltage regulator for  $V_{CC}$ . If relays and other power consuming peripherals need to be used, the system dc voltage,  $V_{sys}$ , can be used (see Figure 3–40). This solution has two advantages:

- The switching noise is generated outside of the MSP430 supply
- The power for the switched parts does not increase the power of the MSP430 supply

Figure 3–39 and 3–40 show four different possible supplies for an MSP430 system from an existing +12 V (or +24 V) power supply.

#### 3.8.4.1 Zener Diode

A simple configuration of a series resistor  $R_V$  with a Zener diode  $D_Z$  delivers an output voltage of +3 V or +5 V. The resistor ( $R_V$ ) is:

$$R_{Vmax} > \frac{V_{sysmin} - V_Z}{I_{zmin} + I_{AM}}$$

Where:

$V_Z$	Zener voltage of the Zener diode	[V]
$I_Z$	Current through the Zener diode	[A]
$V_{sys}$	Nominal system voltage	[V]

#### 3.8.4.2 Zener Diode and Operational Amplifier

If larger currents or a higher degree of decoupling is necessary, then an operational amplifier can be used additionally. This way the series resistor  $R_V$  can have a much higher resistance than without the operational amplifier. The NPN buffer transistor is only necessary if the operational amplifier cannot output the needed system current. The series resistor  $R_V$  is calculated with:

$$R_{Vmax} > \frac{V_{sysmin} - V_Z}{I_{zmin}}$$

### 3.8.4.3 Reference Diode With Operational Amplifier

The low voltage of a reference diode (e.g., LMx85) is amplified with an operational amplifier and also buffered. The series resistor,  $R_v$ , feeds only the reference diode and has a relatively high resistance. Therefore, it is calculated the same way as shown in Section 3.8.4.2, *Zener Diode*. The output voltage,  $V_{out}$ , is calculated with:

$$V_{out} = V_Z \times \frac{R1 + R2}{R2}$$

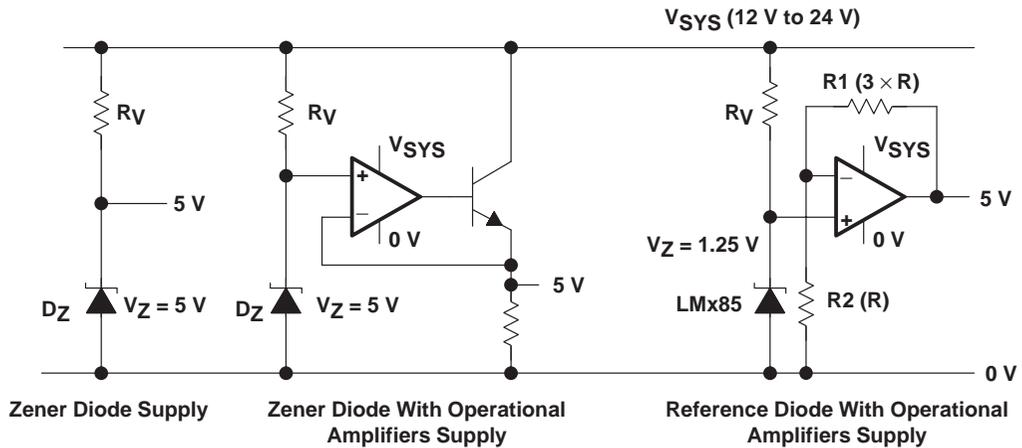


Figure 3–39. Simple Power Supply From Other DC Voltages

### 3.8.4.4 Integrated Voltage Regulator

Figure 3–40 illustrates the use of an integrated voltage regulator. Here a TPS7350 (regulator plus voltage supervisor) is used, so a highly-reliable system initialization is possible. The TPS7350 also allows the use of the RST/NMI terminal of the MSP430 as described in Section 5.7, *Battery Check and Power Fail Detection*. The RST/NMI terminal is used while running a normal program as an NMI (Non-Maskable Interrupt). This makes possible the saving of important data in an external EEPROM in case of power failure. This is because PG

outputs a negative signal starting at  $V_{CC} = 4.75\text{ V}$ , which allows a lot of activities until  $V_{CCmin}$  of the MSP430 (2.5 V) is reached.

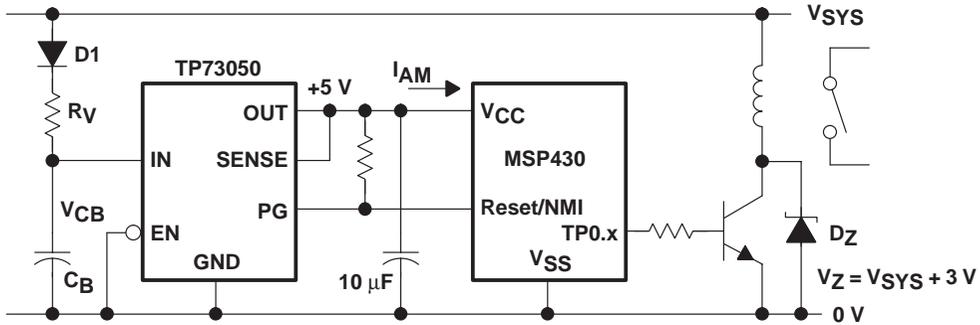


Figure 3–40. Power Supply From Other DC Voltages With a Voltage Regulator

With two additional components (an RC combination) the MSP430 system can be protected against spikes and bridging of supply voltage dropouts is possible. The diode, D1, protects the capacitor, Cb, against discharge during dropouts in voltage Vsys. The series resistor, Rv, is:

$$R_{vmax} < \frac{(V_{sysmin} - V_d - V_{CC} - V_r)}{I_{AM} + I_{regmax}}$$

The minimum capacity of Cb is:

$$C_{bmin} > \frac{\Delta t \times (I_{AM} + I_{reg})}{V_{sysmin} - (I_{AM} + I_{regmax}) \times R_{vmax} - V_{rmax} - V_{CCmin}}$$

Where:

- $I_{AM}$  System current (medium value MSP430 and peripherals) [A]
- $I_{reg}$  Supply current of the voltage regulator [A]
- $V_{sys}$  System voltage (e.g., +12 V) [V]
- $V_d$  Diode forward voltage (< 0.7 V) [V]
- $V_r$  Dropout voltage of the voltage regulator for function [V]
- $V_{CC}$  Supply voltage of the complete MSP430 system [V]
- $\Delta t$  Dropout time of  $V_{sys}$  to be bridged [s]

### 3.8.5 Supply From the M Bus

If the MSP430 system is connected to the M-Bus, three possibilities exist for the supply of the MSP430:

- Battery Supply: The supply of the MSP430 is completely independent of the M-Bus. This method is not shown in Figure 3–41, because it is the normal way the MSP430 is powered (see Section 3.8.1, *Battery Driven Systems*).
- M-Bus Supply: The MSP430 system is always supplied by the M-Bus. During off phases of the M-Bus, the MSP430 is not powered.
- Mixed Supply: Normally the M-Bus supplies the MSP430 and only during off phases of the M-Bus does the battery of the MSP430 provide power.

#### 3.8.5.1 M-Bus Supply

The MSP430 is always powered from the M-Bus. The TSS721 power fail signal, PF, indicates to the MSP430 failure of the bus voltage. This early warning enables the MSP430 to save important data in an external EEPROM. The capacitor,  $C_{ch}$ , must have a capacity that allows this storage:

$$C_{chmin} \geq \frac{I_{AM} \times t_{store}}{V_{DD} - V_{CCmin}}$$

Where:

$I_{AM}$	System current (MSP430 and EEPROM)	[A]
$t_{store}$	Processing time to store important data into the EEPROM	[s]
$V_{DD}$	Supply voltage delivered from the TSS721	[V]
$V_{CCmin}$	Minimum supply voltage of the complete MSP430 system	[V]

### 3.8.5.2 Mixed Supply

The MSP430 is powered from the M-Bus while bus voltage is available. During times without bus voltage, the battery powers the MSP430. Therefore, a smaller battery can be used when normal bus power is available. The MOS transistor switches to the battery when there is a dropout of the M-Bus voltage. Details are described in the *TSS721 M-Bus Transceiver Application Report*.

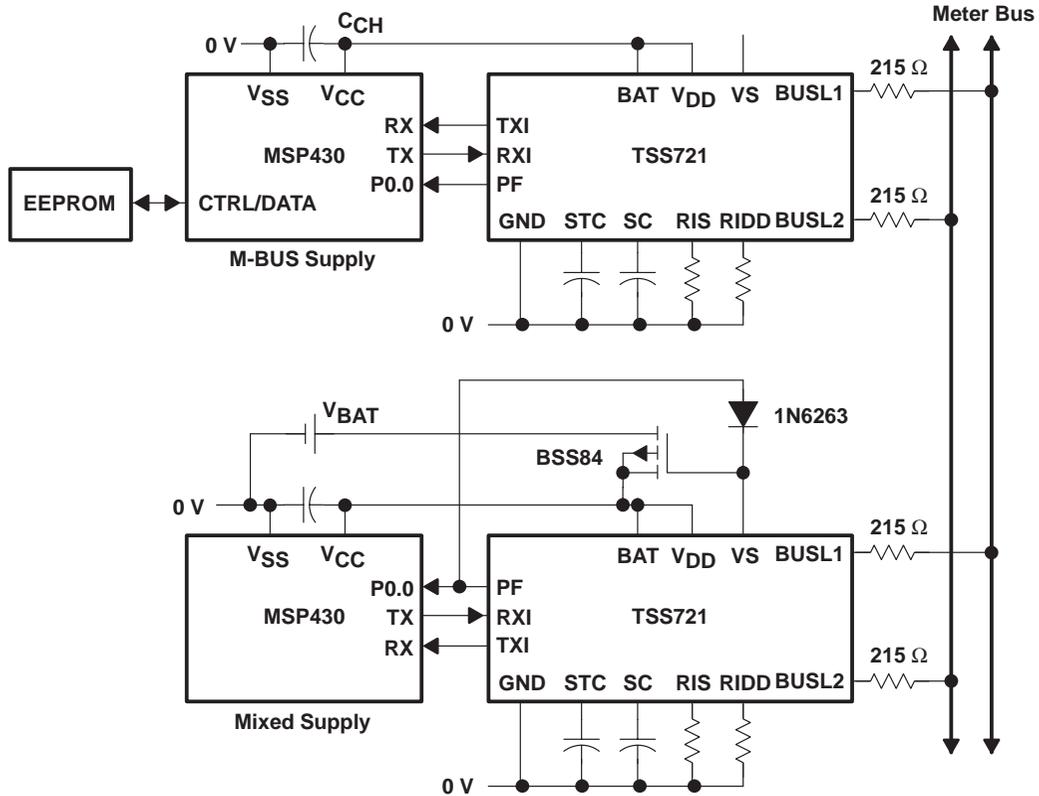


Figure 3–41. Supply From the M Bus

### 3.8.6 Supply Via a Fiber-Optic Cable

The MSP430 needs a supply current of only 400 $\mu$ A, if supplied with a voltage of 3 V and operating with an MCLK of 1 MHz. This low power can be transmitted via a glass-fiber (fiber-optic) cable. This allows completely isolated measurement systems, which are not possible with other microcomputers. This transmission mode is an advantage for applications in strong electric or magnetic fields.

Because the data transmitted from the host to the MSP430 is also used for the supply of the MSP430 system, a certain amount of light is required continuously and is independent of the transmitted data. Possible ways to reach this are:

- Use of extended charge periods between host-to-MSP430 data transfers. The MARK level of the RS232 protocol is used for this purpose. This method is shown in Figure 3–42 with every logical one, stop bit, and MARK level used for the supply.
- Use of a transmission code that always transmits the same number of ones and zeroes, independent of the transmitted data. (e.g., the Bi-Phase Code)

To achieve a positive current balance, a few conditions must be met:

- The complete hardware design uses ultra-low-power devices (operational amplifiers, reference diode, measurement parts etc.).
- The MSP430 is in Low Power Mode 3 anytime processing power is not needed.
- The measurement unit is switched on only during the actual measurement cycle.
- All applicable hints given in Section 4.9, *Ultra-Low-Power Design with the MSP430 Family* are used.

#### 3.8.6.1 Description of the Hardware

The host sends approximately 15 mW of optical power into the fiber-optic cable. This optical power is made with a laser diode consuming 30 mW of electrical power. At the other end of the fiber-optic cable, the optical power is converted into 6 mW of electrical power with a power-converter diode. The open-circuit voltage of the power converter (approximately 6 V) decreases to 5 V with the load represented by the MSP430. The received electrical energy is used to charge the capacitor, C<sub>ch</sub>. The charge-up time required is approximately 300 ms for a capacitor with 30  $\mu$ F.

The uppermost operational amplifier is used for the voltage regulation of the system supply voltage (3 V to 4 V).

If a stabilized supply voltage is unnecessary, then this operational amplifier can be omitted, as well as the diodes and pull-up resistors at the RST/NMI and P0.1 inputs.

The reference for the complete system is an LMx85 reference diode. This reference voltage (1.25 V) is used for several purposes: trigger threshold for the Schmitt-triggers, reference for the calculation of  $V_{CC}$ , and reference for the voltage regulator.

The operational amplifier in the middle works as a reset controller. The Schmitt-trigger switches the RST/NMI input of the MSP430 to a high level when VC reaches approximately 4 V. The RST/NMI input is set low when VC falls below 2.5 V.

The third operational amplifier decodes the information out of the charge voltage and data of the power converter output. This decoder also shows a Schmitt-trigger characteristic.

The measured data is sent back to the host by an IR LED controlled by an NPN transistor. The data format used here is an inverted RS232 protocol and has no current flow for the MARK information (e.g. stop bits).

### **3.8.6.2 Working Sequence**

The normal sequence for a measurement cycle is as follows:

- 1) The host starts a measurement sequence with the transmission of steady light. This time period is used for the initial charge-up of the charge capacitor, Cch.
- 2) When this capacitor has enough charge, which means a capacitor voltage (VC) of approximately 4 V is reached, then the reset-Schmitt-trigger switches the RST/NMI input of the MSP430 from low to high. The MSP430 program starts with execution
- 3) The MSP430 program initializes the system and signals its readiness to the host by the transmission of a defined code via the back channel (a second fiber-optic cable).
- 4) After the receive of the acknowledge, the host sends the first control instruction (data) to the MSP430.
- 5) The MSP430 executes the received control instruction and sends back the measured result to the host via the back channel.

6) Items 4 and 5 are repeated as often as needed by the host.

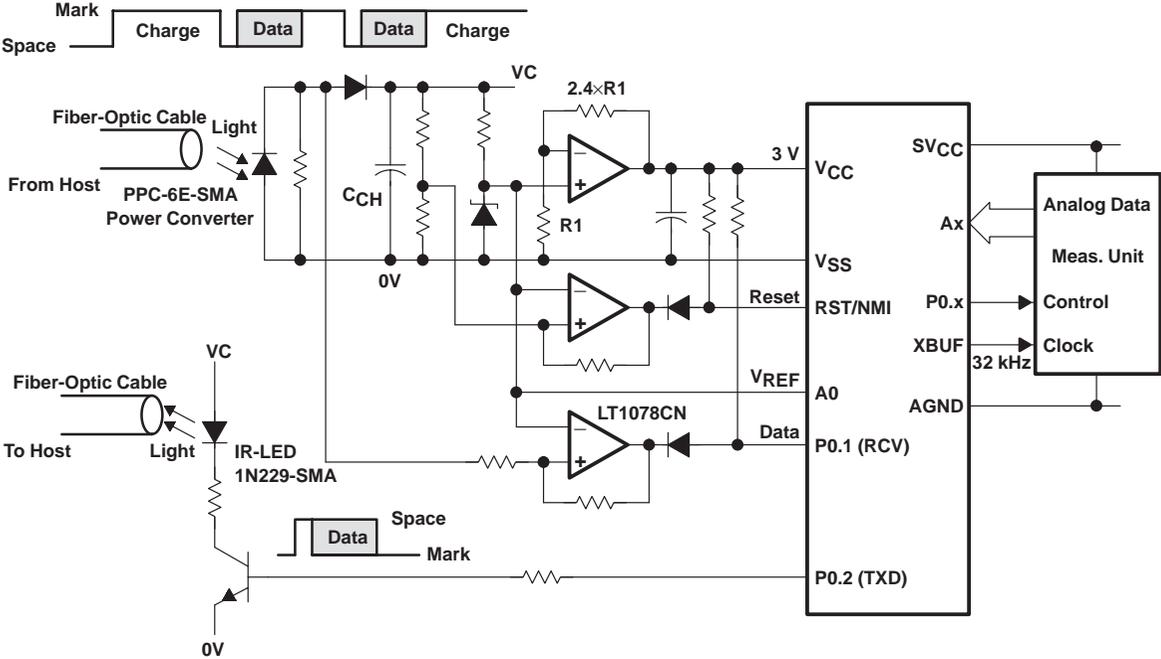


Figure 3-42. Supply via Fiber-Optic Cable

3.8.6.3 Conclusion

The illustrated concepts for supplying the MSP430 family with power demonstrate the numerous ways this can be done. Due to the extreme low power consumption of the MSP430 family, it is possible to supply them with all known power sources. Even fiber-optic cables can be used.