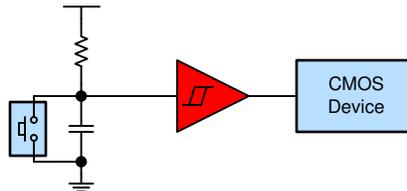


Debounce a Switch



Many physical switches can bounce for hundreds of microseconds after being pressed, while most logic devices respond in just a few nanoseconds. This can result in false triggers and erroneous output. By adding an appropriate debounce circuit between a button and a CMOS input, these bounces can be eliminated.



See more about this use case in the *Logic Minute* video [Debounce a Switch](#).

Design Considerations

- Select a time constant based on the bouncing characteristics of your switch
- Select a resistor based on power consumption, input voltage, or capacitor size limitations
 - Power consumption is calculated with the pullup voltage and resistor value: $P = V^2 \div R$
 - Input voltage is determined by voltage drop across the resistor caused by leakage into the device input. This is calculated with Ohm's Law: $V = I \times R$
 - Capacitor values can be limited due to package size

Time Constants for Common Resistor and Capacitor Values

Capacitor (µF)	Time Constant (ms) ⁽¹⁾		
	R = 10 kΩ	R = 100 kΩ	R = 1 MΩ
1	10	100	1000
0.1	1	10	100
0.01	0.1	1	10

(1) Time constant should be approximately half of the desired debounce time. This is commonly selected as 10 ms to give maximum debounce time while preventing humans from noticing the delay.

- [\[FAQ\] How does a slow or floating input affect a CMOS device?](#)
- Need additional assistance? Ask our engineers a question on the [TI E2E™ logic support forum](#)

Recommended Parts

Part Number	Automotive Qualified	V _{CC} Range	Type	Features
SN74LVC1G17-Q1	✓	1.65 V–5.5 V	Single Buffer	Schmitt-trigger inputs Over-voltage tolerant inputs to 5.5 V
SN74LVC1G17				
SN74AUP1G17		0.8 V–3.6 V	Single Buffer	Schmitt-trigger inputs Over-voltage tolerant inputs to 3.6 V Ultra low power

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated