



ABSTRACT

Changing output voltage on the fly may be needed in some particular applications such as running turbo mode or low-power mode. Some systems may require different supply voltages for each operation mode to achieve best performance. This application report describes how to adjust the TPS40322 regulated output voltage (V_{OUT}) on-the-fly by implementing the TPL0102-100 (100-k Ω end-to-end resistance, 256-taps digital potentiometers).

Table of Contents

1 Introduction	2
2 Circuit Description	2
2.1 Calculation for VOUT Settings.....	2
3 Setup TPL0102-100 EVM	4
3.1 Connection Block Diagram.....	4
3.2 Software GUI Setup.....	6
4 Conclusion	8

List of Figures

Figure 2-1. System Block Diagram.....	2
Figure 2-2. FB Network.....	2
Figure 3-1. Hardware Setup.....	4
Figure 3-2. TPL0102 EVM Board Connection.....	5
Figure 3-3. Charger Device Type.....	6
Figure 3-4. bq24773.bqz Target.....	7
Figure 3-5. Advanced Comm tab.....	7
Figure 3-6. Byte Read/Write Settings.....	8

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

This application note introduces a method to implement the TPS40322 device, changing the output voltage on-the-fly by sending an I2C command to set the TPL0102-100 digital potentiometer.

2 Circuit Description

This section provides the system block diagram, FB network circuit, and calculations for VOUT settings.

Figure 2-1 illustrates the system block diagram.

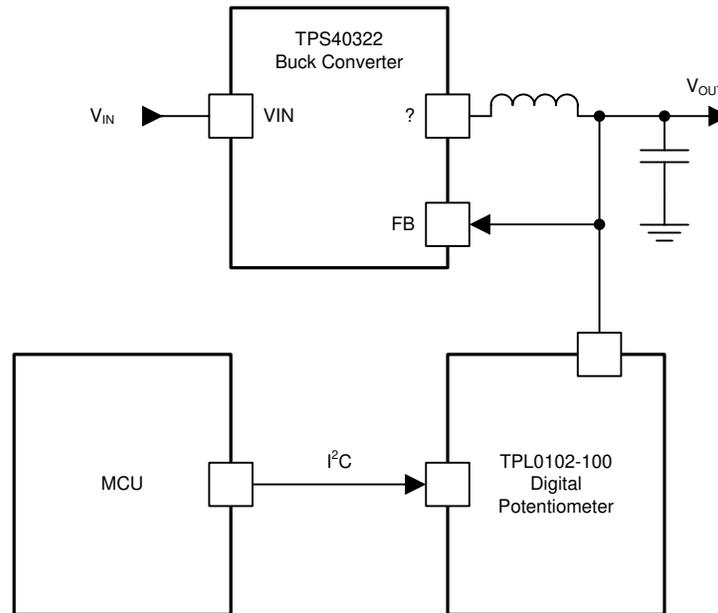


Figure 2-1. System Block Diagram

2.1 Calculation for VOUT Settings

Figure 2-2 shows the FB network circuit.

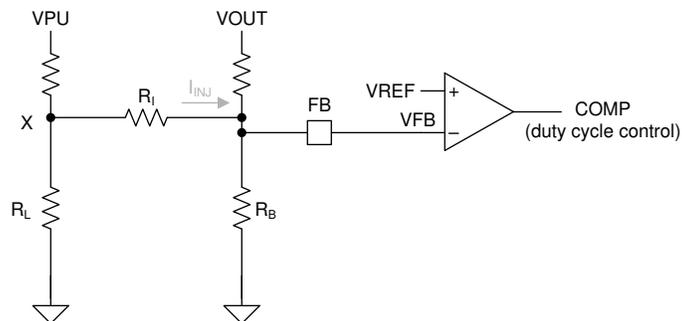


Figure 2-2. FB Network

Converter DC regulation forces $V_{FB} = V_{REF} = 0.6$ V. Therefore, the divider is injecting current i_{INJ} into the FB node to offset the output voltage.

1. Calculate V_{OUT} as a function of i_{INJ}

KCL at FB node:

$$\frac{V_{OUT} - V_{FB}}{R_T} + i_{INJ} = \frac{V_{FB}}{R_B} \quad (1)$$

Rearrange and simplify as [Equation 2](#) shows:

$$V_{OUT} = V_{FB} \left(1 + \frac{R_T}{R_B} \right) - i_{INJ} \times R_T \quad (2)$$

2. Solve for i_{INJ}

$$i_{INJ} = \frac{V_x - V_{FB}}{R_i} \quad (3)$$

KCL @ X to solve for V_x :

$$\frac{V_{PU} - V_x}{R_H} = \frac{V_x}{R_L} + \frac{V_x - V_{FB}}{R_i} \quad (4)$$

Rearrange and simplify as [Equation 5](#) shows:

$$V_x = \frac{V_{PU} \times R_L \times R_i + V_{FB} \times R_L \times R_H}{R_H \times R_i + R_L \times R_H + R_L \times R_i} \quad (5)$$

3. Substitute:

$$V_{OUT} = V_{FB} \left(1 + \frac{R_T}{R_B} \right) - \left(\frac{V_x - V_{FB}}{R_i} \right) \times R_T \quad (6)$$

where V_x equals [Equation 5](#).

These calculations are integrated in the [TPS40322 Resistor Divider Vout Offset Calculator](#) tool.

3 Setup TPL0102-100 EVM

R_H and R_L in Figure 2 are presenting the R_{HW} , R_{WL} of the TPL0102 device. An I2C master connects to the TPL0102 and is required to get control the R_{HW} , R_{WL} of the TPL0102. Figure 3-1 shows a connection example which uses the TI EV2400 tool as a I2C master to set the R_{HW} , R_{WL} values via the bqStudio GUI.

3.1 Connection Block Diagram

This section details the hardware equipment and setup.

Hardware Equipment:

- PC or laptop
- EV2400
- TPL0102 EVM
- DC power supply

Hardware Setup:

1. Insert header caps in J1, J2, and J3 to set A2, A1, and A0, respectively. The board is shipped with the following settings: A2 = 0, A1 = 0, and A0 = 1.
2. Connect the I2C bus of the host(EV2400) to the board via connector J14 (pins marked SCL, SDA). Also connect the GND pin on J14 to GND of the host processor.
3. Apply the positive supply voltage 2.7 V–5.5 V(VDD) to center pin of J4. Apply GND to lowest pin of J4.
4. Apply the negative supply voltage (VSS) to J5. The board is shipped with a header cap that connects VSS to GND.
5. Write to the TPL0102 data registers per protocol in the [TPL0102 Two 256-Taps Digital Potentiometers With Non-Volatile Memory Data Sheet](#).
6. Measure resistance between H, W, L terminals as appropriate on headers J8–J13.

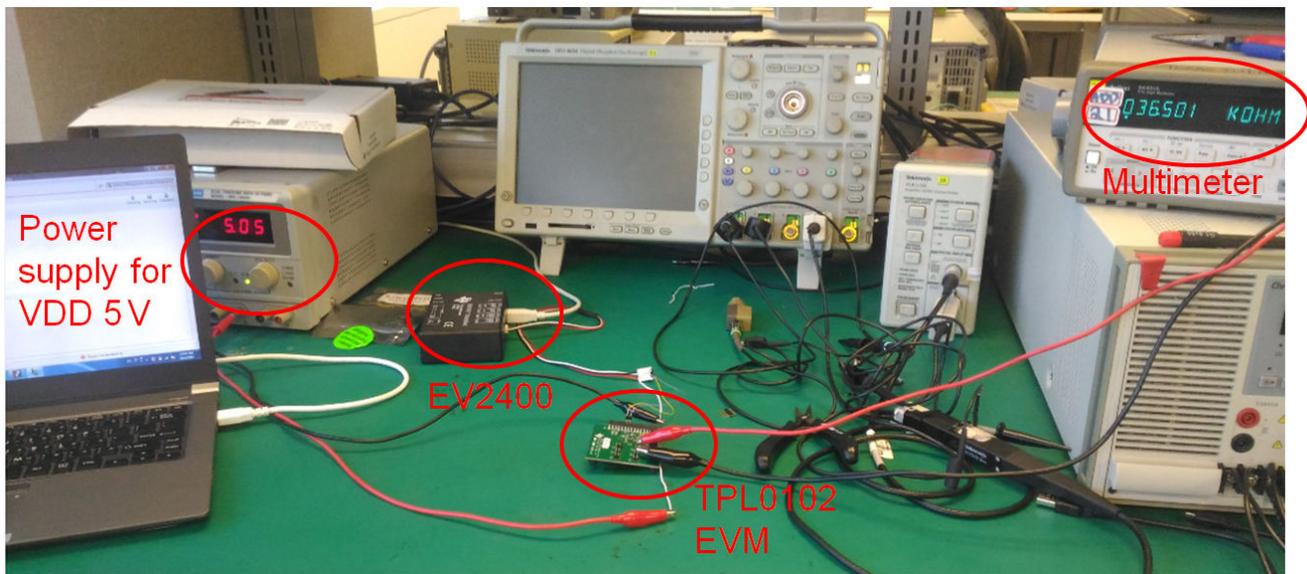


Figure 3-1. Hardware Setup

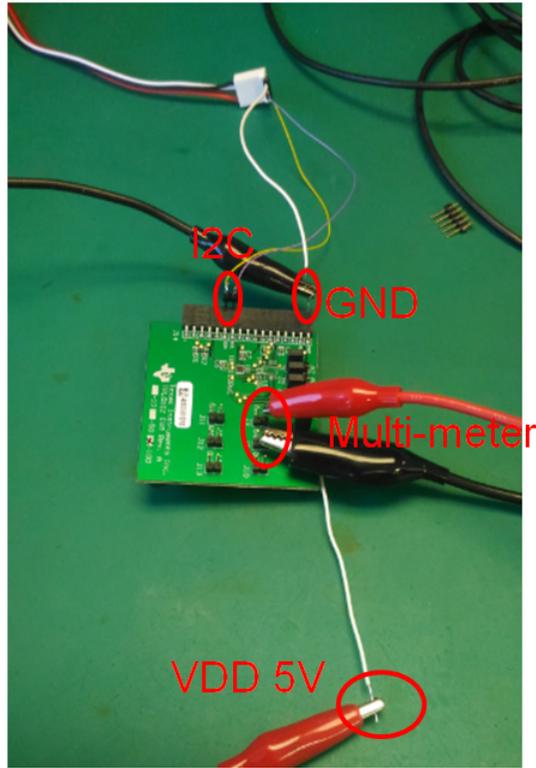


Figure 3-2. TPL0102 EVM Board Connection

3.2 Software GUI Setup

Utilize the [bqStudio GUI](#) for read/write the I2C commands to I2C slave device. Use the following procedure to set up the bqStudio GUI to control the TPL0102-100EVM and adjust as a variable resistor. [Figure 3-5](#) second (fourth) [Figure 3-6](#)

1. Open BqStudio, select *Charger*, and click the *Next* button

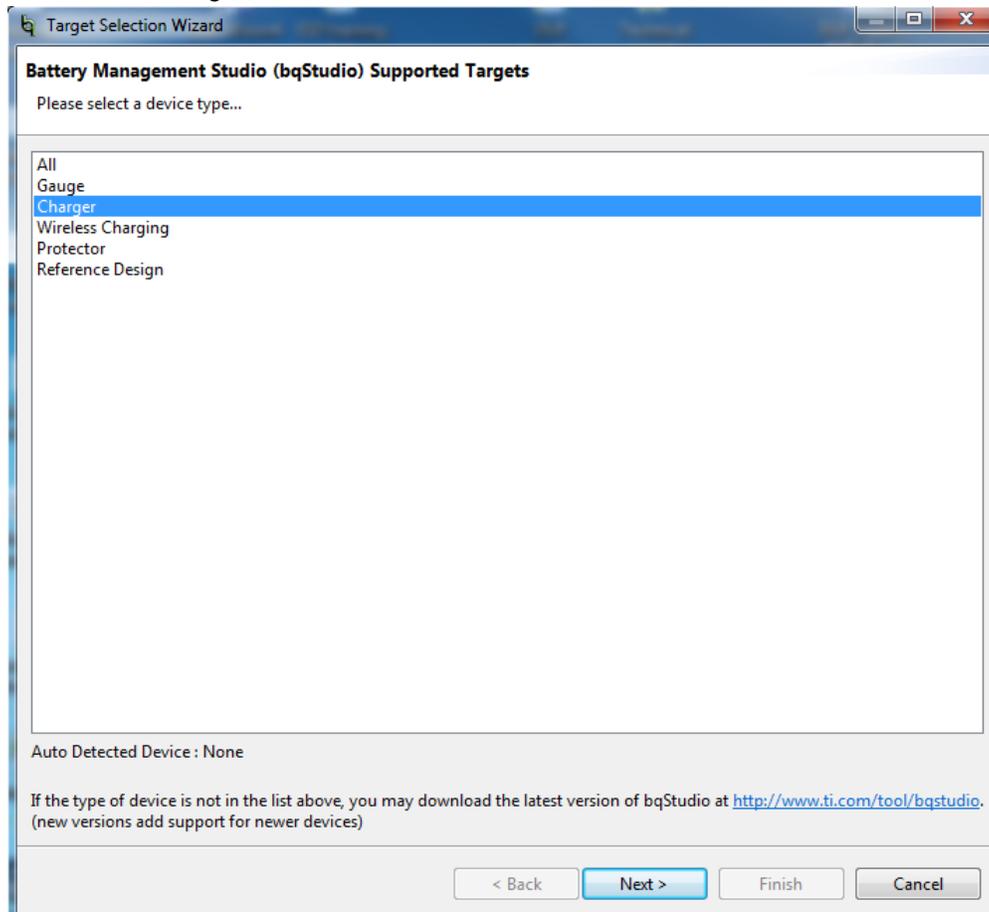


Figure 3-3. Charger Device Type

2. Select the *bq24773.bqz* target and click the *Finish* button

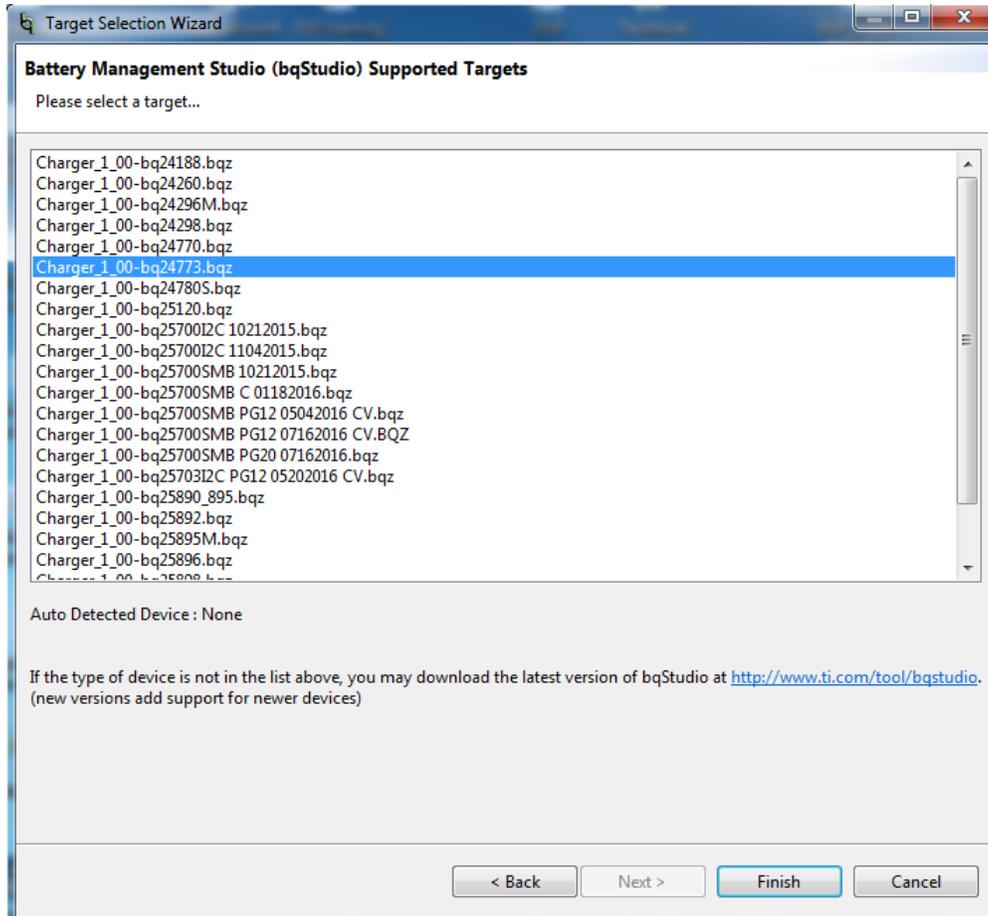


Figure 3-4. bq24773.bqz Target

3. Select the *Advanced Comm* tab

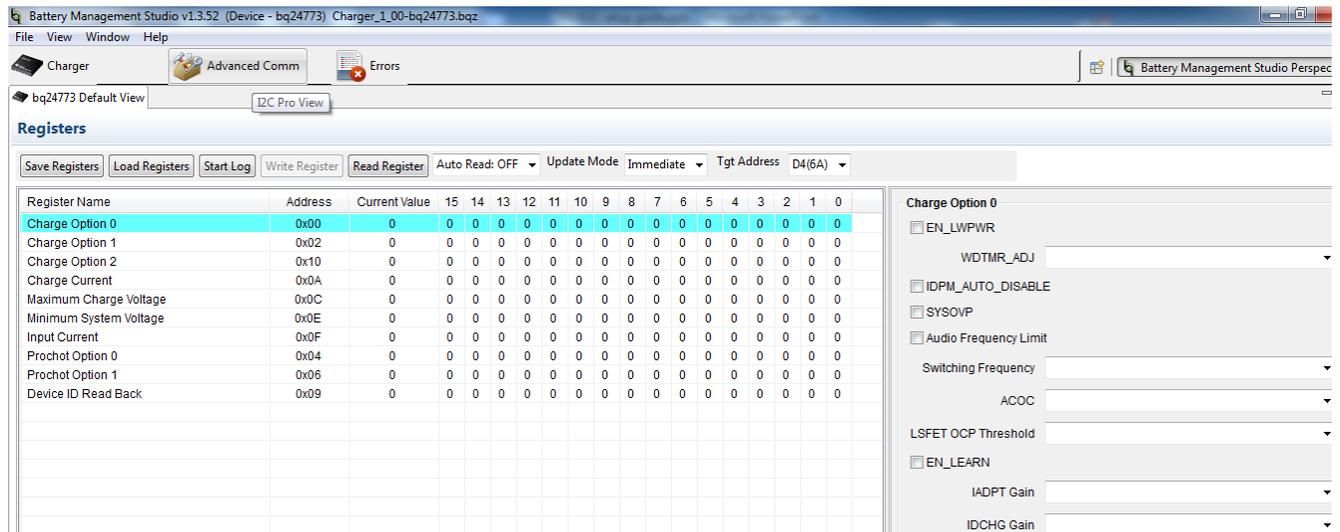


Figure 3-5. Advanced Comm tab

4. Read/Write I2C command to TPL0102-100 EVM

illustrates using the *Advanced Comm* tab to set the device address to 0xA0h and read/write 1 byte data from and to the register 0x00h for accessing the Wiper Resistance Register of Potentiometer A.

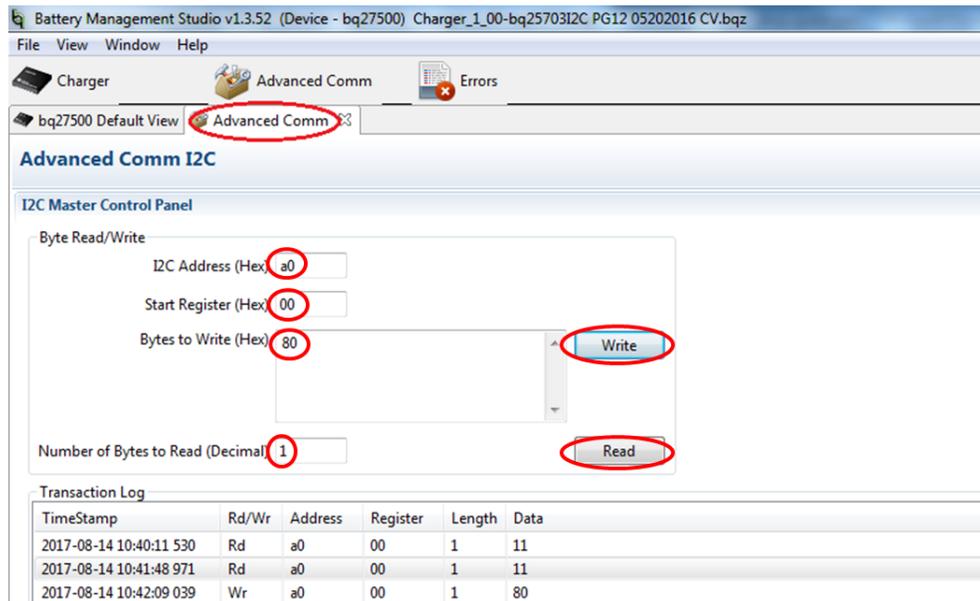


Figure 3-6. Byte Read/Write Settings

4 Conclusion

1. Typically the absolute value of a silicon resistor divider may not very accurate (approximately $\pm 20\%$), but the ratio is very accurate. Use some parallel resistors with the TPL0102 to control the absolute values.
2. The TPL0102 device probably changes the resistance quickly. It would be better to have some capacitance in the circuit to slow down the Vref step change, so regulator does not overshoot.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated