

TI Designs: PMP9775 Reference Guide

PMOLED Display Power Supply with TPS61046



TI Designs

TI Designs are analog solutions created by TI's analog experts. Reference designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Circuit Description


A PMOLED display is mostly used in the wearable device because of its low power consumption and low cost. This reference design is to demonstrate the TPS61046's application in powering a PMOLED display. It includes a MCU MSP430G2230, boost converter TPS61046 and a 32 x 128 pixel PMOLED display. The display shows a picture programed by the MCU when the reference design is powered up.

Design Resources

- [Design Page](#) All Design files
- [TPS61046](#) Datasheet
- [MSP430G2230-EP](#) Datasheet



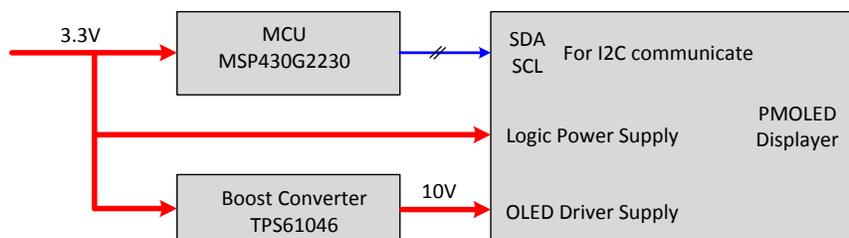[Ask The Analog Experts](#)
[WEBENCH@ Design Center](mailto:WEBENCH@Design.Center)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
WEBENCH is a registered trademark of Texas Instruments

Contents

1	Introduction	3
2	Design Description	3
	2.1 Boost Converter Solution.....	3
	2.2 MCU Solution	4
3	Bench Test Result	5
4	Schematic, Bill of Materials and PCB Layout	6
	4.1 Schematic	6
	4.2 Bill of Material.....	7
	4.3 Layout	7

List of Figures

Figure 1:	Block Diagram of the Reference Design	3
Figure 2	PMOLED Display	3
Figure 3	TPS61046 Boost Converter Schematic.....	4
Figure 4	Schematic of the MCU	5
Figure 5	Output Waveform at Displaying Designed Content.....	5
Figure 6	Output Waveform at All Pixels On	5
Figure 7	Efficiency of TPS61046	6
Figure 8	Schematic of the Reference Design.....	6
Figure 9	Layout of the Reference Design.....	8

1 Introduction

The Reference Design (RD) is to demonstrate one of the TPS61046's applications in powering a PMOLED display which is mostly used in the wearable device. The TPS61046 is a highly integrated boost converter specially designed for this application. Its true shutdown feature disconnects the input and output when the device is disable. This feature helps to reduce the current consumption to 100nA when the display is off. The TPS61046's input voltage ranges from 1.8 V to 5.5 V and output voltage up to 28 V.

In the following chapters, the operation principle of the RD is described firstly. Then the output voltage waveforms in different conditions are measured. Finally, the schematic, BOM and PCB are provided.

2 Design Description

The RD's block diagram is shown in the Figure 1. The input voltage is set to 3.3V for the MCU and the PMOLED display logic power supply. In real application where the system is powered by lithium-ion battery, the battery voltage can power TPS61046 directly, while a LDO or BUCK converter should be added to steps down the battery voltage to 3.3 V for the MCU and the display logic power supply. The part number of the display is VGM128032A5W01 from Visionox.

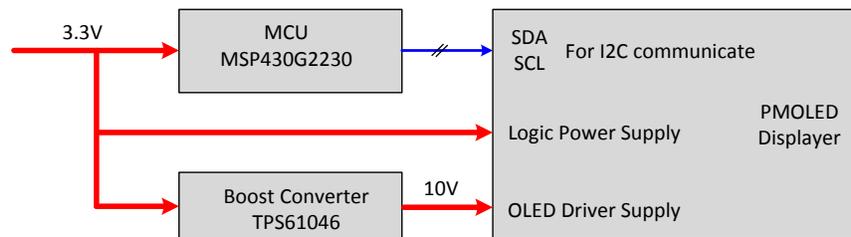


Figure 1: Block Diagram of the Reference Design

The output voltage of the TPS61046 is set to 10 V for the display's driver supply according the display's datasheet. The initialization and screen content of the display is programmed by the MCU through I2C communication line.

After the RD is powered, the MCU enables the boost converter and the display, and the display will show the content programmed by the MCU, as in Figure 2.

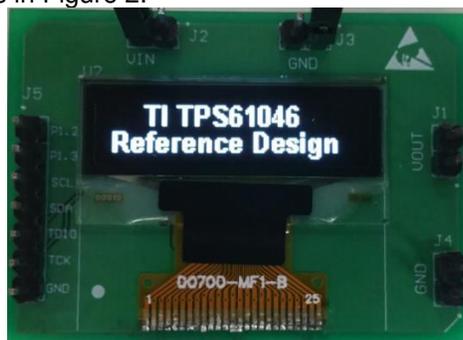


Figure 2 PMOLED Display

2.1 Boost Converter Solution

The schematic of the boost converter solution based on the TPS61046 is shown in Figure 3. The detail operating principle, pin functions and electrical characteristics of the TPS61046 are described in the datasheet (SLVSCQ7).

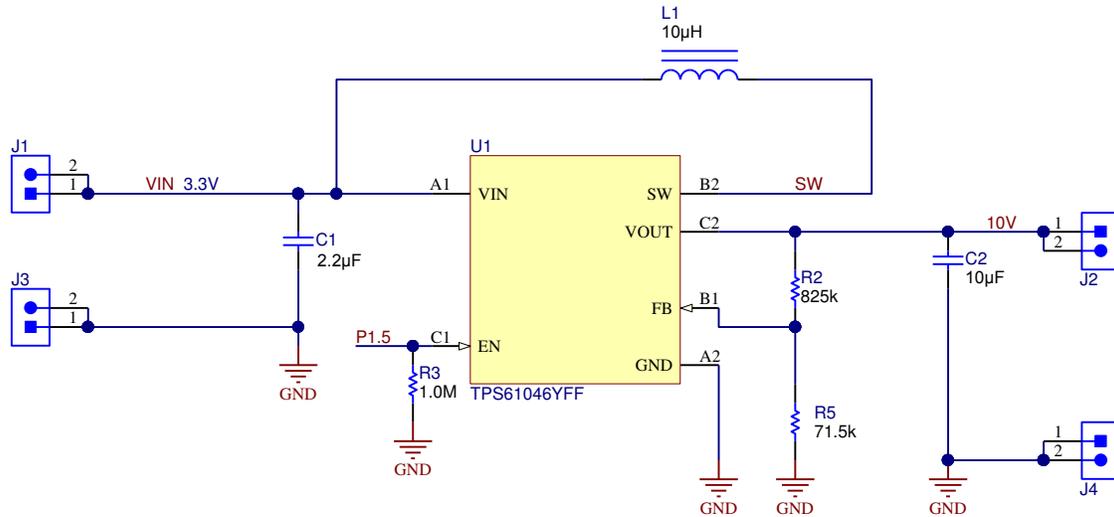


Figure 3 TPS61046 Boost Converter Schematic

The current requirement of the PMOLED display in “Normal Mode” can be calculate by formula (1), which $P_{t_{MAX}}$ is the maximum output power when all pixels is on. The “NORMAL MODE” is defined in the datasheet of VGM128032A5W01 as “driving voltage 10V, Contrast setting 0x35, Frame rate 104Hz, and Duty setting 1/32”.

$$I_{OUT} = \frac{P_{t_{MAX}}}{V_{OUT}} = \frac{130mW}{10V} = 13mA \quad (1)$$

The maximum input current of the boost converter can be calculated by formula (2), where η is efficiency of the boost converter.

$$I_{IN_MAX} = \frac{I_{OUT} \cdot V_{OUT}}{V_{IN} \cdot \eta} = \frac{130mW}{3.3V \times 0.8} \approx 49mA \quad (2)$$

The minimum input peak current of TPS61046 is 600mA, higher than the input current requirement. So the TPS61046 is good for the application.

The 10µH inductor 1239AS-H-100M (size 2.5x2x1.2 mm) from TOKO is used for the boost converter. A inductor with larger inductance and small ESR help to improve the efficiency but could result in larger size and higher cost.

The value of the input and output capacitors can be selected following the “Recommended Operating Condition” table in the TPS61046 datasheet. Care must be taken in evaluating a ceramic capacitor’s effective capacitance, because the effective capacitance of a ceramic capacitor could significantly decrease under the increase of dc bias voltage.

A 2.2-µF capacitor with 1.7-µF effective capacitance at 3.3V is selected for the input capacitor, and 10-µF capacitor with 2-µF effective capacitance at 10V is selected for the output capacitor.

2.2 MCU Solution

The schematic of the MCU MSP430G2230-EP is showed in Figure 4. The MSP430G2230 is an ultra-low-power mixed signal microcontroller with four I/O pins and a built-in communication capability using synchronous protocols (SPI or I2C) and a 10-bit A/D converter. In the reference design, the P1.2 and P1.5 I/O pins are used to control the display and the boost converter. The P1.6 and P1.7 pins are configured to the I2C function for communication with the display.

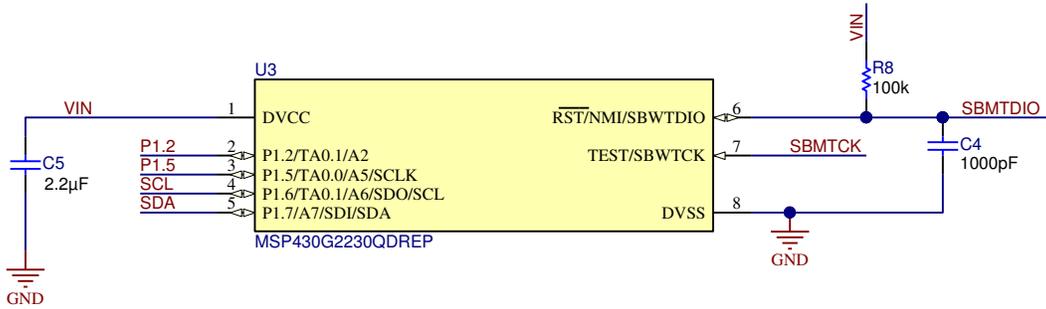


Figure 4 Schematic of the MCU

3 Bench Test Result

Figure 5 shows the waveform of the TPS61046's output voltage and output current when the PMOLED display is set to "NORMAL MODE" and shows "TI TPS61046 Reference Design" as in Figure 2.

From Figure 5, the TPS61046 output voltage is stable and output ripple is approximate 20mV.

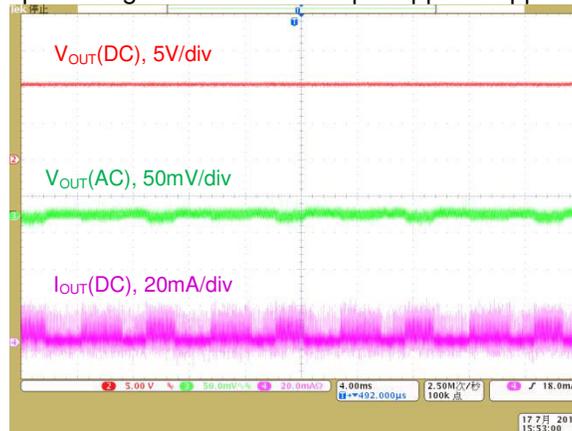


Figure 5 Output Waveform at Displaying Designed Content

Figure 6 shows the waveform of TPS61046's output voltage and current when all pixels of the PMOLED are on at "NORMAL MODE". The output current of TPS61046 is approximate 10mA, and the peak to peak ripple of output voltage is lower than 20mV.

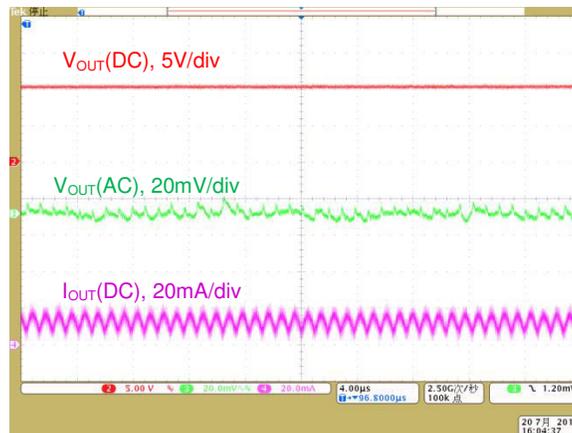


Figure 6 Output Waveform at All Pixels On

The efficiency of the TPS61046 at VOUT=10V, VIN=3V, 3.6V, 4.0V condition is shown in Figure 7. The data is measured with the inductor 1239AS-H-100M (size 2.5x2x1.2 mm) from TOKO.

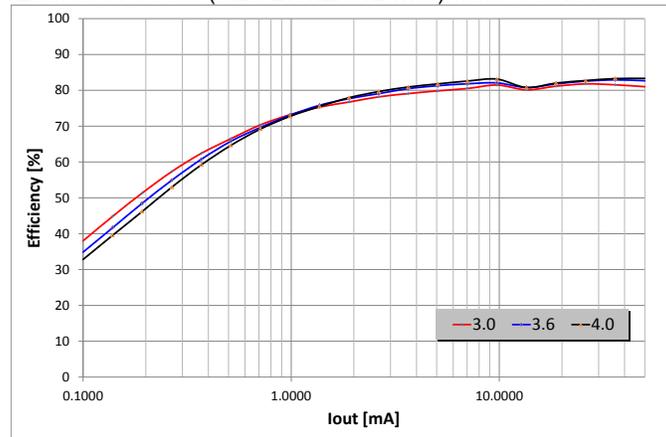


Figure 7 Efficiency of TPS61046

4 Schematic, Bill of Materials and PCB Layout

4.1 Schematic

The schematic of the whole reference design is shown in Figure 8. Some components are not installed and are placed for debugging. The R7 is to change the PMOLED's I2C address. The C7 and C9 are tantalum capacitors which can replace the ceramic capacitor C6 and C8 if the ceramic capacitor generates high acoustic noise.

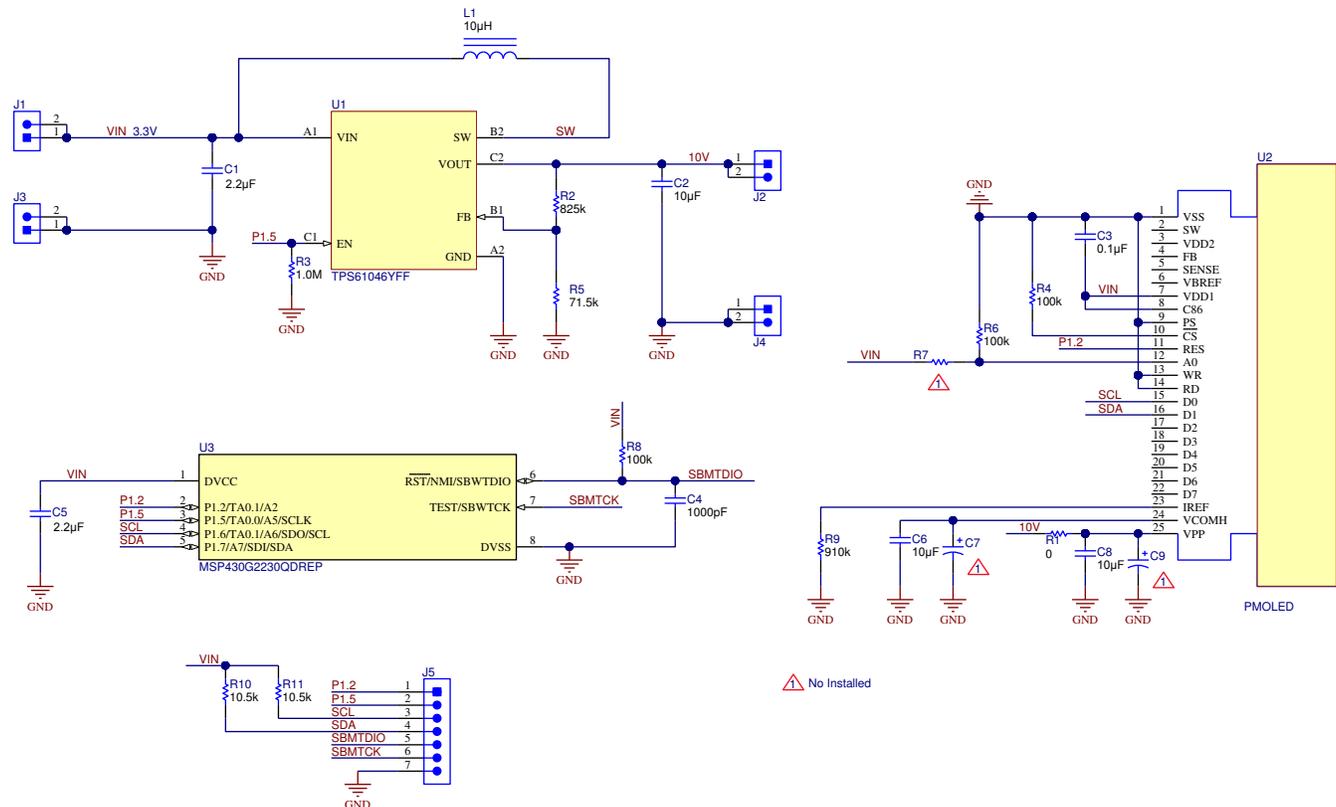


Figure 8 Schematic of the Reference Design

4.2 Bill of Material


The bill of material (BOM) of the reference design is listed at table 1.

Table 1 Bill of Material


Designator	Quantity	Value	Description	Package	PartNumber	Manufacturer
C1, C5	2	2.2uF	CAP, CERM, 2.2 μ F, 10 V, +/- 10%, X5R, 0603	0603	GRM188R61A225KE34D	MuRata
C2, C6, C8	3	10uF	CAP, CERM, 10 μ F, 25 V, +/- 20%, X5R, 0603	0603	GRM188R61E106MA73	MuRata
C3	1	0.1uF	CAP, CERM, 0.1 μ F, 6.3 V, +/- 10%, X7R, 0603	0603	GRM188R70J104KA01D	MuRata
C4	1	1000pF	CAP, CERM, 1000 pF, 50 V, +/- 10%, X5R, 0603	0603	GRM188R61H102KA01D	MuRata
C7, C9	2	4.7uF	CAP, TA, 4.7 μ F, 16 V, +/- 10%, 0.8 ohm, SMD	3528-21	T495B475K016ZTE800	Kemet
L1	1	10uH	Inductor, Shielded, Ferrite, 10 μ H, 1 A, 0.4 ohm, SMD	2.5x1.2x2mm	1239AS-H-100M	Toko
R1	1	0	RES, 0, 5%, 0.125 W, 0805	0805	CRCW08050000Z0EA	Vishay-Dale
R2	1	825k	RES, 825 k, 1%, 0.1 W, 0603	0603	CRCW0603825KFKEA	Vishay-Dale
R3	1	1.0Meg	RES, 1.0 M, 5%, 0.1 W, 0603	0603	CRCW06031M00JNEA	Vishay-Dale
R4, R6, R7, R8	4	100k	RES, 100 k, 1%, 0.1 W, 0603	0603	CRCW0603100KFKEA	Vishay-Dale
R5	1	71.5k	RES, 71.5 k, 1%, 0.1 W, 0603	0603	RC0603FR-0771K5L	Yageo America
R9	1	910k	RES, 910 k, 1%, 0.1 W, 0603	0603	RC0603FR-07910KL	Yageo America
R10, R11	2	10.5k	RES, 10.5 k, 1%, 0.1 W, 0603	0603	CRCW060310K5FKEA	Vishay-Dale
U1	1		28-V Output Voltage Boost Converter, YFF0006AAAA	YFF0006AAAA	TPS61046YFF	Texas Instruments
U2	1		128x32 dot matrix monochrome OLED display module		VGM128032A5W01	visionox
U3	1		MIXED SIGNAL MICROCONTROLLER, D0008A	D0008A	MSP430G2230QDREP	Texas Instruments

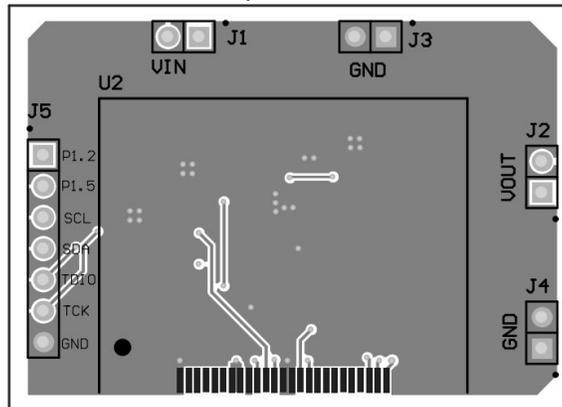4.3 Layout

The PCB layout of the reference design evaluation board is shown in Figure 9. The display is on the top layer, and the boost converter, MCU and their external components are on the bottom layer.



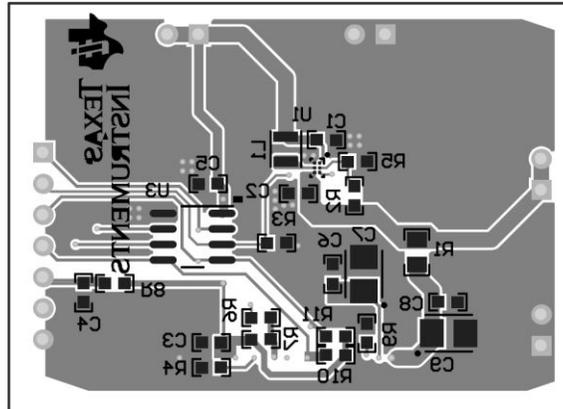(a) Top Layer of the Reference Design PCB



(b) Bottom Layer of the Reference Design PCB

Figure 9 Layout of the Reference Design

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated