

Bidirectional Current Sensing Circuit With Unidirectional Current Shunt Monitor



Amplifiers

Design Goals

The design goal is the realization of a bidirectional current sensing circuit with a unidirectional current sense amplifier.

Input		Output		Supply		Error
I_{Min}	I_{Max}	$V_{\text{out, min}}$	$V_{\text{out, max}}$	V_{CC}	V_{EE}	Over input current range
-10 A	+10 A	About 100 mV	About 4 V	5 V	0 V	$\leq 3\%$ at room temperature $\leq 5\%$ from 0°C to 85°C

Design Description


This design utilizes a unidirectional current shunt monitor to measure a bidirectional load current. This concept only works for low-side current sensing applications. The load current range is from -10 A to +10 A, the output range is from 100 mV to 4 V, and the supply voltages are 5 V and ground.

Design Notes

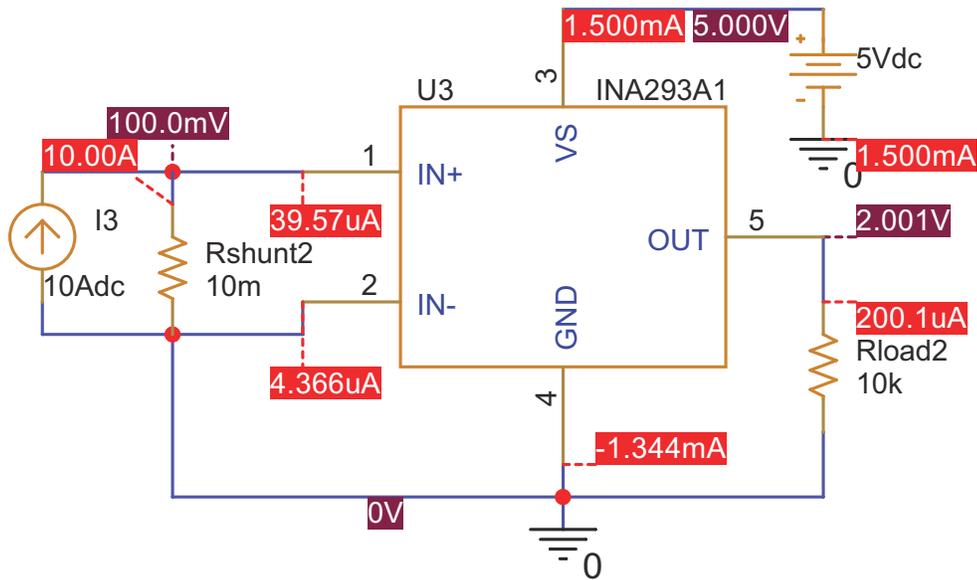1. Analyze unidirectional current measurement circuit
2. Change the circuit to measure bidirectional current.
Use 0.1% tolerance resistors for R1 and R2 with a temperature coefficient of 10 ppm. An example, is the TNPW0603e3 resistor from Vishay®
3. Error calculation over input current and temperature
4. As an example, the INA293A1 amplifier is used in this design note, but the concept is valid for many different current shunt monitors with input-bias-current information available and capable of low-side measurement
5. Be sure to Kelvin-connect the shunt resistor
6. Conduct a 1-point offset calibration at 25°C to compensate for resistor tolerances

Design Steps


- Unidirectional current measurement standard circuit:



Standard Unidirectional Current Sensing - PSpice® for TI Simulation

Reversing the current in the previous example results in a negative voltage at the IN+ pin of the INA293A1 which will not disturb the part but results in an output voltage close to 0 V.

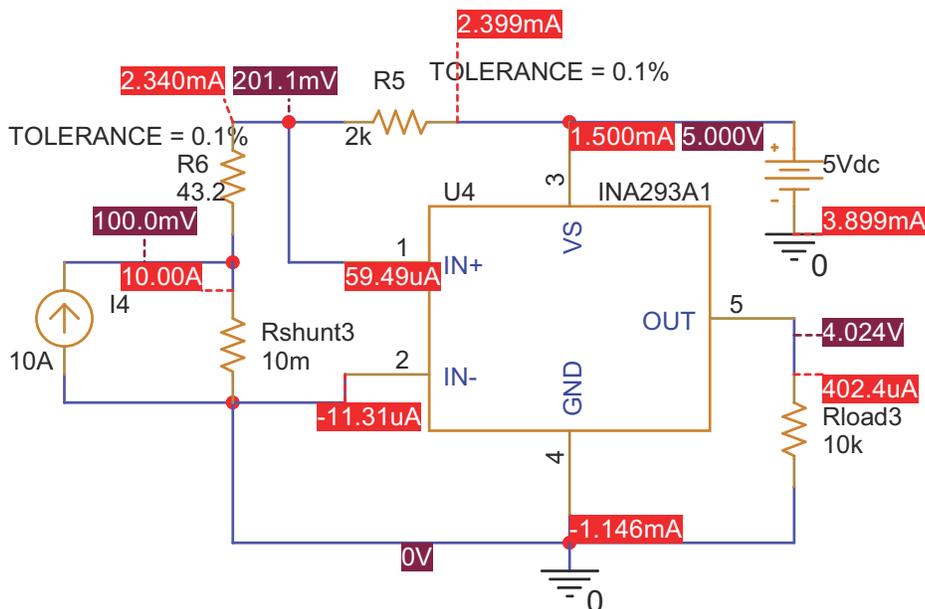
- Biasing the input voltage of the INA293A1 by 100 mV makes it possible to measure a bidirectional current from –10 A to 10 A with an input voltage from about 0 to 200 mV and an output voltage from close to 0 V to 4 V:



Modified Circuit With Biased Shunt Monitor Input Voltage

Choosing R1 with 2 kΩ results in an error current of $I_{\text{error}} = (5 \text{ V} - 0.201 \text{ V}) / 2 \text{ k}\Omega = 2.4 \text{ mA}$ which can be compensated after digitization in μC SW. To calculate R2, the input bias current of the INA293A1 must be considered. The input bias current into IN+ is taken from the data sheet: At 200 mV the current is typically about 60 μA (see the red dotted lines in *INA239x1 Input Bias Current vs V_{SENSE}*), but could vary by $\pm 20\%$.

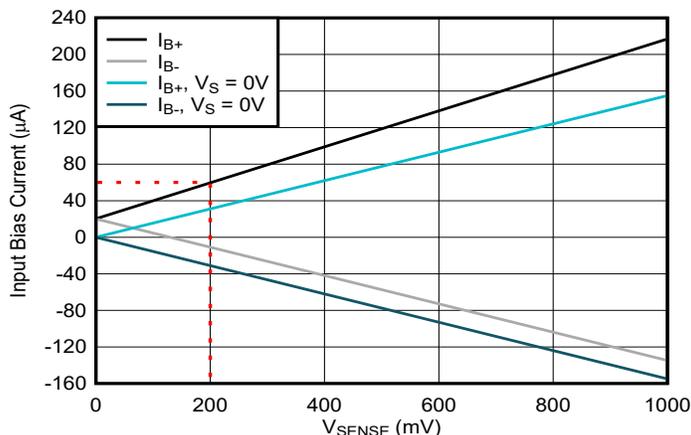The simulation in the previous circuit shows the typical value. Because the IN– pin is connected to ground, this current can be ignored.



INA239x1 Input Bias Current vs V_{SENSE}


$R2 = 100 \text{ mV} / (2.4 \text{ mA} - 60 \text{ } \mu\text{A}) = 42.7 \text{ } \Omega$. The closest E96 value is 43.2 Ω which results in a slightly higher input voltage of 201.1 mV as the [Error Calculations R1 MAX R2 MIN](#) simulation shows. Choosing the higher value for R2 will also prevent the input going negative in case a current of –10 A is applied.

- R1 and R2 are the only additional error contributors compared to a unidirectional measurement. To get the worst-case values for the input voltage of the current shunt monitor in the [Error Calculations R1 MAX R2 MIN](#) schematics, a DC sweep from –10 A to +10 A is performed using [PSPICE-FOR-TI](#).

Design Results


To calculate the worst-case error over temperature, check these two scenarios:

- R1max in combination with R2min

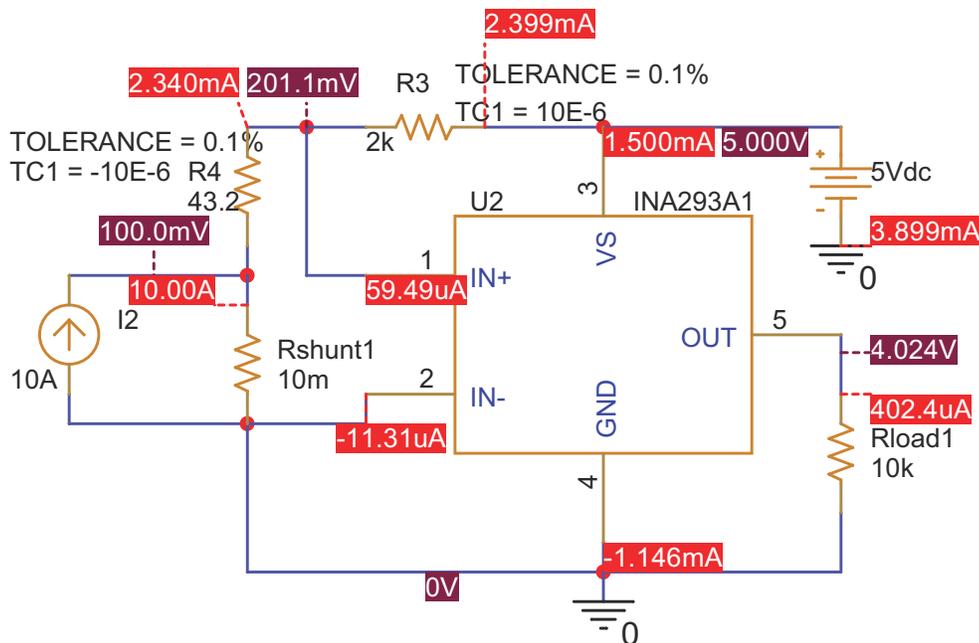

Error Calculations R1 MAX R2 MIN

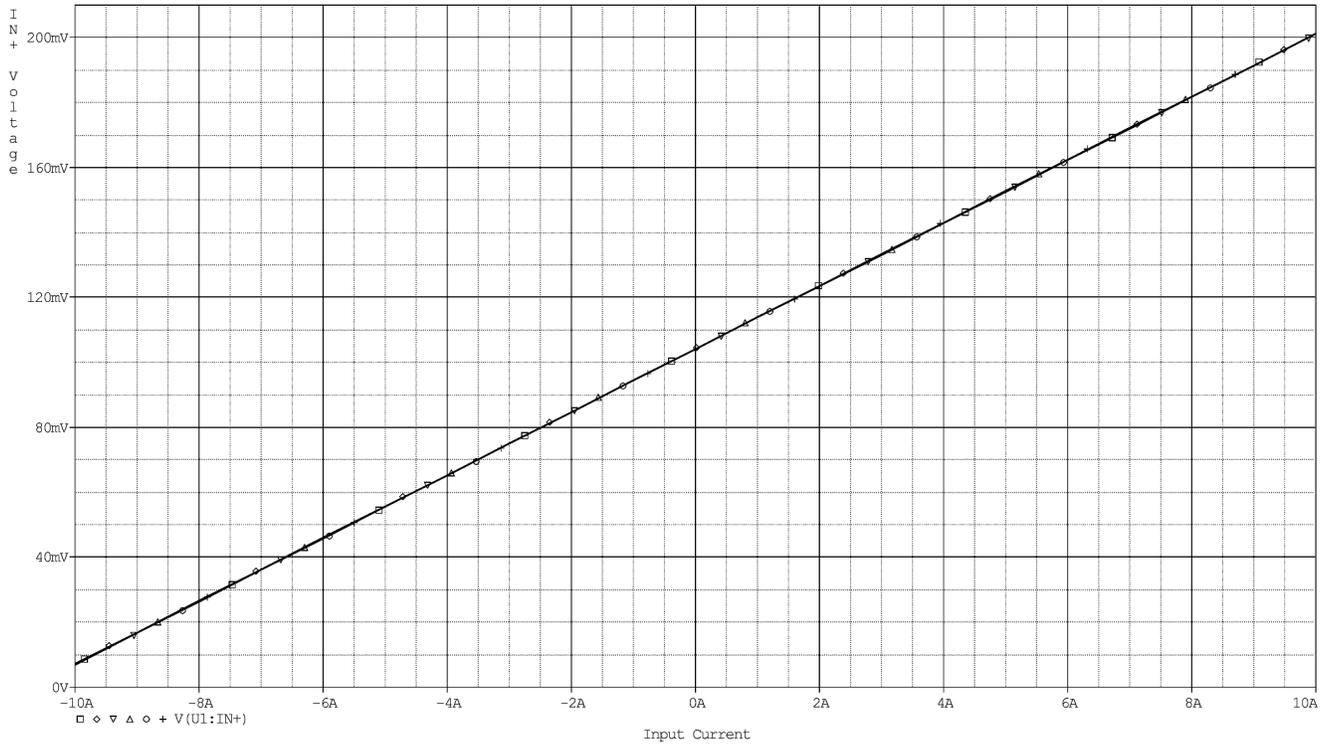Error Calculations:
All cases are simulated:




IN+ Voltage vs Input Current

Measurement Table

Measurements (mV)	(1)	(2)	(3)	(4)	(5)	(6)
Max(V(U1:IN+))	201.16	201.36	201.11	201.31	200.99	201.19
Min(V(U1:IN+))	7.01	7.22	6.96	7.17	6.84	7.04

- (1) Nominal Values at 0°C
- (2) Worst-Case Values at 0°C
- (3) Nominal Values at 27°C
- (4) Worst-Case Values at 27°C
- (5) Nominal Values at 85°C
- (6) Worst-Case Values at 85°C

2. R1min in combination with R2max

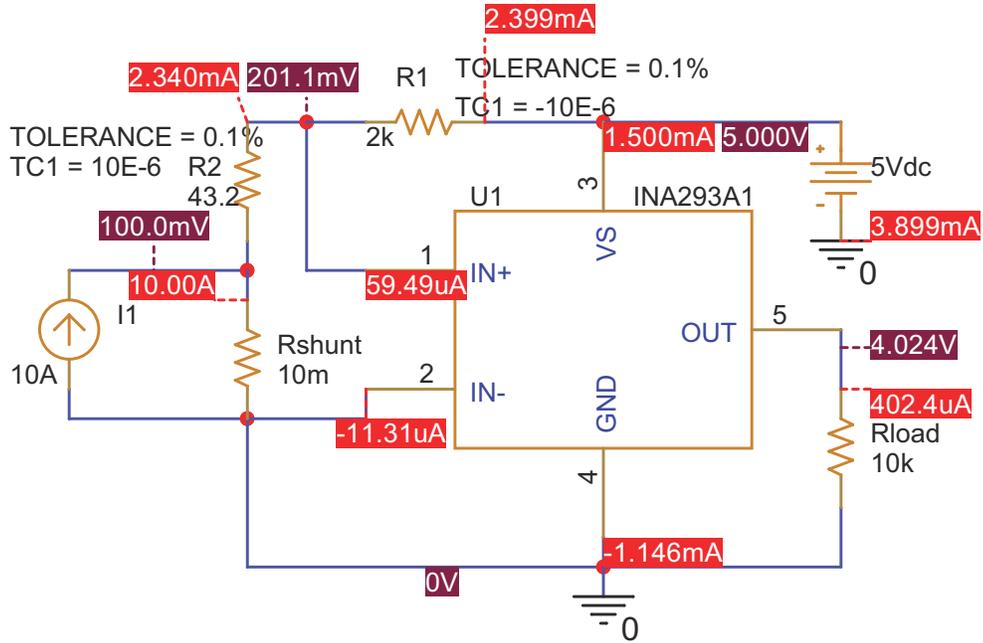

R1 MIN R2 MAX

The input-voltage vs. input-current plot looks almost the same as under *R1max in combination with R2min*.

Measurement Table

Measurements (mV)	(1)	(2)	(3)	(4)	(5)	(6)
Max(V(U1:IN+))	201.06	201.25	201.11	201.31	201.23	201.42
Min(V(U1:IN+))	6.90	7.11	6.96	7.17	7.08	7.29

- (1) Nominal Values at 0°C
- (2) Worst-Case Values at 0°C
- (3) Nominal Values at 27°C
- (4) Worst-Case Values at 27°C
- (5) Nominal Values at 85°C
- (6) Worst-Case Values at 85°C

Error at 27°C Room Temperature

Because the difference between the worst-case (column 4) and nominal (column 3) curve is constant, this results in an error caused by R1 and R2 at 27°C of

$$201.31 \text{ mV} / 201.11 \text{ mV} - 1 = 0.1\% \text{ at } +10 \text{ A and}$$

$$7.17 \text{ mV} / 6.96 \text{ mV} - 1 = 3\% \text{ at } -10 \text{ A.}$$

Error Over Temperature Range

From the measurement tables, the minimum and maximum input voltages at IN+ are:

- -10 A: 6.84 mV and 7.29 mV, highlighted in green in the measurement tables
- +10 A: 200.99 mV and 201.42 mV, highlighted in blue in the measurement tables

Summary of Errors

Input Current	Error at Room Temperature 27°C	Error from 0°C to 85°C
-10 A	+3%	+4.47% -1.72%
+10 A	+0.1%	+0.15% -0.06%

Because the delta of the worst-case voltages at V_{IN} stays constant over the whole current range, the error becomes smaller with higher input voltage.

V_{OUT} can be calculated with V_{IN} multiplied by 20, the gain of the INA293A1:

$$V_{out,min} = 6.84 \text{ mV} \times 20 = 137 \text{ mV and } V_{out,max} = 201.42 \text{ mV} \times 20 = 4.03 \text{ V which meets the design goal.}$$

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Download the PSpice files for this circuit – www.ti.com/lit/zip/SBOA529.

For more information on the INA293 device, see the [INA293 –4-V to 110-V, 1-MHz, High-Precision Current Sense Amplifier](#) data sheet.

Additional Resources

- PSpice® for TI design and simulation tool: [PSPICE-FOR-TI](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated