

Chris Glaser



Programmable logic controllers (PLCs) are more and more common in industrial automation systems. Controlling all sorts of machines in every conceivable manufacturing environment requires programmability for various functions, from moving the valves on a mixing tank in a chemical plant to controlling the speed on conveyer belts on a manufacturing line. The same PLC card can be used for multiple, different processes; the only difference is the programmed instructions on a given PLC unit.

The programmability and data retention of these programmed instructions sometimes requires a backup power source to store enough energy to properly power down the PLC during a sudden input voltage loss. Such a power loss occurs frequently in PLC cards which are hot-plugged into a rack-mount type of system.

In order to provide a proper power down, energy must be stored on the PLC card. The simplest way to do this is to take the input voltage and directly drive a capacitor bank. But, this requires a larger capacitor bank than what you'd need if the input voltage was boosted with the capacitors storing the energy at a higher voltage. Then, the system must also support operation at this higher, stored voltage, complicating the system design and increasing its cost.

The [PMP9761](#) TI Designs reference design provides a “both/and” solution to this dilemma. A buck-boost converter used bi-directionally boosts both the input voltage to the storage capacitors and steps down the capacitor voltage to the system. The system power supplies remain the same, with just the capacitor bank and buck-boost converter added to provide the [backup function](#). This simple and straightforward implementation provides an essential function for some PLCs.

The same architecture is useful for any system that needs to properly shut down, even when their input supply voltage is removed, as well as for systems that need to ride through a brown out of the input bus. Such mission-critical systems might include medical devices, sensors and monitoring systems in a factory, or fail-safe user safety systems like conveyor belt disconnect devices. In these systems, reliable operation during input power transients is required or the system must enter a known safe state upon sudden removal of its power source. Storing energy in a backup power system is one method to achieve both of these goals.

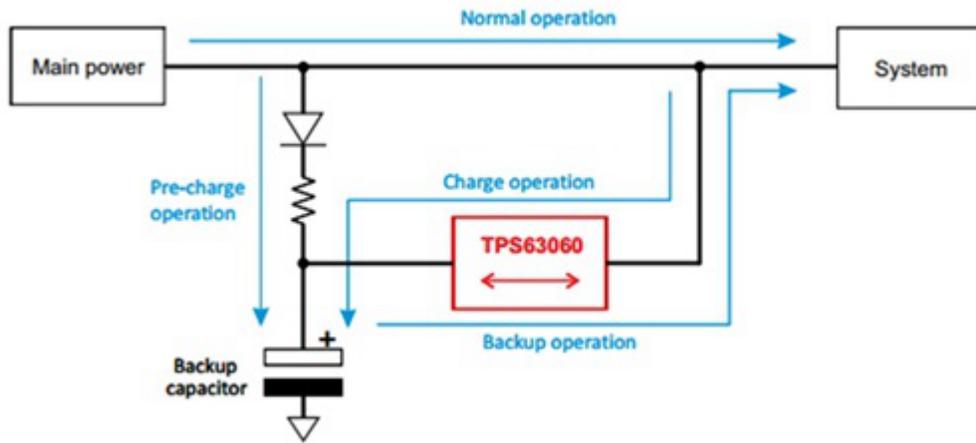


Figure 1. The **TPS63060** Provides Bi-directional Operation for Systems Which Require a Backup Power Function

Which of Your Systems Need to Store Energy to Properly Power Down?

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated