

## PMP15034 Test Results

### System Description


A piezoelectric sounder is a loudspeaker that uses the piezoelectric effect to generate sound. It is widely used in the application where sound volume and high pitch are more important than sound quality, such as toys, air conditioner, microwave oven and alarm equipment.

The piezoelectric sounder normally required a 1-KHz to 5-KHz rectangular voltage to operate. The sound press mainly depends on the amplitude of the driving voltage. The higher driving voltage, the higher sound press will be. For example, the PKM13EPYH4002 from Murata requires 0-V to 30-V or +15-V to -15-V rectangular voltage. The power supply in these applications could be two cell alkaline battery, lithium-ion battery or 3.3-V, 5-V power rail, which is much lower than the target voltage. Therefore, a high performance, simple boost converter TLV61046A is required for this application.

TLV61046A is 1.8-V - 5.5-V input, up to 28-V output, full integrated boost converter. It integrates low side MOSFET, high side rectifier diode and the isolation MOSFET. The isolation MOSFET disconnects the pass-through path between input and output when the device is disabled. This function helps to reduce the battery power loss when the piezoelectric sounder doesn't work.


Based on TLV61046A, the reference design introduces two driving circuit of piezoelectric sounder. With PWM signal from MCU, one circuit provides rectangular wave driving voltage between 0-V and 28-V; the other circuit provides  $\pm 15$ -V rectangular wave driving voltage.

The block diagram of the 28-V driver circuit is shown in Figure 1. The output voltage of the TLV61046A is set to 28V. A PWM signal from MCU drives Q1 to control the voltage across the piezoelectric sounder LS. When PWM signal is logic high, the Q1 turns on, so 28V is applied to LS. When PWM signal is logic low and Q1 turns off, the LS is discharged by the resistor in parallel. The frequency of the PWM signal should be equal to the recommended frequency of the sounder. The duty of the PWM should be as low as possible to reduce the power loss when the sound press is acceptable.

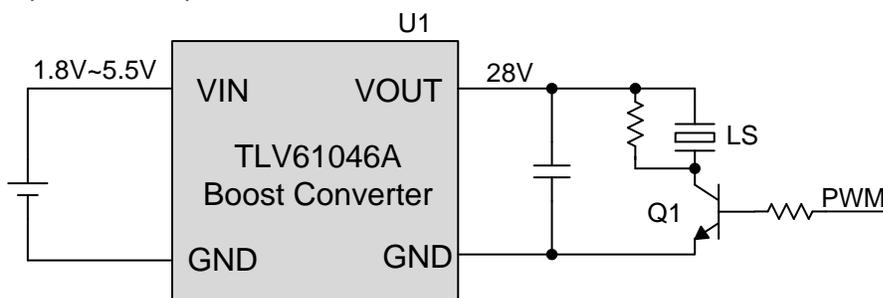

**Figure 1: Block Diagram of the 28-V Driver Circuit**

The block diagram of  $\pm 15$ -V driving circuit is shown in Figure 2. The output of the TLV61046A is set to 15V. An additional charge pump circuit doubles the output voltage to approximately 30V. When Q1 turn off and Q2 turn on, the voltage according the sounder LS is 15V; when Q1 turns on and Q1 turns off, the voltage according LS is -15V. The frequency of driving voltage follows the PWM input from MCU. By modifying the feedback divider of the TLV61046A and selecting proper Q1, Q2, this circuit supports  $\pm 28$  V for the sound. The resistor in parallel with LS can discharge the voltage to zero after the boost converter is disabled.

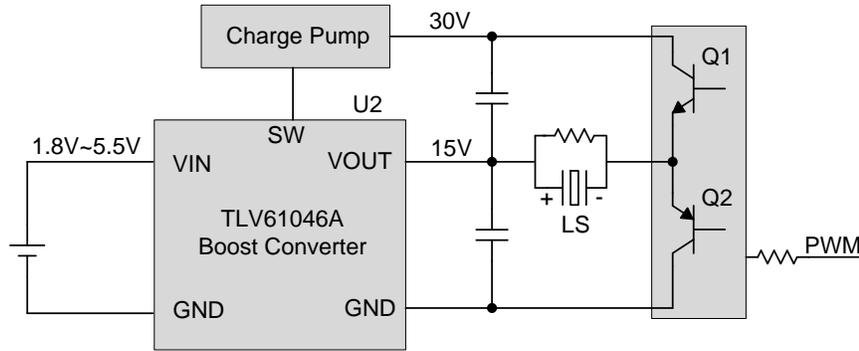

**Figure 2: Block Diagram of ±15-V Driver Circuit**

## Design Theory

The schematic of the 28-V driver circuit is shown in Figure 3. The output voltage of the boost converter is configured by R1 and R3. This voltage should be set to as high as possible to get highest sound.

Q1 is a NPN device driven by the PWM signal from the MCU. The sounder TS1 is charged to 28V when Q1 turns on, and discharged by the R2 to 0V when Q1 turns off. The frequency of the PWM should be equal to the recommended operating frequency of the sounder, which is 4KHz in this reference design.


The duty cycle of the PWM and the R2 resistance impact the sound press of TS1. They also impact the power loss of the driver circuit because the current flows through R2 to ground when Q1 turns on.

The power loss of R2 is calculated by equation (1), where D is duty cycle of the input PWM signal.

$$P_{R2} = V_{OUT}^2 \times D \div R2 \quad (1)$$


Follows are two steps to find suitable R2 and duty cycle to compromise the sound press and power loss:

- Setting the duty cycle to 50%, select a 1-KΩ to 10-KΩ resistor that minimize the power loss without suffering the sound press
- Using R2 selected by step 1, slowly decrease the duty cycle to minimize the power loss if the sound press requirement is met.

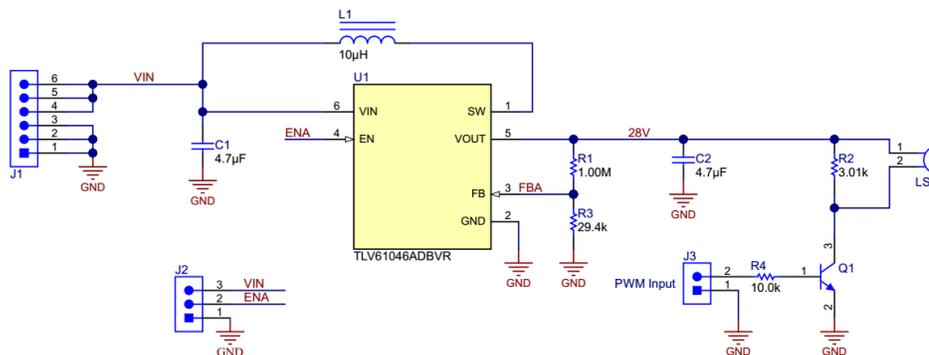

**Figure 3: 28-V Rectangular Waveform Driver Circuit**



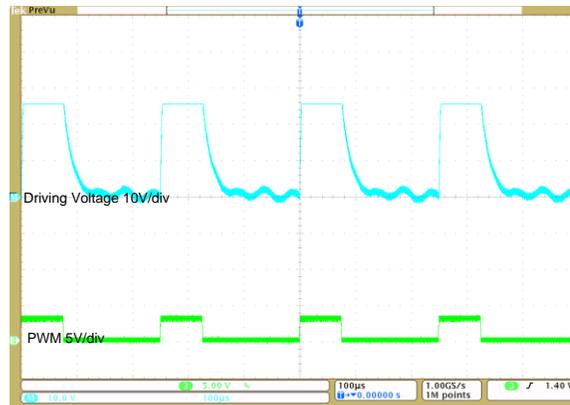


**Figure 6: Operating Waveform with 4-KHz PWM**

The startup by EN waveform of the  $\pm 15\text{-V}$  circuit is shown in Figure 7, the two output voltage ramps up to target value within 7ms.



**Figure 7: Startup at VIN=3.3V**

Figure 8 shows the operating waveform with 4-KHz, 30% duty PWM input when VIN=3.3V. The rising and falling time is very short because the totem pole has strong driving capability.

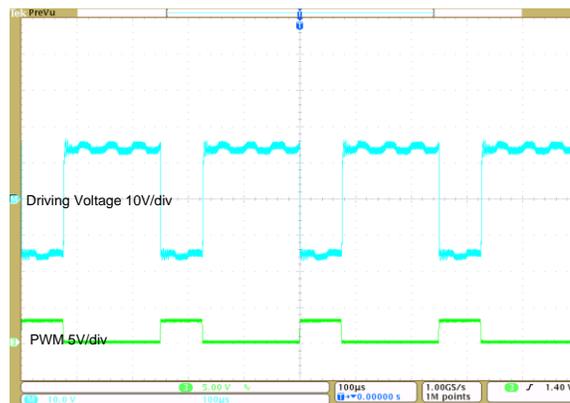

**Figure 8: Operating Waveform with 4-KHz PWM**

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated